


NAME - KARUNA KUMARI

ROLL NO - M200203EE

SUBJECT - SMRC ASSIGNMENT - 2

BRANCH - POWER ELECTRONICS

Ques 1. a) To find :- I_{C1} , I_{C2}

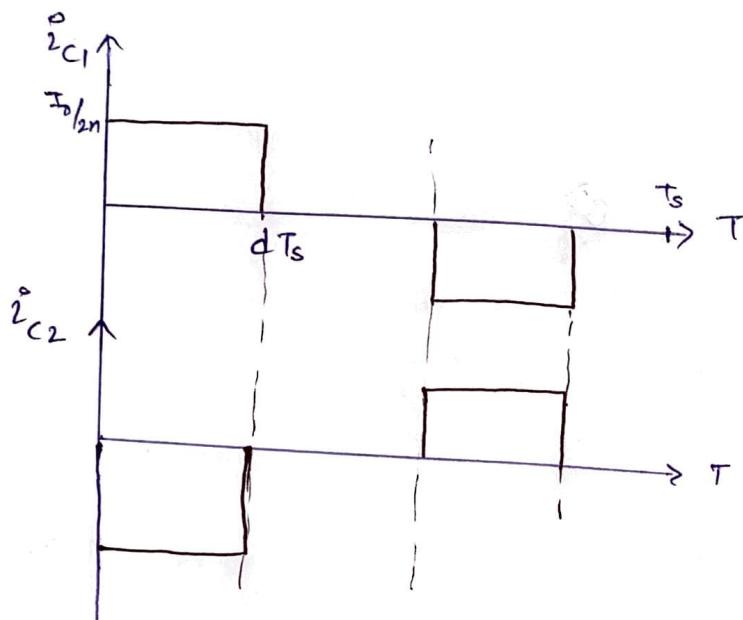

$$\frac{I_0}{2n} = \frac{10}{2 \times 9} = 0.556$$

$$V_o = \frac{DV_{in}}{n}$$

$$V_o = \frac{D \times 300}{9}$$

$$D = 0.36$$

$$\therefore i_{C1} = \frac{\frac{I_0}{2n} \times dT_s}{\frac{Ts}{2}} = \frac{\frac{I_0}{2n} \times dT_s \times \frac{2}{Ts}}{2} = \frac{I_0 d}{n}$$

$$i_{C1} = \frac{10 \times 0.36}{9}$$

$$i_{C1} = -i_{C2} = 0.4 \text{ A}$$

b) leakage inductance = 3%

Duty ratio = ?

$$L_e = 0.03 \times 2.7 \text{ m} \\ = 81 \text{ mH}$$

$$\text{Voltage loss} = \frac{3}{2} \frac{L_e i_o f_s}{n^2} = \frac{3}{2} \times \frac{81 \text{ mH} \times 10 \times 50 \text{ kHz}}{81} = 0.75 \text{ V}$$

$$\therefore V_o = \frac{dV_{in}}{n} - V_{ios}$$

$$12 = \frac{d \times 300}{9} - 0.25$$

$$D = 0.3825$$

Ques 3. EC '65 / 22 / 13

$$\text{Core Area} = 266 \text{ mm}^2$$

$$\text{Window area} = 537 \text{ mm}^2$$

$$\text{Mean turn length} = 150 \text{ mm}$$

$$\text{Mag. Path length} = 146.3 \text{ mm}$$

$$l_{tr} = 2200$$

$$\Phi_L = 4833 \text{ mH} / \text{T}^2$$

Soln:-

$$K_i = \left(1 + \frac{0.2}{2} \right) = 1.1$$

$$A_p = \frac{1}{2} L I^2 \left(\frac{2 K_i}{K_s J B_{max}} \right)$$

$$L = \frac{A_p K_s J B_{max}}{I^2 \times K_i}$$

$$J = 4 \times 10^6 \text{ A/m}^2$$

$$L = \frac{1.428 \times 10^{-7} \times 0.36 \times 4 \times 10^{-6} \times 10^6}{130}$$

$$L = 41.54 \text{ mH}$$

$$N = \frac{I_s J \Phi_w}{I} = \frac{0.36 \times 4 \times 537 \times 10^{-6} \times 10^6}{30}$$

$$N = 25.776 \approx 26$$

$$L = \frac{\mu_0 l_{tr} N^2 A}{4 \pi g l_{tr}}$$

$$l_{tr} = 2200$$

$$l_e = 146.3 \text{ mm} = 0.1463 \text{ m}$$

$$\mu_0 = 4\pi \times 10^{-7}$$

$$41.54 \times 10^{-6} = \frac{4\pi \times 10^{-7} \times 2200 \times 26^2 \times 266 \times 10^{-6}}{0.1463 + 2 \times 2200}$$

$$g = 2.68 \text{ mm} \rightarrow \text{Required Air gap.}$$

$$I_{LP} = 250 - 400 \text{ V}$$

$$O_{LP} = 12 \text{ V}$$

$$I_o = 5 \text{ A} - 20 \text{ A}$$

O_{LP} Ripple < 2% P-P

$$\Delta I_L < 4 \text{ A} \text{ P-P}$$

I_{mp} < 20% of I_o

$$f_S = 50 \text{ kHz}$$

$$d_{max} = 0.45$$

$$V_o = \frac{d V_{in}}{n}$$

$$n = \frac{d_{max} V_{in\ min}}{V_o} = \frac{0.45 \times 250}{12}$$

$$n = 9.375$$

$$n \approx 9$$

$$\therefore d_{min} = \frac{n V_o}{V_{in\ (max)}} = \frac{9 \times 12}{400}$$

$$d_{min} = 0.27$$

$\therefore d$ vary from 0.27 to 0.45

$$\Delta I_L = \frac{V_o (0.5 - d) T_S}{L}$$

$$\begin{aligned} \text{Using } d_{min} \Rightarrow L &= \frac{V_o (0.5 - d) T_S}{\Delta I_L} \\ &= \frac{12 (0.5 - 0.27)}{4 \times 50 \times 10^{-3}} \end{aligned}$$

$$L = 13.8 \mu H$$

Now, ESR $\times 4 = 0.24$

$$ESR = 0.24 / 4$$

$$ESR = 0.06 \Omega$$

Assuming 500A 2 electrolytic Capacitor

$$C = \frac{500 \text{ A}}{R}$$

$$C = \frac{500 \times 10^{-6}}{0.06}$$

$$C = 833.33 \mu\text{F}$$

$$C \approx 1000 \mu\text{F}$$

$$\text{Now, } \Delta I_L = \frac{V_o (0.5 - d_{\max})}{f_s \cdot L}$$



$$\Delta I_L = \frac{12 \times (0.5 - 0.45)}{50 \times 10^3 \times 12.8 \times 10^{-6}}$$

$$\Delta I_L = 0.869 \text{ A}$$

∴ Secondary Current varies between 19.56 A to 20.43 A.

Reflected Secondary Current varies from 2.1739 A to 2.2205 A with average current of 2.22 A.

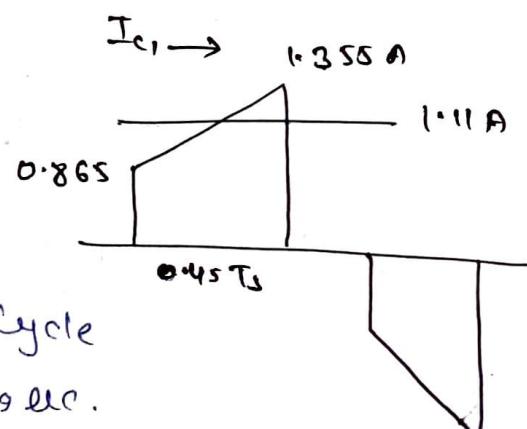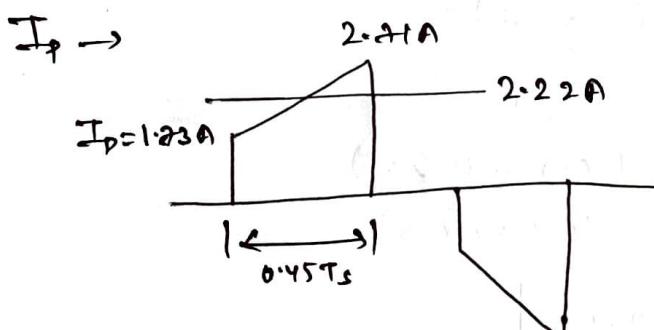∴ Primary Current varies between (2.17 - 0.44) A to (2.22 + 0.44) A



I_c is half of this.

∴ Charge contained in the half cycle

$$= \frac{1.11 \times 0.45}{50 \times 10^3} = 9.99 \mu\text{C}$$

Permitted P-P ripple in volt. splitting Capacitor and DC Blocking Capacitor = 5%.

$$\therefore \frac{250}{2} \times 0.05 \times C = 9.99 \mu F$$

$$C_1 = C_2 = 888 \mu F$$

Splitting Cap = $C_1 = C_2 \approx 1 \mu F$

Charge contained in one half cycle of $I_p = \frac{0.45 \times 2.22}{50 \times 10^3}$

$$C_b = 2.22 \mu F$$

$$C_b \approx 2.2 \mu F \rightarrow \text{Blocking Cap.}$$

- Switch peak Current $\approx 2.71 A \approx 3 A$
- Switch avg Current $= 2.22 A$
- Switch rms Current $= 2.2 \sqrt{0.45} = 1.425 A$
- Primary rms Current $= 2.2 \sqrt{0.9} = 2.087 A$
- $(I_{\text{secondary}})_{\text{rms}} = 13.284 A$

\therefore The O/P diode peak Current $= 22 A$ ($22 A > 20 A$)

• O/P diode avg Current $= 20 \times 0.45 + 2 \times 0.05 \times 10 = 10 A$

• O/P diode rms Current $= 13.8 A$

• O/P Inductor rms Current $= 20 A$

• O/P Capacitor rms Current $= 2/15 A$

• Lm of primary $= \frac{dV_m T_s}{a} = \frac{\alpha V_o T_s}{a}$

$$V_o = \frac{dV_{in}}{n}$$

$$L_p = \frac{g \times 12}{0.88 \times 50 \times 10^3}$$

$$(L_m)_p = 2.45 \text{ mH}$$

Area product calculation in Half Bridge Converter

$$\text{Primary rms Current} = \frac{I_o}{n} \sqrt{2d_{max}}$$

$$\text{Secondary rms Current} = \frac{I_o}{2} \sqrt{2d_{max+1}}$$

$$k_s A_w = n_p \times \frac{I_o}{n} \sqrt{\frac{2d_{max}}{J}} + \frac{I_o}{2J} \sqrt{2d_{max+1}} \times 2n_s$$

$$\frac{n_p}{n_s} = n = g$$

$$k_s A_w = 2.33 \frac{n_s I_o}{J}$$

$$A_c = \frac{n_s V_o T_s}{2 B_m}$$

$$A_p = A_c A_w = \frac{2.33 V_o I_o T_s}{2 B_m J k_s}$$

$$A_p = 2.6628 \times 10^{-8} \text{ mm}^4$$

$$A_p = 26628 \text{ mm}^4$$

Hence, E 42/21/15 nos $A_c A_w = 45525 \text{ mm}^4$

$$\therefore n_s = \frac{1}{\frac{2 f_s B_m A_c}{V_o}}$$

$$n_s = 3.29 \approx 4$$

$$n_s = n n_s = 9 \times 4 = 36 \text{ turns}$$

RMS value of $I_L \approx 20 \text{ A}$

Copper area of a turn = $10/3 = 3.33 \text{ mm}^2$


$$ShA = 13$$

$$\text{Cu Area} = 4.289 \text{ mm}^2$$

$$\text{Cu dia} = 2.337 \text{ mm}$$

$$\text{Overall dia} = 2.441 \text{ mm}$$
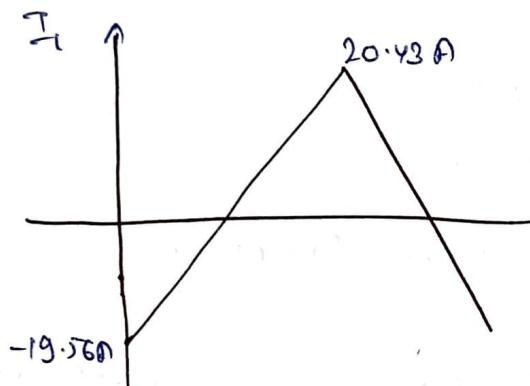
$$N = \frac{LI_{\max}}{Ac B_{\max}} = \frac{13.8 \times 10^{-6} \times 20.43}{Ac \times B_{\max}}$$



$$L_{\text{chosen}} = 12.8 \text{ mH}$$

$$\text{Design } B_{\max} = 0.2 \text{ Wb/mm}^2$$

$$J = 3 \text{ A/mm}^2$$

$$K_i = \frac{20.43}{20} = 1.0215$$

$$k_s = 0.35$$

$$A_P = \frac{1}{2} L I^2 \frac{2 K_i}{k_s J B_{\max}}$$

$$= \frac{1}{2} \times 13.8 \times 10^{-6} \times (20)^2 \times 2 \times 1.0215$$

$$0.35 \times \frac{3}{10^6} \times 0.2$$

$$A_P = 26850.85 \text{ mm}^2$$

We will use the core
EE 42/21 115

$$A_w = 256 \text{ mm}^2$$

$$A_c = 178 \text{ mm}^2$$

$$A_p = 455.68 \text{ mm}^2$$

$$\text{Mean turn length} = 4 \left[29.5 + \frac{29.5 - 12.5}{2} \right] \\ = 86 \text{ mm}$$

$$N \approx 8$$

$N=8$ is taken

$$\text{Winding Height} = 2 \times 14.8 \\ = 29.6 \text{ mm}$$

1mm thick Bobbin + 2mm Creepage.

$$\text{Winding Height} = 29.6 - 3 \times 2 = 23.6 \text{ mm}$$

$$\text{Wire diameter} = 2.44 \text{ mm}$$

$$\left(\frac{23.6}{2.44} \right) = 9.668 \approx 9 \text{ turns in 1 layer.}$$

So here one turn extra i.e., $(9-8) = 1$ turn.

$$h = 0.866d$$

$$h = 0.866 \times 2.337$$

$$h = 2.028 \text{ mm}$$

$$\frac{N_d}{h} = \frac{8 \times 2.337}{23.6} = 0.79$$

$$A = \text{Skin depth at } 50 \text{ kHz} = 0.141 \text{ mm}$$

$$f_R = \frac{2\sqrt{f_L}}{A} = \frac{2 \cdot 0.0238 \sqrt{0.29}}{0.141}$$

$$f_R = 12.25$$

X - Co-ordinate at Do - well's Curve $f_R = 12.25$

$$R_{ac} = R_R \cdot R_{dc}$$

$$R_{dc} = \frac{76 \text{ mm} \times 23.6}{1000} \times 0.001 \frac{\Omega}{\text{m}} \times 1.2$$

4.2 / mm for such IB wire & 1.25 f for
temp.

$$R_{dc} = 8.609 \text{ m}\Omega \text{ at } 20^\circ\text{C}$$

$$R_{ac} = 12.25 \times 8.609$$

$$R_{ac} = 109.76 \text{ m}\Omega$$

$$Cu_{loss} = (20)^2 \times 8.609 \times 10^{-3} + \left(\frac{0.43}{\sqrt{3}} \right)^2 \times 0.10976$$

$$Cu_{loss} = 8.45 \text{ Watt}$$

Ques 7: $V_P = 250 - 400 \text{ V}$

$$O_P = 12 \text{ V}$$

$$I = 2.5 \text{ A}$$

O_P Ripple < 2% peak to peak

$$f = 100 \text{ KHz}$$

Mosfet Voltage Rating = 900V

$$B_m = 0.25 \text{ Wb/m}^2$$

$$J = 3 \text{ A/mm}^2$$

$K_s = 0.35$ for
T1F coil

$$\text{coil T} = 1 \text{ mm}$$

$$\text{Creepage D} = 2 \text{ mm}$$

Soln 5 from the 2nd design eqn

$$1.3 [V_{inmax} + n(V_o + V_r)] \leq 0.8 V_R$$

$$\therefore V_r = 1 \text{ V}$$

$$1.3 [400 + n(12+1)] \leq 0.8 \times 900$$

$$1.3 [400 + n(13)] = 720$$

$$n = 11.83$$

$$[n \approx 12 \text{ turns}]$$

for d_{max} .

$$d_{max} \left(1 + \frac{V_{min,ir}}{n(V_o + V_r)} \right) \leq 0.8$$

$$d_{max} = \frac{0.8}{1 + \frac{V_{min,ir}}{n(V_o + V_r)}} = \frac{0.8}{1 + \frac{250}{12(12+1)}}$$

$$[d_{max} = 0.31]$$

$$\therefore d_{max} = \frac{\sqrt{2L_p P_{omax} f_s}}{V_{min,ir}}$$

$$P_{omax} = V_o \times I_{omax} = 12 \times 5 = 60 \text{ Watt}$$

$$P_{omin} = V_o \times I_{omin} = 12 \times 2 = 24 \text{ Watt}$$

$$\therefore 0.31 = \frac{\sqrt{2 \times L_p \times 60 \times 100 \text{ Hz}}}{250}$$

$$L_p = 500.5 \text{ mH}$$

$$\text{Now, } I_p = \frac{V_{min,ir} d_{max}}{L_p f_s}$$

$$I_p = \frac{250 \times 0.31}{500.5 \text{ mH} \times 100 \text{ Hz}}$$


$$I_p = 1.54 \text{ A}$$

$$I_p \approx 1.5 \text{ A}$$

$$\therefore (i_p)_{om} = (i_{sw})_{om} = \sqrt{\frac{1}{T_s} \int_0^{dT_s} \left(\frac{1.5}{dT_s}\right)^2 dt}$$

$$= \sqrt{\frac{1}{T_s} \times \frac{(1.5)^2}{(0.31)^2} \times 3}$$

$$[(i_p)_{om} = 0.482 \text{ Amp}]$$

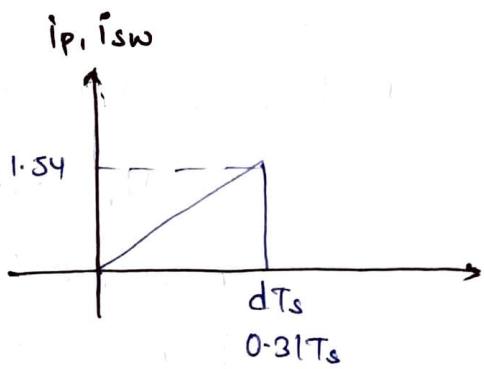


Now, we need to calculate T_r for secondary diode current.

$$T_r = \frac{\text{dmax} \times \text{min} T_s}{n(V_o + V_r)} = \frac{0.31 \times 250 \times T_s}{12 \times 13} = 0.496 T_s$$

$$\boxed{T_r = 0.496 T_s}$$

$i_{\text{sec}, \text{diode}}$

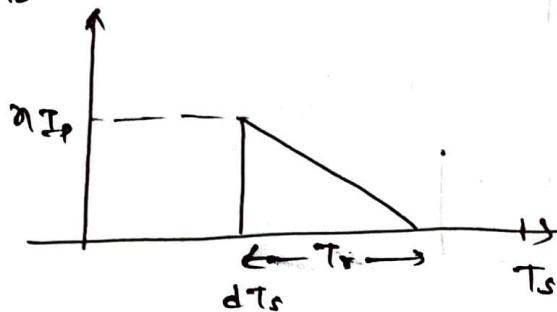

$$(i_{\text{diode}})_{\text{om}} = \sqrt{\frac{1}{T_s} \int_0^{0.496 T_s} \left(\frac{n I_p}{T_r} t \right)^2 dt}$$

$$\frac{n I_p}{T_r} = \frac{12 \times 1.5}{0.496 T_s} = \frac{36.29}{T_s}$$

$$\therefore (i_{\text{diode}})_{\text{om}} = \sqrt{\frac{1}{T_s} \int_0^{0.496 T_s} \left(\frac{36.29}{T_r} t \right)^2 dt}$$

$$= \sqrt{\frac{1}{T_s^3} \times \left(\frac{36.29}{T_r} \right)^2 \times \frac{1}{3} (0.496)^3 T_s^3} \\ = 7.31 \text{ A.}$$

$$\boxed{(i_{\text{diode}})_{\text{om}} = 7.31 \text{ A.}}$$

- Diode peak current rating $\geq n I_p$
 $\geq 12 \times 1.5$
 $\geq 18 \text{ A.}$

- Diode Avg Current rating $\geq 5 \text{ A.}$

- Diode τ_{on} Current $\geq 7.31 \text{ A.}$

$P_{\text{max}} = 6.7 \text{ W}$

$I_{\text{max}} = 5 \text{ A}$

- Mosfet peak Current $\geq I_p \geq 1.5 \text{ A}$
- Mosfet avg Current $\geq 0.24 \text{ A}$
- Mosfet RMS Current $\geq (I_{\text{rms}})_{\text{avg or (ip)}}$
 - $(I_{\text{mosfet}})_{\text{rms}} \geq 0.482 \text{ A}$
- Transformer Design
- Primary wire rms Current = $(I_{\text{rms}})_{\text{avg}}$
 - $(I_{\text{primary}})_{\text{rms}} = 0.482 \text{ A}$
- Primary wire size
 - $B_m = 0.25 \text{ wb/mm}^2$
 - $J = 3 \text{ A/mm}^2$
 - $J = I/A \Rightarrow 3 = \frac{0.482}{A}$
 - $A = 0.16 \text{ mm}^2$
- Secondary wire RMS Current = $(I_{\text{diode}})_{\text{rms}} = 7.31 \text{ A}$
- Secondary wire size = 2.436 mm^2
 - $J = 3 \text{ A/mm}^2 = I/A$
 - $3 = \frac{7.31}{A} \Rightarrow 2.436 \text{ mm}^2$
- Transformer :
 - $L_p = 500.5 \text{ mH}$
 - $n = 12$

Ques 8. flyback Converter CCM

$$V_{in} = 250 - 400 \text{ V}$$

$$\circ I_D = 12 \text{ V}, 2A - 5A$$

$$f_S = 100 \text{ kHz}$$

$$\text{Mosfet Rating} = 900 \text{ V}$$


Soln:-

Using $n=12$ (already calculated)

$$(L_P)_{min} = \left(\frac{12 \times 13 \times 400}{12 \times 13 + 400} \right)^2 \times \frac{1}{2 \times 100 \times 10^3 \times 24} \quad \left\{ \begin{array}{l} P_{min} = V_o \times I_{min} \\ = 12 \times 2 \\ = 24 \text{ W.} \end{array} \right.$$

$$= 2.33 \text{ mH}$$

Secondary RMS Calculation

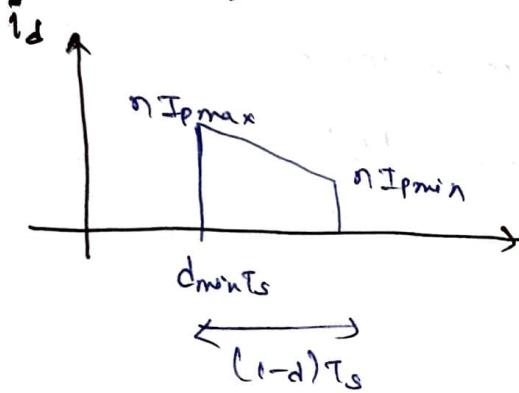

Using $d = d_{min}$

$$V_{in} = V_{in \max}$$

$$i_d = \left(\frac{n I_{pmax}}{1-d} \right) \cdot t + n I_{pmin}$$

for I_{pmax} and I_{pmin}

$$\frac{I_{pmax} + I_{pmin}}{2} = \frac{I_o}{n(1-d)}$$

$$I_{pmax} + I_{pmin} = \frac{2 P_{max}}{\circ V_o (1 - d_{min})}$$

$$d_{min} = \frac{n (V_o + V_r)}{\circ (V_o + V_r) + V_{in \max}}$$

$$= \frac{12 (12 + 1)}{12 \times 13 + 400}$$

$$d_{min} = 0.28$$

$$-I_y \text{ d}_{\max} = \frac{\alpha(V_o + V_r)}{\alpha(V_o + V_r) + k_{\min}}$$

$$= \frac{12 \times 13}{12 \times 13 + 250}$$

$$\boxed{d_{\max} = 0.884}$$

$$\therefore I_{p_{\max}} + I_{p_{\min}} = \frac{2 \times 60}{12 \times 12 (1 - 0.28)}$$

$$\left. \begin{aligned} P_{p_{\max}} &= V_o I_{p_{\max}} \\ &= 12 \times 5 \\ &= 60 \end{aligned} \right\}$$

$$I_{p_{\max}} + I_{p_{\min}} = 1.157 \quad \text{--- (1)}$$

$$I_{p_{\max}} - I_{p_{\min}} = \frac{\alpha(V_o + V_r)(1 - d_{\min})}{L_P f_s}$$

$$= \frac{12(13)(1 - 0.28)}{2.33 \times 100K}$$

$$I_{p_{\max}} - I_{p_{\min}} = 0.482 \quad \text{--- (2)}$$

from (1) and (2)

$$\boxed{I_{p_{\max}} = 0.8195 \text{ A}}$$

$$\boxed{I_{p_{\min}} = 0.3375 \text{ A}}$$

$$I_{\text{secondary}} \approx \left(\frac{\alpha I_{p_{\max}} + \alpha I_{p_{\min}}}{2} \right) \sqrt{1 - d_{\min}}$$

$$\approx \left(\frac{12 \times 0.8195 + 12 \times 0.3375}{2} \right) \sqrt{1 - 0.28}$$

$$\boxed{(I_{\text{sec}})_{\text{av}} \approx 8.89 \text{ A}}$$

$$I_{\text{avg}} = I_o = \frac{P_o}{V_o} = \frac{60}{12} = 5 \text{ A}$$

$$\boxed{I_{\text{avg}} = 5 \text{ A}}$$

$$(I_d)_{peak} = n I_{pmax} = 12 \times 0.8195 \\ = 9.834 A$$

$$(I_d)_{avg} = \left(\frac{n I_{pmax} + n I_{pmin}}{2} \right) (1 - d_{min}) \\ = \left(\frac{12 \times 0.8195 + 12 \times 0.3775}{2} \right) (1 - 0.28) \\ = 4.992$$

$$I_d \text{ avg} \approx 5 A$$

Now, primary Conducts most Order Vimin^{Kondⁿ},
 \rightarrow Using $d = d_{max} = 0.384$

$$I_{pmax} + I_{pmin} = \frac{2 I_{pmax}}{n (1 - d_{max})} = \frac{2 \times 10}{12 (1 - 0.384)} \\ = \frac{2 \times 5}{12 (1 - 0.384)} = 1.3528 \quad (1)$$

$$I_{pmax} - I_{pmin} = \frac{n (V_o + N_r) (1 - d_{max})}{L_p f_s} \\ = \frac{12 \times 13 (1 - 0.384)}{2.33 \text{ m} \times 100 \text{ k}} \\ = 0.412 \quad (11)$$

from (1) and (11)

$$I_{pmax} = 0.8824 \\ I_{pmin} = 0.4704$$



$$(I_{primary})_{avg} = \sqrt{\frac{I_{pmax} + I_{pmin}}{2}} \sqrt{d_{max}}$$

$$(I_{\text{RMS}})_{\text{avg}} = \left(\frac{0.8824 + 0.4704}{2} \right) \sqrt{0.384}$$

$$(I_{\text{primary}})_{\text{avg}} = 0.692 \text{ A}$$

$$I_{\text{peak}} = I_{\text{max}} = 0.8824 \text{ A}$$

$$I_{\text{avg}} = \left(\frac{I_{\text{max}} + I_{\text{min}}}{2} \right) \times d$$

= ~~Sum of all areas~~

$$= \left(\frac{0.8824 + 0.4704}{2} \right) \times 0.384$$

$$I_{\text{avg}} = 0.259 \text{ A}$$

MosfET : Peak = 0.8824 A , Avg = 0.259 A , RMS = 0.692 A

Diode : Peak = 9.834 A , Avg = 5 A , RMS = 5.89 A

To find Area Product

$$I_{\text{max}} = 0.8824 \text{ A}$$

$$L_P I_{\text{max}} = A_C n_p B_m$$

$$2.33 \times 0.8824 = A_C n_p B_m$$

$$\text{Using } B_m = 0.25 \text{ wb/mm}^2$$

$$A_C = \frac{2.33 \times 0.8824}{n_p \times 0.25 \times 10^{-6} \times 10^6} = \frac{8093}{n_p} \propto \frac{8093 \cdot g}{n_p}$$

$$A_w = n_p \times A_p + n_s \times A_s$$

$$= \frac{n_p}{1 \times s} \left[A_p + \frac{n_s}{n_p} A_s \right]$$

$$A_w = \frac{n_p}{K_s} \left[0.141 + \frac{2}{12} \right] \text{mm}^2 \quad \left\{ K_s = 0.35 \right.$$

$$A_c A_w = \frac{8223}{0.35} \times \frac{n_p}{K_s} \left[0.141 + \frac{2}{12} \right] \text{mm}^2 \\ = \frac{8223}{0.35} \left[0.141 + \frac{2}{12} \right]$$

$$A_c A_w = 7228.4 \text{ mm}^2$$

$$E/32/66/4 \quad A_c = 97 \text{ mm}^2$$

$$A_w = 14784 \text{ mm}^2$$

$$A_p = 14340 \text{ mm}^2$$

With given A_c

$$n_p = \frac{8223}{97} = 84.77$$

$$n_s = \frac{84.77}{12} = 7.06$$

$$\therefore \boxed{n_p = 96}$$

$$\boxed{n_s = 8}$$

$$\therefore n = \frac{n_p}{n_s}$$

$$12 = \frac{n_p}{\cancel{n_s} 8}$$

$$\boxed{n_p = 96}$$

Potential = 96 turns of SWG 26

Secondary = 8 turns of SWG 16

Ques 9. Boost Converter

$$V_i = 10.8 \text{ to } 13.6 \text{ V}$$

$$V_o = 24 \text{ V}$$

$$L = 25 \mu\text{H}$$

$$C = 680 \mu\text{F}$$

$$T = 40 \mu\text{s}$$

$$f = 50 \text{ kHz}$$

$$I_o = 1.4 \text{ A}$$

$$\text{Sensing gain} = 0.125 \text{ V/A}$$

Soln :-

Boost Converter

for Duty Cycle,

$$V_o = \frac{V_{in}}{1-D}$$

$$24 = \frac{10.8}{1-D}$$

$$1-D = 0.45$$

$$\boxed{D = 0.55}$$

$$\therefore \boxed{D_{max} = 0.55}$$

Condition	1 - D	D
Max	0.45	0.55
Min	0.566	0.433
Avg	0.508	0.491
Max	0.566	0.433
Min	0.45	0.55
Avg	0.508	0.491

$$\text{Now, } P_{op} = P_{IP}$$

$$V_{in} I_{in} = V_o \cdot I_o$$

$$V_{in} I_{in} = \frac{V_o}{1-D} I_o$$

$$I_{in} = \frac{I_o}{1-D}$$

$$I_{in} = \frac{1}{1-0.55} = 2.22 \text{ A} \quad \left\{ \text{for } I_o = 1 \text{ A} \right.$$

$$I_{in} = \frac{4}{1-0.55} = 8.88 \text{ A} \quad \left\{ \text{for } I_o = 4 \text{ A} \right.$$

$$\text{Sensing gain} = 0.125 \text{ V/A}$$


$$\text{for } I = 1 \text{ A}, V = 0.125 \text{ V}$$

$$I = 8.88 \text{ A} \Rightarrow V = 8.88 \times 0.125 = 1.11 \text{ A}$$

let $\alpha = 1$

$$I = 8.88 \text{ A}, V = 1.11 \text{ V}, V_{\text{fwd}} = 0.6$$
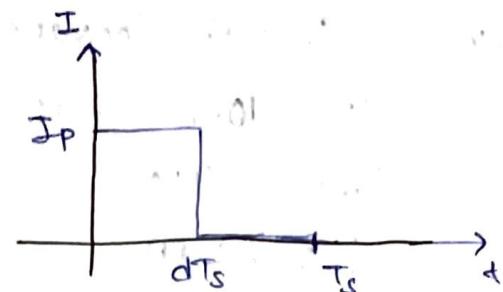
$$D_{\text{max}} = 0.55 \quad f_s = 50 \text{ kHz}$$



$$\eta L_m \geq \frac{100 D_{\text{max}} (V + V_{\text{fwd}})}{\eta f_s I}$$

$$= \frac{100 \times 0.55 (1.11 + 0.6)}{1 \times 50 \times 10^3 \times 8.88}$$

$$\eta L_m = 211.82 \text{ LH.T}$$

n	$(L_s)_{\text{max}}$	$B_m (\text{mW/m}^2)$
T ₁₀	27.6	0.023
T ₁₂	12.9	0.036
T ₁₅	14.2	0.046
T ₂₀	18.7	0.035
T ₂₂	11.4	0.037
T ₃₂	8.7	0.075
T ₄₅	8.9	0.074

$$B_m \leq \frac{D_{\text{max}} (V + V_{\text{fwd}})}{\eta f_s A_c} = \frac{0.55 (1.11 + 0.6)}{50 \times 10^{-3} \eta A_c}$$

$$= \frac{1.851 \times 10^{-3}}{\eta A_c}$$

$$\text{let } J = 2.5 \text{ A/mm}^2$$

$$J = I/A$$

$$A = \frac{I}{J} = \frac{0.074}{2.5} = 0.03 \text{ mm}^2$$

So we choose T45 / 89 T / SWG 32

$$V_b = \frac{D_{\text{max}}}{1 - D_{\text{max}}} (V + V_{\text{fwd}}) - V_{\text{fwd}}$$

$$V_b = \frac{0.55}{1-0.55} (1.11 + 0.6) - 0.59$$

$$= 1.5 \text{ V}$$

$$\text{Power rating of gen} = \frac{\text{Im } I_m^2 f_s}{2}$$

$\left\{ \begin{array}{l} \text{Im} = 10\% \text{ of } I \\ = 0.1 \times 8.88 \end{array} \right.$

$$= \frac{2.32 \times 10^{-6} \times (0.1 \times 8.88)^2 \times 50 \times 10^3}{2}$$

$$= 468.8 \text{ kW}$$

for this power rating we need $n = 88$, $I = 1.62 \text{ A}$, $V = 0.835 \text{ V}$

$$\text{Now, } R_s = \frac{nV}{I} = \frac{88 \times 0.835}{1.62}$$

$$= 44 \Omega.$$

$$\boxed{R_s = 44 \Omega}$$

$$\text{RMS of current through } R_s = 0.0188 \sqrt{0.2}$$

$$= 8.45 \times 10^{-3}$$

$$\therefore \text{Power in } R_s = (8.45 \times 10^{-3})^2 \times 44$$

$$= 3.14 \text{ mW}$$

so 44 Ω is $1/4 \text{ W}$ resistance. \rightarrow Design.

Ques 10. $I = 1.11 \text{ A}$ $V = 0.139 \text{ V}$

$$0.125 \text{ V} \rightarrow 1 \text{ A}$$

$$1.11 \text{ A} \rightarrow 1.11 \times 0.125 = 0.139 \text{ V}$$

$$\text{Im} \geq \frac{3.2 \text{ V}}{I_f} = \frac{3.2 \times 0.139}{50 \times 10^3 \times 1.11}$$

$$\left| \begin{array}{l} 1\% \text{ of } 1.11 \\ = 0.011 \text{ A.} \end{array} \right.$$

$$\text{Im} = \frac{dV}{2 \pi L_{nf}} = \frac{0.36 \times 0.139}{2 \times 8.01 \times 10^{-6} \times 50 \times 10^3} = 0.0624$$

$I_m = 0.0624 > \text{Inv. of 1.11 i.e., } 0.011$

$$\text{So, } 0.011 = \frac{0.36 \times 1}{2 \times 50 \times 10^{-3} n L_m}$$

$$n L_m = \frac{0.36 \times 1}{0.011 \times 2 \times 50 \times 10^{-3}}$$

$$n L_m = 327.27 \text{ EH.T}$$

η	I_s	B_m
T_{10}	427	1.39×10^{-4}
T_{12}	217	1.5×10^{-4}
T_{14}	290	
T_{20}	209	
T_{22}	176	
T_{32}	134	
T_{45}	138	

$$B_m = \frac{dV}{2\pi s A}$$

$$J = 2.5 \text{ A/mm}^2 = I/A$$

$$A = \frac{I}{J} = \frac{4.22}{2.5} = 2 \text{ mm}^2$$

So, choose T_{45} toroid core


SWG 15

138 turns of SWG 15

(2.62 mm^2 , 1.92 mm dia)

$$R_s = \frac{0.139 \times 138}{1.11} = 17.21 \Omega / \text{sw.}$$

Ques 18

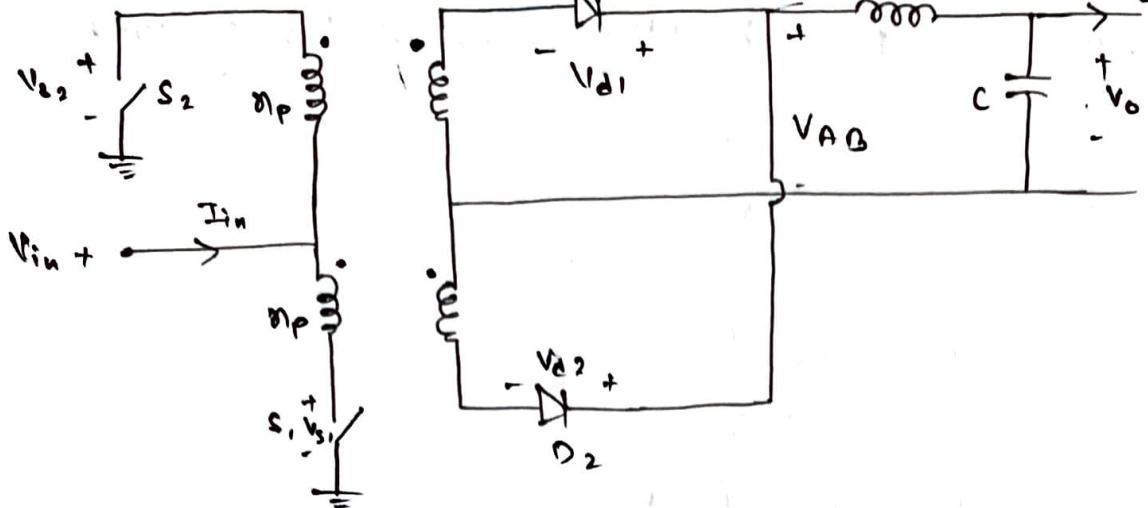

$$V_{in} = 180 - 240 \text{ V}$$

$$V_o = 12 \text{ V}$$

$$n = 6$$

$$L_{on} = 0.5 \text{ mH} \quad f_s = 40 \text{ kHz}$$

$L = 68 \mu\text{H}$, $C = 40 \text{ nF}$ family at the O/P

$$I = 4 - 10 \text{ A}$$

$$\text{Sensing gain} = 0.5 \text{ V/A}$$

$$\text{Now, } V_o = \frac{2 V_{load}}{n}$$

$$d_1 = \frac{n V_o}{2 \cdot V_{in}} = \frac{6 \times 12}{2 \times 240}$$

{ Using $V_{in \max} = 240 \text{ V}$

$$d_1 = 0.15$$


$$d_2 = \frac{6 \times 12}{2 \times 180}$$

{ Using $V_{in \min} = 180 \text{ V}$

$$\approx 0.064$$

$$d_2 = 0.2$$

$$\therefore d_{\max} = 0.2$$

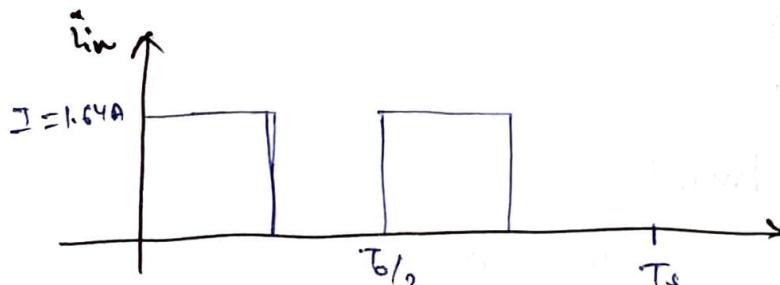

Considering. $I = 1.6 \text{ A}$, $V = 0.835 \text{ V}$, $V_{FW} = 0.6$

$D_{max} = 0.2$, $f_s = 80 \text{ kHz}$, $T_m < 1\%$ of 1.6 A

$$\text{for } 1 \text{ A} \rightarrow 0.5 \text{ V}$$

$$1.6 \text{ A} \rightarrow 0.835 \text{ V}$$

$$n_{Lm} \geq \frac{100 D_{max} (V + V_{FW})}{n f_s I}$$

$$\geq \frac{100 \times 0.2 (0.835 + 0.6)}{1 \times 80 \times 10^3 \times 1.6}$$

$$= 0.214 \text{ on H.T}$$

	n	$(I_s)_{mm}$	$B_m (\text{wb/m}^2)$
T10	280	2.66×10^{-3}	2.066×10^{-3}
T12	182	4.1×10^{-3}	1.642×10^{-3}
T10	145	5.15×10^{-3}	1.232×10^{-3}
T20	190	3.93×10^{-3}	3.38×10^{-4}
T22	116	6.43×10^{-3}	/
T32	88	8.48×10^{-3}	/
T45	90	8.29×10^{-3}	/

$$B_m = \frac{D_{max} (V + V_{FW})}{n f_s \cdot A} = \frac{0.2 (0.835 + 0.6)}{n A_c \times 80 \times 10^3 \times 10^{-6}}$$

$$= \frac{3.58}{n A_c}$$

$$J = 2.5 \text{ A/mm}^2$$

$$T32, n = 88, I_s = 8.48 \times 10^{-3}$$

$$J = I/A$$

$$A = I/J = \frac{8.48 \times 10^{-3}}{2.5} \\ = 0.0039 \text{ mm}^2$$

SWG 45

T42 / 887 / SWG 45

$$V_g = \frac{d_{max}}{1-d_{max}} (V_f + V_{fw}) \\ = \frac{0.2}{1-0.2} (0.835 + 0.6) \\ = 0.458$$

$$\text{Power rating of generator} = \frac{\text{Len} \cdot \text{Em}^2}{2} f_s \\ = \frac{2.44 \times 10^{-6} \times (0.01 \times 1.62)^2 \times 800}{2} \\ = 27.2 \text{ W}$$