


DEPARTMENT OF ELECTRICAL ENGINEERING
National Institute of Technology Calicut
END SEMESTER EXAM- WINTER SEMESTER JUNE 2021
EE6308DSWITCHED MODE & RESONANT CONVERTERS

Time : 2 Hrs

Maximum : 20 Marks

Answer All Questions

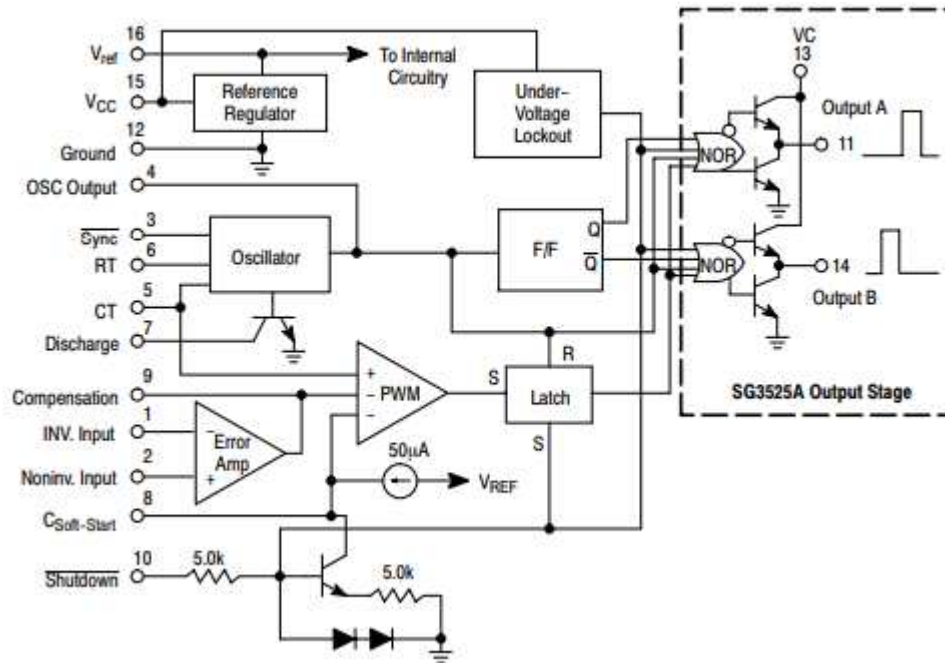1. (a) **Distinguish between** Running Average, Cycle Average and Local Average of variables in the context of mathematical modelling of SMPS. (0.5 Marks)
(b) **Explain the role and function** of PWM Modulator that comes after the Compensator and provides drive to the switch. This Modulator is usually taken as a unity gain block in controller analysis. **Discuss** the validity of this assumption. (1.5 Marks)
2. (a) All the three types of compensators commonly employed in Voltage Mode Control of SMPS have a common factor $1/s$ in their transfer functions. **Explain why** this factor is needed in all compensator transfer functions. (0.5 Marks)
(b) Two non-isolated Buck Converters with same input voltage and output specifications employ different capacitor sizes. They are otherwise identical. Design-A uses a $1000\mu\text{F}$ electrolytic capacitor from $80\mu\text{s}$ family and Design-B uses a $125\mu\text{F}$ from $10\mu\text{s}$ family. Voltage Mode Control is used in both. It is seen that when designed for the same phase margin of 60° , one of them needs a Type-3 compensator whereas the other requires only a Type-2. **Explain** why, starting with the control-to-output transfer function of a Buck Converter? **Identify** which design will require Type-3 compensator with justification for your decision. (1.5 marks)
3. (a) **Explain the different factors** that lead to a choice of gain crossover frequency in the design of compensators for Voltage Mode Control of SMPS. (1 Mark)
(b) The Professor who teaches SMRC to you says – “A Buck Converter that is ideal, that is, with zero resistances in inductor, capacitor, switch and diode, *requires* a Type-3 Compensator for *any positive phase margin value*. Type-1 and Type-2 simply will not be enough in this case.” Starting with Buck Converter control-to-output transfer function, **show that** what he stated is correct. (1 Mark)
4. (a) **Explain how** Current Mode Control is implemented ? **List and explain** all the advantages of Current Mode Control. (1 ½ Marks)
(b) **What is** meant by Subharmonic Instability in CMC? **How** is it prevented? (1 Mark)
(c) **Explain the design procedure** for designing the Outer Voltage Control Loop in the case of a Buck Converter under Current Mode Control? (1 ½ Marks)
5. A representative diagram of a PWM Control IC SG3525 is shown below. (4 x 1 = 4 Marks)
 - (a) Explain the functions of the under-voltage lockout, latch and the flip flop.
 - (b) Explain how a Type-2 Compensator can be implemented by using the Error amplifier.
 - (c) Explain how soft start control is achieved when this IC is used.
 - (d) Explain how a Boost Converter with a duty ratio requirement range of [0.5 0.65] can be driven by a SG3525.



6. A Boost Converter data is given : 5V input, 12V/2A resistive load output, 50kHz Switching, $L = 30\mu\text{H}/0.05\Omega$, $C = 1000\mu\text{F}/0.01\Omega$, Switch Resistance and Diode resistance = 0.05Ω , Diode Cut-in Voltage = 0.5V .
- Find the Control-to-Output transfer function** around an operating point 5V input, 12V 2A Output. Use $d_o = 0.64$ in evaluating transfer function. You do not have to derive equations and you may refer to class notes. (0.5 marks)
 - Choose a gain crossover frequency of 5kHz. **Find the maximum phase margins** that can be realized with this crossover frequency if Type-3 VMC Compensator is employed. (1 Mark)
 - Design a Type-3 compensator** function such that crossover frequency is 5kHz and Phase Margin of the closed loop system is 60 deg. (1 Mark)
 - Assuming the error signal, i.e, $(V_o - 12)$ is available as input, **design** an Opamp based circuit to implement this compensator function and **show the circuit** with component values marked. (1.5 Marks)
7. **Explain** how the Shunt Regulator diode TL 431 can be used to feedback output voltage without breaking isolation barrier in a SMPS. **Draw** the circuit diagram for a Voltage Mode PI Controller using TL431 and an Optocoupler and explain how to arrive at component values. (2 Marks)

=====