

Advanced power Electronics (APEC)

Module 3

Date 13/03/2022
Page



APEC

$$\text{Power factor} = \frac{\text{Active power}}{\text{Apparent power}} \rightarrow \cos\phi$$


$(V \cos\phi) \quad (VI)$

$$\text{Power} = V I \cos\phi$$

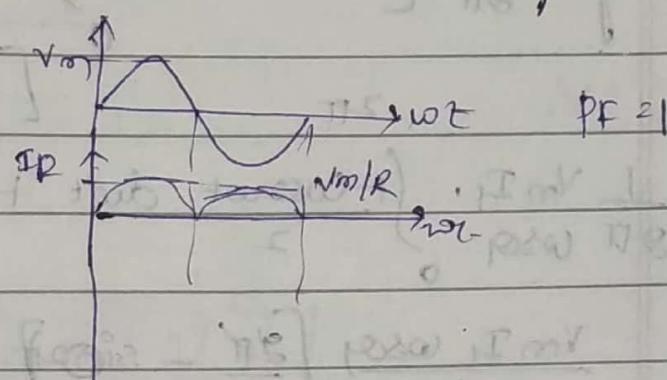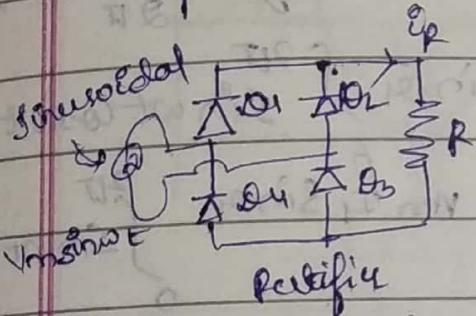Assumption \rightarrow we have assumed V & I are pure sinusoidal



when we use 'c'

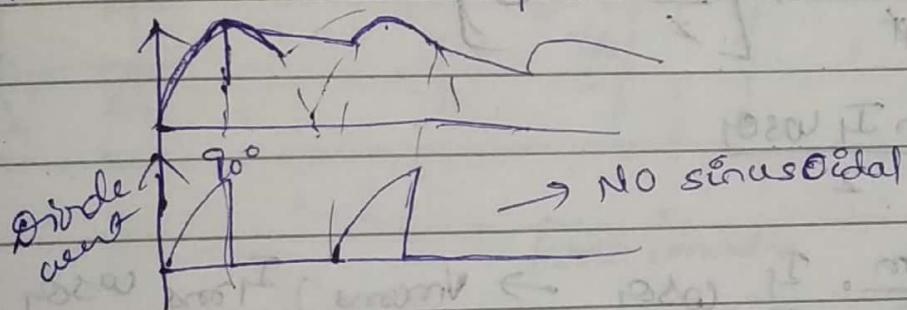

$$PF = \frac{\text{Active power}}{\text{Apparent power}}$$

first power

$$P(t) = V(t) \cdot E(t)$$

$$V(t) = V_m \sin \omega t$$

$$E(t) = \sum n_i I_n \sin(\omega n t + \theta_n)$$

$$P(t) = V_m \sin \omega t \times \sum n_i I_n \sin(\omega n t + \theta_n)$$

$$= V_m \left[(\sin \omega t \sin \omega n t \cdot \cos \theta_n) I_n + \sum n_i I_n \right] \cdot \sum n_i I_n$$

Consider $n=1$ & take the average value

$$P(t) = V_m I_1 [\sin \omega t \sin \omega t \cos \omega t + \sin \omega t \cos \omega t \sin \omega t]$$

$$P_{avg} = V_m I_1 \left[\frac{\sin^2 \omega t \cos \omega t}{2\pi} + \frac{\sin \omega t \cos \omega t \sin \omega t}{2\pi} \right]$$

Average value

$$\text{Avg } P = \frac{i}{2\pi} \int_0^{2\pi} (V_m I_1 \sin^2 \omega t \cos \omega t dt) + \frac{i}{2\pi} \int_0^{2\pi} (V_m I_1 \sin \omega t \cos \omega t \sin \omega t dt)$$

$$\text{Power} = \frac{1}{2\pi} \left[V_m I_1 \cos \omega t \int_0^{2\pi} \sin^2 \omega t dt \right] + \frac{1}{2\pi} V_m I_1$$

$$P_{avg} = \frac{1}{2\pi} V_m I_1 \cdot \frac{1 - \cos 2\omega t}{2} dt + \frac{1}{2\pi} V_m I_1 \sin \omega t \int_0^{2\pi} \sin^2 \omega t dt$$

$$\Rightarrow \frac{V_m I_1 \cos \omega t}{2\pi} \left[\frac{\pi}{2} - \sin 2\omega t \right]$$

$$\text{Power} \Rightarrow \frac{V_m I_1 \cos \omega t}{2}$$


$$\text{Power} \Rightarrow \frac{V_m \cdot I_1}{2} \cos \omega t \rightarrow V_m \cos \omega t \cdot I_m \cos \omega \theta$$

Apparent power = $V_m \cos \omega t \cdot I_m$
 (not for one is not true)
 (because one is not true)

$$\text{PF} = \frac{V_m \cos \omega t \cos \omega \theta}{V_m \cos \omega t \cdot I_m} \Rightarrow \frac{I_m \cos \omega \theta}{I_m \cos \omega \theta}$$

Distortion factor \times Displacement factor
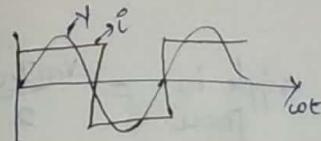
$$\text{PF} = (\text{Distortion factor} \times \text{Displacement factor})$$



Displacement factor \approx



Date _____
Page _____

(Displacement \rightarrow phase difference)

By improving PF we can reduce the

rms value of source current required

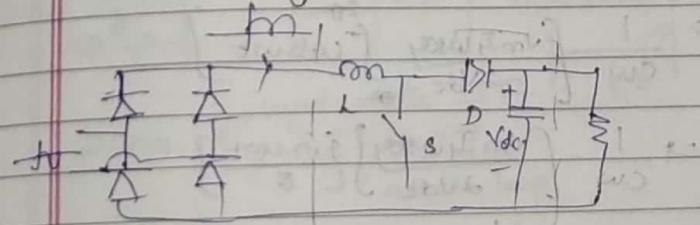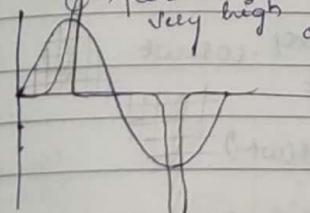\Rightarrow Plate is very high so damage to equipment so shaping current is important



Boost PFC \Rightarrow V_{dc} controlled by duty ratio
 \Rightarrow Shaping current.

Design of capacitor :-

\rightarrow using capacitor to reduce (or) eliminate the ripple in V_d
 & want less instantaneous power

$$P(t) = V_m I_1 \cos \omega t \cdot \sin^2 \omega t$$

$$\Rightarrow V_m I_1 \cos \omega t (1 - \cos 2\omega t)$$

$$\Rightarrow \frac{V_m I_1 \cos \omega t}{2} - \frac{V_m I_1 \cos \omega t \cdot \cos 2\omega t}{2}$$

Constant \Rightarrow Power Val = 0

Sulekha

$$P_{avg} = \frac{V_m I_{avg} \cos\phi}{2}$$

$$\text{ripple in power} = \frac{V_m I_{avg} \cos\phi}{2} \cdot \frac{1}{2} \text{ (2nd harmonic component)}$$

$$V_{dc} \times \text{ripple} = \frac{V_m I_{avg} \cos\phi}{2} \cos 2\omega t$$

vg ac voltage flowing through capacitor to 'o'

$$I_{ripple} = \frac{V_m I_{avg} \cos\phi}{2} \cdot \frac{\cos 2\omega t}{V_{dc}}$$

$$\Delta V_{dc} = \frac{1}{Cw} \left[\text{ripple d}(t) \right]$$

$$= \frac{1}{Cw} \left[\frac{V_m I_{avg} \cos\phi}{2V_{dc}} \right] \cos 2\omega t$$

$$\Rightarrow \frac{1}{Cw} \left[\frac{V_m I_{avg} \cos\phi}{2V_{dc}} \right] \left[\frac{\sin 2\omega t}{2} \right]$$

$$\Delta V_{dc(\max)} = \frac{1}{4Cw} \times \frac{V_m I_{avg} \cos\phi}{V_{dc}}$$


$$C \geq \frac{V_m I_{avg} \cos\phi}{4W \cdot \Delta V_{dc(\max)} V_{dc}}$$

$$\frac{1}{Cw} \left[\frac{\sin 2\omega t}{2} \right]$$

$$I_d = \frac{dV}{dt}$$

$$R_w = \frac{1}{C} \int I_d dt$$


15/3/22

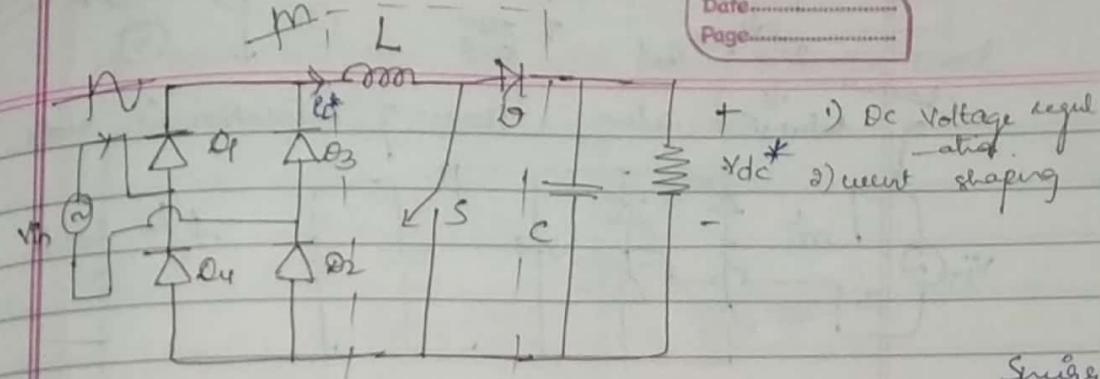


Date.....
Page.....

- 1) DC voltage regulation
- 2) current shaping

Simpler

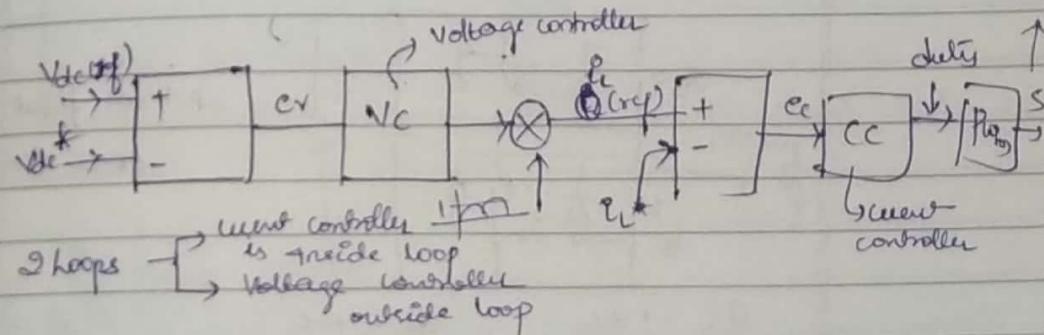

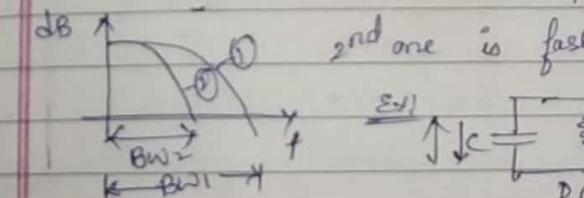2 loops
is inside loop
Voltage controller outside loop



2nd one is faster compared to 1st


$$|G(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_p}\right)^2}}$$

$$f_r = \frac{1}{2\pi\omega_p}$$

$$\tau_r = \frac{1}{2\pi f_r} \rightarrow \text{constant}$$



$$\downarrow BW = \frac{1}{\tau_r} \quad \downarrow BW = k_{p1}$$

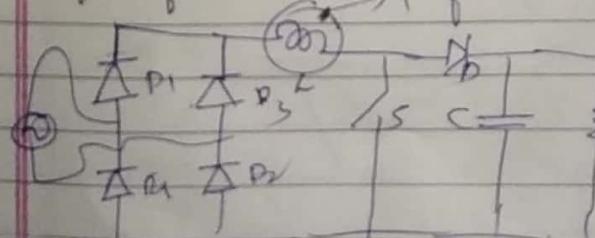Design of Inductor :-
prefixed the side leg size required
by eqn






AC $\rightarrow \sqrt{3} I_e$
DC $\rightarrow I_e$

Sulekha

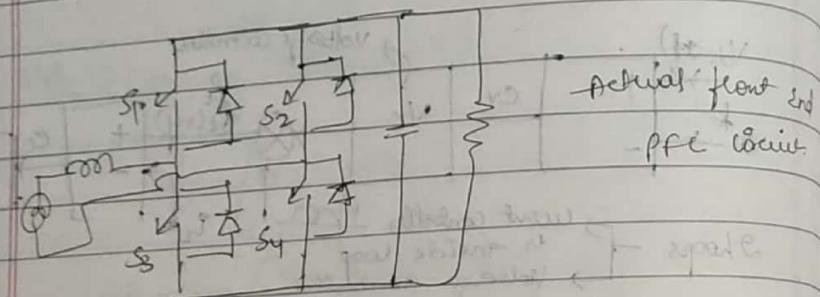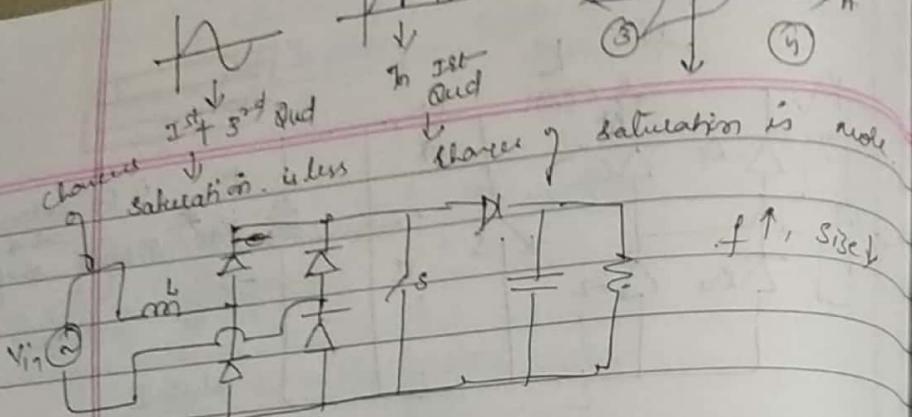

$AC \rightarrow DC$ $de - AC$
 $S_3 \rightarrow +v$ $S_1 \rightarrow +ne$
 $S_4 \rightarrow -v$ $S_2 \rightarrow -ne$

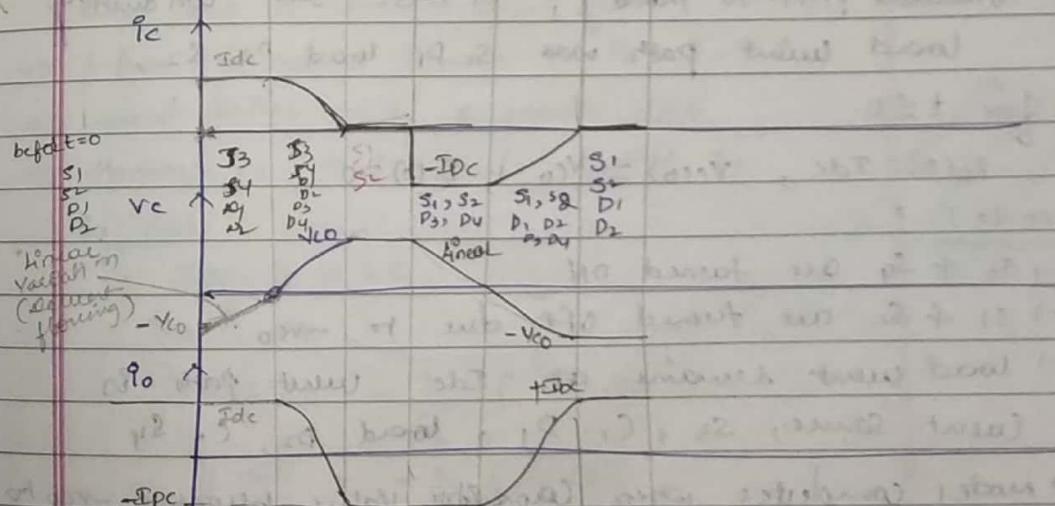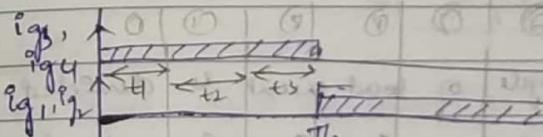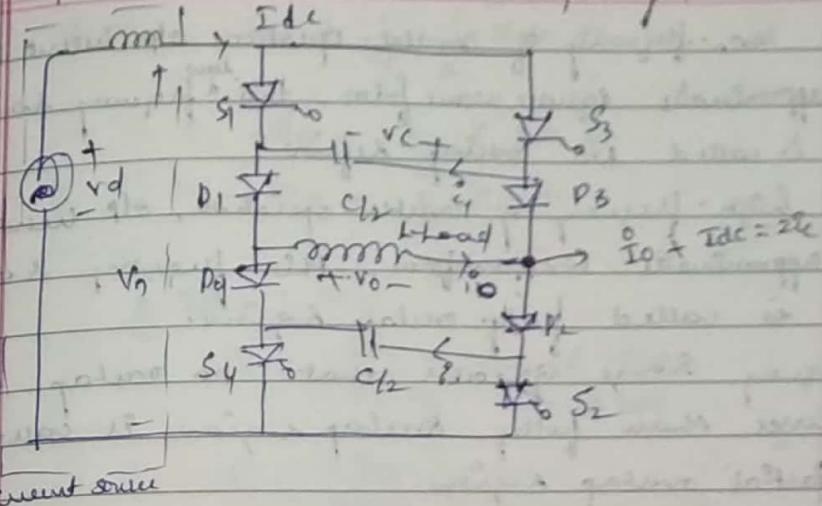10/03/22
 1) load commutated CSI with purely Inductive load.



→ At low frequency of inverter operation, OLP current I_{dc} is constant. This frequency band is called No overlap region.

→ At high frequency of inverter operation, OLP current I_{dc} is zero. This frequency band is called fully overlap region.

→ Frequency range greater than no overlap region and lesser than fully overlap region is called partial overlap region.

CSI in No overlap region :-

(Diagram) → one cycle of load current is divided into 6 modes. Prior to mode 1, S_1, S_2 are conducting. Load current path was $S_1 P_1$ load $P_2 S_2$.

for $t \leq 0$,

$$I_{o(0)} = I_{dc}, V_{c(0)} = -V_{CO}, I_{C(0)} = 0$$

Mode 1 :-

→ $S_3 + S_4$ are turned ON

→ $S_1 + S_2$ are turned OFF due to $-V_{CO}$

→ Load current remains at I_{dc} . Load path is current source, S_3, C_1, P_1 , load P_2, C_2, S_4

→ Mode 1 completes when capacitor value becomes zero.

$$V_{c(t)} = -V_{CO} + \frac{1}{C} \int_0^t I_{dc} dt$$

$$= -V_{CO} + \frac{2}{C} \int_0^t I_{dc} dt$$

$$\Rightarrow -V_{CO} + \frac{2}{C} I_{dc} t$$

t_1 = duration of model.

$$\frac{2}{C} I_{dc} t_1 = V_{CO}$$

$$t_1 = \frac{V_{CO}}{2 I_{dc}} \Rightarrow \frac{C V_{CO}}{2 I_{dc}}$$

$$t_1 = \frac{C V_{CO}}{2 I_{dc}}$$

Mode 2 :-

→ When $V_C = 0$, $D_3 + D_4$ become ON. (as voltage across load also zero due to constant current flowing through the load 'L')

→ $L + C$ are shorted through $D_1, D_2, D_3 + D_4$

→ Current enters to L, C parallel circuit

→ Through S_3 and leaves through S_4

By KCL

$$I_{dc} + I_o = 2 I_c$$

$$V_o = -V_C$$

$$L \frac{di_o}{dt} = -\frac{1}{C} \int_0^t i_c dt$$

$$L \frac{di_o}{dt} = -\frac{2}{C} \int_0^t i_c dt$$

$$\frac{di_o(t)}{dt} = -\frac{2}{LC} i_c(t)$$

Since all are conducting
to load until
not constant

$$\frac{d\phi_0(t)}{dt} = -\frac{2}{LC} \phi_c t$$

$$\phi_0(s) = \frac{I_0}{L}$$

$$\begin{cases} \dot{\phi}_0(t) = -\frac{2}{L} \frac{\phi_c + t^2}{C} \\ \phi_0(t) = -\frac{\phi_c}{L} + \frac{t^2}{C} \end{cases}$$

$$\dot{\phi}_0(t) = I_{DC} (2\omega_{N0}t - 1)$$

$$\frac{L\ddot{\phi}_0(t)}{dt} = -\frac{2}{C} \int_0^t \phi_c dt$$

$$\frac{L\ddot{\phi}_0(t)}{dt^2} = -\frac{2}{C} \dot{\phi}_c(t)$$

$$Ls^2 \dot{\phi}_0(s) = -\frac{2}{C} I_{DC}$$

$$\dot{\phi}_0(s) =$$

$$\frac{L\ddot{\phi}_0}{dt} = -\frac{1}{C} \int_0^t \phi_c dt$$

$$= -\frac{1}{C} \int_0^t I_{DC} + \phi_0(t) dt$$

Initial conditions for node 2

$$\dot{\phi}_0(0) = 0 I_{DC}$$

$$\frac{L\ddot{\phi}_0}{dt} \Big|_{t=0} = V_C \Big|_{t=0} = 0$$

25/03/22

Date _____
Page _____

$$\frac{L\ddot{\phi}_0}{dt} = -\frac{2}{C} \int_0^t I_{DC} + \phi_0(t) dt$$

$$\frac{L\ddot{\phi}_0}{dt^2} = -\frac{2}{C} I_{DC} + \dot{\phi}_0(t)$$

$$\frac{L\ddot{\phi}_0(s)}{dt^2} = -\frac{2}{C} I_{DC} + \frac{\dot{\phi}_0(0)}{C}$$

$$\frac{L\ddot{\phi}_0}{dt^2} + \frac{2}{C} \dot{\phi}_0(t) = -\frac{2}{C} I_{DC}$$

$$Ls^2 \dot{\phi}_0(s) + \frac{2}{C} \dot{\phi}_0(s) = -\frac{2}{C} I_{DC}$$

$$\dot{\phi}_0(s) \left[Ls^2 + \frac{1}{C} \right] = -\frac{2}{C} I_{DC}$$

$$\dot{\phi}_0(s) = -\frac{I_{DC}}{Ls^2 + \frac{1}{C}}$$

$$\Rightarrow -I_{DC} s$$

$$\frac{Ls^2 + 1}{s}$$

$$\Rightarrow -I_{DC} \left[\frac{1}{(s^2 + \frac{1}{L^2 C})} \right]$$

$$\Rightarrow -I_{DC} [$$

$$\dot{\phi}_0(t) = I_{DC} (2\omega_{N0}t - 1)$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\dot{\phi}_{CH} = I_{DC} (2\omega_{N0}t - 1) + \dot{\phi}_0$$

Sulekha

$$i_{c(t)} = I_{dc} [\cos(\omega_0 t) + 1]$$

$$i_{c(t)} = I_{dc} \cos \omega_0 t$$

mode 2 completing when $i_{c(t)} = 0$

$$0 = I_{dc} \cos \omega_0 t$$

~~value~~ =

$$i_{c(t)} = I_{dc} \cos \omega_0 t$$

$$V_{(CM)} = \frac{1}{C} \int_0^t i_{c(t)} dt$$

$$\Rightarrow \frac{1}{C} \int_0^t I_{dc} (2 \cos \omega_0 t - 1) dt$$

$$\Rightarrow 2 \frac{I_{dc}}{C} \left[2 \sin \omega_0 t - (t - t_0) \right]$$

$$\Rightarrow \frac{2I_{dc}}{C} \left[2 \sin \omega_0 t - t \right]$$

$$\Rightarrow 2 \cdot \frac{L}{C} I_{dc} \sin \omega_0 t$$

$$V_{CO} \sin \omega_0 t$$

$$V_{CO} = 2 \sqrt{\frac{L}{C}} I_{dc}$$

mode 2 ends when $i_c = 0$

$$\omega_0 t = \pi/2$$

$$t_0 = -I_{dc}$$

$$\text{Duration of mode 2} \quad (\omega_0 t = \pi/2)$$

$$t_2 = \frac{\pi}{2\omega_0}$$

Date.....
Page.....

Recent commutation interval $t_c = t_1 + t_2$

$$t_c = \frac{I_{dc} C_0}{2I_{dc}} + \frac{\pi}{2\omega_0}$$

- As $i_c = i_{diode} = 0$, $P_1 + P_2$ become off (but $i_c = 0$)
(same current flowing)

Mode 3 current path is source, S_3 , D_3 load D_4 & S_4
 $i_c = 0$, $P_0 = -I_{dc}$, $V_C = V_{CO} = 2\sqrt{\frac{L}{C}} I_{dc}$

→ this mode continues till S_1 & S_2 are turned ON at $\pi/2$
 $t_3 = \pi/2 \equiv (t_1 + t_2)$

$$\Rightarrow \frac{\pi}{2} = \left[\frac{C V_{CO}}{2I_{dc}} + \frac{\pi}{2\omega_0} \right]$$

$$\Rightarrow \frac{\pi}{2} = \left[\frac{C \cdot 2\sqrt{\frac{L}{C}} I_{dc}}{2I_{dc}} + \frac{\pi}{2\omega_0} \right]$$

$$\Rightarrow \frac{\pi}{2} = \left[\sqrt{L/C} + \frac{\pi}{2\omega_0} \right]$$

$$\Rightarrow \frac{\pi}{2} = \left[\sqrt{L/C} + \frac{\pi \sqrt{L/C}}{2} \right]$$

$$\Rightarrow \frac{\pi}{2} = (t_1 + \pi/2)/\omega_0$$

Mode 4 :-

During mode 4 S_1 & S_2 are turned ON & $S_3 + S_4$ are turned off due to $V_C = +V_{CO}$


the load current remains in the same direction
path is S_1 , S_2 , D_3 , load, D_4 , S_2 , & S_3 .



$\rightarrow V_{CO}$ reduces linearly to zero

$$\rightarrow \omega_0 = -\frac{2}{T_{NO}}$$

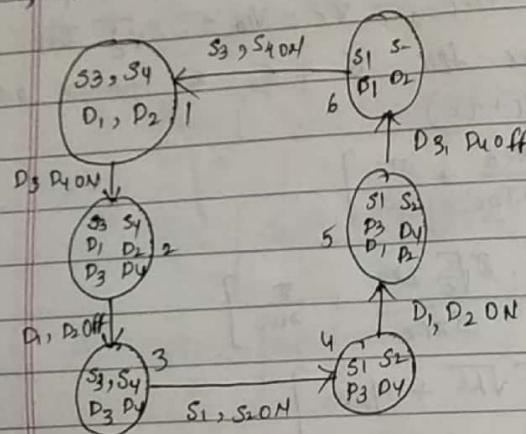Transition diagram of 1φ CSI in no-overlap region of frequency
for no over range of frequency, sequence of operating modes
6, 1, 2, 3, 4, 5, 6.



$$\rightarrow \text{commutation interval } t_c = \frac{1}{\omega_0} [1 + \pi] = \frac{2.57}{\omega_0}$$

$$\rightarrow \text{duration of mode 3 } t_3 = \frac{1}{2} - \frac{2.57}{\omega_0}$$

\rightarrow for higher frequency t_3 will effect (less)

\rightarrow when inverter frequency is increased, T is decreased and t_3 is also decreased.

\rightarrow at the limiting values of no overlap range of frequency, t_3 becomes zero

$$T_{NL} - \frac{2.57}{\omega_0} = 0$$

$T_{NL} \rightarrow$ No overlap period.

Date _____
Page _____

$\rightarrow T_{NL}$ is the minimum period for no overlap condition

$$\frac{T_{NL}}{2} = \frac{2.57}{\omega_0}$$

\rightarrow maximum frequency limit for no overlap condition


$$\omega_{NL} = \frac{\omega_0}{5.14} = \frac{0.19}{\sqrt{Lc}}$$

beyond

\rightarrow ω_{NL} we get partial overlap conditions

29/3/22

partial overlap frequency range :-

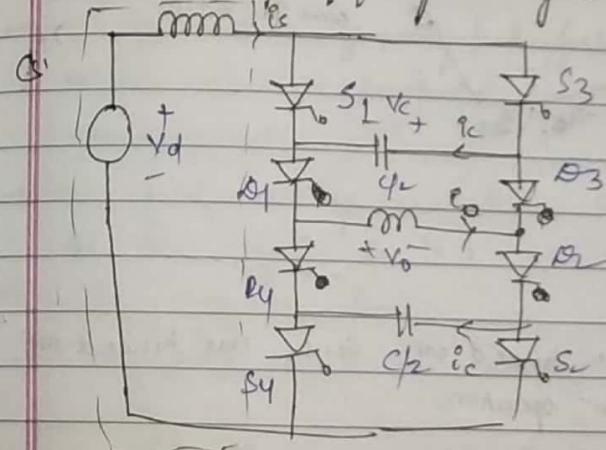

\rightarrow inverter frequency is greater than $\omega_{NL} = \frac{0.19}{\sqrt{Lc}}$

\rightarrow modes 3 + 6 are absent


\rightarrow for ω_{CO} , the inverter was in mode 5, $S_1, S_2, D_1, D_2, P_3, P_4$ were conducting

load current was oscillatory

i_L & V_C were -ve, i_O is +ve

Sukanya

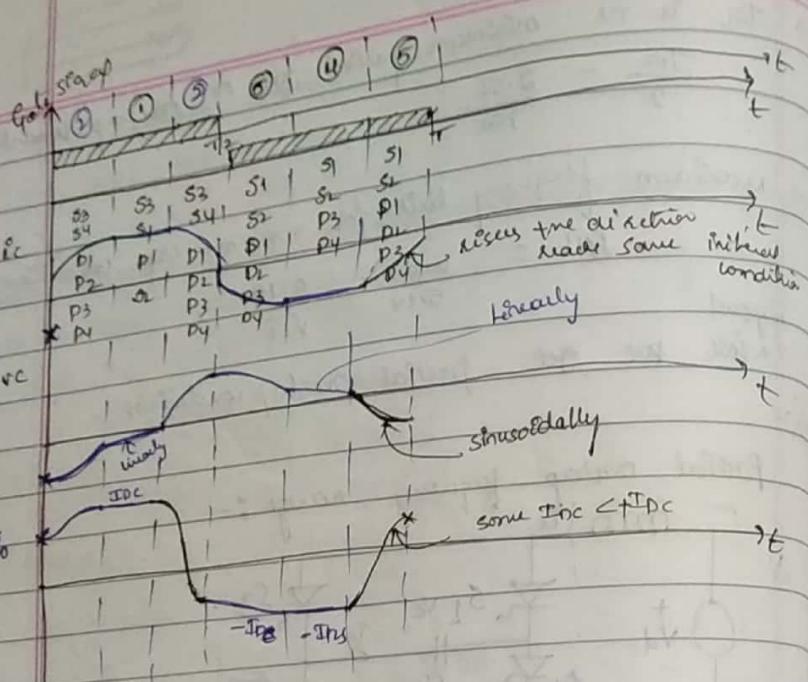(hybridized pulse
controlled by IGBT pulley
for CSI)



- At $t=0$, S_3, S_4 are turned ON. S_1, S_2 are turned off. This results in mode 2 operation.
- V_c becomes zero and rises in the +ve direction.
- I_{DC} which is zero rises to a constant value I_{DC} .
- V_b rises with a +ve slope.
- drop across the load becomes zero due to constant current of I_{DC} . D_3, D_4 are turned off.
- This results in mode 1 operation.
- Current path: source, S_3 , C , D_1 , load, D_2 , C , S_4


- Date _____
Page _____
- mode 1 ends when $V_c = 0$, $P_3 + P_4$ are brought into conduction resulting node 2 condition.
 - V_c rises in the -ve direction, I_{DC} reduces to a value less than I_{DC} .
 - In partial overlap condition, sequence of nodes in one cycle is 2, 1, 3, 4, 5.
 - maximum frequency limit for partial overlap condition is $f_{PL} = \frac{0.24}{\sqrt{Lc}}$.

Fully Overlap Condition :-


- If the inverter frequency is further increased, all the diodes conduct continuously resulting in the same load current.
- In fully overlap condition, sequence of nodes in one cycle is 2, 3, 5.

Series Inverters :-

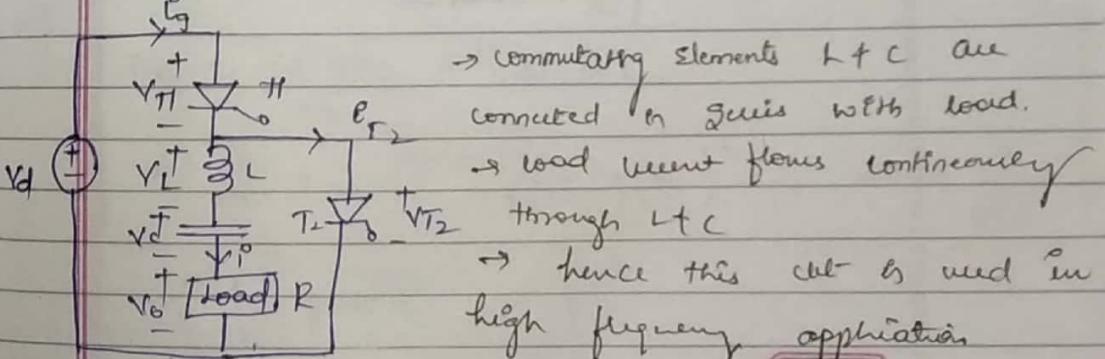- Commutation elements are connected in series with load.



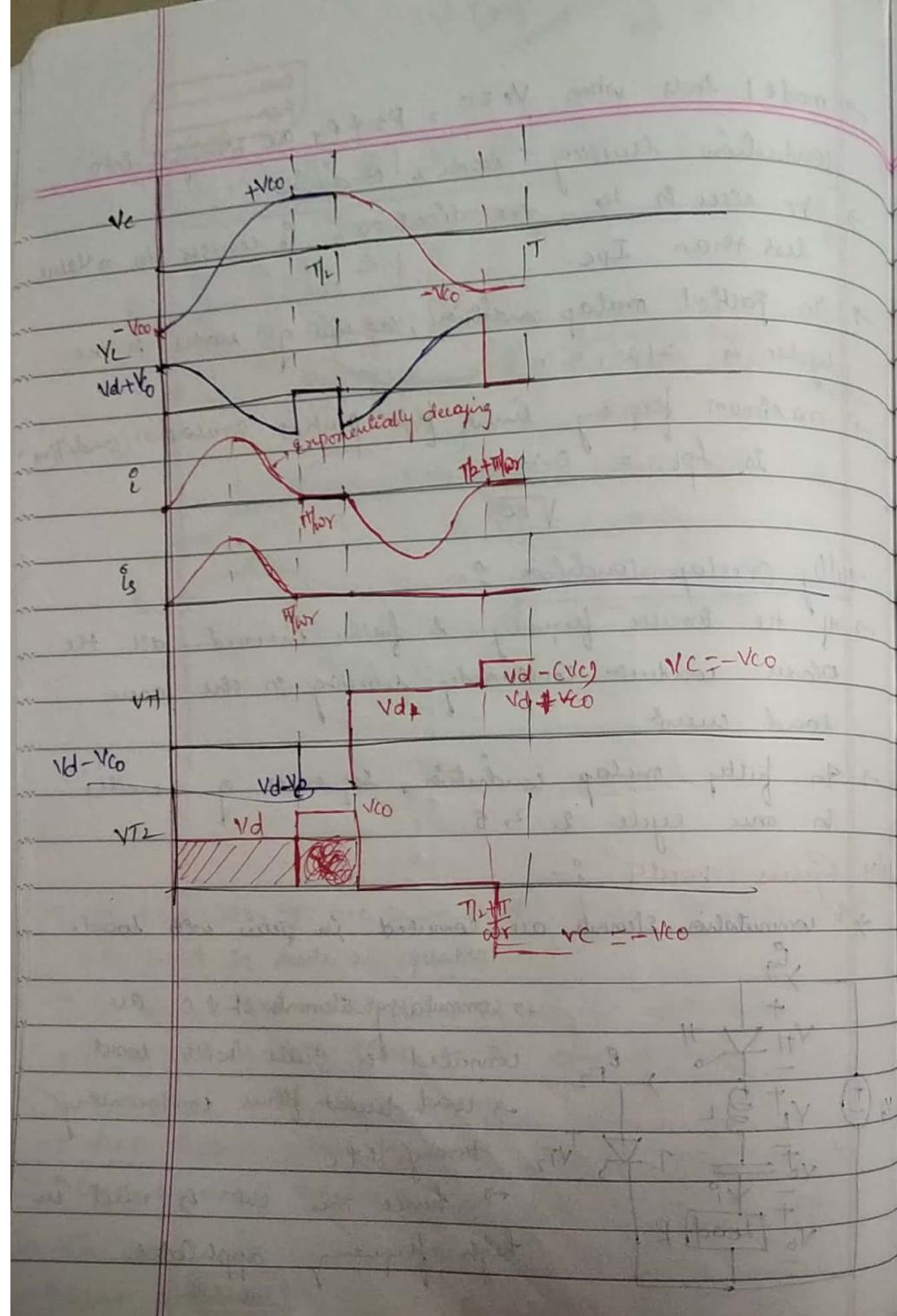- Commutating elements L & C are connected in series with load.
- Load current flows continuously through L & C .
- Hence this circuit is used in high-frequency applications.



$\rightarrow L$ & C are selected such that the conduction P.L.C is underdamped.

At $t=0$, T_1 is turned ON, T_2 is in the off state

$$V_d = R_i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt + V_{c(0)}, \quad \text{at } t=0$$

At $t=0$

$$i(0) = 0, \quad V_{c(0)} = -V_{co}$$

$$\left. L \frac{di(t)}{dt} \right|_{t=0} = V_d + V_{co}$$

$$\therefore V_d = R_i(0) + V_{co}$$

$$\frac{dV_d}{dt} = R_i(t) \cdot \frac{d}{dt} + L \frac{d^2i(t)}{dt^2} + \frac{1}{C} \cdot i(t) + \frac{1}{C} \cdot V_{c(0)} - V_{co}$$

$$\frac{V_d}{s} = R_s \cdot I(s) + L s^2 I(s) + \frac{1}{C} I(s) + \frac{V_{co}}{s}$$

$$\frac{V_d}{s} = I(s) [R_s + s^2 L + \frac{1}{Cs}]$$

$$I(s) = \frac{V_d}{s [R_s + s^2 L + \frac{1}{Cs}]}$$

$$i(t) = \frac{V_d + V_{co}}{W_r L} e^{-\delta t} \sin \omega_r t$$

$$\delta = \frac{R}{2L}, \quad \omega_r = \sqrt{\left(\frac{1}{LC}\right) - \left(\frac{R}{2L}\right)^2}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_r = \sqrt{\omega_0^2 - \delta^2}$$

$$0 = R \frac{di(t)}{dt} + L \frac{d^2i(t)}{dt^2} + \frac{1}{C} \int i(t) dt + 0$$

$$Ri(t)s + Ls^2i(t) + \frac{1}{C} \int i(t) dt = 0$$

$$Ri(t)s + L \cdot \frac{d}{dt} \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt = 0$$

$$Ri(t)s + (Vd + V_{co}) \frac{d}{dt} + \frac{1}{C} \int i(t) dt = 0$$

$$i(t) \left[R + \frac{1}{Cs} \right] = -\frac{(Vd + V_{co})}{s}$$

$$i(t) \cdot \left[\frac{Rcs^2 + 1}{Cs} \right] = -\frac{(Vd + V_{co})}{s}$$

$$i(t) = -\frac{(Vd + V_{co})}{Rcs^2 + 1}$$

Date _____
Page _____

$$i(t) = \frac{Vd + V_{co}}{wsL} e^{-\delta t} \sin \omega t$$

$$V_L(t) = L \frac{di(t)}{dt} \Rightarrow \frac{Vd + V_{co}}{wsL} \left[e^{-\delta t} \cdot \cos(\omega t) ws + \sin(\omega t) (-\delta) \cdot e^{-\delta t} \right]$$

$$= \frac{Vd + V_{co}}{wsL} \left[e^{-\delta t} \cdot ws \cdot \cos(\omega t) - \delta \sin(\omega t) \cdot e^{-\delta t} \right]$$

$$= \frac{Vd + V_{co}}{wsL} e^{-\delta t} ws \cdot \cos \omega t - \frac{Vd + V_{co} \delta \sin \omega t}{wsL} e^{-\delta t}$$

$$v(t) = (Vd + V_{co}) e^{-\delta t} \cos(\omega t + \phi) \cdot \frac{\omega_0}{\omega r}$$

$$\phi = \tan^{-1} \left[\frac{\delta}{\omega r} \right]$$

$$v(t) = Vd - V_L - CR ; V_{T1} = 0, V_{T2} = Vd, V_0 = i(t)R$$

At $t = \pi/\omega r$, $i(t) = 0$, T_1 is turned off

$\rightarrow \pi/\omega r < t < \pi/\omega$

Both switches are off

$$i(t) = 0, v(t) = 0, V_L(t) = 0, V_C = V_{max}$$

10/10/22

$\rightarrow \pi/\omega < t < \pi/\omega + \pi/\omega r$

$$t' = t - \pi/\omega$$


at $t' = 0$, T_2 is turned on

$\rightarrow 0 < t' < \pi/\omega$

$$0 = Ri(t') + L \frac{di(t')}{dt} + \frac{1}{C} \int i(t') dt + V_{max}$$

at $t' = 0$

$$i(0) = 0, v(0) = V_{max}$$

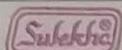

$$\frac{d(i(t))}{dt} \Big|_{t=0} = -\frac{V_{max}}{L}$$

at $t=0$
 $V_{(0)} = V_{max}, i(0) = 0,$

$$L \frac{di(t)}{dt} + \frac{1}{C} i(t) + R i(t) + V_{max} = 0$$

$$-L^2 i(t) + \frac{1}{C} i(t) + SR i(t) + V_{max} = 0$$

$$(S^2 L + \frac{1}{C} + SR) i(t) = -V_{max}$$

$$i(t) = \frac{-V_{max}}{S^2 L + \frac{1}{C} + SR}$$

$$i(t) = \frac{V_{max}}{\omega_r L} e^{-\omega_r t} \sin(\omega_r t)$$

$$i(t) = \frac{V_{max}}{\omega_r L} e^{-\omega_r t} \sin(\omega_r t)$$

$$\delta = \frac{R}{L}, \omega_r = \sqrt{\left(\frac{1}{LC}\right) - \left(\frac{R}{L}\right)^2}, \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_r = \sqrt{\omega_0^2 - \delta^2}$$

$$v(t) = L \frac{di(t)}{dt} = -\frac{\omega_0}{\omega_r} V_{max} e^{-\omega_r t} \cos(\omega_r t + \phi)$$

$$v(t) = -V_L - PR$$

$$V_{T1} = +V_d, V_{T2} = 0, V_o = -i(t)R$$

at $\omega_r = \pi, i(t) = 0, T_2$ is turned off

Characteristics of series inductor

- 1) maximum inductor frequency is limited to value less than the circuit ringing frequency (ω_r)
- 2) for very low values of inductor frequencies load voltage is highly distorted.

Design of 'L' :-

→ 'L' is chosen on the basis of attenuation factor.

$$Q_{LM} = \frac{V_d + V_{CO}}{\omega_r L} e^{\frac{R}{2L}t} \sin \omega_r t$$

peak value of $i(t)$ is $\frac{V_d + V_{CO}}{\omega_r L} e^{\frac{R}{2L}T/2\omega_r}$. ($T = \pi/2$)

→ If there is no attenuation, then $i(t)$ would be

$$\frac{V_d + V_{CO}}{\omega_r L} \sin \omega_r t \text{ & peak value} = \frac{V_d + V_{CO}}{\omega_r L}$$

$$\rightarrow \text{attenuation factor (AF)} = \frac{\frac{V_d + V_{CO}}{\omega_r L} e^{-\frac{R}{2L} \frac{T}{2\omega_r}}}{\frac{V_d + V_{CO}}{\omega_r L}} = e^{-\frac{R}{2L} \frac{T}{2\omega_r}}$$

$$\ln(\text{AF}) = \frac{-R}{8f_r L}$$

$$L = \frac{-R}{8f_r \ln(\text{AF})}$$

L selected such that AF = 0.5

R - min load resistance.

Design C :-

→ i_c is selected from the value of w_r

$$w_r = \sqrt{\left[\frac{1}{L_C} - \left(\frac{R}{2L}\right)^2\right]}$$

$$C = \frac{1}{L} \left[\frac{1}{w_r^2 + \left(\frac{R}{2L}\right)^2} \right]$$

→ If the load is variable, then C is selected for the maximum possible value of L so that the circuit is under damped.

→ Voltage rating of i_c is ~~V_{max}~~ V_{max}

Selection of thyristor :-


→ Forward blocking voltage rating must be greater than V_{max}

→ Peak current rating must be greater than peak load current for minimum load resistance

$$\frac{V_d + V_{CO}}{w_r L} < \frac{R_{min}}{2L} \cdot \frac{T}{2w_r}$$

→ t_q must be less than t_c = $\frac{T}{2} - \pi/w_r$

Modified Series Inverter

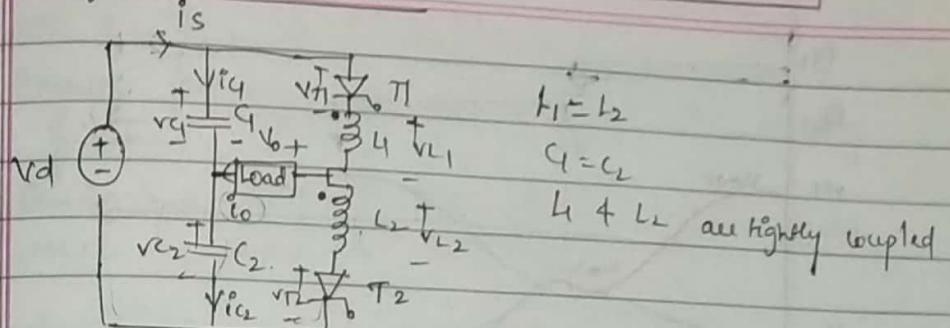

→ for t=0, T₂ ON

$$V_Q = V_{Cmax}$$

$$V_{C2} = -V_{min}$$

I_O is Negative.

$$I_O = E_O \times R$$

I_{C1} is positive & I_{C2} is -ve.

I_S is +ve, V_{L1} is -ve, V_{L2} is -ve

• At t=0, T₁ is turned ON

V_{C1} is coupled across L₁ = V_{L2}, T₂ is commutated off

• G₁ discharge through L₁ + load.


• V_{C1} changes from V_{Cmax} to V_{min}, C₂ gets charged through T₁, L₁ and load.

$$I_O = I_S - I_Q$$

$$I_{C2} = I_Q + E$$

$$I_S = I_{C2} (+ve)$$

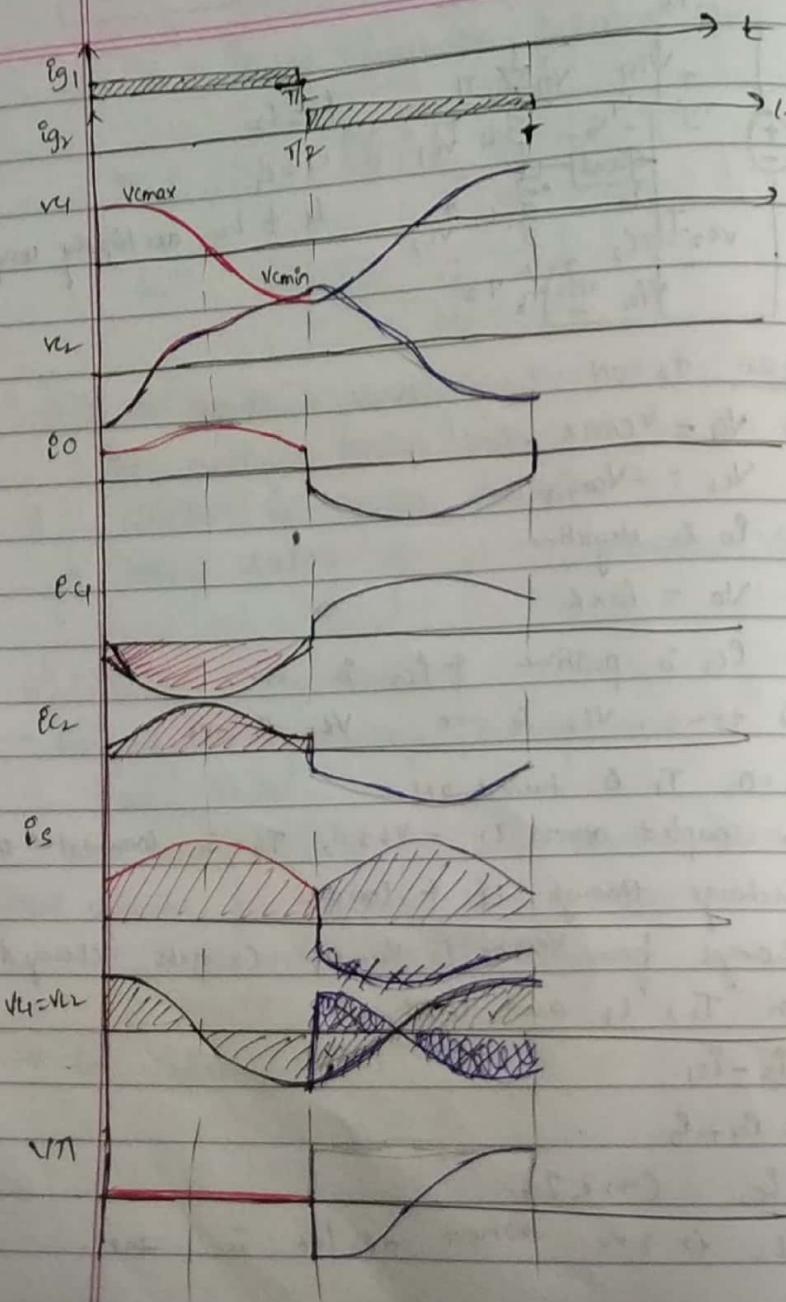
V_{L1} = V_{L2} is +ve when dI_O/dt is +ve



- At $t = T/2$, T_2 is turned ON
- Inverter frequency can be less than the ringing frequency
- During one half cycle also source supplies power lesser distortion in source current.

22/4/22

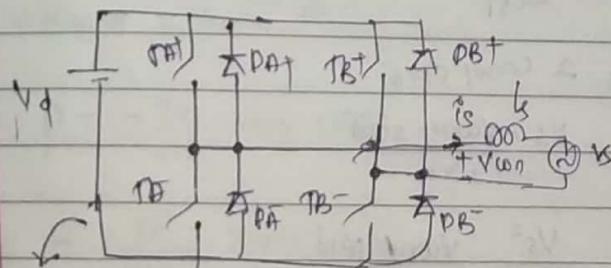- Rectifier mode of operation occurs during regenerative braking of an induction motor load connected to a DC source through an inverter.
- Kinetic energy associated with motor and load is recovered and fed back to the DC source.



→ A single phase induction motor is connected DC source through inverter

$L_s \rightarrow$ Winding Inductance

$V_s \rightarrow$ back EMF (sinusoidal with fundamental frequency)

$$V_{con} = V_{Ls} + V_s$$

$$V_{Ls} = L_s \text{ dis}/dt$$

fundamental


$$V_{con1} = V_{ls1} + V_s$$

$$V_s = V_{con1} - V_{ls1}$$

$$= V_{con1} - j\omega L_1 I_{s1}$$

→ direction of I_{s1} decides the converter and rectifier mode of operation.

Inversion mode

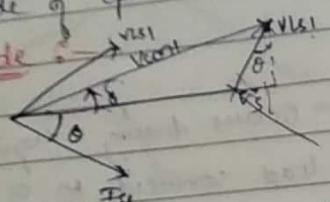

- V_{con1} leads V_s by an angle ' δ '

• Real power at the AC side

$$P = V_s I_{s1} \cos \theta$$

$$= V_s \times \frac{V_{ls1}}{\omega L_1} (\cos \theta)$$

$$V_{ls1} \cos \theta = V_{con1} \sin \delta$$

$$P = V_s \cdot \frac{V_{con1} \sin \delta}{\omega L_1}$$

$$P = \frac{V_s^2}{\omega L_1} \frac{V_{con1} \sin \delta}{V_s}$$

→ V_{con1} leads V_s and active components of I_{s1} is inphase with V_s .

power flows from AC side to AC side → Inversion mode

Reactive power at the AC side


$$Q = V_s I_{s1} \sin \theta$$

$$= V_s \frac{V_{ls1}}{\omega L_1} \sin \theta$$

$$V_{ls1} \sin \theta = V_{con1} \cos \delta - V_s$$

$$Q = \frac{V_s}{\omega L_1} [V_{con1} \cos \delta - V_s]$$
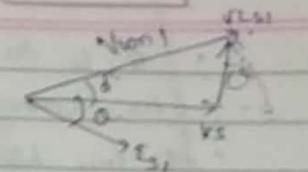
$$= \frac{V_s^2}{\omega L_1} \left[\frac{V_{con1}}{V_s} (\cos \delta - 1) \right]$$



Rectification mode :-


• V_{con1} lags the V_s by an angle ' δ '

• Real power at the AC side

$$P = V_s I_{s1} \cos(180 + \theta)$$


$$= -V_s V_{ls1} \cos \theta$$
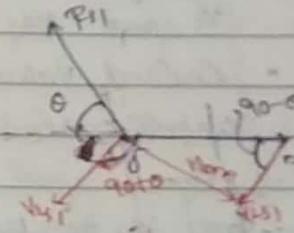
$$V_{ls1} \cos \theta = V_{con1} \sin \delta$$



$$P = -\frac{V_s}{\omega L_1} V_{con1} \sin \delta$$
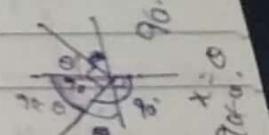
$$= -\frac{V_s^2}{\omega L_1} \frac{V_{con1} \sin \delta}{V_s}$$



$$180^\circ = 90^\circ + 70^\circ + 20^\circ$$

$$\Rightarrow \theta = 20^\circ$$


Rectified power at the AC side :-

$$Q = V_s I_{s1} \sin(180 + \theta)$$

$$= -V_s \frac{V_{ls1}}{\omega L_1} \sin \theta$$

$$Q = -\frac{V_s}{\omega L_1} [V_s - V_{con1} \cos \delta]$$

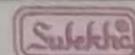
$$R = \frac{V_s^2}{\omega L_1} \left[\frac{V_{con1}}{V_s} \cos \delta - 1 \right]$$




Date _____
Page _____

Refer
(red notes
Chapter 5 & 6)


- Q is the sum of reactive power absorbed by the converter and inductance L_s .
- At very high switching frequencies L_s can be made very small.
- Then Q is the reactive power absorbed by the converter.
- For given value of AC side potential (back emf) V_s and the chosen value of inductance L_s , desired values of $P \neq Q$ can be obtained by controlling the magnitude and phase angle δ of V_{con} .
- V_{con} can be varied by keeping the magnitude of I_{S1} and V_s constant.

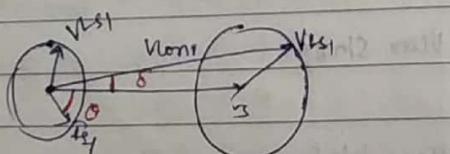

Generation at UPF :-

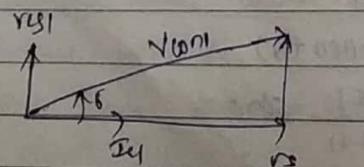


Distribution at UPF :-

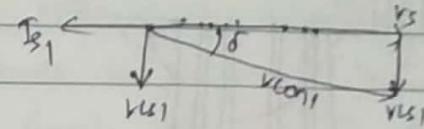

- In both cases

$$V_{con1} = \sqrt{V_s^2 + (wL_s I_s)^2}$$

- For the desirable magnitude and direction of $P \neq Q$, the magnitude of V_{con1} & the phase angle ' δ ' must be controlled.
- PWM converter works in the linear range ($\alpha \leq 1$)
- V_d must be of sufficiently large magnitude $|V_d| > |V_s|$
- Reactive power flow can be controlled by introducing a phase shift between V_S & V_{con}
- From V_S based static VAR compensation
- From VSI based SVCS - are viable solution to problems associated with passive shunt compensators, thyristor controlled reactors.
- They are capable of delivering controlled amount of lagging and leading vars to a load on a bus system rapidly.

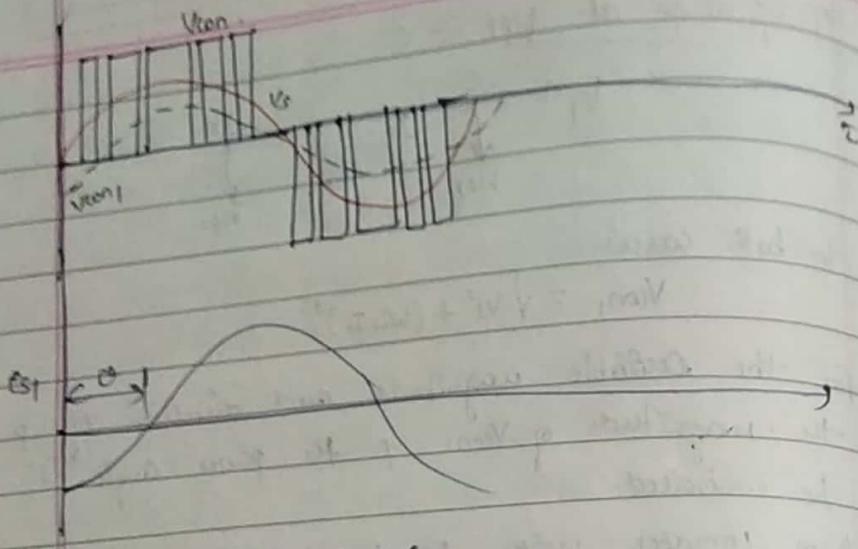

26/04/22 Resonant converters :-

High frequency Switchmode power converters :-

Advantages :-

- high efficiency

• Devices operate at the maximum

Efficient points like cut off & saturation points

• multi output is possible.



• Size and cost are much lower especially at high power levels.

Limitations :-

• Greater circuit complexity compared to linear converters.


• Controllable switches (operated in a switch mode) are required to turn on and off the entire load current during each switching

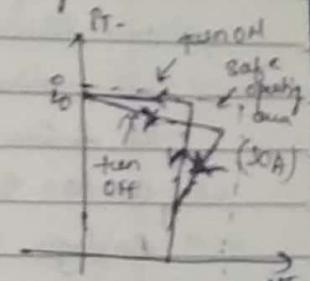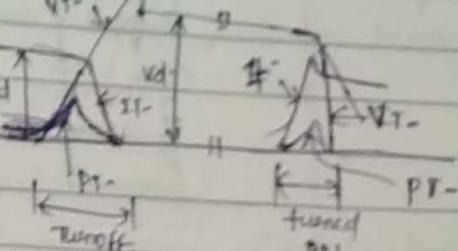
- occurrence of large dI/dt and dV/dt during switching hence high electromagnetic interference
- high stress levels on devices that increases linearly with the switching frequency of the power converter.
- higher switching losses at higher frequencies



Dissipative Snubber cells :-

- the switching stresses can be reduced by connecting simple dissipative circuits in series and parallel with the switches in the switch mode converters.
- these snubbers shift the switching power loss from the switches to the snubber circuit and do not provide a reduction in the overall switching power loss.
- To minimize these problems, switches are made to change the status of turn on to turn off (ON via V_{DS}) when the voltage across it (V_{DS}) went through zero at the switching instant.

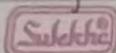

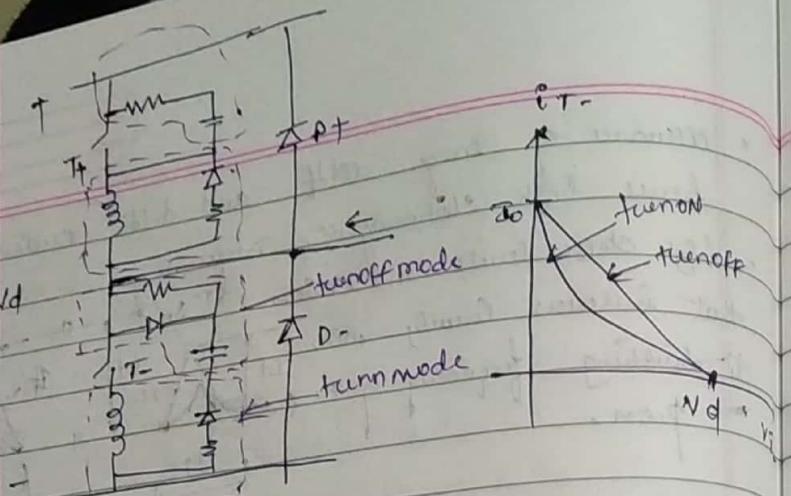

- These topologies require some form of LC resonance and hence they are classified as resonant converters.

- The switch voltage and current are shaped so as to get zero voltage & (or) zero current switching and are known as soft switching converters.

Advantages of soft switching resonant converters:

- Reduced power loss at high switching frequency
- Low size and hence high power density
- High efficiency
- Less stress on the devices.

(Zero current)


Classification of Resonant Converters.

Resonant Switch converters :-

- Additional (LC) elements are added to get zero voltage & zero current switching and are called resonant switch converters.
- i) Zero current switching (ZCS) topology
- ii) Zero voltage switching (ZVS) topology
- iii) Zero Voltage switching, clamped voltage. (ZVS CV) topology
- LC Resonance is utilized to shape the switch voltage and current to provide zero-voltage and/or zero-current switching
- During one switching period, there are resonant as well as non-resonant operating intervals. therefore these converters are also known as quasi-resonant converters.


Zero current switching (ZCS) converters :-

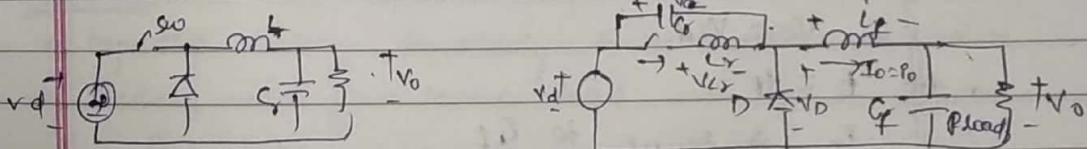- The switch turn ON and turn off occurs at zero current.
- I_o & C_L are the resonant elements used to get zero current turn on & turn off condition.



Initial conditions :-

- Let the switch is in the off condition.
- Diode is in the ON state
- $V_C = V_D$, $i_T = 0$
- At $t = t_0$ switch is turned ON.
- Due to the presence of inductance, turn on occurs at two instant
- $L_x + C_x$ are shorted through switch.
- $V_{D0} = V_D - V_C = 0$
- $V_C = V_D$
- Diode continuous to conduct.
- $V_D = V_C = V_D$

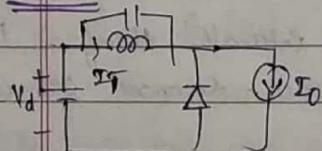 $t_0 \rightarrow t_1$ 

$$V_{D0} = V_D$$

i_T rises linearly.

i_T is less than i_{f0} .

$$e_D = I_0 - i_T$$

- D continues to conduct until $i_T = I_0$



$$V_C = V_D$$

At $t = t_1$

e_T is equal to e_{if}

- D stops conducting

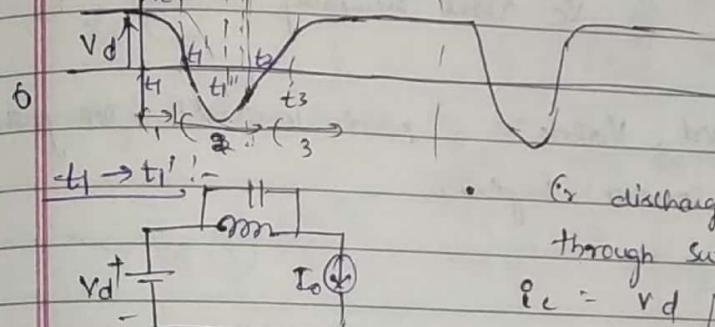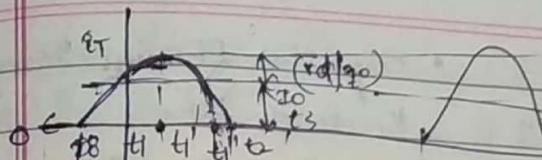- $L_x + C_x$ form a parallel resonant circuit.



Cx discharges from V_D to zero through switch & L_x

$$i_c = V_D \sqrt{\frac{4\pi}{LC}} \sin \omega t$$

$$\omega_0 = \frac{1}{\sqrt{L_x C_x}}$$

$$e_T = I_0 + e_c$$

- At t_1' e_T & i_c are to their peak value V_C reaches zero.

 $t_1' \rightarrow t_1''$

- i_c decreases sinusoidally to zero

- At t_1'' , $i_c = 0$, $e_T = I_0$, V_C reaches $-V_D$

 $t_1'' \rightarrow t_2$

- Capacitor discharge sinusoidally in the negative direction.

- Discharge current flows towards load circuit


$$e_T = I_0 - i_c$$

- i_T reduces to zero sinusoidally.

- Switch is turned off naturally

- Turn off occurs at two instant.

$t_2 \rightarrow t_3$:-

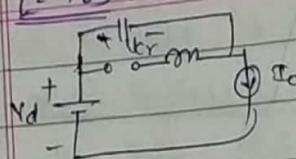

- capacitor discharges through the load circuit.

$$i_L = I_0 \text{ which is constant}$$

V_C rises linearly to V_d .

$t = t_3$

$V_C = V_d$, $V_{diode} \approx 0$ \Rightarrow diode conducts, off period

at $t = t_3$ buck converter begins.


$t_3 \rightarrow t_4$

- switch is off
- load current freewheels through diode
- $V_C = V_d$
- $i_L = 0$
- at $t = t_4$ gate pulse given to switch.


15/27

ZVS Switching (ZVS) Condition :-

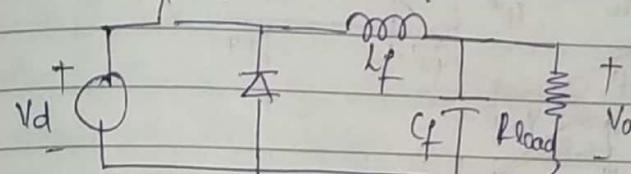- the switching turn on & turn off occurs at zero voltage.



modified Buck converter to get ZVS

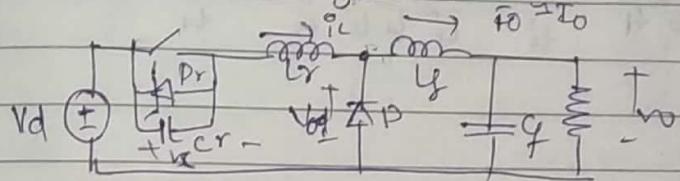

Initial condition :-

- the switch is in ON state. D is off
- $V_C = 0$
- $i_L = I_0$
- $V_O = V_d$
- At $t = t_0$ switch is turned off (at ZVS condition begin)
- Due to the presence of capacitance turn off occurs at ZVS


$t_0 \rightarrow t_1$:-

- i_L which is constant load current flows through the capacitor
- V_C rises linearly from zero to V_d .
- at $t = t_1$, $V_C = V_d$, $V_O = V_d - V_C = 0$, diode starts conducting.

$t_1 \rightarrow t_1'$:-

- switch is off and D is on
- $C_r + L_r$ resonates

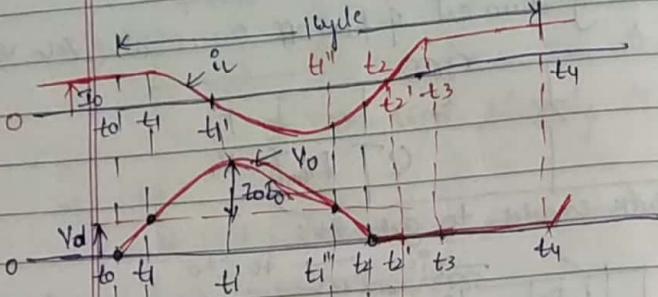- c' gets charged to a potential greater than V_d due to -ve voltage acc L_r .
- $V_c > V_d$
- at t_1' , i_L is zero V_c is maximum $= V_d + V_{cr}$



t_1' to t_1'' :

- capacitor discharges through dc source, D + L_r
- i_L reverses sinusoidally due to $L_r - C_r$ resonance.
- $i_o = I_o - i_L$, At t_1'' $V_c = V_d$.

- $i_L = -I_o$, at t_2 $V_c = 0$.

- $V_{Dr} = 0$, Dr starts conducting

- V_c continues to be at zero

$t_2 \rightarrow t_3$:

- P + Dr conduct, $V_{cr} = 0$, $V_{Lr} = V_d$

- i_L rises linearly to I_o through Dr.

Switch is reverse biased while Dr is conducting.

- at t_3' , $i_L = i_{Dr} = 0$, Dr becomes off &

switch goes to the on state if gating signal

is provided. to achieve on state of switch

Date.....
Page.....

- converter circuit.

- Gating signals are applied to the switch during this interval

- V_{cr} continues to be at zero potential and turn on occurs at zero voltage.

- peak voltage acc the switch is $2V_d$.

- reverse recovery voltage of diode $2v = 2V_d$.

- switch becomes on at t_3' when $i_L = I_o = 0$ & Dr is off $\Rightarrow V_c$ remains at zero. turn on occurs at zero voltage condition

$t_3' \rightarrow t_4$:

- i_L rises linearly to I_o , P is still conducting $V_{Lr} = V_d$

$t_3 \rightarrow t_4$:



- $i_L = I_T = I_o$, $V_{cr} = 0$, $V_o = V_d$.

- at t_4 switch is turned off again at zero voltage

Sulekha

8/5/22

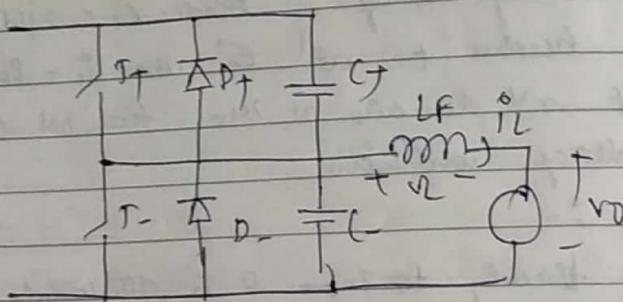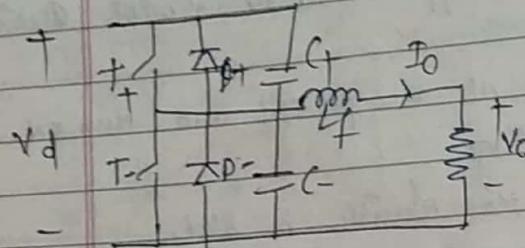ZVS Switching clamped v (ZVS-CV) topology



- Switches turn on & off at zero 'v'
- Peak 'v' across the switches is clamped to the supply dc 'v'
- Cf is considered as very large & hence load is replaced by a v source (the v remains constant).
- Initial conditions: T+ is on & T- is off

$$V_L = V_d - V_o \text{ (constant)}$$

i_L rises linearly

$$V_c = V_{o1} = V_d; \quad V_{T+} = 0$$


Date _____
Page _____

at $t = t_0$; T- is turned off at $2V_{d\text{max}}$ value to V_{c+}


- $C_+ = C_- = V_{c+}$ are selected as of small values
- the resonant frequency $f_0 = \frac{1}{2\pi\sqrt{Lc}}$ is very large compared to switching frequency.
- Lf/c is very large & variation in lf is small
- $i_L = i_o = i_{c+} + i_{c-}$

at $t_0 \rightarrow t_0'$

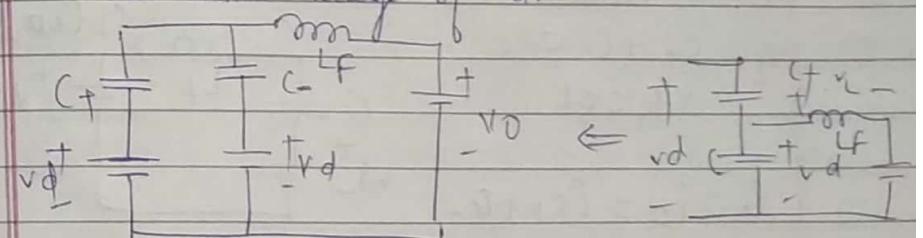T+, T-, D+, & D- are in the off state
C- has initial voltage of V_d .



Equivalent circuit

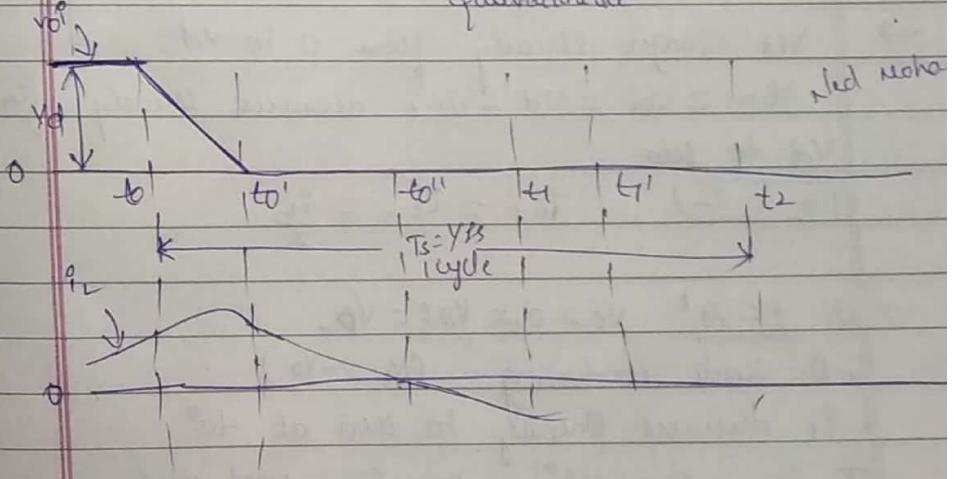

$\rightarrow t_1 \rightarrow t_1'$ T_f & T are off, $-ve$ i_L flows through i_L
 (+ discharge from V_d to $0'$ through L_f & T_{IP})
 Source $-ve$ gets charged from 0 to V_d .


$\rightarrow t_1' \rightarrow t_2$ when V_{C+} is zero, Diode conducts $-ve$ i_L
 $V_L = V_d - V_o$ is $+ve$ (as buck converter $V_o < V_d$)
 $\frac{di_L}{dt} = +ve$ (I rises)
 $\frac{di_L}{dt} V_{C-} = V_o i_L = V_d$

T_f is gated while D^+ is conducting.
 T_f starts conducting when D^+ becomes off when
 i_L is reduced to zero.

$$C_p = C_+ + C_- = C$$

$$V_{TH} = V_d$$

$$i_L = i_o = i_{C+} + i_{C-}$$

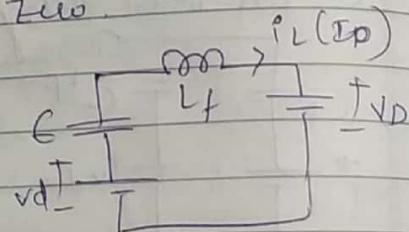

$\rightarrow V_{C+}$ changes linearly from 0 to V_d .
 $V_{C-} = V_o = V_d - V_{C+}$ decreases linearly from
 V_d to zero.

$$(C_+ = C_-) \quad i_{C+} = i_{C-} = \frac{i_L}{2}$$

\rightarrow at $t = t_1'$ $V_{C+} = 0, V_o = V_{D-}$

- D^- starts conducting ($V_L = -V_o$)

- i_L decreases linearly to zero at t_1''

T^- is gated while D^- is conducting

Date.....
Page.....

T^- starts conducting when D^- becomes off due to
 Zero i_L at t_1''

at t_1'' D^- goes to the off state and T^- is gated
 at some instant between t_1' & t_1''

at t_1'' D^- becomes off, T^- starts conducting
 i_L reverse (~~-ve~~ (+ve)) direction

at $t_1'' \rightarrow t_1$ i_L flows through T^-

{ Mem v wrong
 all T_f & V_d

at t_1 T^- is turned off $i_L \rightarrow ve$ value