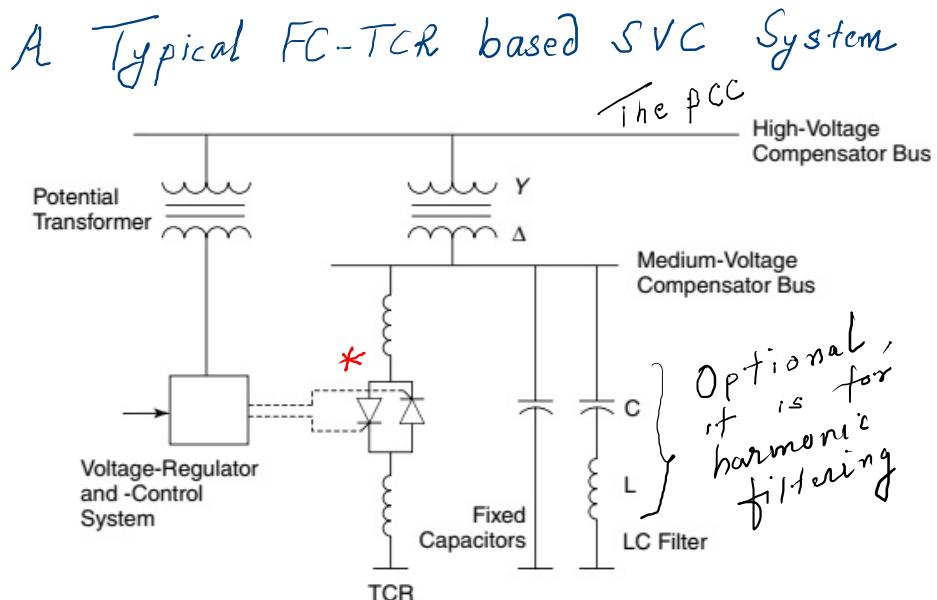


# The Fixed Capacitor - Thyristor Controlled Reactor (FC-TCR) Static VAR Generator and Its Control



A 1-line diagram of a TCR compensator with fixed-shunt capacitors.

\* A single Thyristor used in FACTS controllers can block 4 to 9 kV, and carry 3000 - 6000 A forward current. 10 to 20 such units are connected in a series string

To raise blocking voltage capability and many such strings are connected in parallel to increase current carrying capability.

## Operation of a TCR

[ You can use the following as Text books for this portion .


1. Understanding FACTS by Hingomani & Gyugyi, Section 5.2
2. Thyristor-based FACTS Controllers for Electrical Transmission Systems by R. Mohan & Rajiv K. Varma, IEEE Press, Wiley Interscience Section 3.4

# The Fixed Capacitor - Thyristor Controlled Reactor (FC-TCR)



## Static VAr Generator and Its Control

A Single-phase TCR Unit

$$V_{bus} = V_m \cos \omega t$$

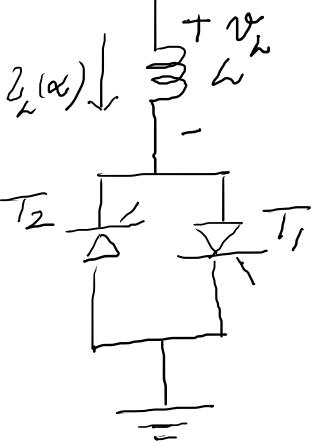

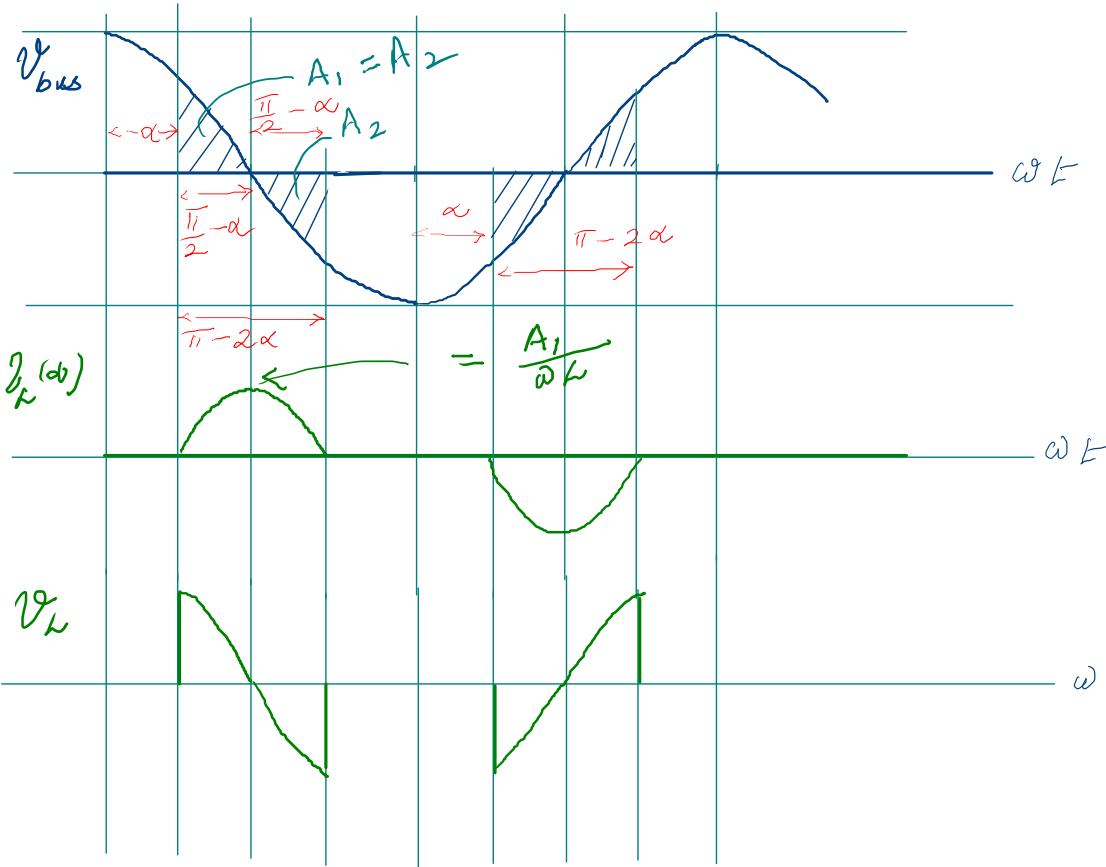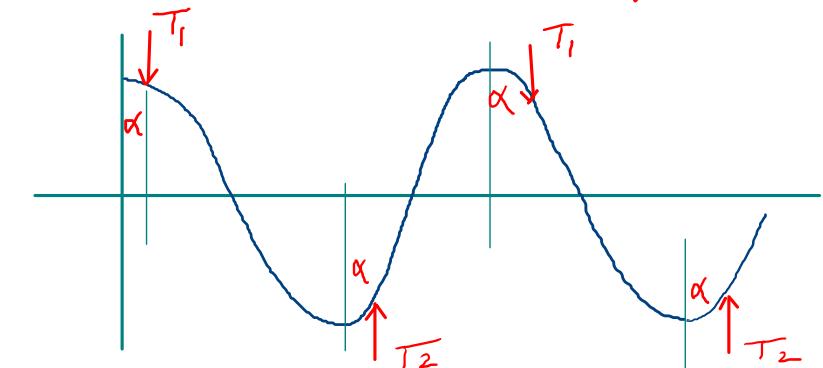Firing angle of  $T_1$  is  $\alpha$  degrees after the peak position of voltage in +ve half-cycle and firing angle of  $T_2$  is  $\alpha$  degrees after the peak of voltage in -ve half-cycle.



Maximum delay in obeying a firing angle change command =  $T/2$  sec

# The Fixed Capacitor - Thyristor Controlled Reactor (FC-TCR)

## Static VAr Generator and Its Control

$$I_{LF}(\alpha) = \text{amplitude of fundamental}$$

$$= \frac{V_m}{\omega L} \left( 1 - \frac{2}{\pi} \alpha - \frac{1}{\pi} \sin 2\alpha \right)$$


with  $\alpha$  in radians.

Susceptance at fundamental frequency  $\triangleq B_L(\alpha)$

$$\therefore B_L(\alpha) = \frac{1}{\omega L} \left( 1 - \frac{2}{\pi} \alpha - \frac{1}{\pi} \sin 2\alpha \right)$$

Range of  $\alpha = 0$  to  $90^\circ$  and  $\alpha$  is measured from  $90^\circ$  position on Sine wave.

$$\omega L \times B_L(\alpha)$$

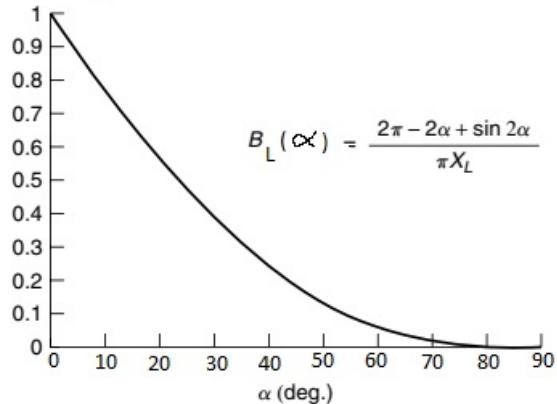


$$I_{Ln}(\alpha) = \text{amplitude of } n^{\text{th}} \text{ harmonic}$$

$$= \frac{V_m}{\omega L} \frac{4}{\pi} \left\{ \frac{\sin n\alpha - n \cos n\alpha \sin n\alpha}{n(n^2 - 1)} \right\}$$

for odd  $n$  and  $n \neq 1$

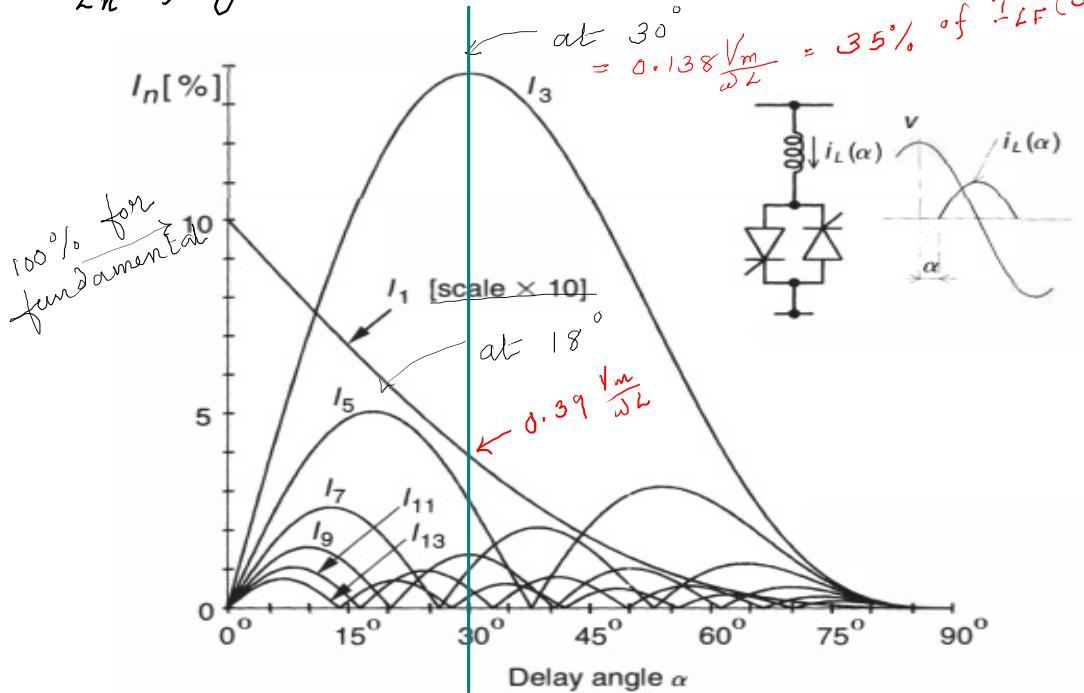
$I_{Ln}(\alpha)$  goes to a max when  $n\alpha = 90^\circ$



Amplitudes of the harmonic components in the current of the TCR versus the delay angle  $\alpha$ .

# The Fixed Capacitor - Thyristor Controlled Reactor (FC-TCR)

## Static VAr Generator and Its Control

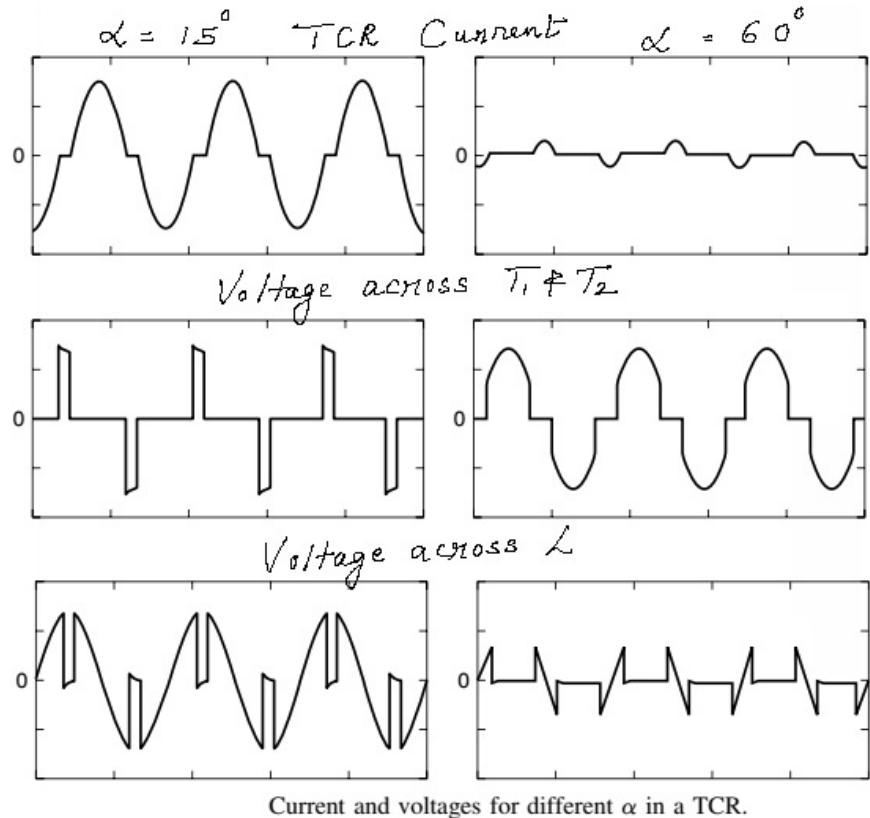


- Can there be even order harmonics ?

Yes, if the  $\alpha$  value in +ve and -ve half-cycles are different. In that case  $I_\alpha(\omega)$  will contain a DC component also.

### Control of Harmonics in a $3\phi$ TCR

1. Delta Connection.

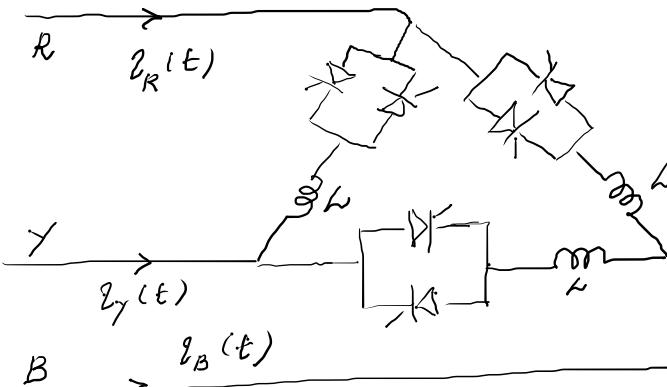



#### Assumptions -

- The value of  $L$  in three legs are equal
- Thyristors are fired with same firing delay  $\alpha$
- $3\phi$  symmetry is maintained accurately
- Line Voltages are balanced

Then, triplen harmonic currents circulate BE present in  $I_R(t)$ ,  $I_Y(t)$  and  $I_B(t)$ .



# The Fixed Capacitor - Thyristor Controlled Reactor (FC-TCR)

## Static VAr Generator and Its Control

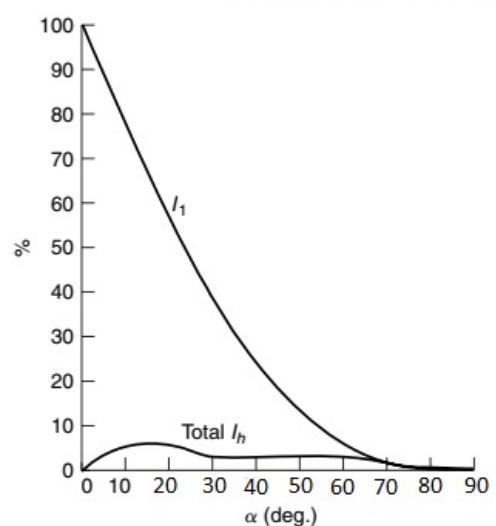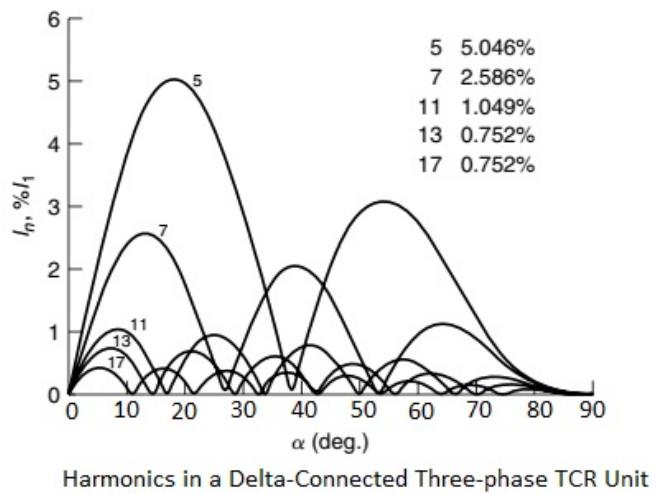

But if firing in the 3 legs are not exactly at  $120^\circ$  or if the supply voltage is unbalanced (in amplitude or in phase or in both), the tripleton harmonics will flow in the lines.

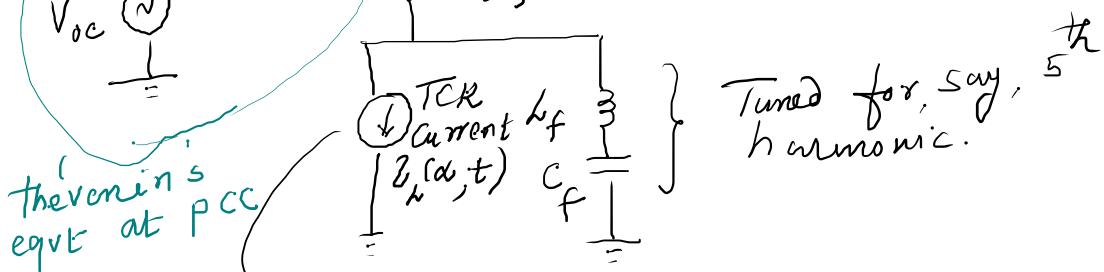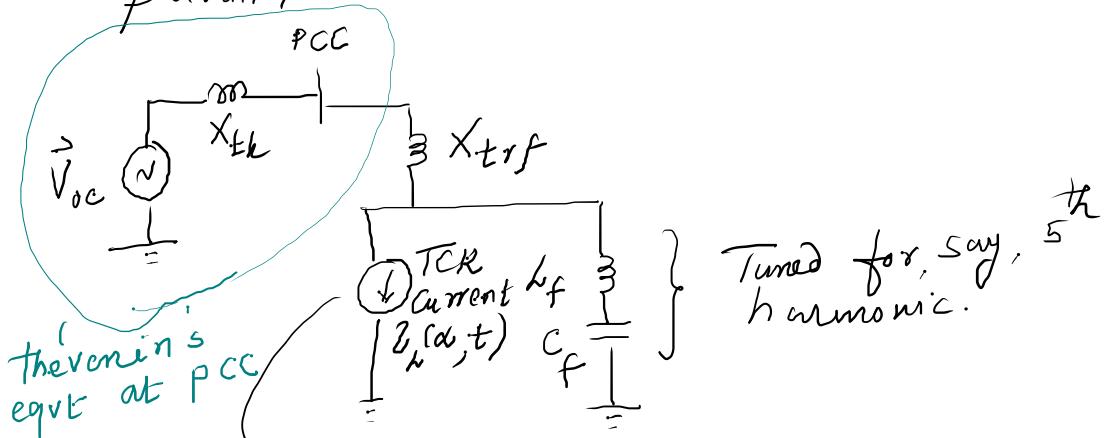- Use passive parallel Tuned Harmonic filters on TCR.




has  $50\text{Hz}$ ,  $250\text{Hz}$ ,  $350\text{Hz}$  ... Current components

Problem: One tuned structure per harmonic order to be cancelled will be needed.


# The Fixed Capacitor - Thyristor Controlled Reactor (FC-TCR)
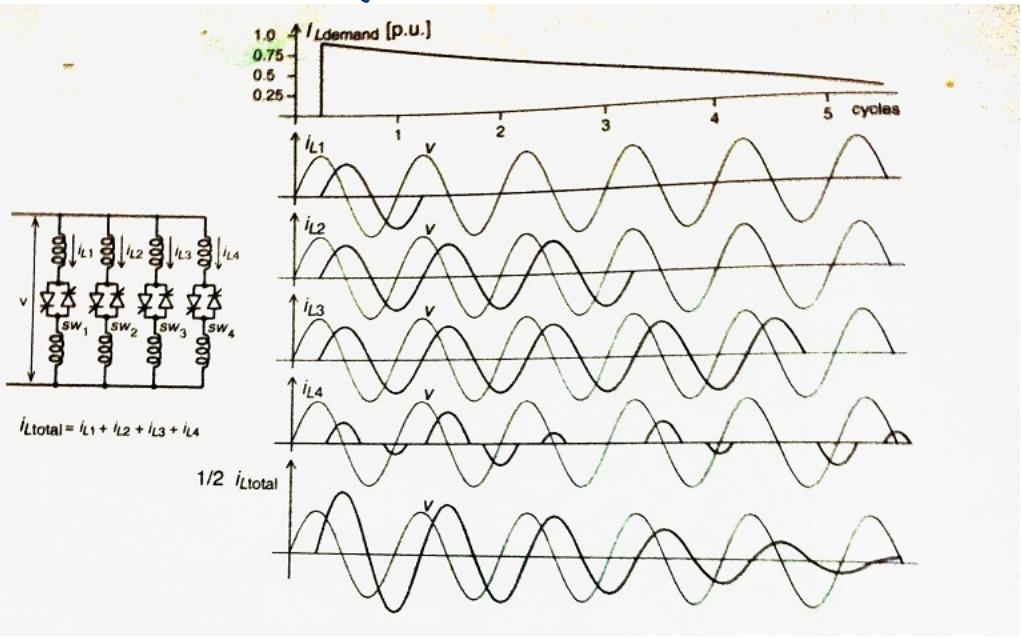
## Static VAr Generator and Its Control

- Use Segmented TCR  
Total required TCR rating is distributed equally among 'n' smaller units.



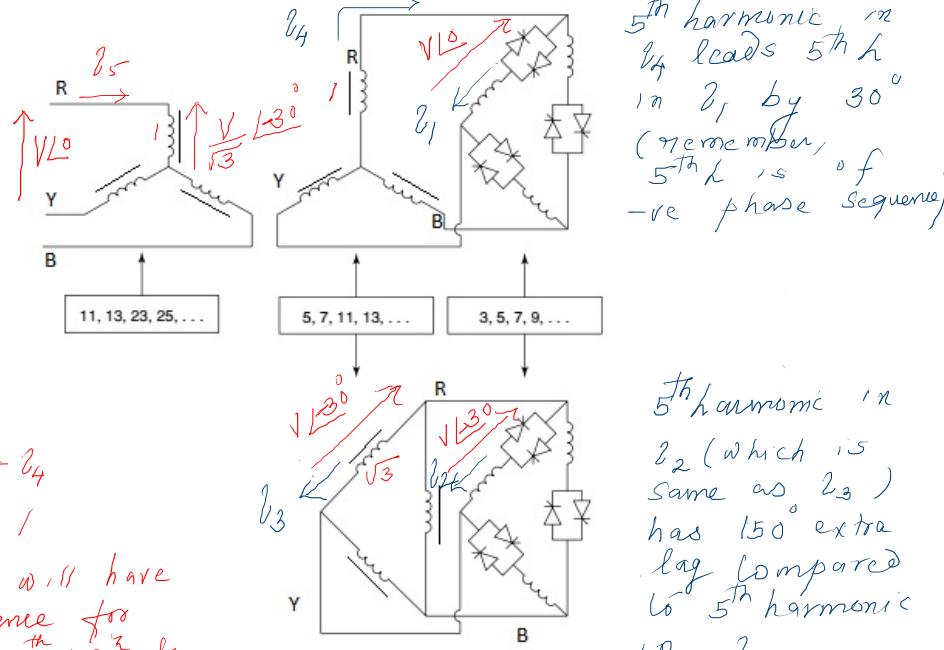
- Use TCR in 12-pulse arrangement  $6(2k-1) \pm 1$  with  $k=1, 2, 3, \dots$  order harmonic current amplitudes go to 0 in the primary - 5, 7, 17, 19, 29, 31, 41, 43, ... etc disappear 11, 13, 23, 25, ... etc present



# The Fixed Capacitor - Thyristor Controlled Reactor (FC-TCR)

## Static VAr Generator and Its Control
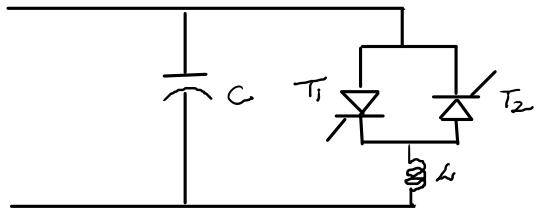
### Reactive Power Capability and Loss Behaviour of FC-TCR SVG



$$\text{Susceptance} = \frac{j}{\omega C} \quad \text{Susceptance} = -j B_L$$

$$j B_C = j \omega C \quad -j \frac{1}{\omega L} \left( 1 - \frac{2}{\pi} \alpha - \frac{1}{\pi} \sin 2\alpha \right)$$

$\frac{1}{\omega L}$  is usually  $> \omega C$  and hence when  $\alpha=0$  FC-TCR takes lagging reactive power of value  $V^2 \left( \frac{1}{\omega L} - \omega C \right)$  and when  $\alpha=90^\circ$ , it takes leading reactive power of  $V^2 (\omega C)$  where  $V$  is system voltage in pu.

Rating is based on nominal voltage and nominal voltage in pu is taken as 1 pu.

$$\text{So } Q_{L\max} = \left( \frac{1}{X_L} - \frac{1}{X_C} \right) \text{ where } X_L \text{ & } X_C \text{ are in pu}$$



and  $Q_{C\max} = \frac{1}{X_C} ; X_C \text{ in pu.}$

Rating of  $C, Q_{Cr} = Q_{C\max} \text{ pu}$

Rating of  $L, Q_{Lr} = (Q_{C\max} + Q_{L\max}) \text{ pu.}$

Reactive Capability curve at Nominal Voltage of 1 pu

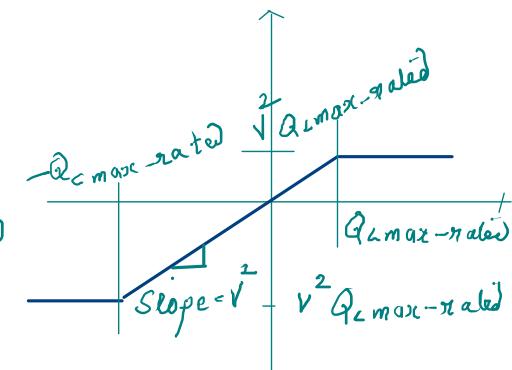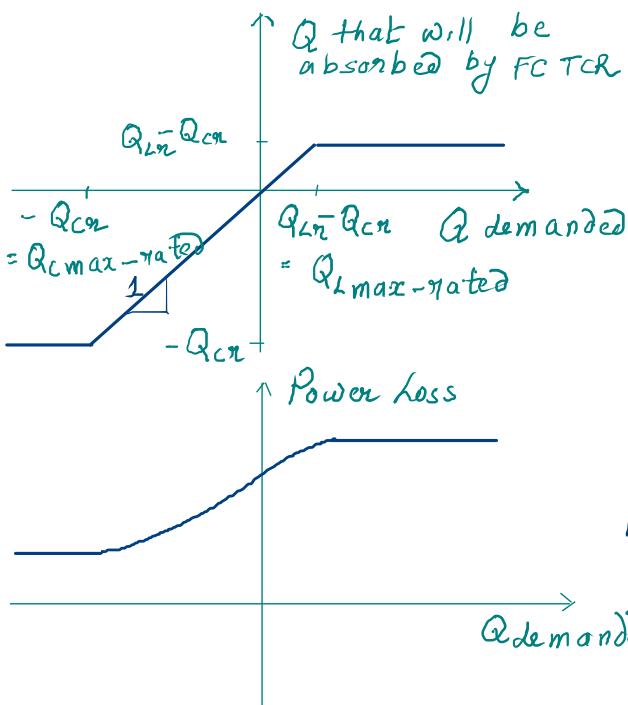Reactive Capability Curve at System Voltage  $V$  pu



$\therefore$  Suitable when average capacitive demand is high (as in PF Correction) and not suitable when it is low as in dynamic compensation in power transmission system.

# The Fixed Capacitor - Thyristor Controlled Reactor (FC-TCR)

## Static VAr Generator and Its Control

### Internal Control of FC-TCR SVG


A Single TCR unit is assumed.

Input - is the value of  $I_{LF}$  desired, represented by a suitable DC control voltage.

Assumption - Nominal voltage = 1 pu.

Let  $V_R$  (say 5V) be the voltage used to represent maximum lagging current possible from TCR (when  $\alpha=0$ ). It will be equal to rating of L in pu.

Strategy to get firing positions



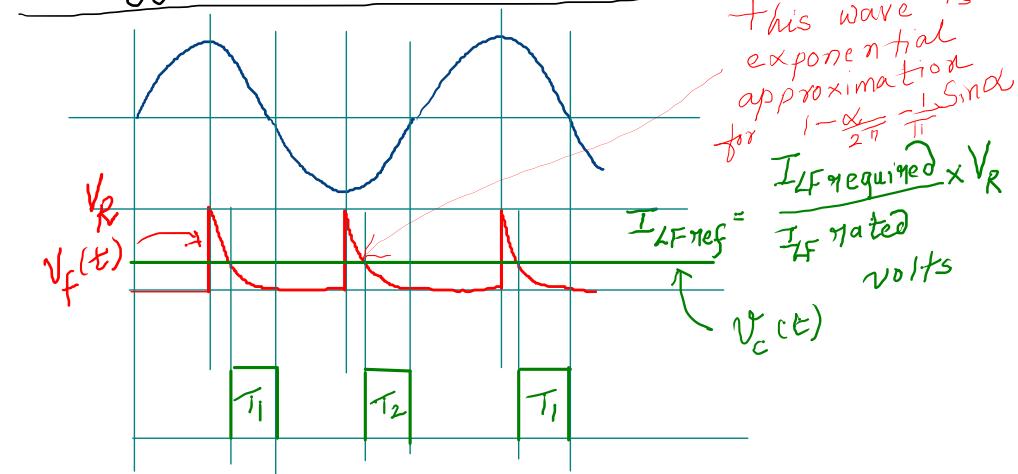


Problem - Where  $V \neq 1 \text{ pu}$ , actual  $I_{LF}$  realised will be  $V \times I_{LF}$  required

Solution - Make peak of  $v_f(t) \propto V$ .

But then  $v_f(t)$  has to be limited (i.e. saturated at  $V$ ) at slightly less than  $V \times V_R$  ( $V$  in pu,  $V_R$  is the voltage needed to represent rated current from TCR).

To generate  $v_f(t)$

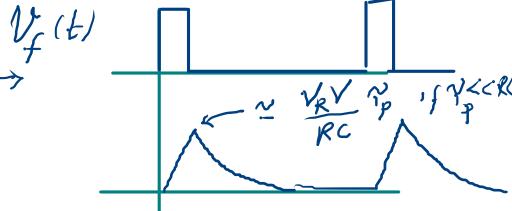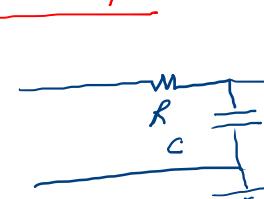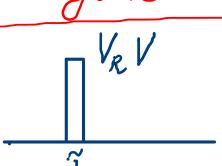

Take  $\tau_p = 0.1 \text{ ms}$  Then  $RC$  can be 1 ms.

Let  $V_R = 5 \text{ V}$ .

# The Fixed Capacitor - Thyristor Controlled Reactor (FC-TCR)

## Static VAr Generator and Its Control

