

Rectifiers

Classification of Rectifiers

1. Uncontrolled rectifiers

- **line frequency ac is converted into fixed voltage dc.**
(uses uncontrollable devices like diodes)
- **2. Fully controlled rectifiers**
line frequency ac is converted into variable voltage dc
(uses controllable devices like SCRs, IGBT)
- **3. Half controlled converters**
line frequency ac is converted into variable voltage dc
(uses both uncontrollable and controllable devices)

Uncontrolled and Halfcontrolled Converters

- average output voltage is always positive.
- Power flow is from ac source to dc load
- Unidirectional converters
- operating points lie in the first quadrant of $V_d - I_d$ Plane
- Single quadrant converters

Uncontrolled Rectifiers

APPLICATIONS

Switching power supplies

ac motor drives


dc motor drives

battery chargers

electrochemical processes

HVDC Transmission

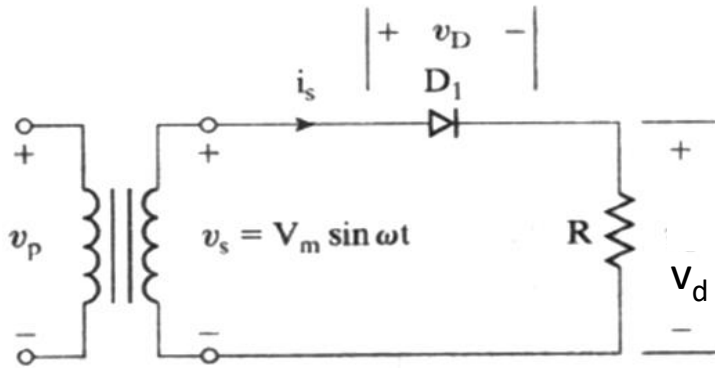Single phase Half wave rectifier - R load



$$V_s = V_m \sin \omega t = \sqrt{2} V_s \sin \omega t$$

V_s – RMS value of source voltage

0 - π D_1 conducts.

$$v_d(\omega t) = v_s(\omega t)$$

$$i_d(\omega t) = v_d(\omega t) / R = i_s(\omega t)$$

$$\text{Diode voltage } v_{D1}(\omega t) = 0$$





$\pi - 2\pi$ D_1 is off

$$i_d(\omega t) = 0,$$

$$V_d(\omega t) = 0$$

$$i_s(\omega t) = 0,$$

$$v_{D1}(\omega t) = v_s(\omega t)$$

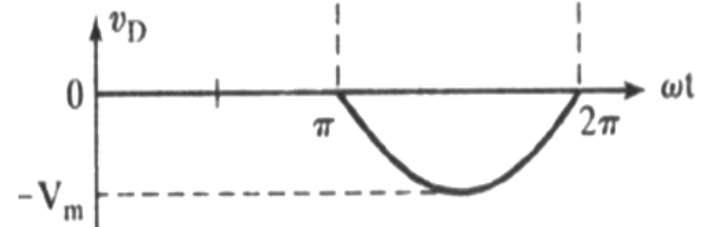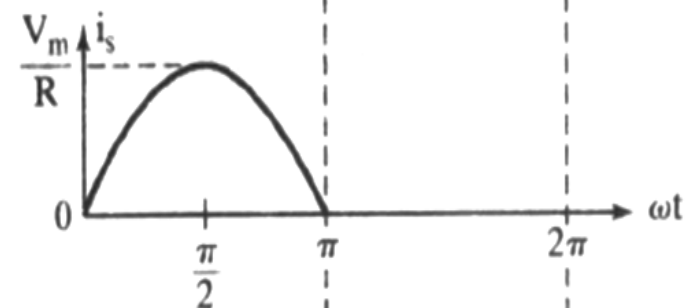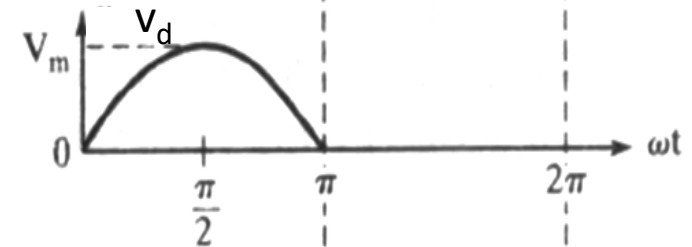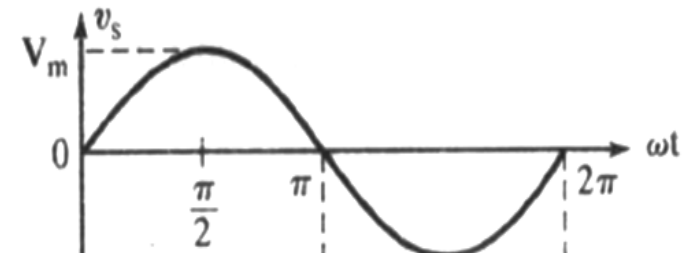

Performance parameters

- Average value of output voltage V_{davg}

$$\begin{aligned} V_{\text{davg}} &= \\ &= \frac{1}{2\pi} \int_0^{2\pi} v_d d\omega t = \\ &= \frac{1}{2\pi} \left[\int_0^{\pi} v_s d\omega t + \int_{\pi}^{2\pi} 0 d\omega t \right] \\ &= \frac{1}{2\pi} \int_0^{\pi} \sqrt{2} V_s \sin \omega t d\omega t = \frac{\sqrt{2} V_s}{\pi} = \frac{V_m}{\pi} \end{aligned}$$

- Average load current $I_{\text{davg}} = \frac{\sqrt{2} V_s}{\pi R}$ = Average current rating of diode

- Peak load current = $\frac{\sqrt{2} V_s}{R}$

- Peak current rating of diode = $\frac{\sqrt{2} V_s}{R}$

RMS load voltage V_{dRMS}

$$V_{dRMS} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (v_d)^2} = \frac{V_s}{\sqrt{2}}$$

RMS load current $I_{dRMS} = \frac{V_s}{\sqrt{2}R}$

Load current Form factor $= \frac{I_{dRMS}}{I_{davg}} = 1.57$

RMS source current $I_{sRMS} = \frac{V_s}{\sqrt{2}R}$

- DC power delivered to the load $P_{dc} = V_{davg} \times I_{davg}$

$$= \frac{\sqrt{2}V_s}{\pi} \times \frac{\sqrt{2}V_s}{\pi R}$$

Transformer Utility factor TUF

DC power delivered /Transformer power rating

If transformer RMS current rating is same as I_{drms} , then

$$\text{TUF} =$$

$$= P_{dc} / (V_s \times I_{dRMS}) = 29\%$$

Power rating of transformer must be greater by 1/.29 (=3.5) times the dc load power rating

Rectifier efficiency η

$$\begin{aligned} &= \text{dc side load power} / (\text{ac load power} + \text{rectifier loss}) \\ &= \frac{\text{dc side load power}}{\text{ac side power} + \text{rectifier loss}} = \\ &= \frac{I_{davg}^2 R}{I_{dRMS}^2 (R + R_f)} = \frac{40.6}{1 + \frac{R_f}{R}} = \end{aligned}$$

R_f ----forward resistance of diode

- Ripple factor γ

= RMS value of ripple content in load voltage / V_{davg}

$$\gamma = \frac{\sqrt{V_{dRMS}^2 - V_{davg}^2}}{V_{davg}} = 1.21$$


- **Input source pf** = $\frac{\text{source side actual power}}{\text{source side apparent power}}$

$$= \frac{P_{dc}}{\text{source side RMS voltage} \times \text{RMS current}}$$

$$= \frac{2V_s^2}{\pi^2 R_L} / V_s \frac{V_s}{\sqrt{2}R_L} = 0.286$$

- **Peak Inverse voltage PIV**
- **Maximum instantaneous voltage that appears across the diode during the blocking state**
- $= \sqrt{2}V_s$

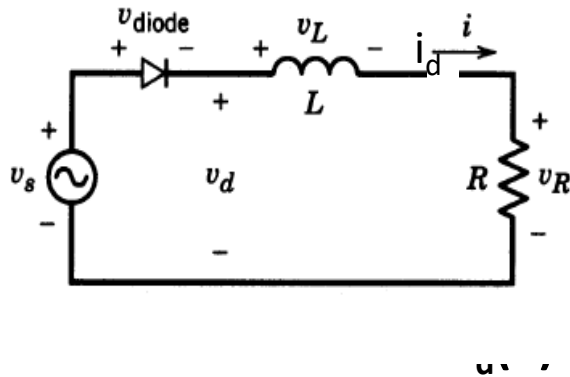Single Phase Half wave uncontrolled Rectifier with R-L Load



During positive half cycle diode is on

$$v_d = v_s = \sqrt{2}V_s \sin \omega t = Ri_d(t) + L \frac{di_d(t)}{dt}$$

$0, \quad (di_d/dt) /_{t=0} = 0$

$$i_d(t) = \frac{V_m}{Z} \sin \phi e^{-Rt/L} - \frac{V_m}{Z} \sin(\omega t - \phi) \quad Z = \sqrt{R^2 + (\omega L)^2}$$

$$\phi = \tan^{-1}(\omega L/R)$$

$$V_R(t) = i_d(t) \times R$$

$$V_L(t) = L (di_d/dt) = V_d(t) - V_R(t)$$

- During positive half cycle diode is on

$$V_d = V_s = Ri_d(t) + L \frac{d}{dt}(i_d(t))$$

$$V_m = \sqrt{2}V_s$$

$$\frac{V_m \sin \omega t}{s^2 + \omega^2} = RI_d(s) + L[sI_d(s)]$$

$$I_d(s) = \frac{V_m \omega}{(s^2 + \omega^2)^2 (R + Ls)}$$

$$I_d(s) = \frac{k_1}{(R + Ls)} + \frac{k_2}{(s + j\omega)} + \frac{k_3}{(s - j\omega)}$$

$$i_d(t) = \frac{V_m}{Z} \sin \phi e^{-Rt/L} - \frac{V_m}{Z} \sin(\omega t - \phi)$$

$$Z = \sqrt{R^2 + \omega^2 L^2}$$

$$\phi = \tan^{-1}(\omega L / R)$$

- 0- t_3

$$L \frac{d}{dt} (i_d(t)) = V_L$$

$$\int_0^{t_3} di_d(t) = \int_0^{t_3} \frac{V_L}{L} dt$$


$$i_d /_{t=0} = 0, \quad i_d /_{t=t_3} = 0$$

$$\int_0^{t_3} \frac{V_L}{L} dt = 0$$


$$\int_0^{t_1} \frac{V_L}{L} dt + \int_{t_1}^{t_3} \frac{V_L}{L} dt = 0$$

$$\int_0^{t_1} \frac{V_L}{L} dt = - \int_{t_1}^{t_3} \frac{V_L}{L} dt$$

- **Area A = Area B**

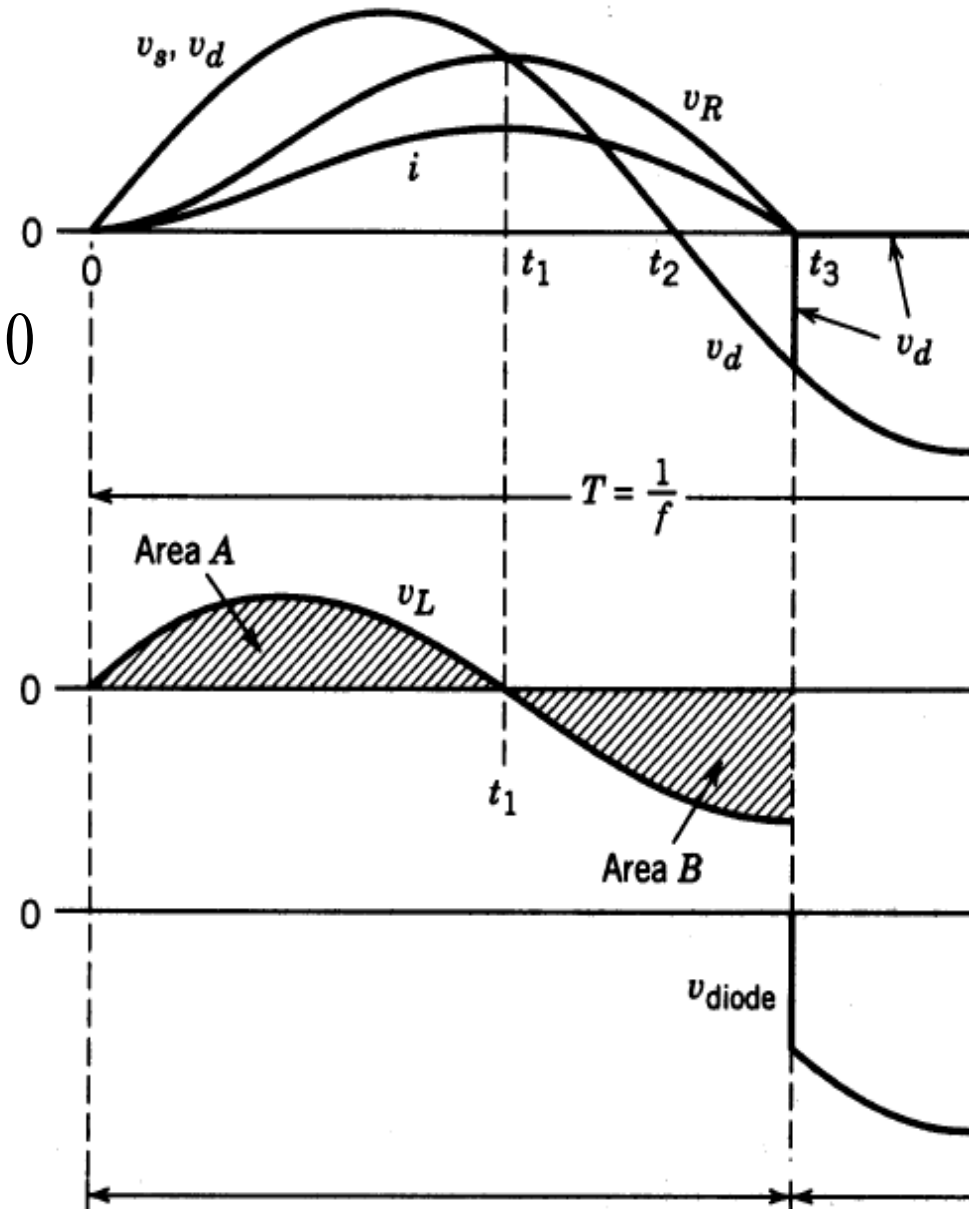

R-L load with free wheeling diode

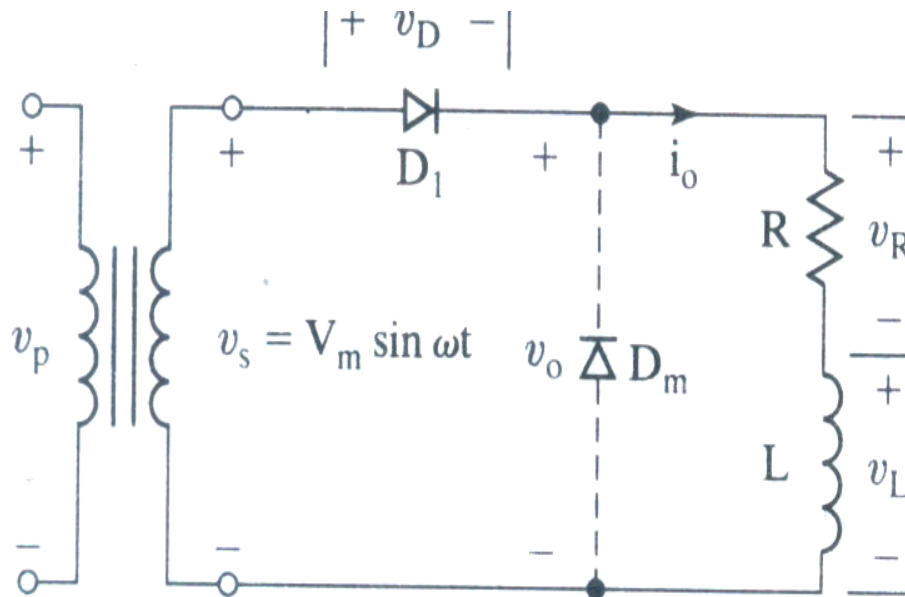

$V_s, i_o, v_R, v_L, v_{D1}, v_{dm}$

Average voltage (and current) can be increased by adding a freewheeling diode D_m .


The effect of this diode is to prevent a negative voltage appearing across the load.

At $t_1 = \pi/\omega$ the current from D_1 is transferred to D_m and this process is called commutation of diodes.

Continuity of the load current depends on its time constant $\tau = \omega L/R$.

L-E load

(dc motor with back emf)

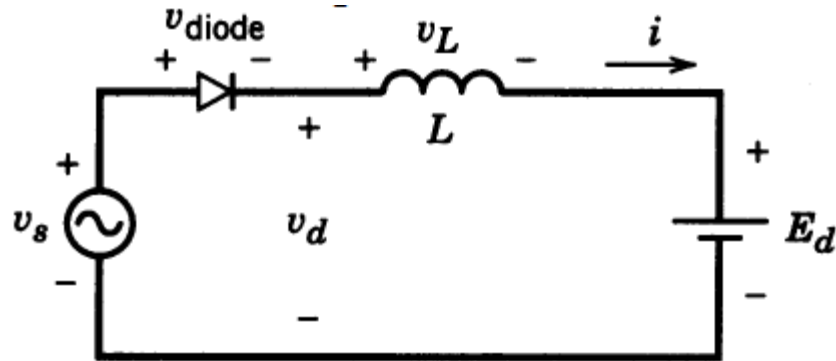

- Diode is forward biased when

$$V_s \geq E_d$$




$$\text{At } \omega t = \omega t_1 = \alpha; \quad v_s = E_d$$

$$\sqrt{2}V_s \sin \alpha = E_d \quad \alpha = \sin^{-1} \frac{E_d}{\sqrt{2}V_s}$$

For $\omega t \geq \omega t_1$, D_1 is on, $V_{\text{diode}} = 0$

$$\sqrt{2}V_s \sin \omega t = L \frac{di}{dt} + E_d$$

$$i(t) =$$

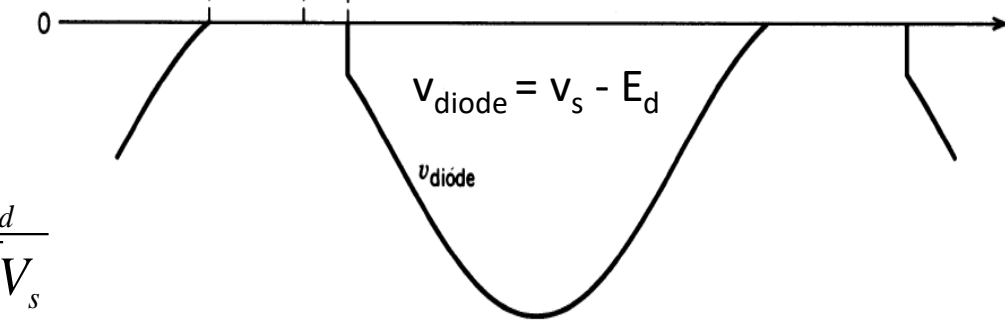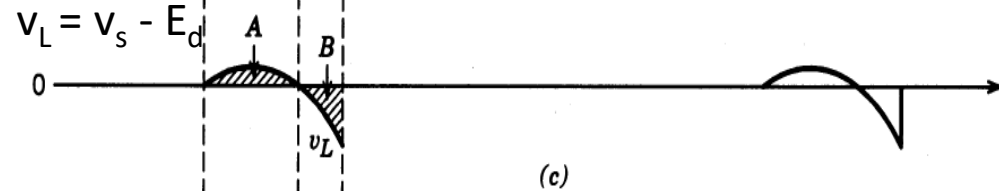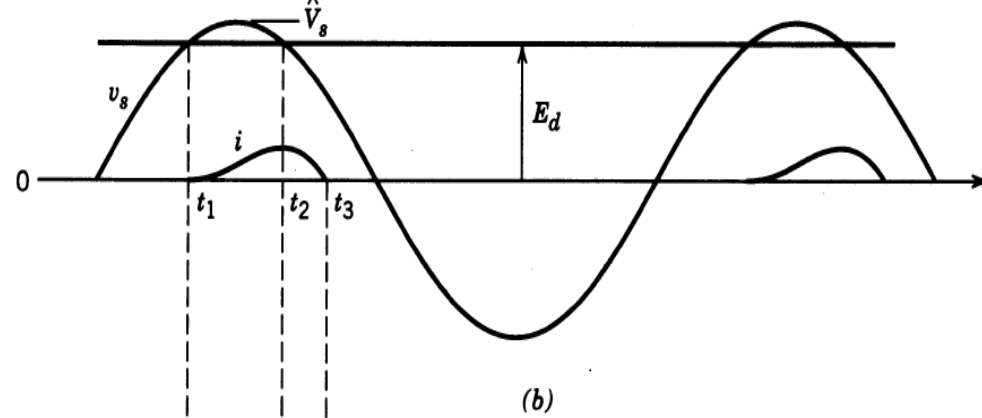


$$\text{At } \omega t = \alpha \quad i = 0$$

$$\sqrt{2}V_s \sin \alpha = L \frac{di}{dt} + E_d$$


$$\frac{di}{dt} \Big|_{\omega t = \alpha} = (\sqrt{2}V_s \sin \alpha - E_d) / L = 0$$

- Current continues to flow for a while even after the input voltage has gone below the dc back-emf

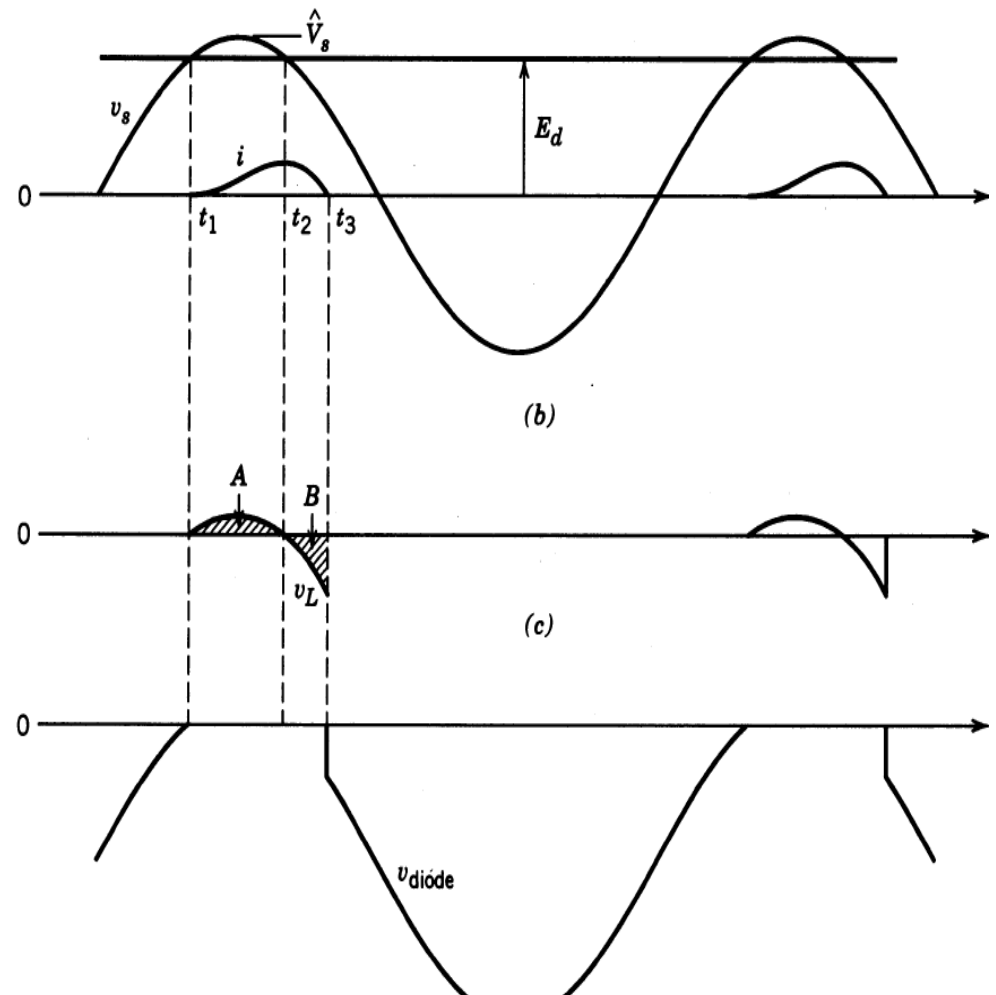- $\underline{t_3} \rightarrow 2\pi/\omega$
- $i = 0$
- $di/dt = 0, \quad v_L = 0$
- $V_{\text{diode}} = v_s - E_d$



Battery charging circuit

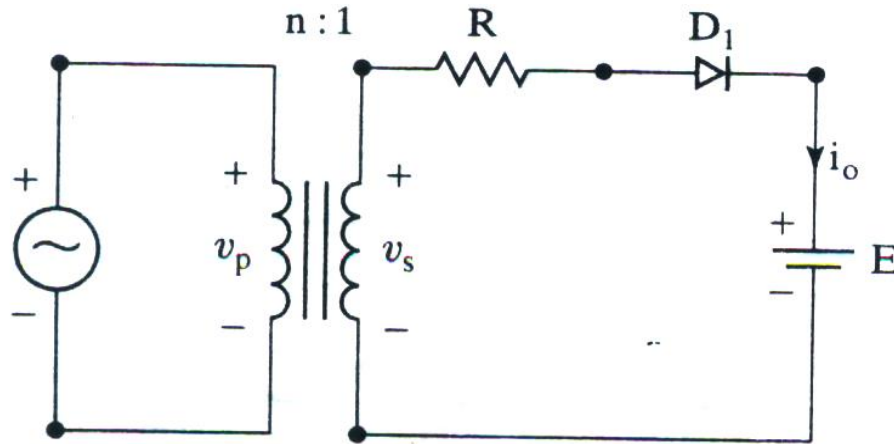


For $V_s > E$, diode $D1$ conducts.

$$\alpha = \sin^{-1} \frac{E}{V_m}$$

The charging current $i_o(t)$

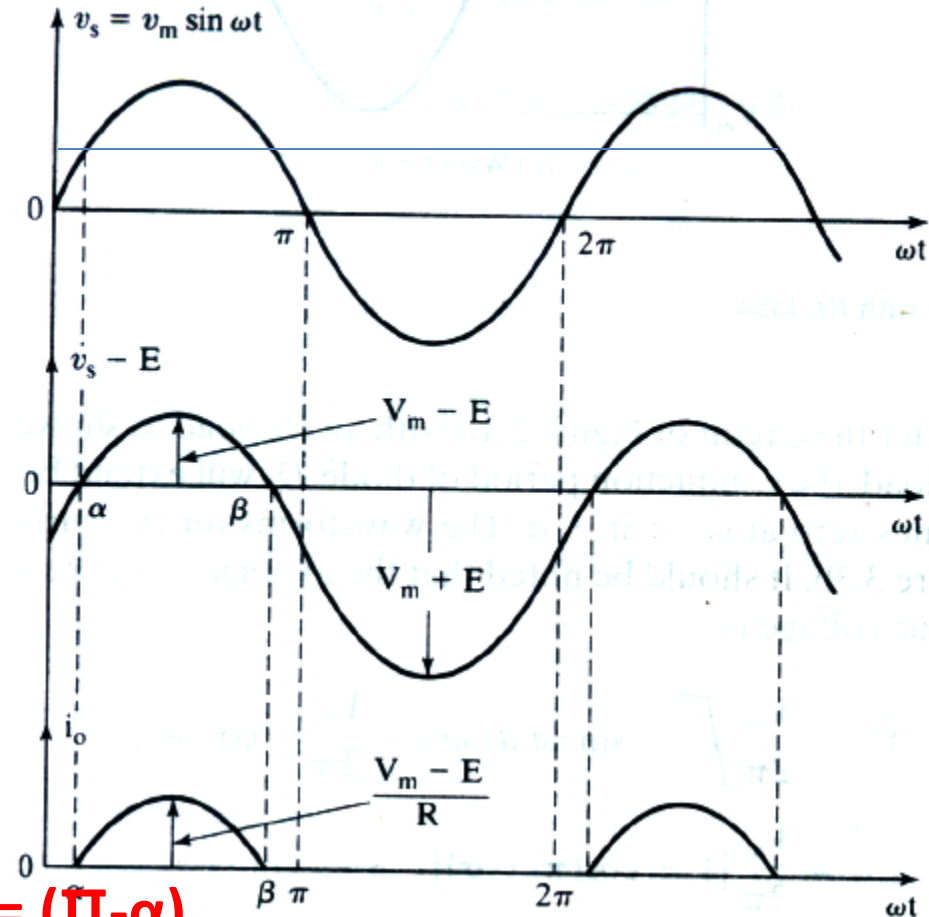D_1 is turned off when $i_o(t)=0$ at $\beta = (\pi - \alpha)$



$$i_o(t) = \frac{v_s - E}{R} = \frac{\sqrt{2}V_s \sin \omega t - E}{R} \quad \text{for } \alpha \leq \omega t \leq \beta$$

Performance parameters

- Average charging current I_{0avg}

$$I_{0avg} = \frac{1}{2\pi} \int_{\alpha}^{\pi-\alpha} \frac{\sqrt{2}V_s \sin \omega t - E}{R} d\omega t$$

$$= \frac{1}{2\pi R} (2V_m \cos \alpha + 2E\alpha - \pi E)$$


- Series connected resistance $R =$

$$R = \frac{1}{2\pi I_{0avg}} (2V_m \cos \alpha + 2E\alpha - \pi E)$$

RMS value of Charging current I_{ORMS}^2

$$I_{ORMS}^2 = \frac{1}{2\pi} \int_{\alpha}^{\pi-\alpha} \left(\frac{\sqrt{2}V_s \sin \omega t - E}{R} \right)^2 d\omega t$$
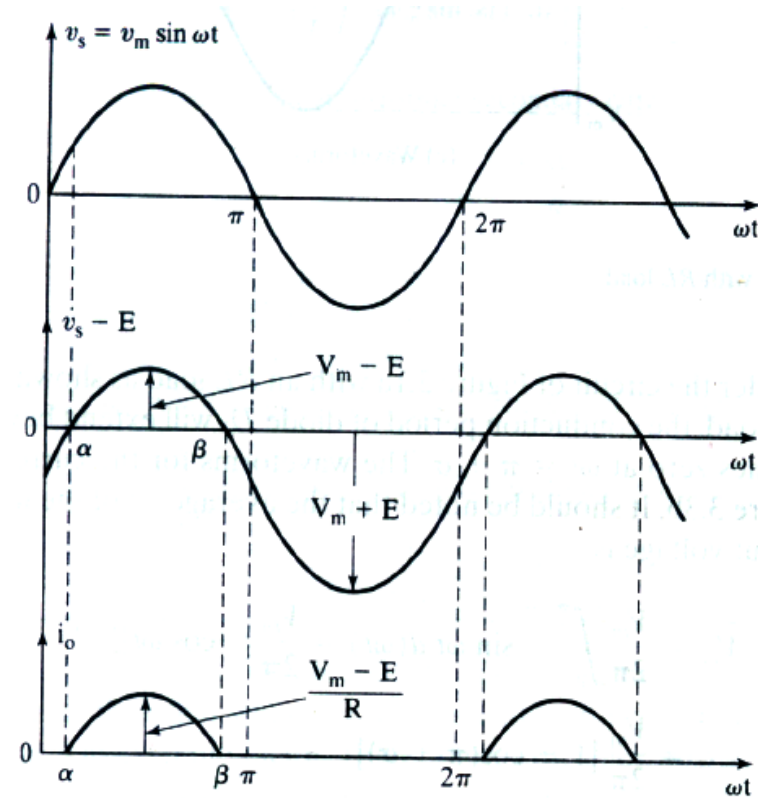
$$= \frac{1}{2\pi R^2} \left[\left(\frac{V_m^2}{2} + E^2 \right) (\pi - 2\alpha) + \frac{V_m^2}{2} \sin 2\alpha - 4V_m E \cos \alpha \right]$$




- Power delivered to the battery

$$P_{dc} = E \times I_{0avg}$$

- Power rating of resistance R,

$$P_R = I_{ORMS}^2 \times R$$

- Rectifier efficiency =

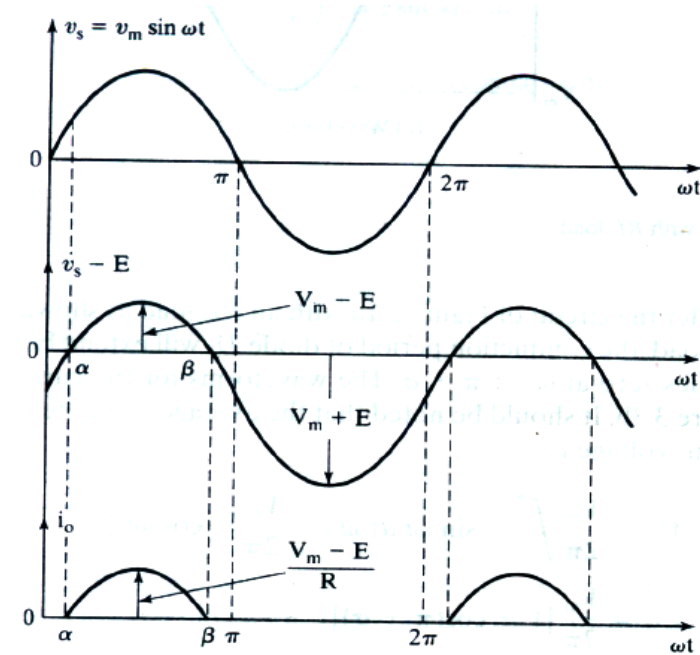

Power delivered to battery / total input power

$$\eta = \frac{P_{dc}}{P_{dc} + P_R}$$

- Peak inverse voltage of diode= $PIV = V_m + E$

- A battery has a voltage of $E=12V$ and capacity $100Wh$. The average charging current should be $I_{dc}=5A$. The primary input voltage is $V_p=120V$, $50Hz$ and the transformer has a turns ratio of $2:1$.

Calculate

- (a) conduction angle δ of the diode.
- (b) current limiting resistor R
- (c) power rating P_R of R
- (d) charging time
- (e) the rectifier η and (f) PIV of diode

- Secondary voltage =
- $\alpha =$
- Conduction angle $\delta =$
- Average charging current = $I_{dc} =$
- $R =$

Power rating of resistor =

$$I_{oRMS}^2 R =$$


Power delivered to the battery =

$$E I_{dc} =$$

$$\eta =$$



$$PIV =$$

Single phase Fullwave Bridge rectifiers

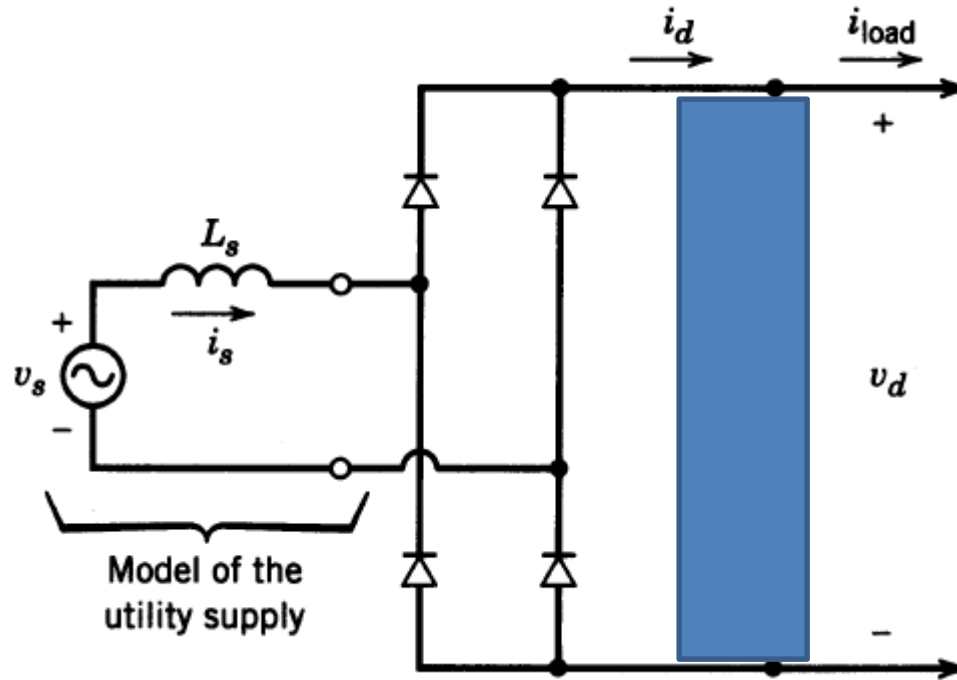


$$v_s = \sqrt{2}V_s \sin \omega t$$

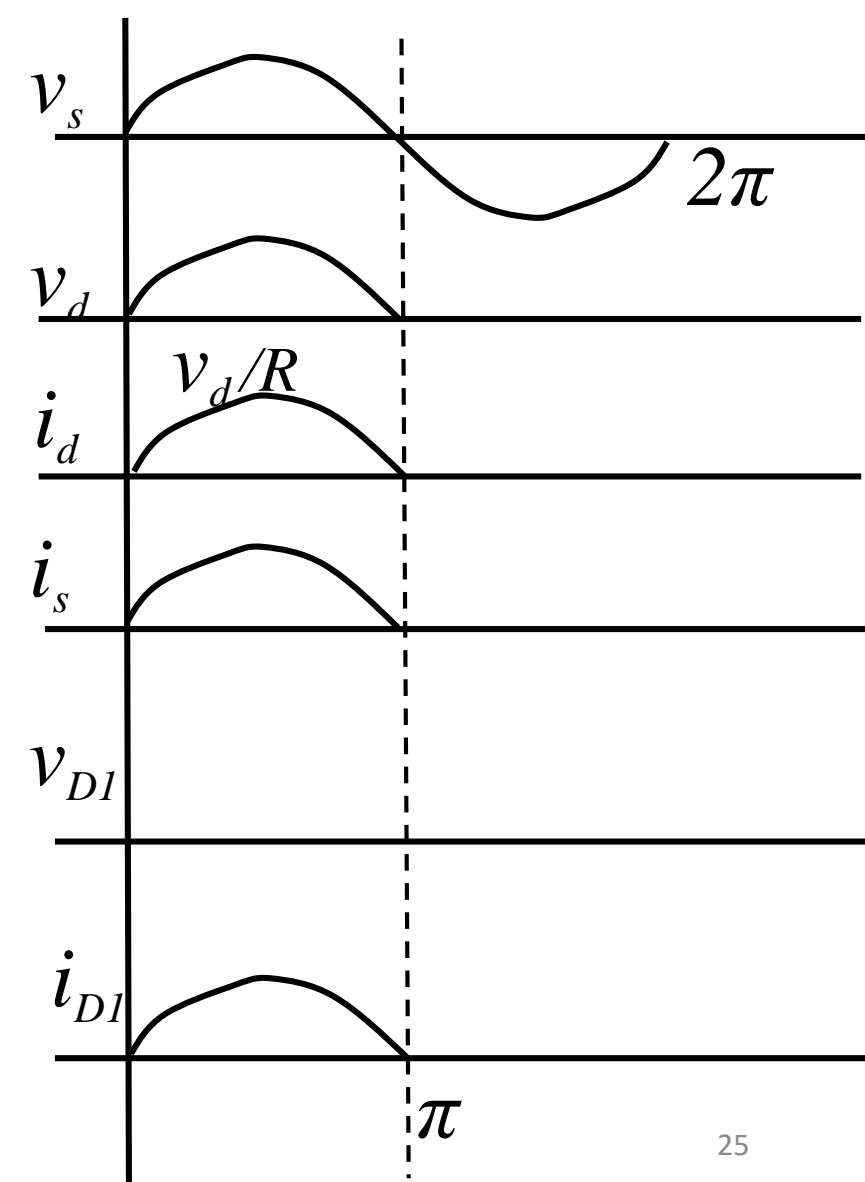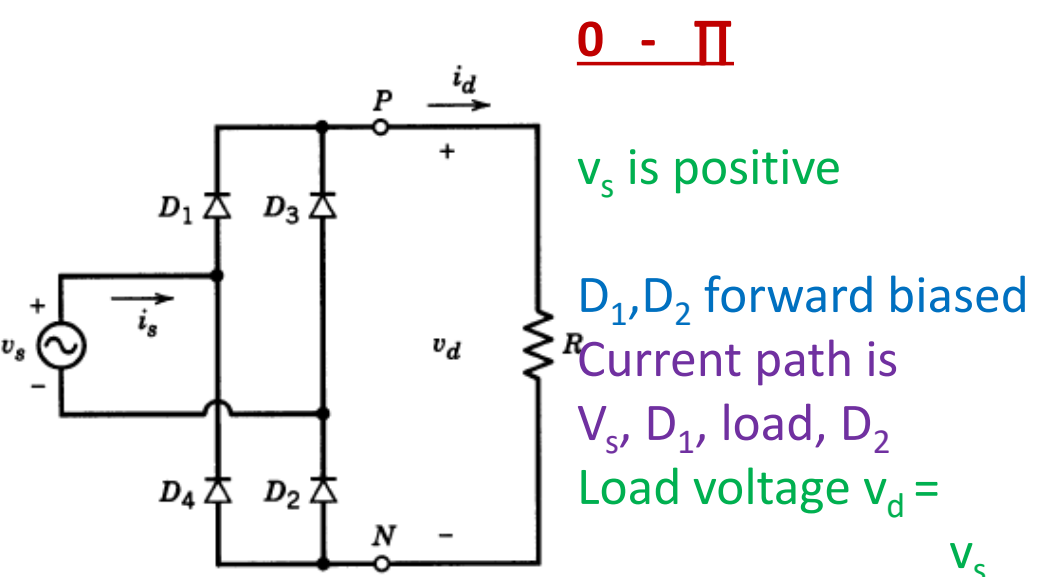Source inductance $L_s = 0$, Load is pure resistance



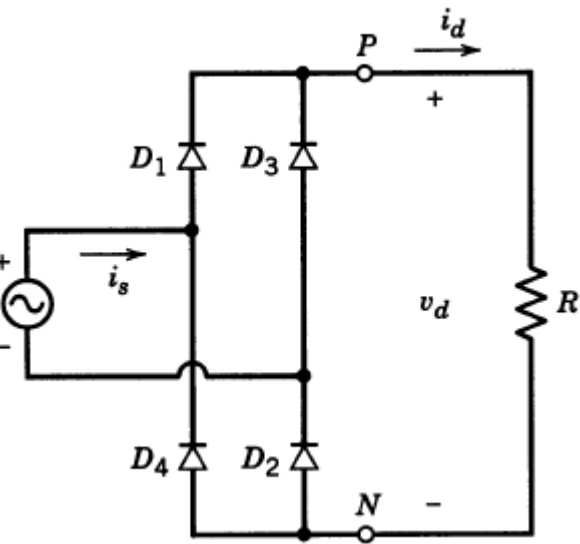Source inductance $L_s = 0$, Load is pure resistance



$\Pi - 2\Pi$


V_s is negative

D_3, D_4 forward biased
Current path is
 $v_s, D_3, \text{load}, D_4$

$$V_d = -V_s$$

$$i_d = v_d / R$$

$$i_s = -i_d$$

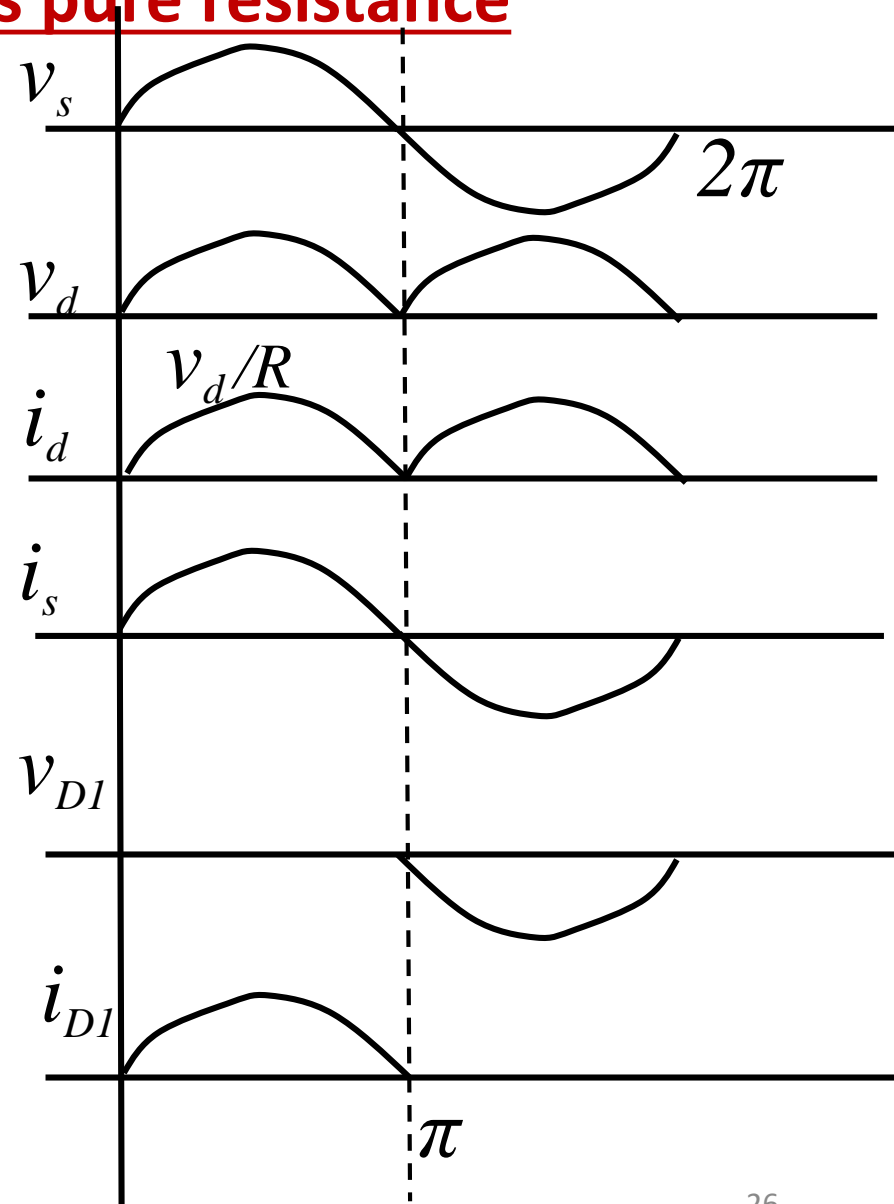

Performance parameters

- Average load voltage V_{davg}

$$V_{davg} = \frac{1}{\pi} \int_0^{\pi} (\sqrt{2}v_s \sin \omega t) d\omega t = \frac{2\sqrt{2}V_s}{\pi}$$

- Average load current I_{davg}

$$I_{davg} = \frac{2\sqrt{2}V_s}{\pi R}$$

- RMS load voltage V_{dRMS}

$$V_{dRMS} = \left[\frac{1}{\pi} \int_0^{\pi} (\sqrt{2}v_s \sin \omega t)^2 d\omega t \right]^{1/2} = V_s$$

- RMS load current $I_{dRMS} = V_s/R$

- **Peak load current** $= \frac{\sqrt{2}V_s}{R}$

- **DC power developed in load**


$$P_{dc} = V_{davg} \times I_{davg} = \frac{2\sqrt{2}V_s}{\pi} \times \frac{2\sqrt{2}V_s}{\pi R} = \frac{0.8113V_s^2}{R}$$

- **Transformer utility factor** $\frac{P_{dc}}{V_{dRMS} \times I_{dRMS}} = 81.13\%$

- **PIV** $= \sqrt{2}V_s$

- **Ripple factor** $= \sqrt{\frac{V_{dRMS}^2 - V_{davg}^2}{V_{davg}^2}} = 0.482$

Source inductance $L_s = 0$, Load is R-L

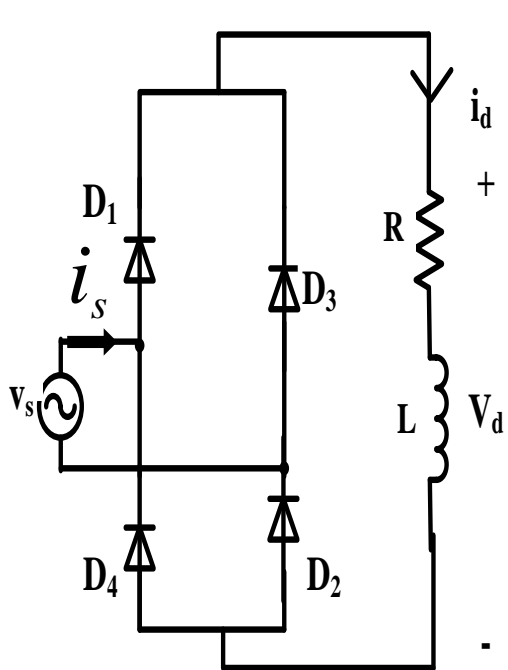

- 0 - π
- v_s is positive,
- D_1, D_2 forward biased
- $v_d = v_s$,


$$Ri_d(\omega t) + L \frac{di_d(\omega t)}{d\omega t} = \sqrt{2}V_s \sin \omega t$$

$$i_d(\omega t) /_{t=0} = + I_o$$


$$\frac{di_d(\omega t)}{dt} /_{\omega t=0} \text{ is } \frac{R I_o}{L}$$

$$i_d(\omega t) =$$

$$i_c(\omega t) = i_d(\omega t)$$

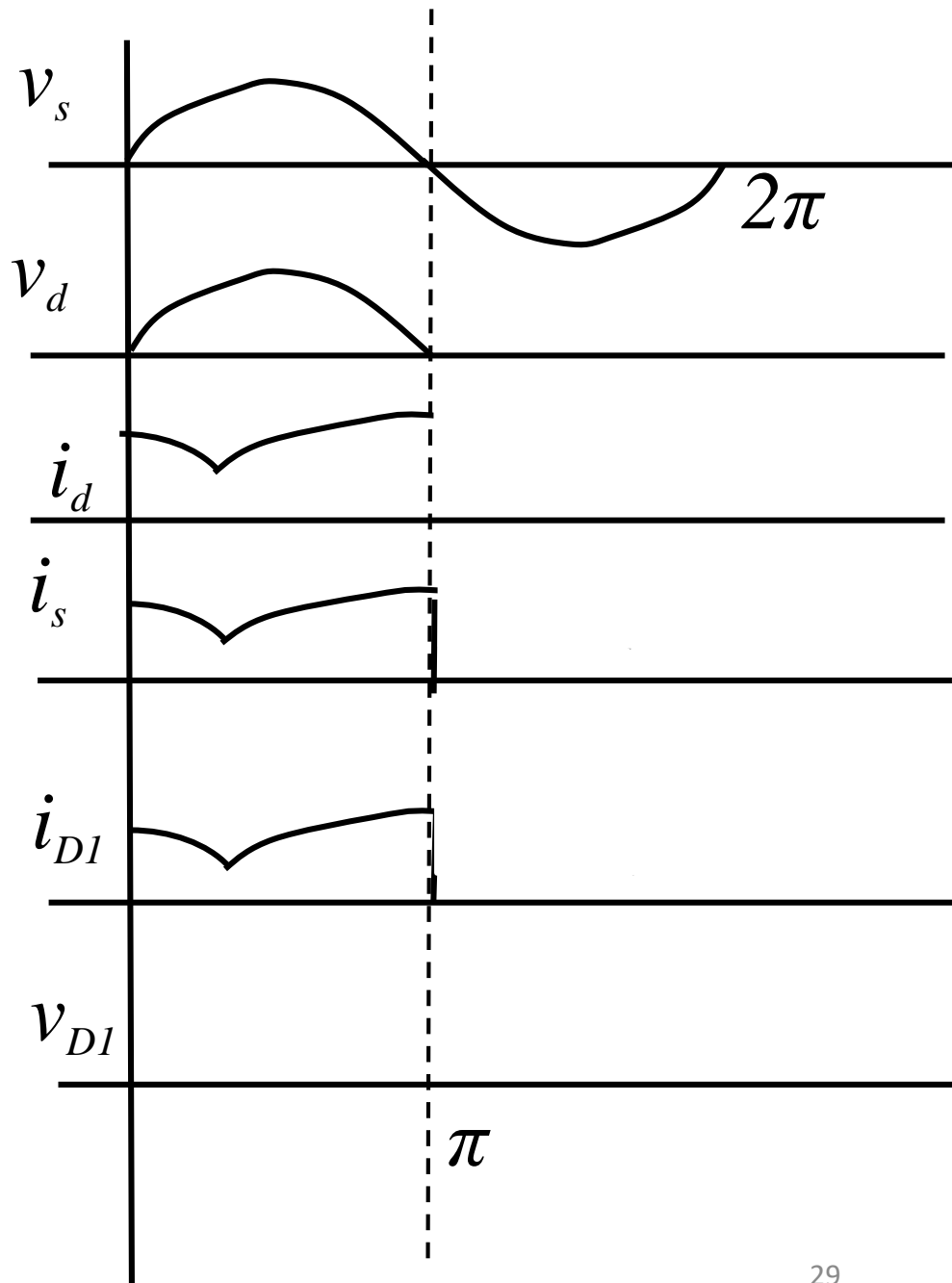

Source inductance $L_s = 0$, Load is R-L

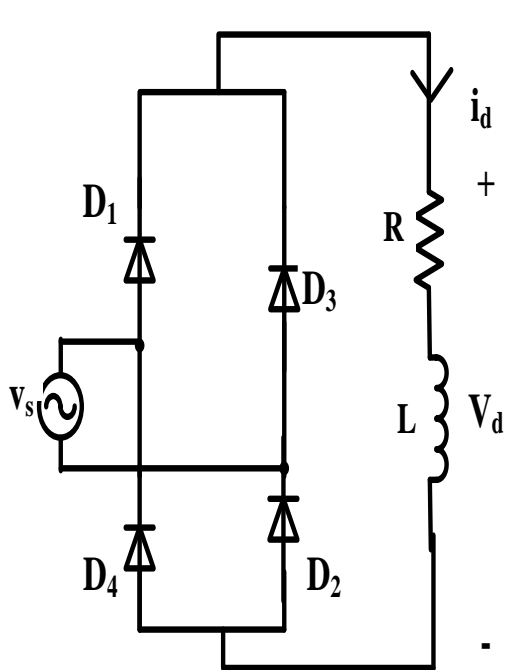

- $\pi - 2\pi$
- v_s is negative,
- D_3, D_4 forward biased
- $v_d = -v_s$


$$Ri_d(\omega t) + L \frac{di_d(\omega t)}{d\omega t} = \sqrt{2}V_s \sin \omega t$$

$$i_d(\omega t) /_{\omega t = \pi} = + I_0$$

$$\frac{di_d(\omega t)}{dt} /_{\omega t = \pi} \text{ is } \frac{-RI_0}{L}$$


$$i_d(\omega t) =$$

$$i_c(\omega t) = -i_d(\omega t)$$

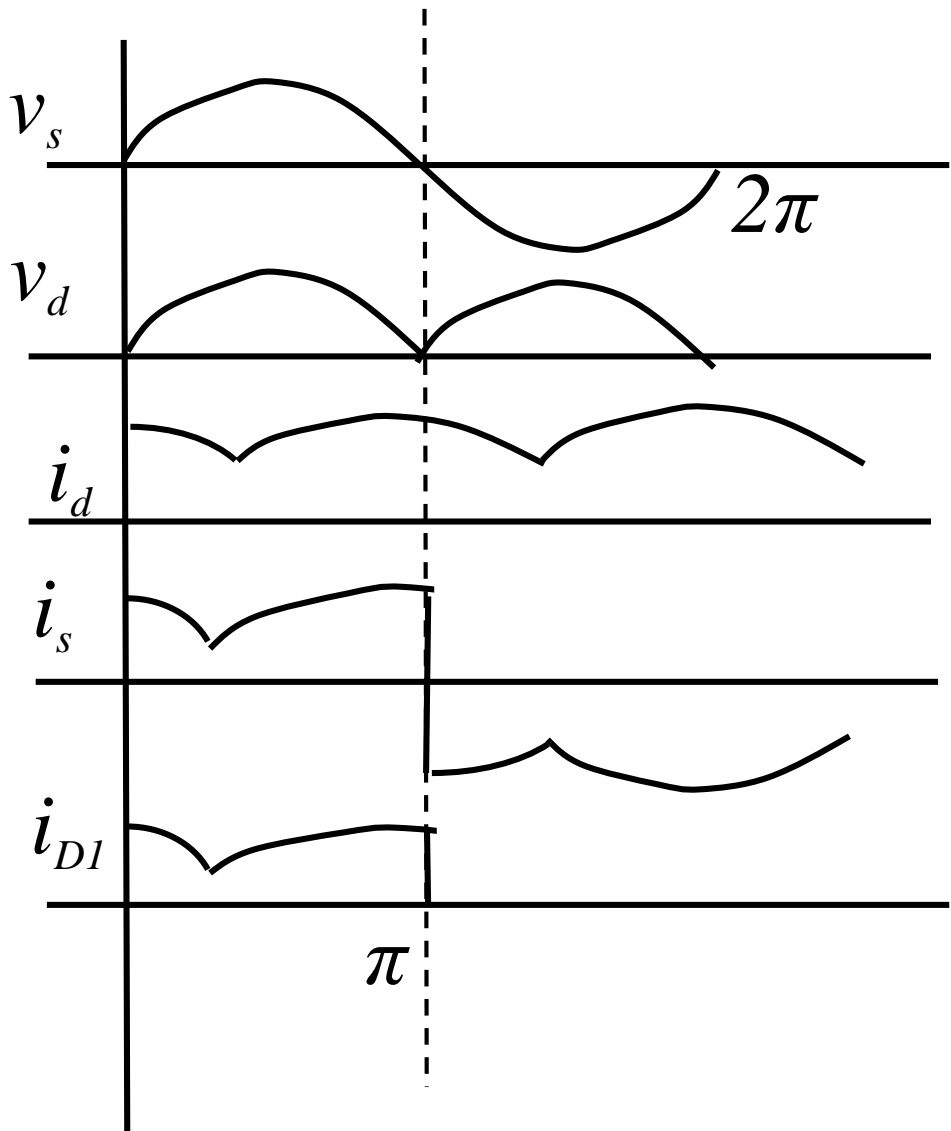

$L_s = 0$, Load is highly inductive so that i_d is constant at I_d

$$\omega L \gg R$$

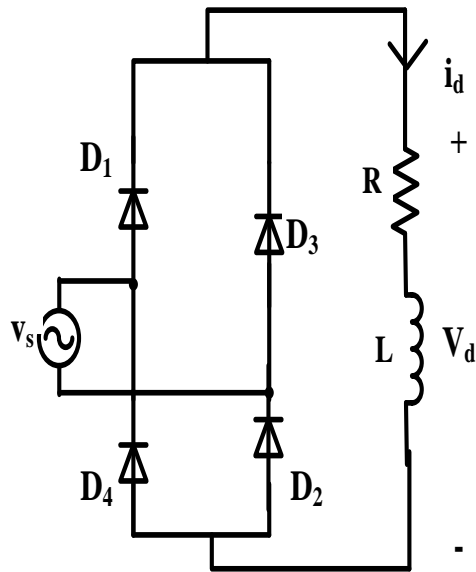

0 - π


v_s is positive

D_1, D_2
forward
biased

$$V_d = V_s$$


$$i_d = I_d$$

$$i_s = +I_d$$

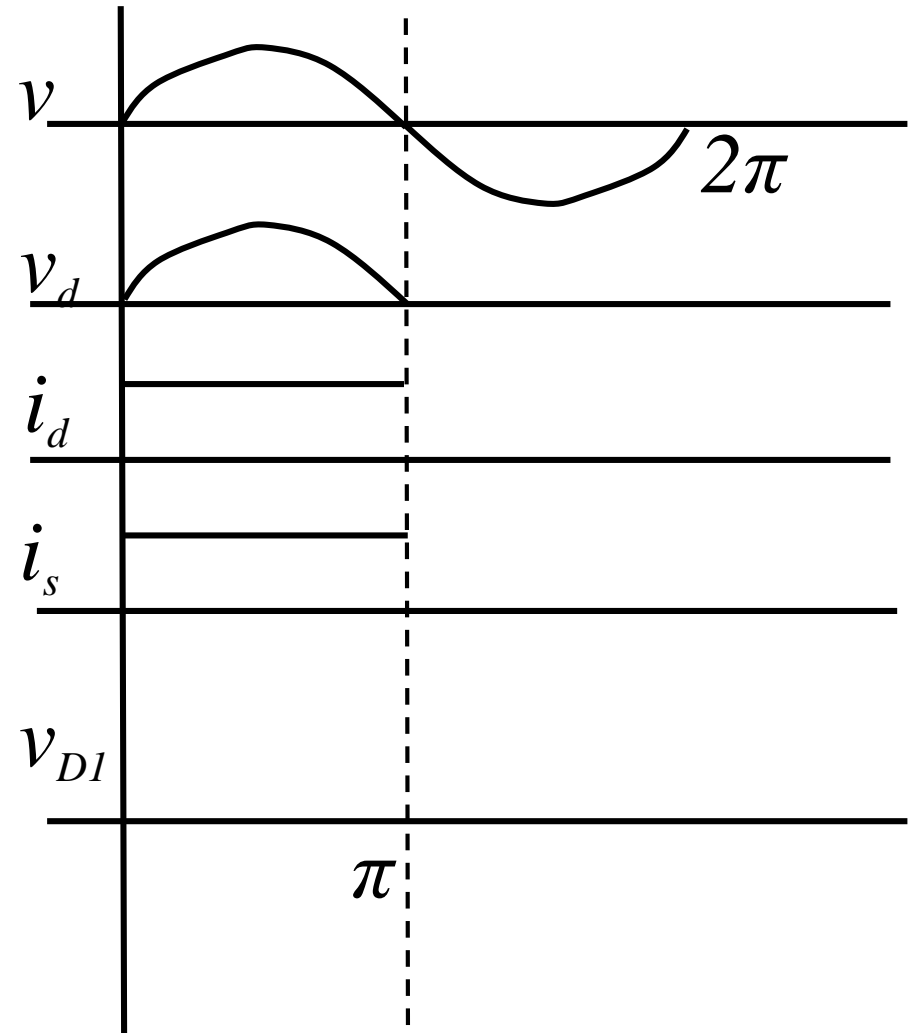

$L_s = 0$, Load is highly inductive so that i_d is constant at I_d

• $\omega L \gg R$

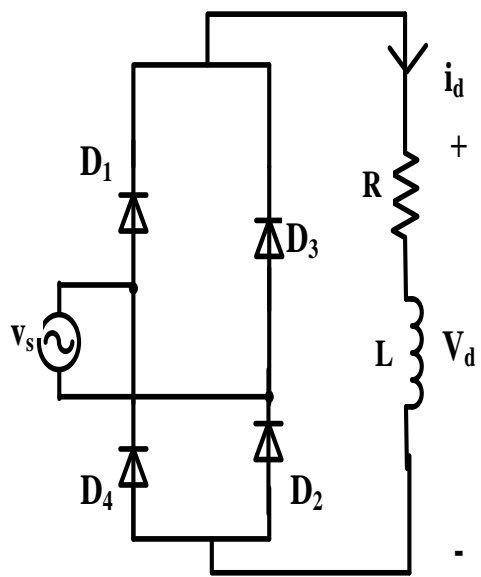

$V_d = -V_s$


$I_d = I_d$

$i_s = -I_d$

$\pi - 2\pi$

v_s is negative
 D_3, D_4 forward
 biased


Average output
 voltage

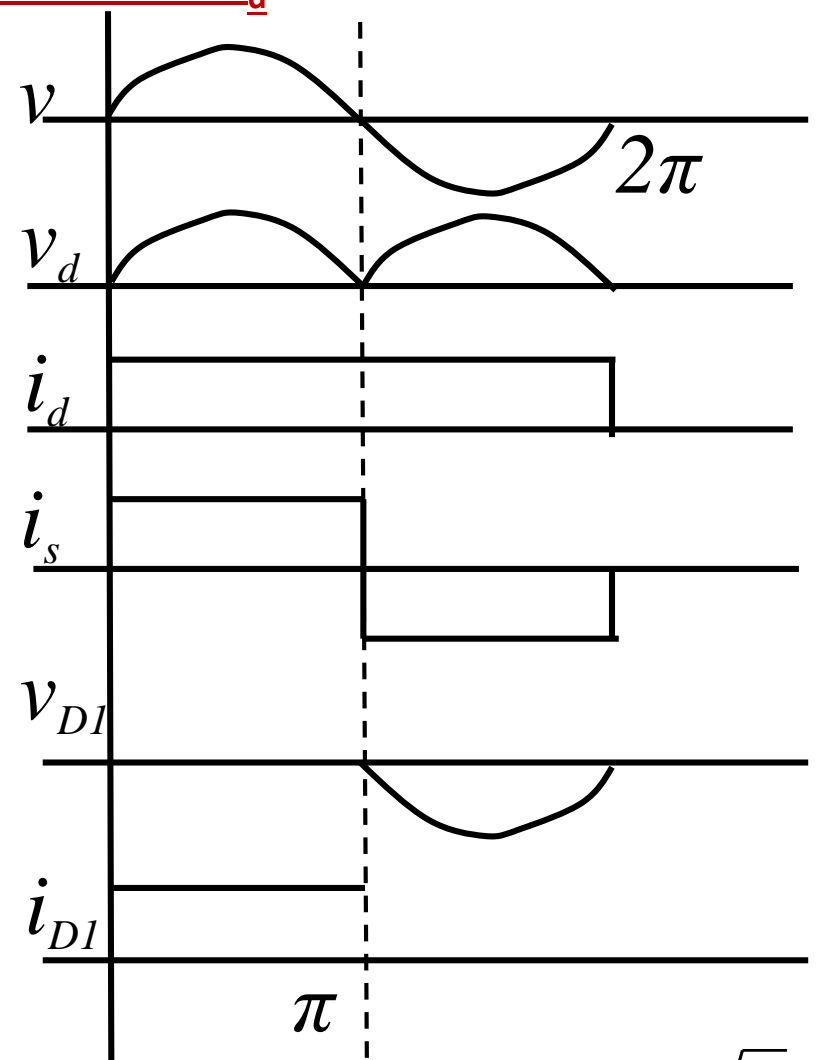

$$V_{davg} = \frac{1}{\pi} \int_0^{\pi} (\sqrt{2}v_s \sin \omega t) d\omega t = \frac{2\sqrt{2}V_s}{\pi}$$

$= 0.9V_s$ 32

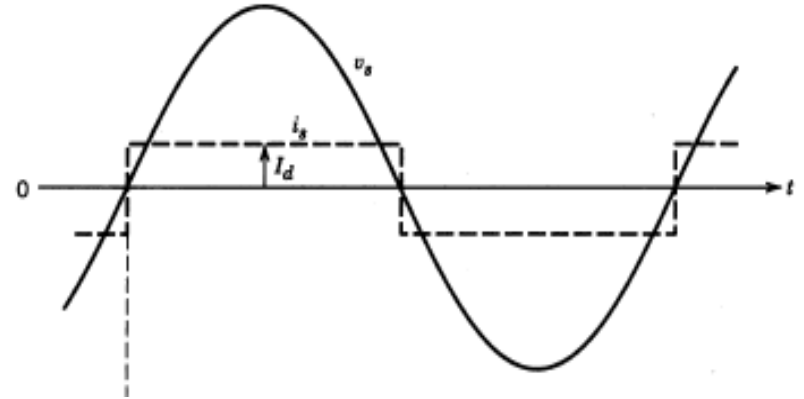Source inductance is zero. Hence transition from positive to negative value of source current is instantaneous.



$$i_s(t) = I_{dc} + \sum_{n=1}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t$$

$$I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i_s(t) d\omega t = \mathbf{0}$$


$$a_n = \frac{1}{\pi} \int_0^{2\pi} i_s(t) \cos(n\omega t) d\omega t = \mathbf{0}$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} i_s(t) \sin(n\omega t) d\omega t = \frac{2I_d}{n\pi} [1 - \cos n\pi] = \frac{4I_d}{n\pi} \text{ for } n = 1, 3, 5, 7..$$

$$= \mathbf{0} \text{ for } n = 2, 4, 6, 8..$$

$$\phi_n = \tan^{-1} a_n / b_n = 0$$
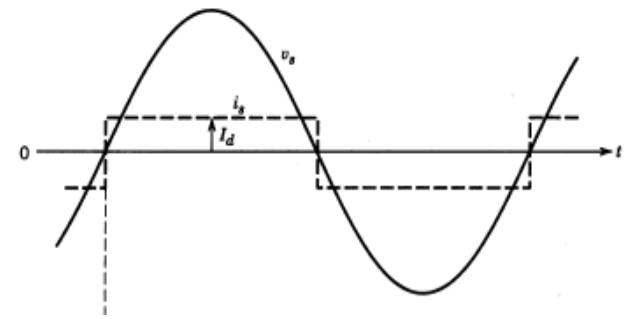
$$i_s(t) = \sum_{n=1}^{\infty} \frac{4I_d}{n\pi} \sin n\omega t \quad n = 1, 3, 5, \dots$$



$$i_s(t) = \frac{4I_d}{\pi} \left(\frac{\sin \omega t}{1} + \frac{\sin 3\omega t}{3} + \frac{\sin 5\omega t}{5} + \dots \right)$$

$$i_{s1}(t) = \frac{4I_d}{\pi} \sin \omega t$$

$$i_{s5}(t) = \frac{4I_d}{5\pi} \sin 5\omega t$$

$$i_{s3}(t) = \frac{4I_d}{3\pi} \sin 3\omega t$$

RMS value of fundamental component of input current I_{s1}

$$I_{s1} = \frac{4I_d}{\pi\sqrt{2}} = 0.9I_d$$

- **RMS value of nth harmonic of source current i_{sn}**


$$I_{sn} = \begin{cases} 0 & \text{for even values of } n \\ \frac{I_{s1}}{n} & \text{for odd values of } n \end{cases}$$

RMS value of total source current $I_s = I_d$


THD of source current $= \sqrt{\frac{(I_d^2 - I_{s1}^2)}{I_{s1}^2}} = 48.4\%$

- Displacement factor of source current $DF = \cos\phi_1 = 1$

Harmonic components of Source Current

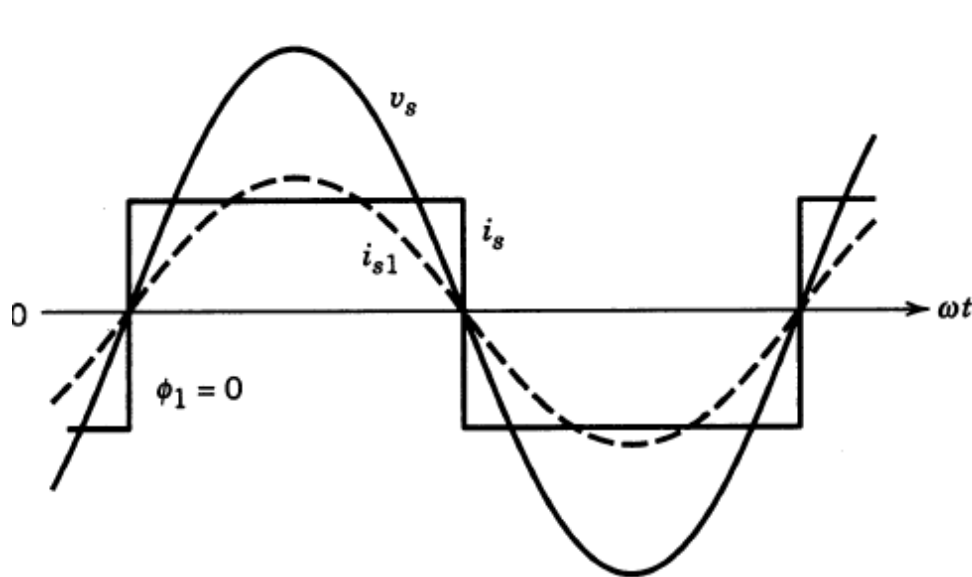

Source current and fundamental component

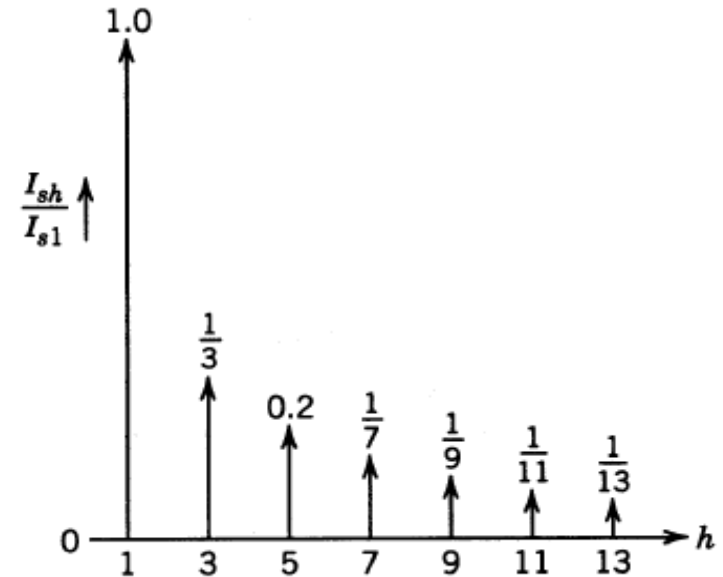

Harmonic components of I_s

AC source side Power factor = Actual power / Apparent power

$$\begin{aligned}
 \text{Actual power} &= \frac{1}{2\pi} \int_0^{2\pi} v_s i_s = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega_1 t [i_{s1} + i_{s3} + i_{s5} + \dots] \\
 &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega_1 t) I_{s1 \text{ peak}} \sin(\omega_1 t - \phi_1) \\
 &\quad + \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega_1 t) I_{s3 \text{ peak}} \sin(3\omega_1 t - \phi_3) \\
 &\quad + \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega_1 t) I_{s5 \text{ peak}} \sin(5\omega_1 t - \phi_5) \\
 &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega_1 t \left[\begin{aligned} &I_{s1 \text{ peak}} \sin(\omega_1 t - \phi_1) + \\ &I_{s3 \text{ peak}} \sin(3\omega_1 t - \phi_3) \\ &+ I_{s5 \text{ peak}} \sin(5\omega_1 t - \phi_5) + \dots \end{aligned} \right] \\
 &= \frac{V_m}{\sqrt{2}} \frac{I_{m1}}{\sqrt{2}} \cos \phi_1 = V_s I_{s1} \cos \phi_1
 \end{aligned}$$

Apparent power = $V_s I_s$

Power Factor =

$$\frac{V_s I_{s1} \cos \phi_1}{V_s I_s}$$

$$= I_{s1} / I_s = \frac{2\sqrt{2}I_d}{\pi I_d}$$

Peak current rating of diode =

$$= I_d$$


RMS current rating of diode =

$$= I_d / \sqrt{2}$$


PIV of diode =

$$V_m$$

Effect of source inductance L_s

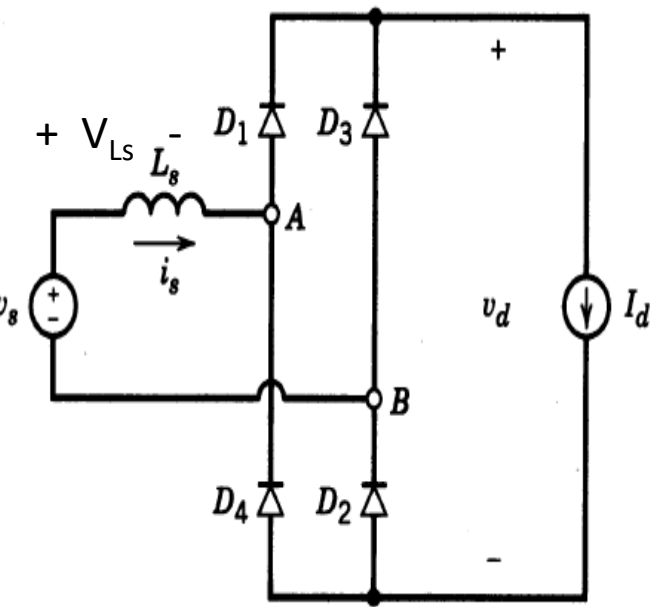

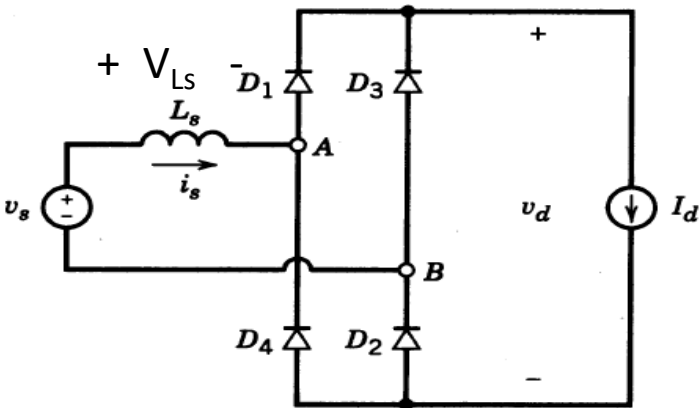- Due to source inductance the transition of ac side current from $+I_d$ to $-I_d$ is not instantaneous
- A finite time interval is required for the transition of current from outgoing diodes to incoming diodes.
- This time interval is called current commutation period μ .



- During the commutation
- interval μ , all four diodes conduct.

$$V_d = 0$$

Drop in the inductance V_{Ls}


$$V_{LS} = +V_s$$

$$L_s \frac{di_s(t)}{dt} = \sqrt{2}V_s \sin \omega t$$

$$\omega L_s \frac{di_s(t)}{d\omega t} = \sqrt{2}V_s \sin \omega t$$

$$di_s =$$
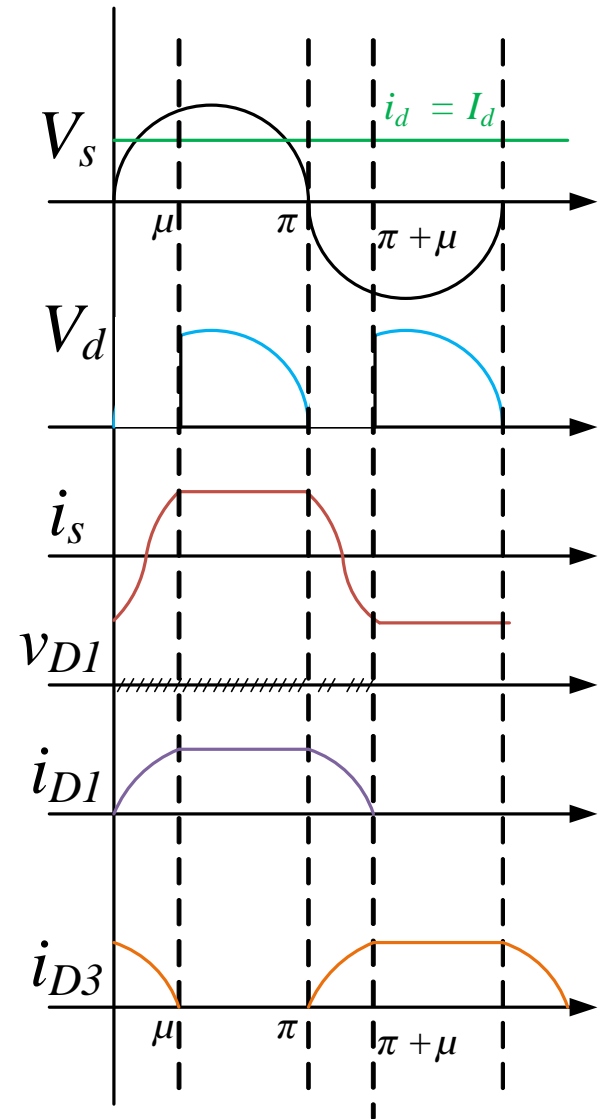
$$\frac{\sqrt{2}V_s}{\omega L_s} \sin \omega t \quad d(\omega t) = di_s$$



$$\frac{\sqrt{2}V_s}{\omega L_s} \sin \omega t \quad d(\omega t) = di_s$$

During 0 to μ i_s varies
from $-I_d$ to $+I_d$

$$\int_0^{\mu} \frac{\sqrt{2}V_s}{\omega L_s} \sin \omega t \quad d\omega t = \int_{-I_d}^{+I_d} di_s$$

$$\left| i_s \right|_{-I_d}^{+I_d} = \frac{\sqrt{2}V_s}{\omega L_s} [1 - \cos(\omega t)]$$

$$2I_d = \frac{\sqrt{2}V_s}{\omega L_s} (1 - \cos(\mu))$$

$$\cos \mu = 1 - \frac{\sqrt{2}\omega L_s I_d}{V_s}$$

commutation interval $\mu =$


- Average voltage $V_{davg} =$

$$V_{davg} = \frac{1}{\pi} \int_{\mu}^{\pi} \sqrt{2} V_s \sin \omega t d(\omega t)$$

$$= \frac{\sqrt{2} V_s}{\pi} (1 + \cos \mu)$$

$$= \frac{2\sqrt{2} V_s}{\pi} - \left\{ \frac{2\omega L_s I_d}{\pi} \right\}$$


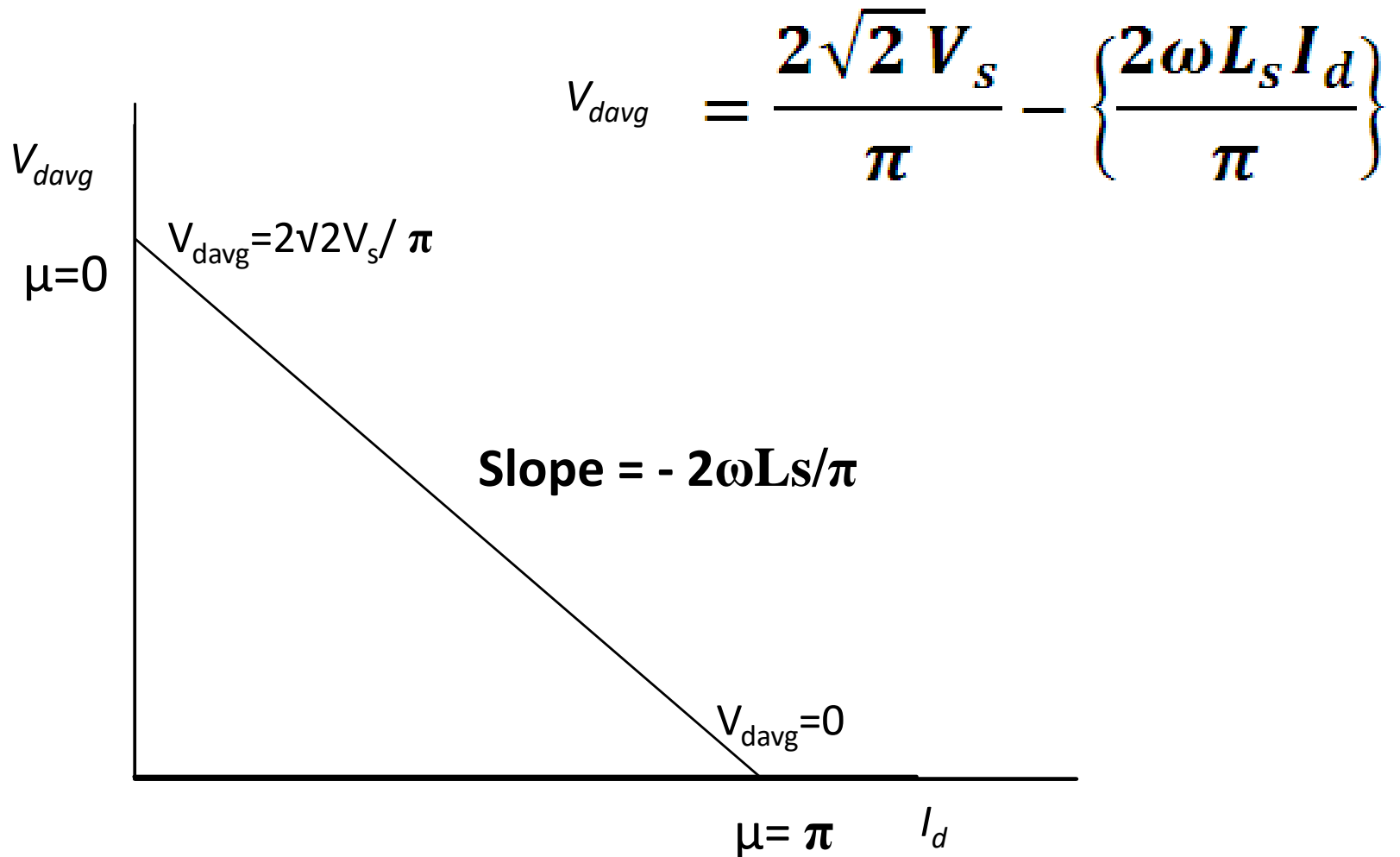
Average output voltage is reduced by $\frac{2\omega L_s I_d}{\pi}$



- Large values of current or/and source Inductance result in larger value of μ and make average voltage zero.

Bridge Rectifier with R-L-E load

- Continuous current mode

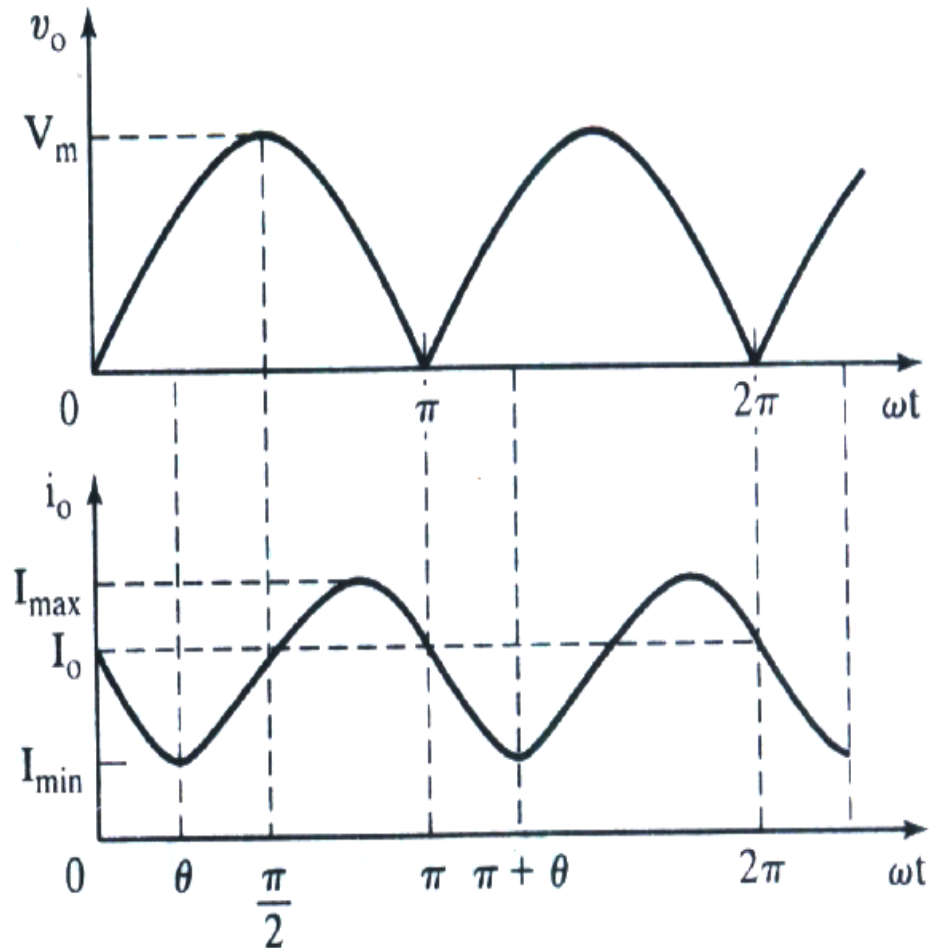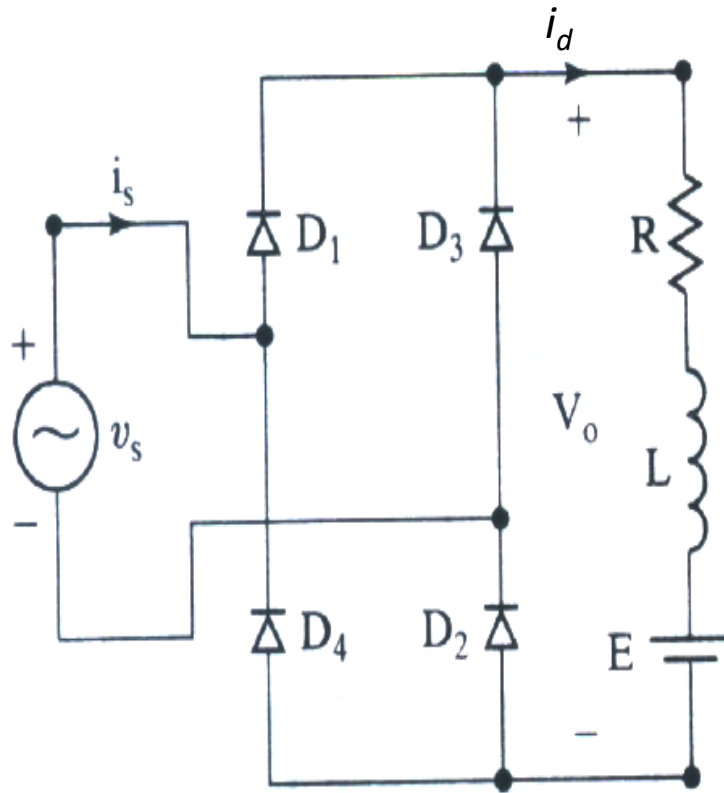


Effect of diode rectifier on utility voltage & Current

- **Line current distortion**

Source current deviates significantly from the sinusoidal waveform.

- **Line voltage distortion**

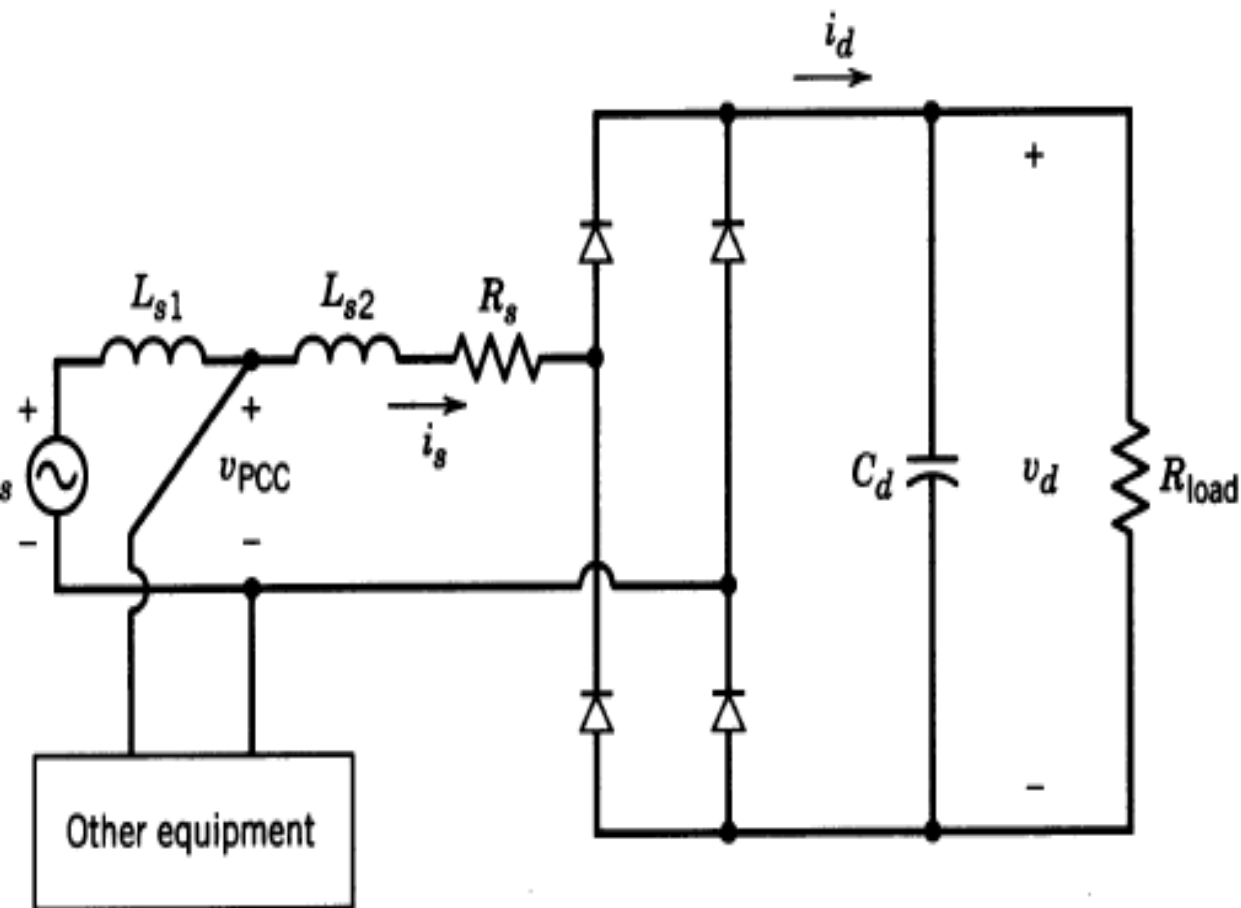Distortion in the line current results in the distortion of line voltage waveform.



L_{s1} – Inductance of the utility side

L_{s2} – Inductance due to the power electronic equipment

R_s – represents the diode resistance


PCC- point of common coupling where other loads and power electronic load are connected

V_{pcc} Voltage across the PE equipment and other loads at the point of common coupling

$$V_{pcc} = V_s - L_{s1} \frac{di_s}{dt}$$

- **Source current i_s**
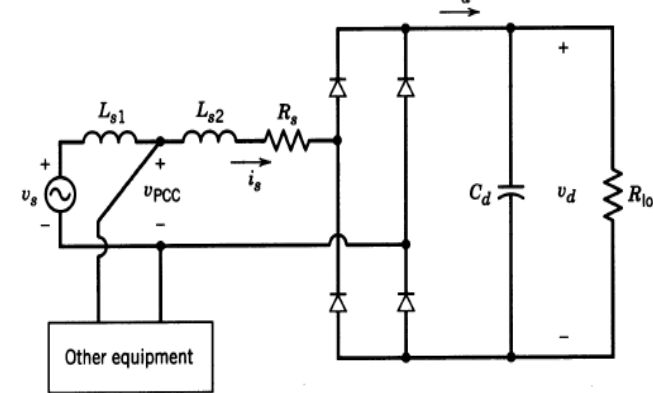
$$i_s = i_{s1} + \sum_{h=3,5,\dots}^{\infty} i_{sh}$$



$$V_{pcc} = V_s - L_{s1} \frac{di_{s1}}{dt} - L_{s1} \sum_{h=1,3,5,\dots}^{\infty} \frac{di_{sh}}{dt}$$

$$= V_{pcc1} - L_{s1} \sum_{h=1,3,5,\dots}^{\infty} \frac{di_{sh}}{dt}$$

$$V_{pcc1} = V_s - L_{s1} \frac{di_{s1}}{dt}$$


- **Distortion in voltage at PCC due to harmonics in line current**

$$V_{pccdis} = L_{s1} \sum_{h=3,5,\dots}^{\infty} \frac{di_{sh}}{dt}$$

- Voltage available at the point of common coupling is highly deviated from the ideal sine waveform
- This is usually referred to voltage pollution in power system
- This is one of the reasons of power quality problems

Effect of Single phase rectifiers on the neutral current in 3 Φ 4 wire systems

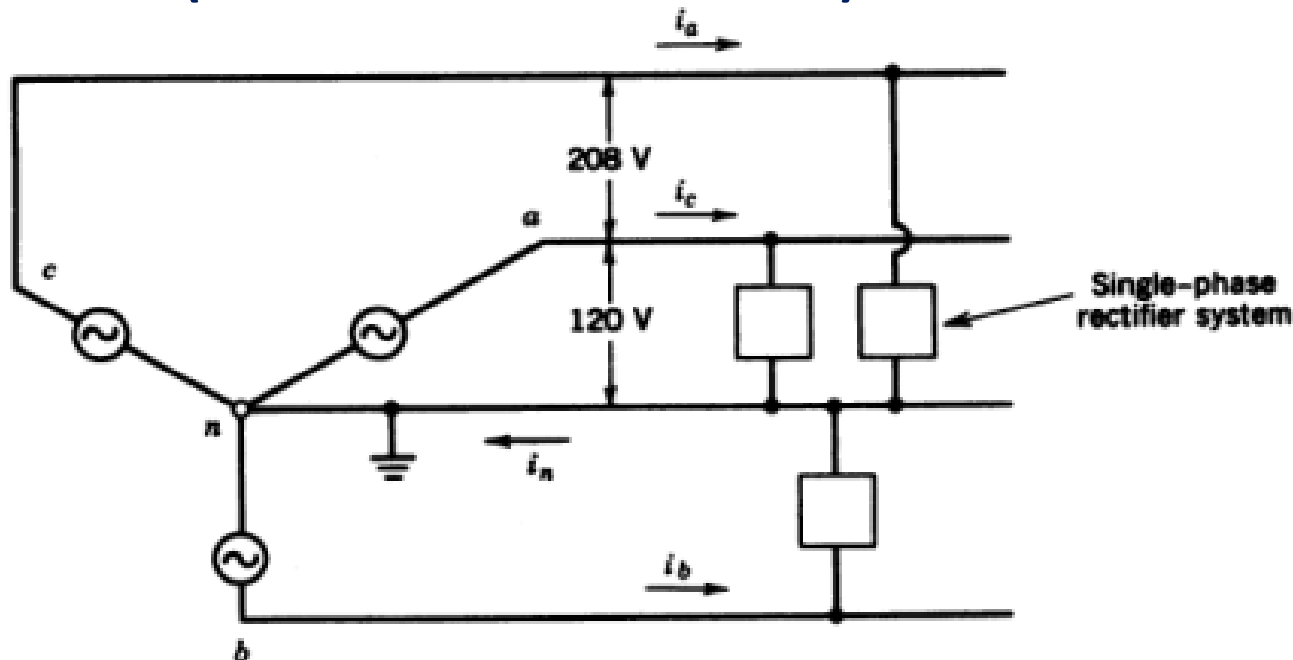- When all the 3 phases are loaded equally or balanced, neutral current $i_n = 0$.
- When single phase rectifiers are connected, $i_n \neq 0$
- Consider identical rectifiers connected between each phase and neutral (balanced load condition)



- **Phase a current**

$$i_a = i_{a1} + \sum_{n=2k+1}^{\infty} i_{an} \quad k=1,2,3,\dots$$

- $i_a = \sqrt{2}I_{s1}\sin(\omega t - \phi_1) + \sum_{n=2k+1}^{\infty} (\sqrt{2}I_{sn} \sin(n\omega t - \phi_n))$

$$i_b = \sqrt{2}I_{s1}\sin(\omega t - \phi_1 - 120) + \sum_{n=2k+1}^{\infty} \sqrt{2}I_{sn}\sin(n\omega t - \phi_n - 120n)$$

$$i_c = \sqrt{2}I_{s1}\sin(\omega t - \phi_1 - 240) + \sum_{n=2k+1}^{\infty} \sqrt{2}I_{sn}\sin(n\omega t - \phi_n - 240n)$$

• **Neutral current** $i_N = i_a + i_b + i_c$

$$= i_{a1} + \sum_{n=2k+1}^{\infty} i_{an} + i_{b1} + \sum_{n=2k+1}^{\infty} i_{bn} + i_{c1} + \sum_{n=2k+1}^{\infty} i_{cn}$$

Sum of the three phase fundamental components and non-triplen harmonics is zero.

- $i_{a1} + i_{b1} + i_{c1} = 0$

$$i_N = \sum_{n=3(2k-1)}^{\infty} i_{an} + i_{bn} + i_{cn}$$

Neglecting all higher order harmonics,

$$i_N = i_{a3} + i_{b3} + i_{c3} = 3 i_{a3} \approx i_{a1}$$

- **Thus, neutral wire carries 3 times 3rd harmonic current flowing through a phase**
- **neutral current is almost equal to or greater than the fundamental line current.**

Neutral current

