

ques (1)

$$V = 11 \text{ kV}$$

$$\text{mVAR Rating} = 1 \text{ mVAR}$$

$$Q_c = 1 \text{ mVAR}$$

$$Q_L = 0.3 \text{ mVAR}$$

$$\text{S.C. Capacity} = 20 \text{ MVA @ } 0 \text{ PF lagg.}$$

(a.)


$$S = \frac{V^2}{Z}$$

$$Z = \frac{V^2}{S} = \frac{\left(\frac{11}{\sqrt{3}}\right)^2 \times 10^6}{20 \text{ MVA}}$$

$$Z = 2.0167 \Omega$$

SO; at 0 PF
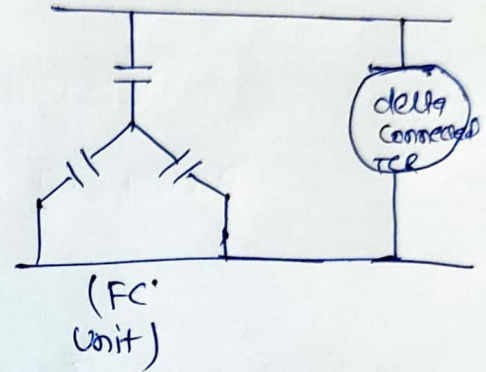
$$X_L = Z = \underline{\underline{j2.0167 \Omega}}$$



Now;

$$\sqrt{3} V_L I_L = 1 \text{ mVAR}$$

(a.)

$$\sqrt{3} \times 11 \times 10^3 \times I_L = 1 \times 10^6$$

$$I_L = \frac{1 \times 10^6}{\sqrt{3} \times 11 \times 10^3}$$

$$I_L = \underline{\underline{52.4863 \text{ A}}}$$

for delta connection

$$I_{ph} = \left(\frac{I_L}{\sqrt{3}}\right) = \underline{\underline{30.303 \text{ A}}}$$

$$\text{SO; } X_{cph} = \left(\frac{V_{ph}}{I_{ph}}\right) = \frac{11 \times 10^3}{30.303}$$

$$\boxed{X_{cph} = 363 \Omega}$$

(\because delta connection
 $\therefore V_{ph} = V_L$)

For TCR unit

$$Q_L = 0.3 \text{ MVAR}$$

$$\sqrt{3} V_L I_L = 0.3 \text{ MVAR}$$

$$I_L = \frac{0.3 \times 10^6}{\sqrt{3} \times 11 \times 10^3}$$

$$I_L = 15.746 \text{ A} \Rightarrow I_{ph} = \left(\frac{15.746}{\sqrt{3}} \right) = 13.31 \text{ A}$$

$$\text{So: } (X_L)_{ph} = \frac{V_{ph}}{(I_L)_{ph}}$$

$$= \frac{11 \times 10^3}{13.31}$$

$$(X_L)_{ph} = 1210 \Omega$$

(b) let $V_{base} = 11 \text{ kV}$

$$(S)_{base} = 10 \text{ MVA}$$

$$\text{s.c. Capacity} = \left(\frac{20}{10} \right) = 2 \text{ PU}$$

$$X = \frac{1}{\text{s.c. Capacity}}$$

$$X = 0.5 \text{ P.U.} \left(\frac{20}{11} \right)$$

$$\Delta V_L = 11 \text{ kV} - 11.4 \text{ kV} = -0.4 \text{ kV}$$

$$= -\frac{0.4 \times 10^3}{11 \times 10^3} = -0.0364 \text{ PU}$$

$$\Delta V_L = Q_L (V \times X)$$

$$Q_L = \frac{\Delta V_L}{(V \times X)}$$

$$Q_L = \frac{-0.0864}{1.04 \times 0.5}$$

$$= -0.07 \text{ PU}$$

$$V = \left(\frac{11.04}{11} \right) = 1.04$$

$$= 1.0867$$

$Q \rightarrow -ve \Rightarrow$ (inductive)

$$Q_L = (0.07) \times 10$$

$$= 0.7 \text{ mVAR.}$$

max^m inductive compensation is = 0.3 mVAR

\therefore max^m inductive/Reactive power

$$\text{drawn by the load} = (0.7 - 0.3)$$

$$= 0.4 \text{ mVAR}$$

~~So Range of Reactive power \Rightarrow 1 mVAR Cap. to 0.4 mVAR inductive.~~

(c) for $V = 11 \text{ KV}$

Range of Reactive power

drawn by load \Rightarrow 1 mVAR Cap. to 0.3 mVAR

inductive.

(d) $\Delta V = 11 - 10.4$

$$= \left(\frac{0.6}{11} \right) = 0.0545 \text{ PU}$$

$$V_{PU} = \frac{10.4}{11}$$

$$= 0.945 \text{ PU}$$

$$Q_C = \frac{0.0545}{0.945 \times 0.5}$$

$$= 1.153 \text{ mVAR}$$

max^m compensation available = 1 mVAR

\therefore load should draw 0.153 mVAR Capacitive Reactive Power.

②

$$V_{oc} = 10.8 \text{ kV}$$

1 mVA load

$$PF = 0.8 \text{ lagg.}$$

Bus voltage maintained

$$\text{at } 11 \text{ kV.}$$

$$\Delta V = \left(\frac{0.2}{11} \right) = 0.0182 \text{ PU} \quad V_u = \left(\frac{10.8}{11} \right) = \underline{\underline{0.9818}}$$

$$Q_c = \frac{0.0182}{0.9818 \times 0.5} = \underline{\underline{0.0371 \text{ PU}}}$$

$$Q_c = 0.371 \text{ mVAR.}$$

$$\text{inductive Reactive Power req.} = \underline{\underline{1 - 0.371 = 0.629 \text{ mVAR}}}$$

Reactive power drawn

$$\text{by load} = 1 \times \{ \sin(\cos^{-1}(0.8)) \}$$

$$= 0.6 \text{ mVAR}$$

$$\therefore \text{Inductive power drawn by TCR} = 0.6 - 0.629$$

$$= 0.029 \text{ mVAR}$$

$$= \underline{\underline{0.0029 \text{ PU}}}$$

$$\therefore 0.0029 = 0.0371 \left(1 - \frac{2}{\pi} \alpha - \frac{1}{\pi} \sin 2\alpha \right)$$

$$\frac{2}{\pi} \alpha + \frac{1}{\pi} \sin 2\alpha = 0.9218$$

$$\alpha = ?$$

Ques ② Given: ; 11kV, 3- ϕ TSC-TCR unit

$$\text{Capacity} = 1 \text{ mVAR} \quad \{\text{for 4 units}\}$$

\therefore Capacity of one TSC unit

$$= 0.25 \text{ mVAR}$$

for 5th harmonic Compensation,

inductive Reactance Used = 4%.

$$\therefore \text{Net Capacitive power} = (1 - 0.04) \times 0.25 \\ = 0.24 \text{ mVAR.}$$

for TSC

$$\sqrt{3} V_L I_L = 0.24$$

$$(I_L) = 12.6 \text{ A}$$

$$(I_L)_{ph} = 7.273 \text{ A}$$

$$X_C = \left(\frac{11 \text{ kV}}{7.273} \right) = 1512.44 \Omega$$

For TCR

inductive power = 0.3 mVAR

$$\sqrt{3} V_L I_L = 0.3 \text{ mVAR}$$

$$(I_L) = \frac{0.3 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 15.746 \text{ A}$$

$$(I_L)_{ph} = 9.091 \text{ A}$$

$$X_L = \frac{11 \times 10^3}{9.091} = \underline{1210 \Omega}$$