
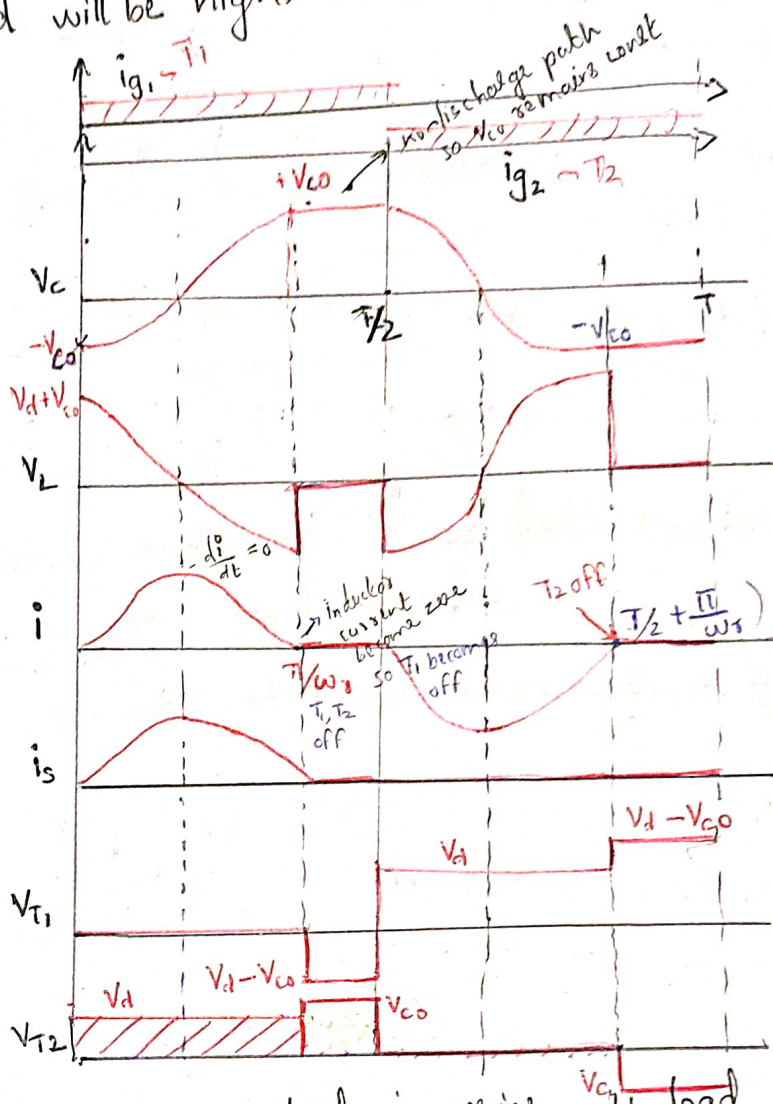



Series Invested

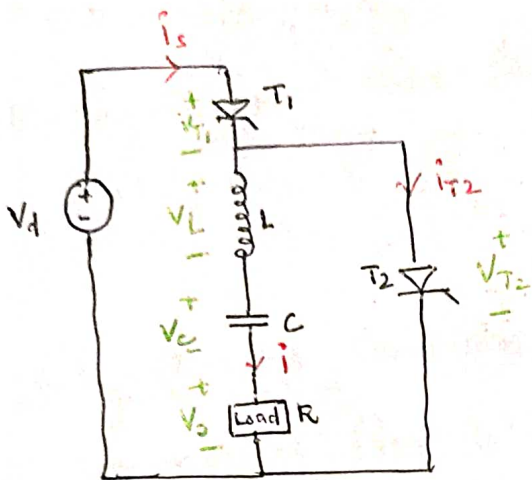* Application in high power, high freq applications.
Otherwise L and C will required will be high.
↑ $i_g \rightarrow T_1$




- * The commutating elements L & C are connected in series with load.
- * Load current flows continuously through L & C.
- * Hence, this ckt is used in high freq applications.
- * Initially T_1 is made to conduct for 1st half cycle.

current path

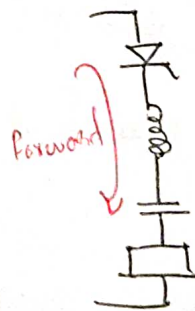

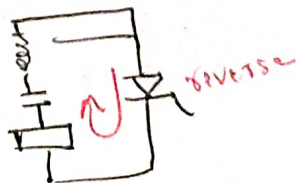Then T_2 is made to conduct for 2nd half cycle
current path



* L & C are selected such that combination R-L-C is underdamped

* At $t=0$, T_1 is turned on
 T_2 is off state

$$V_d = R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt + V_c(0) \quad , \quad 0 < t < T/2$$

Initial conditions, At $t=0 \rightarrow$ (1) $i(0) = 0$ (2) $V_c(0) = -V_{co}$

(3) $\left. \frac{d(i)}{dt} \right|_{t=0} = (V_d + V_{co})$

$$\frac{V_d}{s} = R I(s) + L (s I(s) + \overset{0}{I_0}) + \frac{1}{Cs} I(s) + \frac{V_c(0)}{s}$$

$$\frac{V_d}{s} = R I(s) + L s I(s) + L \overset{0}{I_0} + \frac{I(s)}{Cs} + \frac{V_c(0)}{s}$$

$$\frac{V_d - V_c(0)}{s} = I(s) \left[R + Ls + \frac{1}{Cs} \right] + L \overset{0}{I_0}$$

$$I(s) = \frac{V_d - V_c(0) - L \overset{0}{I_0}}{s \left(R + Ls + \frac{1}{Cs} \right)} = \frac{(V_d - V_c(0) - L \overset{0}{I_0}) Cs}{RCs + LCs^2 + 1}$$

$$I(s) = \frac{(V_d - V_c(0)) Cs}{LC \left(s^2 + \frac{R}{L}s + \frac{1}{LC} \right)} = \frac{V_d + V_{co}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \quad \text{where } \frac{1}{LC} = \omega_0^2$$

$$= \frac{\sqrt{\frac{C}{L}} (V_d - V_c)}{\sqrt{L}} \times \frac{\omega_0}{s^2 + 2\zeta\omega_0 s + \omega_0^2} = \sqrt{\frac{C}{L}} (V_d - V_c) \times \frac{\omega_0}{s^2 + 2\zeta\omega_0 s + \omega_0^2}$$

Finding roots $s_1, s_2 = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{-2\zeta\omega_0 \pm \sqrt{(2\zeta\omega_0)^2 - 4\omega_0^2}}{2}$

$$= \frac{V_d + V_{co}}{L} \times \frac{1}{\left(s^2 + \frac{SR}{L} + \frac{1}{LC} + \left(\frac{R}{2L} \right)^2 - \left(\frac{R}{2L} \right)^2 \right)}$$

$$i(t) = \frac{1}{\left(s + \frac{R}{2L} \right)^2 + \left(\sqrt{\frac{1}{LC} - \left(\frac{R}{2L} \right)^2} \right)^2} \times \frac{\omega_0}{\omega_0} \times (V_d + V_{co})$$

complete the derivation

$$i(t) = \frac{V_d + V_{co}}{\omega_r L} e^{-\delta t} \sin(\omega_s t) \quad \text{Laplace inverse}$$

$$\delta = \frac{R}{2L}, \quad \omega_s = \sqrt{\left(\frac{1}{\sqrt{LC}}\right)^2 - \left(\frac{R}{2L}\right)^2}, \quad \omega_o = \frac{1}{\sqrt{LC}}$$

$$\begin{aligned} * \quad V_L(t) &= L \frac{di(t)}{dt} = \frac{\omega_o}{\omega_r} [V_d + V_{co}] e^{-\delta t} \cos(\omega_s t + \phi) \\ &= \left[\phi = \tan^{-1} \frac{\delta}{\omega_r} \right] \end{aligned}$$

$$* \quad V_c(t) = V_d - V_L - iR$$

$$\begin{aligned} * \quad \text{when } t < \frac{\pi}{\omega_r}, \quad V_{T1} &= 0, \\ V_{T2} &= V_d \quad \& \quad V_o = i(t)R \end{aligned}$$

$$* \quad \text{At } t = \frac{\pi}{\omega_r}, \quad i(t) = 0, \quad T_1 \text{ is turned off}$$

$$\frac{\pi}{\omega_r} < t < \frac{T}{2} : \quad \begin{array}{l} \text{Both switches are off} \\ \text{Load current} \quad \text{source current} \\ i(t) = 0, \Rightarrow i_s(t) = 0 \end{array}$$

$$V_L(t) = 0, \quad V_c = V_{cmax}$$

$$\underline{\frac{T}{2} < t < \left(\frac{T}{2} + \frac{\pi}{\omega_r}\right)}$$

$$t' = t - \frac{T}{2}$$

$$* \quad \text{At } t' = 0, \quad T_2 \text{ is turned on.}$$

$$* \quad \underline{0 < t' < \frac{T}{2}}$$

$$0 = Ri(t') + L \frac{di(t')}{dt} + \frac{1}{C} \int i(t') dt + V_{cmax}$$

19/4/22

initial conditions at $t'=0 \Rightarrow i(0)=0, V_c(0)=V_{max}$.

solving

$$0 = RI(s) + L(sI(s) + \overset{0}{I_0}) + \frac{1}{Cs} (I(s)) + \frac{V_c(0)}{s} \quad \left| \frac{di(t')}{dt} \right|_{t'=0} = -\frac{V_{max}}{L}$$

$$I(s) = \frac{-V_{max}}{L} \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$i(t) = \frac{-V_{max}}{\omega_s L} e^{-\delta t} \sin(\omega_s t')$$

$$\delta = \frac{R}{2L} \quad \omega_s = \sqrt{\left(\frac{1}{LC}\right)^2 - \left(\frac{R}{2L}\right)^2} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$* \quad V_L(t) = \frac{L di(t)}{dt} = -\frac{\omega_0}{\omega_s} V_{max} e^{-\delta t'} \cos(\omega_s t' + \phi)$$

$$* \quad V_c(t) = -V_L - iR$$

$$= -\frac{\omega_0}{\omega_s} V_{max} e^{-\delta t'} \cos(\omega_s t' + \phi) + \frac{R V_{max}}{\omega_s L} e^{-\delta t'} \sin(\omega_s t')$$

$$* \quad V_{T1} = -V_d$$

$$* \quad V_{T2} = 0$$

Draw backs of Series Inverter

① Maximum Inverted frequency is limited to a value less than circuit ringing frequency (ω_r).

② For very low values of inverted frequencies, load voltage is highly distorted.

Design of L

- * L is chosen on basis of attenuation factor.

$$i(t) = \frac{V_d + V_{co}}{\omega_s L} e^{-R/2Lt} \sin(\omega_s t)$$

$$\Rightarrow \text{Peak value of } i(t) \text{ is } \frac{V_d + V_{co}}{\omega_s L} e^{-\frac{R\pi}{2L \cdot 2\omega_s}}$$

- * If there is no attenuation, then $i(t)$ would be

$$\frac{V_d + V_{co}}{\omega_s L} \sin \omega_s t \text{ and peak value is } \frac{V_d + V_{co}}{\omega_s L}$$

$$\text{Attenuation factor } AF = \frac{\frac{V_d + V_{co}}{\omega_s L} e^{-\frac{R}{2L} \cdot \frac{\pi}{2\omega_s}}}{\frac{V_d + V_{co}}{\omega_s L}} = e^{-\frac{R}{2L} \cdot \frac{\pi}{\omega_s}}$$

$$\log_{10}(AF) = \frac{-R}{8f_s L}$$

$$L = \frac{-R}{8f_s \log_{10}(AF)}$$

- * L is selected such that $AF = 0.5$

Design of C

- * C is selected from value of ω_s .

$$\omega_s = \sqrt{\left(\frac{1}{LC} - \left(\frac{R}{2L}\right)^2\right)}$$

\Rightarrow

$$C = \frac{1}{L} \left[\frac{1}{\omega_s^2 + \left(\frac{R}{2L}\right)^2} \right]$$

$$\omega_s \text{ selected such that } \frac{\omega_s}{\pi} < \frac{1}{2}$$

* If Load is variable, then C is selected for maximum possible value of R so that circuit is under damped.

* Voltage rating of C is $V_d + V_{comax}$

Selection of Thyristor


* Forward blocking voltage rating must be greater than $V_{comax} + V_d$ ($V_d + V_{comax}$)


* Peak current rating must be greater than peak load current for minimum load resistance.

$$\frac{V_d + V_{co}}{\omega R L} e^{-\frac{R_{min}}{2L}} \cdot \frac{\pi}{2\omega R}$$

* t_2 must be less than $t_c = \frac{T}{2} - \frac{\pi}{\omega R}$

modified Series Inverter

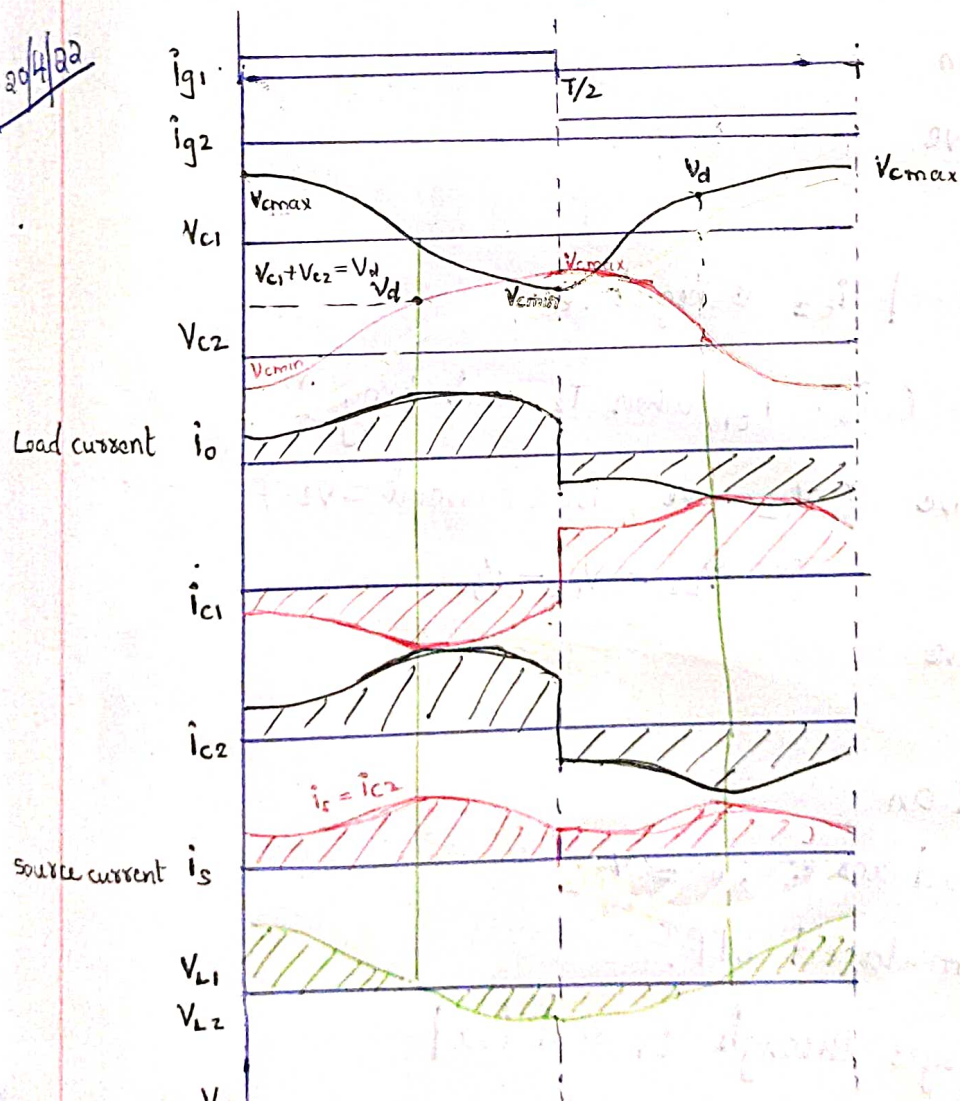

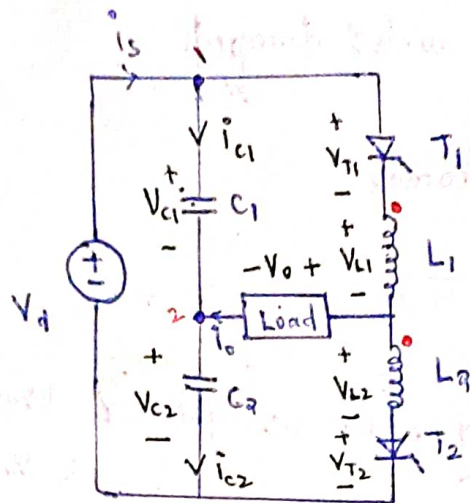

$$L_1 = L_2$$

$$C_1 = C_2$$

L_1 & L_2 are tightly coupled - high coef of coupling (mutual inductance)

* For $t \leq 0$ T_2 is on

$$V_{c1} = V_{cmax}$$

$$V_{c2} = -V_{cmin}$$

i_o is negative

$$V_o = i_o \times R$$

i_{c1} is +ve | i_{c2} is negative

i_s is +ve ($i_s = i_{c1}$ when T_2 conducting.)

V_{L2} negative ($V_{c2} = -ve$, load current -ve)

$$\text{so } V_{L2} = V_{c2} - V_o$$

V_{L1} negative

* At $t = 0$ T_1 is turned on

V_{c1} is coupled across $L_1 = V_{L2}$

T_2 is commutated off.

C_1 discharges through L_1 and load

* V_{c1} changes from V_{c1max} to V_{c1min}

C_2 gets charged through T_1, L_1 and Load

$$i_o = i_s - i_{c1} \quad \text{KCL at node 1}$$

$$i_{c2} = i_{c1} + i_o \quad \text{KCL at node 2}$$

$$i_s = i_{c2}$$

* At $t = \frac{T}{2}$, T_2 is turned on

V_{c2} is coupled across $L_2 = V_{L1}$

T_1 is commutated off

C_2 discharges through L_2 and load

V_{c2} changes from V_{c2max} to V_{c2min}

C_1 gets charged through load, T_2 , & L_2

$$i_o =$$

$$V_{T1} = V_d - V_{L1} - V_{L2} = V_d - 2V_{L2}$$

Advantages over series inverter.

Inverter freq can be less than singing freq

During -ve half cycle also source supplies power \Rightarrow Less distortion in source current.