
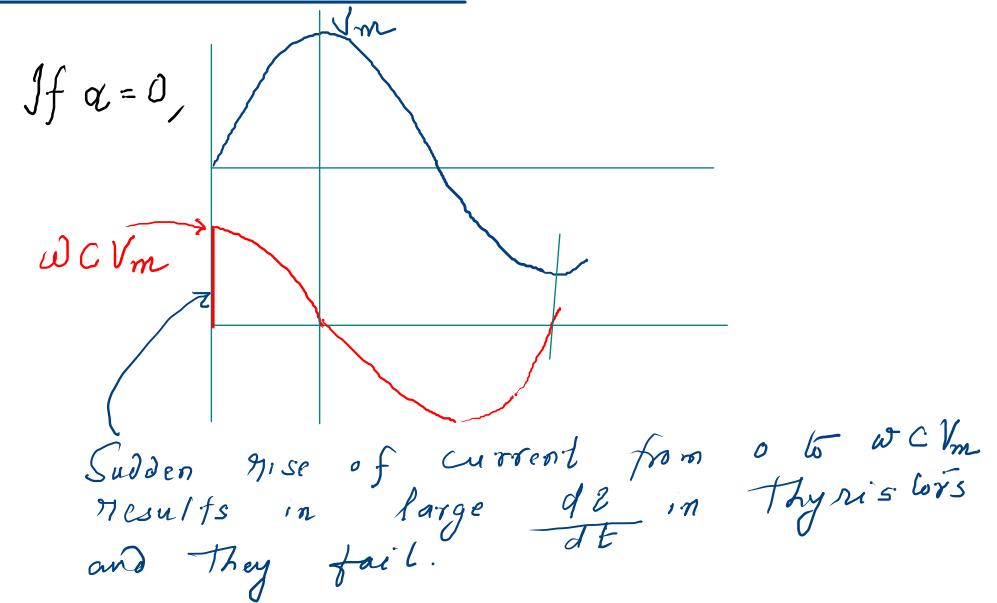


The TSC-TCR Static VAr Generator and Control


[You can use the following as Text books for this portion.

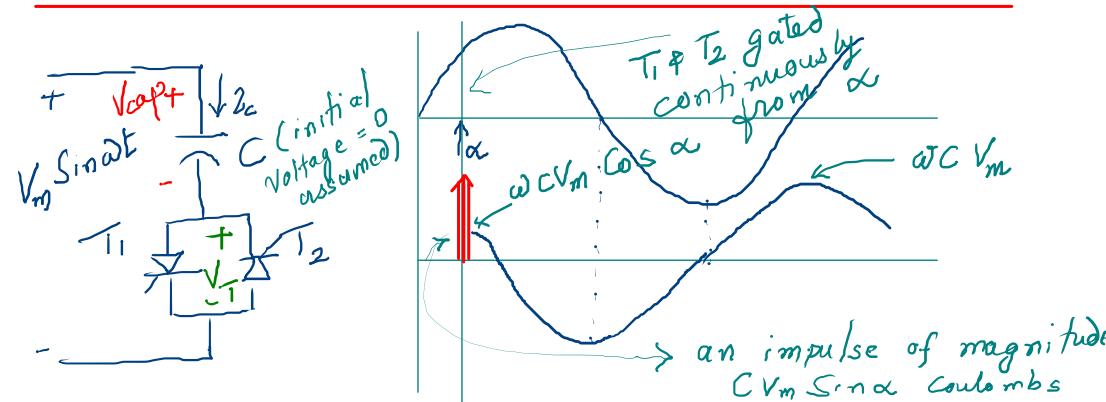1. Understanding FACTS by Hingorani & Gyugyi,
Section 5.2
2. Thyristor-based FACTS Controllers for Electrical Transmission Systems
by R. Mohan & Rajiv K Varma
IEEE Press, Wiley Interscience
Section 3.8

Why a Thyristor Controlled Capacitor Similar to TCR is not practical?




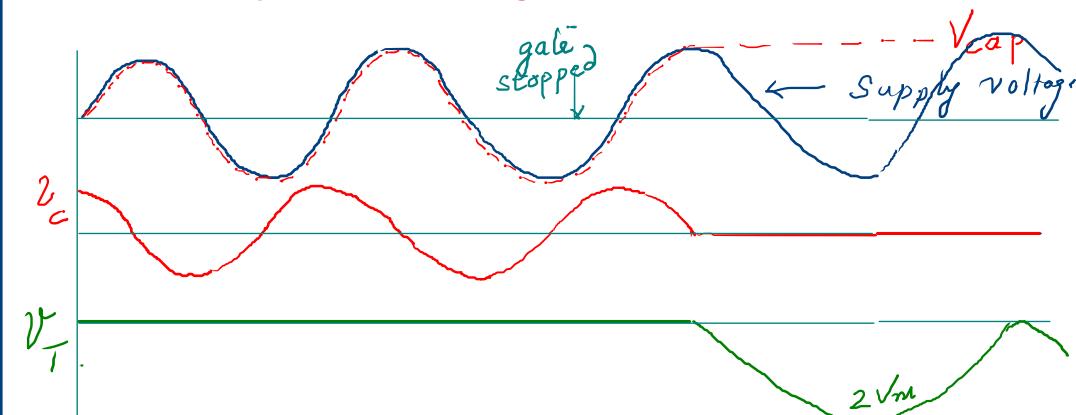When Thyristor Gate Signals Are Withdrawn....



The TSC-TCR Static VAr Generator and Control

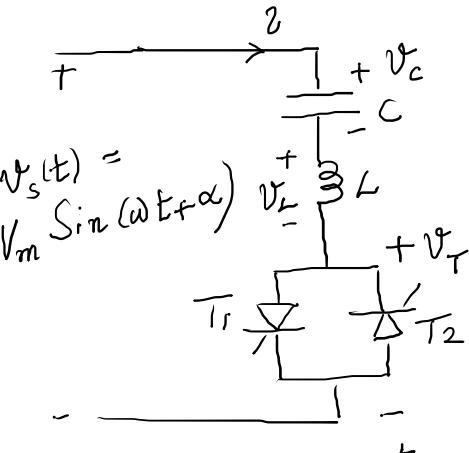Transient-free Switching-ON of a Capacitor With the help of a Reactor in Series



$$V_s(t) = V_m \sin(\omega t + \alpha)$$

T_1 & T_2 are gated continuously starting from $t=0$

$$V_c(0^-) = V_{co}$$

$$i(0^-) = 0$$

$$V_s(t) = \frac{1}{C} \int i dt + V_{co} + L \frac{di}{dt}$$

$$\therefore L \frac{d^2 i}{dt^2} + \frac{1}{C} i = \frac{d V_s(t)}{dt}$$

$$\frac{d^2 i}{dt^2} + \frac{1}{LC} i = \frac{\omega V_m}{L} \cos(\omega t + \alpha), \quad t \geq 0$$

$$i(0^+) = i(0^-) = 0$$

$$V_c \text{ at } t=0^+ \text{ is } V_m \sin \alpha - V_{co}$$

$$\therefore \frac{dV_c}{dt}|_{0^+} = \frac{V_m \sin \alpha - V_{co}}{L}$$

Particular Solution :

$$= \frac{V_m}{\omega L - \frac{1}{\omega C}} \sin(\omega t + \alpha - 90^\circ)$$

$$= -\frac{\omega C V_m}{1 - \omega^2 L C} \sin(\omega t + \alpha - 90^\circ)$$

$$= \frac{\omega C V_m}{1 - \omega^2 L C} \cos(\omega t + \alpha)$$

$$\text{Let } n \triangleq \sqrt{\frac{1}{\omega C}} = \sqrt{\frac{1}{\omega^2 L C}} = \frac{\omega_0}{\omega}$$

$$= \frac{n^2}{n^2 - 1} \omega C V_m \cos(\omega t + \alpha)$$

$$\omega_0 \triangleq \frac{1}{\sqrt{LC}}$$

Complementary Solution is

$$A \cos \omega_0 t + B \sin \omega_0 t \quad \text{where}$$

$$A \text{ & } B \text{ are constants and } \omega_0 = \frac{1}{\sqrt{LC}}$$

The TSC-TCR Static VAr Generator and Control

$$z(t) = \frac{n^2}{n^2-1} \omega C V_m \cos(\omega t + \alpha) + A \cos \omega_0 t + B \sin \omega_0 t$$

Since $z(0^+)$ = 0, $A = -\frac{n^2}{n^2-1} \omega C V_m \cos \alpha$ — ①

Since $\frac{dz}{dt}|_{0^+} = V_m \frac{\sin \alpha}{L} - V_{CO}$

$$-\frac{n^2 \omega^2 C V_m \sin \alpha}{n^2-1} + \omega_0 B = \frac{V_m \sin \alpha}{L} - V_{CO}$$

$$\omega_0 B L = V_m \sin \alpha - V_{CO} + \frac{n^2 \omega^2 L C}{n^2-1} V_m \sin \alpha$$

$$= V_m \sin \alpha \left(1 + \frac{1}{n^2-1}\right) - V_{CO}$$

$$\therefore (\omega_0 L) B = \frac{n^2}{n^2-1} V_m \sin \alpha - V_{CO} — ②$$

From ① & ② it follows that transient-free switching is possible if $\alpha = \frac{\pi}{2}$ and $V_{CO} = \frac{n^2}{n^2-1} V_m$ OR $\alpha = \frac{3\pi}{2}$ & $V_{CO} = -\frac{n^2}{n^2-1} V_m$

If these conditions are not met, there will be a ringing transient at $\omega_0 = \frac{1}{\sqrt{LC}}$ rad/sec in capacitor current. Capacitor voltage and inductor voltage. This ringing transient usually gets damped down to 0 in a few cycles due to losses in reactor and thyristors. After that, steady-state solution is

$$z(t) = \frac{n^2}{n^2-1} \omega C V_m \cos(\omega t + \alpha)$$

$$V_C(t) = \frac{n^2}{n^2-1} V_m \sin(\omega t + \alpha)$$

$$V_L(t) = \frac{-1}{n^2-1} V_m \sin(\omega t + \alpha)$$

$$V_T(t) = 0$$


$T_{1,2}$ gate signal is withdrawn for $T_1 \neq T_2$

The TSC-TCR Static VAr Generator and Control

$\frac{1}{\omega C}$ value is usually 4 to 10% of ωL value. Usually it is 4%. With 4% L, the series combination will work as a passive tuned harmonic filter at 5th harmonic as well. With 4% L, value of n is 5 and the amplification factor of capacitor voltage is $\frac{25}{24} = \frac{1}{1-0.04} = 1.04$

Maximum delay in obeying OFF command = $T/2$

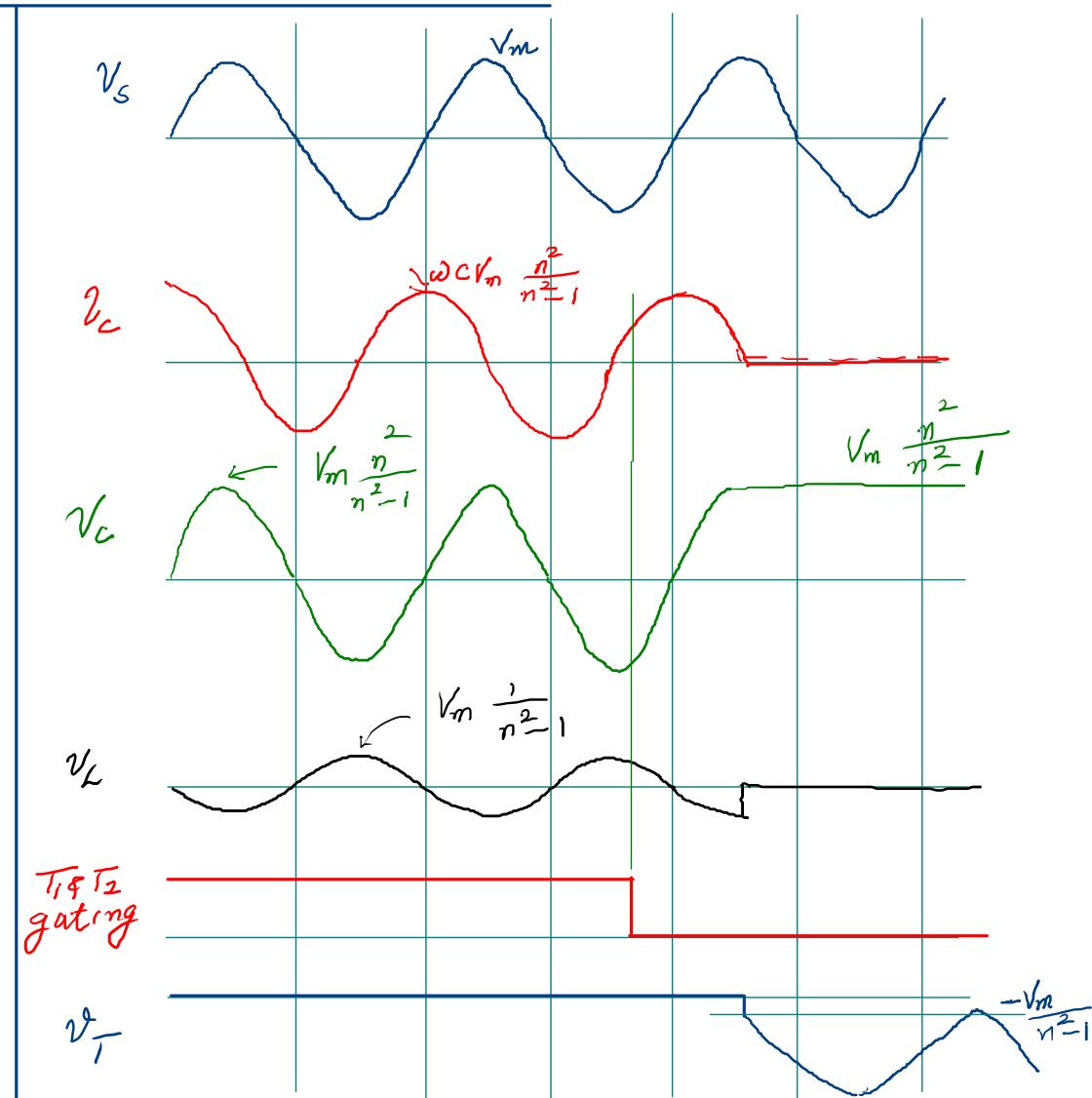If capacitor voltage does not leak down and if V_m does not change over time, releasing gate triggers to T_1 & T_2 at the peak of input voltage will result in transient-free switching ON of TSC next time.



The TSC-TCR Static VAr Generator and Control

Further look at transient component in current

$$i(t) = \frac{\omega^2}{n^2-1} wCV_m \cos(\omega t + \alpha) + A \cos \omega_0 t + B \sin \omega_0 t$$

$$\text{where } n^2 = \frac{1}{\omega^2 LC} = \left(\frac{\omega_0}{\omega}\right)^2, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$A = \frac{-n^2}{n^2-1} wCV_m \cos \alpha$$

$$B = \frac{1}{\omega_0 L} \left(\frac{n^2}{n^2-1} V_m \sin \alpha - V_{co} \right)$$

$$\text{Total amplitude of transient} = \sqrt{A^2 + B^2}$$

Case (i) - $V_{co} < V_m$, with V_{co} +ve

Say, we release gate to T_1 & T_2 when source voltage is equal to V_{co} & $V_T = 0$

$$\text{i.e. } V_m \sin \alpha = V_{co}$$

$$\text{Then } V_m \cos \alpha = \sqrt{V_m^2 - V_{co}^2} = V_m \sqrt{1 - \left(\frac{V_{co}}{V_m}\right)^2}$$

$$A = \frac{-n^2}{n^2-1} wCV_m \sqrt{1 - \left(\frac{V_{co}}{V_m}\right)^2}$$

$$B = \frac{V_{co}}{\omega_0 L} \left(\frac{n^2}{n^2-1} - 1 \right) = \frac{V_{co}}{(n^2-1)\omega_0 L}$$

Skipping the algebraic steps,

$$\sqrt{A^2 + B^2} = \underbrace{\left(\frac{n^2}{n^2-1} wCV_m \right)}_{\text{amplitude of fundamental current.}} \times \sqrt{1 - \left(\frac{V_{co}}{V_m} \right)^2 \left(1 - \frac{1}{n^2} \right)}$$

So, amplitude of transient component is $<$ amplitude of fundamental current in this strategy.

Case (ii) : $V_{co} > V_m$, with V_{co} +ve


Say, we release gate to T_1 & T_2 when source voltage is at peak and Thyristor voltage is minimum. i.e. $\alpha = 90^\circ$

$$\text{Then } A = 0, \quad B = \frac{1}{\omega_0 L} \left(\frac{n^2}{n^2-1} V_m - V_{co} \right)$$

$$\text{Amplitude of transient} = \left(\frac{n^2 wCV_m}{n^2-1} \right) \left[n \left(\frac{n^2-1}{n^2} \frac{V_{co}}{V_m} - 1 \right) \right]$$


The TSC-TCR Static VAr Generator and Control

The ON/OFF Controller for a TSC Unit

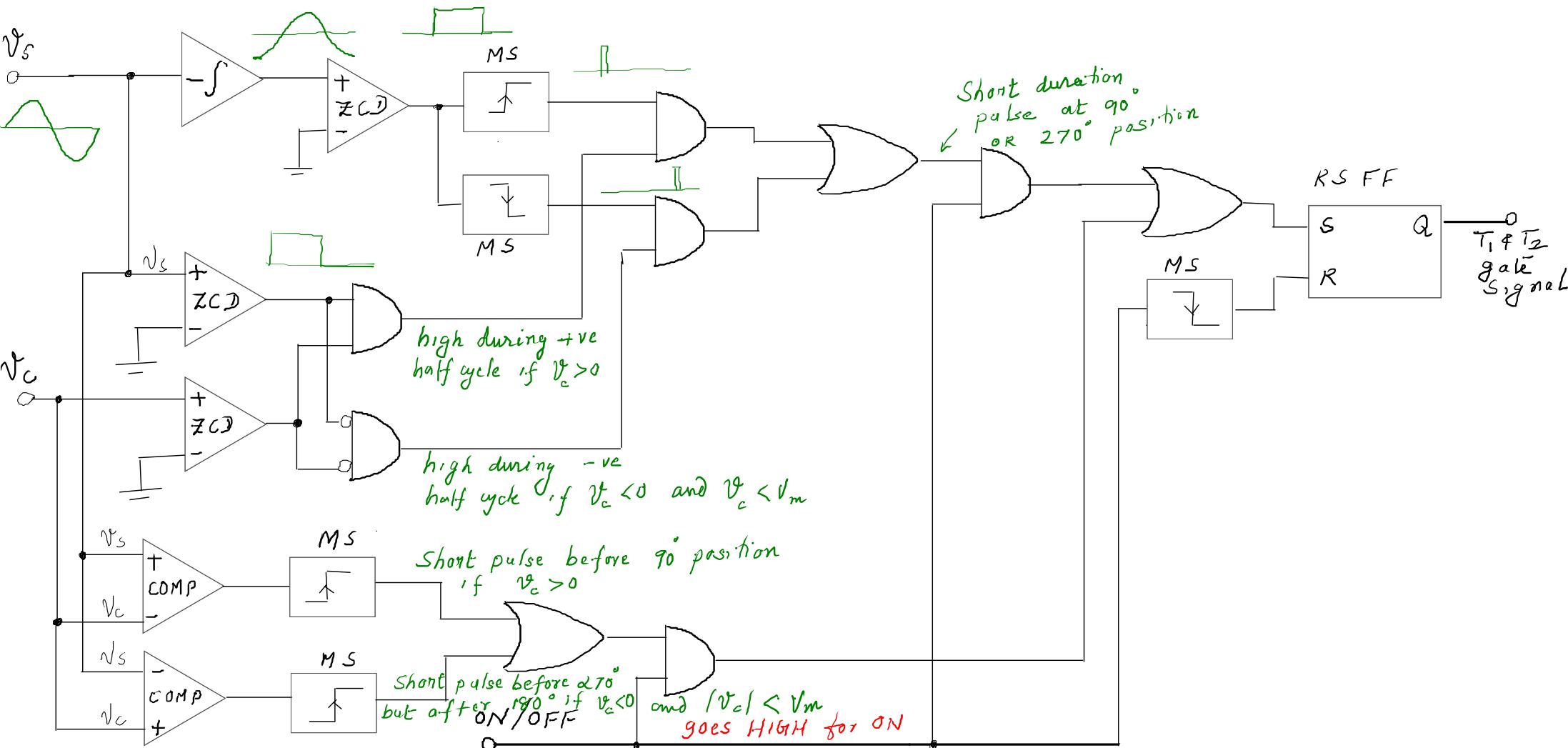


The TSC-TCR Static VAr Generator and Control

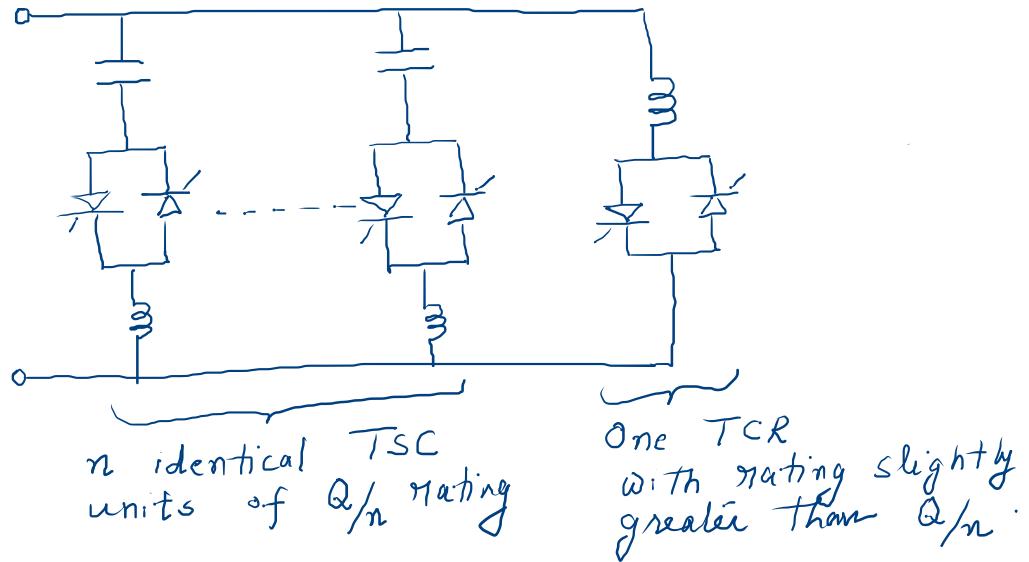The Single-Phase TSC-TCR System : Why the rating of TCR has to be more than that of individual TSC Unit?



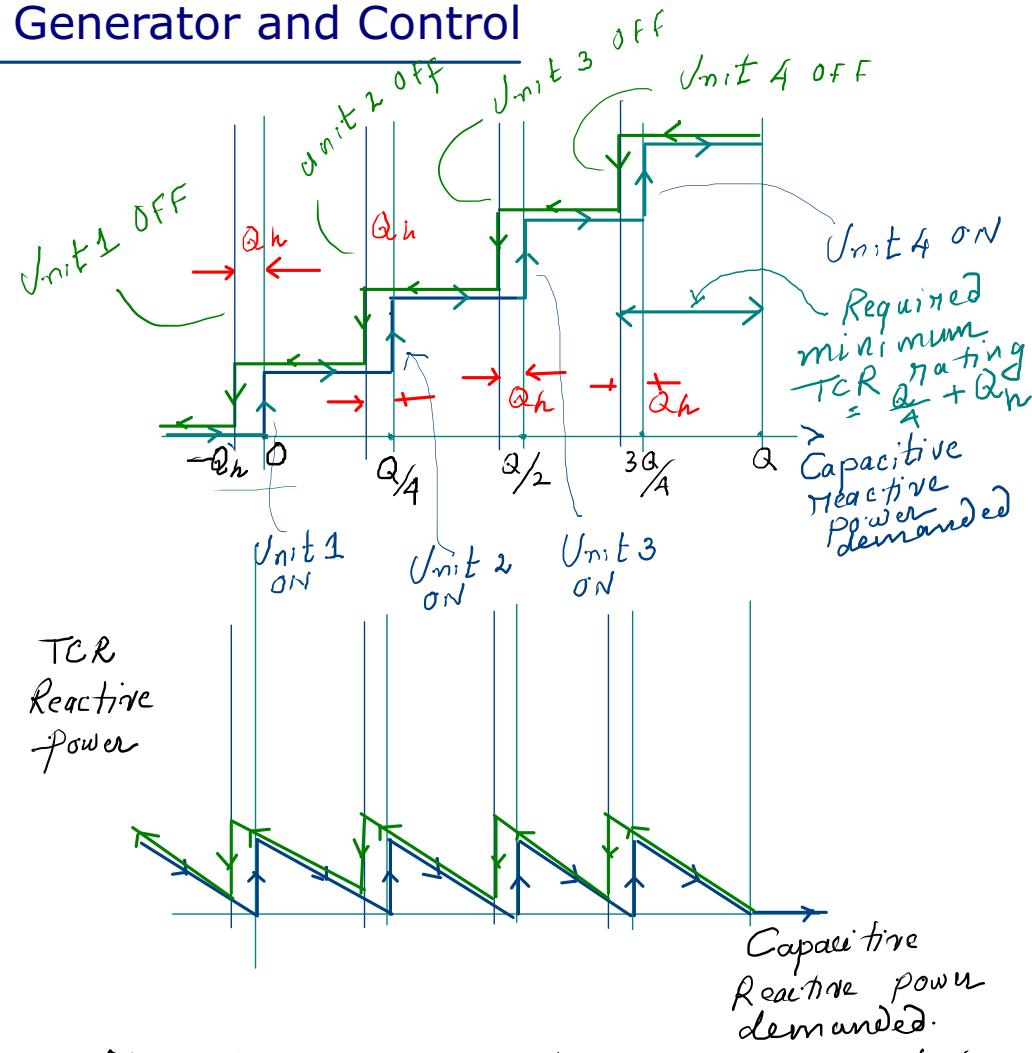TCR Rating has to be $> Q/n$ so that we can adopt hysteretic switching of TSC units and thereby avoid chattering in TSC units.





The TSC-TCR Static VAr Generator and Control

The ON/OFF Signal Generator for TSC Units


Input - Desired Capacitive Current I_{Cref} in the form of a DC Voltage. I_{Cref} for all TSC Units in ON condition is represented by a DC Voltage V_R (say 5V). i.e full capacity at nominal voltage is represented by V_R .

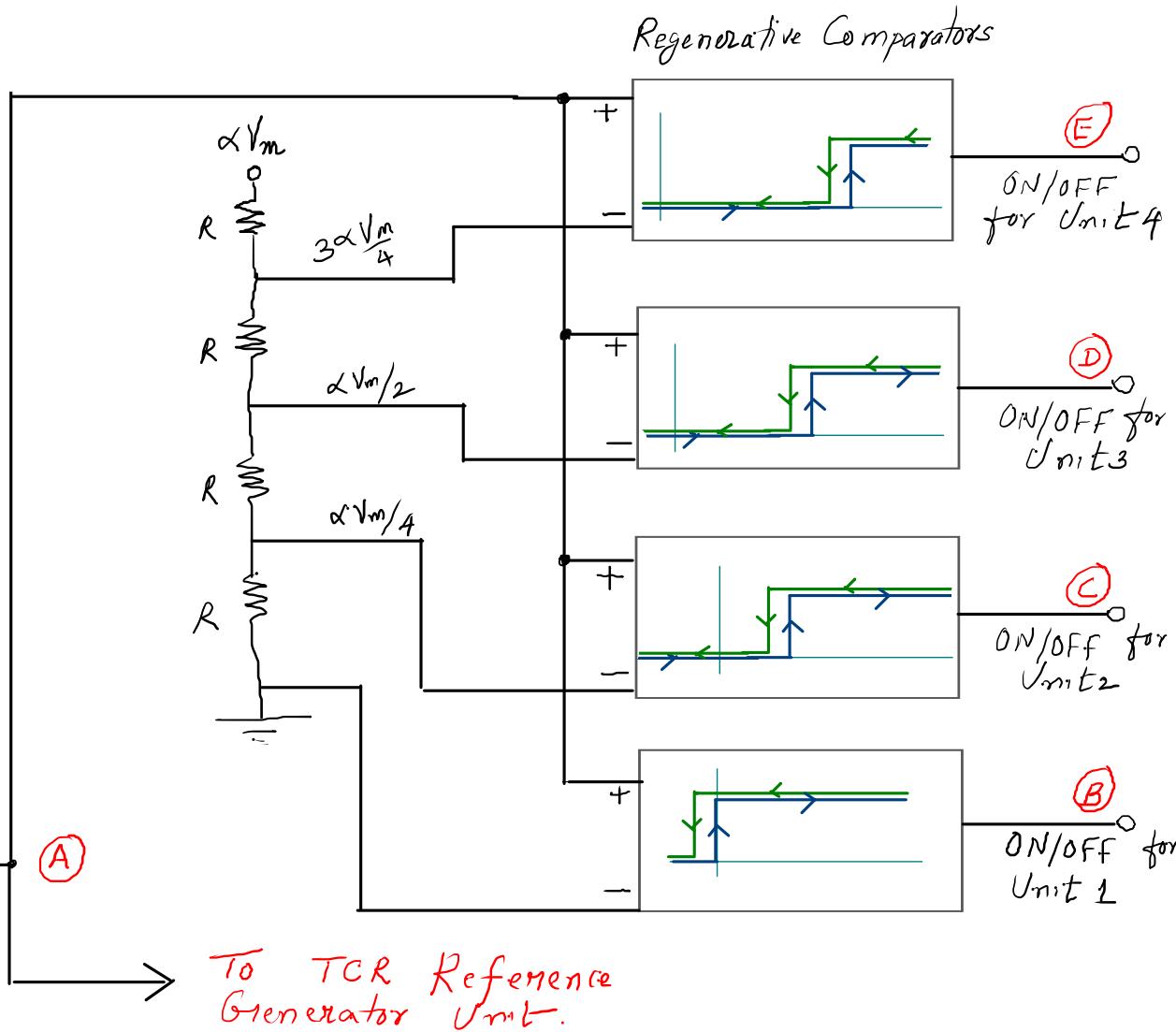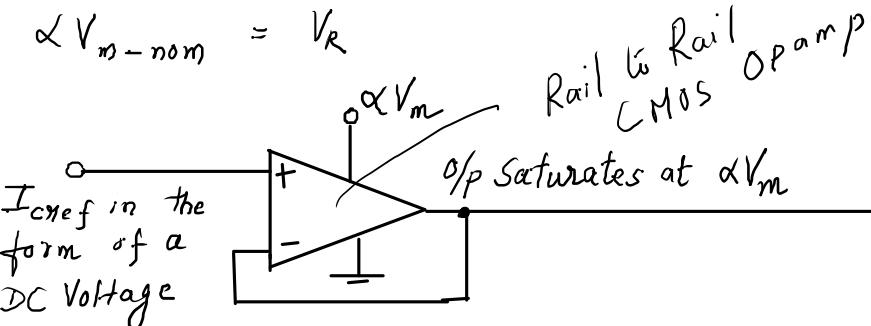Potential Trf + Potential Divider + Full Bridge Rectifier + Capacitor Filter prepares a DC Voltage $= \alpha V_m$ with α such that



The TSC-TCR Static VAr Generator and Control

The TCR Reference Generator Unit

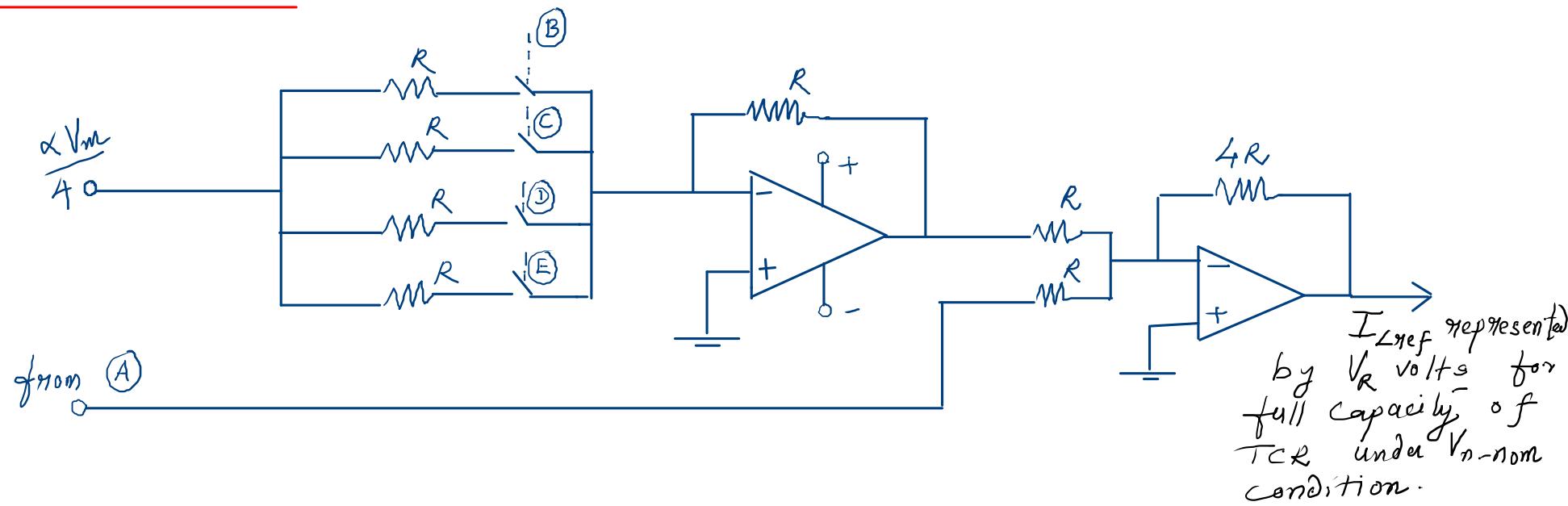

In addition a TCR Internal Controller Unit will also be needed.
It was covered in an earlier lecture.