

- ① Non-Isolated Buck Converter & Non-Isolated Boost Converter
- ⓐ Roles of L and C
- ⓑ Size of L and C when f_s increasing with ΔI_L , ΔV_C is constant

- ⓐ In Non-Isolated Buck Converter,
- L and C both are acts as a voltage Averaging Circuit.
i.e; Inductor and Capacitor (L,C) both are formed Low pass Second order filter.

$$\Delta I_L = \frac{V_{in} - V_o}{L} dT_s = \frac{(1-d)V_o}{f_s L} \quad (\text{Ripple in Inductor Current})$$

$$\Delta V_C = \frac{d(1-d)V_{in}}{8f_s^2 LC} = \frac{(1-d)V_o}{8f_s^2 LC} \quad (\text{Ripple in Capacitor voltage})$$

to reduce the ripple in the Current & voltage L & C values we have to increase.

In Non-Isolated Boost Converter,
L and C are have different roles. Here L (inductor) is used to Convert voltage into Constant current and C is used to remove the AC component across the output.
i.e; C is act like a filter (1st order)

$$\Delta I_L = \frac{dV_{in}}{L f_s}$$

$$\Delta V_C = \frac{dI_o}{f_s C}$$

To reduce the Ripple in the Current, we have to Increase the L value & to decrease the Ripple voltage we have to increase C value.

Here ΔV_C in terms of 1st order of frequency But in Buck Converter it is 2nd order of frequency.

(b) From ΔI_L & ΔV_C equations,
for Buck Converter,
if ΔI_L is constant & ΔV_C is constant and f_s increases
 L and C values are decreases.
i.e; if you increase switching frequency the size of
Inductor and Capacitor will be decreases for given
Peak to Peak ripple in current and voltage.

for Boost Converter,
If ΔI_L is constant & ΔV_C is constant and f_s increases
then L and C values are decreases
i.e; if you increase switching frequency the size of
Inductor & Capacitor will be decreases for given
Peak to Peak ripple in current and voltage.

After writing notes on Buck converter
Buck converter (forward) and boost converter (forward) at last

Notes on Buck converter (forward) and boost converter (forward) at last

Forward converter (forward) and boost converter (forward) at last

Forward converter (forward) and boost converter (forward) at last

Forward converter (forward) and boost converter (forward) at last

Forward converter (forward) and boost converter (forward) at last

Forward converter (forward) and boost converter (forward) at last


Forward converter (forward) and boost converter (forward) at last

Forward converter (forward) and boost converter (forward) at last

Forward converter (forward) and boost converter (forward) at last

Forward converter (forward) and boost converter (forward) at last

③ Buck Converter Specifications

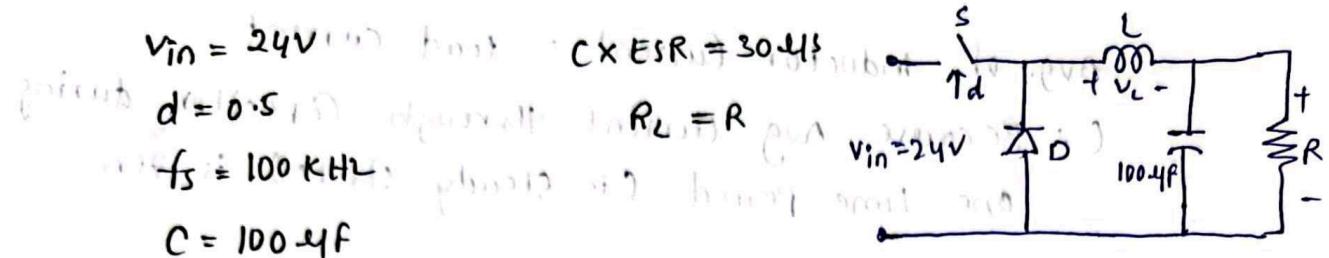


Inductor Current varying between 2.5A and 3.5A
(under steady state)

- i) L ii) R iii) v_o and % P-P ripple in output voltage.

Assumptions:

- ① All Components are Ideal
- ② Switching is Instantaneous
- ③ L is Ideal i.e; zero Core loss, resistance of winding is zero and zero winding Capacitance
- ④ C is ideal i.e; zero ESR and ESL and infinite Parallel resistance
- ⑤ The Converter is in steady state Conduction in CCM with V_{in} that is Pure DC Input voltage.

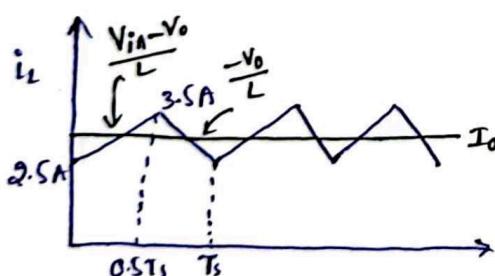Inductor Current is Given with $d=0.5$; $v_o = d V_{in} = 12V$



$$\Delta I_L, \text{Peak to Peak Ripple Current} = 1A = \bar{i}_{L\max} - \bar{i}_{L\min}$$

$$\Delta I_L = \frac{(V_{in}-v_o)}{L} d T_S \quad (\text{In CCM mode})$$

$$1A = \frac{(24-12)(0.5)}{L} \frac{1}{100 \times 10^3}$$

$$L = \frac{12 \times 0.5}{100 \times 10^3} = 0.06 \text{ mH}$$

$$V_o = dV_{in}$$

$$= 0.5 \times 24 = 12V$$

Avg. of Inductor Current = Load current

C: Because Avg Current through Capacitor during one time period (in steady state) is zero

Avg. Value of Inductor Current = I_o (load)

(Load phasor shown)

$$\therefore R = \frac{V_o}{I_o} = \frac{12}{3} = 4\Omega$$

\Rightarrow P-P ripple in output voltage = $\Delta I_L * r_c$

$$C \times ESR = 30\mu s$$

$$C = 100\mu F$$

$$r_c = ESR = \frac{30\mu s}{100\mu F}$$

$$r_c = 0.3\Omega$$

\therefore P-P ripple in output voltage = $0.3 \times 1A$

$$\Delta V_o = 0.3V_{in}$$

$$V_o = 12V$$

\Rightarrow P-P ripple in output voltage = $\frac{30\mu s}{12} = 2.5\%$

= 2.5% of V_o



Half bridge inverter, half bridge inverter

③ Non Isolated Buck Converter

$$V_{in} = 120V$$

$$V_o = 24V$$

operating with a fixed duty ratio, $d = 0.2$

$$f_s = 40\text{ kHz}$$

$$L = 0.48\text{ mH}$$

Output Current in the range $\Rightarrow 0$ to $5A$

Variation of Output DC voltage levels Derivation & Plot ??


$$\text{P-P ripple current through Inductor, } \Delta I_L = \frac{V_{in} - V_o}{L} d T_s \\ = \frac{120 - 24}{0.48 \times 10^{-3}} (0.2) \frac{1}{40 \times 10^{-3}}$$

$$\Delta I_L = 1A$$


i.e; Output Current from $0.5A$ to $5A$, Non Isolated Buck Converter in CCM for given L value. &
at $0.5A$, Buck Converter operates in BCM &
 0 to $0.5A$, Buck Converter operates in DCM

$[\because \text{due to } T_{min} \geq \frac{\Delta f_s}{2} \text{ then Converter operates in CCM}]$
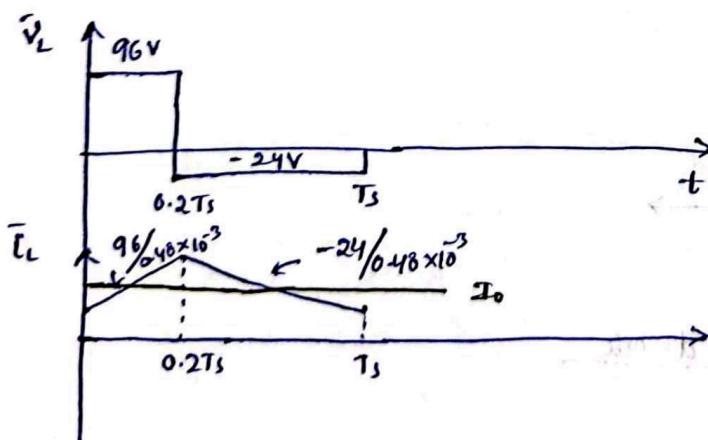
$$V_o = d V_{in} = 24V \text{ for C.C.M [under steady state]}$$



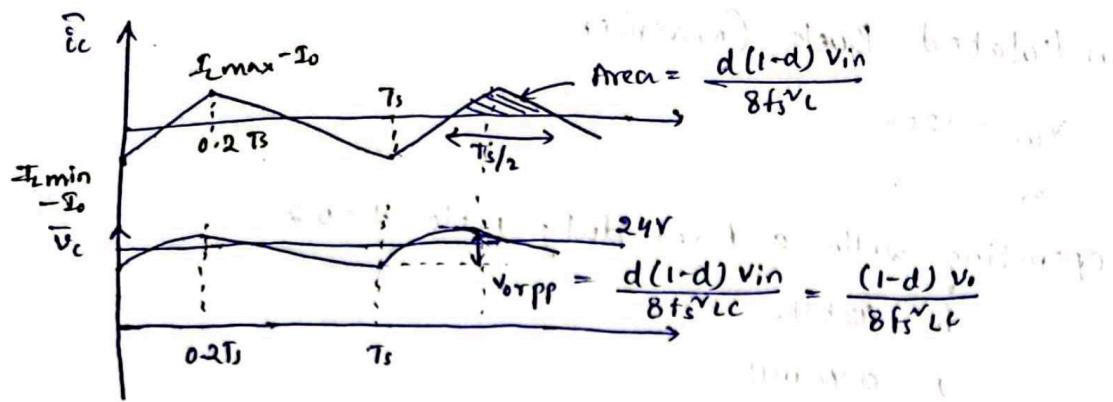
above Graph v_L, i_L for $I_o > 0.5A$ under steady state CCM mode.



Avg output voltage is always 24V in CCM mode

(under Ideal Condition) for $I_0 > 0.5A$

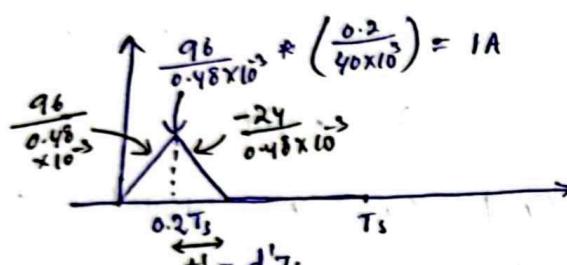Here peak-peak output ripple is inversely proportional to C
 $I_0 < 0.5A$, Converter operates in DCM:



$$(i_{L,Avg})_{DCM} = \left[\frac{1}{2} \left(\frac{V_{in} - V_o}{L} dT_s \right) (d + d')T_s \right] \div T_s$$


$$i_{L,Avg} = \frac{d^2}{(2f_s L)^2} \frac{(V_{in} - V_o)}{d^2} V_{in} = I_0$$

$$\frac{24}{0.48 \times 10^3} \cdot t' = 1A$$

$$t' < 2 \times 10^{-5}$$

$$V_o = \frac{V_{in}}{1 + \frac{2f_s L I_0}{d^2 V_{in}}}$$

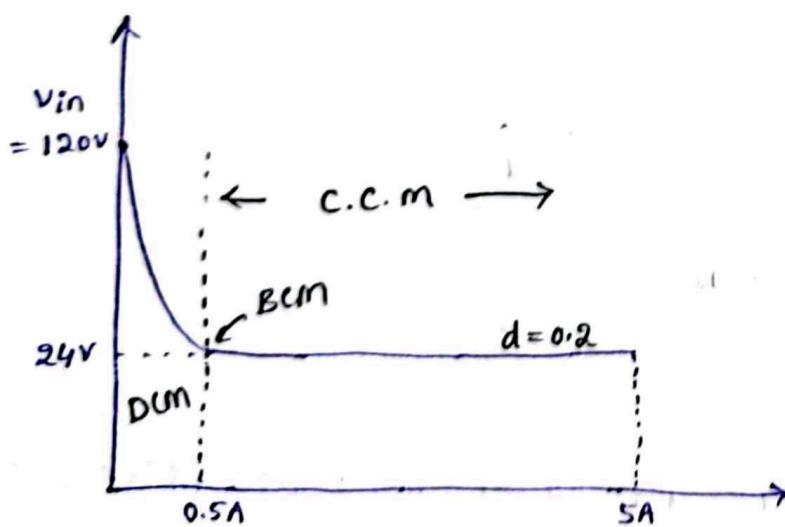If you Substitute $d_0 < 0.5$ then, Relation b/w output & input is non-linear. It shows below characteristics.
at $I_0 = 0A$, $V_o = V_{in}$ Because at $I_0 = 0$ denominator is 1.



④ Boost Converter has specifications as follow

$$V_{in} = 24V ; d = 0.5$$

$$f_s = 100\text{kHz} ; C = 100\mu\text{F}$$



$$C \times \text{ESR} = 30\mu\text{s}$$

steady state Current is periodic &
Raised triangular waveform between 2.5A to 3.5A

Load Resistance, $R_L = R$

find i) L ii) R iii) V_o and % P-P ripple in o/p voltage.

All Components are ideal.

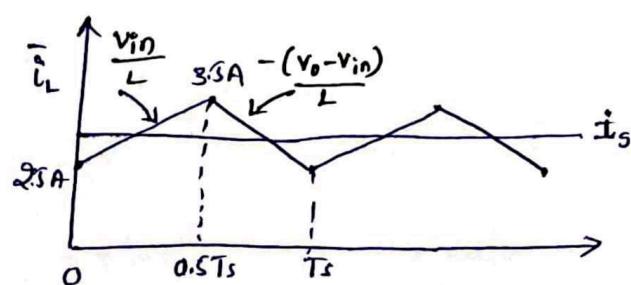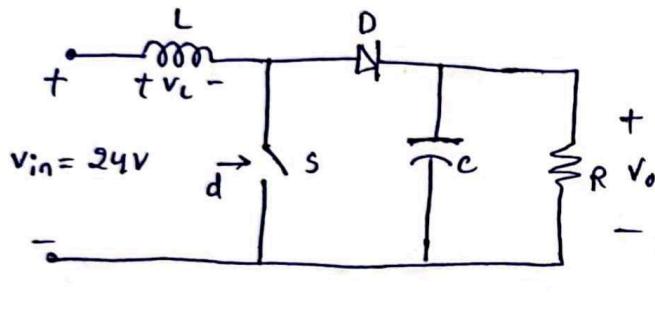

Peak to Peak Inductor Current, $\Delta i_L = 1A = I_{max} - I_{min}$

$$\Delta i_L = \frac{V_{in}}{L} d T_s \quad [\text{ccm under steady state}]$$

$$1A = \frac{24}{L} (0.5) \left[\frac{1}{10^5} \right]$$

$$L = \frac{12}{10^5} = 120\mu\text{H}$$

\therefore Converter operating Continuous conduction mode (CCM)
(Because in Current always above zero)

$$V_o = \frac{1}{1-d} V_{in} = \frac{1}{1-0.5} 24 \\ = 48V$$

Avg. Current of (i_L) Inductor = 3A

$$\text{Load Current, } I_o = (1-d) i_{L \text{ Avg}} \\ = 1/2 \times 3 = 1.5A$$

$$\text{Load Resistance, } R_L = \frac{V_o}{I_o} = \frac{48}{1.5} \\ R = 32\Omega$$

Peak to Peak ripple voltage = $i_{L\max} \times r_{circuit}$

$$C = 100 \mu F \quad \& \quad ESR \times C = 30 \mu S$$

$$ESR = r_L = \frac{30 \mu S}{100 \mu F} = 0.3 \Omega$$

Peak to Peak ripple voltage = 0.3×3.5

$$\text{Total peak to peak current } \Delta V_C = 1.05 \text{ VDC}$$

$$V_o = 48 \text{ V}$$

$$\therefore \text{Peak to peak ripple in output voltage} = \frac{10\%}{48 \text{ V}} = 0.218\%$$

Total load current = 10A



Now, we have to calculate the required value of load

resistor to produce 10A and 48V output.

$$\left(\frac{V_o}{I_o} \right) \text{ or } \frac{48}{10} = 4.8$$

$$\text{Required load} = 4.8 \Omega$$

Now, we have to calculate the output power required.

Output power = $V_o \times I_o$ = 48×10 = 480W

$$\text{Efficiency} = \frac{P_o}{P_i} = \frac{480}{500} = 0.96$$

Efficiency = 96% (In theory)

Now, we have to calculate the input power

Input power = P_i

Input power = $\frac{P_o}{\text{Efficiency}}$ = $\frac{480}{0.96}$ = 500W

⑤ Ideal Buck Converter:

$$V_{in} = 120V$$

$$d = 0.4$$

$$f_s = 50 \text{ kHz}$$

$$L = 576 \mu\text{H}$$

$$C = 10 \mu\text{F}$$

i) $V_o = ?$

ii) $\Delta I_L = ?$


iii) $\Delta V_C = ?$

} @ $I_o = 5A$

ii) $i_s, v_s, i_d, v_d, i_L, v_L, i_C$ and v_C

with $d=0.4$ & $I_o = 5A$

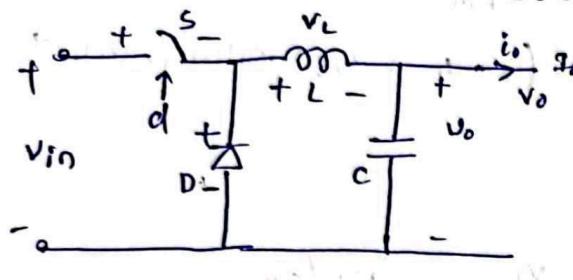iii) Output voltage if Load Current is reduced to $0.2A$ @ $d=0.4$ (Derivation)



$$V_o = d V_{in} = 0.4 \times 120 \\ = 48V$$


P-P Ripple Current in Inductor, $\Delta I_L = \frac{V_{in} - V_o}{L} d T_s$

$$= \frac{120 - 48}{576 \times 10^{-6}} (0.4) \left[\frac{1}{50 \times 10^3} \right] \\ = \frac{28.8}{28.8} = 1A$$

Peak-Peak Ripple Voltage in Capacitor, $\Delta V_C = \frac{1}{2} \left(\frac{T_s}{2} \right) \left[\frac{V_{in} - V_o}{2L} \right] \frac{d T_s}{C}$

$$= \frac{0.5 \times 0.5 \times 0.5}{50 \times 10^3 \times 10 \times 10^{-6}} \\ = 0.25V$$

iv)

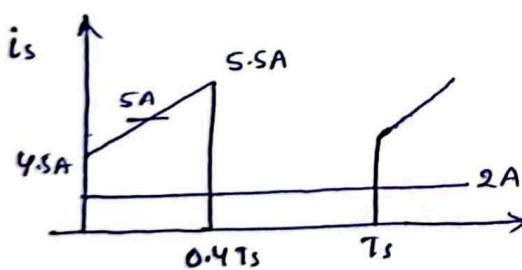

$$\bar{i}_s = 5 \times 0.4$$

$$i_{s\text{Avg}} = 2A$$


$$i_{s\text{RMS}} = \sqrt{\int_0^{0.4} (4.5 + 2.5t)^2 dt}$$


$$= \sqrt{\int_0^{0.4} (4.5)^2 + 6.25t^2 + 22.5t dt}$$

$$= \sqrt{20.25(0.4) + 6.25 \left(\frac{0.4^3}{3} \right) + 22.5 \frac{0.4}{2}}$$

$$= 8.1 + 0.133 + 1.8$$


$$= 3.16 A$$

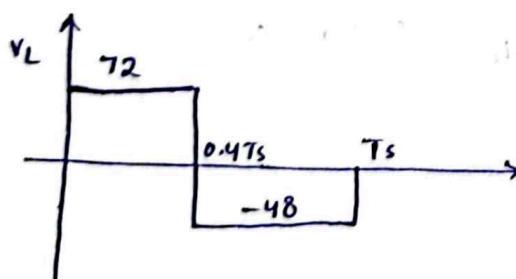

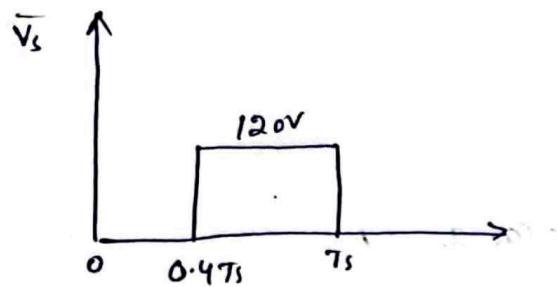

$$\bar{V}_s \text{ Avg} = \frac{120}{Ts} (0.6Ts) = 72V$$

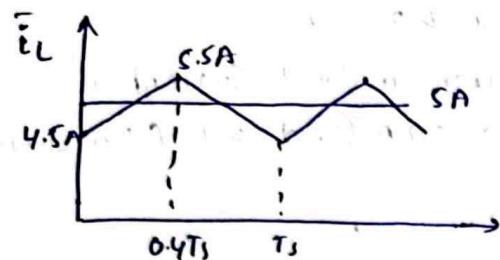
$$\begin{aligned}\bar{V}_s \text{ RMS} &= 120 \sqrt{0.6} \\ &= 92.95V\end{aligned}$$



$$\bar{i}_L \text{ Avg} = 5A$$


$$i_{L \text{ RMS}} \approx 5A$$

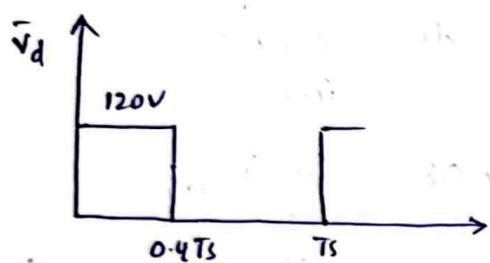$\because \bar{i}_L \text{ and } \bar{V}_s$ orthogonal to each other,




$$\begin{aligned}V_d \text{ Avg} &= 120 (0.4) \\ &= 48V\end{aligned}$$
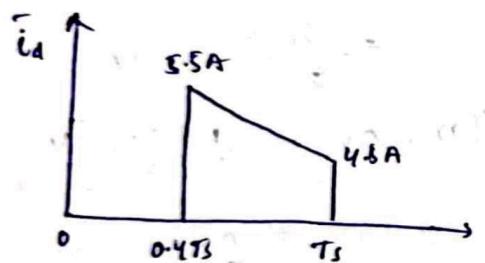
$$\begin{aligned}V_d \text{ RMS} &= 120 \sqrt{0.4} \\ &= 75.89V\end{aligned}$$



$$\begin{aligned}i_d \text{ Avg} &= 5 \times 0.6 \\ &= 3A\end{aligned}$$
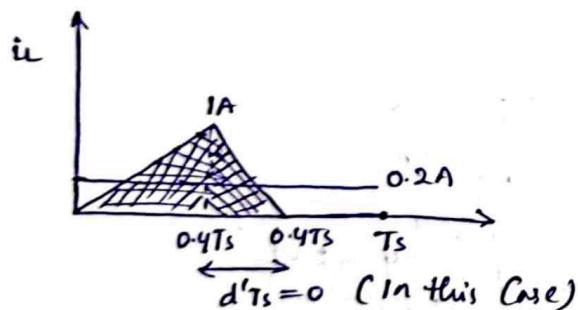
$$\begin{aligned}i_d \text{ RMS} &= 5 \sqrt{0.6} \\ &= 3.87A\end{aligned}$$



$$Ts I_0 = \frac{(d+d') Ts * \Delta I_u}{2} \Rightarrow I_0 = \frac{(d+d') \Delta I_u}{2}$$

$$Ts * 0.2 = \frac{(0.4+d') Ts * 1}{2}$$

$$0.4 = (0.4+d') * 1$$

$$d' = 0$$

$$d' T_s = \frac{V_{in} - V_o}{L} d T_s + V_o / L = \frac{V_{in} - V_o}{V_o} d T_s$$

$$i_{L\text{Avg}} = \left[\frac{1}{2} \left(\frac{V_{in} - V_o}{L} \right) d T_s (d + d') T_s \right] \div T_s$$

$$= \frac{d^2}{2f_s L} \frac{V_{in} - V_o}{V_o} V_{in}$$

$$i_{L\text{Avg}} = I_0$$


$$\frac{d^2}{2f_s L} \left(\frac{V_{in}^2}{V_o} - V_{in} \right) = I_0$$

$$\frac{V_o}{V_{in}^2} = \frac{1}{V_{in} + \frac{2f_s L I_0}{d^2}}$$

$$V_o = \frac{V_{in}}{1 + \frac{2f_s L I_0}{d^2 V_{in}}}$$

$$V_o = \frac{120}{1 + \frac{2(50 \times 10^3)(576 \times 10^{-6})(0.2)}{(0.4)^2 \times 120}}$$

$$V_o = 75V$$

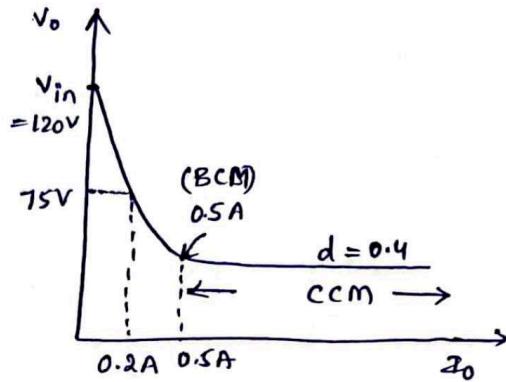

⑥ Buck Converter - ccm design

$$V_{in} = 40V \text{ to } 56V$$

$$V_o = 24V$$

$$I_o = 0.4A \text{ to } 4A$$

Max. P-P ripple in $V_o < 50mV$

Max. P-P ripple in $i_L < 1A$

$$f_s = 40\text{kHz}; \quad r_{cc} = 50\mu s$$

$$d_{max} = \frac{V_o}{V_{in\min}} = \frac{24}{40} = 0.6$$

$$d_{min} = \frac{V_o}{V_{in\max}} = \frac{24}{56} = 0.428$$

$$\Delta I_L = \frac{V_{in} - V_o}{L} d T_s = \frac{V_o (1-d)_{min}}{L f}$$

$$L_{min1} = \frac{24 (1-0.428)}{40 \times 10^3} = 0.343\text{mH}$$

$$L_{min1} = 343\mu H$$

CCM Condition check, L_{min2}

$$0.4 = \frac{V_o (1-d_{min})}{2 L_{min2} f_s}$$

$$L_{min2} = \frac{24 (1-0.428)}{2 \times 0.4 \times 40 \times 10^3}$$

$$= 0.429\text{mH}$$

$$= 429\mu H$$

$$L = \max (L_{min1}, L_{min2})$$

$$L = 429\mu H \text{ for CCM}$$

$$\Delta V_C = \frac{V_o (1-d)}{8 L f' C}$$

$$50 \times 10^{-3} = \frac{24 (1-d_{min})}{8 \times 429 \times 10^{-6} \times 40 \times 40 \times 10^6 \times C}$$

$$C = \frac{24 (1-0.428)}{8 \times 40 \times 40 \times 10^6 \times 10^{-6} \times 429 \times 50 \times 10^{-3}} = 50\text{nF}$$

∴ Electrolytic Capacitor is cured.

$$t_{\text{cure}} = \frac{50 \times 10}{50 \times 70} \times 1000$$

$$50 \text{ mV} = \Delta I_L * R_C$$

$$50 \text{ mV} = 0.8 * R_C$$

$$R_C = \frac{50}{0.8} * 10^3 = 62.5 \text{ m}\Omega$$

from this $R_C * C = 50 \text{ mV}$

$$C = \frac{50 \times 10^{-6}}{62.5 \times 10^{-3}} = 800 \mu\text{F}$$

$$\therefore C \approx 1000 \mu\text{F}$$

③ Given data:




$$IRF540: r_s = 44 \text{ m}\Omega$$

$$MBR10100: r_d = 60 \text{ m}\Omega; V_f = 0.2 \text{ V}$$

$$d = 0.5; r_L = 30 \text{ m}\Omega$$

$$V_{in} = 48 \text{ V}; I_o = 4 \text{ A}$$
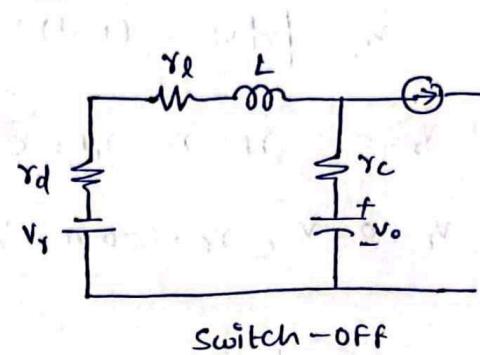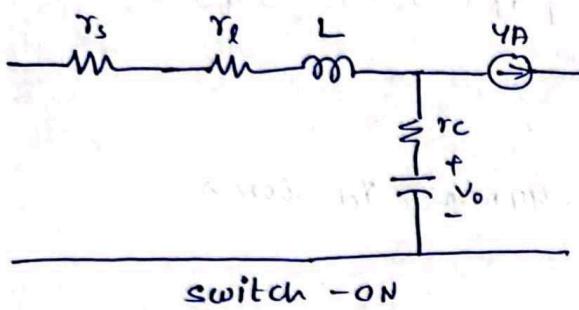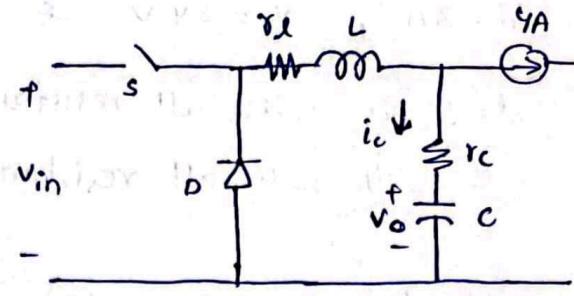
$$L = 429 \text{ mH}; C = 800 \text{ nF}; r_C = 62.5 \text{ m}\Omega$$



$$v_L(t) \approx V_{in} - v_o(t) - (r_s + r_L) i_L(t)$$

$$A_+ = dT_s V_{in} - \int_0^{dT_s} v_o(t) dt - (r_s + r_L) \int_0^{dT_s} i_L(t) dt$$

$$A_- = A_+$$

$$dT_s V_{in} - \int_0^{dT_s} v_o dt - (r_s + r_L) \int_0^{dT_s} i_L dt = \int_{dT_s}^{T_s} v_o dt + (1-d) T_s V_f + (r_d + r_L) \int_{dT_s}^{T_s} i_L dt$$

$$\therefore v_o = [d V_{in} - (1-d) V_f] - r_L i_o - r_s \left(\frac{1}{T_s} \int_0^{T_s} i_L dt \right) - r_d \frac{1}{T_s} \int_{dT_s}^{T_s} i_L dt.$$

$$v_o = [d V_{in} - (1-d) V_f] - [r_L + d r_s + (1-d) r_d] i_o$$

$$\therefore v_o = [0.5(48) - (1-0.5)0.2] - [30 \times 10^{-3} + 0.5(44 \times 10^{-3}) + (1-0.5)60 \times 10^{-3}] 4$$

$$= 24 - 0.1 - 0.328$$

$$= 23.572 \text{ V}$$

⑧

Problem ⑦ $\Rightarrow I_o = 4A, d = 0.5; V_{in} = 48V$

- find Switching power loss in MOSFET = ??

Conduction power loss in MOSFET = ??

$$R_g = 22\Omega$$

IRF540: $r_{ds(on)} = 44m\Omega, C_{gd1} = 450\text{ pF}, C_{gd2} = 125\text{ pF}, C_{gs1} = 2400\text{ pF}$

$C_{gs2} = 1800\text{ pF}, C_{ds1} = 1100\text{ pF}, C_{ds2} = 500\text{ pF}$

Conduction losses = ~~$I^2 R_g$~~

$$= \cancel{\frac{I^2 R_g}{2}} \cancel{(44 \times 10^{-3})}$$

$$= \cancel{\frac{I^2 R_g}{2} \cdot 1100 \cdot 10^{-12}}$$

Switching losses = Switch off losses + Switch on losses.


Switch off losses:

We know that, $V_{gs(crit)} \approx 3.76V$
(from datasheet)

$$t_2 = \frac{V_{in} - V_{ds(crit)}}{\frac{V_{gs(crit)}}{R_g C_{gd}}} \approx \frac{V_{in}}{V_{gs(crit)}} R_g C_{gd2}$$

$$t_2 = \frac{48}{3.76} 22 \times 125 \times 10^{-12}$$

$$= 35.10 \text{ ns}$$

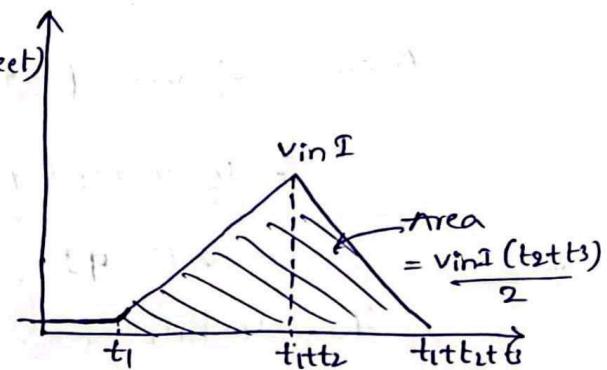

$$t_3 = \tau \ln \frac{V_{gs(crit)}}{V_T} = R_g (C_{gd2} + C_{gs2}) \ln \frac{V_{gs(crit)}}{V_T}$$

$$= 22 (125 + 1800) \times 10^{-12} \ln \left[\frac{3.76}{2.5} \right]$$

$$= 17.28 \text{ ns}$$

$$\text{Area} = \frac{1}{2} V_{in} I (t_2 + t_3)$$

$$= \frac{1}{2} 48 \times 4 \times (17.28 + 35.10) \times 10^{-9}$$

$$= 5.028 \times 10^{-6}$$

$$f_s = 40 \text{ kHz}$$

\therefore Power loss due to switch-off operations

$$= 40 \text{ kHz} * 5.028 \text{ J}$$


$$= 0.201 \text{ W}$$

Switch ON losses:

Here schottky diode is used & there is no reverse recovery i.e; $t_3 = 0$ (in below graph)

so, we know that,
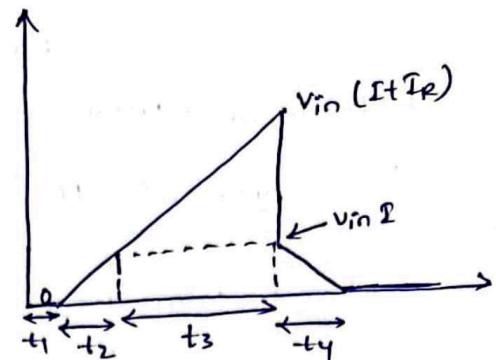
$$\begin{aligned} t_2 &= R_g C_{iss2} \ln \frac{V - V_T}{V - V_{gscr}} \\ &= 22 (125 + 1800) \times 10^{-12} \ln \left[\frac{10 - 2.5}{10 - 3.76} \right] \\ &= 7.789 \text{ ns} \end{aligned}$$



$$\begin{aligned} t_4 &= \left(\frac{v_{in} - V_{dscr}}{V - V_{gscr}} \right) R_g C_{gd2} \\ &= \left(\frac{48 - 1.26}{10 - 3.76} \right) 22 \times 125 \times 10^{-12} \\ &= 20.59 \text{ ns} \end{aligned}$$

$$\begin{aligned} \text{Area} &= \frac{1}{2} v_{in2} \left(\frac{t_2 + t_4}{2} \right) \\ &= \frac{1}{2} 48 * 4 (7.789 + 20.598) \times 10^{-9} \\ &= 2.725 \mu\text{J} \end{aligned}$$

$$f_s = 40 \text{ kHz}$$

Power loss due to Switch-on operations

$$\begin{aligned} &= 40 \text{ kHz} * 2.725 \times 10^{-6} \\ &= 0.109 \text{ W} \end{aligned}$$

Total switching power loss in MOSFET

$$\begin{aligned} &= 0.201 + 0.109 \\ &= 0.31 \text{ watt} \end{aligned}$$

⑧ Converter Spec's:

$$I_o = 3A \quad v_o = 24V \quad & \quad v_{in} = 40V$$

$d = ?$ i) with all resistances & v_r ignored

ii) with all resistances & v_r included.

We know that, from Ans ⑦

$$v_o = [d v_{in} - (1-d) v_r] - [r_L + d r_S + (1-d) r_D] I_o$$

Case: i) $v_r = 0$; $r_L = r_S = r_D = 0$

ii) $v_r = 0.2V$, $r_L = 30m\Omega$, $r_S = 44m\Omega$, $r_D = 60m\Omega$

$$i) \quad v_o = d v_{in}$$

$$24 = d(40)$$

$$d = \frac{24}{40} = 0.600$$

$$ii) \quad v_o = [d \times 40 - (1-d) 0.2] - [30 \times 10^{-3} + d(44 \times 10^{-3}) + (1-d) 60 \times 10^{-3}] 3$$

$$24 = 40d - 0.2 + 0.2d - (90 \times 10^{-3}) - d(132 \times 10^{-3}) - (180 \times 10^{-3}) + (180 \times 10^{-3})d$$

$$24 = 40d - 0.2 + 0.2d - 0.27 + 0.048d$$

$$24.47 = 40.248d$$

$$d = \frac{24.47}{40.248}$$

$$d = 0.6079$$

⑩ Boost Converter - ccm design

$$V_{in} = 10.5 \text{ to } 12.5 \text{ V}$$

$$V_o = 24 \text{ V}$$


$$I_o = 1 \text{ A to } 3 \text{ A}$$

$$\Delta V_o < 200 \text{ mV}$$

$$\Delta i_L < 1 \text{ A}$$

$$f_s = 40 \text{ kHz}$$

$$r_c C = 30 \mu\text{s}$$

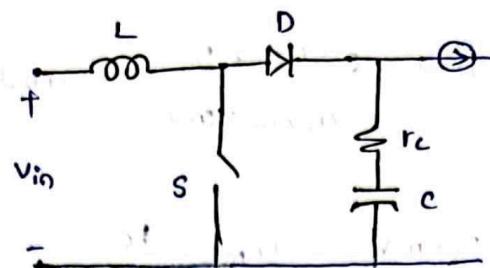

$$d_{min} = 1 - \frac{12.5}{24} = 0.479$$

$$d_{max} = 1 - \frac{10.5}{24} = 0.5625$$

$d_{min} < 0.5$ and $d_{max} > 0.5$

Take $d=0.5$ in Calculating L_{min1}

$$I_A \geq \frac{d(1-d)V_o}{f_s L} = \frac{0.25 * 24}{40 * 1000 * L}$$

$$L = 150.4 \text{ H}$$

Another value of L is L_{min2} obtained by CCM.

$$I_o \geq \frac{d(1-d)V_o}{2f_s L}$$

$$I \geq \frac{0.479(1-0.479)24}{2 * 40 * 10^3 * L}$$

$$L = 39.4 \text{ H}$$

Choose $L = \max(L_{min1} \text{ & } L_{min2})$

$$\approx 150.4 \text{ H}$$

$$d_{min} \text{ & } d_{max} > \frac{1}{2}$$

so, d_{min} we taken
for I_o Calculation.

Calculate C value,

$$\Delta V_C = 200mV = \frac{dI_0}{f_S C} \quad [\because \text{here } d_{\max} \& I_{0\max} \text{ for max } C]$$

$$C \geq \frac{0.5625 \times 3}{40 \times 10^3 \times 0.2} = 210.4 \mu F \quad (\text{more than } 20 \mu F \\ \text{so electrolyte cap})$$

$$\text{So, } 200mV = i_{L\max} r_C$$

$$i_{L\max} = \frac{I_0}{1-d} + \frac{1}{2} \frac{d(1-d)V_0}{f_S L}$$
$$= \frac{3}{1-0.5625} + \frac{1}{2} \frac{0.5625 (1-0.5625) 24}{40 \times 10^3 \times 10 \times 10^{-6}}$$
$$= 6.857 + 0.4921$$

$$i_{L\max} = 7.349 A$$

$$200 \times 10^3 = 7.349 \times r_C$$

$$r_C = 27.21 m\Omega$$

$$C \geq \frac{30 \times 10^{-6}}{27.21 \times 10^{-3}}$$

$$C = 1.1 mF$$

⑪ Given data: (Boost Converter)

$$\text{IRF 540 ; } r_s = 44 \text{ m}\Omega \text{ (100V/23A)} \quad \text{i) } v_{in} = 10.5 \text{ V} \quad \text{ii) } v_{in} = 12.5 \text{ V}$$

$$I_o = 1 \text{ A} \quad I_o = 1 \text{ A}$$

$$\text{MUR 820 ; } V_f = 0.5 \text{ V}, r_d = 40 \text{ m}\Omega$$


$$\text{iii) } v_{in} = 10.5 \text{ V} \quad \text{iv) } v_{in} = 12.5 \text{ V}$$

$$r_L = 50 \text{ m}\Omega \quad I_o = 3 \text{ A} \quad I_o = 3 \text{ A}$$


v_o Versus duty ratio in the range $d=0.5$ to $d=0.8$

Duty ratio variation range that is needed to maintain output voltage at 24V

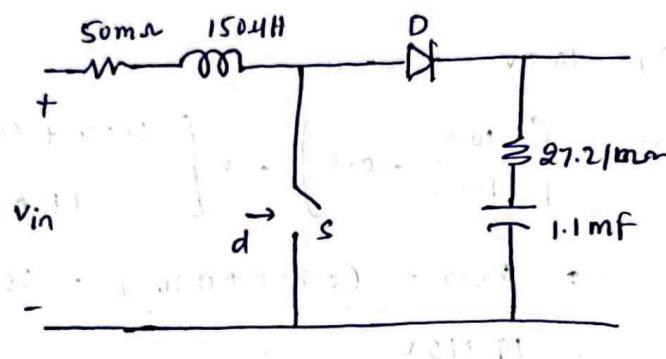from Q10. $C = 1.1 \text{ mF}$ & $L = 1504 \text{ H}$; $r_c = 27.21 \text{ m}\Omega$



i) S-ON

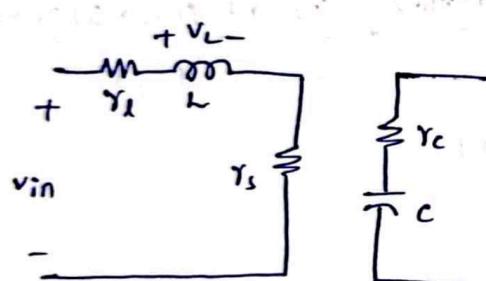

$$v_L(t) = v_{in} - i_L(t) [r_L + r_s]$$


$$A_f = v_{in} d T_s - (r_L + r_s) \int_0^{d T_s} i_L(t) dt$$

$$A_f = A_-$$

$$v_{in} d T_s - (r_L + r_s) \int_0^{d T_s} i_L(t) dt = (v_o + v_f - v_{in} - r_c I_o) (1-d) T_s + (r_L + r_d + r_c) \frac{I_o}{T_s}$$

$$\therefore v_o = \left[\frac{v_{in}}{1-d} - v_f \right] - I_o \left[\frac{r_L + d r_s}{(1-d) v} + \frac{r_d + d r_c}{1-d} \right]$$

ii) S-OFF

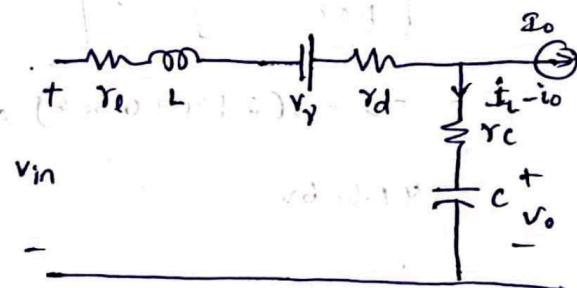

$$v_L(t) = v_{in} - i_L(t) [r_L + r_d + r_c] - v_f$$

$$- v_o + I_o r_c$$

$$A_- = (v_{in} - v_o - v_f + I_o r_c) (1-d) T_s$$

$$- (r_L + r_d + r_c) \int_{d T_s}^{T_s} i_L(t) dt$$

$$i) V_{in} = 10.5V, I_o = 1A$$

$$\underline{d=0.5} \quad v_o = \left[\frac{10.5}{1-0.5} - 0.5 \right] - 1 \left[\frac{\frac{50 \times 10^{-3}}{(1-0.5)} + (0.5 \times 44 \times 10^{-3})}{(1-0.5)^2} + \frac{\frac{40 \times 10^{-3}}{(1-0.5)} + (0.5 \times 27.21 \times 10^{-3})}{1-0.5} \right]$$

$$= 20.5 - (0.288 + 0.107) = 20.5 - 0.395$$

$$= 20.104V$$

$$\underline{d=0.8} \quad v_o = \left[\frac{10.5}{1-0.8} - 0.5 \right] - 1 \left[\frac{\frac{50 \times 10^{-3}}{(1-0.8)} + (0.8 \times 44 \times 10^{-3})}{(1-0.8)^2} + \frac{\frac{40 \times 10^{-3}}{(1-0.8)} + (0.8 \times 27.21 \times 10^{-3})}{1-0.8} \right]$$

$$= 52 - (2.130 + 0.308) = 52 - 2.438$$

$$= 49.562V$$

$$ii) V_{in} = 10.5V, I_o = 3A$$

$$\underline{d=0.5} \quad v_o = \left[\frac{10.5}{1-0.5} - 0.5 \right] - 3 \left[\frac{\frac{50 \times 10^{-3}}{(1-0.5)} + (0.5 \times 44 \times 10^{-3})}{(1-0.5)^2} + \frac{\frac{40 \times 10^{-3}}{(1-0.5)} + (0.5 \times 27.21 \times 10^{-3})}{1-0.5} \right]$$

$$= 20.5 - 3(0.288 + 0.107) = 20.5 - 1.185$$

$$= 19.315V$$

$$\underline{d=0.8} \quad v_o = \left[\frac{10.5}{1-0.8} - 0.5 \right] - 3 \left[\frac{\frac{50 \times 10^{-3}}{(1-0.8)} + (0.8 \times 44 \times 10^{-3})}{(1-0.8)^2} + \frac{\frac{40 \times 10^{-3}}{(1-0.8)} + (0.8 \times 27.21 \times 10^{-3})}{1-0.8} \right]$$

$$= 52 - 3(2.130 + 0.308) = 52 - 7.314$$

$$= 44.686V$$

$$iii) V_{in} = 12.5V, I_o = 1A$$

$$\underline{d=0.5} \quad v_o = \left[\frac{12.5}{1-0.5} - 0.5 \right] - 1 \left[\frac{\frac{50 \times 10^{-3}}{(1-0.5)} + (0.5 \times 44 \times 10^{-3})}{(1-0.5)^2} + \frac{\frac{40 \times 10^{-3}}{(1-0.5)} + (0.5 \times 27.21 \times 10^{-3})}{1-0.5} \right]$$

$$= 24.5 - 0.395$$

$$= 24.105V$$

$$\underline{d=0.8} \quad v_o = \left[\frac{12.5}{1-0.8} - 0.5 \right] - 1 \left[\frac{\frac{50 \times 10^{-3}}{(1-0.8)} + (0.8 \times 44 \times 10^{-3})}{(1-0.8)^2} + \frac{\frac{40 \times 10^{-3}}{(1-0.8)} + (0.8 \times 27.21 \times 10^{-3})}{1-0.8} \right]$$

$$= 62.5 - 2.348$$

$$= 60.062V$$

$$iv) V_{in} = 12.5V, I_0 = 3A$$

$$\underline{d=0.5} \quad v_o = \left[\frac{12.5V}{1-0.5} - 0.5 \right] - 3 \cdot \left[\frac{\frac{50 \times 10^3 + (0.5 \times 44 \times 10^3)}{(1-0.5)^2} + \frac{40 \times 10^3 + (0.5 \times 27.21 \times 10^3)}{1-0.5}}{1-0.5} \right]$$


$$= 24.5 - 1.185$$

$$= 23.315V$$

$$\underline{d=0.8} \quad v_o = \left[\frac{12.5}{1-0.8} - 0.5 \right] - 3 \cdot \left[\frac{\frac{50 \times 10^3 + (0.8 \times 44 \times 10^3)}{(1-0.8)^2} + \frac{40 \times 10^3 + (0.8 \times 27.21 \times 10^3)}{1-0.8}}{1-0.8} \right]$$

$$= 62.5 - 7.314$$

$$= 55.186V$$

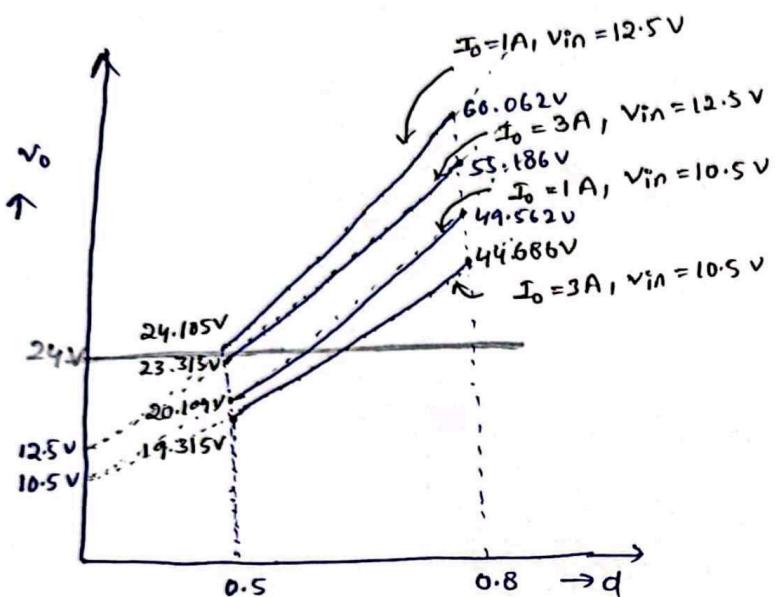

(12) Given data:

Problem no. 11

$$I_0 = 3A, V_0 = 24V$$

$$V_{in} = 12V$$

- i) Conduction losses in the switch & Diode.
- ii) switching losses in the inductor &
- iii) Conduction losses in inductor & Capacitor.
 $d = 0.52$ from Prob (1) from graph.
- iv) RMS value of MOSFET Current $I_{DS(\text{rms})} = I_0 / (1-d)$

$$= 3 / (1 - 0.52) \sqrt{0.52}$$

$$= 4.51A$$

ON state resistance of MOSFET $r_{ds(on)} = 44m\Omega$

$$\begin{aligned} \text{Conduction losses on MOSFET} &= I_{\text{rms}}^2 r_{ds(on)} \\ &= (4.51)^2 \times 44 \times 10^{-3} \\ &= 0.8937W \end{aligned}$$

RMS value of diode current $I_{D(\text{rms})} = I_0 / (1-d)$

$$\begin{aligned} &= 3 / (1 - 0.52) \sqrt{0.52} \\ &= 4.33A. \end{aligned}$$

ON state resistance of diode, $r_d = 40m\Omega$

$$\begin{aligned} \text{Conduction loss on diode} &= 4.33^2 \times 40 \times 10^{-3} \\ &= 0.75W \end{aligned}$$

v) for switch off losses

$$V_{DS} = V_0 = 24V$$

$$I = I_0 / (1-d) = 3 / (1 - 0.52) = 6.25A$$

$$R_g = 22\Omega \text{ & } C_{gd2} = 125\text{fF}$$

$$V_{gscr} = 4.2 V$$

$$V_T = 2.5 V$$

$$V_{dscre} = 1.5 V$$

$$t_2 = \frac{V_{DS}}{V_{gscr}} R_g C_{gd} = \frac{24}{4.2} \times 22 \times 125 \times 10^{-12} \\ = 15.71 \text{ ns}$$

$$t_3 = R_g (C_{gs2} + C_{gd2}) \ln \frac{V_{gscr}}{V_T} \\ = 22 \times (1.800 + 125) \times 10^{-12} \ln \left[\frac{4.2}{2.5} \right] \\ = 21.97 \text{ ns}$$

$$\text{Turn off loss} = \frac{1}{2} V_{DS} I (t_2 + t_3) f_s$$

$$= \frac{1}{2} (24 \times 6.25) \times (15.71 + 21.97) \times 10^9 \times 40 \times 10^3 \\ = 0.11304 W$$

for switch on losses

$$T_F = 20 \text{ ns} \quad \& \quad I = 1 A$$

$$Q = 20 \text{ ns} * A$$

$$E_{on} = V_{DS} I \left[T_F + \frac{V_{DS} - V_{dscre}}{V_T - V_{gscr}} \times \frac{R_g C_{rss2}}{2} \right] \\ = 24 \times 6.25 \left[20 \times 10^{-9} + \frac{24 - 1.5}{10 - 4.2} \times \frac{22 \times 125 \times 10^{-12}}{2} \right] \\ = 3.8 \times 10^{-6}$$

$$\text{Turn on loss.} = E_{on} f_s$$


$$= 3.8 \times 10^{-6} \times 40 \times 10^3 \\ = 0.152 W$$

$$\text{Total switching loss} = 0.1130 + 0.152 \\ = 0.26504 W$$

$$\text{iii) RMS value of inductor current} = \frac{I_0}{\sqrt{1-d}} = \frac{3}{\sqrt{1-0.52}} \\ = 6.25 A$$

$$r_L = 50 m\Omega$$
$$\text{Conduction loss in inductor} = 6.25^2 \times 50 \times 10^{-3} \\ = 1.95 W$$

iv) Capacitor Current

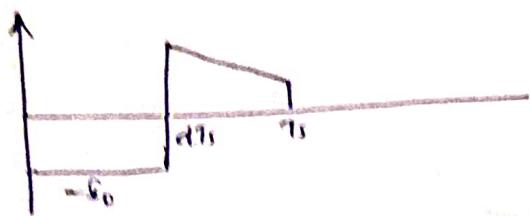

RMS value of Capacitor Current

$$= \frac{I_0}{\sqrt{1-d}} + \left[\frac{I_0}{1-d} - I_0 \right] \sqrt{1-d}$$

$$= 3\sqrt{0.52} + \left[\frac{2}{1-0.52} - 3 \right] \sqrt{1-0.52}$$

$$\approx 4.415 \text{ A}$$

$$T_c = 0.02721$$


$$\begin{aligned}\text{Capacitor Conduction losses} &= 4.415 * 0.02721 \\ &= 0.5304 \text{ W}\end{aligned}$$

(13)

1. Converter

Buck Converter spec's

36V/5V, 10A

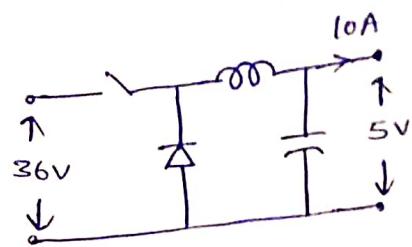MOSFET : 60V, 25A, 40m Ω [designed]
: 300V, 75A, 20m Ω [available]

frequent MOSFET Burnout of the MOSFET due to Gate driver voltage, Parasitic Components (Inductance, Capacitance). i.e; New MOSFET have more Capacitances (C_{iss} , C_{oss} , C_{rdss}) compared to older MOSFET it causes more time taken for switching ON & switching OFF. This time causes increases the switching losses in the circuit (i.e; MOSFET losses) it causes over heating. One more reason is Parasitic Components. i.e; this Parasitic Inductance & Capacitance produce the damping i.e; this damping causes extra losses in the circuit so it produces the heating.

Problem Solutions:

- 1) Use proper heat sinks Based on rating & thermal effects.
- 2) Use Snubber circuit to protect from over heating.
- 3) Give/design Proper Gate driver voltage/circuit.

(14) 12V/120V Converter

$$I_o = 0.5A$$

Designed Converter: Boost


$$d = 0 \text{ to } 1 \quad \text{Max } V_o = 50V \text{ @ } I_o = 0.5A.$$

For 12V/120V, $I_o = 0.5A$ conversion, Boost topology is not suitable. Because you want 120V as output with 12V input. i.e; 10 times of input voltage. But you will get maximum output at Practical. Boost topology is 4-8 times of input voltage.

In Boost Converter,

We know that,
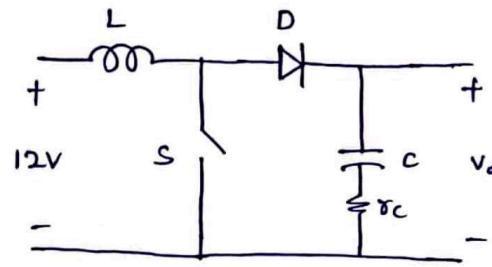
$$V_o = \left[\frac{V_{in}}{1-d} - V_r \right] - I_o \left[\frac{r_L + d r_S}{(1-d)^2} + \frac{r_D + d r_C}{1-d} \right] \quad \text{--- (1)}$$



In practical,

$$V_r \approx 0.2V$$

$$r_L, r_S, r_D \approx 10's \text{ to } 100's \text{ of milli ohms.}$$


$$\text{And your } V_{in} = 12V, I_o = 0.5$$

If you placed above values in eq(1) and you will get very the duty ratio then you will get V_{max} as 5-8 times. ~~That's why~~ you are getting 50V as V_{max} .

i.e; If you draw the graph between V_o vs d for fixed

$$V_{in} = 12V \text{ & } I_o = 0.5A$$

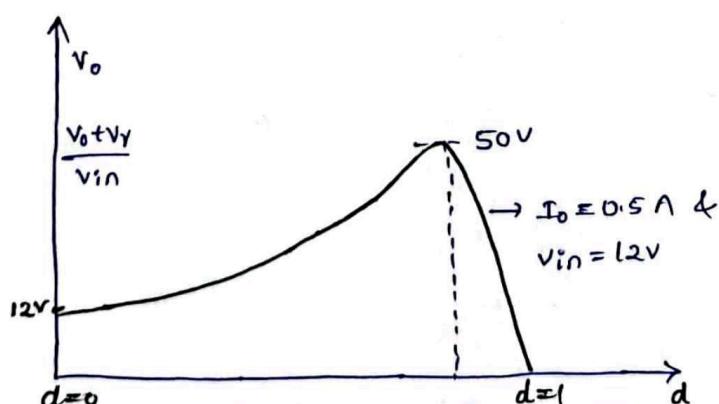You are getting 50V output at duty ratio near to 1.




(Is)

$$\left. \begin{array}{l} 120V = V_{in} \\ 24V = V_o \end{array} \right\} \text{Buck Converter}$$

$$d = 0.2 ; f_s = 20 \text{ kHz}$$

$$L = 0.48 \text{ mH}$$

$$I_o = 0.5 \text{ A}$$

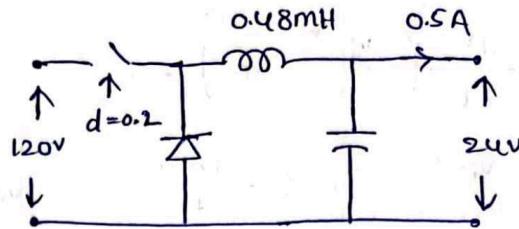

Ideal Components

from Buck Converter, Inductor Basic Principle (at steady state)

$$\Delta I_L = \frac{V_{in} - V_o}{L} dTs$$

$$\Delta I_L = \frac{120 - 24}{0.48 \times 10^{-3}} * \frac{0.2}{20 \times 10^{-3}}$$

$$= 2 \text{ A}$$

But in Query I_0 is given 0.5 A

i.e; Minimum Current of I_0 ,

to maintain Converter in CCM is

$I_{min} > \frac{\Delta I_L}{2}$ i.e; $I_{min} > 1 \text{ A}$ then Converter operates in CCM.

Here, $I_0 = 0.5 \text{ A}$ i.e; Converter operates in DCM

so, DCM (Discontinuous Conduction)

From the graph,



$$d'Ts = \frac{V_{in} - V_o}{L} dTs \div \frac{V_o}{L}$$

$$= \frac{V_{in} - V_o}{V_o} dTs$$

$$(i)_{avg} = \frac{\text{Area of Triangle}}{\text{Total time}}$$

$$= \left[\frac{1}{2} \left(\frac{V_{in} - V_o}{L} dTs \right) (d + d') Ts \right] \div Ts$$
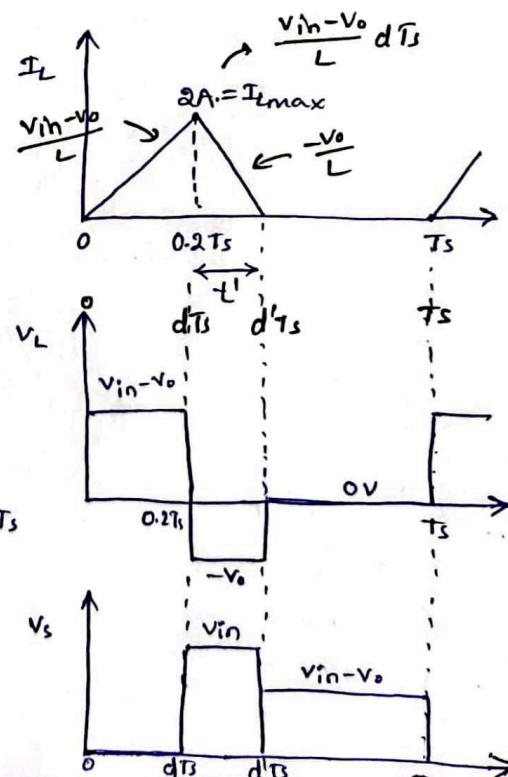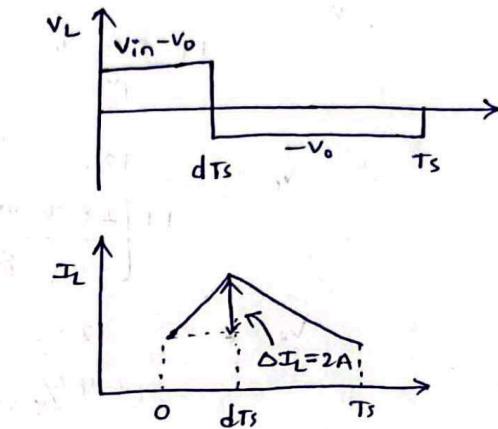
$$(i)_{avg} = \frac{d'}{2f_s L} \left(\frac{V_{in} - V_o}{V_o} \right) V_{in}$$



This must be $I_o = \text{Avg. Load Current}$

$$\frac{dV}{2fSL} \left(\frac{v_{in}}{V_o} - v_{in} \right) = I_o$$


$$\frac{V_o}{V_{in}} = v_{in} + \frac{2fSL I_o}{d^2}$$

$$\frac{V_o}{V_{in}} = \frac{1}{v_{in} + \frac{2fSL I_o}{d^2}}$$

$$V_o = \frac{v_{in}}{1 + \frac{2fSL I_o}{d^2 v_{in}}}$$

$$\therefore V_o = \frac{120}{1 + \left[\frac{2 \times 20 \times 10^3 + 0.48 \times 10^{-3} \times 0.5}{(0.2)^2 \times 120} \right]}$$
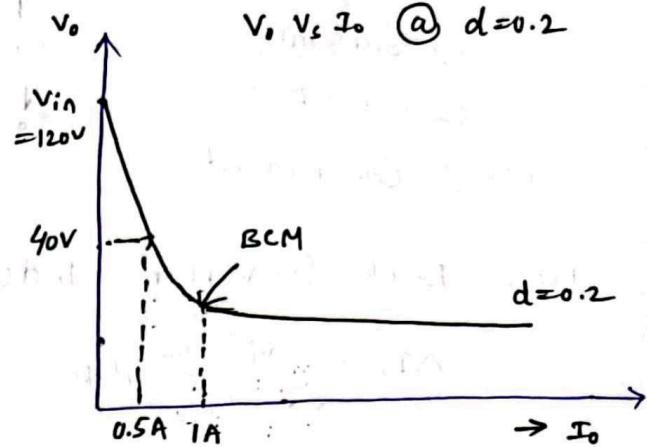
$$V_o = \frac{120}{1 + 9.6/4.8} = \frac{120}{3} = 40V$$



(16)

Buck Converter

$$V_{in} = 48V ; V_o = 12V ; I_o = 10A$$

$$L = 100 \mu H ; f_s = 20kHz$$

$$V_{GS} = 7.5V ; 48A = I_D ; V_T = 3.5V$$

$$V_G = 12V ; R_g = 4\Omega ; C_{iss1} = 2000\text{ pF} ; C_{iss2} = 1300\text{ pF}$$

$$C_{rss1} = 600\text{ pF} ; C_{rss2} = 200\text{ pF} ; C_{oss1} = 1200\text{ pF} ; C_{oss2} = 400\text{ pF}$$

$$1.24 \text{ m}^2/\text{A} = T$$

- (a) Switching delays in the voltage across the diode.
 (b) find switching power loss ?? (relevant waveforms & calculations)

Saturation Drain Current, I_D

$$I_D = \frac{\beta}{2} (V_{GS} - V_T)^2$$

\therefore from Quay & Semiconductor Physics.

$$48 = \frac{\beta}{2} (7.5 - 3.5)^2$$

$$\beta = 48/8 = 6$$

~~Ohmic region~~ Drain Current, I_D

$$I_D \approx \frac{\beta}{2} (V_{GS} - V_T - \frac{V_{DS}}{2}) V_{DS}$$

$$10 = 6 \left(7.5 - 3.5 - \frac{V_{DS,ON}}{2} \right) V_{DS,ON}$$


~~$V_{DS,ON} = 0.44V$~~

for $I_D = 10A ; V_{GS} = V_{GSCR} ; V_T = 3.5V$

$$10 = \frac{\beta}{2} (V_{GSCR} - 3.5)^2$$

$$V_{GSCR} = 5.325V \quad [\text{for } V_{GS} = 12V \text{ & } I_D = 10A]$$

$$V_{DS,CR} = 2.125V$$

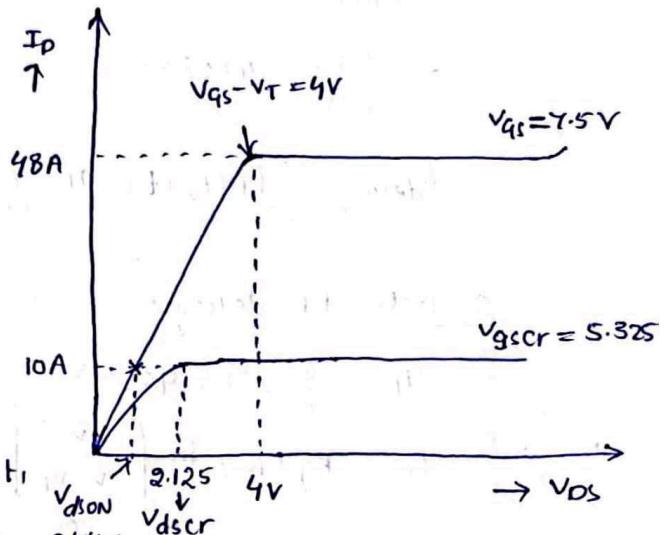

Switching delays in the voltage across diode:

Switch ON delay:

$$t_1 = \gamma \ln \frac{V}{V_{gscr}}$$

$$= R_g (C_{gs1} + C_{ds1}) \ln \frac{V}{V_{gscr}}$$

$$= 47 (2000 \times 10^{-12}) \ln \left[\frac{12}{5.325} \right]$$

$$= 76.37 \text{ ns}$$

$$t_2 \approx \frac{V_{in}}{V_{gscr}} R_g C_{gd}$$

$$= \frac{48}{5.325} (47 \times 200 \times 10^{-12}) = 84.73 \text{ ns}$$

$$t_{\text{delay}} = t_1 + t_2 + t_3 = 76.37 + 84.73 + 25.64 = 186.74 \text{ ns}$$

$$t_3 = \gamma \ln \frac{V_{gscr}}{V_T}$$

$$t_3 = 47 \times 1300 \times 10^{-12} \ln \left[\frac{5.325}{9.5} \right] = 25.64 \text{ ns}$$

Switch OFF delay:

$$\gamma_f = \frac{Q}{I} = 1.24 \text{ s}$$

$$t_1 = R_g C_{iss2} \ln \left[\frac{V}{V - V_T} \right]$$

$$= 47 \times 1300 \times 10^{-12} \ln \left[\frac{12}{12 - 3.5} \right] = \boxed{21.06 \text{ ns}}$$

$$t_2 = R_g C_{iss2} \ln \left[\frac{V - V_T}{V - V_{gscr}} \right]$$

$$= 47 \times 1300 \times 10^{-12} \ln \left[\frac{12 - 3.5}{12 - 5.325} \right] = 14.76 \text{ ns}$$

$$t_3 = \sqrt{2 \gamma_f t_2} - t_2$$


$$= \sqrt{2(1.2 \times 10^{-6})(14.76 \times 10^{-9})} - (14.76 \times 10^{-9}) = 173.45 \text{ ns}$$

$$t_4 = \frac{V_{in} - V_{dscr}}{V - V_{gscr}} * R_g C_{iss2}$$

$$= \frac{48 - 2.125}{12 - 5.325} * 47 \times 200 \times 10^{-12} = 64.6 \text{ ns}$$

$$t_{\text{delay}} = t_1 + t_2 + t_3 + t_4$$
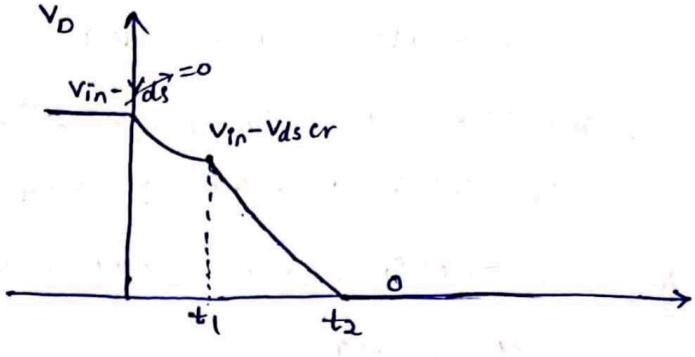
$$= (21.06 + 14.76 + 173.45 + 64.6) \text{ ns} = 273.81 \text{ ns}$$



(b) Switch ON

Calculation already done before part.


$$I + I_R = I \sqrt{\frac{2T_F}{T_2}} \\ = 10 \sqrt{\frac{2(1.2 \times 10^{-6})}{(14.76 \times 10^{-9})}} \\ = 127.51 \text{ A}$$

$$E_{on} = 48 \times 10 \left[1.2 \times 10^{-6} + \frac{48 - 2.125}{12 - 5.325} \times \frac{47 \times 200 \times 10^{-12}}{2} \right] \\ \therefore E_{on} = v_{in} I \left[T_F + \frac{v_{in} - v_{ds(on)}}{v - v_{gscr}} \frac{r_g C_{rssL}}{2} \right] v_{diode}$$

$$= 0.591 \text{ mJ}$$

Power loss at 20 kHz is,
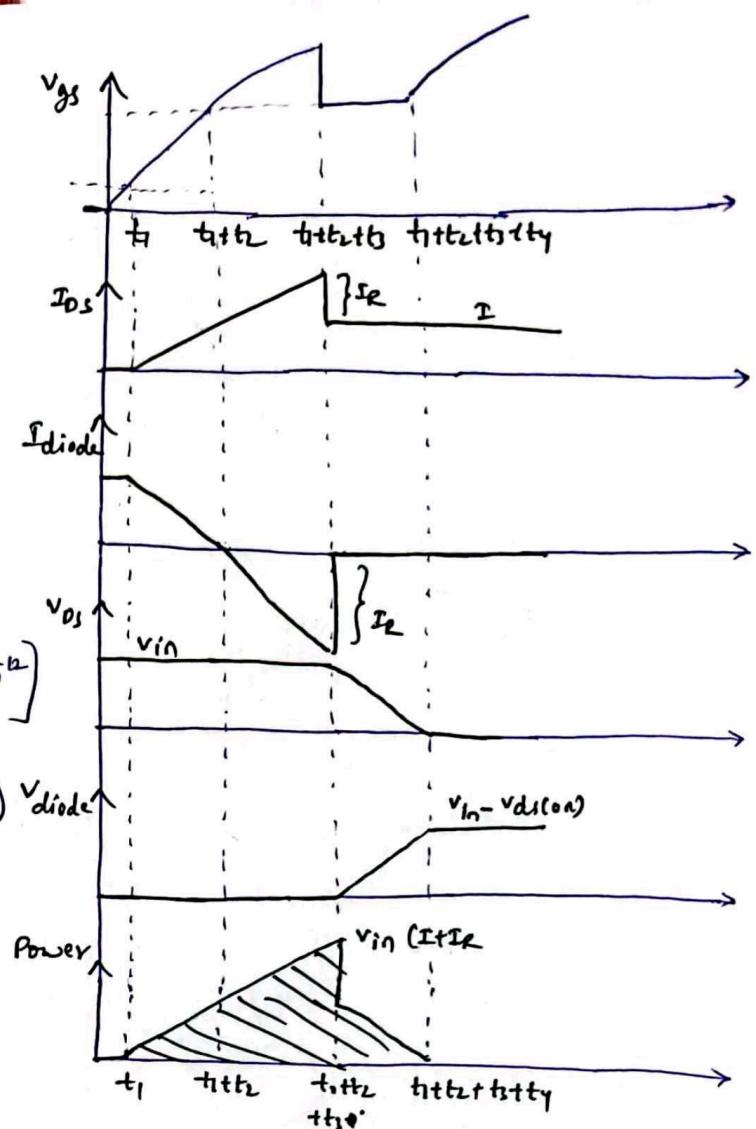
$$= 0.591 \text{ mJ} \times 20 \times \text{kHz} \\ = 11.82 \text{ W}$$




Switch off

$$\text{Area} = \text{Energy} = \frac{1}{2} \times v_{in} \times I_0 \times (t_2 + t_3) / 2 \\ = \frac{1}{2} 48 \times 10 \times \left(\frac{84.72 + 25.64}{2} \right) \times 10^{-9} \\ = 0.0132 \text{ mJ}$$

Power loss at 20 kHz is

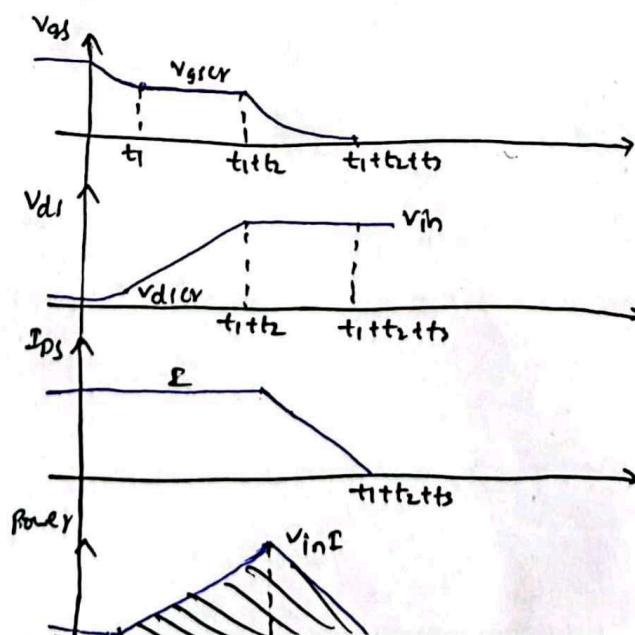
$$= 0.0132 \times 20 \\ = 0.264 \text{ W}$$



(18)


$$d = 0.5 ; \quad f_s = 100 \text{ kHz}$$

Circuit diagram

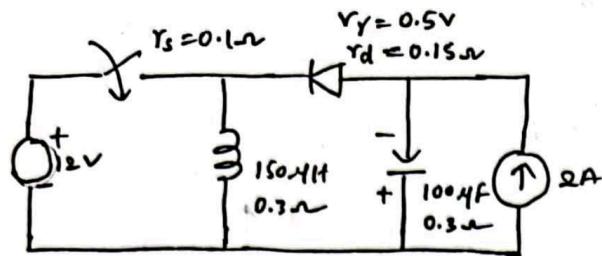

$$V_o = ?$$

$$\Delta V_C = ?$$

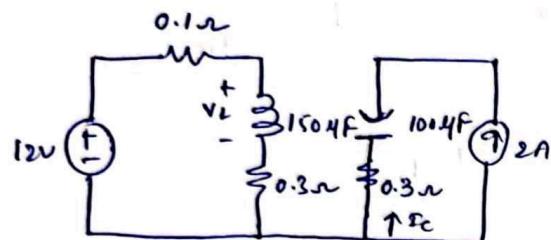Switch ON:


$$V_L(t) = 12 - I_L(t) [0.4]$$

Area of +ve half-cycle of $V_L(t)$

$$\int_0^{dT_s} V_L(t) dt = 12 \int_0^{dT_s} dt - 0.4 \int_0^{dT_s} I_L(t) dt$$

$$A_+ \Rightarrow \int_0^{dT_s} V_L(t) dt = V_{in} \int_0^{dT_s} dt - (r_s + r_L) \int_0^{dT_s} I_L(t) dt$$
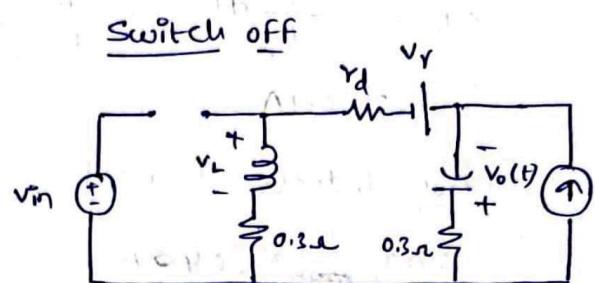
$$A_f = A_- \quad (\text{Avg. Voltage across Inductor zero})$$



$$-V_L(t) = I_L(t) r_L + (I_L(t) - I_0) r_C + V_o(t) + V_Y + r_d I_L(t)$$

Area of -ve half cycle of $V_L(t)$

$$A_- = - \int_{dT_s}^{T_s} V_L(t) dt = V_o(t) \int_{dT_s}^{T_s} dt + V_Y \int_{dT_s}^{T_s} dt - I_0 r_C (1-d) T_s + (r_L + r_C + r_d) \int_{dT_s}^{T_s} I_L(t) dt$$

$$\therefore \quad \frac{dV_{in}}{dT_s} - (r_L + r_s) \frac{I_0 d}{(1-d)} T_s = (V_o + V_Y - I_0 r_C) (1-d) T_s + (r_L + r_C + r_d) I_0 T_s$$

$$dV_{in} - (r_L + r_s) \frac{I_0 d}{(1-d)} = (V_o + V_Y - I_0 r_C) (1-d) + (r_L + r_C + r_d) I_0$$

$$V_o (1-d) = dV_{in} - V_Y (1-d) + I_0 r_C (1-d) - (r_L + r_C + r_d) I_0 - (r_L + r_s) \frac{I_0 d}{1-d}$$

$$V_o (1-d) = dV_{in} - V_Y (1-d) + I_0 \left[r_C (1-d) - (r_L + r_C + r_d) - \frac{(r_L + r_s) d}{1-d} \right]$$

$$\therefore V_o = \left[\frac{d}{1-d} V_{in} - V_Y \right] + I_0 \left[r_C - \frac{r_L + r_C + r_d}{1-d} - \frac{d(r_L + r_s)}{(1-d)} \right]$$

From above formula \Rightarrow


$$V_o = \left(\frac{12(0.5)}{1-0.5} - 0.5 \right) - 2 \left(0.3 - \frac{0.3+0.3+0.15}{0.5} - \frac{0.5(0.3+0.1)}{(0.5)^2} \right)$$

$$= 11.5 - 2 [0.3 - 1.5 - 0.8]$$

$$= 11.5 - 4$$

$$V_o = 7.5V$$
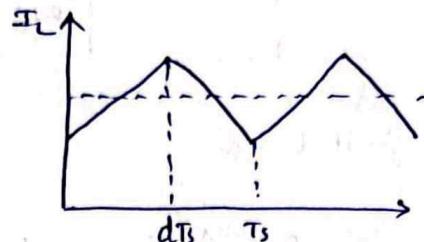
$$\Delta I_L \approx \frac{V_{in}}{L} dt_s = \frac{12}{150 \times 10^{-6}} \left(\frac{0.5}{100 \times 10^3} \right) \\ \approx 0.4A$$



Avg. Inductor Current $\Rightarrow 4A$ (from graph)

$$\therefore \Delta I_L = 0.4A$$

$$\therefore \Delta V_C = 0.4 + 0.3 \\ = 0.12V$$

- ⑥ If you increase the no. of MOSFETs (Parallel Connected MOSFETs), then you will less Conduction power loss due to less $r_{ds(on)}$ (\because Parallel Connected r_{ds} 's results less $r_{ds(on)}$) But switching losses will increases due to more no. of switches Because, switching losses are dissipated each switch i.e; If you Connected MOSFET's in Parallel then due to more MOSFET more switching's are needed to operate the Converter i.e; more switching losses that way you are getting instead of 94% you got 75% (Conduction loss \downarrow But switching losses \uparrow)

Improve the Converter efficiency by

- * wound the Inductor very tightly i.e; near to ideal one.
- * Sholder the Components very closely i.e; Then you won't get parasitic Inductances.
- * use Proper R_g value & select MOSFET Based on rating.

(19)

Boost Converter

$$V_{in} = 12V, d = 0.75, f_s = 50\text{kHz}, L = 60\mu H$$


$$C = 1000\mu F, C \times ESR = 30\mu s$$

- a) Converter operates no load means, circuit operates like a LC series circuit i.e; large current flows through Diode (D) and Capacitor charges upto $2V_{in}$. So there is no problem. But Current in the CLT is very large Because

$I_p = V_{in} \sqrt{\frac{C}{L}} \approx 12 \sqrt{\frac{1000}{60}} \approx 49A$. It causes diode will get damage and switch also get blown. when it is tested on no load.

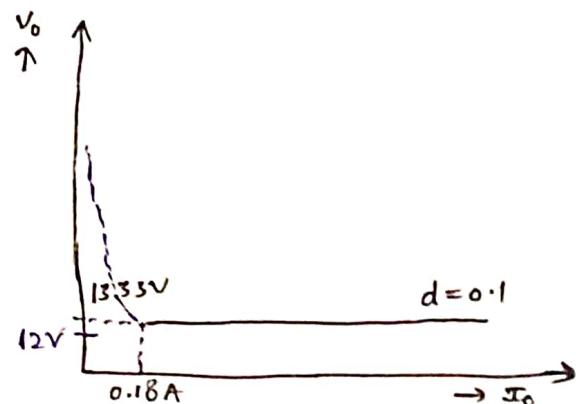b) $d = 0.1$

$$\begin{aligned}\frac{\Delta I_L}{2} &= \frac{d(1-d)V_{in}}{2f_s L} \\ &= \frac{(0.1)(1-0.1)12}{2 \times 50 \times 10^3 \times 60 \times 10^{-6}} \\ &= \frac{0.1(12)(0.9)}{6} = 0.18A\end{aligned}$$



Min. Current, $I_{o\min} > \frac{\Delta I_L}{2}$ then Converter operates CCM.

$$\therefore I_{o\min} = 0.18A$$

$$V_o = \frac{V_{in}}{1-d} = 13.33V$$

$$R_{min} = \frac{V_o}{I_{o\max}} ; R_{max} = \frac{V_o}{I_{o\min}}$$

$$\therefore R_{max} = \frac{13.33}{0.18}$$

$$= 74.07\Omega$$