

① Given,

$$V_{in} = 300V$$

$$C_1 = C_2 = 4.7 \mu F$$

$$L = 35 \mu H$$

$$V_o = 12V$$

$$C = 220 \mu F$$

$$n = 9$$

$$f_s = 50 \text{ kHz}$$

$$L_p = 2.7 \mu H$$

②  $V_o = \frac{d V_{in}}{n}$


$$12 = \frac{d \times 300}{9} \Rightarrow d = 0.36$$

$$\dot{i}_L = I_o = 10A$$

$$\Delta i_{LPP}^o = \frac{V_o (0.5 - D)}{f_s L} = \frac{12(0.5 - 0.36)}{35 \times 10^{-6} \times 50 \times 10^{-3}} = 0.96A$$

$$i_{Lmin} = C = I_o - \frac{\Delta i_{LPP}^o}{2} = 9.52A$$
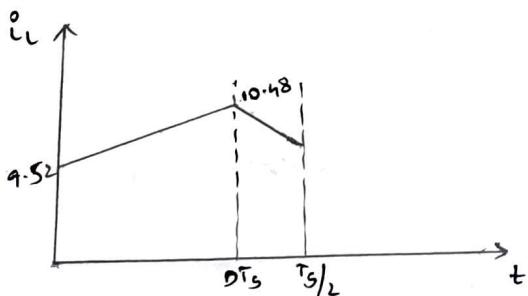
$$i_{Lmax} = b = I_o + \frac{\Delta i_{LPP}^o}{2} = 10.48A$$



secondary current  $\rightarrow 9.52A - 10.48A$


Reflected secondary current  $\rightarrow \frac{i_L}{n} \rightarrow 1.06A - 1.16A$

$$\text{magnetizing current } a = \frac{V_{in}}{2L_{pm}} DT_S \times \frac{1}{2} = \frac{300}{2 \times 2.7 \times 10^{-3}} \times 0.36 \times \frac{1}{2 \times 50 \times 10^{-3}}$$

$$a = 0.2A$$

$$\therefore i_p \text{ varies } b/w \frac{C-a}{n} \leftrightarrow \frac{b}{n} + a \rightarrow 0.86A - 1.36A$$
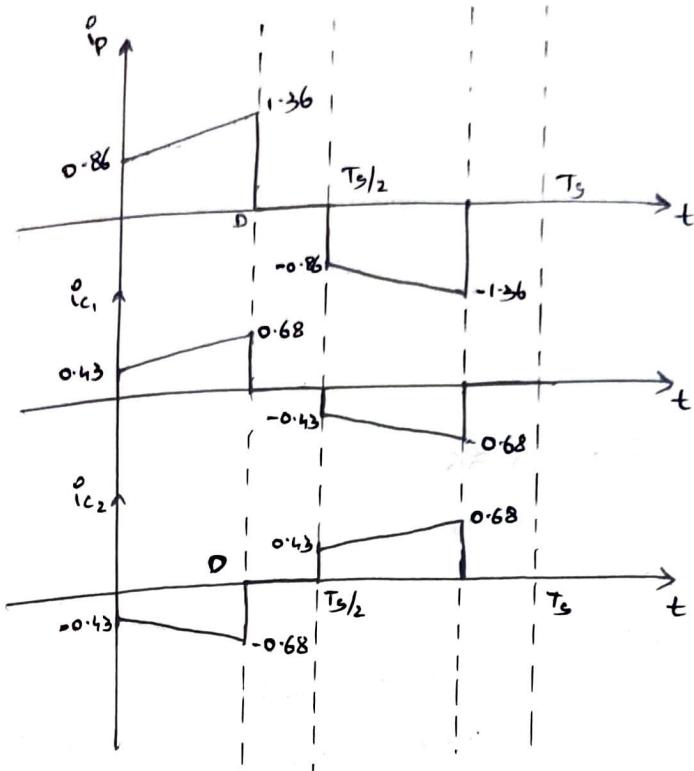
$$i_{C_1}^o = \frac{i_p^o}{2}, \quad i_{C_2}^o = -\frac{i_p^o}{2}$$



(b)

$$L_p = 2.7 \mu H$$

$$L_x = 30\% \text{ of } L_p = 0.03 L_p = 8.1 \times 10^{-5} H$$

$$V_o = \frac{D V_{in}}{n} = \frac{3}{2} \frac{f_S L_p I_o}{n^2}$$

$$12 = \frac{D \times 300}{9} - \frac{3}{2} \times \frac{50 \times 10^3 \times 8.1 \times 10^{-5} \times 10}{9^2}$$

$$12 = \frac{100 \times D}{3} - 0.75$$

$$\boxed{D = 0.3825}$$

② (i) Given,

input 250V - 400V

output 12V

$I_o$  2A - 5A

$f_s$  100kHz

→ Flyback converter is an indirect energy transfer converter. When the switch is on, the primary inductance will store energy but the secondary diode is reverse biased so, current won't fly to secondary.

→ When the switch is off, the stored energy in the inductor is given to switch capacitance and output capacitance.

→ As there is no load the capacitor cannot discharge and for every cycle the energy keeps on increasing in capacitance and this leads to blow up capacitor and switch.

→ For CCM,

$$I_{P\min} - I_{P\max} = \frac{V_{in}}{L_p} \Delta T_s$$

$$\epsilon = \frac{1}{2} L I^2 = \frac{1}{2} L (I_{P\max} - I_{P\min})^2$$

This is the power transferred for one cycle  
average power transferred.

$$P_o = \frac{1}{2} L (I_{P\max} - I_{P\min})^2$$

$$P_0 = V_0 I_0$$

$$V_0 I_0 = \frac{1}{2} L (I_{P_{\max}} - I_{P_{\min}})^2 \times f_s$$

$$V_0 = \frac{D^2 V_{in}^2}{2 f_s L P I_0}$$

but  $I_0 = 0$

$$V_0 = \frac{D^2 V_{in}^2}{2 f_s L P I_0} \approx 0$$

→ This is the reason why capacitor will be blown

ii) No, Her professor didn't teach her wrong, flyback converter should be tested with less duty cycle and less value of load

→ so that energy stored in primary inductance will be less and is given to the output or secondary side when the switch is off.

(3)

Given,

$$A_c = 266 \text{ mm}^2$$

$$A_w = 537 \text{ mm}^2$$

$$A_p = A_c A_w = 142842 \text{ mm}^2$$

$$I = 30A \pm 3A$$

$$I_{\max} = 33A, I_{\min} = 27A$$

$$K_p = \frac{I_{\max}}{I} = \frac{33}{30} = 1.1$$

$$K_s = 0.36$$

$$J = 4A/\text{mm}^2$$

$$B_{\max} = 0.2 \text{ wb/mm}^2 = 0.2 \times 10^{-6} \text{ wb/mm}^2$$

$$A_p \geq \left( \frac{1}{2} L I^2 \right) \left( \frac{2 K_i}{K_s B_{\max} J} \right)$$

$$L_{\max} = \frac{A_p K_s J B_{\max}}{K_i I^2}$$

$$= \frac{142842 \times 0.36 \times 4 \times 0.2 \times 10^{-6}}{1.1 \times 30^2}$$

$$\boxed{L_{\max} = 41.55 \mu\text{H}}$$

$$N = \frac{L K_i I}{A_c B_{\max}} = \frac{41.55 \times 10^{-6} \times 1.1 \times 30}{266 \times 0.2 \times 10^{-6}}$$

$$N = 25.77$$

$$\boxed{N \approx 26}$$

$$L = \frac{\mu_0 N^2 A_c}{L_e + 2g \frac{\mu_0}{\mu_0}}$$

$$g = \frac{\mu_0 N^2 A_c}{2L} - \frac{\mu_0 e}{2\mu_0}$$

$$g = \frac{4\pi \times 10^{-7} \times 26^2 \times 266 \times 10^{-6}}{2 \times 41.55 \times 10^6} - \frac{148 \times 10^{-3}}{2 \times 2200}$$

$$\boxed{g = 2.68 \mu m}$$

④ Given,

$$V_{in} = 108V - 135V$$

$$V_o = 12V$$

$$I_o = 2A - 5A$$

$$\Delta I_L < 1A$$

$$\Delta V_o < 1\% \text{ of } V_o$$

$$f_s = 20 \text{ KHz}$$

$$D_{max} = 0.45$$

$$V_o = \frac{D V_{in}}{n}$$

$$12 = \frac{D_{max} \times V_{in_{min}}}{n}$$

$$n = \frac{0.45 \times 108}{12} \approx 4.05 \approx 4$$

$$V_o = \frac{D_{min} \times V_{in_{max}}}{n} \Rightarrow 12 = \frac{D_{min} \times 135}{4} \Rightarrow D_{min} = 0.36$$

$$\Delta l_L^0 = \frac{(1-D) v_0 \times D T_s}{L}$$

$$\Delta l_L^0 = \frac{(1-D_{\min}) v_0}{f_s L}$$

$$L = \frac{(1-0.36) \times 12}{40000 \times 1}$$

$$L = 192 \mu H$$

$$\Delta l_L^0 = \frac{(1-D_{\max}) v_0}{f_s L}$$

$$\Delta l_L^0 = \frac{(1-0.45) \times 12}{40000 \times 192 \times 10^6} = 0.859$$

$$I_{L_{\min}} = I_0 - \frac{\Delta l_L^0}{2} = 4.57 A$$

$$I_{L_{\max}} = I_0 + \frac{\Delta l_L^0}{2} = 5.429 A$$

$$k_I^0 : \frac{I_{L_{\max}}}{I} = \frac{5.429}{5} = 1.0859$$

$$A_P = \left( \frac{1}{2} L I^2 \right) \left( \frac{2 k_I^0}{k_s B_{\max} J} \right)$$

$$A_P = \left( \frac{1}{2} \times 192 \times 10^6 \times 5^2 \right) \left( \frac{2 \times 1.0859}{0.4 \times 3 \times 0.2 \times 10^{-6}} \right)$$

$$A_P = 21718 \text{ mm}^4$$

fd, EE 40/16/12

$$A_c = 1494 \text{ mm}^2$$

$$A_w = 2 \times 10.5 \times \left( \frac{28.6 - 12.5}{2} \right) = 169 \text{ mm}^2$$

$$A_p = A_c A_w$$

$$A_p = 251.88 \text{ mm}^2$$

∴ we choose EE 40/16/12 core

$$\text{Mean turn length} = 4 \times \left( 12.5 + \frac{28.6 - 12.5}{2} \right)$$

$$L_m = 82.2 \text{ mm}$$

RMS value of current  $\approx 5 \text{ A}$

$$\text{coffet area} = \frac{I}{f} = \frac{5}{3} = 1.667 \text{ mm}^2$$

for SWG 16,

$$\text{Cu area} \rightarrow 2.075 \text{ mm}^2$$

$$\text{Cu dia} \rightarrow 2 \sqrt{\frac{2.075}{\pi}} = 1.625 \text{ mm}$$

$$\text{dia} \rightarrow 1.709 \text{ mm}$$

∴ we choose SWG 16 wire

$$N \phi = L I$$

$$N = \frac{L I}{\phi} = \frac{L I_{\max}}{A_c B_{\max}}$$

$$N = \frac{192 \times 10^{-6} \times 5.489}{149 \times 0.2 \times 10^{-6}}$$

$$N = 35.5 \approx 36 \text{ turns} \rightarrow 40 \text{ turns}$$

$$\text{window height} = 2 \times 10.5 = 21 \text{ mm}$$

$$\text{useful window} = 21 - (2 \times 1 + 2 \times 2) = 15 \text{ mm}$$

$$\text{No. of turns/layer} = \frac{15}{1.709} = 8.77$$

for no turns

wind 8 turns per layer for 5 layers

$$P = .5$$

$$h = 0.866 \times d = 0.866 \times 1.625 = 1.407$$

$$F_L = \frac{n \times d}{w} = \frac{8 \times 1.625}{15} = 0.866$$

$$\Delta = 0.31 \text{ mm} @ 50 \text{ kHz}$$

$$\rightarrow \frac{h \sqrt{F_L}}{\Delta} = \frac{1.407 \sqrt{0.866}}{0.31} = 4.22$$

$$F_X = \frac{2P^2 + 1}{3} \times \frac{h \sqrt{F_L}}{\Delta}$$

$$F_X = \frac{2 \times 5^2 + 1}{3} \times \frac{1.407 \sqrt{0.866}}{0.31} = 71.74$$

$$\frac{R_{ac}}{R_{dc}} = 71.74$$

$$R_{dc} = \frac{82.2 \times 15}{1000} \times 0.0083 \times 1.2$$

$$R_{dc} = 12.2 \text{ m}\Omega$$

$$R_{ac} = R_{dc} \times F_X = 12.2 \text{ m}\Omega \times 71.74 = 0.88 \Omega$$

$$\text{Cu loss} = I_{dc}^2 R_c + I_{ac}^2 R_{ac}$$

$$P_{cu} = 12.2 \times 10^{-3} \times 5^2 + 0.88 \times \left( \frac{0.429}{\sqrt{3}} \right)^2$$

$$P_{cu} = 0.305 + 0.0539$$

$$P_{cu} = 0.358 \text{ W}$$

core loss,

B changes b/w  $0.2 \text{ Wb/m}^2$  &  $0.48 \text{ Wb/m}^2$

$$0.2 \times \frac{4.57}{5.429} = 0.168$$

$$\Delta B_m = \frac{0.2 - 0.168}{2} = 15.8 \text{ mWb/m}^2$$

$$\Delta B_m \approx 16 \text{ Wb/m}^2$$

Relative core loss for  $\Delta B_m$  @  $40 \text{ kHz}$

$$\approx 1.8 \text{ mW/cc}$$

core volume =  $11.5 \text{ cc}$

$$\text{core loss} = P_c = 1.8 \times 11.5 \times 10^{-3}$$

$$P_c = 0.0207 \text{ W}$$

Total loss:  $0.358 + 0.0207$

$$P_T = 0.378 \text{ W}$$

Diesel peak current =

Diesel RMS current =

Diesel peak voltage =

MOSFET peak current =

MOSFET peak voltage =

MOSFET RMS current =

for capacitance,

$$ESP \times 1 = 0.12$$

$$ESP = 0.12 \Omega$$

$$C = \frac{40 \times 10^{-6}}{0.12} = 333.3 \mu\text{F}$$

$$C = \frac{30 \times 10^{-6}}{0.48} = 62.5 \mu\text{F}$$

(5)

Given,

$$V_{in} = 200V - 280V$$

$$V_0 = 24V$$

$$I_0 = 2A - 5A$$

$$\Delta V_0 \leq 2\% \text{ of } V_0$$

$$\Delta I_L \leq 1A$$

$$f_s = 75kHz, D_{max} = 0.45$$

$$V_0 = \frac{2DV_{in}}{n}$$

$$V_0 = \frac{2 \times D_{max} \times V_{in, min}}{n}$$

$$n = \frac{2 \times 0.45 \times 200}{24} = 7.5$$

$$n \approx 8$$

$$D_{min} = \frac{n \times V_0}{2 \times V_{in, max}} = \frac{24 \times 8}{2 \times 280} = 0.34$$

$$\Delta I_L = \frac{V_0(0.5 - D) T_s}{L}$$

$$L = \frac{24(0.5 - 0.34)}{75000 \times 1} = 51.2 \mu H$$

$$L = 51.2 \mu H$$

for capacitance,

$$ESR \times I = 0.48$$

$$ESR = 0.48 \Omega$$

$$C = \frac{30 \times 10^{-6}}{0.48} = 62.5 \mu F$$

$$\Delta I_L^0 = \frac{24(0.5 - 0.45)}{\frac{6}{10 \times 75000 \times 51.2}}$$

$$\Delta I_L^0 = 0.3125 A$$

$$I_{L\min} = I_0 - \frac{\Delta I_L^0}{2} = 4.8437 A$$

$$I_{L\max} = I_0 + \frac{\Delta I_L^0}{2} = 5.1562 A$$

$$k_i^0 = \frac{I_{L\max}}{I} = \frac{5.1562}{5} = 1.0312$$

$$k_S = 0.4$$

$$A_P = \left( \frac{1}{2} L I^2 \right) \left( \frac{2 k_i^0}{0.4 \times 3 \times 0.2 \times 10^{-6}} \right)$$

$$A_P = \left( \frac{1}{2} \times 51.2 \times 10^{-6} \times 52 \right) \left( \frac{2 \times 1.0312}{0.4 \times 3 \times 0.2 \times 10^{-6}} \right)$$

$$A_P = 6284.19 \text{ mm}^4$$

for EE 30/15/7

$$A_c = 60 \text{ mm}^2$$

$$A_w = 2 \times 9.7 \times \left( \frac{19.5 - 7.2}{2} \right) = 119.31 \text{ mm}^2$$

$$A_P = A_c A_w = 7158.6 \text{ mm}^4$$

$$\text{mean flux length} = 4 \times \left( 7.2 + \frac{19.5 - 7.2}{2} \right)$$

$$d_m = 53.4 \text{ mm}$$

RMS value of current  $\approx 5 A$

$$\text{copper area} = \frac{I}{J} = \frac{5}{3} = 1.667 \text{ mm}^2$$

'SWG 16.

$$\text{Cu area} = 2.075 \text{ mm}^2$$

$$\text{Dia} = 1.709 \text{ mm}$$

$$\text{Cu dia} = 1.625 \text{ mm}$$

$$N = \frac{LI_{\max}}{A_c B_{\max}} = \frac{51.2 \times 10^6 \times 5.1562}{60 \times 0.2 \times 10^{-6}}$$

$$N = 21.8 \approx 24$$

$$\text{window height} = 2 \times 9.4 = 19.4 \text{ mm}$$

$$\begin{aligned}\text{utilized window height} &= 19.4 - (2 \times 1 + 2 \times 2) \\ &= 13.4 \text{ mm}\end{aligned}$$

$$\text{coil dia} = 1.709 \text{ mm}$$

$$\text{Number of turns/layer} = \frac{13.4}{1.709} = 7.84$$

choose 6 turns for 4 layers  $\rightarrow 24$  turns

$$h = 0.866 \times 1.625$$

$$h = 1.407 \text{ mm}$$

$$F_L = \frac{6 \times 1.625}{13.4} = 0.727$$

$$\Delta = 0.25 \text{ @ } 75 \text{ kHz}$$

$$\frac{h \sqrt{F_L}}{\Delta} = \frac{1.407 \times 0.727}{0.25} = 4.095$$

$$F_R = \frac{2P^2 + 1}{3} \times \frac{h \sqrt{F_L}}{\Delta}$$

$$F_R = 45.045$$

$$R_{DC} = \frac{53.2 \times 13.4}{1000} \times 0.0083 \times 1.2$$

$$R_{DC} = 7.1 \text{ m}\Omega$$

$$R_{AC} = 7.1 \text{ m}\Omega \times 45.045 + 0.32 \Omega$$

Copper loss,  $I_{DC}^2 R_{DC} + I_{AC}^2 R_{AC} = P_{Cu}$

$$P_{Cu} = 7.1 \times 10^{-3} \times 5^2 + 0.32 \times \left( \frac{6.156}{\sqrt{3}} \right)^2$$

$$P_{Cu} = 0.18 \text{ W}$$

Cores loss,

$$B_m \text{ varies from } 0.2 \text{ wb/m}^2 \rightarrow 0.2 \times \frac{4.843}{5.156}$$

$$0.2 \text{ wb/m}^2 - 0.187 \text{ wb/m}^2$$

$$\Delta B_m = \frac{0.2 - 0.187}{2} = 6.5 \times 10^{-3}$$

$$\Delta B_m = 7 \text{ mwb/m}^2$$

$$cl = 2 \text{ mw/m}^2$$

$$P_c = 4 \times 2 = 8 \text{ mw}$$

$$P_T = P_{Cu} + P_c$$

$$P_T = 0.18 + 0.008$$

$P_T = 0.188 \text{ W}$

for transformer.

$$P_0 = (1.4 + \eta_{Bmax} J f_s k_s) (A_p)$$

$$\text{let } \eta = 10\%$$

$$A_p = \frac{P_0}{1.4 + \eta B_{max} J f_s k_s}$$

$$A_p = \frac{24 \times 5}{1.49 \times 0.9 \times 0.2 \times 10^6 \times 3 \times 75000 \times 0.35}$$

$$A_p = 5758.4 \text{ mm}^2$$

$\therefore$  for EE 30/15/7

$$A_p = 7158.6 \text{ mm}^2$$

$\therefore$  we choose EE 30/15/7 core

⑥

Given,

$$V_{in} = 250 - 400 V$$

$$V_o = 12 V$$

$$I_o = 5 A - 20 A$$

$$\Delta V_o < 2\% P-P$$

$$\Delta i_L < 4 A P-P$$

$$f_S = 50 \text{ kHz}$$

$$D_{max} = 0.45$$

$$V_o = \frac{D V_{in}}{n}$$

$$n = \frac{D_{max} V_{in(min)}}{V_o} = \frac{0.45 \times 250}{12}$$

$$n = 9.32 \approx 9$$

$$\therefore D_{min} = \frac{n V_o}{V_{in(max)}} = \frac{9 \times 12}{400} = 0.27$$

D values from 0.27 to 0.45

$$\Delta i_L^o = \frac{V_o(0.5 - D) T_S}{L}$$

$$\Delta i_L^o = \frac{12(0.5 - 0.27)}{4 \times 50 \times 10^{-3}}$$

$$L = 13.8 \mu H$$

Capacitance, ESR  $\times 4 = 0.24$

$$ESR = 0.24 / 4 = 0.06 \Omega$$

$$C = \frac{50 \times 10^{-6}}{0.06} = 833.3 \mu F$$

$$\Delta i_p = \frac{V_o (0.5 - 0.45)}{50 \times 10^3 \times 13.8 \times 10^{-6}}$$

$$\Delta i_p = 0.869 A$$



$$i_{p_{\max}} = 20.43 A$$

$$i_{p_{\min}} = 19.56 A$$

Reflected secondary currents,  $2.174 - 2.270 A$

$\therefore$  primary current varies b/w  $(2.17 - 0.44) A$  to  $(2.27 + 0.44) A$

$\rightarrow 1.73 A$  to  $2.71 A$

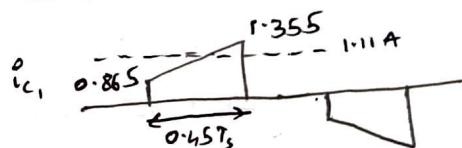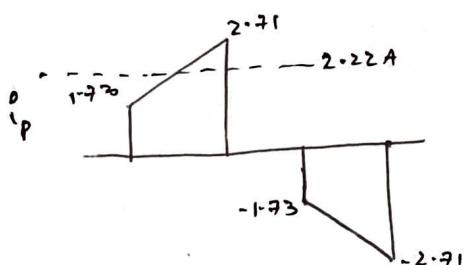

$$\text{charge contained in +ve half cycle} = \frac{1.11 \times 0.45}{50 \times 10^3} = 9.99 \mu C$$

5% P-P ripple is allowed in  $C_1$  &  $C_2$

$$\therefore \left(\frac{V_{in}}{2}\right) \times 0.05 \times C = 9.99 \mu C$$

$$C_1 = C_2 = 1.6 \mu F \rightarrow \text{proper capacitor}$$

$$\begin{aligned} \text{charge contained in one half cycle of } i_p &= 2.22 \times 0.45 \times 20 \times 10^6 \\ &= 19.98 \mu C \end{aligned}$$

$$\therefore \frac{2.50}{2} \times 0.05 \times C_b = 19.98 \mu C$$

$$C_b = 3.3 \mu F$$

switch peak current =  $2.71A$


switch avg current =  $(i_p)_{avg} = 2.22A$

switch RMS current =  $(i_p)_{RMS} \sqrt{\frac{T_s}{2}} = 2.7 \sqrt{0.45} = 1.475A$

o/p diode peak current =  $20 + 2 = 22A$

o/p diode avg current =  $\frac{(I_L)_{avg}}{2} = \frac{20}{2} = 10A$

o/p diode RMS current = secondary RMS =

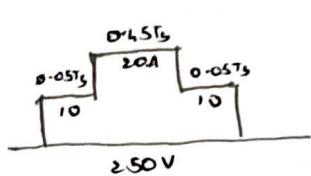

$$\Rightarrow \sqrt{\frac{20^2 \times 0.45 \times 20 \times 10^{-6} + 10^2 \times 2 \times 0.05 \times 20 \times 10^{-6}}{20 \times 10^{-6}}} = 13.78A$$

$$= \underline{13.78A}$$

Transformer:

$$\text{primary RMS} = \frac{I_0}{n} \sqrt{2D_{max}}$$

$$\text{secondary RMS} = \frac{I_0}{2} \sqrt{2D_{max} + 1}$$

$$k_s A_w = n_p \times \frac{I_0}{n} \sqrt{\frac{2D_{max}}{J}} + \frac{I_0}{2J} \sqrt{2D_{max} + 1} \times 2n_s$$

$$D_{max} = 0.45$$

$$k_s A_w = 2.33 n_s \frac{I_0}{J}$$

$$A_w = \frac{2.33 n_s I_0}{k_s J}$$

$$\rightarrow n V_o T_s = 2 B_m A_c n_p$$

$$A_c = \frac{n v_o T_s}{2 n_p B_m} = \frac{v_o}{2 f_s B_m n_s}$$

$$A_c A_w = \frac{2 \cdot 33 V_o I_o}{k_s J B_m f_s} = \cancel{5.8 \times}$$

$$\therefore A_p = 26628.57 \text{ mm}^2$$

for EE42/21/25

$$A_c = \frac{178}{2} \text{ mm}^2$$

$$A_w = (2 \times 14.8) \times \left( \frac{29.5 - 12.2}{2} \right) = 256.04 \text{ mm}^2$$

$$45568$$

$$A_p = \cancel{59913.36} \text{ mm}^2$$

Hence we choose EE42/21/25 core for Tf

$$n_s = \frac{1}{\frac{2 f_s B_m A_c}{v_o}} = \frac{v_o}{2 f_s B_m A_c} = 3.37$$

$$n_s \approx 4$$

$$n_p = n \times n_s = 9 \times n_s$$

$$n_p = 9 \times 4 = 36$$

Inductor,

RMS value of  $I_s \approx 20 \text{ A}$

$$\text{copper area} = \frac{\pi}{J} = \frac{20}{3} : 6.667 \text{ mm}^2$$

$\therefore$  SWG 11 has

$$\text{cu area} \rightarrow 6.818 \text{ mm}^2$$

$$\text{cu dia} \rightarrow 2.946 \text{ mm}$$

$$\text{dia} \rightarrow 3.068 \text{ mm}$$

calculated  $L = 13.8 \mu\text{H}$

$$k_p = \frac{I_{max}}{I} = \frac{20.43}{20} = 1.0215$$

$$k_s = 0.35$$

$$A_p = \frac{1}{2} L \cdot I^2 \cdot \frac{2 k_p}{k_s A_{Bmax}}$$

$$A_p = \frac{1}{2} \times \frac{13.8 \times 10^{-6} \times 20^2 \times 2 \times 1.0215}{0.35 \times 3 \times 0.2 \times 10^{-6}}$$

$$A_p = 26850.85 \text{ mm}^2$$

$\therefore$  EE 42/20/15 core is selected

$$\text{Mean turn length} = 4 \times \left( 12.2 + \frac{29.5 - 12.2}{2} \right)$$

$$l_m = 83.4 \text{ mm}$$

$$N = \frac{L I_{max}}{A_c B_{max}} = \frac{13.8 \times 10^{-6} \times 20.43}{178 \times 0.2 \times 10^{-6}} = 7.91$$

$$N = 7.91 \approx 8$$

$$\text{window height} = 2 \times 14.8 = 29.6 \text{ mm}$$

$$\text{utilize height} = 29.6 - 6 = 23.6 \text{ mm}$$

$$\text{number of turns/layer} = \frac{23.6}{3.068} = 7.69$$

$$\therefore 4 \times 2 \text{ layer} = 8 \text{ turns}$$

$$h: 0.866 \times d = 0.866 \times 2.946$$

$$= 2.5512 \text{ mm}$$

$$F_d = \frac{N \times d}{W} = \frac{4 \times 2.946}{23.6} = 0.496$$

$$A = 0.141 \text{ mm} @ 50 \text{ KHz}$$

$$\therefore \frac{h\sqrt{F_d}}{\Delta} = 12.74$$

$$\therefore F_8 = \frac{2P^2+1}{3} \frac{h\sqrt{F_d}}{\Delta} = \frac{2 \times 2^2 + 1}{3} \times 12.74$$

$$F_8 = 38.22$$

$$R_{DC} = \frac{83.4 \times 23.6}{1000} \times 0.0025 \times 1.2$$

$$R_{DC} = 5.9 \text{ m}\Omega @ 70^\circ\text{C}$$

$$R_{AC} = 5.9 \text{ m}\Omega \times 38.22 = 0.225 \Omega$$

$$\text{Cu loss} = 20^2 \times 5.9 \times 10^{-3} + \left( \frac{0.43}{\sqrt{3}} \right)^2 \times 0.225$$

$$\text{Cu loss} = 2.36 + 0.0139$$

$$\text{Cu loss} = 2.37 \text{ Watt}$$

• Bm changes from  $0.2 \text{ wb}/\text{m}^2 \rightarrow 0.2 \times \frac{19.56}{20.43}$

$$\Delta B_m = \frac{0.2 - 0.19}{2} = 5 \text{ mT}$$

$$\therefore \text{core loss at } 50 \text{ KHz} = 0.6 \text{ mW/cc}$$

$$\text{core volume} = 17.3 \text{ cc}$$

$$P_c = 17.3 \times 0.6 \text{ mW} = 10.38 \text{ mW}$$

$$P_t = P_{Cu} + P_c = 2.384 \text{ W}$$

⑦ Given,

$$V_{in} = 250 - 400V \quad \text{MOSFET - } 900V \quad (V_R)$$

$$V_0 = 12V \quad J = 3A/mm^2$$

$$I = 2.5A \quad B_M = 0.25wb/mm^2$$

$$\Delta V_0 = 2V \text{ P-P}$$

$$f_s = 100kHz$$

from MOSFET voltage rating find 'n'

$$1.3(V_{in\max} + n(V_0 + V_g)) \leq 0.8 \times V_R \quad V_g = 1V \text{ for silicon}$$

$$1.3(400 + n(12 + 1)) \leq 0.8 \times 900$$

$$n = 11.83 \approx 12 \text{ turns}$$

use 'n' & find  $D_{max}$

$$D_{max} \left( 1 + \frac{V_{in\min}}{n(V_0 + V_g)} \right) \leq 0.8$$

$$D_{max} = \frac{0.8}{1 + \frac{250}{12(12+1)}} = 0.31$$

$$D_{max} = \sqrt{\frac{2L_P P_{0max} f_s}{V_{in\max}^2}}$$

$$0.31 = \sqrt{\frac{2 \times L_P \times 12 \times 5 \times 100 \times 10^3}{250^2}}$$

$$L_P = \frac{(0.31 \times 250)^2}{2 \times 60 \times 100 \times 10^3} = 500.5 \mu H$$

leakage inductance  $\rightarrow$  L<sub>L</sub> of LP

$$L_L = 20.02 \text{ mH}$$

$$\rightarrow V_{in} + n(V_o + V_g) = 250 + 12(12+1) = 406$$

$$V_{in} + V_c > 406$$

If we want  $V_{in} + V_c = 600$

$$V_c = 600 - 406 = 194 \text{ V}$$

$$R_c = \frac{2V_c (V_c - n(V_o + V_g))}{f_s L_L I_p^2}$$

$$I_p = \frac{V_{in} \times D_{max}}{L_p f_s} = \frac{250 \times 0.31}{500.5 \times 10^{-6} \times 100 \times 10^3}$$

$$I_p = 1.55 \text{ A}$$


$$R_c = \frac{2 \times 194 (194 - 12(12+1))}{100 \times 10^3 \times 20 \times 10^{-6} \times 1.55^2}$$

$$R_c = 3068.4 \Omega$$

$$C_C > \frac{1}{2\pi f_s R_c} = 518.69 \text{ pF}$$

primary RMS current =

$$I_p^0 = \frac{1.55 t}{0.31 T_s}$$

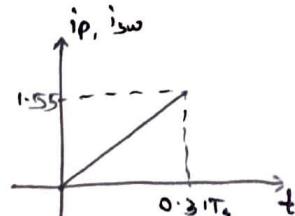

$$(i_p)_{rms} = \sqrt{\frac{1}{T_s} \int_0^{0.31 T_s} \left( \frac{1.55 t}{0.31 T_s} \right)^2 dt} = 0.492 \text{ A}$$

$$\text{flux linkage in primary} = l_p \times I_p \\ = 500.5 \times 10^6 \times 1.55 \\ = 775.7 \mu\text{Wb}$$

$$775.7 = A_c \times n_p \times B_m$$

$$A_c = \frac{775.7 \times 10^{-6}}{0.2 \times 10^{-6} \times n_p}$$

$$k_s A_w = n_p \times 0.24 \text{ mm}^2 + n_s \times 2.67 \text{ mm}^2$$

$$A_w = n_p \left( 0.24 + \frac{2.67}{12} \right)$$

$$A_w = \frac{0.4625}{0.35} n_p = 1.32 n_p$$

$$\therefore A_c A_w = 5119.62 \text{ mm}^2$$

we choose E 30/15/7 core  $\rightarrow A_p = 7100 \text{ mm}^2$

$$A_c = 59.7 \text{ mm}^2$$

$$A_w = 119 \text{ mm}^2$$

$$A_c = \frac{775.7}{0.2 n_p} \Rightarrow n_p = \frac{775.7}{0.2 \times 59.7}$$

$$n_p = 64.9 \approx 65 \text{ turns}$$


$$n_s = \frac{n_p}{n} = \frac{65}{12} = 5.4 \approx 6 \text{ turns}$$

for DCM.

$$T_3 = DT_3 + t_d + t_d$$

diode conducts during  $t_d$
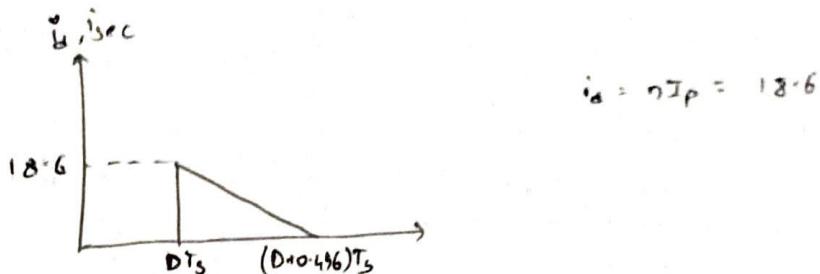
$$t_d = \frac{D_{\max} V_{\min} T_3}{n(V_o + V_R)} = \frac{0.31 \times 250}{12 \times 13} T_3 = 0.496 T_3$$



$$i_d = \frac{18.6 + t}{0.496 T_3} = \frac{37.5 t}{T_3}$$

$$i_{\text{sec(rms)}} = \sqrt{\frac{1}{T_3} \int_0^{0.496 T_3} \left( \frac{37.5 t}{T_3} \right)^2 dt}$$

$$i_{\text{sec(rms)}} = 7.81 \text{ A}$$

Diode RMS current = 7.81 A

Diode peak current = 18.6 A

Mosfet RMS current = +55 A 0.492 A

Mosfet peak current = 1.55 A

$$\text{primary wire} = \frac{I}{J} = \frac{0.492}{3} = 0.164 \text{ mm}^2 \rightarrow \text{SWG 24}$$

size = 0.245 mm<sup>2</sup>

$$\text{secondary wire} = \frac{I}{J} = \frac{7.81}{3} = 2.436 \text{ mm}^2 \rightarrow \text{SWG 15}$$

size = 2.67 mm<sup>2</sup>

Transformer,

with  $L_p = 500 \text{ mH}$

$n = 12$

(8)

$$1.3 \left[ V_{in\ max} + n(V_o + V_x) \right] \leq 0.8 V_p$$

$$V_x = 1V$$

$$1.3 \left[ 400 + n(12+1) \right] \leq 720$$


$$(I_p)_{min} = \frac{n(V_o + V_x) V_{in\ max}}{n(V_o + V_x) + V_{in\ max}} \times \frac{1}{2f_s P_{o\ min}}$$

$$n = 11.83 \approx 12$$

$$L_{p\ min} = \left( \frac{12 \times 13 \times 400}{12 \times 13 + 400} \right)^2 \times \frac{1}{2 \times 100 \times 10^3 \times 24}$$

$$L_{p\ min} = 2.33 \mu H$$

### Secondary RMS

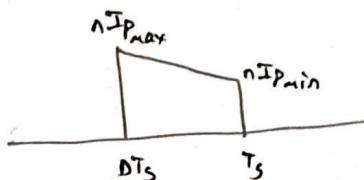

$$D_{min} = \frac{n(V_o + V_x)}{n(V_o + V_x) + V_{in\ max}} = \frac{12(13)}{12(13) + 400} = 0.28$$

$$D_{max} = \frac{n(V_o + V_x)}{n(V_o + V_x) + V_{in\ min}} = \frac{12 \times 13}{12 \times 13 + 250} = 0.384$$

$$I_{p\ max} + I_{p\ min} = \frac{2 I_o}{n(1 - D_{min})} = \frac{2 \times 5}{12(1 - 0.28)} = 1.157 \text{ — (1)}$$

$$I_{p\ max} - I_{p\ min} = \frac{n(V_o + V_x)}{f_s L_p} (1 - D) = \frac{12(13)(1 - 0.28)}{2.33 \times 10^3 \times 100 \times 10^{-3}}$$

$$I_{p\ max} - I_{p\ min} = 0.482 \text{ — (2)}$$

from (1) & (2)

$$I_{p\ max} = 0.8195 A$$

$$I_{p\ min} = 0.3375 A$$

$$I_{sec} \approx \left( \frac{n I_{P_{max}} + n I_{P_{min}}}{2} \right) \sqrt{1 - D_{min}}$$

$$I_{sec_{avg}} = \left( \frac{12 \times 0.8195 + 12 \times 0.3375}{2} \right) \sqrt{1 - 0.28}$$

$$I_{sec_{avg}} = 5.89 A$$

$$I_{avg} = I_0 = \frac{P_0}{V_0} = 5 A$$

$$I_d \text{ peak} = n I_{P_{max}} = 12 \times 0.8195 = 9.834 A$$

$$I_{d_{avg}} = \left( \frac{n I_{P_{max}} + n I_{P_{min}}}{2} \right) (1 - D_{min}) = 5.9 \approx 5 A$$

Primary RMS:

$$\overline{I}_{P_{max}} + \overline{I}_{P_{min}} = \frac{2 \overline{I}_{O_{max}}}{n(1 - D_{max})} = \frac{2 \times 5}{12(1 - 0.384)} = 1.3528 \quad (3)$$

$$\overline{I}_{P_{max}} - \overline{I}_{P_{min}} = \frac{n(V_0 + V_8)(1 - D_{max})}{E_P f_S} = \frac{12(13)(1 - 0.384)}{2.33 \times 10^5 \times 100 \times 10^3} = 0.12 \quad (4)$$

from (3) & (4)

$$I_{P_{max}} = 0.8824 A$$

$$I_{P_{min}} = 0.4704 A$$

$$(i_p)_{avg} = \left( \frac{\overline{I}_{P_{max}} + \overline{I}_{P_{min}}}{2} \right) \sqrt{D_{max}}$$

$$(i_p)_{avg} = \left( \frac{0.8824 + 0.4704}{2} \right) \sqrt{0.384} = 0.692 A$$

$$i_{avg} = \left( \frac{\overline{I}_{P_{max}} + \overline{I}_{P_{min}}}{2} \right) D_{min} : 0.259 A$$

## Transformers

$$I_{P_{\max}} = 0.8824A$$

$$L_P I_{P_{\max}} = A_c n_p B_m$$

$$A_c = \frac{L_P I_{P_{\max}}}{n_p B_m}$$

$$A_c = \frac{2 \times 3.3 \times 10^{-3} \times 0.8824}{n_p \times 0.25 \times 10^{-6}} = \frac{8223.9}{n_p}$$

$$k_s A_w = n_p \times A_p + n_s \times A_s$$

$$A_w = \frac{n_p}{k_s} \left( A_p + \frac{n_s}{n_p} A_s \right)$$

$$A_w = \frac{n_p}{0.35} \left( 0.141 + \frac{2}{12} \right)$$

$$A_p = A_c A_w = \frac{8223.9}{n_p} \times \frac{n_p}{0.35} \left( 0.141 \times \frac{2}{12} \right)$$

$$A_c A_w = 7228.4 \text{ mm}^2$$

$\therefore$  we choose E 32/16/11 core

$$\rightarrow A_c = 97 \text{ mm}^2$$

$$A_p = 14340 \text{ mm}^2$$

$$\therefore n_p = \frac{8223}{A_c} = \frac{8223}{97} = 84.77$$

$$n_s = \frac{84.77}{12} = 7.06$$

$$\therefore \boxed{n_p = 96, n_s = 8}$$

↙ SWG26      ↓ SWH16

(9)

$$V_o = \frac{V_{in}}{1-D}$$

$$24 = \frac{10.8}{1-D}$$

$$1-D = 0.45$$

$$D_{max} = 0.55$$

$$24 = \frac{13.6}{1-D}$$

$$1-D = 0.566$$

$$D = 0.433$$

$$P_o = P_{in}$$

$$I_{in} = \frac{I_o}{1-D}$$

for  $I_o = 1A$ ,  $I_{in} = 2.22A$


$$I_o = 4A, I_{in} = 8.88A$$

Sensing gain =  $0.125V/A$

$$I = 1A, V = 0.125V$$

$$I = 8.88A, V = 1.11V$$

Assume  $\alpha = 1\%$ .

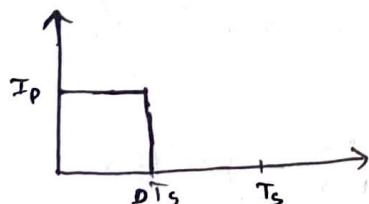

$$I = 8.88A$$

$$V = 1.11V$$

$$V_{f\omega} = 0.6V$$

$$D_{max} = 0.55$$

$$nL_m \geq \frac{100D_{max}(V + V_{f\omega})}{2\pi f_s I}$$

$$nL_m = \frac{100 \times 0.55 (1.11 + 0.6)}{1 \times 50 \times 10^3 \times 8.88}$$

$$nL_m = 211.82 \mu H \cdot T$$

$$B_m = \frac{D_{max} (V + V_{fw})}{n f_s A_c} = \frac{0.55 (1.11 + 0.6)}{50 \times 10^3 \times n \times A_c}$$

$$B_m = \frac{1.881 \times 10^{-5}}{n A_c}, \text{ we choose T}_{32} \text{ core, } n = 87$$

Core	$A_c$	$A_W$	$A_L$	$I_s = \frac{I_{Pms}}{n}$	$B_m$	$n$
T <sub>10</sub>	6.2	19.6	765	0.023	0.0108	226
T <sub>12</sub>	12	44.2	1180	0.036	8.7 × 10 <sup>-3</sup>	179
T <sub>16</sub>	20	78.5	1482	0.046	,	142
T <sub>20</sub>	22	95	1130	0.035	,	187
T <sub>27</sub>	42	16.5	1851	0.037	,	114
T <sub>32</sub>	61	16.5	2427	0.075	,	87
T <sub>45</sub>	93	616	2367	0.074	,	89

$$J = 3A/mm^2$$

$$J = I/A \rightarrow A = \frac{I}{J} = \frac{0.075}{3} = 0.025 mm^2$$

∴ SWG 32 wire is selected

$$V_g = (V + V_{fw}) \left( \frac{D_{max}}{1 - D_{max}} \right) - V_{fw}$$

$$V_g = (1.11 + 0.6) \left( \frac{0.55}{1 - 0.55} \right) - 0.6$$

$$V_g = 1.49V$$

$$\text{power rating of genel} = \frac{L_m I_m^2 f_s}{2}$$

$$L_m = \frac{211.8 \times 10^6}{87} = 2.43 \times 10^6$$

$$P = \frac{2.43 \times 10^6 \times (0.01 \times 8.88)^2 \times 50000}{2} \approx 0.479 \text{ mW}$$

$$R_s = \frac{V}{I/f_n} = \frac{1.11}{8.88/8.7}$$

$$\boxed{R_s = 10.875 \Omega}$$

$$P = I^2 R_{ms} R$$

$$P = (0.075)^2 \times 10.8 = 0.061 W$$

(10)

$$I = 1.11 A \rightarrow V = 0.139 V$$

$$0.125 V \rightarrow 1A$$

$$1.11 A \rightarrow 1.11 \times 0.125 = 0.139 V$$

$$nL_m \geq \frac{3.2V}{I f_s}$$

$$nL_m = \frac{3.2 \times 0.139}{50 \times 10^3 \times 1.11} \approx 8.01 \mu H \cdot T$$

$$I_m = \frac{DV}{2nL_m f_s} = \frac{0.36V}{2nL_m f_s}$$

$$I_m = \frac{0.36 \times 0.139}{2 \times 8.01 \times 10^{-6} \times 50K} = 0.0624$$

but  $I_m >> 1\% \text{ of } I$

$$1\% \text{ of } I = 0.011$$

$$0.011 = \frac{0.36 \times 1}{2 \times 50000 \times nL_m}$$

$$nL_m = 327.27 \mu H \cdot T$$

$$B_m = \frac{DV}{2 \pi f_s A_c} = \frac{0.36 \times 0.139}{2 \times 50000 \times \pi A_c}$$

core	$A_c$	$A_L$	$n$	$B_m$
T <sub>10</sub>	6.2	765	427	$1.39 \times 10^{-4}$
T <sub>12</sub>	12	1180	217	$1.5 \times 10^{-4}$
T <sub>20</sub>	22	1130	209	
T <sub>32</sub>	61	2427	134	
T <sub>45</sub>	93	2367	138	

$$J = 2.5 A/m^2 = I/A$$

$$A = I/J = 4 \times \frac{1.22}{2.5} = 1.76 \text{ mm}^2 \rightarrow \text{SWG } 15$$

So, we choose T<sub>45</sub> toroid core

138 turns of SWG 15

$$R_s = \frac{V}{I/n} = \frac{0.139}{\frac{1.11}{138}}$$

$$R_s = 17.28 \Omega$$

$$P = I_{rms}^2 R_s = 4.41^2 \times 17.28 = 1.14$$

$$R_s = 17.28 \Omega / 1.5 W$$

(11)

$$V_o = \frac{2V_{in} \Delta}{n}$$

$$D_{max} = \frac{n V_o}{2 V_{in} \Delta} = \frac{6 \times 12}{2 \times 180} = 0.2$$

CT design parameters

$$I = \frac{10}{6} = 1.67 A$$

$$\alpha = 1.1.$$

$$D_{max} = 0.2$$

$$V = 0.5 \times 1.67 = 0.833$$

$$f_s = 80 \text{ kHz}$$

$$v_{f\omega} = 0.6$$

$$I_m = 1\% \text{ of } I$$

$$nL_m = \frac{100 D_{max} (V + v_{f\omega})}{2 f_s I} = \frac{100 \times 0.2 (0.833 + 0.6)}{1 \times 80 \times 10^3 \times 1.67}$$

$$nL_m = 0.215 \mu H$$

core	n	$(I_s)_{rms}$	B_m
T <sub>10</sub>	280	$2.66 \times 10^{-3}$	$2.06 \times 10^{-3}$
T <sub>12</sub>	182	$4.1 \times 10^{-3}$	$1.64 \times 10^{-3}$
T <sub>20</sub>	190	$3.9 \times 10^{-3}$	1
T <sub>32</sub>	88	$8.48 \times 10^{-3}$	1
T <sub>45</sub>	90	$8.29 \times 10^{-3}$	1

T<sub>32</sub>, n=88,  $I_s = 8.48 \times 10^{-3}$  is chosen

$$A = \frac{8.48 \times 10^{-3}}{2.8} = 0.0033 \text{ mm}^2$$

SWG 32 is chosen

$$v_d = \frac{D_{max}}{1-D_{max}} (v + v_{fw})$$

$$v_d = \frac{0.2}{0.8} (0.833 + 0.6) = 0.358V$$

power rating of zener =  $\frac{4\pi I_m^2 R_s}{2}$

$$= \frac{2.42 \times 10^{-6} \times (0.01 \times 1.67)^2 \times 80 \times 10^3}{2}$$

$$= 27.1 \mu W$$

$$R_s = \frac{v}{I_m} = \frac{0.833}{1.67/88} = 43.89 \Omega$$