

1. Given data:

DC Separately Excited motor

$$V_{dc} = 600V$$


$$R_a = 0.05\Omega$$

$$K_t = 1.527 \text{ V/A rad/sec}$$

$$I_a = 250 \text{ A}$$

$$I_f = 2.5 \text{ A}$$

$$d = 0.6$$

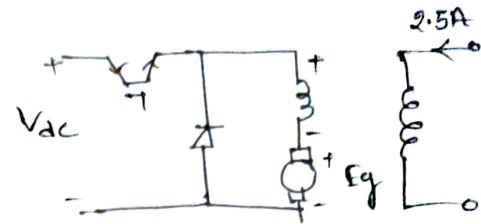

a) Input power ^{from} source = ?

b) Rim of the dc source-DC converter = ?

c) Motor speed = ?

d) Torque = ?

$$V = dV_{dc}$$

$$= 0.6 \times 600$$

$$V = 360V$$

$$V = I_a R_a + E_b$$

$$360 = 250(0.05) + E_b$$

$$360 = 12.5 + E_b$$

$$E_b = 360 - 12.5$$

$$E_b = 347.5$$

a) Assume, loss free DC-DC converter

$$\text{then, } V_{in} I_{in} = V \times I_a$$

$$P_{in} = 360 \times 250$$

$$= 90 \text{ kW}$$

$$b) R_{in} = \frac{V_{in}}{I_{in}}$$

$$I_{in} = \frac{P_{in}}{V_{in}} = \frac{90 \times 10^3}{600}$$

$$I_{in} = 150$$

$$R_{in} = \frac{600}{150}$$

$$R_{in} = 4 \Omega$$

$$c) \text{ Motor speed} = \frac{E_b}{K_b I_f} \quad \left\{ K_b \times I_f = K = 3.8175 \right\}$$

$$= \frac{347.5}{2.5 \times 1.527}$$

$$= 91.028 \text{ rad/sec}$$

$$= 869.25 \text{ rpm}$$

d) Developed torque,

$$\omega_m = \frac{dV}{K} - \frac{R_a}{K^2} T$$

$$\Rightarrow 91.028 = \frac{360}{3.8175} - \frac{0.05}{3.8175^2} (T)$$

$$\Rightarrow T = 3.274 (3.8175)^2 / 0.05$$

$$\therefore T = 954.921 \text{ N-m}$$

2. Given data

Regenerative Braking

Dc Series motor

$$V_s = 600V$$


$$R_a = 0.02 \Omega$$

$$R_f = 0.03 \Omega$$

$$K_v = 15.27 \text{ mV/A rad/sec}$$

$$I_a = 250 \text{ A}$$

$$d = 0.6$$

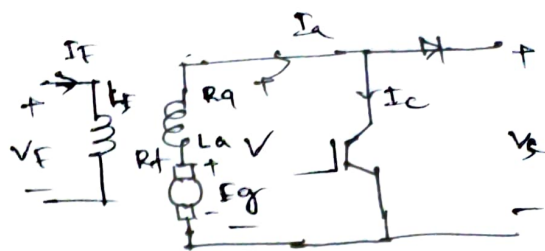

ckt diagram

- Avg voltage across the converter = ?
- Power gen to the dc supply = ?
- Eq. resistance of motor acts as gen = ?
- motor speed = ?

From the figure, it looks like a boost converter

- V is the voltage across the converter

$$\begin{cases} V_o = \frac{1}{1-d} V_{in} \end{cases}$$

$$\text{Here, } V_o = V_s$$

$$V_{in} = V$$

$$V = V_s (1-d)$$

$$= 600 (1-0.6)$$

$$= 240$$

b) Gen power = $E_g I_a$

$$E_g I_a = 252.5 \times 250$$
$$= 63.125 \text{ kW}$$

c) Seq. resistance = $\frac{V}{I_a} = \frac{240}{250} = 0.96 \Omega$

d) Motor speed, $\omega_m \Rightarrow$

$$V = E_g - (I_a R_a + I_a R_{sc})$$

$$240 = E_g - 250(0.02 + 0.03)$$

$$E_g = 240 + 250(0.05)$$

$$E_g = 252.5 \text{ V}$$

$$\text{Speed} = \frac{E_g}{K}$$

$$K = K_b I_a = 15.27 \times 10^{-3} \times 250 \text{ V rad/sec}$$
$$= 3.817 \text{ V/rad/sec}$$


$$\text{Speed} = \frac{252.5 \text{ V}}{3.817 \text{ V/rad/sec}}$$

$$= 66.15 \text{ rad/sec}$$

$$= 631.68 \text{ rpm}$$

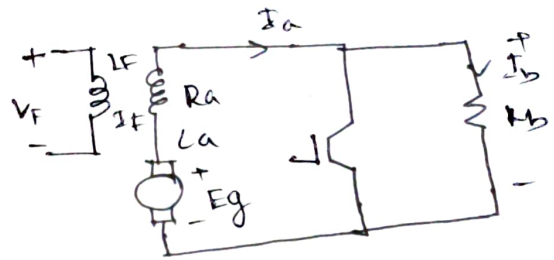3. Given data

Rheostat Braking
DC Separately excited Motor



$$R_a = 0.05 \Omega$$

$$R_b = 5 \Omega$$

$$K_v = 1.527 \text{ V/A rad/sec}$$

$$I_f = 1.5 \text{ A}$$

$$I_a = 150 \text{ A}$$

$$d = 0.4$$

$$K = K_v I_f$$

$$= 1.527 \times 1.5$$

$$= 2.29 \text{ V rad/sec}$$

$$I_b = I_a (1-d) \text{ as per boost converter topology}$$

$$i_b = 150 (1 - 0.4)$$

$$= 90 \text{ A}$$

$$V_b = i_b \times R_b$$

$$= 90 \times 5 = 450 \text{ V}$$

$$V = 450 (1 - 0.4)$$

$$= 270 \text{ V}$$

$$E_g = V + I_a R_a$$

$$= 270 + (250 \times 0.05)$$

$$E_g = 282.5 \text{ V}$$

a) Voltage across converter = 270V

b) Power dissipated in $R_b = I_b^2 R_b$

$$= 90^2 \times 5$$

$$= 40.5 \text{ kW}$$

c) Eq. Resistance = $\frac{270}{1.50}$

$$= 1.8 \Omega$$

d) Motor speed; $\omega_m = \frac{E_g}{k}$

$$= \frac{282.5}{2.29}$$

$$= 123.36 \text{ rad/sec}$$

$$= 1178.02 \text{ rpm}$$

4. Given data:

$$V_m = 24V$$

$$f_s = 1\text{kHz}$$

$$d = ?$$

Speed \Rightarrow 0 to 1 pu

$$\text{load} = 2\text{ pu}$$

Motor details:

$$1\text{hp}; 10V, 2500\text{rpm}$$

$$\eta = 78.5\%, R_a = 0.01\Omega$$

$$L_a = 0.002\text{H}$$

$$k_b = 0.03019\text{ V rad/sec}$$

$$\text{chopper drop voltage} = 1V$$

1st quadrant

Normalized values,

$$V_b = 10V (\text{Base})$$

$$V_n (\text{normalized voltage}) = \frac{V_s}{V_b} = \frac{24-1}{10} = 2.5\text{ pu}$$

$$\omega_m = \frac{2500 \times 2\pi}{60} = 261.79\text{ rad/sec}$$

$$I_{an} = \frac{0/p}{V_b \times \eta} = \frac{1 \times 746}{10 \times 0.785} = 95\text{A} = I_b (\text{base})$$

$$R_{au} = \frac{I_b R_a}{V_b} = \frac{95 \times 0.001}{10}$$

$$= 0.095 \text{ pu}$$

$$T_{eq} = 2 \text{ pu}$$

Duty cycle

$$d = \frac{T_{eq} R_{au} + \omega_m}{V_n}$$

$$\left\{ \begin{array}{l} \because \omega_m = \frac{dv}{k} - \frac{R}{k^2} T \\ \text{Here, } k = 1 \text{ pu} \end{array} \right\}$$

$$d_{min} = \frac{2 \times 0.095 + 0}{2.3}$$

$$= 0.0826$$

$$d_{max} = \frac{2 \times 0.095 + 1}{2.3} = 0.517$$

So, Range of duty $\Rightarrow 0.0826 \leq d \leq 0.517$