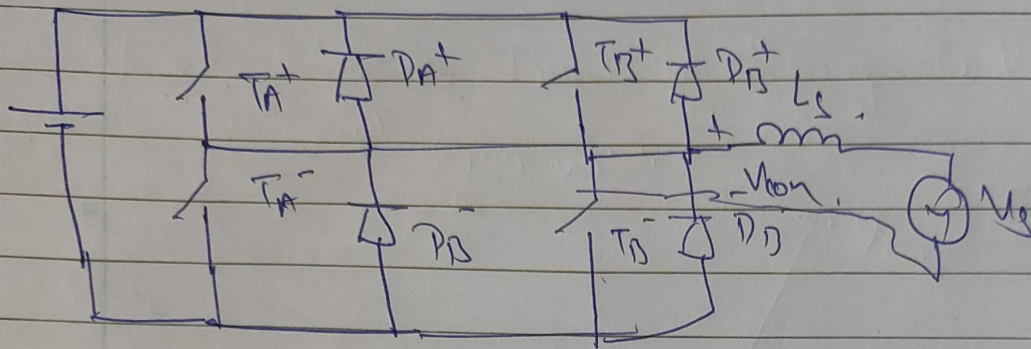


1- $\phi$  full bridge ~~rectifier~~ inverter connected to P.M.



$V_s$   $\rightarrow$  induced back emf of 1- $\phi$  P.M.

$$V_{con} = V_{cs} + V_s$$

$$V_s = L \frac{di_s}{dt}$$

fundamental component of Converter 1,

$$V_{con1} = V_{cs1} + V_s$$

~~Direction of~~

Back emf,  $V_s = V_{con1} - V_{cs1}$   
 $= V_{con1} - \int i_s L_s \frac{d\omega}{dt}$


Direction of  $i_s$   $\rightarrow$  decides the direction of inverter & rectification  
 Modes of operation

## Inversion Mode.

$V_s$  remain const. for small instant.

$I_{s1}$  is lagging  $V_s$  by angle  $\theta$ .

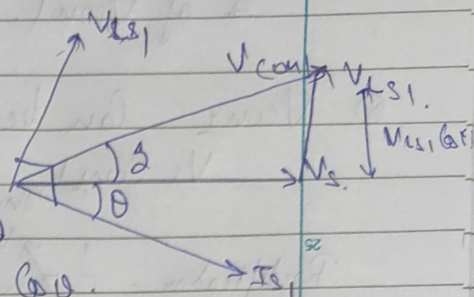$V_{con1}$  leads  $V_s$  by angle  $\phi$ .



$$\text{Real power at AC Side } P = P = V_s I_{s1} \cos \theta$$

$$= V_s \times \frac{V_{con1}}{\omega L_e} \cos \theta$$

$$V_{s1} \cos \theta = V_{con1} \sin \phi$$

$$P = \frac{V_s}{\omega L_e} V_{con1} \sin \phi = \frac{V_s^2}{\omega L_e} \frac{V_{con1}}{V_s} \sin \phi$$

Power flows from dc Side to AC Side  $\rightarrow$  Inversion Mode

$$\text{Reactive Power } Q = V_s I_{s1} \sin (180^\circ - \theta)$$

$$= - V_s I_{s1} \sin \theta$$

$$= - V_s \frac{V_{con1}}{\omega L_e} \sin \theta$$

$$V_{con1} \sin \theta = [V_s - V_{con1} \cos \phi]$$


$$Q = \frac{V_s^2}{\omega L_e} \left[ \frac{V_{con1}}{V_s} \cos \phi - 1 \right]$$

- $\rightarrow$  'Q' is Sum of reactive Power absorbed by Converter & inductor L.
- $\rightarrow$  At very high Switching frequency  $L_e$  can be made very small.
- $\rightarrow$  Then Q is the reactive Power absorbed by the Converter.




⊗ For a given Value of AC Side Side Potential (Back emf)  $V_s$  and the Chosen Value of Inductance  $L_c$ , desired Value of PF  $\cos \phi$  Can be obtained by controlling magnitude & phase angle  $\phi$  of  $V_{con1}$ .

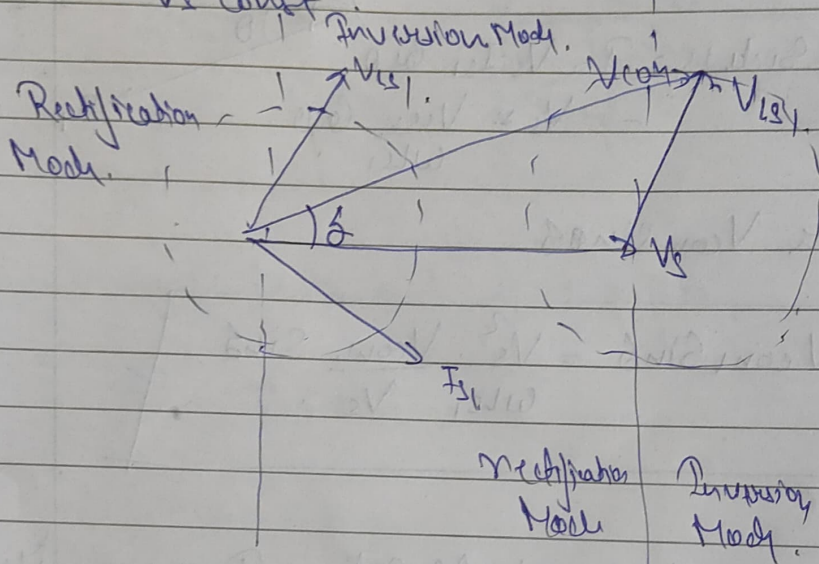
⊗  $V_{con1}$  Can be Varied by keeping the Magnitude of  $I_{s1}$  &  $V_s$  Const.



⊗ Inversion at UPF

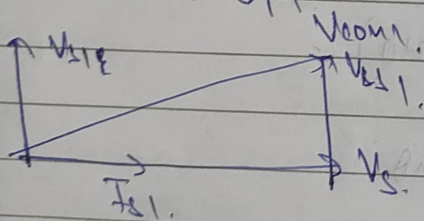

⊗ Rectification at UPF

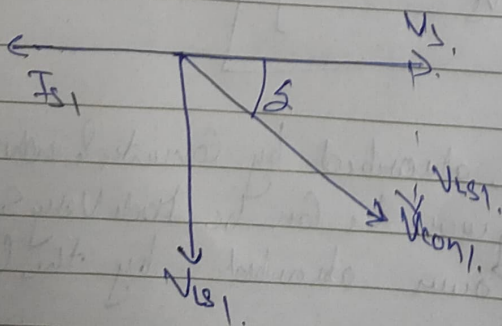

In both Case  $V_{con1} = \sqrt{V_s^2 + (\omega L_c I_{s1})^2}$