

Electrical Drives

Lecture 11 (05-02-2024)

CONVERTERS - Module 2

AC-DC controlled rectifier

approximate model
SIMULINK examples
open-loop
closed-loop

Switch Mode DC-DC converter



2-Q and 4-Q converters
Small signal modeling
unipolar
bipolar
SIMULINK example

Current-controlled for SM converters

Bridge converter
hysteresis
fixed frequency
3-phase VSI
hysteresis
fixed frequency
SVM-based

Switch mode DC-DC converter



Two-quadrant converter

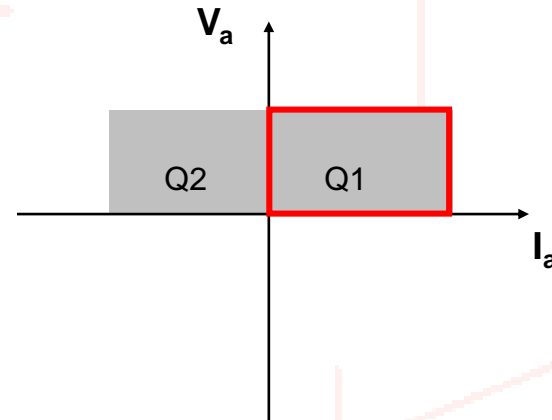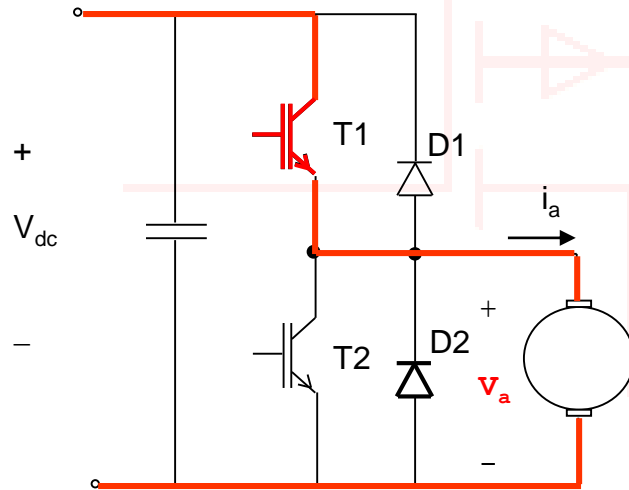


T1 conducts $\rightarrow v_a = V_{dc}$

Switch mode DC-DC converter

Two-quadrant converter

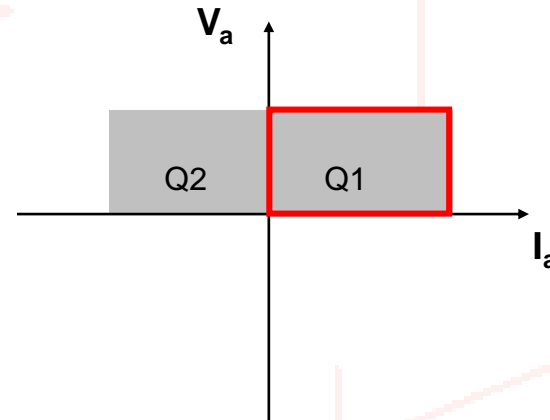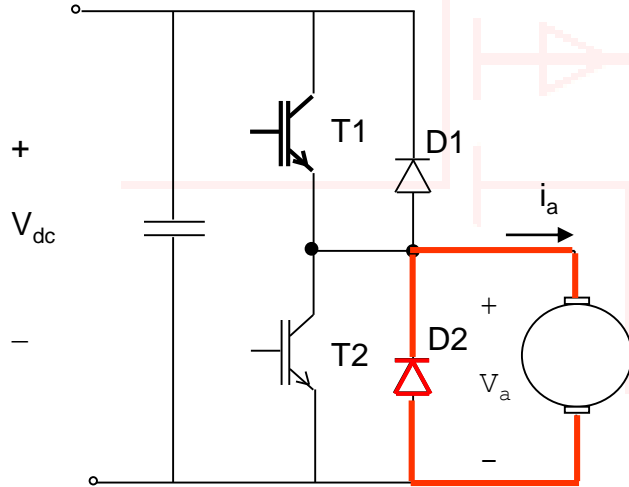


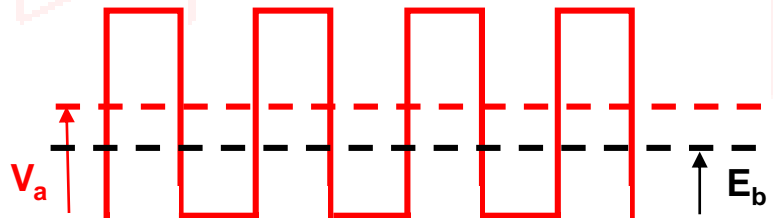
D2 conducts $\rightarrow v_a = 0$ T1 conducts $\rightarrow v_a = V_{dc}$



Quadrant 1 The average voltage is made larger than the back emf

Switch mode DC-DC converter



Two-quadrant converter

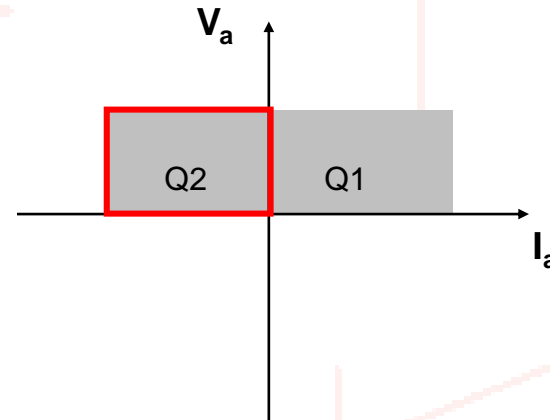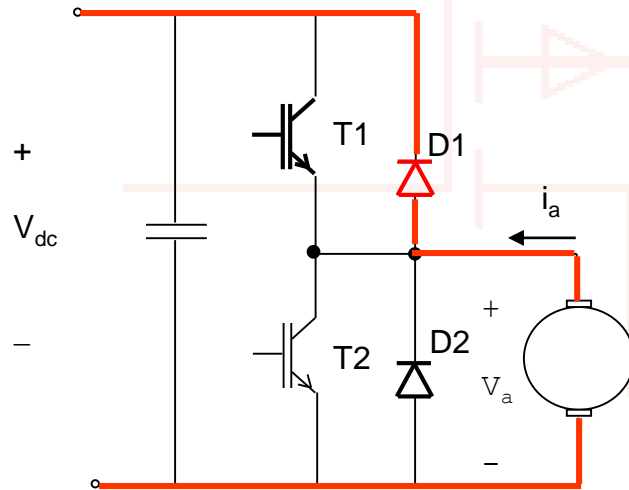


D1 conducts $\rightarrow v_a = V_{dc}$

Switch mode DC-DC converter

Two-quadrant converter

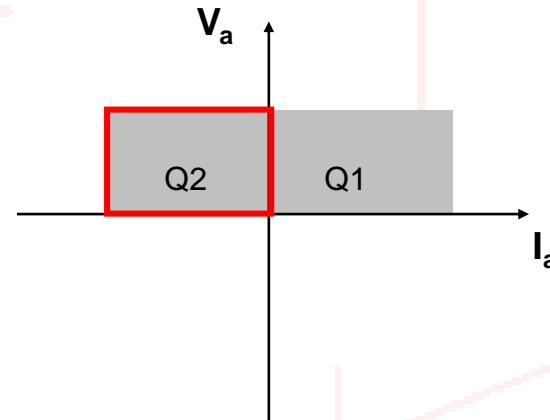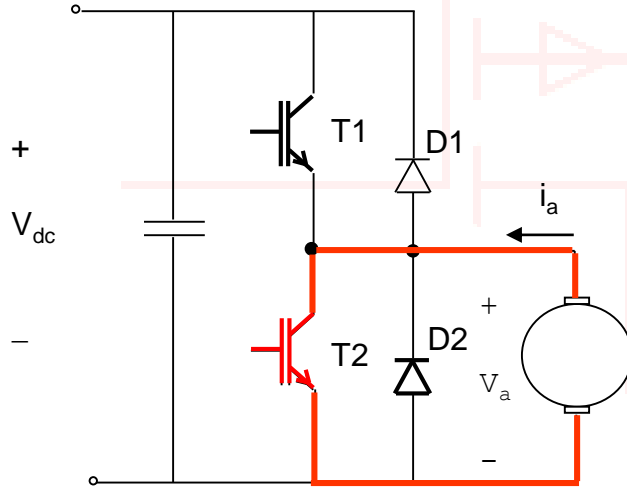

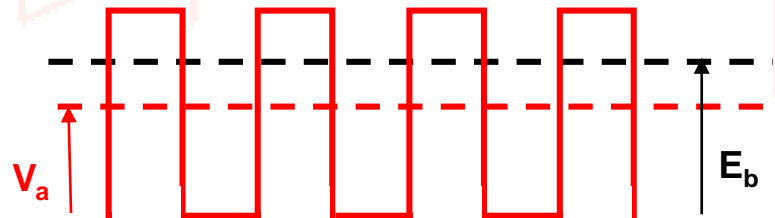T2 conducts $\rightarrow v_a = 0$ D1 conducts $\rightarrow v_a = V_{dc}$




Quadrant 2 The average voltage is made smaller than the back emf, thus forcing the current to flow in the reverse direction


Switch mode DC-DC converter

Two-quadrant converter

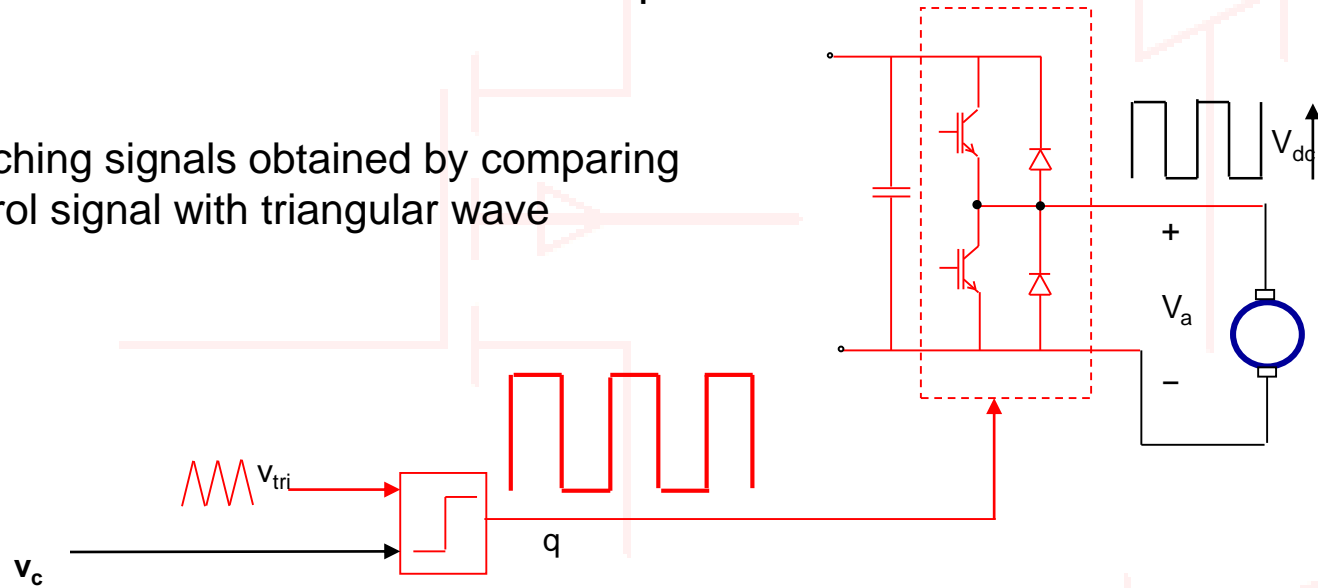Switching signals obtained by comparing control signal with triangular wave



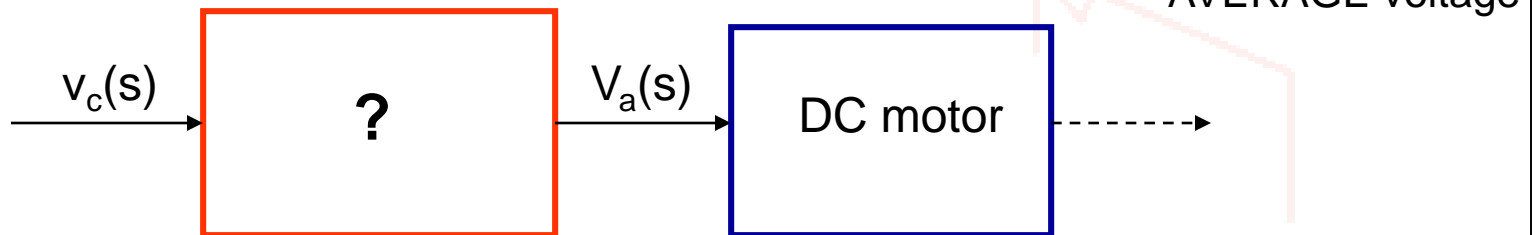
We want to establish a relation between v_c and V_a



AVERAGE voltage

Switch mode DC-DC converter

Two-quadrant converter

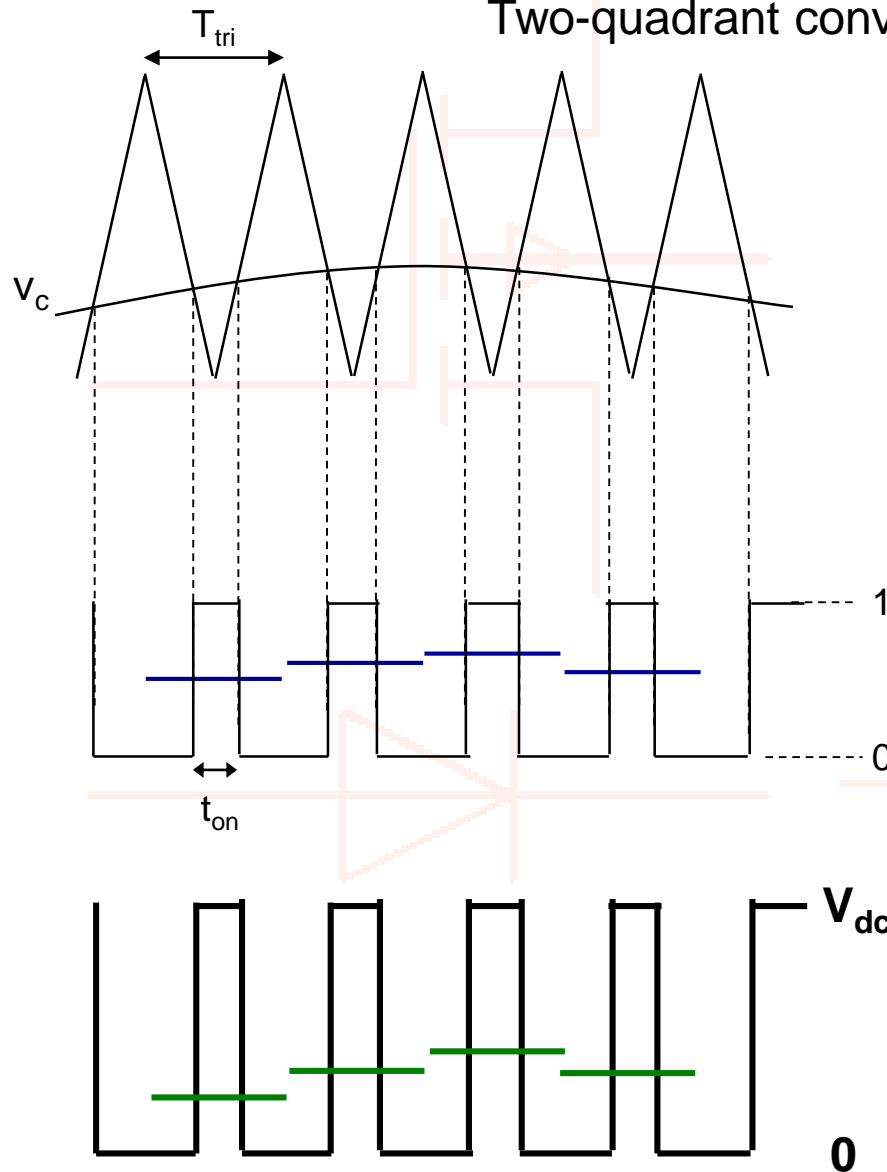

$$q = \begin{cases} 1 & V_c > V_{tri} \\ 0 & V_c < V_{tri} \end{cases}$$


$$d = \frac{1}{T_{tri}} \int_t^{t+T_{tri}} q dt$$

$$= \frac{t_{on}}{T_{tri}}$$

$$V_a = \frac{1}{T_{tri}} \int_0^{dT_{tri}} V_{dc} dt = dV_{dc}$$

Switch mode DC-DC converter


Two-quadrant converter

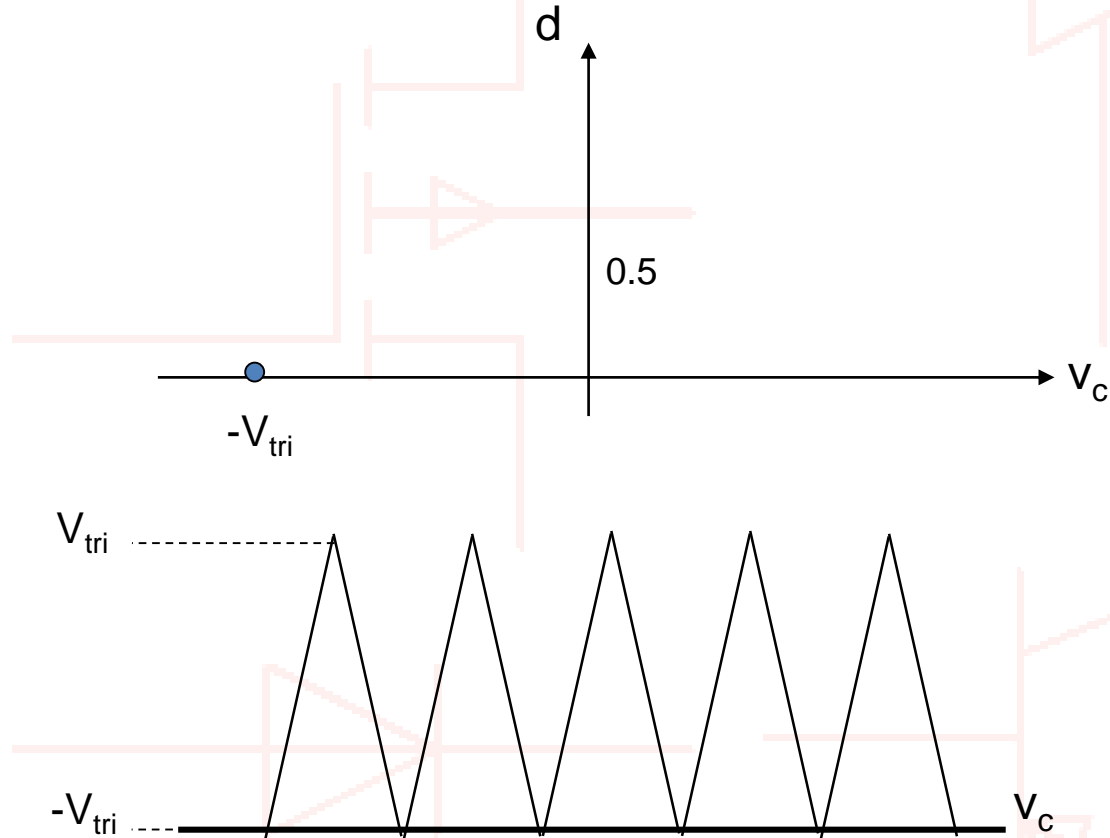

For $v_c = -V_{tri} \rightarrow d = 0$

Switch mode DC-DC converter

Two-quadrant converter

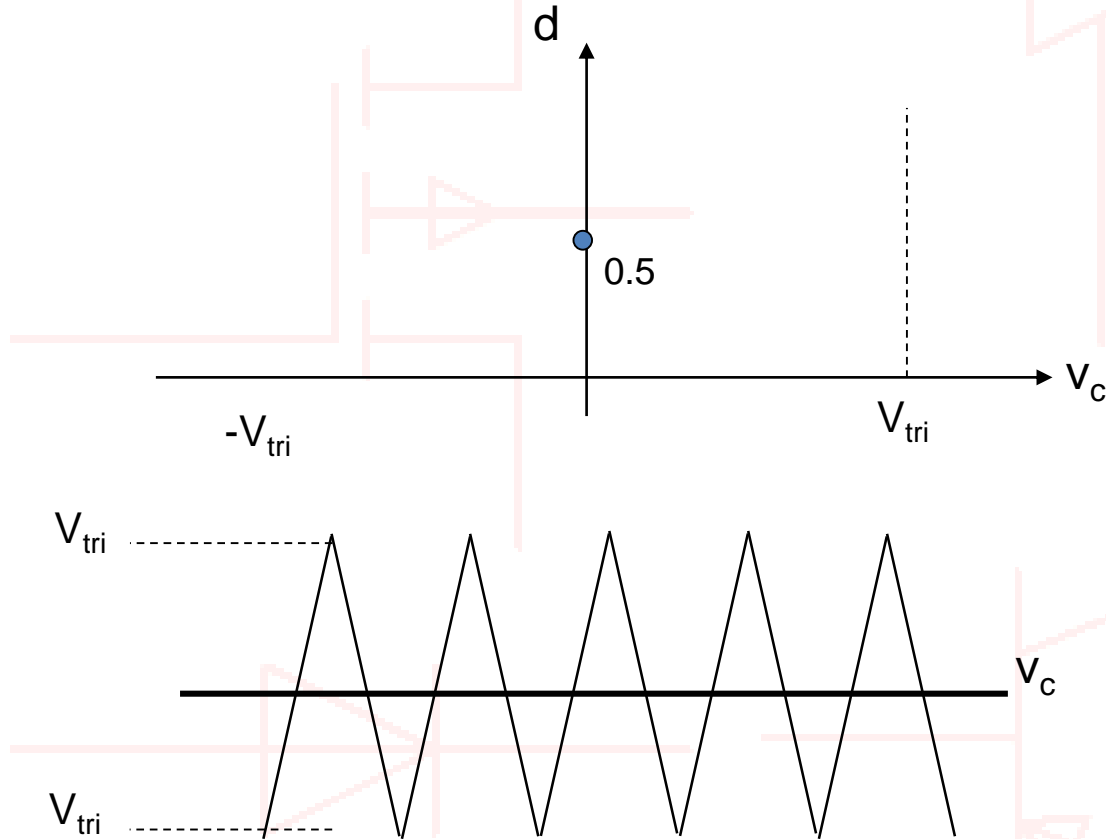


For $v_c = -V_{tri} \rightarrow d = 0$

For $v_c = 0 \rightarrow d = 0.5$

For $v_c = V_{tri} \rightarrow d = 1$

Switch mode DC-DC converter

Two-quadrant converter

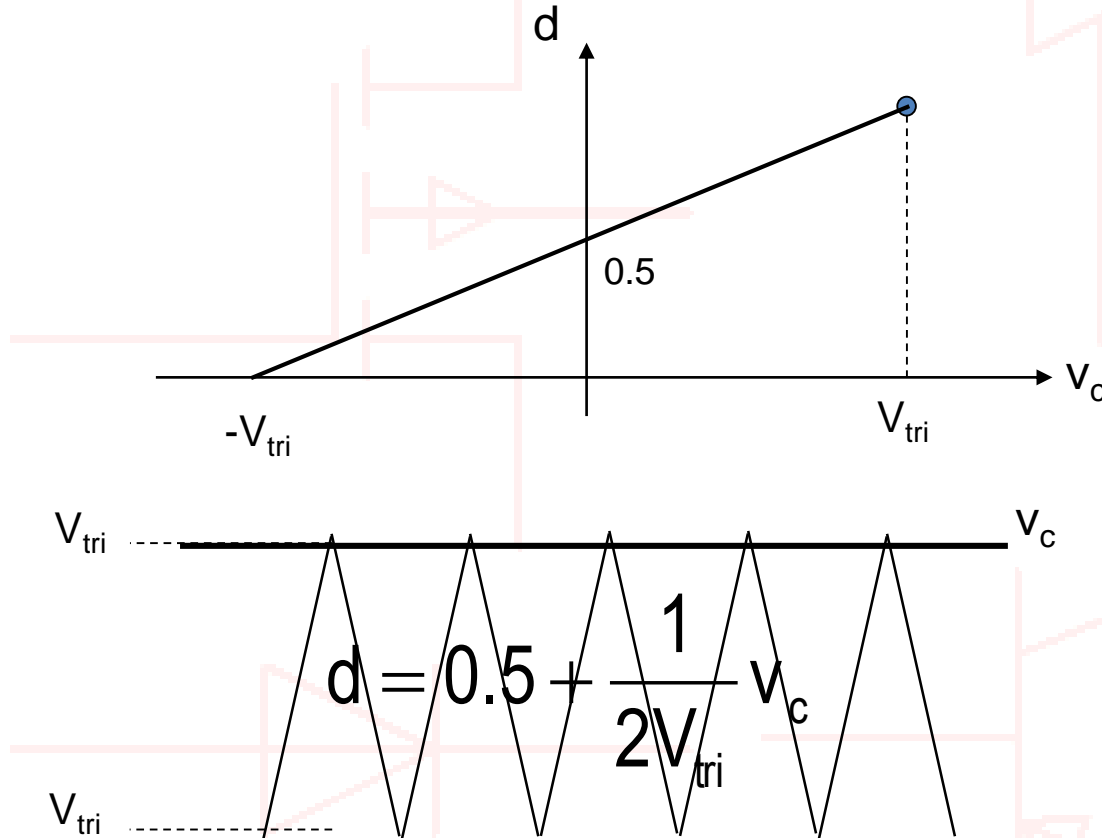

For $v_c = -V_{tri} \rightarrow d = 0$

For $v_c = 0 \rightarrow d = 0.5$

For $v_c = V_{tri} \rightarrow d = 1$

Switch mode DC-DC converter

Two-quadrant converter

Thus relation between v_c and V_a is obtained as:

$$V_a = 0.5V_{dc} + \frac{V_{dc}}{2V_{tri}} v_c$$

Introducing perturbation in v_c and V_a and separating DC and AC components:

DC:

$$V_a = 0.5V_{dc} + \frac{V_{dc}}{2V_{tri}} v_c$$

AC:


$$\tilde{v}_a = \frac{V_{dc}}{2V_{tri}} \tilde{v}_c$$

Switch mode DC-DC converter

Two-quadrant converter


Taking Laplace Transform on the AC, the transfer function is obtained as:
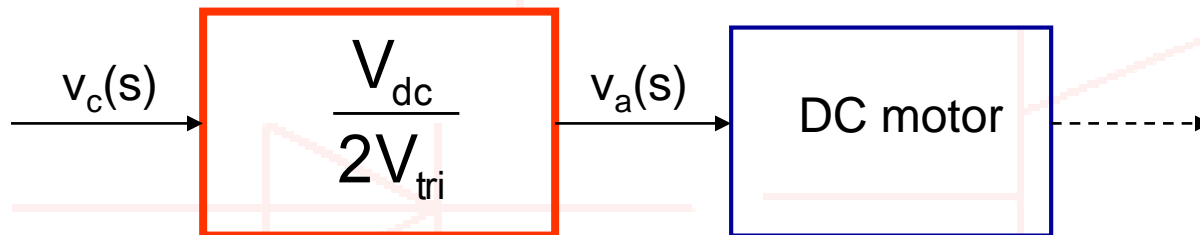
$$\frac{v_a(s)}{v_c(s)} = \frac{V_{dc}}{2V_{tri}}$$



Switch mode DC-DC converter

Four-quadrant converter

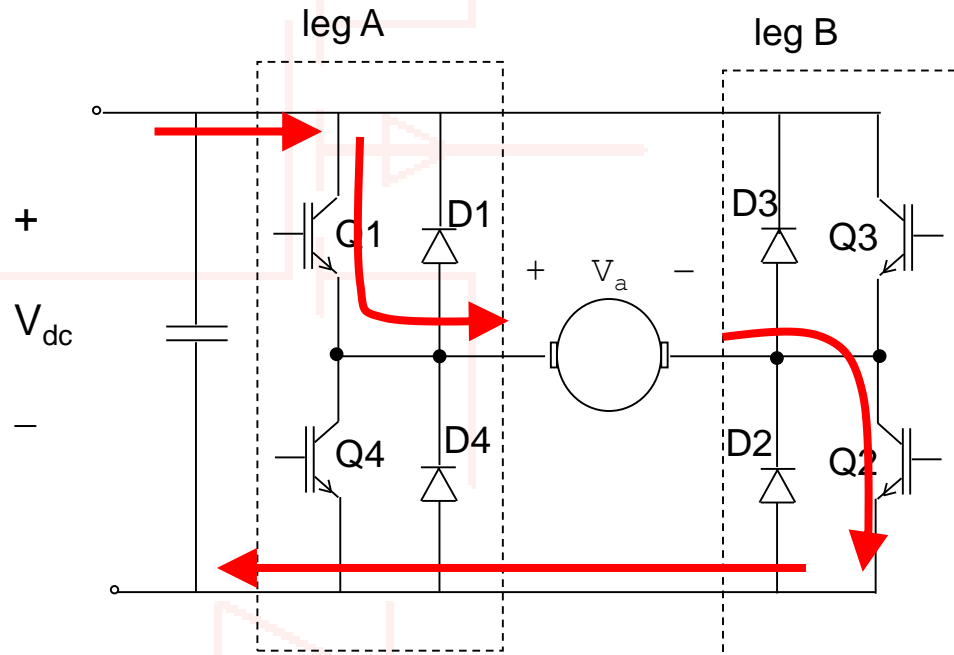


Positive current

$$v_a = V_{dc} \quad \text{when Q1 and Q2 are ON}$$

Switch mode DC-DC converter

Four-quadrant converter

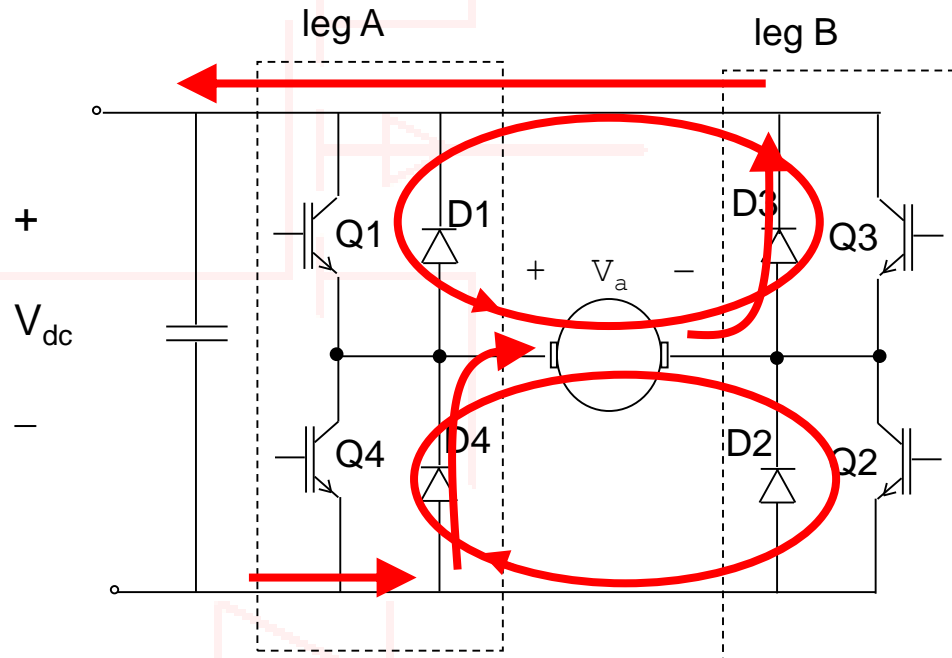

Positive current

$$v_a = V_{dc}$$

when Q1 and Q2 are ON

$$v_a = -V_{dc}$$


when D3 and D4 are ON

$$v_a = 0$$

when current freewheels through Q and D

Switch mode DC-DC converter

Four-quadrant converter

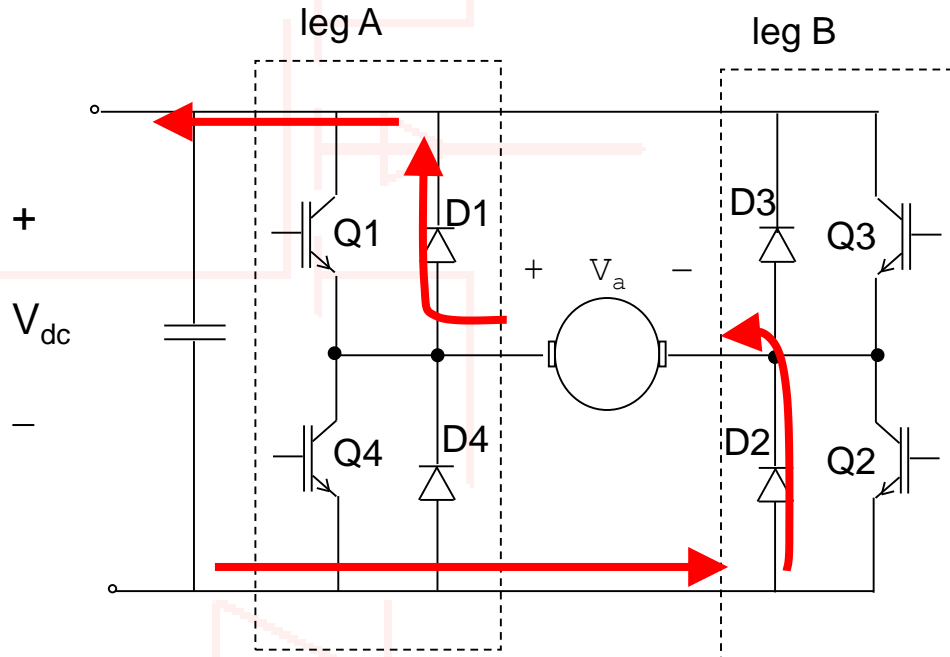

Positive current

$$v_a = V_{dc}$$

when Q1 and Q2 are ON

$$v_a = -V_{dc}$$

when D3 and D4 are ON

$$v_a = 0$$

when current freewheels through Q and D


Negative current

$$v_a = V_{dc}$$

when D1 and D2 are ON

Switch mode DC-DC converter

Four-quadrant converter

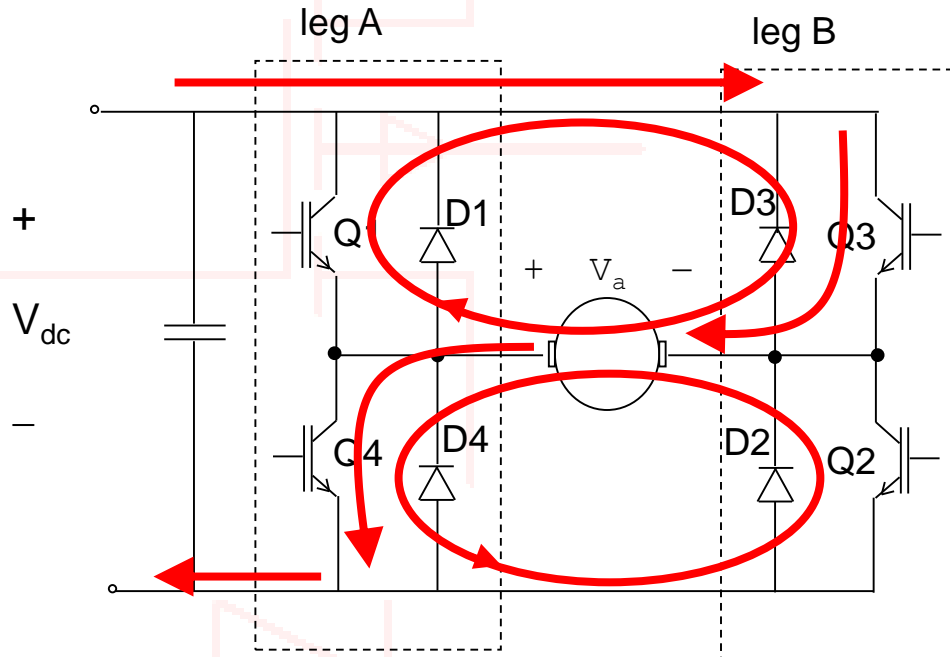

Positive current

$$v_a = V_{dc}$$

when Q1 and Q2 are ON

$$v_a = -V_{dc}$$

when D3 and D4 are ON

$$v_a = 0$$

when current freewheels through Q and D

Negative current

$$v_a = V_{dc}$$

when D1 and D2 are ON

$$v_a = -V_{dc}$$

when Q3 and Q4 are ON



$$v_a = 0$$

when current freewheels through Q and D

Switch mode DC-DC converter

Four-quadrant converter

Bipolar switching scheme

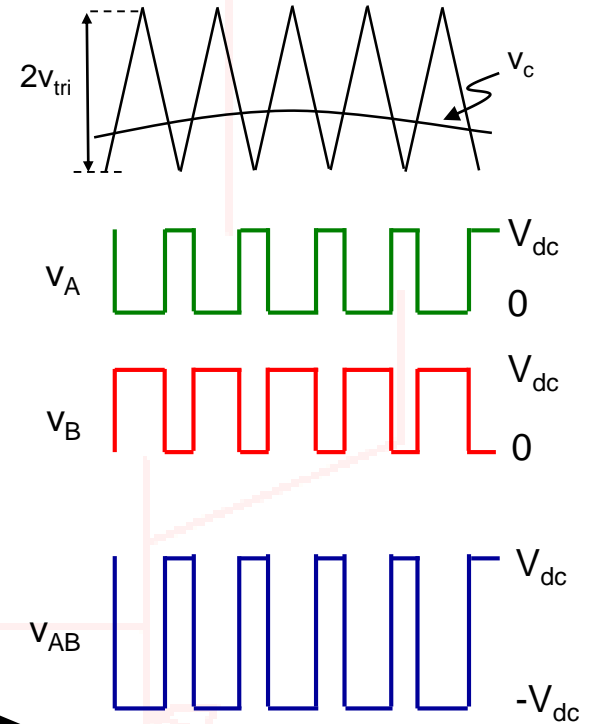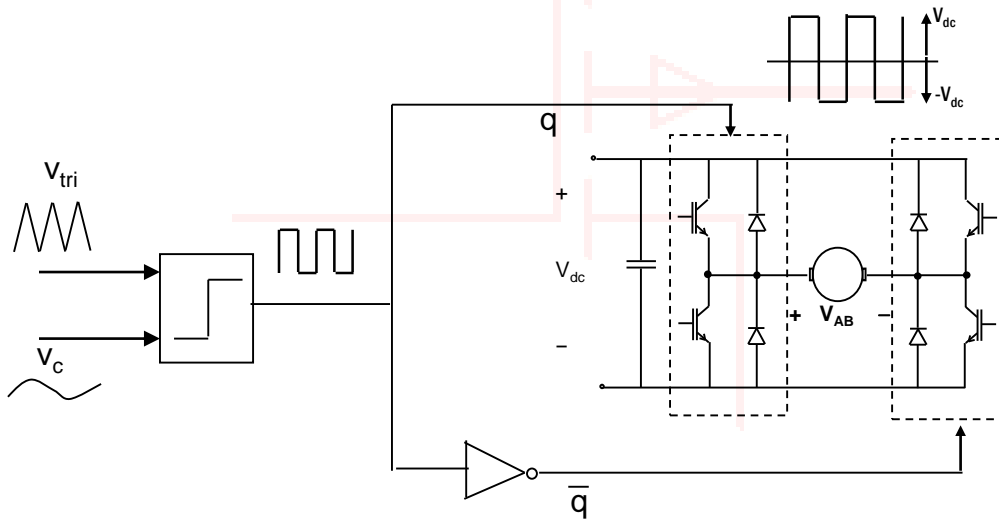

$$d_A = 0.5 + \frac{v_c}{2V_{tri}}$$

$$d_B = 1 - d_A = 0.5 - \frac{v_c}{2V_{tri}}$$

$$V_A = 0.5V_{dc} + \frac{V_{dc}}{2V_{tri}} v_c$$

$$V_B = 0.5V_{dc} - \frac{V_{dc}}{2V_{tri}} v_c$$


$$V_A - V_B = V_{AB} = \frac{V_{dc}}{V_{tri}} v_c$$

Switch mode DC-DC converter

Four-quadrant converter

Bipolar switching scheme


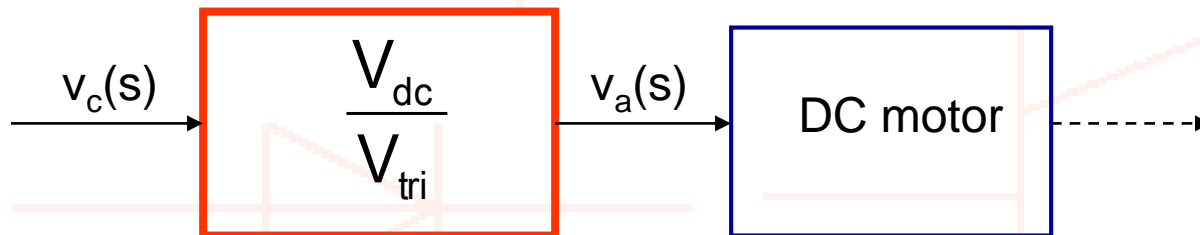
$$\frac{v_a(s)}{v_c(s)} = \frac{V_{dc}}{V_{tri}}$$



Switch mode DC-DC converter

Four-quadrant converter

Unipolar switching scheme

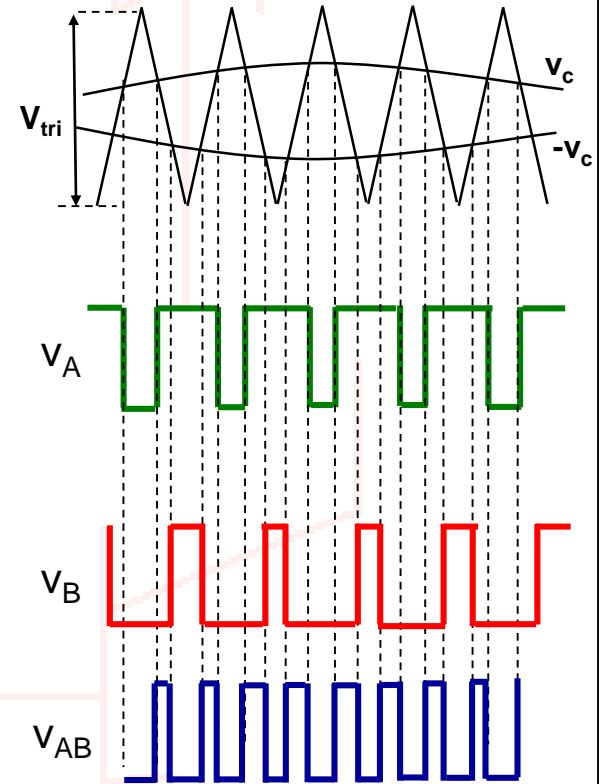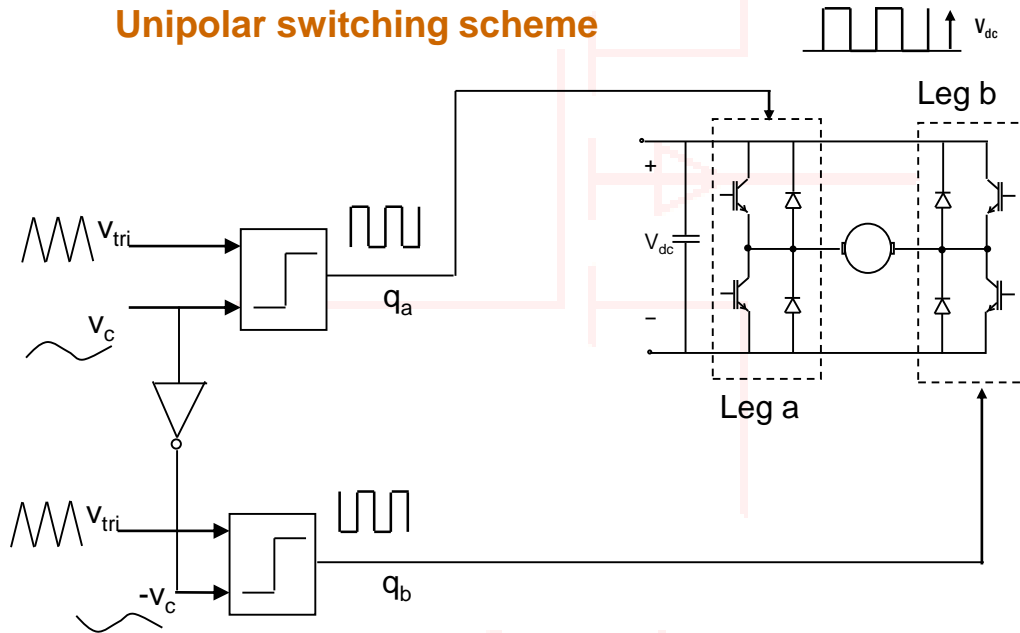

$$d_A = 0.5 + \frac{v_c}{2V_{tri}}$$

$$d_B = 0.5 + \frac{-v_c}{2V_{tri}}$$

$$V_A = 0.5V_{dc} + \frac{V_{dc}}{2V_{tri}} v_c$$

$$V_B = 0.5V_{dc} - \frac{V_{dc}}{2V_{tri}} v_c$$

$$V_A - V_B = V_{AB} = \frac{V_{dc}}{V_{tri}} v_c$$


The same average value we've seen for bipolar !

Switch mode DC-DC converter

Four-quadrant converter

Unipolar switching scheme
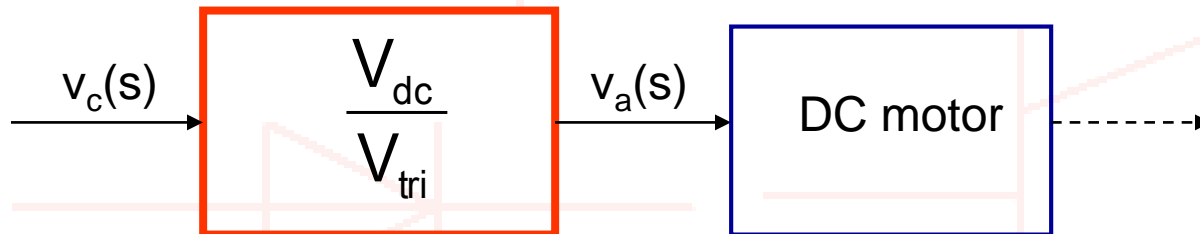
$$\frac{v_a(s)}{v_c(s)} = \frac{V_{dc}}{V_{tri}}$$




Closed-Loop Control of DC Drives

- The speed of dc motors changes with the load torque.
- To maintain a constant speed, the armature (and or field) voltage should be varied continuously by varying the delay angle of ac-dc converters or duty cycle of dc-dc converters.
- In practical drive systems it is required to operate the drive at a constant torque or constant power; in addition, controlled acceleration and deceleration are required.
- Most industrial drives operate as closed-loop feedback systems.
- A closed-loop control system has the advantages of improved accuracy, fast dynamic response, and reduced effects of load disturbances and system nonlinearities.

Closed-Loop Control of DC Drives

- The block diagram of a closed-loop converter-fed separately excited dc drive is shown in Figure .
- If the speed of the motor decreases due to the application of additional load torque, the speed error V_e increases.
- The speed controller responds with an increased control signal V_c , change the delay angle or duty cycle of the converter, and increase the armature voltage of the motor.
- An increased armature voltage develops more torque to restore the motor speed to the original value.
- The drive normally passes through a transient period until the developed torque is equal to the load torque.

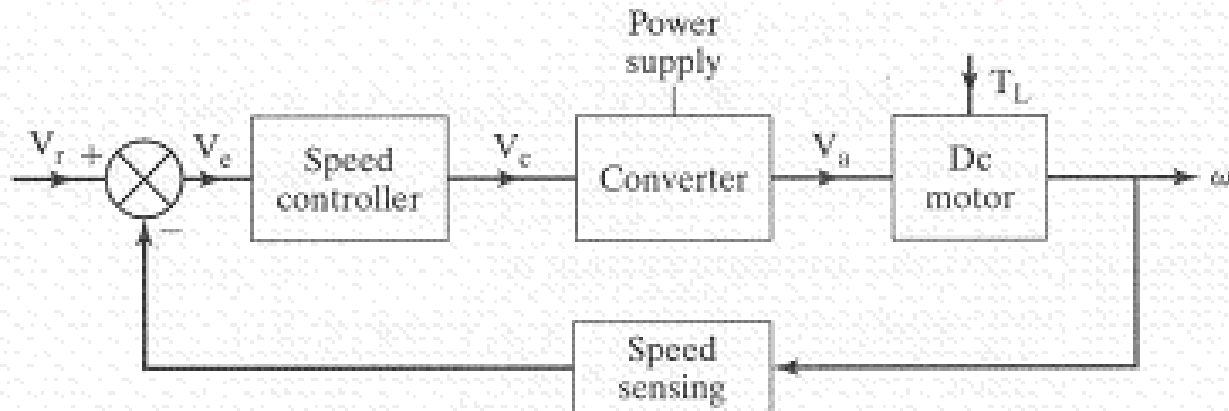

Modelling of Converters

A control technique to overcome this nonlinear characteristic and the accompanying undesirable dynamic behavior is given in the following. The control input to determine the delay angle is modified to be

$$\alpha = \cos^{-1} \left(\frac{v_c}{V_{cm}} \right) = \cos^{-1} (v_{cn})$$

where v_c is the control input and V_{cm} is the maximum of the absolute value of the control voltage.

$$V_{dc} = \frac{3}{\pi} V_m \cos \alpha = \frac{3}{\pi} V_m \cos (\cos^{-1} v_{cn})$$

$$= \left[\frac{3}{\pi} V_m \right] v_{cn} = \left[\frac{3}{\pi} \frac{V_m}{V_{cm}} \right] v_c = K_r v_c$$

where v_{cn} is the normalized control voltage and K_r is the gain of the converter,

Modelling of Converters

$$K_r = \frac{3}{\pi} \frac{V_m}{V_{cm}} = \frac{3\sqrt{2}V}{\pi V_{cm}} = 1.35 \frac{V}{V_{cm}}$$

where V is the rms line-to-line voltage.

Then the modified transfer characteristic is linear with a slope of K_r . The control voltage is normalized to keep its magnitude less than or equal to 1, to be able to obtain the inverse cosine of it.

Transfer function model of 3 ϕ Converter

The converter can be considered as a black box with a certain gain and phase delay for modeling and use in control studies. The gain of the linearized controller-based converter for a maximum control voltage V_{cm} is

$$K_r = \frac{1.35V}{V_{cm}}, V/V$$

The converter is a sampled-data system. The sampling interval gives an indication of its time delay. Once a thyristor is switched on, its triggering angle cannot be changed. The new triggering delay can be implemented with the succeeding thyristor gating. In the meanwhile, the delay angle can be corrected and will be ready for implementation within 60° , i.e., the angle between two thyristors' gating. Statistically, the delay may be treated as one half of this interval; in time, it is equal to

$$T_r = \frac{60/2}{360} \times (\text{time period of one cycle}) = \frac{1}{12} \times \frac{1}{f_s}, s$$

Transfer function model of 3 ϕ Converter

For a 60-Hz supply-voltage source, note that the time delay is equal to 1.388 ms. The converter is then modeled with its gain and time delay as

$$G_r(s) = K_r e^{-T_r s}$$

and equation can also be approximated as a first-order time lag and given as


$$G_r(s) = \frac{K_r}{(1 + sT_r)}$$

Many low-performance systems have a simple controller with no linearization of its transfer characteristic. The transfer characteristic in such a case is nonlinear. Then, the gain of the converter is obtained as a small-signal gain given by

$$K_r = \frac{\delta V_{dc}}{\delta \alpha} = \frac{\delta}{\delta \alpha} \{1.35 \text{ V} \cos \alpha\} = -1.35 \text{ V} \sin \alpha$$

3 ϕ Converter fed DC Motor Drive

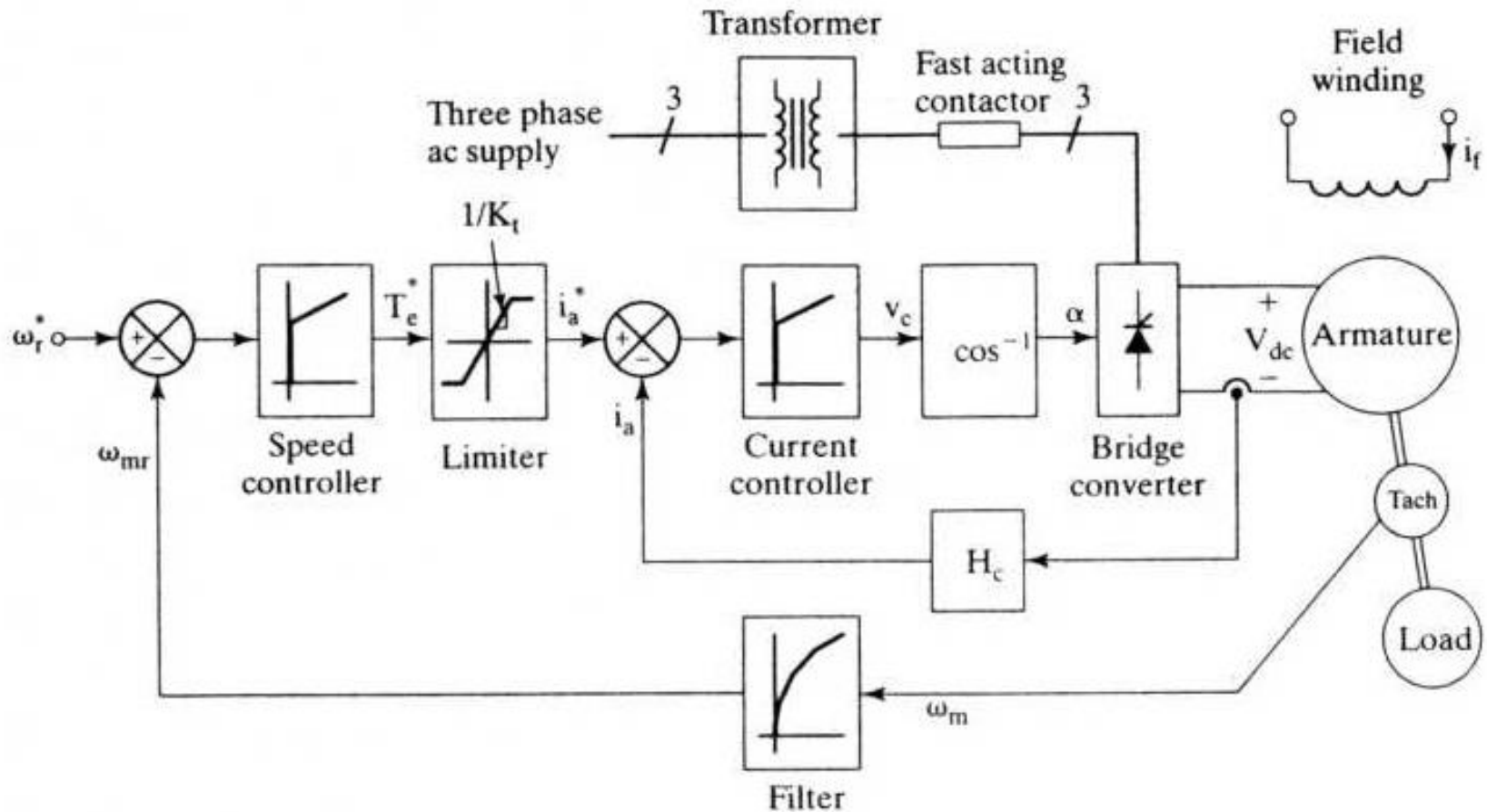The control schematic of a two-quadrant converter-controlled separately-excited dc motor drive is shown in Figure



Transfer functions of the sub systems

DC Motor and load

The dc machine contains an inner loop due to the induced emf. It is not physically seen; it is magnetically coupled. The inner current loop will cross this back-emf loop, creating a complexity in the development of the model. It is shown in Figure

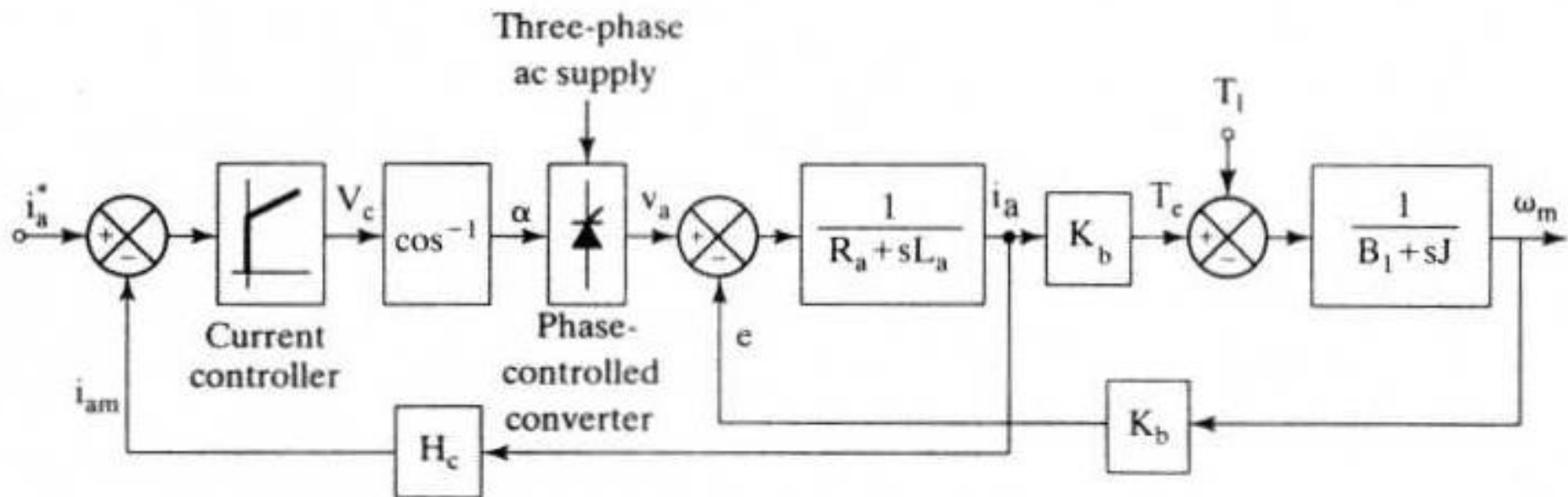


Figure 3.27 DC motor and current-control loop

DC Motor and load

The interactions of these loops can be decoupled by suitably redrawing the block diagram. The development of such a block diagram for the dc machine is shown in Figure 3.28, step by step. The load is assumed to be proportional to speed and is given as

$$T_l = B_l \omega_m$$

To decouple the inner current loop from the machine-inherent induced-emf loop, it is necessary to split the transfer function between the speed and voltage into two cascade transfer functions, first between speed and armature current and then between armature current and input voltage, represented as

$$\frac{\omega_m(s)}{V_a(s)} = \frac{\omega_m(s)}{I_a(s)} \cdot \frac{I_a(s)}{V_a(s)}$$

where


$$\frac{\omega_m(s)}{I_a(s)} = \frac{K_b}{B_t(1 + sT_m)}$$

$$\frac{I_a(s)}{V_a(s)} = K_1 \frac{(1 + sT_m)}{(1 + sT_1)(1 + sT_2)}$$

$$T_m = \frac{J}{B_t}$$


$$B_t = B_1 + B_l$$

DC Motor and load

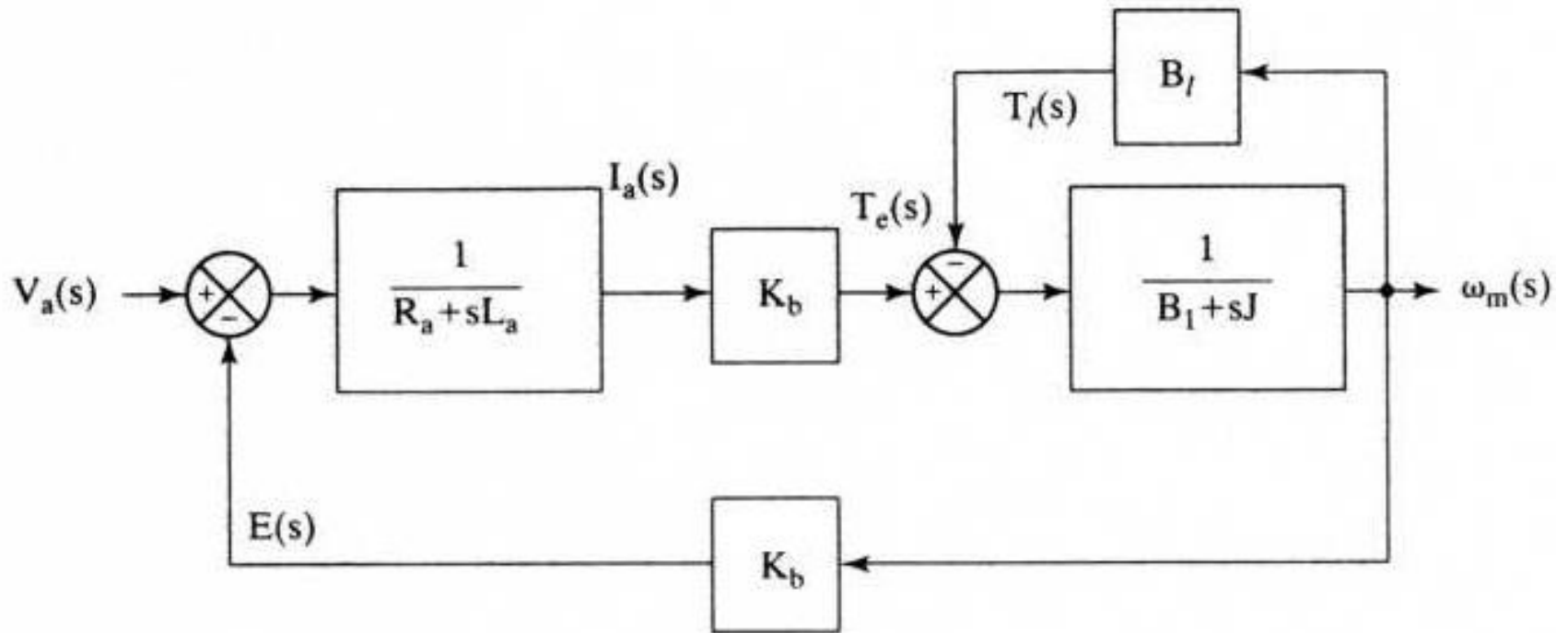


Step 1

DC Motor and load

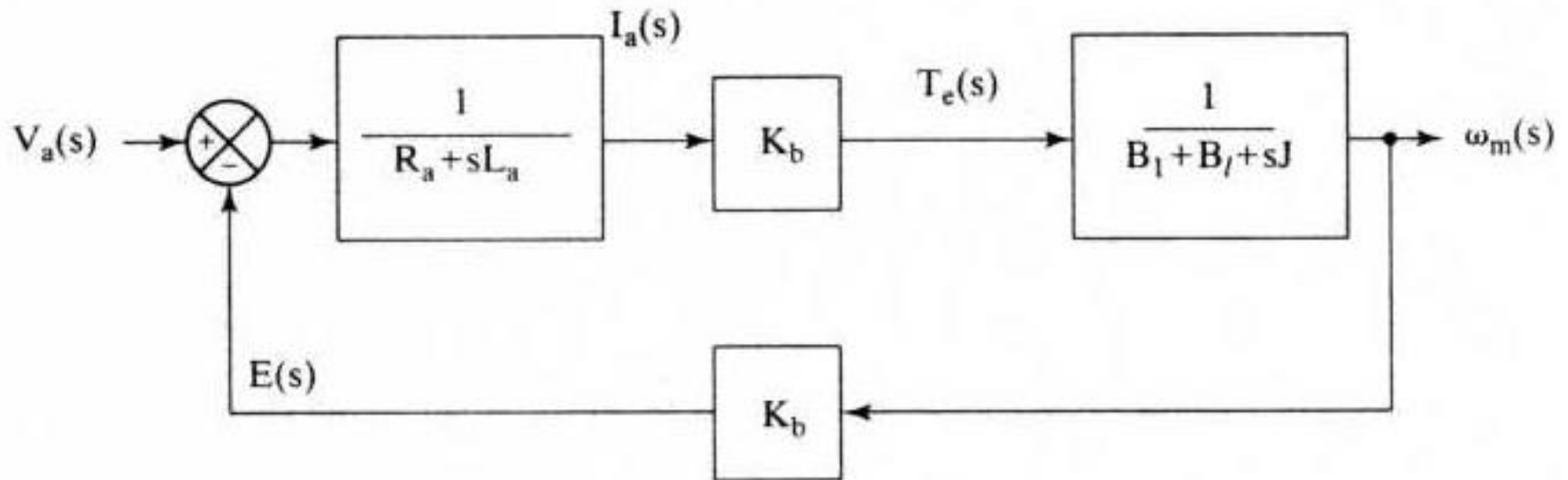


Step 2

DC Motor and load

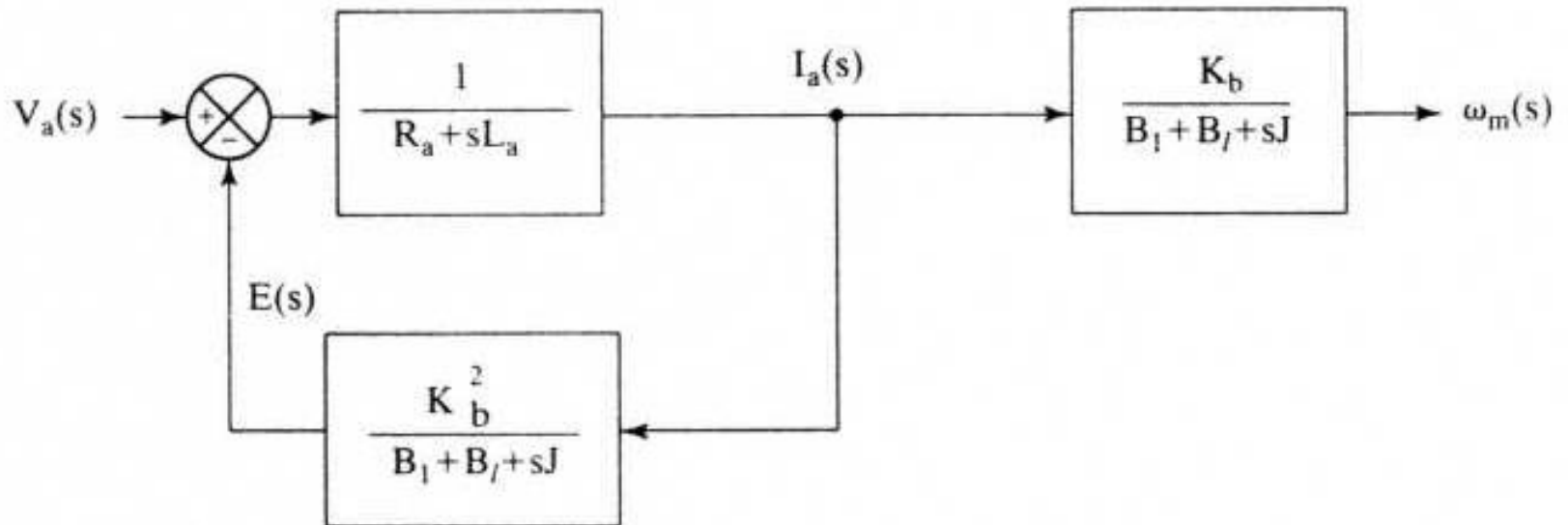

Step 3

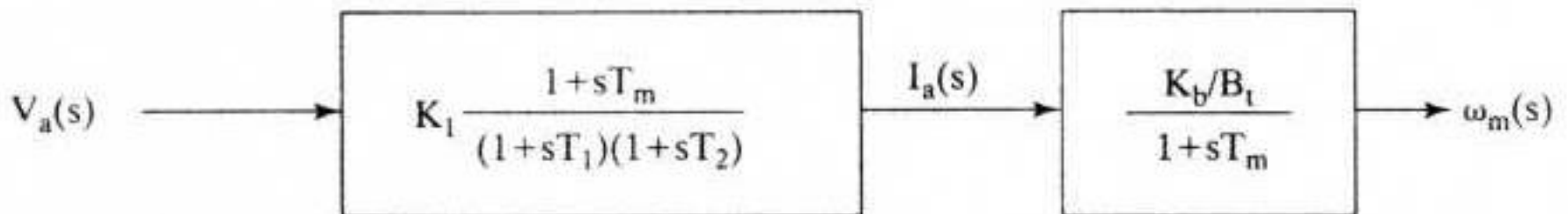

Step 4

DC Motor and load

$$-\frac{1}{T_1}, -\frac{1}{T_2} = -\frac{1}{2} \left[\frac{B_t}{J} + \frac{R_a}{L_a} \right] \pm \sqrt{\frac{1}{4} \left(\frac{B_t}{J} + \frac{R_a}{L_a} \right)^2 - \left(\frac{K_b^2 + R_a B_t}{J L_a} \right)}$$

$$K_1 = \frac{B_t}{K_b^2 + R_a B_t}$$

Converter

The converter after linearization is represented as

$$G_r(s) = \frac{V_a(s)}{v_c(s)} = \frac{K_r}{1 + sT_r}$$

The delay time T_r and gain are evaluated

Current and Speed controllers

The current and speed controllers are of proportional-integral type. They are represented as

$$G_c(s) = \frac{K_c(1 + sT_c)}{sT_c}$$

$$G_s(s) = \frac{K_s(1 + sT_s)}{sT_s}$$

where the subscripts c and s correspond to the current and speed controllers, respectively. The K and T correspond to the gain and time constants of the controllers.

Current feedback

The gain of the current feedback is H_c . No filtering is required in most cases. In the case of a filtering requirement, a low-pass filter can be included in the analysis. Even then, the time constant of the filter might not be greater than a millisecond.

Speed feedback

Most high performance systems use a dc tachogenerator, and the filter required is low-pass, with a time constant under 10 ms. The transfer function of the speed feedback filter is

$$G_w(s) = \frac{K_w}{1 + sT_w}$$

where K_w is the gain and T_w is the time constant.



The motor parameters and ratings are as follows:

220 V, 8.3 A, 1470 rpm, $R_a = 4 \Omega$, $J = 0.0607 \text{ kg} \cdot \text{m}^2$, $L_a = 0.072 \text{ H}$, $B_t = 0.0869 \text{ N} \cdot \text{m} / \text{rad/sec}$, $K_b = 1.26 \text{ V/rad/sec}$.

Obtain the motor transfer function: