

1. (a)


The output current  $I_o$  is given as,  $I_o = 10 \text{ A}$

$$I_p = \frac{I_o}{n} \quad (\because \text{ideal components})$$

$$= \frac{10}{9} = \underline{\underline{1.11 \text{ A}}}$$

And under ideal condition  $I_{c1} = \frac{I_p}{2}$ ,  $I_{c2} = -\frac{I_p}{2}$ .

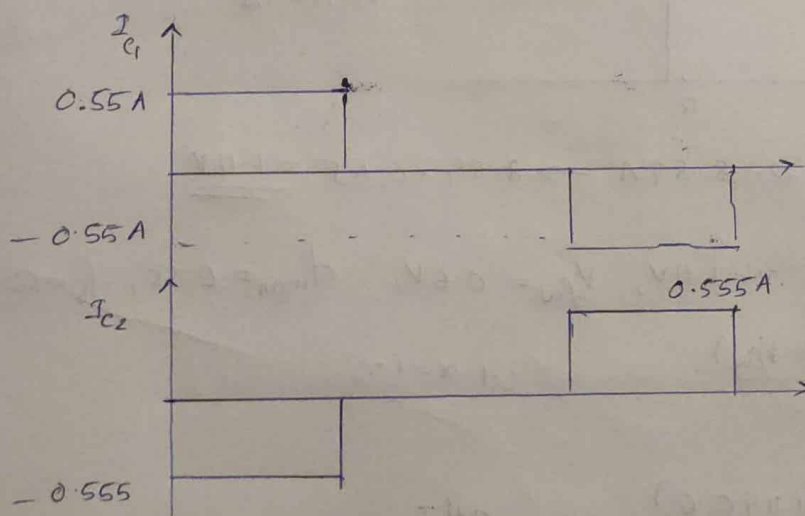If leakage,  $I_L$  ripple, and magnetizing current neglected. Then waveform of  $I_{c1}$  and  $I_{c2}$  can be given as.



(b) voltage drop due to leakage inductance  $= \frac{3}{2} \frac{1}{n^2} f_s L_k I_o$

Leakage inductance  $= 3\%$  of  $2.7 \text{ mH}$   
 $= 0.081 \text{ mH}$

$V_o = 12 \text{ V}$ ,  $I_o = 10 \text{ A}$

$$V_o = \frac{dV_{in}}{n} - \frac{3}{2} \frac{1}{n^2} f_s L_k I_o$$

$$12 = \frac{d \times 300}{9} - \frac{3}{2 \times 9^2} \times 50 \times 10^3 \times 0.081 \times 10^{-3} \times 10$$

$$d = \underline{\underline{0.3825}}$$

3.

$$\begin{aligned}
 A_p &= A_c \times A_w \\
 &= 266 \times 537 \\
 &= 142842 \text{ mm}^2
 \end{aligned}$$

$$A_p = \frac{1}{2} L J^2 \frac{2 k_i}{k_s J B_{\max}}, \quad k_i = 1 + \frac{0.2}{2} = 1.1$$

$$142842 = \frac{\frac{1}{2} \times L \times 30^2 \times 2 \times 1.1}{0.36 \times 0.2 \times 10^{-6} \times 4}$$

$$L = \frac{142842 \times 2 \times 0.36 \times 0.2 \times 4 \times 10^{-6}}{30^2 \times 2 \times 1.1}$$

$$= \underline{\underline{41.55 \mu\text{H}}}$$

$$\begin{aligned}
 N &= \frac{L k_i J}{A_c B_{\max}} = \frac{41.55 \times 10^{-6} \times 1.1 \times 30}{266 \times 0.2 \times 10^{-6}} \\
 &= 25.7 \approx \underline{\underline{26}}
 \end{aligned}$$

And  $L = \frac{\mu_0 N^2 A_c}{l_e + 2g \mu_r}$ ,  $g$  will get from this formula

$$41.55 \times 10^{-6} = \frac{4\pi \times 10^{-7} \times 2200 \times 26^2 \times 266 \times 10^{-6}}{(146.3 \times 10^{-3}) + 2g \times 2200}$$

$$\Rightarrow \underline{\underline{g = 2.685 \text{ mm}}}$$

which is the airgap we require.

9.

$$I_0 = 1A \text{ to } 4A$$


$V_i$  varies from  $10.8V$  to  $13.6V$ , and  $V_0 = 24V$

$$\therefore d_{\text{max}} = 1 - \frac{10.8}{24} = 0.55$$

$$d_{\text{min}} = 1 - \frac{13.6}{24} = 0.433$$

$$I_{0\text{max}} = 4A \quad \therefore \text{Maximum current that to measure} \\ = \frac{4}{1 - 0.55} = \underline{\underline{8.89A}}$$

And the s/w current waveform looks like,

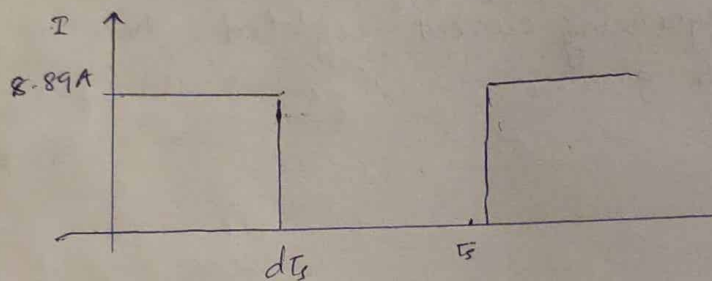

$\therefore$  et design for unidirectional switched currents

$$1A \rightarrow 0.125V, \quad \Rightarrow 8.89A \rightarrow 8.89 \times 0.125 = \underline{\underline{1.11V}}$$

$$\text{Let } V_{\text{fwd}}, I = 8.89A, V = 1.11V, V_{\text{fw}} = 0.6V, d_{\text{max}} = 0.55, f_s = 50\text{kHz}$$

$$nL_m \geq \frac{100 d_{\text{max}} (V + V_{\text{fw}})}{\pi f_s I}, \quad \text{let } \alpha = 1\%$$

$$= \frac{100 \times 0.55 \times (1.11 + 0.6)}{1 \times 50 \times 10^3 \times 8.89} = 211.58 \mu\text{H Turns}$$

	$n$	$(I_s)_{\text{rms}}$	$B_{\text{max}} (\text{wb/m}^2)$
$T_0$	276	0.023	0.011
$T_{12}$	179	0.036	0.0087
$T_{16}$	142	0.046	0.0066
$T_{20}$	187	0.035	0.00457
$T_{27}$	114	0.057	
$T_{32}$	87	0.075	
$T_{45}$	89	0.074	

$$B_m = \frac{0.55 (1.1 \times 40.6)}{50 \times 10^3 \times n A_c}$$

$$= \frac{1.881 \times 10^5}{n A_c}$$

Let  $J = 2.5 \text{ A/mm}^2$ ,  $A = \frac{0.074}{2.5} = 0.03 \text{ mm}^2$

so we choose T45/89T/SWG182

$$V_i = \frac{d_{\max}}{1 - d_{\max}} (V + V_{FW}) - V_{FW} = 1.5 \text{ V.}$$

$$\text{Power rating of zener} = \frac{L_m I_m^2 f_s}{2} = \frac{2.37 \times 10^{-6} \times 50 \times 10^3}{2}$$

$$= \underline{\underline{468.2 \mu\text{W}}}$$

$$R_s = \frac{nV}{I} = \frac{8.89 \times 1.1}{8.89} = 11.2$$

rms current through  $R_s = \frac{1.1}{11} \sqrt{0.55}$

$$= 74 \text{ mA}$$

Power in  $R_s = 0.074^2 \times 11$

$$= \underline{\underline{0.06 \text{ W}}}$$

$\therefore 11.2 / \underline{\underline{\frac{1}{4} \text{ W resistance}}}$

10

$$I = 1.1 \text{ A}, V = 0.139 \text{ V}$$

$$0.425 \text{ V} \rightarrow 0.125 \text{ V}$$

$$1.1 \text{ A} \rightarrow 1.1 \times 0.125$$

$$= 0.139 \text{ V.}$$

$$n L_m \geq \frac{3.2 V}{f_s I}$$

$$1\% \text{ of } 1.1 = 0.011 \text{ A}$$

$$= \frac{3.2 \times 0.139}{50 \times 10^3 \times 1.1} = 8.01 \mu\text{H}$$

$$I_m = \frac{\alpha V}{2 n L_m f_s} = \frac{0.36 \times 0.139}{2 \times 8.01 \times 10^{-6} \times 50 \times 10^3} = 0.0624$$

which is greater than  $1\% \text{ } I = 0.011$



$$\text{So } 0.011 = \frac{0.36 \times 1}{2 \times 50 \times 10^3 \times n \times L_m}$$

$$n L_m = \frac{0.36 \times 1}{0.011 \times 2 \times 50 \times 10^3} = \underline{\underline{327.27 \mu H}}$$

	n	$I_s$	Bm
T10	427	1.56	$1.89 \times 10^{-4}$
T12	217	2.4	$1.5 \times 10^{-4}$
T16	220	3.027	
T20	209	2.8	
T27	176	3.78	
T32	134	4.97	
T45	138	4.82	


$$J = 25 \text{ A/mm}^2$$

$$A = \frac{I}{J} = \frac{4.82}{25} \approx 2 \text{ mm}^2$$

So chose T45 toroid core SWG 15

138 turns of SWG 15 ( $2.627 \text{ mm}^2$ ,  $1.92 \text{ mm}$  dia)
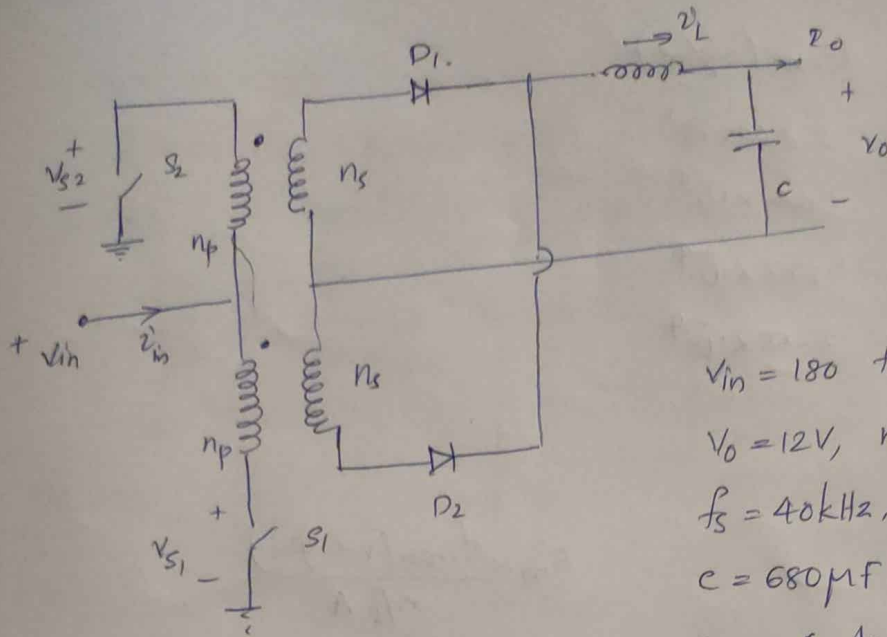
$$R_s = \frac{0.137}{1.1 \times 138} = \underline{\underline{17.2 \Omega / W}}$$



$$V_{in} = 180 \text{ to } 240 \text{ V}$$

$$V_o = 12 \text{ V}, n = 6, l_m = 0.5 \text{ mH},$$

$$f_s = 40 \text{ kHz}, L = 40 \mu\text{H}$$


$$C = 680 \mu\text{F} - 40 \mu\text{s family.}$$

$$I_o = 4 \text{ to } 10 \text{ A}$$

$$V_o = \frac{2 d V_{in}}{n}, \quad d = \frac{n V_o}{2 V_{in}} = \frac{6 \times 12}{2 \times 180} \text{ to } \frac{6 \times 12}{2 \times 240}$$

$$= 0.15 \text{ to } 0.2$$

$$\therefore d_{max} = 0.2$$

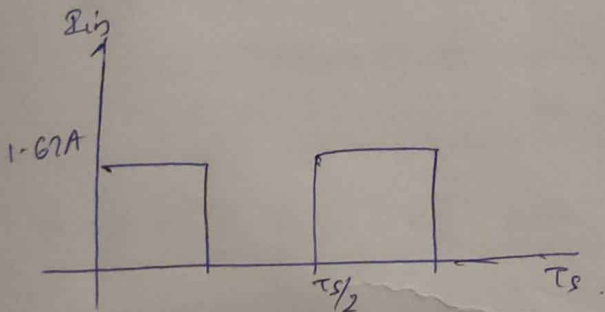

$$I = 1.67 \text{ A}, \quad V = 0.5 \times 1.67 \rightarrow \underline{0.835 \text{ V}} \quad V_{fw} = 0.6$$

$$d_{max} = 0.2, \quad f_s = 80 \text{ kHz}, \quad I_m < 1\% \text{ of } 1.67 \text{ A}$$

$$n L_m \geq \frac{100 d_{max} (V + V_{fw})}{n f_s I}$$

$$= \frac{100 \times 0.2 \times (0.835 + 0.6)}{1 \times 80 \times 10^3 \times 1.67}$$

$$= \underline{\underline{214.8 \mu\text{H}}}$$

	$n$	$(I_s)_{ms}$	$B_{min} (wb/m^2)$
T10	280	$2.66 \times 10^{-3}$	$2.866 \times 10^3$
T12	152	$4.1 \times 10^{-3}$	$1.64 \times 10^3$
T16	145	$5.15 \times 10^{-3}$	$1.237 \times 10^4$
T20	180	$3.93 \times 10^{-3}$	$3.58 \times 10^4$
T30	116	$6.48 \times 10^{-3}$	
T32	88	$8.48 \times 10^{-3}$	
T45	90	$8.24 \times 10^{-3}$	

$$B_m = \frac{d_{man}(v + v_{fw})}{n f_s A}$$

$$= \frac{0.2(0.835 + 0.6)}{86 \times 10^3 \times n A_c \times 10^{-9}}$$

$$= \frac{3.5875}{n A_c}$$

$$J = 2.5 A/mm^2$$

$$T32, n=88, I_s = 8.48 \times 10^{-3}$$

$$J_n = A = \frac{I}{J} = 0.003 mm^2$$

SWG 45 T32/88T / SWG 45

$$V_z = \frac{d_{man}}{1 - d_{man}} (v + v_{fw}) = 2.4588$$

$$\text{Power rating of zener} = \frac{L_m I_m^2 f_s}{2}$$

$$= \frac{2.44 \times 10^{-6} \times (0.01 \times 1.67)^2 \times 80 \times 10^3}{2}$$

$$= 27.2 \mu W$$

$$R_s = \frac{v}{I} = \frac{8 \times 0.835}{1.07} = 44 \Omega$$

$$\text{rms of current through } R_s = 8.45 \times 10^{-3}$$

$$\text{Power of } R_s = (8.45 \times 10^{-3})^2 \times 44$$

$$= 3.14 mW$$


$$\text{SW } R = 47.2 \Omega / 1/4 W$$

5.

$$V_s = 200 - 280V, V_o = 24V, I_o = 2A \text{ to } 5A$$

$$f_s = 75 \text{ kHz}, B_m = 0.2 \text{ Wb/m}^2, J = 2 \text{ A/mm}^2$$
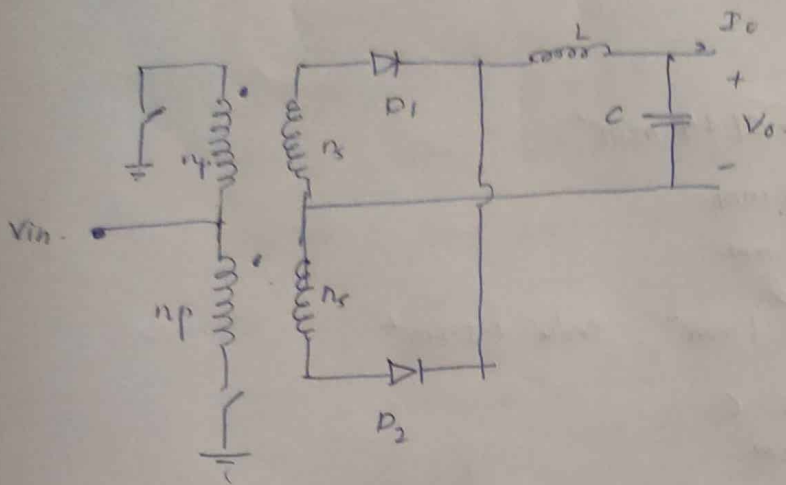
$$k_s = 0.35 \text{ (transform)}, k_f = 0.4 \text{ (inductor)}$$



$$P_o = 24 \times 5 = 120 \text{ W}$$

$$\eta = 0.7$$

$$A_{Aw} = \frac{P_o}{1.47 \eta B_{max} J \frac{k_s}{f_s}} = \frac{120}{1.47 \times 0.7 \times 3 \times 2 \times 10^7 \times 75 \times 10^3 \times 0.45}$$


$$= 7464.32 \text{ mm}^2$$

So we select EE 32/16/11 with  $A_p = 14340.48 \text{ mm}^4$

$$I_o = 5A, d = 0.48$$

$$V_o = \frac{2dV_{in}}{n} \Rightarrow n = \frac{2dV_{in}}{V_o}, \Rightarrow n = 8$$

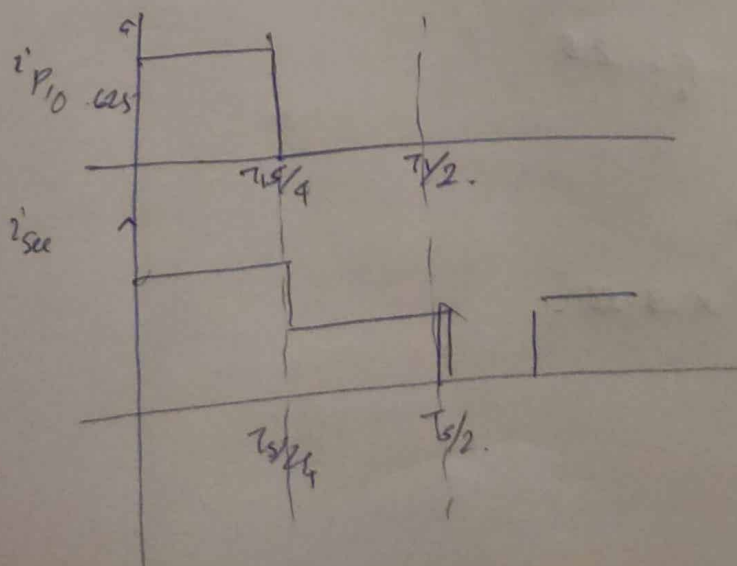primary wire will conduct maximum rms when  $V_p$  is 280V



Primary rms current

$$= 0.625 \sqrt{0.48}$$

$$= 0.433A$$



secondary rms current = 3A

$$2n_p \frac{0.433}{3} + 2n_s \frac{B}{J} = 0.35 \times 147.84$$

$$\Rightarrow n_s = 12$$

$$n_p = 96$$

$$\text{Primary wire area} = \frac{0.433}{3} = 0.144 \text{ mm}^2$$

$$\text{so swg 26, } d_{\text{pr}} = 0.405 \text{ mm.}$$

$$\text{Cu dia} = 0.457 \text{ mm.}$$

$$\text{Secondary wire area} = \frac{3}{3} = 1 \text{ mm}^2, \text{ take } 1.5 \text{ mm}^2$$

$$\text{usable winding height} = 11.2 \times 2 - 6$$
$$= 16.4 \text{ mm}$$

$$\text{Pail thickness} = \frac{1.5}{16.4} = 0.1 \text{ mm.}$$

$$\text{no. of turns Cu layer} = \frac{16.4}{0.505} = 32.$$

so 3 layers with 32 turns.

$$\text{Total wire length} = 47.06 \times 96 \times 2$$
$$= 9.03 \text{ m}$$

$$h = 0.866d = 0.866 \times 0.457 = 0.395$$

$$A = 0.12 \text{ mm.}$$

$$R_{dc} = 0.165 \times 1.2 \times 9.05$$
$$= 1.13 \Omega$$

$$\frac{N_s d}{\omega} = 0.891 = F_2, \sqrt{F_2} = 0.94.$$

$$\frac{h \sqrt{F_2}}{A} = 31, p=3, F_1 = 28$$

$$R_{ac} = 28 \times 1.13 = 31.86 \Omega$$

$$\text{Primary Cu loss} = 0.433^2 \times 9.81$$
$$= 5.96 \text{ W}$$

$$V_i = 250 \text{ to } 400 \text{ V}, V_o = 12 \text{ V}.$$

$$f_s = 100 \text{ kHz}, B_m = 0.25 \text{ Wb/m}^2, J = 3 \text{ A/mm}^2$$

$$K_r = 0.35$$

$$1.3 (V_{in_{max}} + n(V_o + V_r)) \leq 0.8 V_k$$


$$1.3 (250 + n(12 + 1)) \leq 0.8 \times 900$$

$$13n \leq 303.84$$

$$\text{so } n = 23$$

$$d_{max} = \frac{0.8}{1 + \frac{V_{max}}{n(V_o + V_r)}} = \frac{0.8}{1 + \frac{250}{24(12+1)}} = \underline{\underline{0.435}}$$
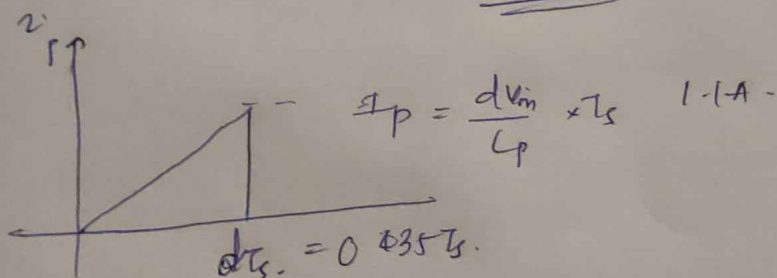
$$L_p = \frac{d_{max}^2 V_{in_{max}}^2}{2 P_{in} f_s} = \frac{0.435^2 \times 250^2}{2 \times 12 \times 5 \times 100 \times 10^3} = \underline{\underline{7.85 \mu\text{H}}}$$



$$I_{p_{rms}} = 0.418 \text{ A}$$

$$L_p I_p = A_s n_p B_m$$

$$A_c = \frac{L_p I_p}{B_m n_p} = \frac{1.1 \times 7.85 \times 10^{-6}}{0.25 \times n_p}$$

$$K_s A_w = 0.165 n_p + n_p \times \frac{2.64}{23}$$

$$A_w = 0.808 n_p$$

$$A_c A_w = \underline{\underline{3501.87 \text{ mm}^2}}$$