

(Note- Use MATLAB to obtain time-domain response plots and Bode plots)

### I Buck Converter Data

110V input, 48V, 4.8A Output

$f_s = 50\text{ kHz}$ ,  $L = 540\mu\text{H}$ ,  $C = 100\mu\text{F}$

Load - Resistive,  $10\Omega$

$\eta_L = 0.3\Omega$ ,  $\eta_S = 0.2\Omega$ ,  $\eta_D = 0.2\Omega$ ,  $\eta_C = 0.5\Omega$

$V_T = 0.5\text{V}$

1(a) Set up the State Space Averaged(SSA) model and evaluate the steady-state duty ratio  $d_0$  when  $V_{in} = 110\text{VDC}$ ,  $V_o = 48\text{V}$  and  $R_L = 10\Omega$ .

(b) Form the LTI Small Signal State Space Model around this operating point and evaluate

$$\frac{\Delta \bar{V}_o(s)}{\Delta d(s)}, \frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{in}(s)}, \frac{\Delta \bar{I}_L(s)}{\Delta d(s)} \text{ and } \frac{\Delta \bar{I}_L(s)}{\Delta \bar{V}_{in}(s)}$$



(c) Use MATLAB and obtain the time-domain response plots for  $\bar{I}_L(t)$  and  $\bar{V}_o(t)$  when duty ratio is suddenly increased by 5% of  $d_0$ .

d) Obtain the time domain response plots for  $\bar{I}_L(t)$  and  $\bar{V}_o(t)$  when input is suddenly changed from 110V to 100V.

e) If  $V_{in}$  contains a  $100\text{Hz}$  ripple of amplitude 5V, find the  $100\text{Hz}$  component amplitude in  $\bar{I}_L$  and  $\bar{V}_o$  under steady state by using frequency response plots of corresponding transfer functions evaluated with the help of MATLAB.

2(a) Obtain the Bode plot of  $\frac{\Delta \bar{V}_o(s)}{\Delta d(s)}$  and predict whether a Type I compensator can be designed with  $f_{C_0} = 5\text{kHz}$  & PM = 45°.

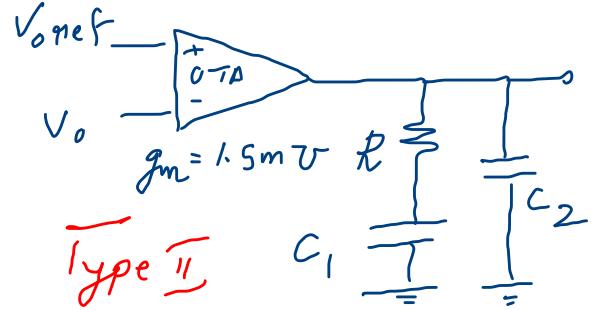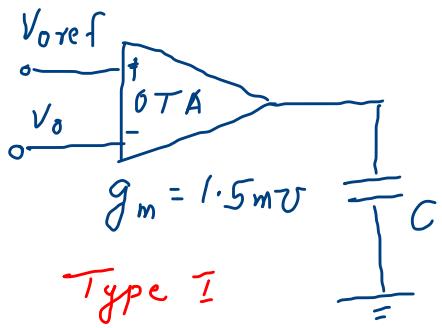- (b) Find  $f_{co}$  to be used if PM obtained by using a Type I Compensator is to be  $60^\circ$ .
- (c) Find  $f_{co}$  to be used if PM obtained by using a Type II Compensator is to be  $60^\circ$ .
- (d) Find  $f_{co}$  to be used if PM obtained by using a Type III Compensator is to be  $60^\circ$ .
- (e) Design the compensator transfer functions in (b), (c) and (d)
- (f) Design circuits to obtain the Type I and Type II compensators using Transconductance amplifiers as below.




- (g) Design a Opamp Circuit to get the Type III compensator arrived at in Part(e).
3. (a) A Type I Compensator with  $60^\circ$  PM, designed under 2(e) is used in the converter. Obtain  $\frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{in}(s)}$ ,  $\frac{\Delta \bar{V}_o(s)}{\Delta V_{oref}}$ ,  $\frac{\Delta \bar{I}_L(s)}{\Delta \bar{V}_{in}(s)}$  and  $\frac{\Delta \bar{I}_L(s)}{\Delta V_{oref}}$  for the closed loop Buck Converter.
- (b) Obtain time-domain response plots using MATLAB for  $\bar{V}_o(t)$  and  $\bar{I}_L(t)$  when  $V_{oref}$  is suddenly changed from 48V to 40V.
- (c) Obtain time-domain response plots for  $\bar{V}_o(t)$  and  $\bar{I}_L(t)$  when  $V_{in}$  is suddenly changed from 110V to 100V and compare with plots in 1(d). Comment on the result.

(a) Find the  $100 \text{ Hz}$  ripple amplitude in  $\bar{I}_L$  and  $\bar{V}_o$  if there is a  $5\text{V}$  amplitude  $100 \text{ Hz}$  component in  $V_{in}$ . Compare the result with the values found under 1(e) and comment.


4(a) This Buck Converter is controlled using Current Mode Control. The peak of  $\bar{I}_L$  will be limited to  $6\text{A}$  under all conditions. The current sensor used to sense  $\bar{I}_L$  has a gain of  $0.5 \text{ V/A}$ . Design a PI Controller for outer voltage control loop if the closed loop system is expected to have a rise time of  $1 \text{ ms}$ .

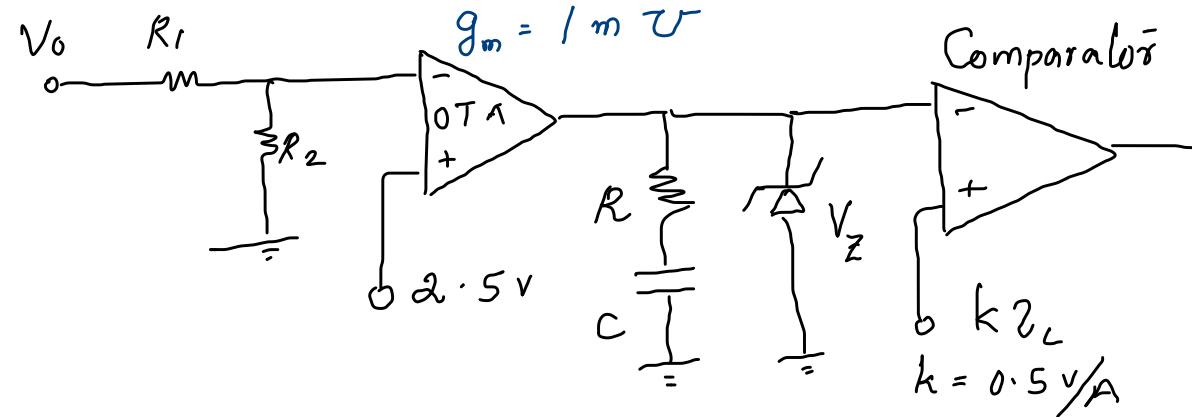(b) Find the Component values in the following implementation of PI Controller



Resistors should be in  $1\text{k}\Omega - 100\text{k}\Omega$  range.

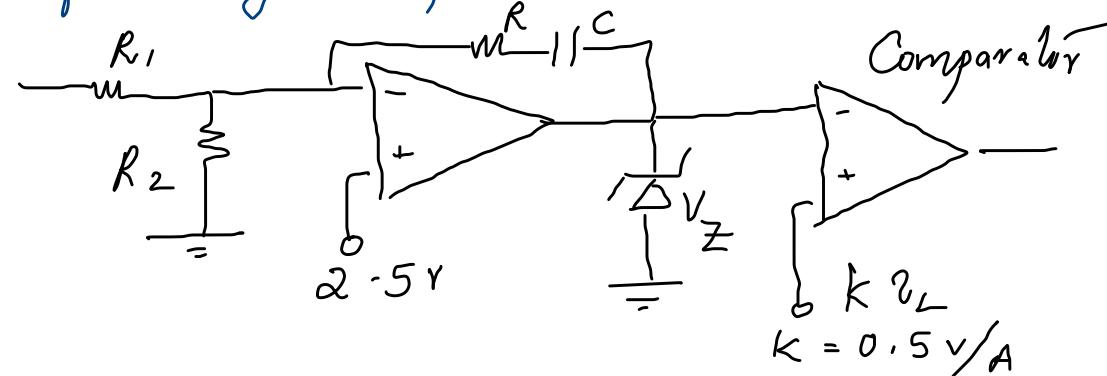c) Find the component values if the following implementation is used.



## II Boost Converter Data

48V input, 110V, 4A Output

$f_s = 50\text{ kHz}$ ,  $L = 270\text{ }\mu\text{H}$ ,  $C = 330\text{ }\mu\text{F}$

$$\eta_L = 0.3\text{ } \eta_S = 0.12 \quad \eta_D = 0.12$$

$$\eta_C = 0.12 \quad \text{Load is resistive} = 27.5\text{ }\Omega$$

$$V_r = 0.5\text{ V}$$

1(a) Set up the State Space Averaged(SSA) model and evaluate the steady-state duty ratio  $d_0$  when  $V_{in} = 110\text{ V}_{DC}$ ,  $V_o = 48\text{ V}$  and  $R_L = 27.5\text{ }\Omega$ . (You may have to iterate)

(b) Form the LTI Small Signal State Space Model around this operating point and evaluate

$$\frac{\Delta \bar{V}_o(s)}{\Delta d(s)}, \frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{in}(s)}, \frac{\Delta \bar{I}_L(s)}{\Delta d(s)} \text{ and } \frac{\Delta \bar{I}_L(s)}{\Delta \bar{V}_{in}(s)}$$



(c) Use MATLAB and obtain the time-domain response plots for  $\bar{I}_L(t)$  and  $\bar{V}_o(t)$  when duty ratio is suddenly increased by 5% of  $d_0$ .

(d) Obtain the time domain response plots for  $\bar{I}_L(t)$  and  $\bar{V}_o(t)$  when input is suddenly changed from 48 V to 44 V.

(e) If  $V_{in}$  contains a  $100\text{ Hz}$  ripple of amplitude 10 V, find the  $100\text{ Hz}$  component amplitude in  $\bar{I}_L$  and  $\bar{V}_o$  under steady state by using frequency response plots of corresponding transfer fns evaluated with the help of MATLAB.

2(a) Obtain the Bode plot of  $\frac{\Delta \bar{V}_o(s)}{\Delta d(s)}$  and predict whether a Type I compensator can be designed with  $f_{co} = 5\text{ kHz}$  & PM = 45°.

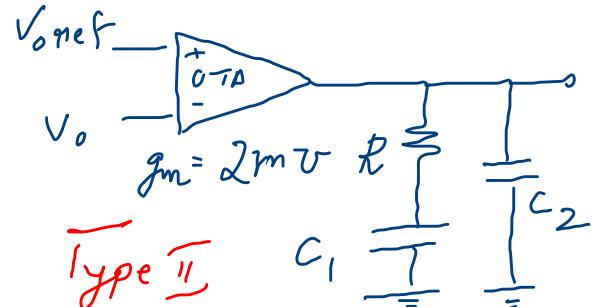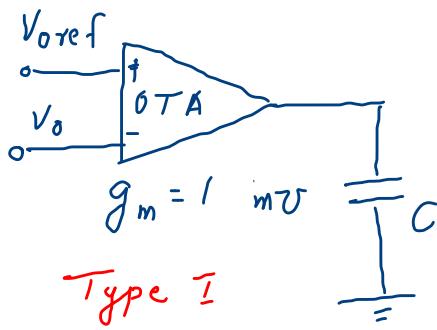- (b) find  $f_{co}$  to be used if PM obtained by using a Type I Compensator is to be  $60^\circ$
- (c) find  $f_{co}$  to be used if PM obtained by using a Type II Compensator is to be  $60^\circ$ .
- (d) find  $f_{co}$  to be used if PM obtained by using a Type III Compensator is to be  $60^\circ$
- (e) Design the compensator transfer functions in (b), (c) and (d)
- (f) Design circuits to obtain the Type I and Type II compensators using Transconductance amplifiers as below.



3. (a) A Type III Compensation with  $60^\circ$  PM, designed under 2(e) is used in the converter. Set up the closed loop control block diagram in MATLAB/Simulink.
- (b) Obtain time-domain response plots using MATLAB for  $\bar{V}_o(t)$  and  $\bar{I}_L(t)$  when  $V_{oref}$  is suddenly changed from 110 V to 120 V.
- (c) Obtain time-domain response plots for  $\bar{V}_o(t)$  and  $\bar{I}_L(t)$  when  $V_{in}$  is suddenly changed from 48 V to 40 V and compare with plots in 1(d). Comment on the result.
- (d) find the 100 Hz ripple amplitude in  $\bar{I}_L$  and  $\bar{V}_o$  if there is a 10 V amplitude 100 Hz component in  $V_{in}$ . Compare the result with the values found under 1(e) and comment.