

\* Char. of ideal switching device:-

1.) ON state

→ it must have ability to carry high forward current.

$$I_f \rightarrow \infty$$

→

$$V_f \rightarrow 0$$

→

$$R_f \rightarrow 0$$

→

$$P_{ON} \rightarrow 0$$

2.) Off state

•  $V_{BR} \rightarrow \infty$  (it must withstand high forward and Reverse voltages.)

$$I_{off} \rightarrow 0$$

$$R_{off} \rightarrow \infty$$

$$P_{off} \rightarrow 0$$

3.)

$$t_{on} \rightarrow 0$$

$$t_{off} \rightarrow 0$$

turn on and turn off process must occur instantaneously so that it can be used for high freq<sup>n</sup> applications.

4.) for turn on and turn off process,

$$P_G \rightarrow 0 \text{ (low gate drive power)}$$

$$V_G \rightarrow 0 \text{ (low gate drive voltage)}$$

$$I_G \rightarrow 0 \text{ (low gate drive current.)}$$

5.) Both turn on and turn off must be Controllable.

it must turn on with a +ve gate signal

must be turned off with -ve (or) zero gate signal.

6.) For turning on and off, it should require a pulse signal only.

A small current digital goes at off time and the turn on time

7.)

8.) Must have a high  $\frac{dv}{dt} \rightarrow \infty$

9.) Must have high  $\frac{di}{dt} \rightarrow \infty$

it must be capable of having

10.) It must have the ability to sustain any fault current for a long time period

$$\hookrightarrow i^2 t \rightarrow 0$$

11.) Low price.

# Classification of power electronics converter.

On the basis of I/P & O/P side power condition

1.) ac - dc (converters) (Rectifiers)

a.) Uncontrolled

(from fixed voltage ac  $\rightarrow$  a fixed voltage dc)

b.) Controlled

large step up & down no need to turn on

2.) ac - ac converter (ac choppers)

### 3.) dc - dc converters (choppers)

Fixed dc voltage to controlled dc voltage

### 4.) dc - ac converters (inverters)

Uncontrolled dc voltage to controlled ac voltage & frequency.

### 5.) Static switches (contactors)

## # Classification (on the basis of switching of devices)

1.) Line commutated (naturally commutated) converters

2.) switching (forced commutated) converters

3.) resonant converters (zero voltage / zero current switching)

## \* outline of the course

### 1.) Converter Circuits




ac - dc converters

dc - ac converters





→ : shib . w7 atm . BH-1
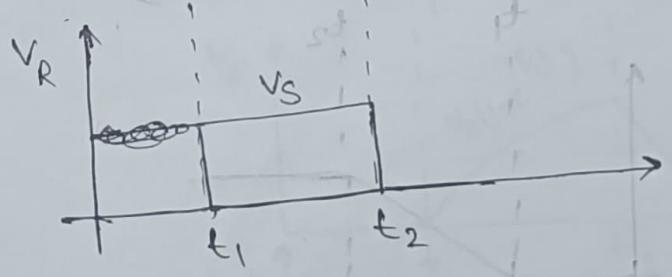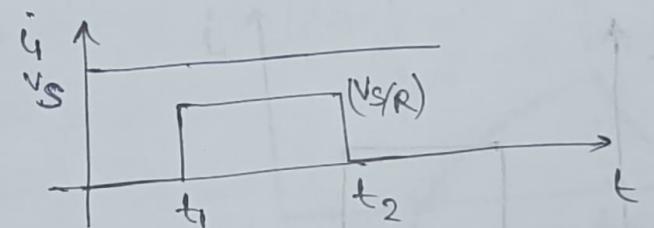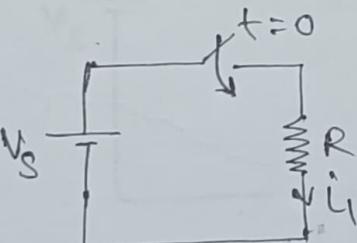
## \* R-CKT:

switch is closed at  $t=t_1$ , and opened at  $t=t_2$





L-Ckt.

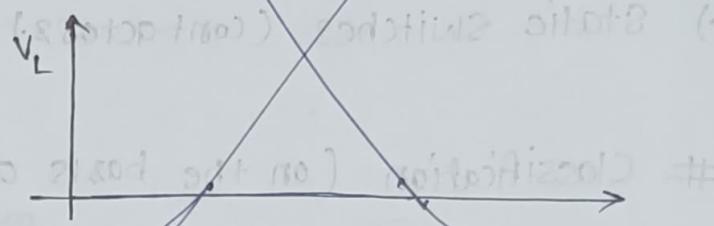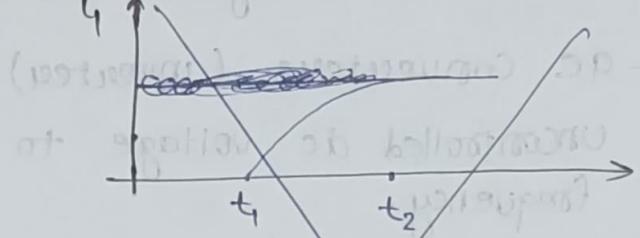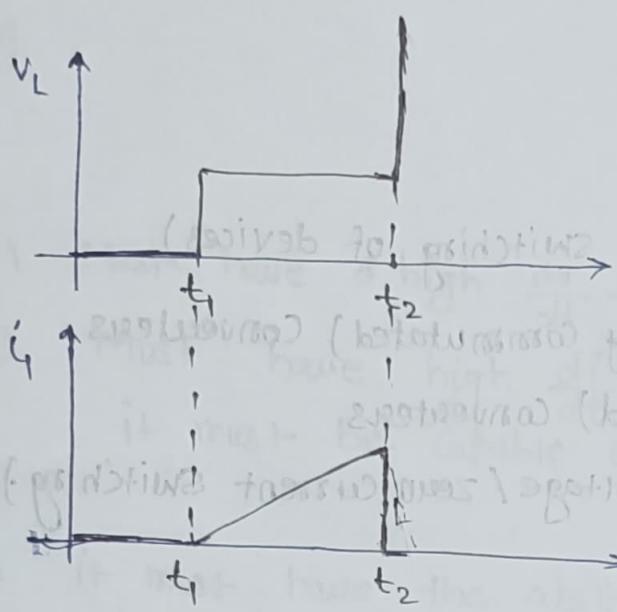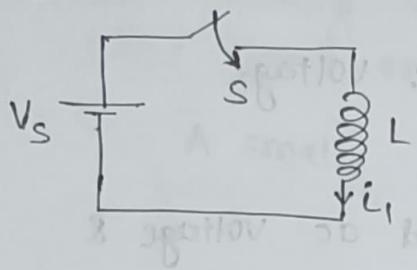

\*at  $t = t_2$  Current becomes instantly zero,

so,  $\frac{di}{dt} \rightarrow 0^-$  and very large.  
 $V_L \rightarrow \infty$


L-Ckt. With F.W. diode : -

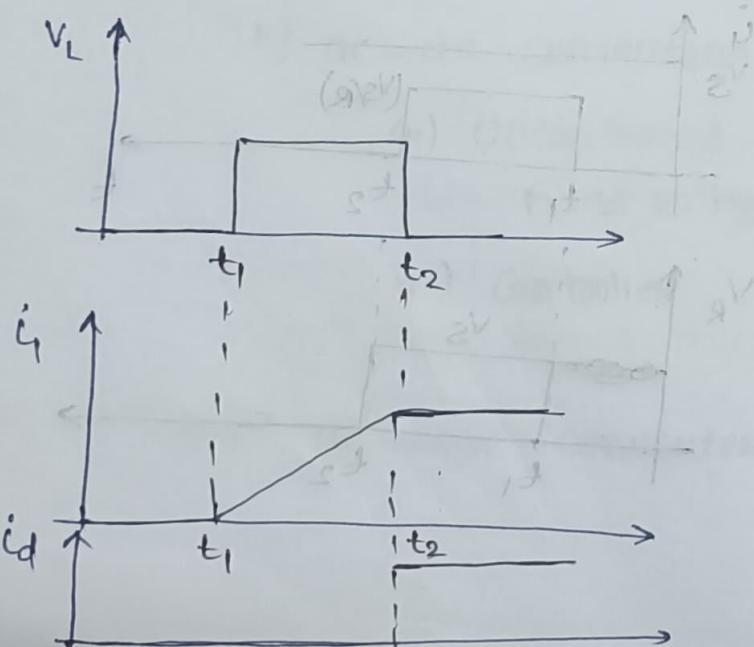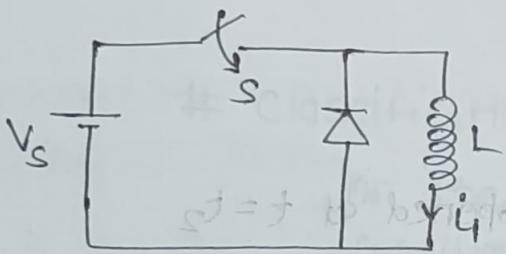

$$\frac{di}{dt} = \frac{I}{L}$$



## R-L CKT.

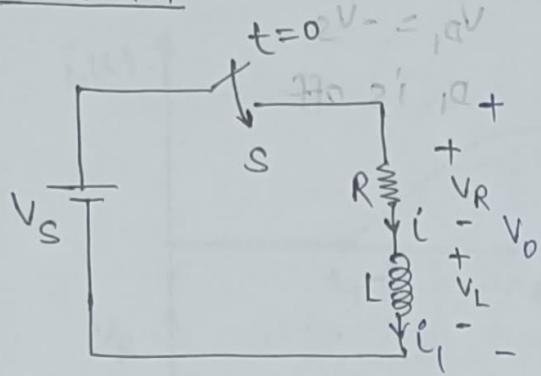

at  $t=t_1$


$$V_s = V_R + V_L = V_o$$

~~(Given  $V_s$ )~~  ~~$R = \frac{V_s}{I}$~~

$$V_o = V_s = R i(t) + L \frac{di(t)}{dt}$$

$$\begin{aligned} i(t) &= i(\infty) + (i(0) - i(\infty)) e^{-\frac{Rt}{L}} \\ &= i(\infty) + (i(0) - i(\infty)) e^{-\frac{Rt}{L}} \end{aligned}$$
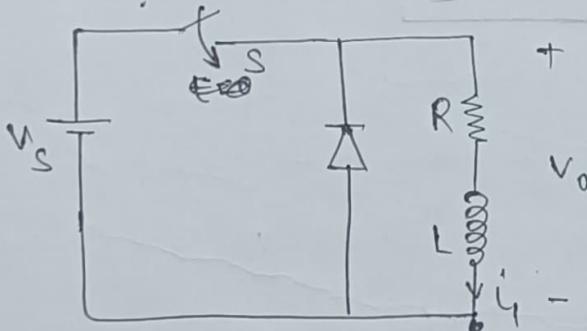
$$\Rightarrow i(t) = \frac{V_s}{R} \left( 1 - e^{-\frac{Rt}{L}} \right)$$




for  $t > t_2$

Diode is conducting —



$$V_o = 0$$

$$R i'(t) + L \frac{di(t)}{dt} = 0$$
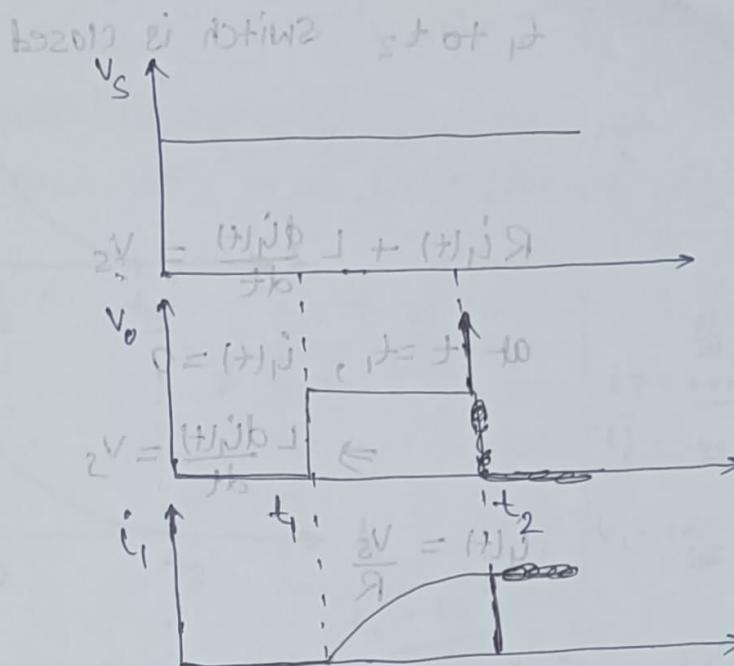
$$\Rightarrow i''(t) = \frac{V_s}{R} e^{\frac{Rt}{L}}$$


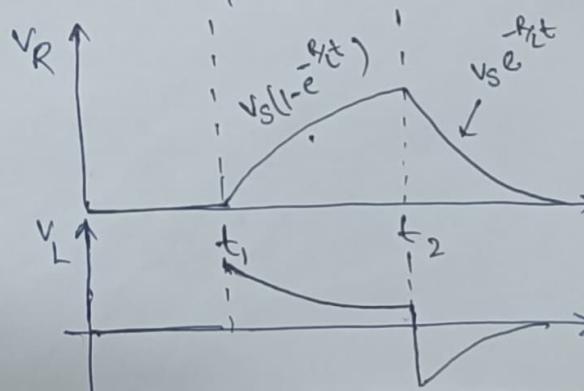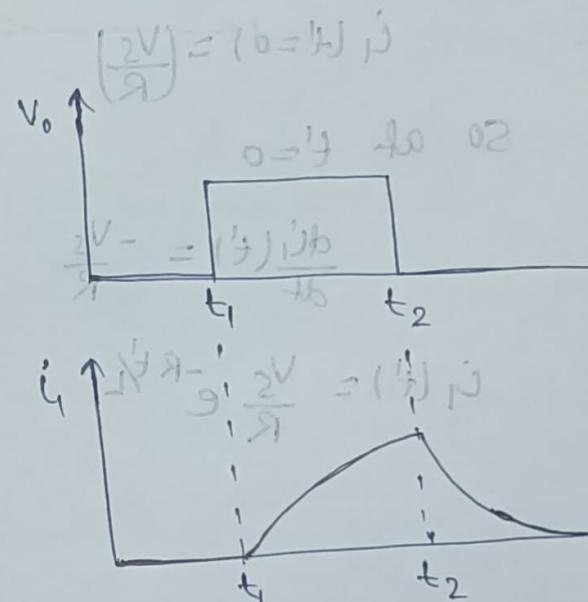
$$\begin{aligned} V_s &= R I(s) + L(s) I(s) - I(0) \\ I(s) [R + Ls] &= V_s \\ I(s) &= \frac{V_s}{R + Ls} \end{aligned}$$



$t_1$  to  $t_2$  switch is closed

$$V_{D_1} = -V_S$$

$D_1$  is off

$$Ri_L(t) + L \frac{di_L(t)}{dt} = V_S$$

at  $t = t_1$ ,  $i_L(t) = 0$

$$\Rightarrow L \frac{di_L(t)}{dt} = V_S$$

$$i_L(t) = \frac{V_S}{R}$$

$i_L(t) = \frac{V_S}{R}$

For  $t > t_2$  switch is open

$$Ri_L(t') + L \frac{di_L(t')}{dt} = 0$$

$$i_L(t'=0) = \left( \frac{V_S}{R} \right)$$

so at  $t'=0$

$$\frac{di_L(t')}{dt} = -\frac{V_S}{R}$$

$$i_L(t') = \frac{V_S}{R} e^{-Rt'/L}$$


$$t' = \frac{t - t_2}{L}$$

$t - t_2$   $t - t_2$

— voltage across diode


$$0 = \frac{W_{ib}}{t_2} t + W_{id}$$

$$0 = \frac{W_{ib}}{t_2} t + W_{id}$$

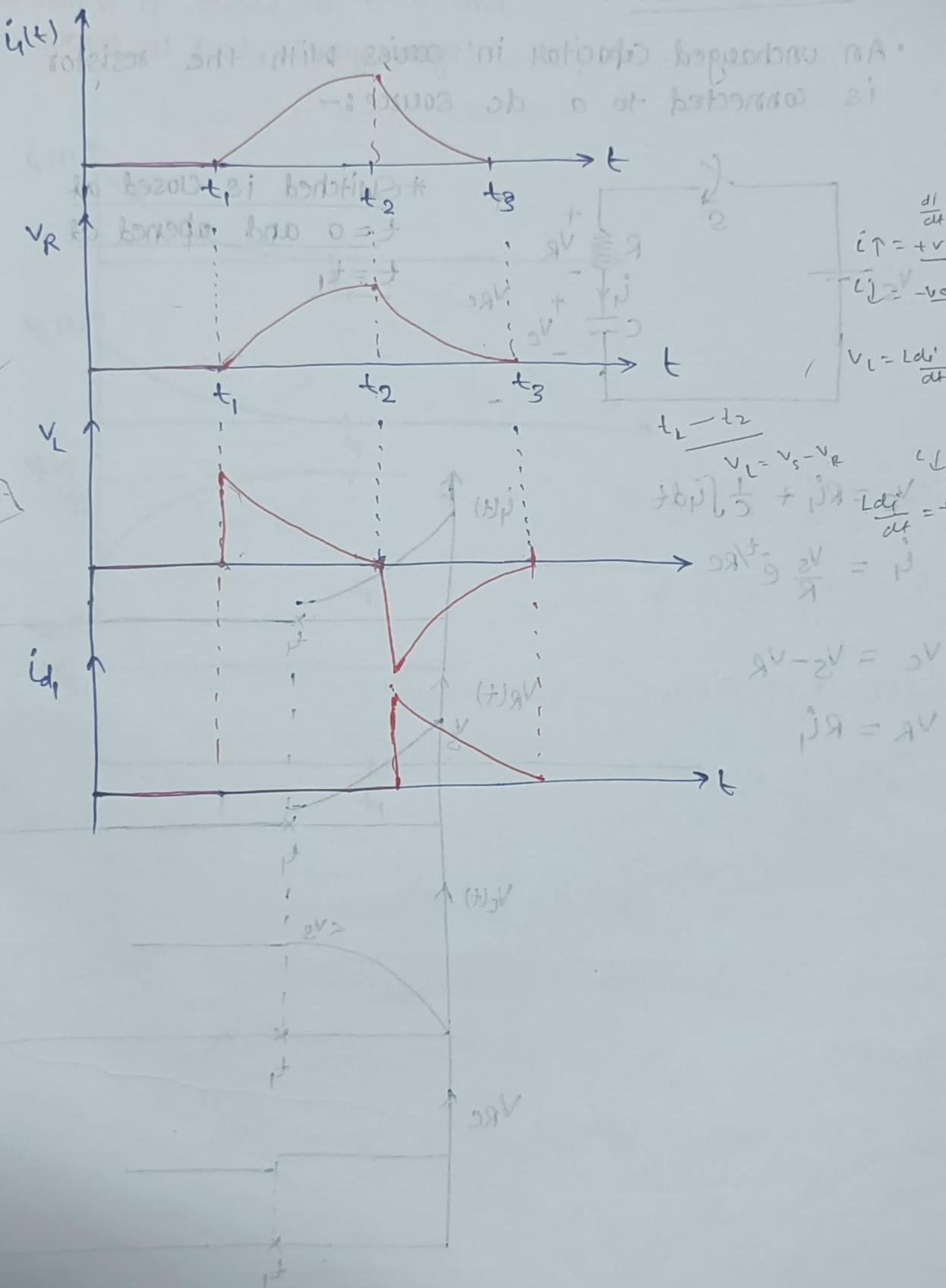
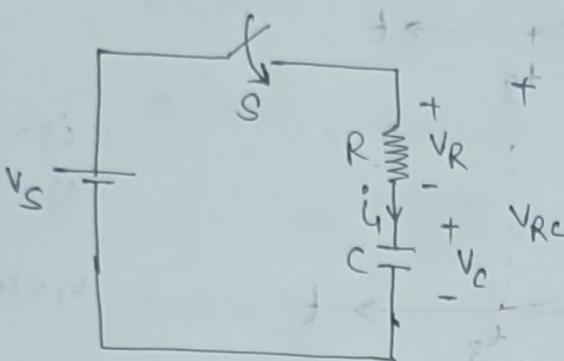
## \* R-C Circuit :-

- An uncharged capacitor in series with the resistor is connected to a dc source:-




\* Switched is closed at  $t=0$  and opened at  $t=t_1$

$$V_s = R i + \frac{1}{C} \int i dt$$


$$i = \frac{V_s}{R} e^{-t/RC}$$

$$V_c = V_s - V_R$$

$$V_R = R i$$

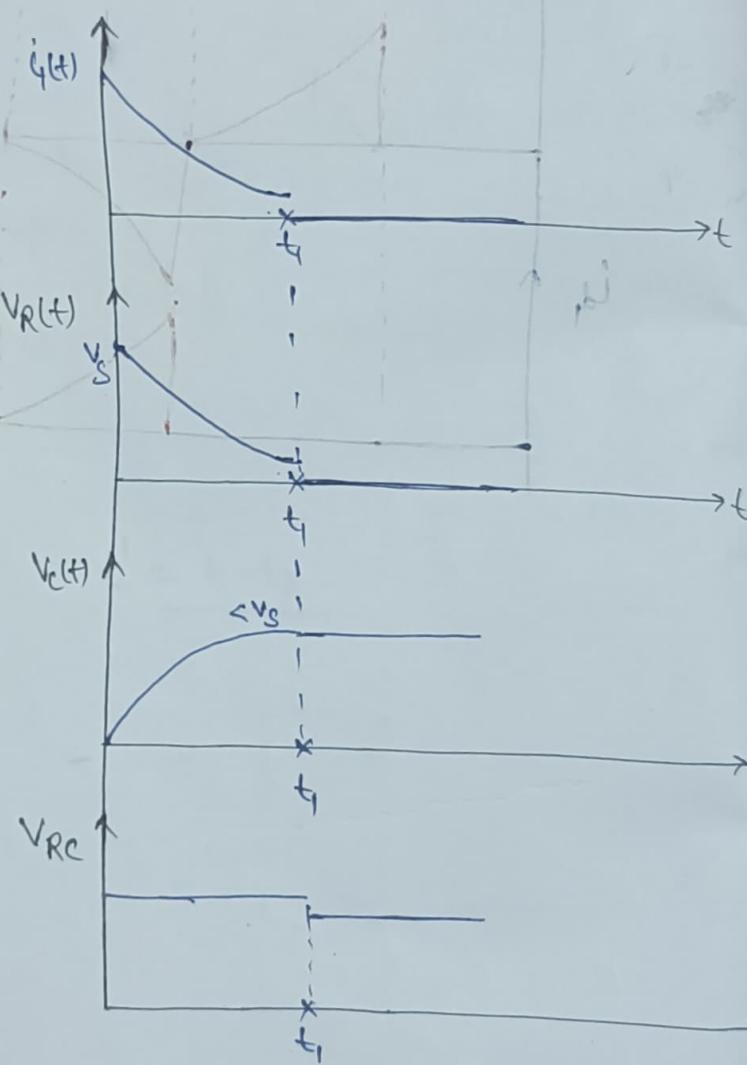

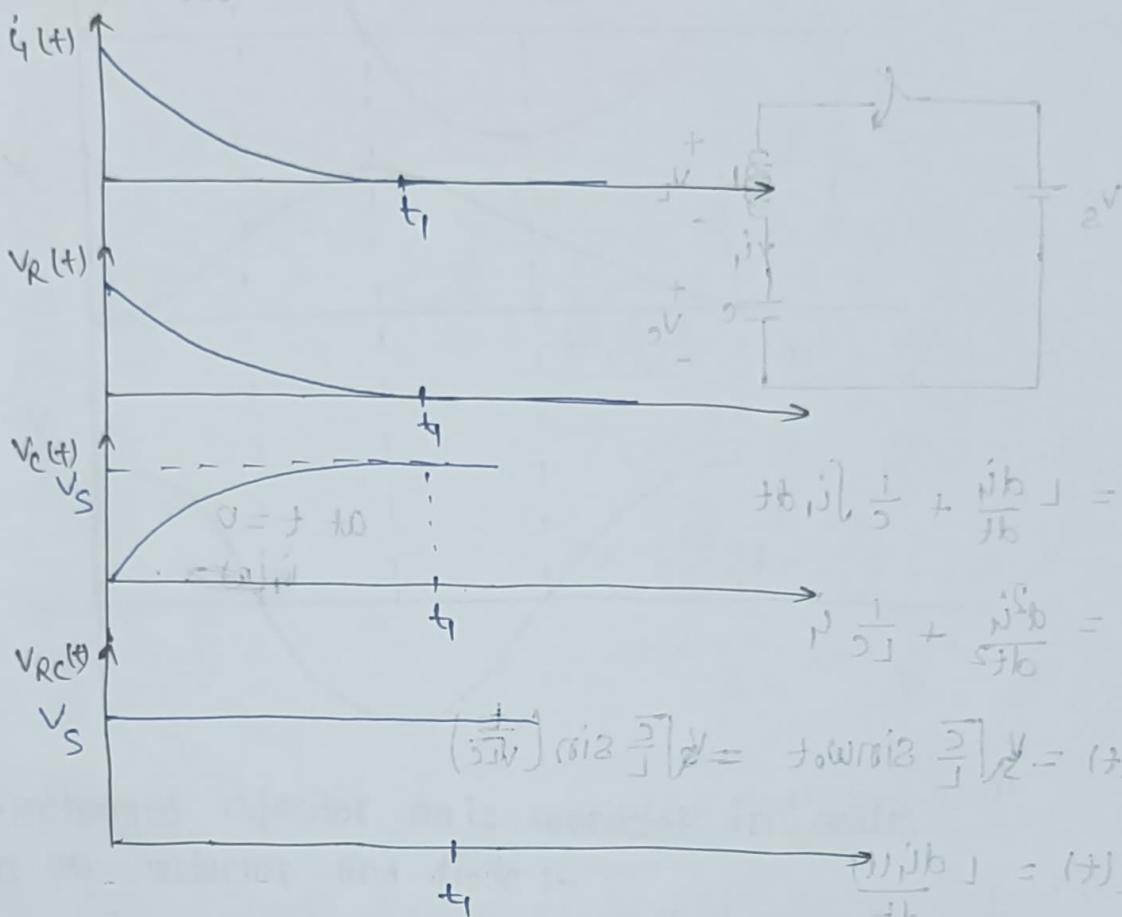\* switch is closed at  $t=0$  and opened at  $t=t_1$  (very large)



$$j\omega L \frac{1}{2} + j\frac{1}{j\omega C} = 2V$$

$$j\frac{1}{2} + j\frac{1}{j\omega C} = 0$$

$$\left(j\frac{1}{j\omega C}\right) \sin \frac{\pi}{2} \left[\phi\right] = -j \omega \sin \frac{\pi}{2} \left[\phi\right] = (-j)\frac{1}{j\omega C}$$

$$\left\{ \left(\frac{1}{j\omega C}\right) \sin \frac{1}{j\omega C} \cdot \frac{1}{j\omega C} \cdot 2V \right\} \cdot j =$$


$$j \left( \frac{1}{j\omega C} \right) 2 \sin \frac{1}{j\omega C} \cdot 2V = -2 \sin \frac{1}{j\omega C} \cdot 2V =$$

$$V - 2V = 1j(t)V$$

$$\left( \frac{1}{j\omega C} \sin -1 \right) 2V = (-2 \sin -1) 2V =$$
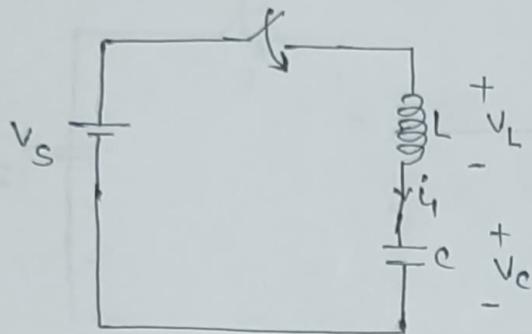
## \* L-C circuit :-

An uncharged capacitor (initially) with an inductor is connected to a dc source.




$$V_s = L \frac{di}{dt} + \frac{1}{C} \int i dt$$

$$0 = \frac{d^2i}{dt^2} + \frac{1}{LC} i$$


$$i(t) = \sqrt{\frac{C}{L}} \sin \omega_0 t = \sqrt{\frac{C}{L}} \sin \left( \frac{t}{\sqrt{LC}} \right)$$

$$\begin{aligned} V_L(t) &= L \frac{di(t)}{dt} \\ &= L \cdot \left\{ V_s \sqrt{\frac{C}{L}} \cdot \frac{1}{\sqrt{LC}} \cos \left( \frac{t}{\sqrt{LC}} \right) \right\} \\ &= V_s \cos \omega_0 t = V_s \cos \left( \frac{t}{\sqrt{LC}} \right) \end{aligned}$$

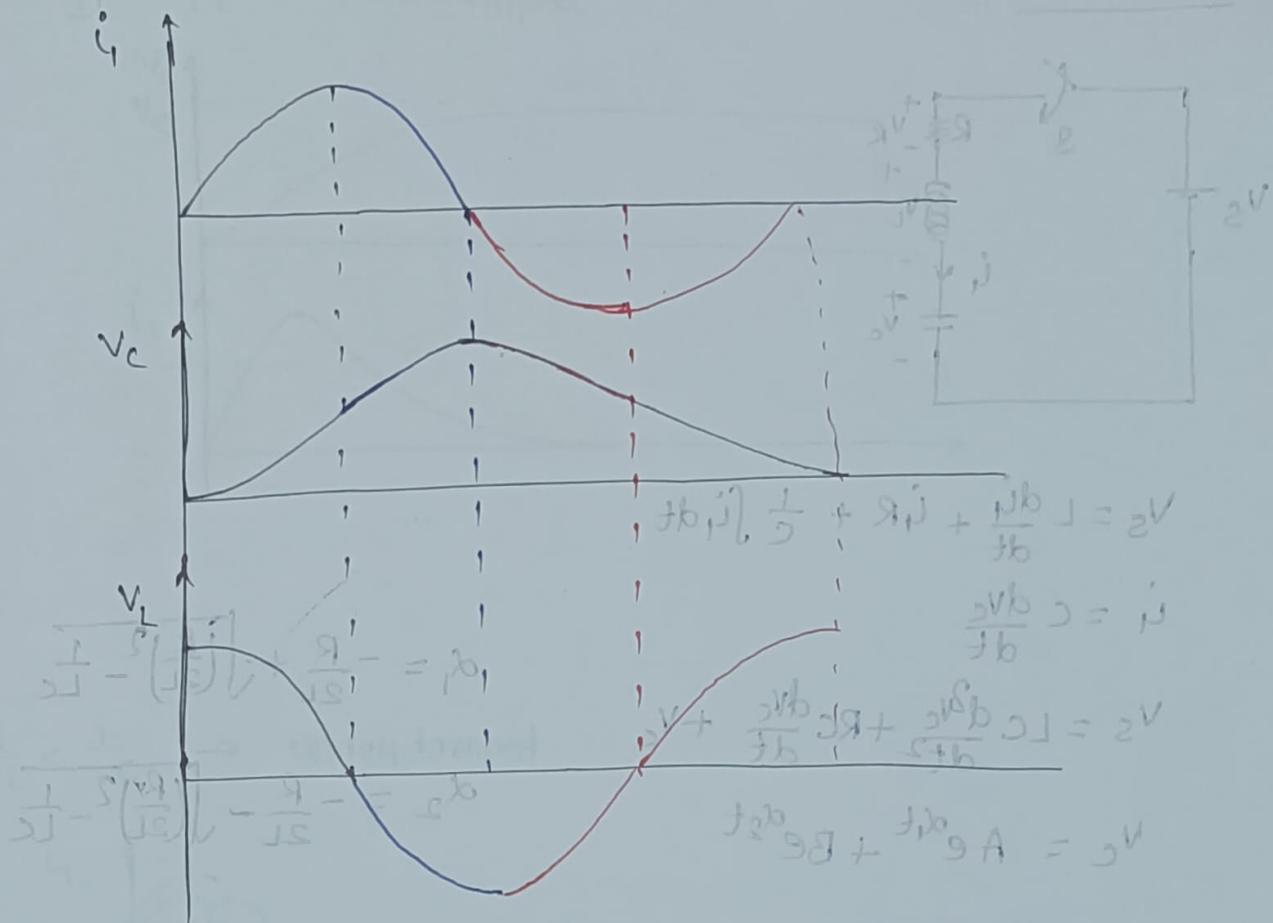
$$\begin{aligned} V_C(t) &= V_s - V_L \\ &= V_s (1 - \cos \omega_0 t) = V_s (1 - \cos \frac{t}{\sqrt{LC}}) \end{aligned}$$



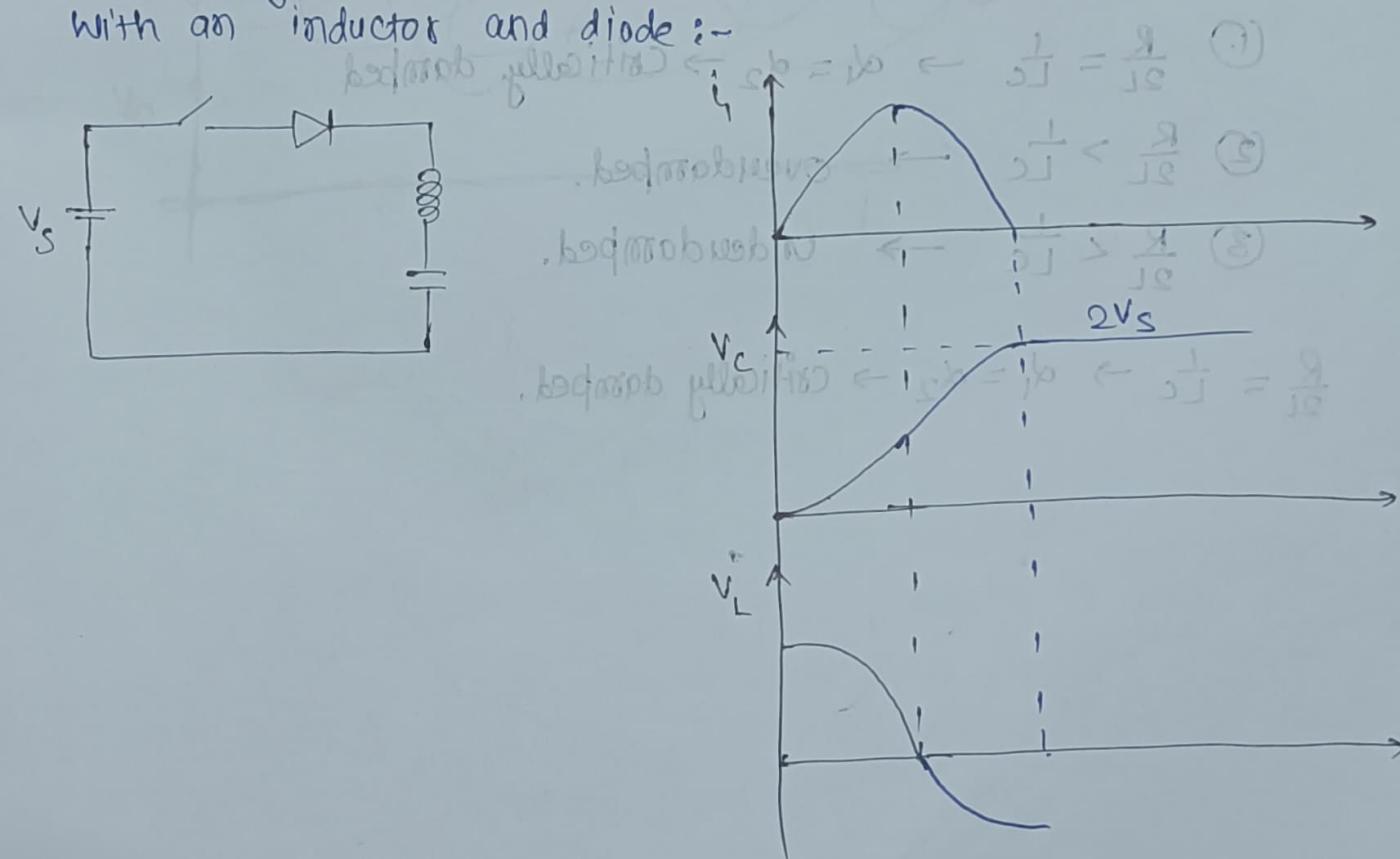\* An uncharged capacitor is connected in series with an inductor and diode :-



## \* R-L-C CKT:-

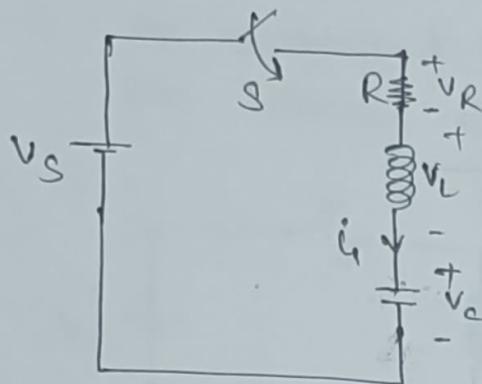

$$V_s = L \frac{di}{dt} + iR + \frac{1}{C} \int i dt$$

$$i = C \frac{dv_c}{dt}$$

$$V_s = LC \frac{d^2v_c}{dt^2} + RC \frac{dv_c}{dt} + V_c$$

$$V_c = A e^{\alpha_1 t} + B e^{\alpha_2 t}$$

$$\alpha_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\alpha_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

there are three conditions

$$\textcircled{1} \quad \frac{R}{2L} = \frac{1}{LC} \rightarrow \alpha_1 = \alpha_2 \rightarrow \text{critically damped}$$


$$\textcircled{2} \quad \frac{R}{2L} > \frac{1}{LC} \rightarrow \text{overdamped.}$$

$$\textcircled{3} \quad \frac{R}{2L} < \frac{1}{LC} \rightarrow \text{underdamped.}$$


$$\frac{R}{2L} = \frac{1}{LC} \rightarrow \alpha_1 = \alpha_2 \rightarrow \text{critically damped.}$$

$\frac{R}{2L} > \frac{1}{LC}$   $\rightarrow$  overdamped.

Final 2-1-9 \*

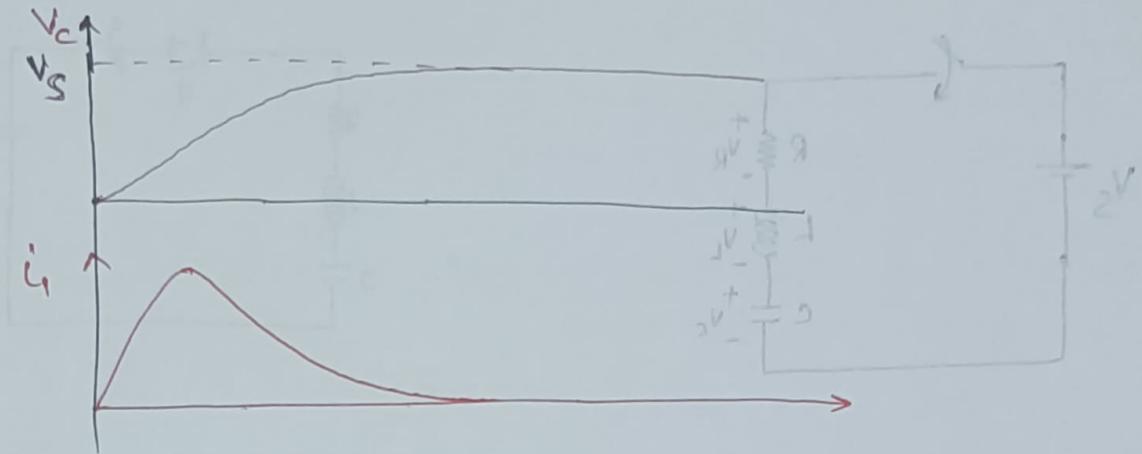


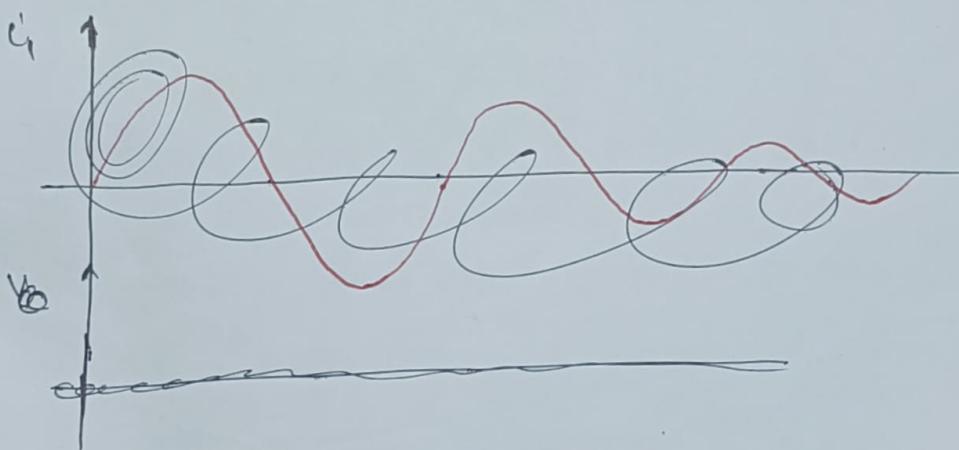$\frac{R}{2L} < \frac{1}{LC}$   $\rightarrow$  underdamped


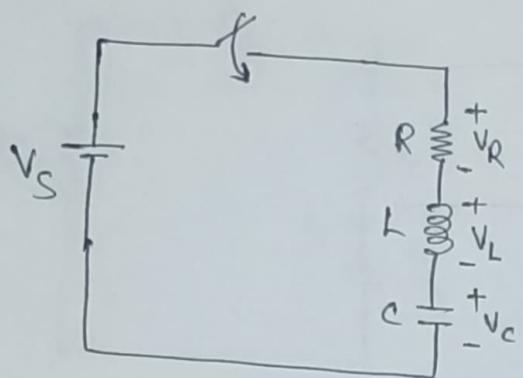
## \* R-L-C circuit

Induced voltage  $\leftarrow \frac{1}{j} \times \frac{1}{L} \times \frac{di}{dt}$



$$V_s = LC \frac{d^2i}{dt^2} + RI + V_c$$

Induced voltage  $\leftarrow \frac{1}{j} \times \frac{1}{L} \times \frac{di}{dt}$

$$V_c = A e^{d_1 t} + B e^{d_2 t}$$

there are three cases

①

$d_1 = d_2 \rightarrow$  over-damped

②

$d_1 \neq d_2 \rightarrow$  under-damped


③

$d_1 = d_2 \rightarrow$  critically damped

$$\frac{R}{2L} = d_2 \rightarrow d_1 = d_2 \rightarrow \text{critically damped.}$$



## \* R-L-C circuit with diode :-

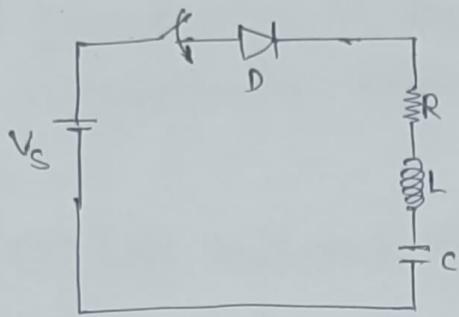

04/09/23

## # Rectifiers :-

book 9 - IITM P-I

### \* Classification of Rectifiers

- ① Uncontrolled Rectifiers :- Line freq<sup>n</sup> AC is converted into fixed voltage dc.  
(uses diode)
- ② Fully controlled Rectifiers :- Line freq<sup>n</sup> AC is converted into variable voltage dc.  
Used devices are SCRs, IGBT etc.
- ③ Half controlled Converters :-

Line freq<sup>n</sup> AC  $\rightarrow$  variable voltage dc. ;  $\downarrow = 0$   
(used device diode, SCR etc.)

### \* Uncontrolled and half-controlled converters :-


- ↳ avg. o/p voltage always +ve.
- ↳ power flow is from ac source to dc load.
- ↳ unidirectional converters.
- ↳ operating points lies in the 1st quad. of avg. voltage  $V_d$   $\rightarrow$  avg. current  $I_d$  plane.
- ↳ single quadrant converters.

### \* Uncontrolled Rectifier :-

Appn:-

- ↳ switching power supplies
- ↳ ac motor drives
- ↳ dc motor drives
- ↳ Battery chargers
- ↳ electrochemical process.
- ↳ HVDC transmission.

$$* \frac{1-\phi}{HWR} - R_{load}$$

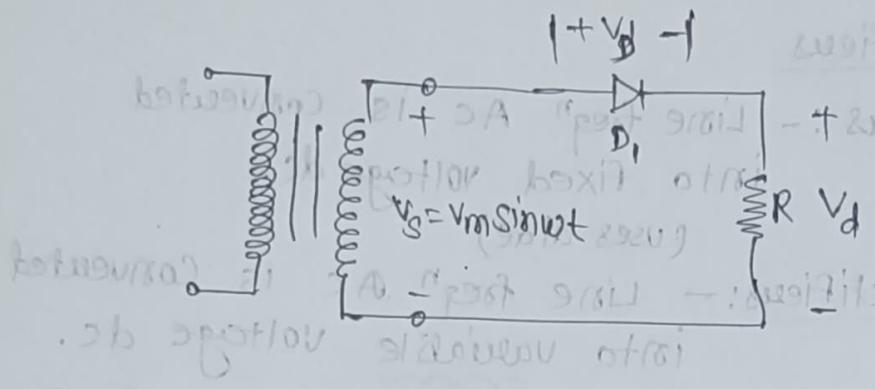

$$V_s = V_m \sin \omega t = \sqrt{2} V_s \sin \omega t$$

$V_s \rightarrow$  RMS value of source voltage

O-X; Di Conducts ~~electric~~ vs - SA (post orri)

$$V_d(\omega t) = V_S(\omega t)$$

$$i_d(wt) = \frac{V_d(wt)}{R} = i_s(wt)$$

## Diode voltage

$$N_{D_1}(w_t) = 0$$

$\frac{\pi - 2\pi}{4}$   $D_1$  is off

$$\dot{d}(wt) = 0$$

$$V_d(\omega t) = 0$$

$$\dot{y}(wt) = 0$$

$$V_{D_1}(\omega+1) = V_S(\omega+1)$$

## # performance parameters :-

- Avg. value of output voltage  $(V_d)_{avg.}$

$$(V_d)_{avg.} = \frac{1}{2\pi} \int_0^{2\pi} V_d d\omega t$$

$$= \frac{1}{2\pi} \left[ \int_0^{\pi} V_s d\omega t + \int_{\pi}^{2\pi} 0 d\omega t \right]$$

$$= \frac{1}{2\pi} \left[ \int_0^{\pi} V_m \sin \omega t d\omega t \right]$$

$$= \frac{1}{2\pi} \left[ V_m \left[ -\cos \omega t \right]_0^{\pi} \right]$$

$$= \frac{1}{2\pi} \left[ V_m (-\cos(\pi) - 1) \right]$$

$$(V_d)_{avg.} = \left( \frac{V_m}{\pi} \right)$$

- Avg. Load current  $(I_d)_{avg.}$

$$(I_d)_{avg.} = \frac{\sqrt{2} V_s}{\pi R} = \text{Avg. current Rating of diode} = \left( \frac{V_m}{\pi R} \right)$$

$$\text{peak load current} = \frac{\sqrt{2} V_s}{R} = \frac{V_m}{R}$$

$$\hookrightarrow \text{peak current Rating of diode} = \frac{\sqrt{2} V_s}{R}$$

- RMS load voltage  $(V_d)_{rms}$

$$(V_d)_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_d^2 d\omega t} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_s \sin \omega t)^2 d\omega t} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_s^2 \sin^2 \omega t d\omega t} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_s^2 (1 - \cos 2\omega t) d\omega t} = \sqrt{\frac{1}{2\pi} \left[ V_s^2 \omega t - \frac{V_s^2}{2} \sin 2\omega t \right]_0^{2\pi}} = \sqrt{\frac{1}{2\pi} \left[ V_s^2 (2\pi) - 0 \right]} = \sqrt{\frac{V_s^2}{2\pi} \cdot 2\pi} = \frac{V_s}{\sqrt{2}}$$

- RMS load current

$$I_{dRms} = \left( \frac{V_s}{\sqrt{2} R} \right) = \left( \frac{V_m}{2R} \right)$$

## Load Current form factor

$$\text{load F.F. } \frac{(I_d)_{\text{rms}}}{(I_d)_{\text{avg}}} = 1.54 \quad \frac{\frac{V_m}{2R} \times \frac{1}{2}}{\frac{V_m}{2R} \times \frac{1}{2}} = \frac{\frac{1}{2}}{\frac{1}{2}} = 1.54$$

## RMS Source current

$$(I_s)_{\text{rms}} = \left( \frac{V_s}{\sqrt{2} R} \right)$$

## DC power delivered to the load

$$P_{dc} = (V_d)_{\text{avg}} \times (I_d)_{\text{avg}} = \frac{\sqrt{2} V_s}{\pi} \times \frac{\sqrt{2} V_s}{\pi R}$$

## Transformer utility factor (TUF)

DC Power delivered / Transformer power Rating.

↪ If transformer RMS Current Rating is same as  $(I_d)_{\text{rms}}$ , then -

$$\begin{aligned} TUF &= \frac{(P_{dc})}{V_s \times (I_d)_{\text{rms}}} = \frac{\frac{\sqrt{2} V_s}{\pi} \times \frac{\sqrt{2} V_s}{\pi R}}{\frac{\sqrt{2} V_s}{\pi} \times \frac{V_s}{\sqrt{2} R}} \\ &= \frac{\sqrt{2} \cancel{V_s} \cdot \sqrt{2} \cancel{V_s}}{\cancel{\pi} \cancel{R}} \cdot \frac{\cancel{\pi}}{\cancel{\sqrt{2} R}} \\ &= 29\% \end{aligned}$$

↪ Power Rating of transformer must be greater by  $\frac{1}{0.29} = 3.5$  times the DC load power rating.

$$\left( \frac{2V}{\sqrt{2}V} \right) = 200\% I$$

- Rectifier efficiency

$$= \frac{\text{dc side load power}}{\text{(ac load power + rectifier loss)}} = \frac{P_{dc}}{(P_{ac}) + P_{rec.}}$$

$$= \frac{\text{dc side load power}}{\text{(ac side power + rectifier loss)}} \rightarrow \text{diode loss}$$

$$= \frac{(I_d)^2 * R}{(I_d)_{RMS}^2 (R+R_f)}$$

$$= \frac{\left(\frac{\sqrt{2}V_s}{\pi R}\right)^2 * R}{\left(\frac{V_s}{\sqrt{2}R}\right)^2 (R+R_f)}$$

$$= \frac{\left(\frac{4}{\pi^2}\right)}{\left(1 + \frac{R_f}{R}\right)^2}$$

$$= \frac{40.6}{\left(1 + \frac{R_f}{R}\right)^2} \% \quad \text{For } R_f = 0 \quad \text{Rectification } \eta = 40.6\%$$

- Ripple factor  $\gamma$ :

$\gamma = \text{RMS value of ripple content in load voltage}$

$$\gamma = \frac{(V_d)_{avg.}}{\sqrt{V_{drms}^2 - V_{avg.}^2}}$$

$$= \sqrt{(FF)^2 - 1}$$

$$\gamma \approx 1.21$$

$$RF = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{avg.}^2}}{V_{avg.}}$$

$$FF = \frac{\text{avg.}}{\text{avg.}}$$

• Input source PF =

$$\frac{\text{Source side actual power}}{\text{Source side apparent power}}$$

↓

$$= \frac{P_{dc}}{\text{source side RMS voltage} \times \text{RMS current}}$$

$$= \frac{2V_S^2}{\pi^2 R}$$

$$= \frac{2\sqrt{2}V_S^2}{\pi^2 R}$$

$$= \frac{(2\sqrt{2})^2 V_S^2}{\pi^2 R}$$

$$= \frac{8V_S^2}{\pi^2 R}$$

$$= \frac{8V_S^2}{(2\pi)^2}$$

$$= \frac{8V_S^2}{4\pi^2}$$

$$= 0.286$$

• Peak inverse voltage PIV:

- Maximum instantaneous voltage that appears across the diode during the blocking time

$$= \sqrt{2}V_S = \underline{V_m}$$

$$\frac{2.04}{(\frac{21}{3})}$$

Y 10001 30001

negative tool mi sotong 30001 70 30001 20001 = 8

B10(hv)

$$B10(hv) - 2000V =$$

B10(hv)

$$L - 977 =$$

12.1 = 6

• Input source PF =  $\frac{\text{Source side actual power}}{\text{Source side apparent power}}$

$\Rightarrow \text{PF} = \frac{P_{dc}}{\sqrt{V_m I_{rms}}}$

$\text{PF} = \frac{2\sqrt{2} V_s}{\pi R}$

$\text{PF} = \frac{2\sqrt{2} (2R+I)}{2\pi R}$

$\text{PF} = \frac{2\sqrt{2} (2R+I)}{2\pi R} = \frac{(2\sqrt{2})}{\pi^2} = 0.286$

• Peak inverse voltage PIV:

- Maximum instantaneous voltage that appears across the diode during the blocking time
- $$= \sqrt{2} V_s = \underline{V_m \left( \frac{2R}{\pi} + 1 \right)}$$

$$\frac{2.04}{\left( \frac{2R}{\pi} + 1 \right)}$$

$$B(v)$$


$$\frac{B(v) - 2mB(v)}{B(v)} =$$

$$B(v)$$

$$1 - \frac{B(v)}{B(v)} =$$

$$1 - 1 = 0$$

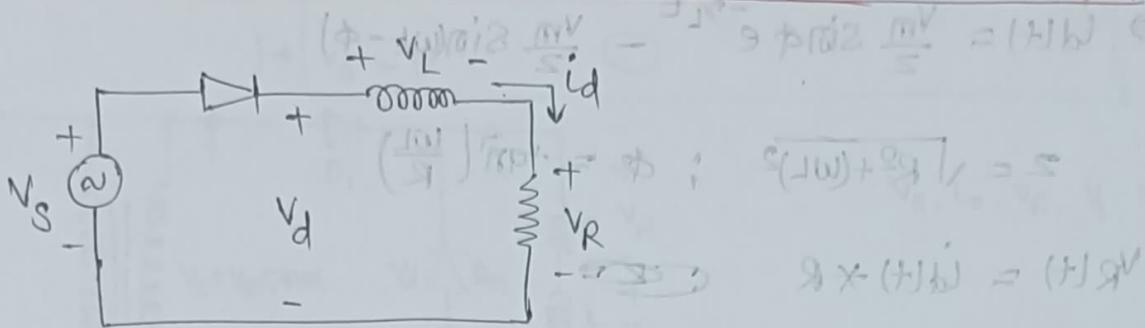\* 1-Φ HW Uncontrolled Rectifier with R-L load :-



during positive half cycle

diode  $\rightarrow$  on

$$V_d = V_s = \sqrt{2} V_s \sin \omega t$$

$$= R i_d(t) + L \frac{d i_d(t)}{dt}$$

$$i_d(0) = 0$$

$$\text{&} L \cdot \frac{d i_d(0)}{dt} = 0$$

$$\Rightarrow V_d = V_s = R i_d(t) + L \frac{d i_d(t)}{dt}$$

$$V_s(s) = R I_d(s) + L s E_d(s)$$

$$V_s(s) = I_d(s) [R + Ls]$$

$$I_d(s) = \frac{V_s(s)}{R + Ls}$$

$$= \frac{V_s(s)/R}{(s + \frac{R}{L})}$$

$$= V_s (1 - e^{-Rt/L})$$

$$i(t) = C e^{-t/\tau} + \frac{V_m}{121} \sin(\omega t - \phi)$$

$$\text{by using initial condn } i(0) = 0$$

$$0 = C + \frac{V_m}{121} \sin(-\phi)$$

$$\Rightarrow C = \frac{V_m}{121} \sin \phi$$

$$\therefore i(t) = \frac{V_m}{121} \sin \phi e^{-t/\tau} + \frac{V_m}{121} \sin(\omega t - \phi)$$

$$|Z| = \sqrt{R^2 + (\omega L)^2}$$

$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right)$$

$$\frac{V_m \sin \omega t}{s^2 + \omega^2} = R I_d(s) + L s E_d(s)$$

$$I_d(s) = \frac{V_m \omega}{(s^2 + \omega^2)(R + Ls)}$$

$$I_d(s) = \frac{k_1}{R + Ls} + \frac{k_2}{(s + j\omega)} + \frac{k_3}{(s - j\omega)}$$

$$\Rightarrow i_d(t) = \frac{V_m}{Z} \sin \phi e^{-Rt/L}$$

$$- \frac{V_m}{Z} \sin(\omega t - \phi)$$

$$Z = \sqrt{R^2 + (\omega L)^2}$$

$$\Rightarrow i_d(t) = \frac{V_m}{2} \sin \phi e^{-R_L t} - \frac{V_m}{2} \sin(\omega t - \phi)$$

$$Z = \sqrt{R^2 + (\omega L)^2} ; \phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$V_R(t) = i_d(t) \times R$$

$$V_L(t) = L \frac{di_d(t)}{dt} = V_d(t) - V_R(t)$$

0 to  $t_3$

$$L \frac{di_d(t)}{dt} = V_L$$

$$\int_{0}^{t_3} i_d(t) dt = \int_{0}^{t_3} \frac{V_L}{L} dt$$

$$i_d|_{t=0} = 0$$

$$i_d|_{t=t_3} = 0$$

$$\Rightarrow \int_{0}^{t_3} \frac{V_L}{L} dt = 0 = \frac{i_d}{\omega R}$$

$$\Rightarrow \int_{0}^{t_1} \frac{V_L}{L} dt + \int_{t_1}^{t_3} \frac{V_L}{L} dt = 0 = (2) \beta$$

means area(A) =  $\beta$

area(B).


$$\int_{0}^{t_1} \frac{V_L}{L} dt = - \int_{t_1}^{t_3} \frac{V_L}{L} dt$$

$$\text{at } \omega t = \beta, i = 0$$


$$\Rightarrow i\left(\frac{\beta}{\omega}\right) = \frac{V_m}{2} \sin \phi e^{-R_L \beta} - \frac{V_m}{2} \sin(\beta - \phi) = 0$$

$$\therefore 0 = \underline{\hspace{2cm}}$$

Solve to find  $\beta$ .

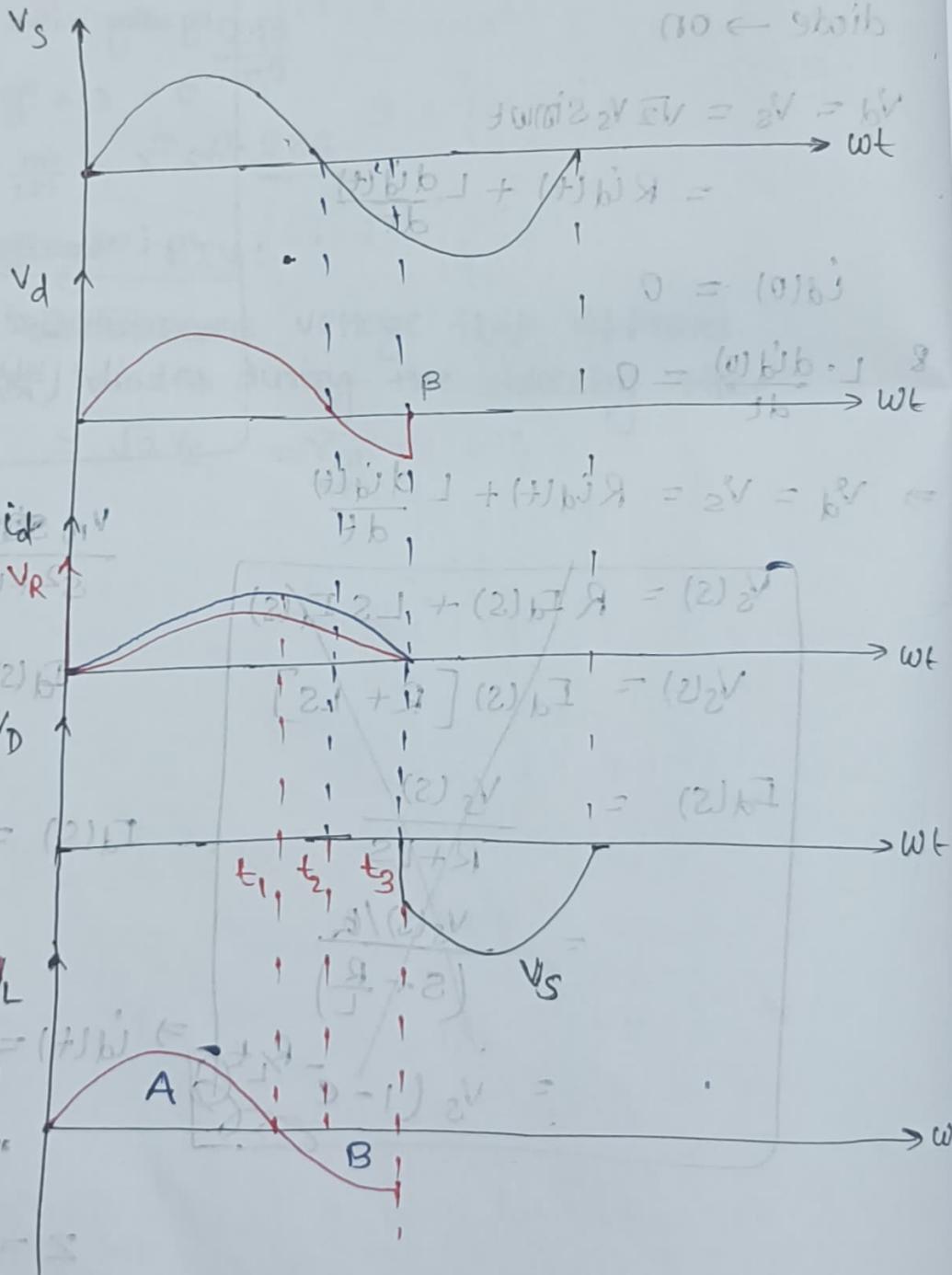
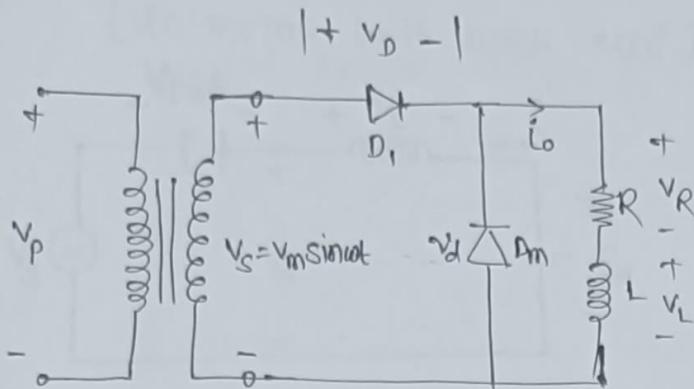
# \* R-L Load With Free Wheeling diode :-



during 0 to t<sub>3</sub>: D<sub>1</sub> is in Forward biased.

for t > t<sub>3</sub>

both D<sub>1</sub> and D<sub>m</sub>  
are in off

Cond'n.


$$i = 0$$

$$V_R = 0$$

$$V_L = 0 \quad (\because i = 0) \\ \therefore \frac{di}{dt} = 0$$

$$N_D = V_S \checkmark$$

$$V_{Dm} = 0$$

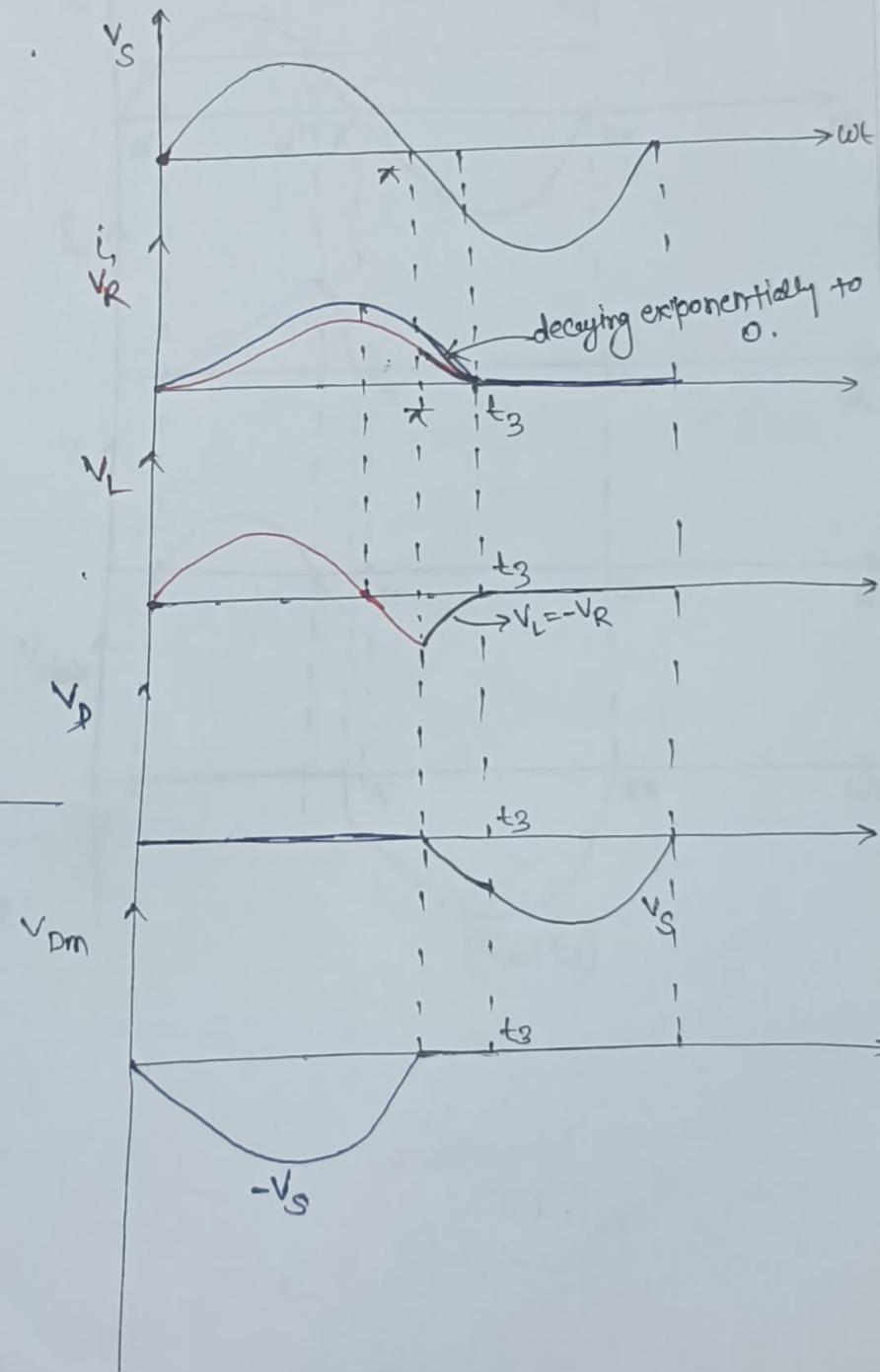


→ The effect of this  
f.w diode is to  
prevent a negative  
voltage appears  
across the load.

$\hookrightarrow$  at



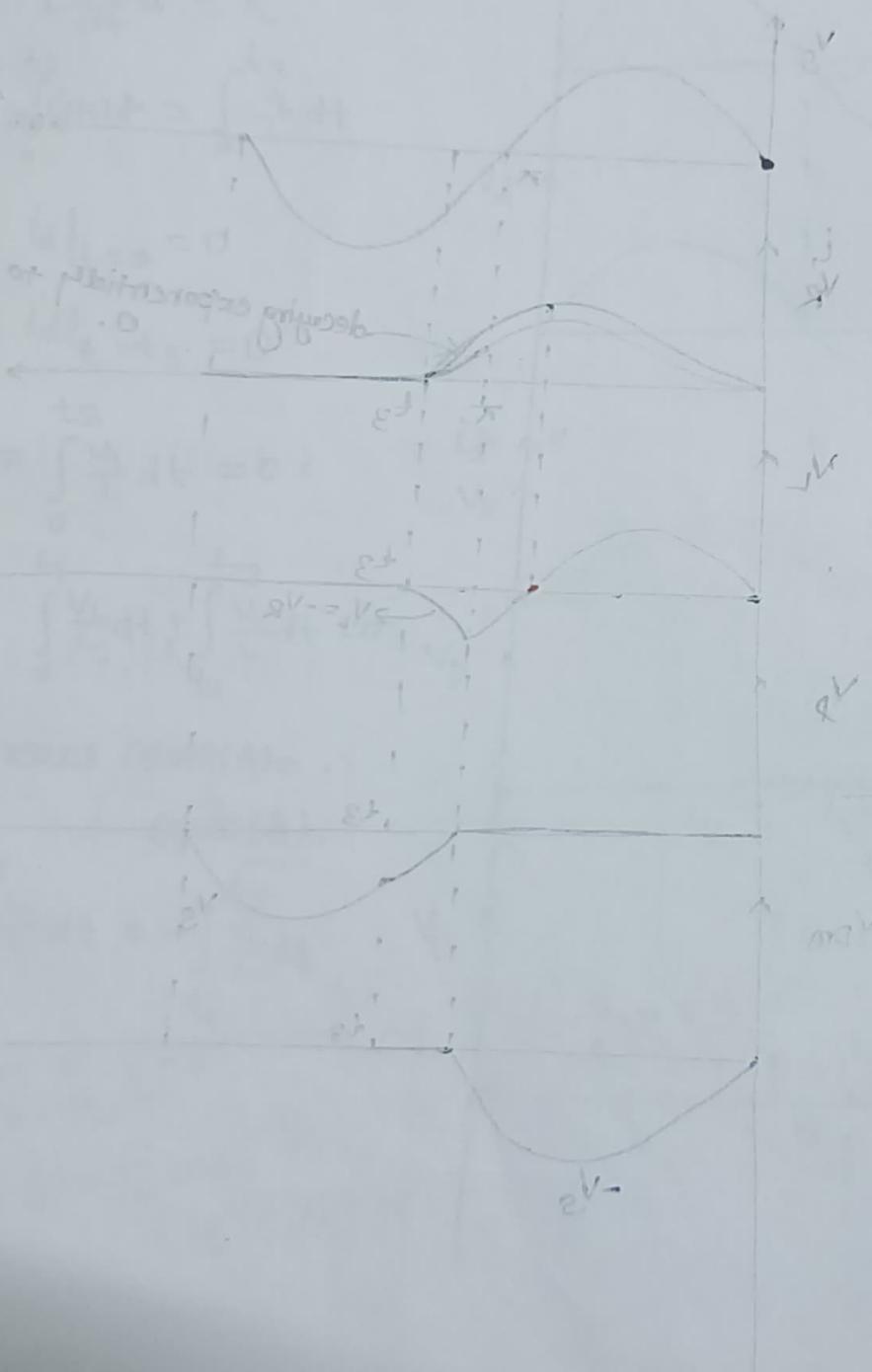current  $i = 10 \text{ A}$ :  $\frac{\pi}{2} \text{ rad}$  from forward direction



path D, and D<sub>1</sub>  
comes out of


$$\begin{aligned} & \text{Current } i \\ & i = V/R \\ & i = \frac{V_0}{R} \cos(\omega t) \\ & i = 10 \cos(10t) \end{aligned}$$

$$\begin{aligned} & v = V \sin(\omega t) \\ & v = 12 \sin(10t) \end{aligned}$$

the effect of this  
on the above  
currents &  
voltage  
and power  
will be seen

## \* L-E load

(dc motor with back emf.)

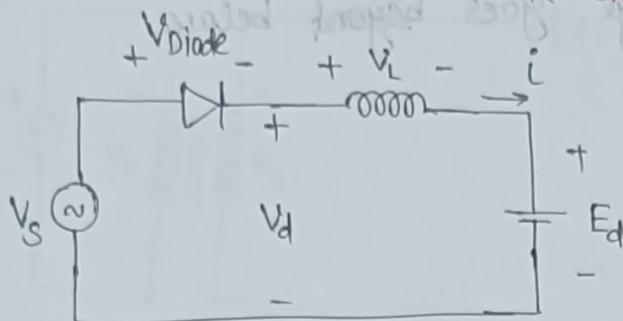

diode is F.B. When

$$V_s \geq E_d$$

$$\text{at } \omega t = \omega t_1 = \alpha$$

$$V_s = E_d$$

$$\sqrt{2}V_s \sin \alpha = E_d$$

$$\alpha = \sin^{-1} \left( \frac{E_d}{\sqrt{2}V_s} \right)$$

for  $\omega t \geq \omega t_1$ ,


D<sub>1</sub> is on,  $V_{\text{diode}} = 0$

$$\sqrt{2}V_s \sin \omega t = L \frac{di}{dt} + E_d$$

$$\text{at } \omega t = \alpha, i = 0$$



$$\Rightarrow \sqrt{2}V_s \sin \alpha = L \frac{di}{dt} + E_d$$

$$\frac{di}{dt} \Big|_{\omega t=\alpha} = \frac{\sqrt{2}V_s \sin \alpha - E_d}{L} = 0$$

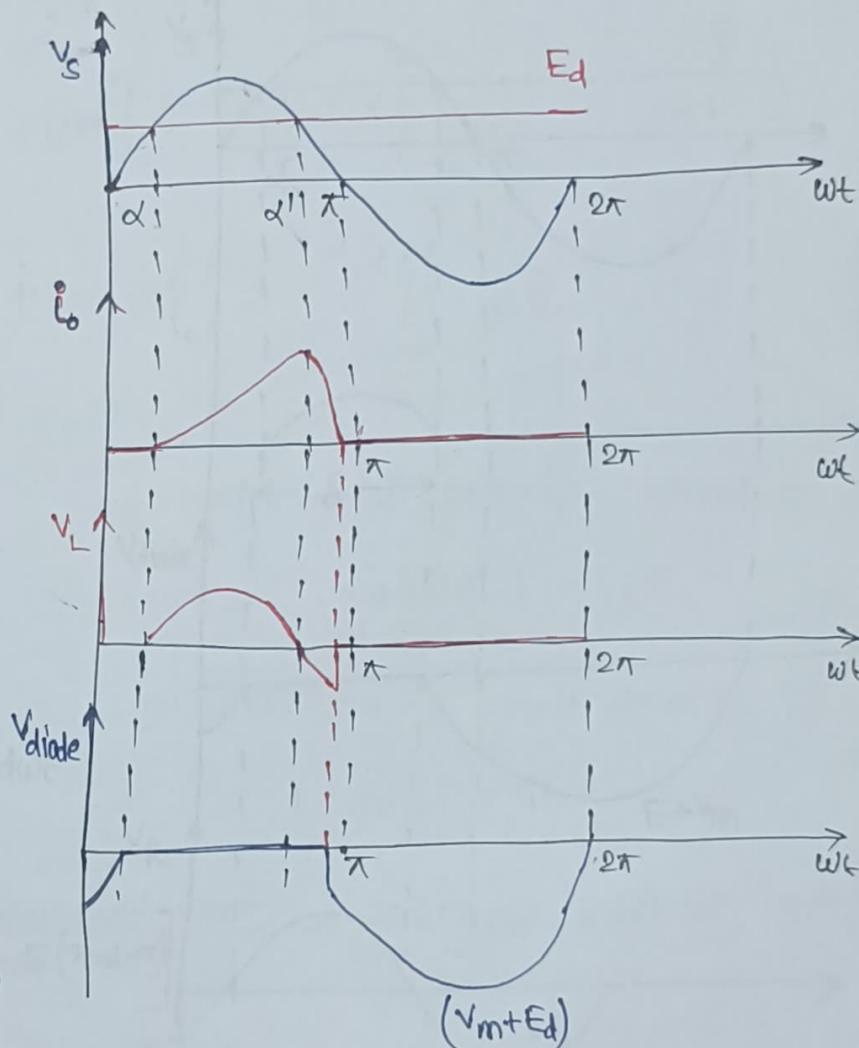

→ Current continues to flow for a while even after the i/p voltage goes beyond below the dc back-emf.

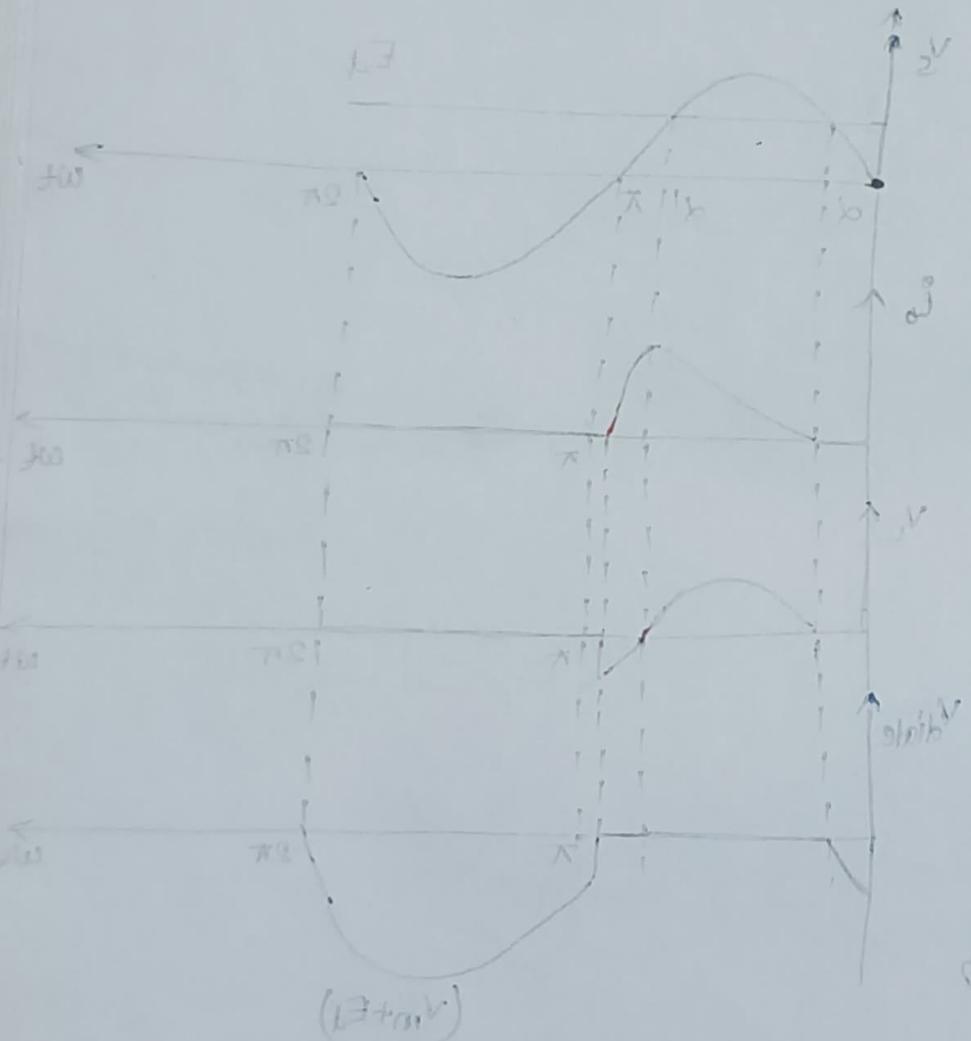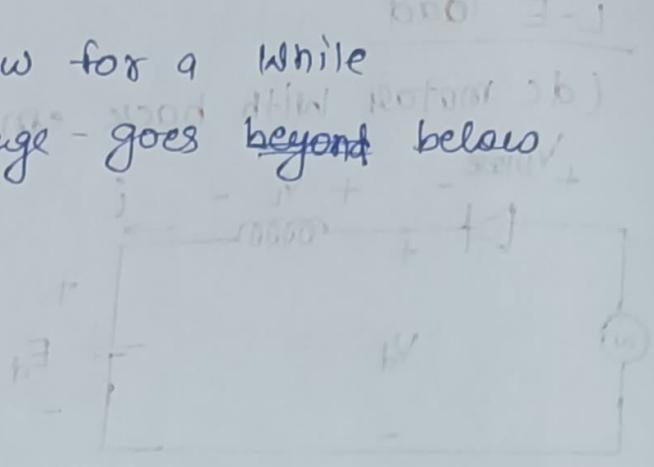- $t_3 \rightarrow 2\pi/\omega$
- $i = 0$
- $\frac{di}{dt} = 0, V_L = 0$



04/01/2017 - 8:17 21 96

$$A_2 < A_1$$

$$\lambda = fL = \omega L$$

$$B = E_0$$

$$B^2 = h_0 B_0^2 Z_0^2$$

$$\left(\frac{h_0}{2\sqrt{Z_0}}\right) B_0 Z_0 = \omega$$

$$f\omega \leq \omega_0$$

$$0 = \omega_0 \sin \theta, \text{ so } 21.19$$


$$B^2 + \frac{1}{f^2} B_0^2 = f\omega B_0 Z_0$$

$$0 = \dot{\theta}, B = f\omega$$

$$B^2 + \frac{1}{f^2} B_0^2 = 20 B_0^2 Z_0^2$$

$$0 = \frac{B^2 - B_0^2 \cos^2 \theta}{f^2} Z_0^2 = \frac{B^2 - B_0^2}{f^2} Z_0^2$$

## \* Battery charging circuit :-

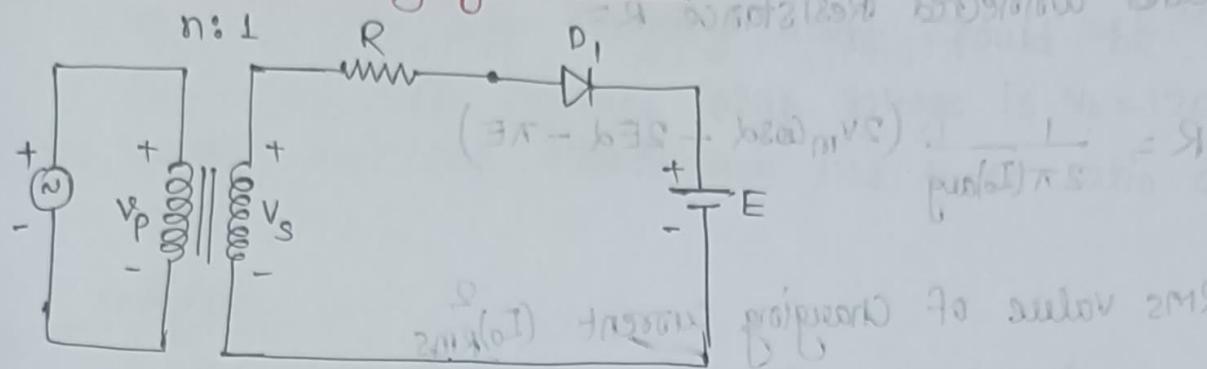

For  $V_s > E$ ,  
diode  $D_1$  conducts.

$$i_o = \frac{V_R}{R} = \left( \frac{V_s - E}{R} \right)$$

$$\alpha = \sin\left(\frac{E}{V_m}\right)$$

• Avg. charging current



$$(I_o)_{avg} = ?$$

$$(I_o)_{avg} = \frac{1}{2\pi} \int_{\alpha}^{\pi-\alpha} \left( \frac{\sqrt{2}V_s \sin \omega t - E}{R} \right) dt$$

$$= \frac{1}{2\pi R} \left[ \int_{\alpha}^{\pi-\alpha} \sqrt{2}V_s \sin \omega t dt + E(\pi - \alpha - \alpha) \right]$$

$$= \frac{1}{2\pi R} \left[ \sqrt{2}V_s \cdot (\cos(\alpha) - \cos(\pi - \alpha)) - E(\pi - 2\alpha) \right]$$
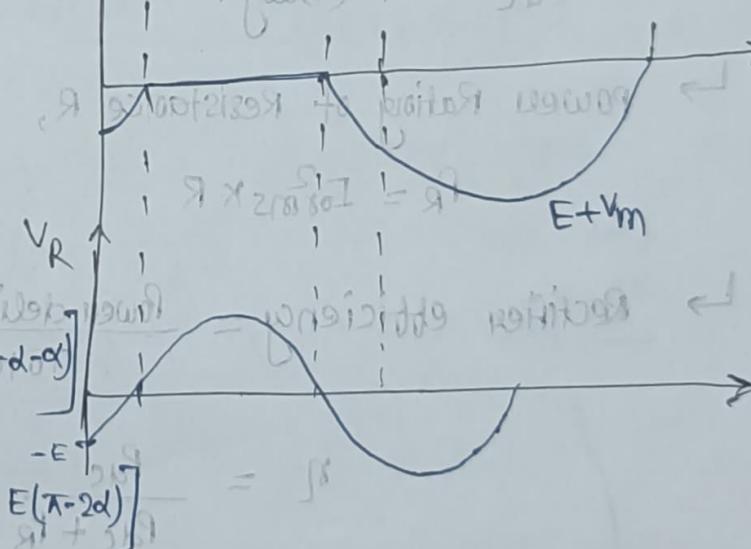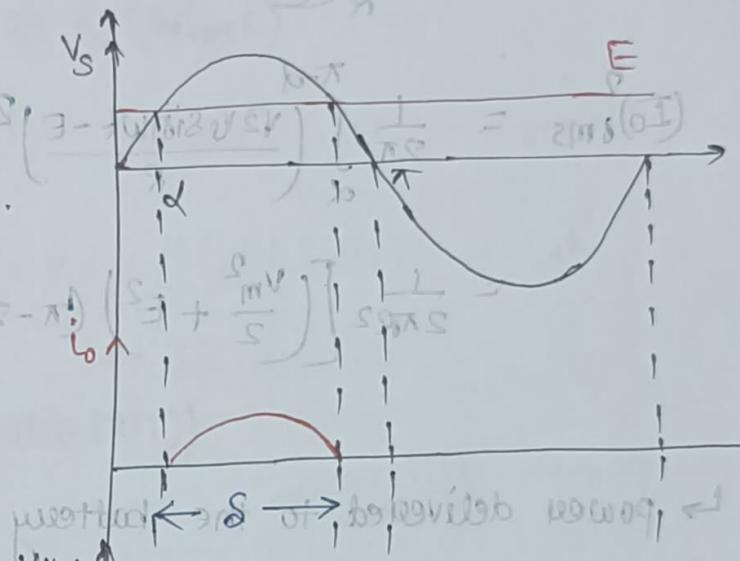
$$= \frac{1}{2\pi R} \left( 2V_m \cos \alpha + 2E\alpha - \pi E \right)$$



$$\pi + mV = 260.6 \text{ to } 270.6$$

- Series connected Resistance  $R =$

$$R = \frac{1}{2\pi(I_0)_{avg}} (2V_m \cos\alpha + 2E_d - \pi E)$$

- RMS value of Charging current  $(I_0)_{RMS}^2$

$$(I_0)_{RMS} = \frac{(V_0)_{RMS}^2}{R}$$

$$(I_0)_{RMS}^2 = \frac{1}{2\pi} \int_{-\alpha}^{\pi-\alpha} \left( \frac{\sqrt{2}V \sin \omega t - E}{R} \right)^2 d\omega t$$

$$= \frac{1}{2\pi R^2} \left[ \left( \frac{V_m^2}{2} + E^2 \right) (\pi - 2\alpha) + \frac{V_m^2}{2} \sin 2\alpha - 4V_m E \cos \alpha \right]$$

↳ Power delivered to the battery

$$P_{DC} = E \times (I_0)_{avg}$$

↳ Power Rating of Resistance  $R$ ,

$$P_R = (I_0)_{RMS}^2 \times R$$

↳ Rectifier efficiency =  $\frac{\text{Power delivered to battery}}{\text{Total input power}}$

$$\eta = \frac{P_{DC}}{P_{DC} + P_R} = \frac{P_{DC}}{(I_0)_{avg} R + (I_0)_{avg} R} = \frac{P_{DC}}{2V_m R}$$

↳ PIV of diode =  $V_m + E$

Ques) A battery has a voltage of  $E = 12V$  and capacity 100 wh. The avg. charging current should be  $I_{dc} = 5A$ . The primary input voltage is  $V_p = 120V$ , 50 Hz, and the transformer has turns ratio of 2:1.

Calculate

- (a) Conduction angle  $\delta$  of the diode ( $180^\circ - 2\alpha$ )
- (b) current limiting Resistors  $R$ .
- (c) Power Rating  $P_R$  of  $R$  ( $I_{rms}^2 R$ )
- (d) charging time
- (e) the rectified  $\eta$
- (f) PIV of diode.

$$V_p = 120V$$

$$\text{so, } \frac{V_p}{V_s} = 60V \quad (\because \text{turns ratio (2:1)})$$

$$\text{so, } \alpha = \sin^{-1}\left(\frac{E}{V_m}\right)$$

$$\alpha = \sin^{-1}\left(\frac{12}{60}\right) \sin^{-1}\left(\frac{12}{\sqrt{2} \times 60}\right)$$

$$\alpha = 11.53^\circ \approx 12^\circ = 8.13^\circ$$

$$\alpha \rightarrow 8.13^\circ$$

$$\begin{aligned} \text{(a) Conduction angle } \delta &= (180^\circ - 2\alpha) \\ &= (180^\circ - 2 \times 12^\circ) \\ &= \underline{156^\circ} \end{aligned} \quad \left. \begin{array}{l} \text{Conduction angle} \\ S = (180^\circ - 2\alpha) \\ = 163.739^\circ \end{array} \right\}$$

$$\begin{aligned} \text{(b) } R &= \frac{1}{2\pi (I_0)_{avg}} (2V_m \cos \alpha + 2E\alpha - \pi E) \\ &= \frac{1}{2\pi \times 5} (2 \times 60 \times \cos(12^\circ) + 2 \times 12 \times (0.2094) - \pi \times 12) \\ &= \frac{1}{10\pi} [117.377 + 5.0256 - 37.6991] \end{aligned}$$

$$R = 2.696 \Omega \quad (4.26)$$

$$(I_0)^2_{rms} = \frac{1}{2\pi(2.696)2} \left[ \left(\frac{60}{2}\right)^2 + (12)^2 \right] (2.7227)$$

$$+ \frac{(60)^2}{2} \sin(24^\circ) - 4 \times 60 \times 12 \times \cos(12^\circ)$$

$$= \frac{1}{2\pi(2.696)} \left[ 5292.92880 + 732.12595 - 2817.065 \right]$$

$$= \frac{3207.9897}{45.6688}$$

$$(I_0)^2_{rms} = 70.2446 \text{ A.} \quad \frac{(286.4 \text{ W})}{(286.4 \text{ W})}$$

$$P_R = (70.2446) \times 2.696$$

$$= 189.3796 \text{ W.}$$

c) power delivered

$$(b) (I_0)_{avg} = \frac{1}{2\pi R} \left[ 2V_m \cos \alpha + 2E \alpha - \frac{\pi E}{R} \right] \quad \frac{1}{2\pi R} \left[ 2V_m \cos \alpha + 2E \alpha - \frac{\pi E}{R} \right] = 0$$

$$\Rightarrow R = \frac{1}{2\pi(I_0)_{avg}} \left[ 2V_m \cos \alpha + 2E \alpha - \frac{\pi E}{R} \right] = \frac{1}{2\pi \times 5} \left[ 2 \times 60 \times 0.9899 + 2 \times 12 \times 0.1418 - \pi \times 12 \right]$$

$$\underline{R} = \underline{\left( \frac{133.78}{10\pi} \right)}$$

$$(3\pi - 6.38 + 6.200mV) = \frac{4.2585\Omega}{\pi} = 9 \quad (d)$$

c) Power Rating of Resistor:  $P_R = (I_0)_{rms}^2 \times R$

$$(I_0)_{rms}^2 = \frac{1}{2\pi} \int \left( \frac{\sqrt{2}V_m \sin \omega t - E}{R} \right)^2 dt = \frac{1}{2\pi R^2} \left[ \left( \frac{V_m^2}{2} + E^2 \right) (\pi - 2\alpha) + \frac{V_m^2}{2} \sin 2\alpha - 4V_m E \cos \alpha \right]$$

$$= \frac{1}{2\pi R^2} \left[ \left( \frac{V_m^2}{2} + E^2 \right) (\pi - 2\alpha) + \frac{V_m^2}{2} \sin 2\alpha - 4V_m E \cos \alpha \right]$$

$$= \frac{1}{2\pi(4.2585)^2} \left[ \left\{ \left( \frac{\sqrt{2} \times 60}{2} \right)^2 + 12^2 \right\} \left( \pi - \frac{0.28379}{0.1487} \right) + \left( \frac{\sqrt{2} \times 60}{2} \right)^2 \sin(8.524) - 4 \times \sqrt{2} \times 60 \times 12 \cos(4.26) \right]$$

=

② charging time  $\Rightarrow \delta = \frac{2\pi}{\omega}(1 - 2\alpha)$

$$\omega t = \delta = 2.8577$$


$$t = \frac{2.8577}{2\pi \times 50} = \underline{\underline{9.09 \text{ msec.}}}$$

③  $\eta_{\text{sec.}} = \left( \frac{P_{dc}}{P_{dc} + P_R} \right) = \frac{E \times (I_o)_{\text{avg}}}{E \times (I_o)_{\text{avg}} + (286.4)}$

$$= \frac{12 \times 5}{12 \times 5 + 286.4} = \underline{\underline{17\%}}$$


④  $PIV = V_m + E$   
 $= \sqrt{2} \times 60 + 12$   
 $= \underline{\underline{96.8528V}}$
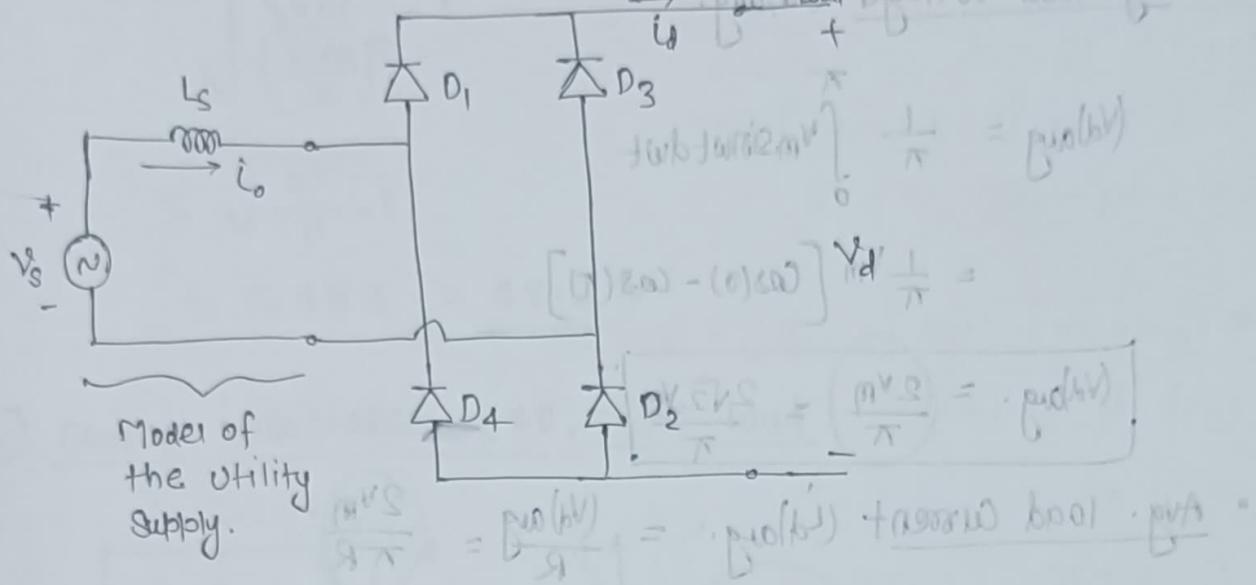
# \* Single-phase Fullwave Bridge Rectifiers :-



$$V_s = \sqrt{2} V_S \sin \omega t$$

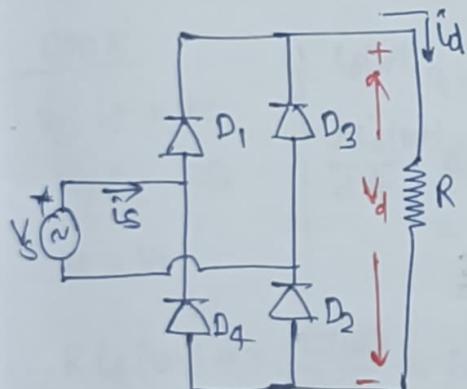① source inductance  
 $L_s = 0$ , Load is  
 pure resistance.




0 to  $\pi$ .

$V_s$  is +ve.  
 $D_1, D_2$  is forward biased

Current path is

$V_s, D_1, \text{ Load}, D_2$

Load voltage  $V_d =$

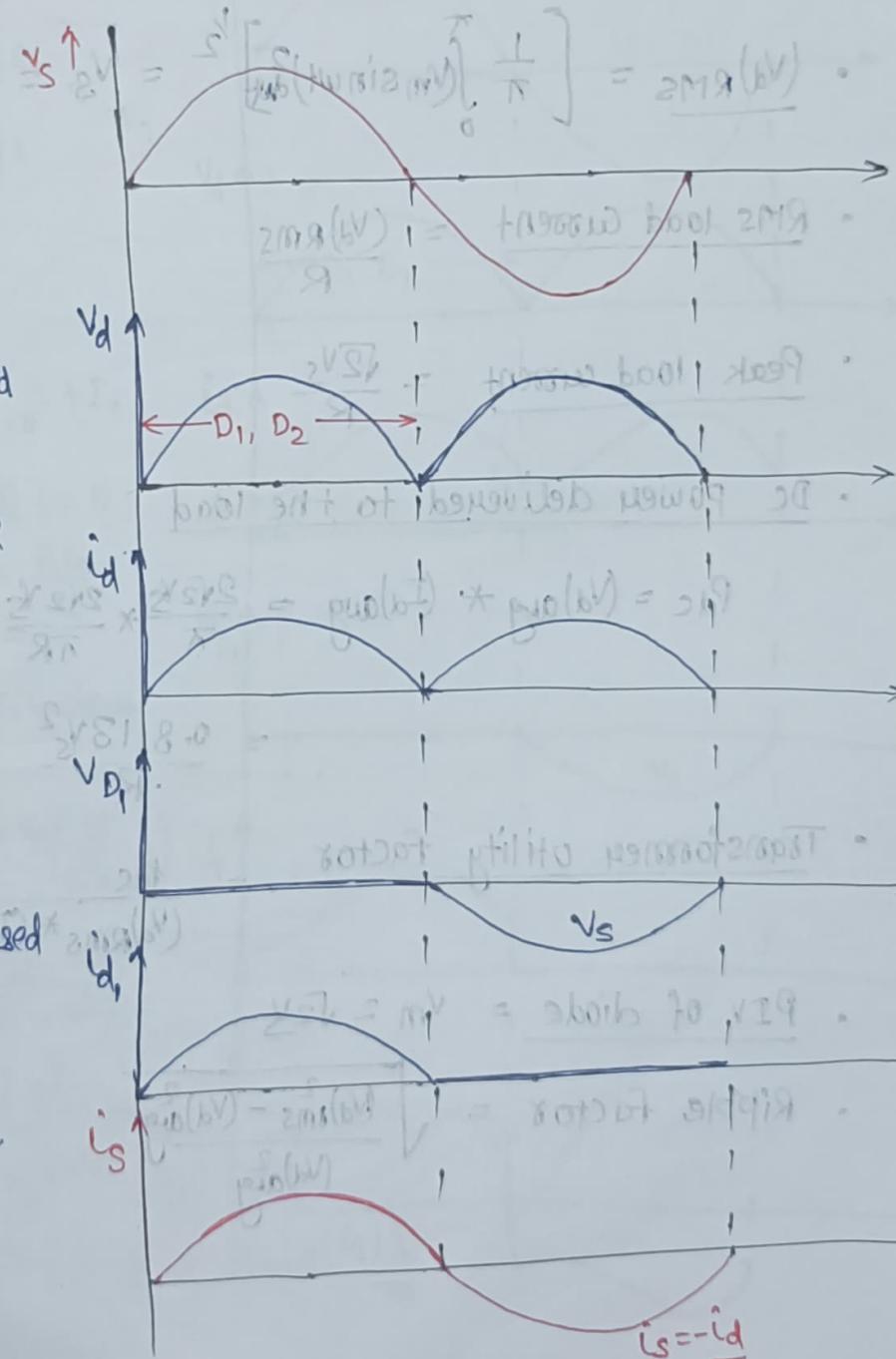

- Avg. load voltage ( $V_d$ )<sub>avg.</sub>

$$(V_d)_{avg} = \frac{1}{\pi} \int_0^{\pi} V_m \sin wt dt$$

$$= \frac{1}{\pi} V_m [\cos(0) - \cos(\pi)]$$

$$(V_d)_{avg} = \frac{2V_m}{\pi} = \frac{2\sqrt{2}V_s}{\pi}$$

- Avg. load current ( $I_d$ )<sub>avg.</sub> =  $\frac{(V_d)_{avg}}{R} = \frac{2V_m}{\pi R}$

$$(V_d)_{RMS} = \left[ \frac{1}{\pi} \int_0^{\pi} (V_m \sin wt)^2 dt \right]^{\frac{1}{2}} = V_s = \frac{V_m}{\sqrt{2}}$$


$$\text{RMS load current} = \frac{(V_d)_{RMS}}{R}$$

$$\text{Peak load current} = \frac{\sqrt{2}V_s}{R}$$

- DC power delivered to the load

$$P_{dc} = (V_d)_{avg} * (I_d)_{avg} = \frac{2\sqrt{2}V_s}{\pi} * \frac{2\sqrt{2}V_s}{\pi R}$$

$$= \frac{0.8113V_s^2}{R}$$

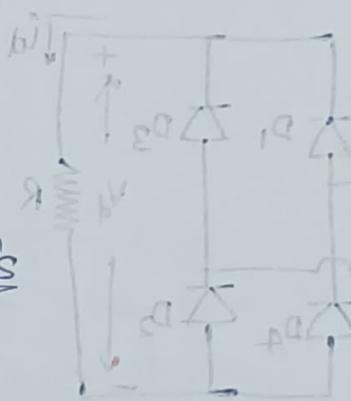

$$\text{Transformer utility factor} = \frac{P_{dc}}{(V_d)_{RMS} * (I_d)_{RMS}} = 81.13\%$$

$$\text{PIV of diode} = V_m = \sqrt{2}V_s$$



$$\text{Ripple factor} = \sqrt{\frac{(V_d)_{RMS}^2 - (V_d)_{avg}^2}{(V_d)_{avg}^2}}$$

$$= \sqrt{\left(\frac{V_m}{\sqrt{2}}\right)^2 - L^2}$$

$$= \sqrt{\frac{\pi^2}{8} - 1}$$

$$= 0.483 = 48.3\%$$

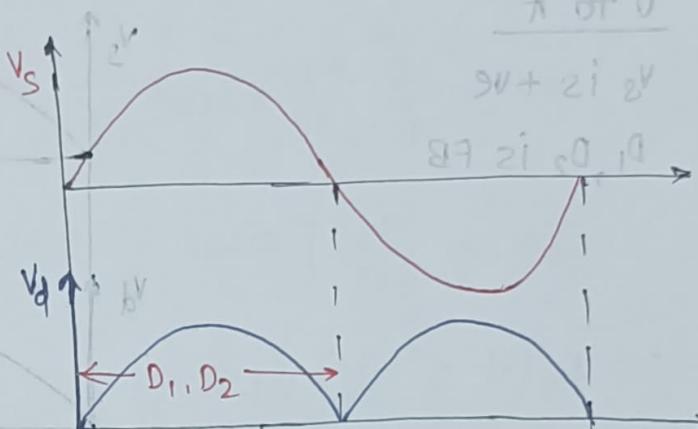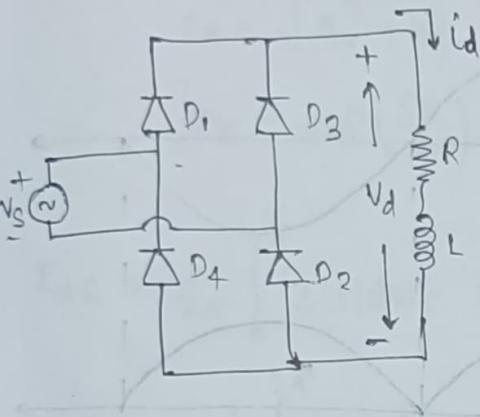② source inductance  $L_s = 0$ , R-L load ( $\omega = 100$ )



at  $t=0$

$V_s$  is +ve

$D_1, D_2$  FB

$V_d = V_s$

$$\begin{aligned} i_d(wt) &|_{t=0} = +I_0 \\ \frac{d i_d(wt)}{dt} @ t=0 &= \frac{R I_0}{L} \end{aligned}$$

$$R i_d(wt) + L \frac{d i_d(wt)}{dt} = \sqrt{2} V_s \sin wt$$

$$R I_0(s) + L s I_0(s) = \sqrt{2} V_s \left( \frac{w}{s^2 + w^2} \right)$$

$$I_0(s) [R + Ls] = \sqrt{2} V_s \left( \frac{w}{s^2 + w^2} \right)$$

$$I_0(s) = \sqrt{2} V_s \left( \frac{w}{s^2 + w^2} \right) \left( \frac{1}{R + Ls} \right)$$

$$I_0(t) = \frac{\sqrt{2} V_s}{|Z|} \sin(wt - \theta) + A_1 e^{-j\beta_L t} - \frac{E}{R}$$

$$@ t=0 \quad I_0(0) = I_0 \rightarrow A_1 = \left\{ I_0 + \frac{E}{R} - \frac{\sqrt{2} V_s \sin \theta}{|Z|} \right\} e^{(j\beta_L) \frac{\pi}{2}}$$

=


- $\pi$  to  $2\pi$
  - $V_S$  is -ve
  - $D_3, D_4$  is forward biased
  - $V_d = -V_S$

\*  $L_s = 0$  and Load is highly inductive so that  $I_d$  is constant at  $I_d$  ( $WL = R$ )

0 to  $\pi$


$V_S$  is +ve

$D_1, D_2$  is FB

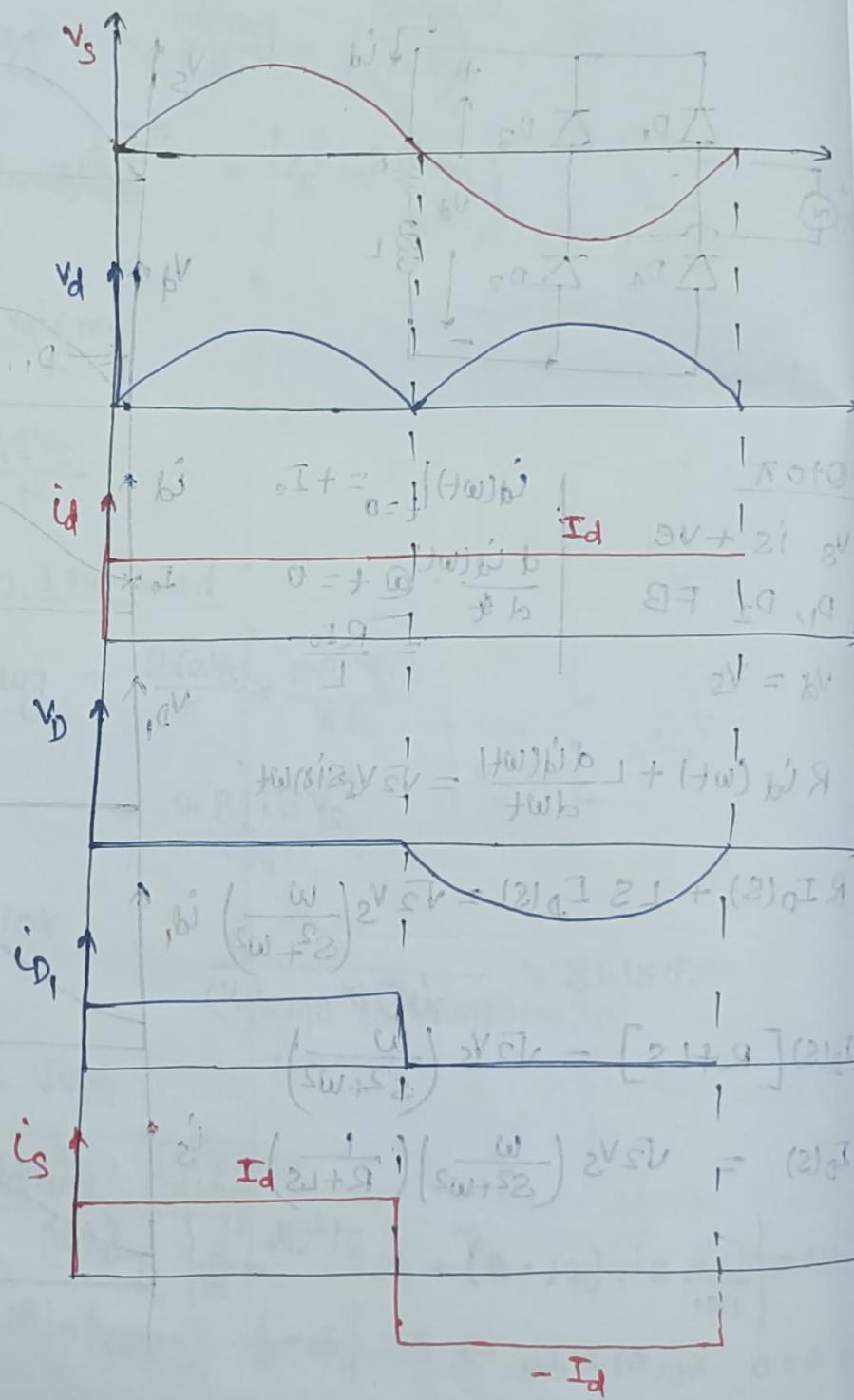

↪ Source inductance is zero, Hence transition from +ve to -ve value of source current is instantaneous.
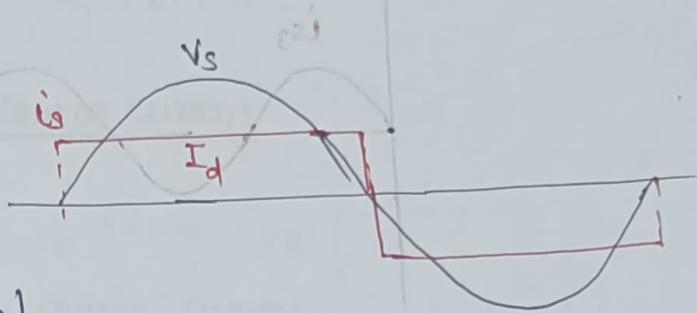
$$i_s(t) = I_{dc} + \sum_{n=1}^{\infty} a_n \cos(n\omega t) + b_n \sin(n\omega t)$$



$$= I_{dc} + C_n \sin(n\omega t - \phi_n)$$

$$C_n = \sqrt{a_n^2 + b_n^2}$$

$$\phi_n = \tan^{-1}\left(\frac{a_n}{b_n}\right)$$

$$I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i_s(t) d\omega t = 0$$

$$a_n = \frac{1}{\pi} \int_0^{2\pi} i_s(t) \cos(n\omega t) d\omega t = 0$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} i_s(t) \sin(n\omega t) d\omega t = \frac{1}{\pi} \int_0^{2\pi} (I_d) \cdot \sin(n\omega t) d\omega t$$


$$= \left( \frac{1}{\pi} \int_0^{2\pi} i_s(t) \right) \left[ \cos(0) - \cos(2n\pi) \right] = 2I_d$$

$$= \frac{2I_d}{\pi} [1 - \cos(2n\pi)] = \frac{2I_d}{\pi} = 2I$$

$$b_n = \frac{2I_d}{n\pi} [1 - \cos n\pi]$$

$$b_n = \frac{4I_d}{n\pi} \quad \text{for } n=1, 3, 5, 7$$

$$= 0 \quad \text{for } n=2, 4, 6, 8$$

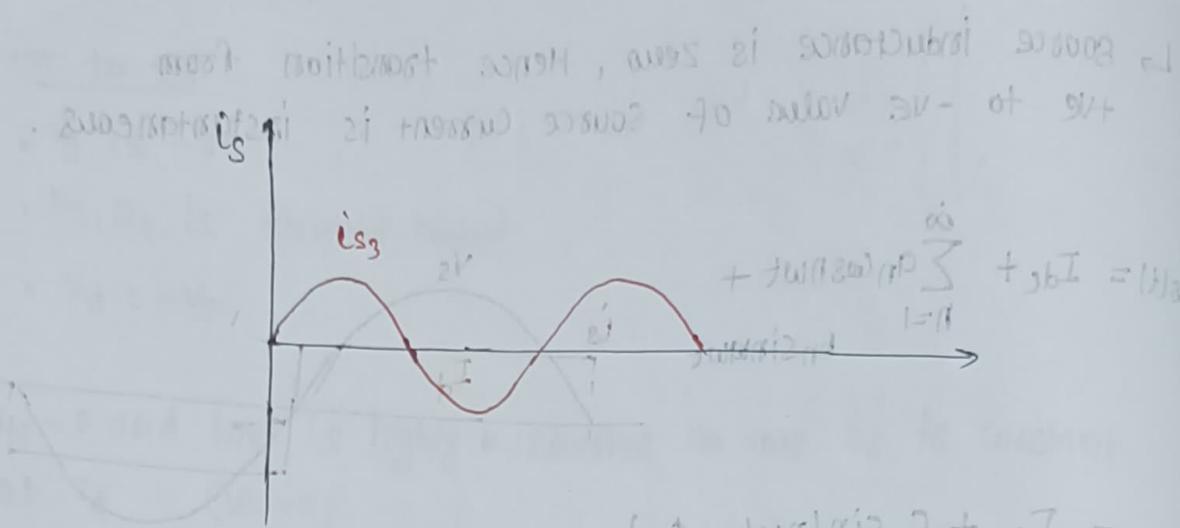

$$i_s(t) = \sum_{n=1}^{\infty} \frac{4I_d}{n\pi} \sin(n\omega t) : n=1, 3, 5, \dots$$

$\frac{4I_d}{\pi} = I_d$   
 $\left(\frac{4I_d}{n\pi}\right) \frac{1}{n} = \frac{4I_d}{n\pi}$

$$i_s(t) = \frac{4I_d}{\pi} \left[ \sin\omega t + \frac{\sin 3\omega t}{3} + \frac{\sin 5\omega t}{5} + \dots \right]$$

$$i_{s_1}(t) = \frac{4I_d}{\pi} \sin\omega t$$

$$i_{s_3}(t) = \frac{4I_d}{3\pi} \sin 3\omega t$$

$$i_{s_5}(t) = \frac{4I_d}{5\pi} \sin 5\omega t.$$

↳ RMS value of fundamental component of

$$\text{i/p current } i_{s_1} = \sqrt{\frac{1}{T} \int_0^T i_{s_1}^2(t) dt} = \sqrt{\frac{1}{T} \int_0^T \left(\frac{4I_d}{\pi} \sin\omega t\right)^2 dt} = \frac{4I_d}{\pi\sqrt{2}}$$

$$i_{s_1} = \frac{4I_d}{\pi\sqrt{2}} = 0.9 I_d$$

$$i_{s_3} = \frac{4I_d}{3\pi\sqrt{2}} = 0.3 I_d$$

$$i_{s_5} = \frac{4I_d}{5\pi\sqrt{2}} = 0.18 I_d$$

↳ RMS values of nth harmonic of source current  $i_{s_n}$

$$i_{s_n} = \begin{cases} 0 & \text{for even values of } n \\ \frac{4I_d}{n\pi} & \text{for odd values of } n \end{cases}$$

↳ RMS value of total source current  $i_s = I_d$

\* Total harmonic distortion (THD)

$$THD = \sqrt{\frac{(I_d^2 - I_s^2)}{I_s^2}} = 48.4\%$$


\* Displacement factor of source current

$$DF = \cos\phi_1 = 1$$

$$+ (\phi - \omega t) \text{ rad} = 180^\circ$$

\* Harmonic components of source current
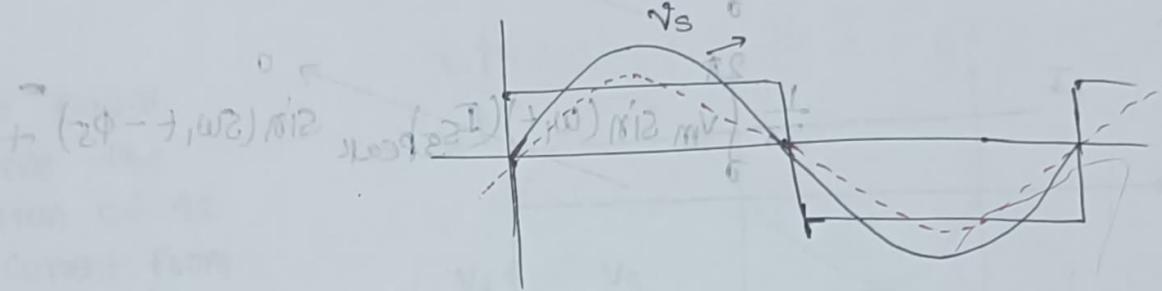
$$+ (\phi - \omega t) \text{ rad} = 180^\circ$$



$$\phi_{202} \cdot 2I \cdot 2V = 12000 \text{ ampere}$$

$$2I \cdot 2V = 12000 \text{ ampere}$$

$$\phi_{202} \cdot 2I \cdot 2V = 12000 \text{ ampere}$$

\* AC source side power factor

$$= \frac{\text{Actual power}}{\text{Apparent power}}$$

$$= \frac{V_S I_S \cos\phi}{V_S I_S}$$

$$\text{Actual power} = \frac{1}{2\pi} \int_0^{2\pi} V_S I_S = \frac{1}{2\pi} \left[ \int_0^{2\pi} V_m \sin\omega t [I_1 + I_3 + \dots] \right]$$

$$\begin{aligned}
 &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega_1 t) \left[ (I_{S1})_{\text{peak}} \sin(\omega_1 t - \phi_1) + \right. \\
 &\quad \left. (I_{S3})_{\text{peak}} \sin(3\omega_1 t - \phi_3) + \right. \\
 &\quad \left. (I_{S5})_{\text{peak}} \sin(5\omega_1 t - \phi_5) + \right] \\
 &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega_1 t) (I_{S1})_{\text{peak}} \sin(\omega_1 t - \phi_1) + \\
 &\quad \cancel{\frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega_1 t) (I_{S3})_{\text{peak}} \sin(3\omega_1 t - \phi_3)} + \\
 &\quad \cancel{\frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega_1 t) (I_{S5})_{\text{peak}} \sin(5\omega_1 t - \phi_5)} + \\
 &= \frac{V_m}{\sqrt{2}} \cdot \frac{I_{S1}}{\sqrt{2}} \cos \phi_1
 \end{aligned}$$

Actual power =  $V_S \cdot I_{S1} \cdot \cos \phi_1$

Apparent power =  $V_S I_S$

$\therefore$  Power factor =  $\frac{\sqrt{2} I_{S1} \cos \phi_1}{\sqrt{2} I_S}$

$$\text{Power factor} = \frac{I_{S1}}{I_S} = \frac{2\sqrt{2} I_d}{\pi I_d} = \frac{0.9}{\pi}$$


\* Peak current rating of diode =  $I_d$

\* RMS current Rating of diode =  $\left(\frac{I_d}{\sqrt{2}}\right)$

\*  $P_{IN}$  of diode =  $V_m \cdot$

## \* Effect of source inductance:-

11/09/23

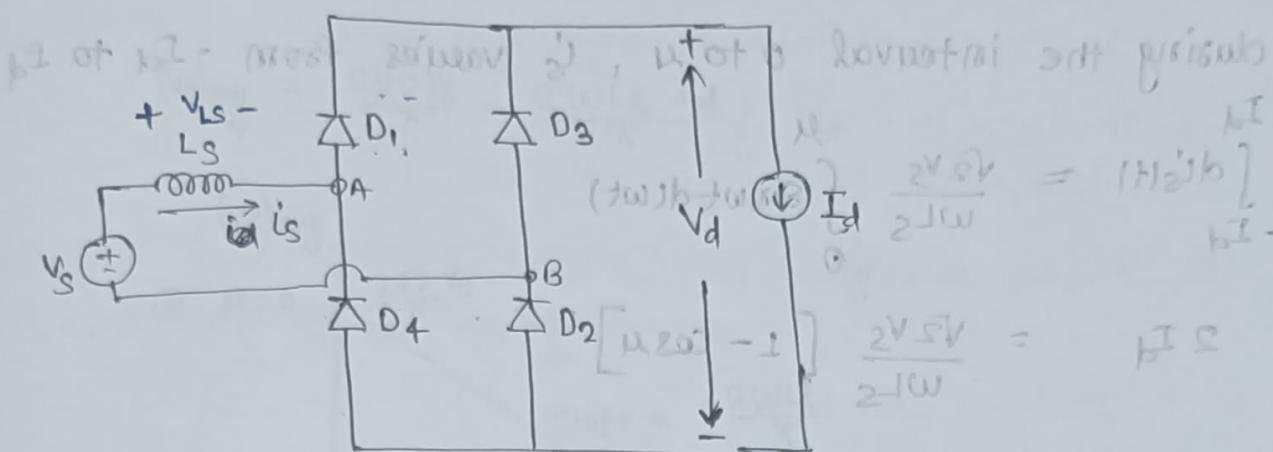

→ due to source inductance the transition of ac side current from  $+I_d$  to  $-I_d$  is not instantaneous.

→ A finite interval is required for the transition of current from outgoing diodes to incoming diodes.

→ During commutation interval  $\mu$ , all four diodes conduct.


$$v_d = 0$$

Drop in the inductance

$$v_{ls} = +v_s$$

$$L_s \cdot \frac{di_s(t)}{dt} = \sqrt{2} v_s \sin \omega t$$
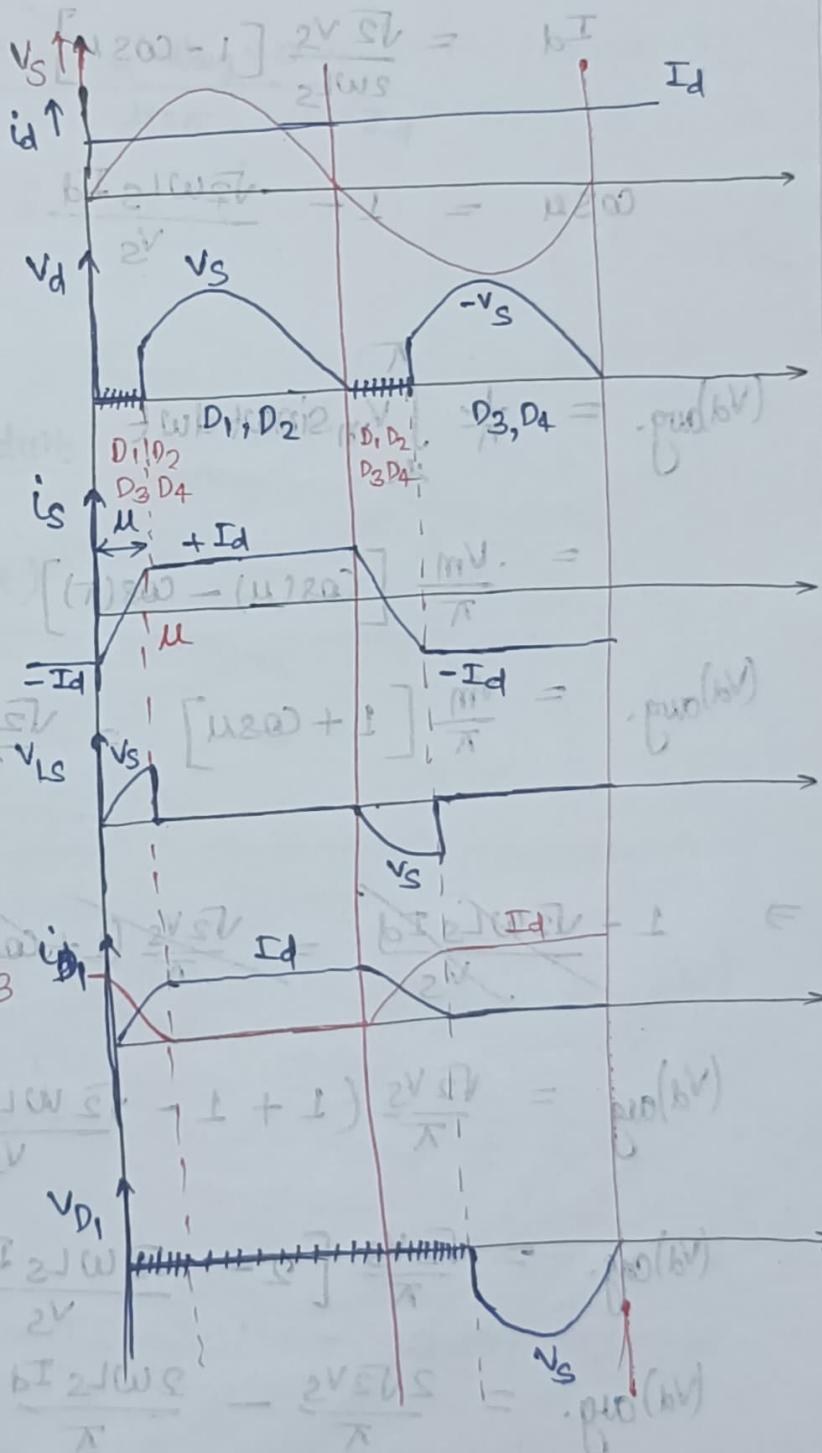
$$W L_s \frac{di_s(t)}{d\omega t} = \sqrt{2} v_s \sin \omega t$$



$$dis(t) = \frac{\sqrt{2}V_s}{wL_s} \sin \omega t dt$$

during the interval 0 to  $\mu$ ,  $t$ 's values from  $-\omega t_0$  to  $\omega t_0$

$I_d$

$$\int_{-I_d}^{I_d} dis(t) = \frac{\sqrt{2}V_s}{wL_s} \int_0^{\mu} \sin \omega t d(\omega t)$$

$$2 I_d = \frac{\sqrt{2}V_s}{wL_s} [1 - \cos \mu]$$

$I_d$

$$= \frac{\sqrt{2}V_s}{2wL_s} [1 - \cos \mu]$$

$$\cos \mu = 1 - \frac{\sqrt{2}wL_s I_d}{V_s}$$

$$(V_d)_{avg.} = \frac{1}{\pi} \int_0^{\mu} V_m \sin \omega t dt$$

$$= \frac{V_m}{\pi} [\cos(0) - \cos(\mu)]$$

$$(V_d)_{avg.} = \frac{V_m}{\pi} [1 + \cos \mu] \Rightarrow \frac{\sqrt{2}V_s}{\pi} (1 + \cos \mu)$$

$\Rightarrow$

~~$$1 - \frac{\sqrt{2}wL_s I_d}{V_s} = \frac{\sqrt{2}V_s}{\pi} (1 + \cos \mu)$$~~

$$(V_d)_{avg.} = \frac{\sqrt{2}V_s}{\pi} \left( 1 + 1 - \frac{\sqrt{2}wL_s I_d}{V_s} \right)$$

$$(V_d)_{avg.} = \frac{\sqrt{2}V_s}{\pi} \left[ 2 - \frac{\sqrt{2}wL_s I_d}{V_s} \right]$$

$$(V_d)_{avg.} = \frac{2\sqrt{2}V_s}{\pi} - \frac{2wL_s I_d}{\pi}$$

So o/p voltage is reduced by  $\frac{2wLs Id}{\pi}$

so o/p voltage is  $V_o = V_s - \frac{2wLs Id}{\pi}$

Ans To find load current  $I_d$

$$(V_d)_{avg} = \frac{2\sqrt{2}V_s}{\pi} - \frac{2wLs Id}{\pi}$$

$(V_d)_{avg}$

@  $\mu=0$

$$\frac{2\sqrt{2}V_s}{\pi}$$

$$\text{Slope} = -\frac{2wLs}{\pi} \text{ b/w } +0.9$$

$$V_o = 0 \text{ when } (V_d)_{avg} = 0 \text{ at } \mu = \pi$$

during ' $\mu$ '

$$V_{LS} = Ls \frac{dI_s}{dt} = \sqrt{2}V_s \sin \omega t$$

$$dI_s = \frac{\sqrt{2}V_s}{wLs} \sin \omega t d\omega t$$

$$I_s = \frac{\sqrt{2}V_s}{wLs} (-\cos \omega t)$$

$$\frac{2\sqrt{2}V_s}{\pi} = P_o (bV)$$

$$V_o = \frac{0.51 \times 2V}{\pi} =$$

$$A_o1 = (b^2)$$


$$A_o2 = 20.0801 = 20.0801$$

Ques ① A single phase uncontrolled bridge rectifier connected to a 120V ac source applies a constant load current of 10A.

- (a) If  $L_s = 0$ , find avg. output voltage and avg. output power. plot  $V_d$  and  $i_s$ .
- (b) If  $L_s = 0.7\text{mH}$ , find avg. output voltage and avg. output power and overlap angle. Plot  $V_d$  and  $i_s$ .

② Repeat the above question if i/p ac source is of square wave with an amplitude of 200V.

Sol:-

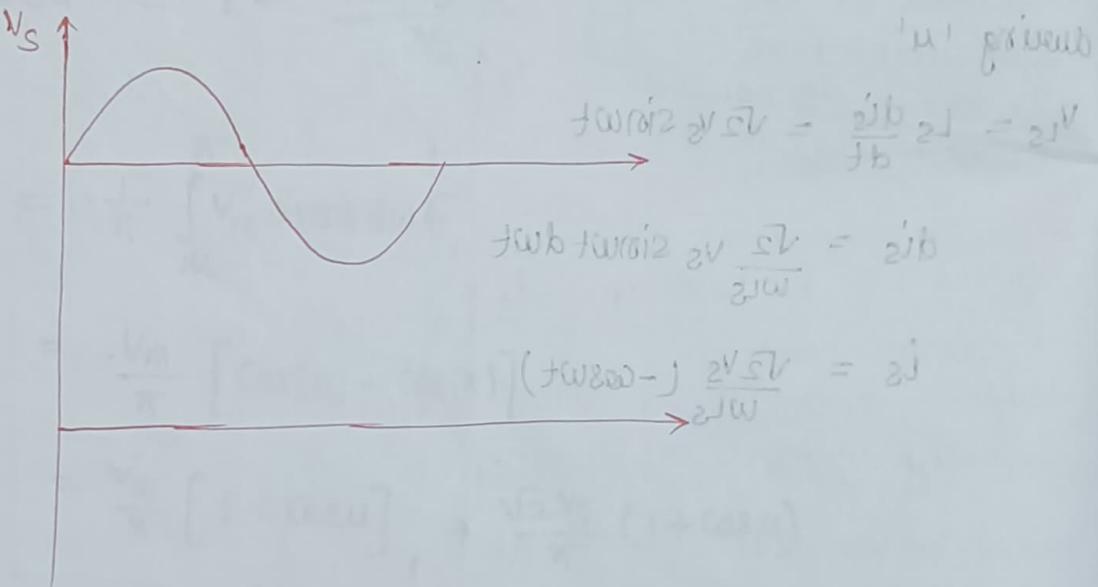

$$(V_d)_{\text{avg.}} = \frac{2\sqrt{2}V_S}{\pi}$$

$$= \frac{2\sqrt{2} \times 120}{\pi} = 108.037 \text{ V.}$$

$$(I_d) = 10 \text{ A}$$

$$\text{avg. o/p power} = 1080.37 \text{ Watts.}$$

(b) For  $L_s = 5mH$

$$(N_d)_{avg} = \frac{2\sqrt{2}V_c}{\pi} - \frac{2\pi f L_s I_d}{\pi}$$
$$= 108.037 - \frac{2\pi \times 2\pi \times 50 \times 5 \times 10^{-3} \times 10}{\pi}$$
$$= 108.037 V \quad 98.037 V$$

~~cos u~~ =

$$(P_o)_{avg} = \cancel{9830.37 \text{ watts}} \quad 983.037 \text{ watts}$$


$$\cos u = 1 - \frac{\sqrt{2} w L_s I_d}{V_s}$$

$$= 1 - \frac{\sqrt{2} \times (2\pi f) \times 5 \times 10^{-3} \times 10}{120}$$

$$u = 35.5^\circ$$

② set

② Soln:-

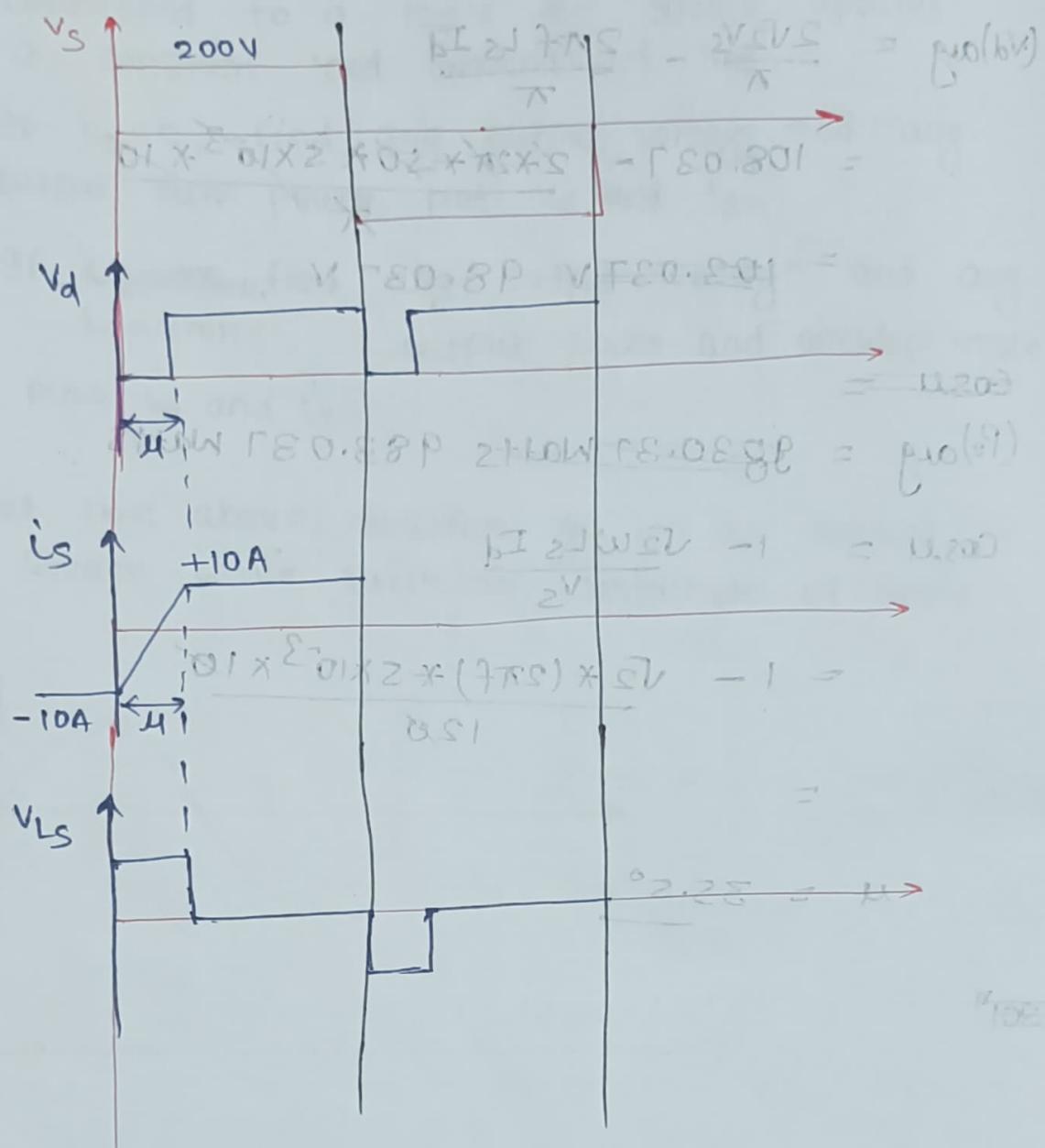

a) Without source inductance.

$$(V_d)_{avg.} = \underline{200V}$$

$$(P_d)_{avg.} = \underline{2000 \text{ Watts}}$$

b) With source inductance

$$\cos \phi = 1 - \frac{\sqrt{2}WLs I_d}{Vs}$$

$$= 1 - \frac{\sqrt{2} \times (2\pi f) \times 50 \times 10^{-3} \times 10}{200}$$

$$\mu = 27.26^\circ$$

$$(V_d)_{avg} = \frac{(180^\circ - 27.26^\circ)}{180^\circ} \times 200$$

$$= 533.1631 \text{ V} \quad 169.711^\circ$$

$$L \frac{dis}{dt} = 200$$

$$dis = \frac{200}{\omega L} dt$$

$$\int_{-10}^{10} dis = \frac{200}{\omega L} [t]_0^4$$

$$= \frac{200 \cdot 10}{\pi f \times 5 \times 10^{-3}} \times 4$$

$$\mu = \pi \times 50 \times 10^{-3} = 0.157 \text{ rad}$$

$$(V_d)_{avg} = \frac{1}{\pi} \int_{90^\circ}^{180^\circ} 200V$$

$$= \frac{200}{\pi} [180^\circ - 90^\circ]$$

$$= \frac{200}{\pi} (90^\circ)$$

$$= \frac{200}{\pi} \times \frac{\pi}{180} \times 180 = 190 \text{ Volt}$$

$$(P_d)_{avg} = 1900 \text{ Watts.}$$

$$\frac{10}{3} \text{ A} \times 2V = 20V$$



Series circuit

$$j + j = 2j$$
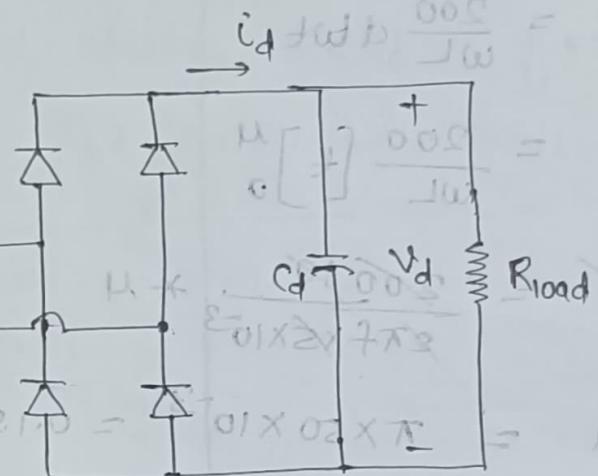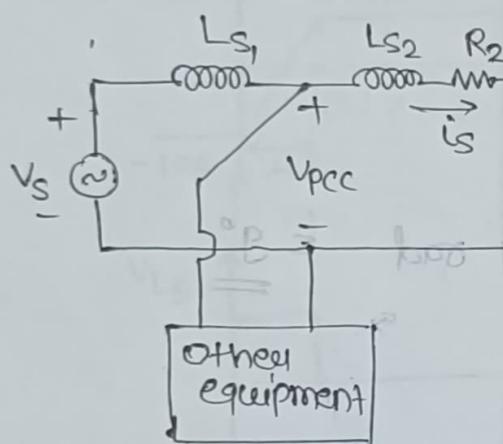
## ~~# 3.0 diode rectified circuits :-~~

\* Effect of diode-Rectified on utility voltage and current:

- Line current distortion: Source current deviates significantly from the sinusoidal waveform.



$L_s$   $\rightarrow$  inductance of the utility side.

$L_{s2}$   $\rightarrow$  " due to the power elec. equipments.

$R_s$   $\rightarrow$  diode Resistance.

PCC  $\rightarrow$  Point of common coupling where other load & PE loads are connected

$V_{pcc}$   $\rightarrow$  Voltage across the

$$V_{pcc} = V_s - L_{s1} \cdot \frac{di_s}{dt}$$

Source current is

$$i_s = i_{s1} + \sum_{h=3,5,\dots}^{\infty} i_{sh}$$

$$V_{PCC} = V_s - L_{S1} \underbrace{\frac{di_{S1}}{dt}}_{\text{due to harmonics}} - L_{S1} \sum_{h=3,5,\dots}^{\infty} \frac{dih}{dt}$$

$$V_{PCC} = V_{PCC1} - L_{S1} \sum_{h=3,5,\dots}^{\infty} \frac{dih}{dt} \quad V_{PCC1} = V_s - L_{S1} \frac{di's_1}{dt}$$

↳ Distortion in voltage at PCC due to harmonics in line current

$$V_{PCC\text{dis.}} = L_{S1} \sum_{h=3,5,\dots}^{\infty} \frac{dih}{dt}$$

↳ Voltage available at the point of common coupling is highly deviated from the ideal sine waveform.

↳ This is referred to voltage pollution in power system

↳ This is one of the reasons of power quality problems.

### \* EFFECT OF SINGLE PHASE RECTIFIERS


on the neutral current in

3-Φ - 4 Wire Systems :-

↳ When all the 3-phases are loaded equally (or) balanced neutral current  $i_n = 0$

↳ When 1-Φ rectifiers are connected to as load to 3Φ,  $i_n \neq 0$

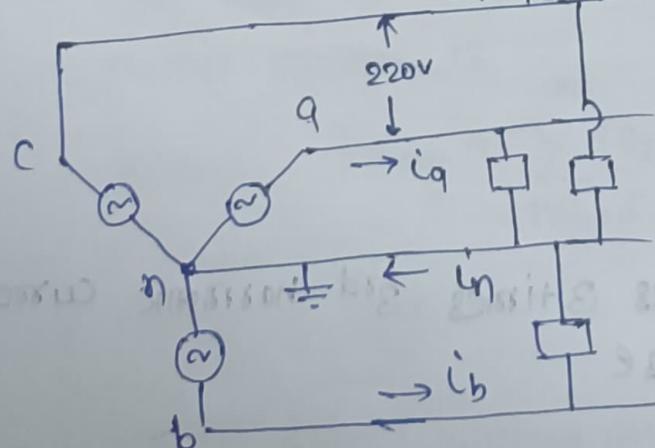↳ Consider identical rectifiers connected between each phases and neutral (balanced load condn.)



$$i_a + i_b + i_c = 0$$

$$i_n = i_a + i_b + i_c$$

• Phase a current

$$i_a = i_{a_1} + \sum_{n=2k+1}^{\infty} i_{an} \quad K=1, 2, 3, \dots$$

$$i_a = \sqrt{2} I_{s_1} \sin(\omega t - \phi_1) + \sum_{n=2k+1}^{\infty} \sqrt{2} I_{sn} \sin(n\omega t - \phi_n)$$

(iii) Connection of sub 329 to 3phov 31 Reductio

Sy

$$i_b = \sqrt{2} I_{s_1} \sin(\omega t - \phi_1 - 120^\circ) + \sum_{n=2k+1}^{\infty} \sqrt{2} I_{sn} \sin(n\omega t - \phi_n - 120^\circ)$$

$$i_c = \sqrt{2} I_{s_1} \sin(\omega t - \phi_1 + 240^\circ) + \sum_{n=2k+1}^{\infty} \sqrt{2} I_{sn} \sin(n\omega t - \phi_n + 240^\circ)$$

• Neutral Current

$$i_N = i_a + i_b + i_c$$

$$= i_{a_1} + \sum_{n=2k+1}^{\infty} i_{an} + i_{b_1} + \sum_{n=2k+1}^{\infty} i_{bn} + i_{c_1} + \sum_{n=2k+1}^{\infty} i_{cn}$$

∴ sum of the 3-ph fundamental components and non- $\omega$  triplen harmonics is zero.

$$i_{a_1} + i_{b_1} + i_{c_1} = 0$$


$$\Rightarrow i_N = i_{a_3} + i_{a_{15}} + \dots + i_{b_3} + i_{b_{15}} + \dots + i_{c_3} + i_{c_{15}}$$

Neglecting all the higher order harmonics

$$i_N = i_{a_3} + i_{b_3} + i_{c_3}$$

$$i_N = 3i_{a_3} \approx i_a$$

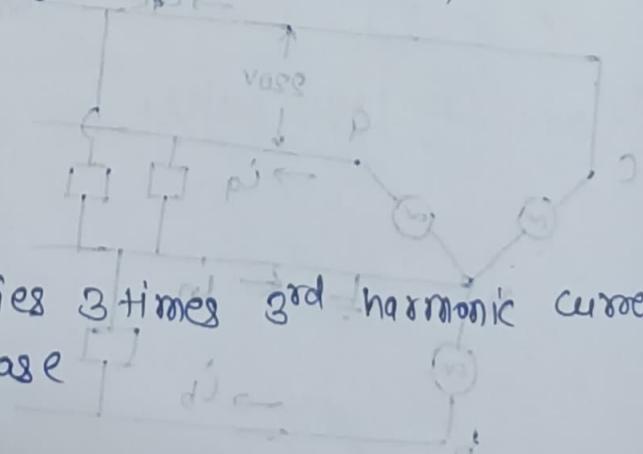↳ Thus neutral wire carries 3 times 3rd harmonic current flowing through a phase



↳ Neutral current is almost equal to or greater than the fundamental line current.

## # Rectifier circuit design :-


↳ Determination of the rating of semiconductor devices

- avg current, rms current, Peak current and PIV.

↳ Design of filters at the output (dc side) to remove voltage harmonics. These are called dc filters.

They are — L, c. and LC type.

### DC - Filters

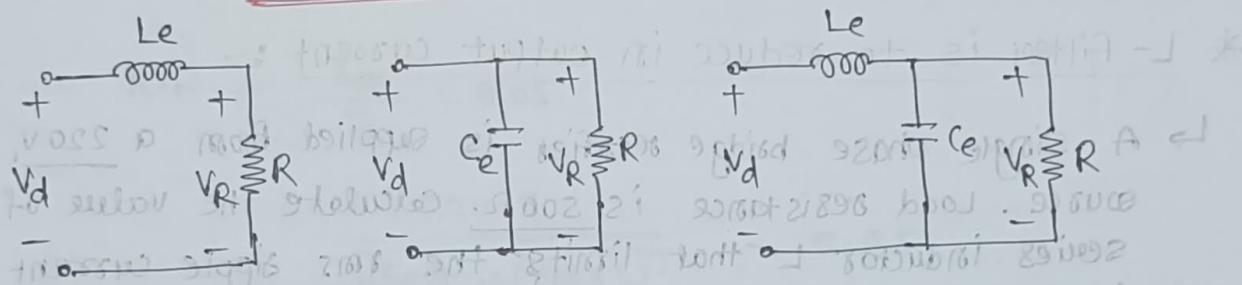

↳ Design of filters at the input (ac side) to remove current harmonics.

These filters are called as ac filters and are usually of LC type.

### DC Filters :-

↳ To design a dc filtered circuit, knowledge of the magnitude and frequency of harmonics at the dc side is required.


⇒ Output voltage is

$$V_d(\omega t) = (V_d)_{avg} + \sum_{n=1,3,5}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

$$\therefore (V_d)_{avg.} = \frac{2V_m}{\pi}$$

$$a_n = \frac{1}{(\pi/2)} \int_0^{\pi} V_m \sin \omega t \cos n\omega t dt = \frac{4V_m}{\pi} \sum_{n=2,4,6,\dots}^{\infty} \frac{(-1)^{(n-1)}}{(n-1)(n+1)}$$
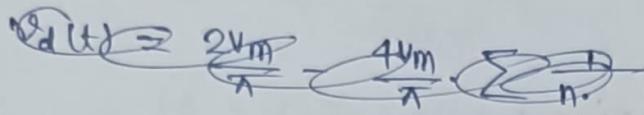
$$b_n = \frac{2}{\pi} \int_0^{\pi} v_m \sin \omega t \cdot \sin n \omega t d\omega t = 0$$





$$V_d(t) = \frac{2v_m}{\pi} - \frac{4v_m}{3\pi} \cos 2\omega t - \frac{4v_m}{15\pi} \cos 4\omega t - \frac{4v_m}{35\pi} \cos 6\omega t$$

↳ Output voltage of the full wave rectifier containing only even harmonics.

↳ Second harmonics at 100 Hz is most dominant.

\* L-Filter is to reduce ripples in output current :-

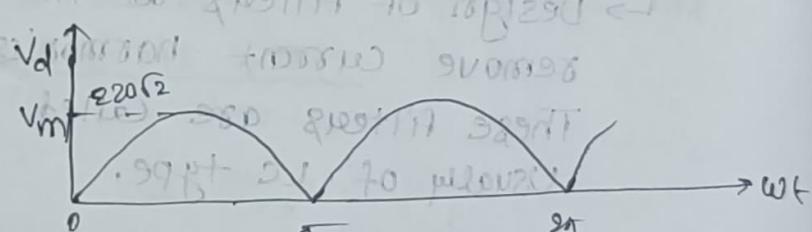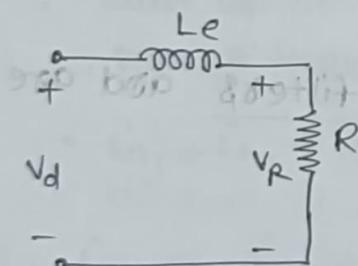↳ A single phase bridge rectifier is supplied from a 220V, 50Hz source. Load resistance is 500Ω. Calculate the value of series inductor L that limits the rms ripple current to be less than 5% of  $I_{DC}$ .



$$V_d(t) = \frac{2v_m}{\pi R} - \frac{4v_m}{3\pi} \cos 2\omega t - \frac{4v_m}{15\pi} \cos 4\omega t - \frac{4v_m}{35\pi} \cos 6\omega t - \dots$$

$$i_d(t) = \frac{2v_m}{\pi R} - \frac{4v_m}{3\pi} \cos 2\omega t - \frac{4v_m}{15\pi} \cos 4\omega t - \frac{4v_m}{35\pi} \cos 6\omega t$$

$$( \text{normalized} + \sqrt{R^2 + (\omega WL)^2} \tan(\frac{\omega WL}{R}) )$$

$$= \frac{2v_m}{\pi R} - \frac{4v_m}{\pi \sqrt{R^2 + (\omega WL)^2}} \left[ \frac{1}{3} \cos(2\omega t + \theta_2) + \frac{1}{15} \cos(4\omega t - \theta_4) + \dots \right]$$

$$\theta = \tan^{-1} \left( \frac{\omega WL}{R} \right)$$

- DC value of output current

$$I_{dc} = \frac{2Vm}{\pi R}$$

- Rms value of Ripple current

$$I_{ac}^2 = \frac{(4Vm)^2}{2\pi^2(R^2 + (2\omega L)^2)} \left(\frac{1}{3}\right)^2 + \frac{(4Vm)^2}{2\pi^2(R^2 + (4\omega L)^2)} \left(\frac{1}{15}\right)^2 + \dots$$

Neglecting all harmonics other than predominant second harmonic

$$I_{ac}^2 = \frac{(4Vm)^2}{2\pi^2(R^2 + (2\omega L)^2)} \left(\frac{1}{3}\right)^2$$

$$R.F. = \frac{I_{ac}}{I_{dc}} = 0.05$$

$$= \frac{93.37089}{\sqrt{(500)^2 + (200\pi L)^2}} = 0.05$$

$$\Rightarrow \frac{93.37089}{\sqrt{(500)^2 + (200\pi L)^2}} = 0.019805$$




$$(500)^2 + (200\pi L)^2 = (4714.51)^2$$

$$200\pi L = 4687.92$$


$$L = 7.4629 \text{ H}$$

$$L \approx 7.5 \text{ H}$$

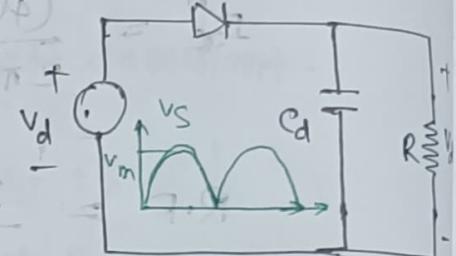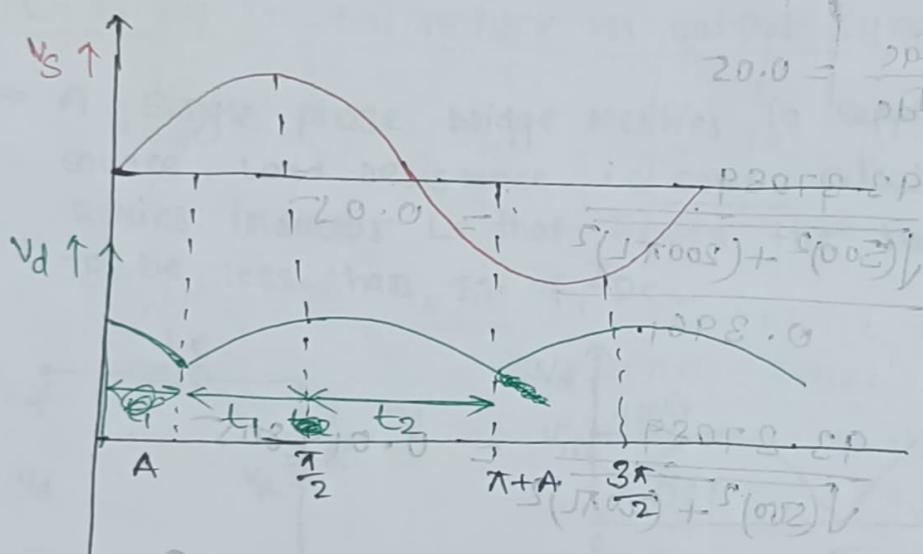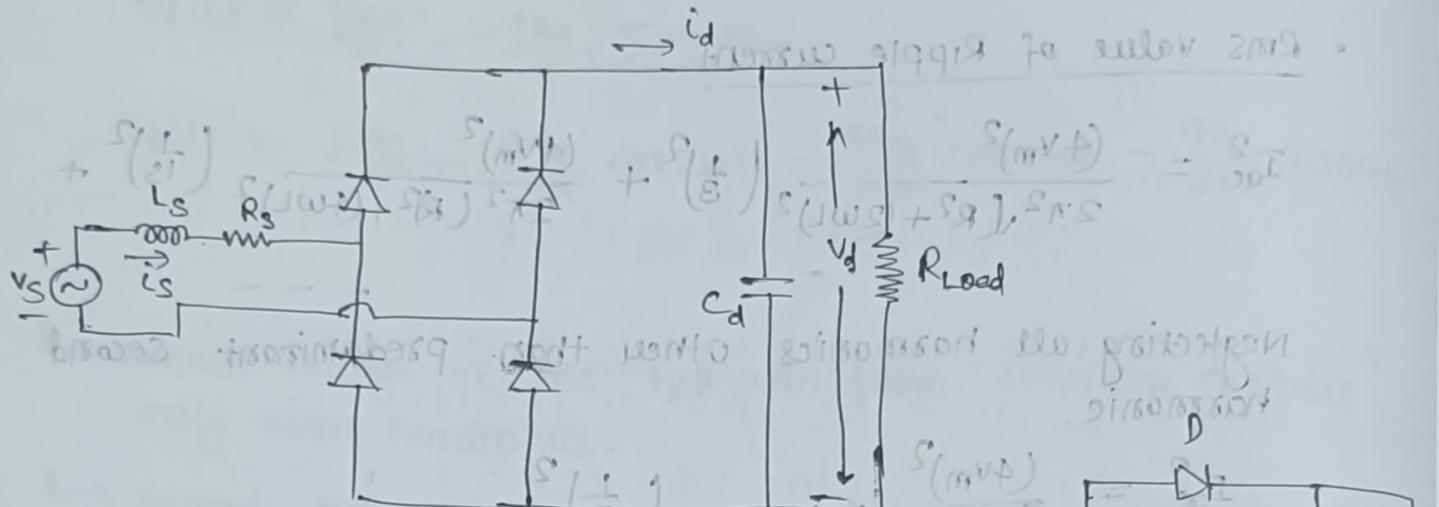
\* Diode bridge rectifier with a capacitor filter to limit the amount of output voltage ripple:-



① Ckt. model.

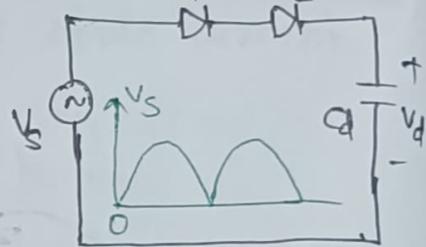


discharging

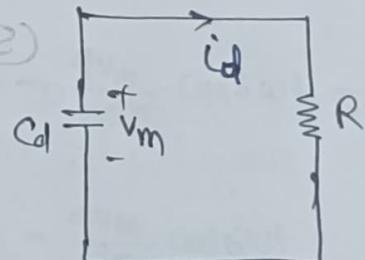

discharging

$$H2 \cdot T \approx 1$$

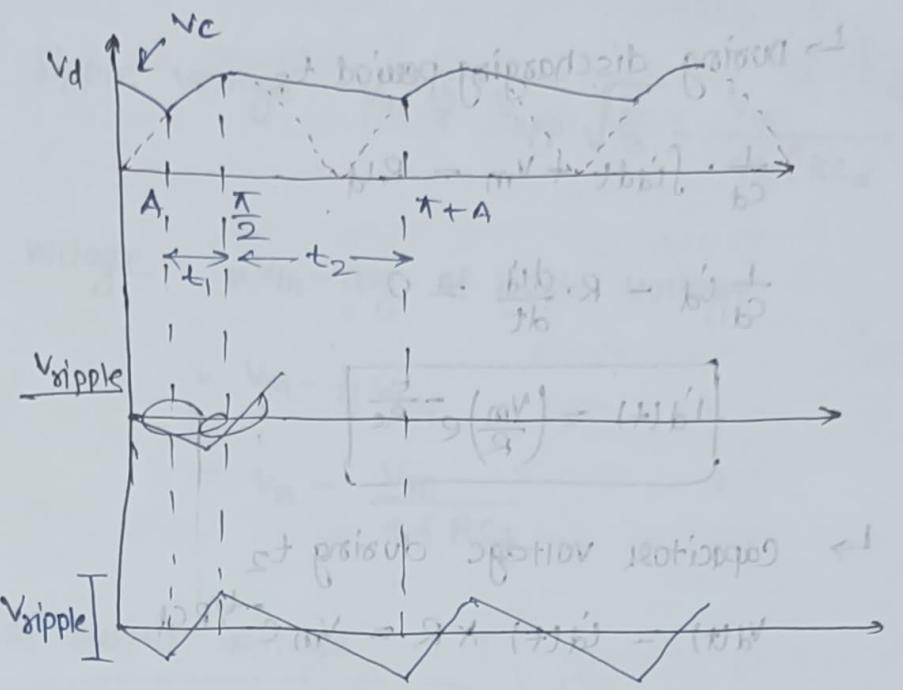

$\Rightarrow v = \sin(\omega t)$  is the waveform for full wave rectifier.

- $0 \rightarrow A$   
 $v_s < v_d$  all diodes are off  $\Rightarrow$  capacitor discharge to load  $R$ .  
load current  $i_o = \frac{v_c}{R}$ ,  $v_d = v_c$
  - $A \rightarrow \frac{\pi}{2}$ ,  $v_s > v_c$   
 $\boxed{\text{diodes } D_1 \text{ and } D_2 \text{ conduct (during } t_1\text{)}}$   
 $v_d = v_c = v_s$   
Capacitor gets charged to  $v_m$ .
  - $\frac{\pi}{2} \rightarrow \pi + A$   $v_s < v_c$   $(\frac{T}{2}) \approx t_2$   
all diodes are off (during  $t_2$ )  
capacitor discharges to load  $R$ .  
 $v_d = v_c$ ,  $i_d = \frac{v_c}{R}$
  - $\pi + A \rightarrow \frac{3\pi}{2}$ ,  $-v_s < v_c$ : capacitor gets charge to  $v_m$ .

↳ During discharging period  $t_2$

$$\frac{1}{C_d} \cdot \int i_d dt + V_m = R i_d$$

$$\frac{1}{C_d} i_d - R \cdot \frac{di_d}{dt} = 0$$

$$i_d(t) = \left( \frac{V_m}{R} \right) e^{-\frac{t}{RC_d}}$$

↳ Capacitor voltage during  $t_2$

$$V_d(t) = i_d(t) \times R = V_m e^{-\frac{t}{RC_d}}$$

maximum capacitor/load voltage to  $V_m$ .

$$\text{minimum capacitor/load voltage } (V_d)_{\min} = V_m e^{-\frac{t_2}{RC_d}}$$

↳ Peak to peak ripple voltage

$$V_{pp} = V_m - V_{d\min} = V_m - V_m e^{-\frac{t_2}{RC_d}}$$

$$= V_m \left( 1 - e^{-\frac{t_2}{RC_d}} \right)$$

$$(1^{\text{st}} \text{ point}) \approx V_m \left[ 1 - \left( 1 - \frac{t_2}{RC_d} \right) \right] \quad \text{When } RC_d > t_2$$

If  $C_d$  is selected as very large then  $t_1$  is very small as compare to  $t_2$ .

$$\text{so } t_2 \approx \left( \frac{T}{2} \right)$$

$$\text{so; } V_{pp} = \frac{V_m T}{2(R C_d)} = \left( \frac{V_m}{2f R C_d} \right) V$$

All of points & steps covered;  $\Delta V > \Delta V_-$ ,  $\frac{\Delta V}{2} < \Delta V$  at  $A + R$ .

$$\frac{\Delta V}{2} = bV, \Delta V = bV$$

• RMS value of ripple voltage  $V_{\text{ac}} \Rightarrow V_{\text{rpp}} \cdot \sqrt{\frac{2}{3}} = \frac{V_m}{\sqrt{6} f R C_d}$

Avg. load voltage =  $V_m - \text{avg. of ripple voltage}$

$$= V_m - \frac{1}{2} V_{\text{rpp}}$$

$$= V_m - \frac{V_m}{4 f R C_d}$$

14/07/23

↳ Ripple factor of output voltage

$$\boxed{RF = \frac{\text{RMS of Ripple voltage}}{\text{Avg. output voltage}}}$$

$$= \frac{V_m \left( \frac{1}{\sqrt{6} f R C_d} \right)}{V_m \left( 1 - \frac{1}{4 f R C_d} \right)}$$

$$= \frac{1}{\sqrt{6} f R C_d} \times \frac{4 f R C_d}{(4 f R C_d - 1)}$$

$$= \frac{4}{\sqrt{6}} \left( \frac{1}{4 f R C_d - 1} \right)$$

$$\boxed{RF = 2 \sqrt{\frac{2}{3}} \frac{1}{(4 f R C_d - 1)}}$$

- $C_d$  is selected such that RF is within the permissible limit.

$$\boxed{C_d = \frac{1}{4 f R} \left[ 1 + \frac{2 \sqrt{\frac{2}{3}}}{R \cdot F.} \right]}$$

Ques A 1-φ bridge rectifier supplied from a 220V, 50Hz source. The load resistance is  $R = 500\Omega$ . Design a C-filter so that Ripple factor of the o/p voltage is less than 5%.

Soln

$$V_m = 220\sqrt{2}$$

$$f = 50 \text{ Hz}$$

$$R = 500\Omega$$

$$R.F. = 0.05$$

$$C_d = \frac{1}{4fR} \left[ 1 + \frac{2\sqrt{\frac{2}{3}}}{R.F.} \right]$$

$$= \frac{1}{4 \times 50 \times 500} \left[ 1 + \frac{2\sqrt{\frac{2}{3}}}{0.05} \right]$$

$$= 0.0003365 \text{ F}$$

$$= 33.6 \mu\text{F}$$


$$\frac{1}{(1+R.F.)} = \frac{1}{(1+0.05)}$$

$$\frac{1}{(1+R.F.)} = \frac{1}{(1+0.05)}$$

$$\frac{1}{(1+R.F.)} = \frac{1}{(1+0.05)}$$

$$\left[ \frac{1}{7.7} + 1 \right] = 0.05$$
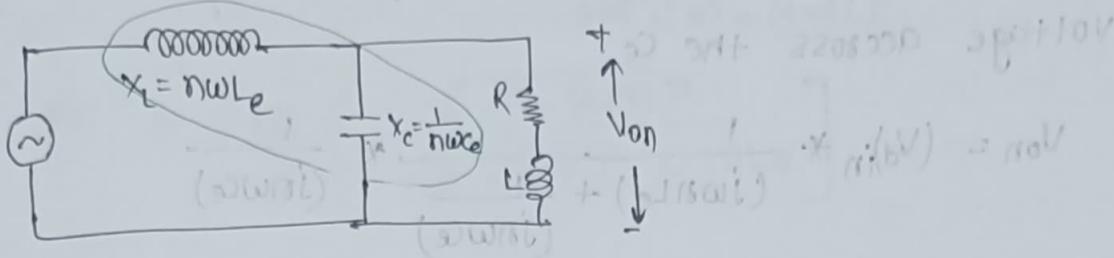
## \* LC Filter to limit the output ripple :-



Rectified Output

$$V_d(wt) = \frac{2V_m}{\pi} - \frac{4V_m}{3\pi} \cos 2wt - \frac{4V_m}{15\pi} \cos 4wt - \frac{4V_m}{35\pi} \cos 6wt - \dots$$

- For  $n$ th harmonic to pass through the capacitor,
- the capacitance impedance must be much smaller than that of the load.

$$\sqrt{R^2 + (nwl)^2} \gg \frac{1}{nwC}$$

$$\left[ \frac{50}{(100)} \frac{1}{3} \right] = 50/3 = 16.7 \text{ V}$$

This condition is satisfied

When the most dominant second harmonic,

$$\sqrt{R^2 + (2wl)^2} = \frac{100}{2wC} = 50 \text{ V} = 50/3 = 16.7 \text{ V}$$

- $C_e$  is selected such that this condition is satisfied.

$$C_e = \frac{5}{w \sqrt{R^2 + (2wl)^2}}$$

$$\left( \frac{50}{30} \right) = 1.67$$

$$C_e = \frac{10}{4\pi f \sqrt{R^2 + (4\pi f TL)^2}}$$

- Load impedance must be very large compared to  $C_e$ .

For  $n$ th harmonic current, load behaves as open circuit.

• The ~~R~~1

The RMS value of harmonic component of voltage across the ce:

$$V_{on} = (V_d)_{in} * \frac{1}{(j\omega n L_c) + \frac{1}{(j\omega n C_e)}} * \frac{1}{(j\omega n C_e)}$$

$$= (V_d)_{in} * \frac{1}{-(n\omega)^2 L_c C_e^2 + 1}$$

$$V_{on} = (V_d)_{in} * \frac{1}{1 - n^2 \omega^2 L_c C_e^2}$$

Total harmonic RMS value of ripple voltage due to all harmonics —

$$(V_o)_{\text{ripple}} = \left[ \sum_{n=2,4,6}^{\infty} (V_{on})^2 \right]^{\frac{1}{2}}$$

Considering only the second harmonic —

$$(V_o)_{\text{ripple}} = V_{o2} = \frac{1}{(2\omega)^2 L_c C_e - 1} (V_d)_2$$

$$V_{d2} = \frac{4V_m}{3\pi\sqrt{2}}$$

$$V_{dc} = \frac{2V_m}{\pi}$$

$$\text{R.F.} = \frac{(V_{o2})}{V_{dc}}$$

$$= \frac{2 \frac{4V_m}{3\pi\sqrt{2}}}{(2\omega)^2 L_c C_e} \left( \frac{1}{1 - (2\omega)^2 L_c C_e} \right)$$

$$\boxed{\text{R.F.} = \frac{\sqrt{2}}{3} \left( \frac{1}{1 - (2\omega)^2 L_c C_e} \right)}$$

$$R.F. = \frac{\sqrt{2}}{3} \left( \frac{1}{1 - \frac{10}{(2\pi f)^2 \sqrt{R^2 + (4\pi f L)^2}}} \right)$$

$$R.F. = \frac{\sqrt{2}}{3} \left[ \frac{\sqrt{R^2 + (4\pi f L)^2}}{\sqrt{R^2 + (4\pi f L)^2} - 10L e} \right]$$

$$\frac{3 R.F.}{\sqrt{2}} = \frac{\sqrt{R^2 + (4\pi f L)^2}}{\sqrt{R^2 + (4\pi f L)^2} - 10L e}$$

$$\frac{3}{\sqrt{2}} (R.F.) = \frac{1}{1 - \frac{10L e}{\sqrt{R^2 + (4\pi f L)^2}}}$$

$$1 - \frac{10L e}{\sqrt{R^2 + (4\pi f L)^2}} = \left( \frac{\sqrt{2}}{3 R.F.} \right) \frac{10}{1.02 \times \pi \times f} = 0$$

$$1 - \frac{\sqrt{2}}{3 R.F.} = \frac{10L e}{\sqrt{R^2 + (4\pi f L)^2}}$$

$$L e = \frac{\sqrt{R^2 + (4\pi f L)^2}}{10} \left[ 1 - \frac{\sqrt{2}}{3 R.F.} \right] = 0$$

$$\left[ \frac{\sqrt{2}}{3 R.F.} - 1 \right] = \frac{(1.02 \times \pi \times 0.002) + 5(0.0)}{1.02 \times \pi \times 0.002} = 0$$

Ques An LC filter is used to reduce the amount of ripple content at the output of a 1-Φ full wave rectifier, the load resistance  $R = 40\Omega$  & load inductance  $L = 10\text{mH}$  & source is  $220\text{V}, 50\text{Hz}$ . Design an LC filter so that R.F of the o/p is 10%.

Soln

$$R = 40\Omega$$

$$L = 10\text{mH}$$

$$V_m = 220\sqrt{2}$$

$$f = 50\text{Hz}$$

$$C_L = \frac{10}{4\pi f \sqrt{(40)^2 + (4\pi \times 50 \times 10 \times 10^{-3})^2}}$$


$$= \frac{10}{4\pi \times 50 \cdot \sqrt{1600 + 1600}} = \frac{10}{160} = 0.0625$$

$$C_L = \frac{3.93\text{ mF}}{0.0625} = 63\text{ mF}$$

$$L_o = \frac{\sqrt{R^2 + (4\pi f L)^2}}{10} \left[ 1 - \frac{\sqrt{2}}{3 \times 0.1} \right]$$

$$= \frac{\sqrt{(40)^2 + (200\pi \times 10^{-2})^2}}{10} \left[ 1 - \frac{\sqrt{2}}{0.3} \right]$$

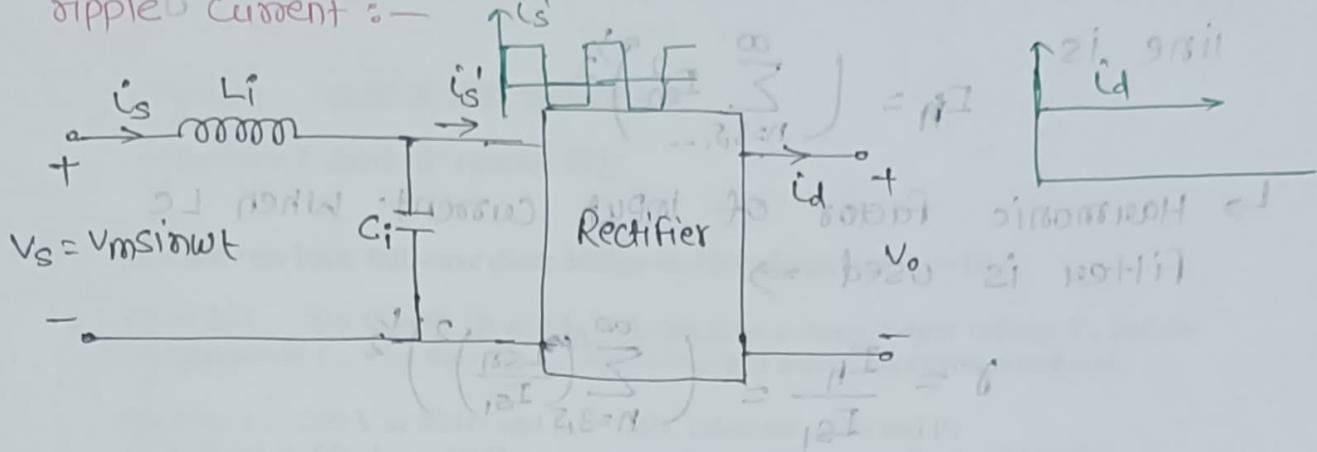\* input LC filter to limit the amount of input ripple current :-



↳  $i_{sn}$  is the  $n^{th}$  harmonic current in the source.

↳  $i_{sn}$  is the  $n^{th}$  harmonic current at the input of rectifier

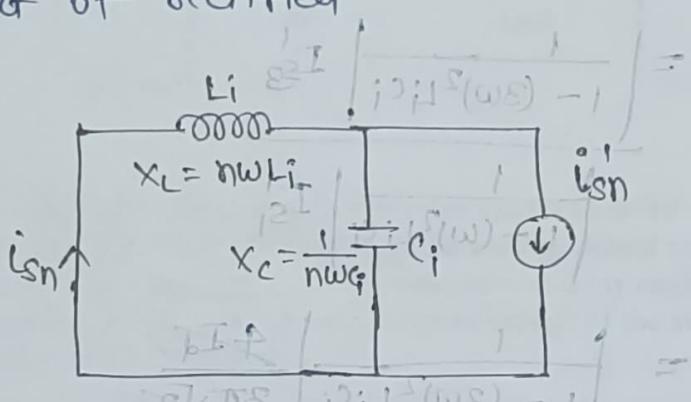


fig. - eq. ckt. for  $n^{th}$  harmonic current.

by current divider rule

$$i_{sn} = \frac{i_{sn} * \frac{1}{jn\omega C_i}}{(jn\omega L_i) + \frac{1}{jn\omega C_i}}$$

$$= i_{sn} * \frac{1}{1 - (n\omega)^2 L_i C_i}$$

$$= \left| \frac{1}{1 - (n\omega)^2 L_i C_i} \right| i_{sn}$$

The total harmonic current in the ac supply line is

$$I_h = \left( \sum_{n=3,5,\dots}^{\infty} I_{sn}^2 \right)^{1/2}$$

↳ Harmonic factor of input current when LC filter is used  $\Rightarrow$

$$\gamma = \frac{I_h}{I_{s1}} = \left( \sum_{n=3,5,\dots}^{\infty} \left( \frac{I_{sn}}{I_{s1}} \right)^2 \right)^{1/2}$$

By considering only the third harmonic  $\rightarrow$

$$\begin{aligned} \gamma &= \frac{I_3}{I_{s1}} = \left( \frac{I_{s3}}{I_{s1}} \right) \\ &= \frac{1}{\left| \frac{1}{1 - (3\omega)^2 L_i C_i} \right|} \frac{I_{s3}}{I_{s1}} \\ &= \frac{1}{\left| \frac{1}{1 - (\omega)^2 L_i C_i} \right|} \frac{I_{s1}}{I_{s1}} \\ &= \frac{1}{\left| \frac{1}{1 - (3\omega)^2 L_i C_i} \right|} \frac{4\pi d}{8\pi \sqrt{2}} \\ &= \frac{1}{\left| \frac{1}{1 - \omega^2 L_i C_i} \right|} \frac{4\pi d}{8\pi \sqrt{2}} \\ &= \frac{1}{\left| \frac{1}{1 - \omega^2 L_i C_i} \right|} + \left( \frac{4\pi d}{8\pi \sqrt{2}} \right) \end{aligned}$$

For specified value of Harmonic factor of i/p current  $\gamma$ ,  $L_i$ ,  $C_i$  can be calculated.



Choose a convenient value of  $C_i$  and then obtain the value of  $L_i$ .

\* Filter Resonant freqn =  $\frac{1}{\sqrt{L_i C_i}}$



Ques

An LC filter is to be designed to limit the amount of ripple in i/p current for a 1-Φ FW Rectifier. The load current is ripple free. Supply  $f_{\text{eqn}} = 50 \text{ Hz}$ .

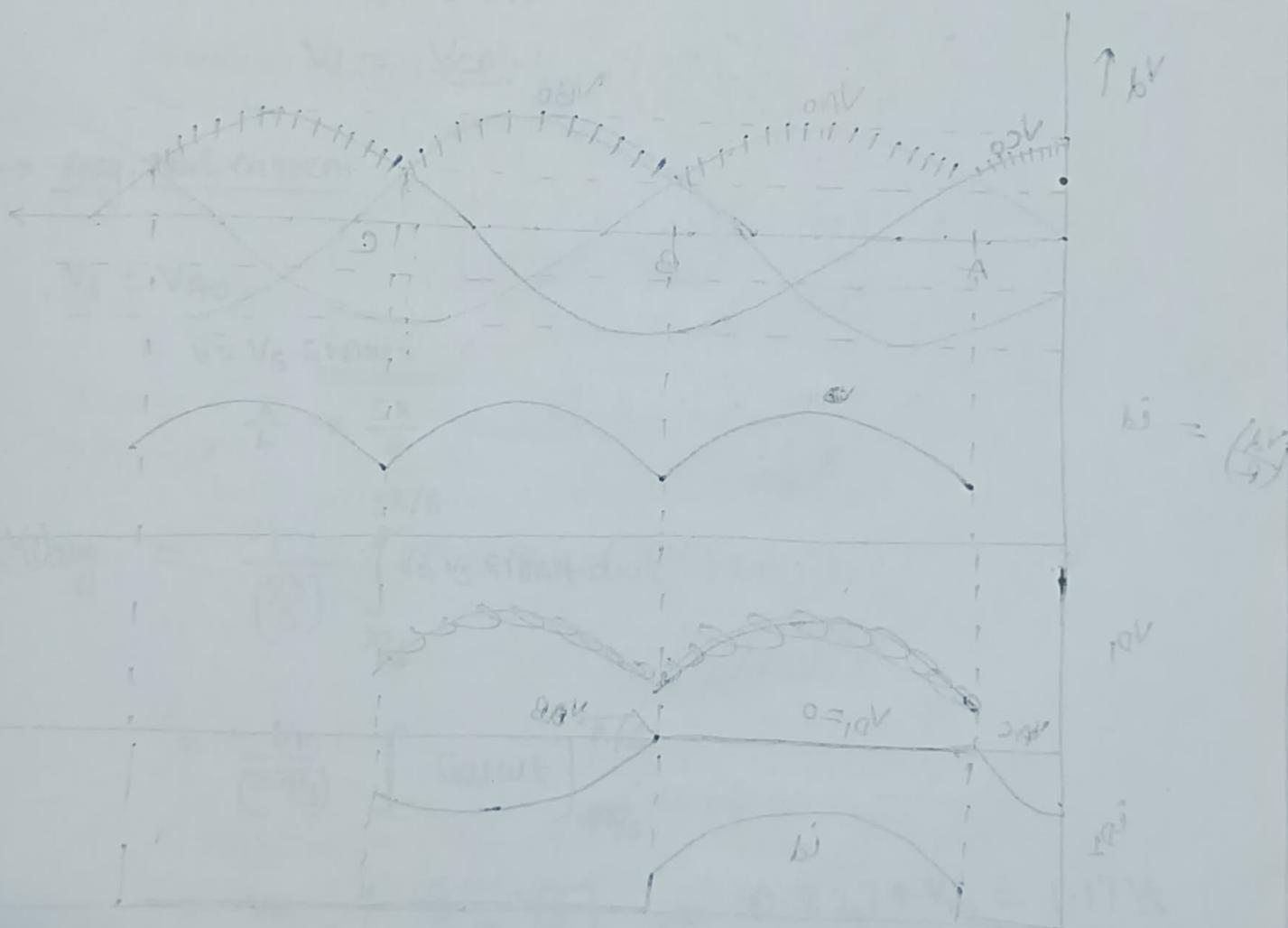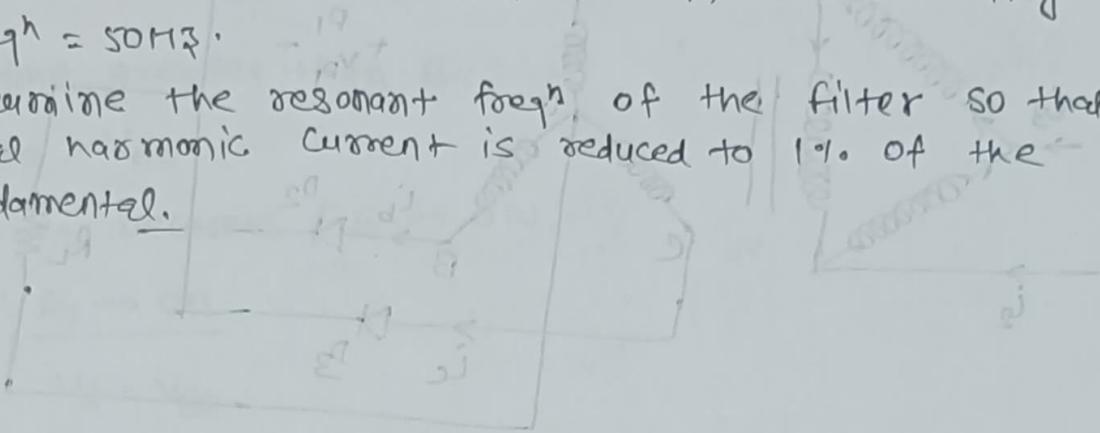Determine the resonant frequency of the filter so that total harmonic current is reduced to 1% of the fundamental.



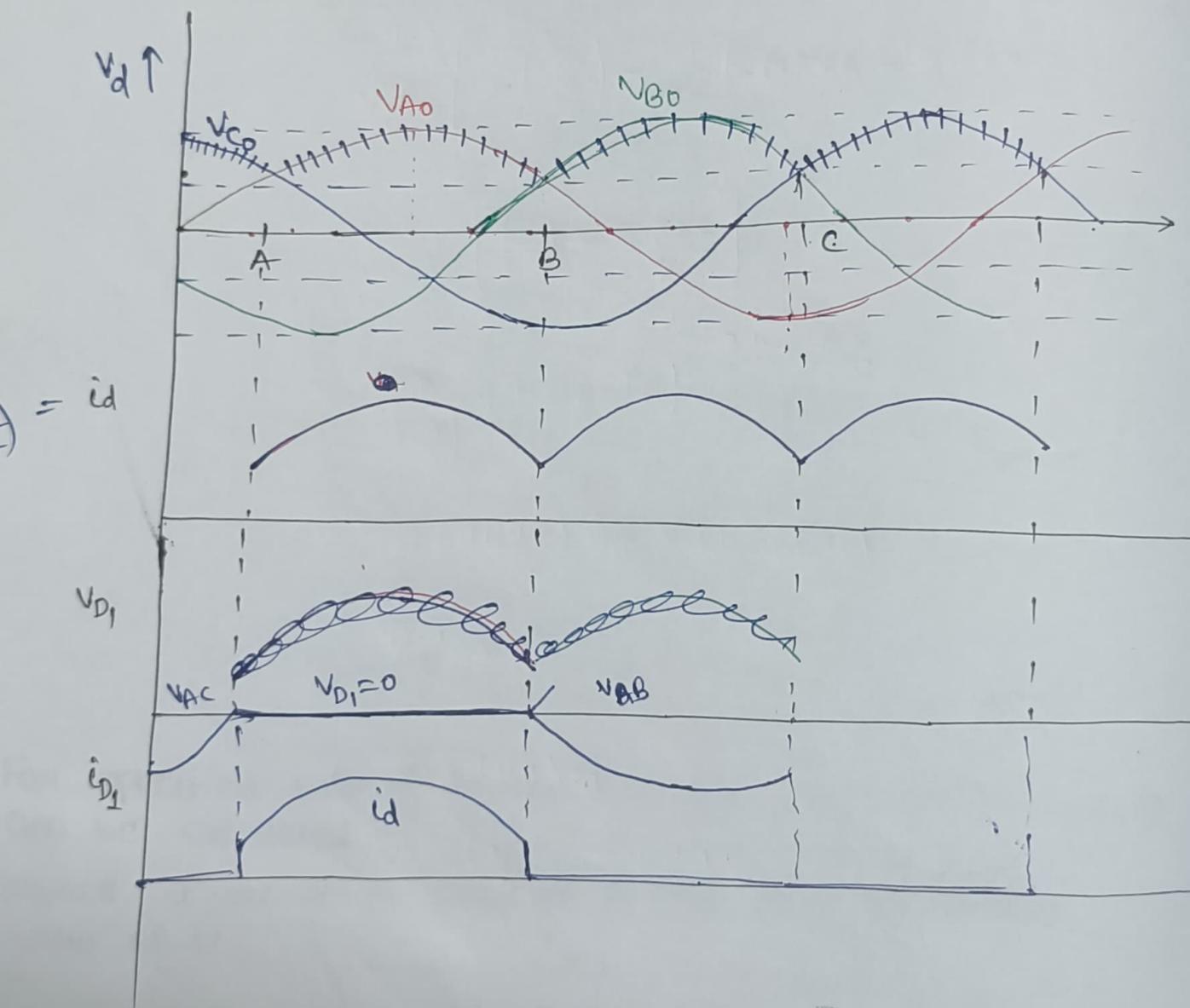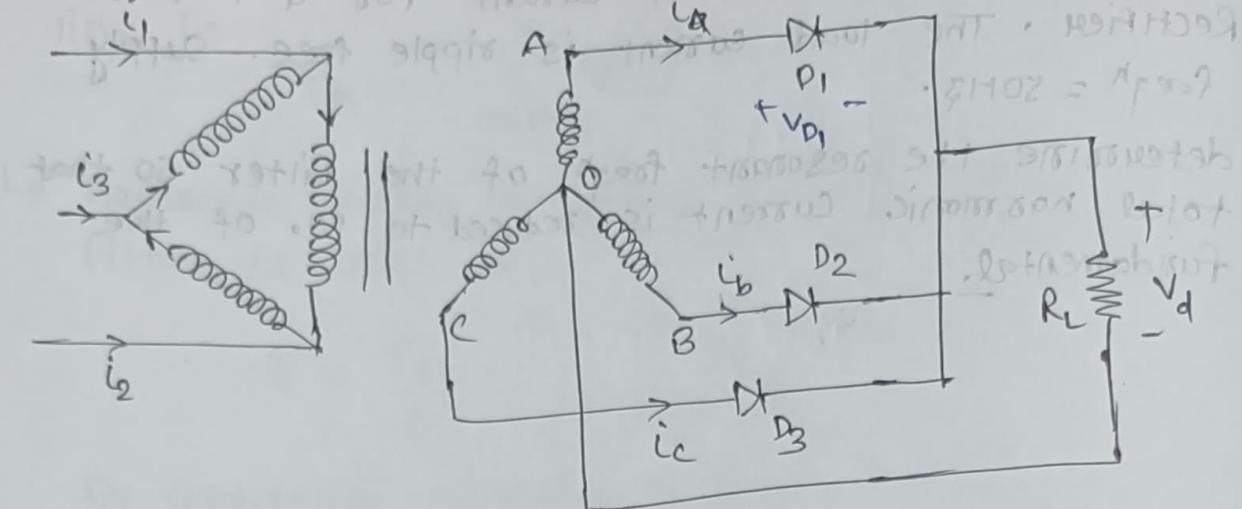\* 3-Φ Half wave Uncontrolled Rectifier Circuit :-



• A → B  $V_{AO}$  is most positive  
 $D_1$  is ON  
 $V_d = V_{AO}$

For time greater than  $B_{\text{ris}} + \frac{\pi}{\omega}$  [  $\frac{1}{\left(\frac{\pi}{\omega}\right)} \cdot \frac{1}{\left(\frac{\pi}{\omega}\right)}$  ]  $= \sin(0)$   
 $V_{BO} > V_{AO}$

∴  $D_2$  becomes F.B → ON.

• B → C :  $D_2 \rightarrow \text{ON}$

$$V_d = V_{BO}$$

• C → A  $V_{CO}$  is most positive

$D_3$  is ON

$$\left[ \left( \frac{228.0}{\frac{\pi}{\omega}} - \frac{\pi}{\omega} \right) \cdot \frac{1}{\frac{\pi}{\omega}} - \left( \frac{\pi}{\omega} \right) \cdot \frac{1}{\frac{\pi}{\omega}} \right] \frac{mV}{\left( \frac{\pi}{\omega} \right)} =$$

↳ Avg. load current

$$V_d = V_{AO}$$

$$= \sqrt{2} V_s \sin \omega t$$

$$\frac{\pi}{6} \rightarrow \frac{5\pi}{6}$$

$$(V_d)_{\text{avg.}} = \frac{1}{\left(\frac{2\pi}{3}\right)} \int_{\frac{\pi}{6}}^{\frac{5\pi}{6}} \sqrt{2} V_s \sin \omega t d\omega t$$

$$= \frac{V_m}{\left(\frac{2\pi}{3}\right)} \left[ \cos \omega t \right]_{\frac{\pi}{6}}^{\frac{5\pi}{6}}$$

$$= \frac{V_m}{\left(\frac{2\pi}{3}\right)} \cdot \left( \frac{\sqrt{3}}{2} + \frac{\sqrt{3}}{2} \right) = 0.8274 V_m = \underline{\underline{1.17 V_s}}$$

$$= \frac{V_m}{\left(\frac{2\pi}{3}\right)} (\sqrt{3})$$

$$= \left( \frac{3\sqrt{3}}{2\pi} \right) V_m = \frac{3\sqrt{3}\sqrt{2}}{2\pi} \frac{V_s}{\pi}$$

$$= \left( 3 \sqrt{\frac{3}{2}} \frac{V_s}{\pi} \right)$$

→ RMS Value of load voltage

$$\begin{aligned}
 (V_d)_{\text{rms}} &= \left[ \frac{1}{\frac{2\pi}{3}} \int_{\frac{\pi}{6}}^{\frac{5\pi}{6}} V_m^2 \sin^2 \omega t dt \right]^{\frac{1}{2}} \\
 &= \frac{V_m^2}{\sqrt{\frac{2\pi}{3}}} \int_{\frac{\pi}{6}}^{\frac{5\pi}{6}} \left( \frac{1 - \cos 2\omega t}{2} \right) dt \\
 &= \left[ \frac{V_m^2}{\sqrt{\frac{2\pi}{3}}} \cdot \frac{1}{2} \left[ \left( \frac{5\pi}{6} - \frac{\pi}{6} \right) - \frac{1}{2} (\sin \frac{5\pi}{6} - \sin \frac{\pi}{6}) \right] \right]^{\frac{1}{2}} \\
 &= \frac{V_m}{\sqrt{\frac{2\pi}{3}}} \left[ \frac{1}{2} \left( \left( \frac{\pi}{3} \right) + 0.866 \right) \right]^{\frac{1}{2}} \\
 &= \frac{V_m}{\sqrt{\frac{2\pi}{3}}} \left[ \left( \frac{\pi}{3} \right) + 0.866 \right]^{\frac{1}{2}} \\
 &= \frac{V_m}{\sqrt{\frac{2\pi}{3}}} \cdot (1.38318) \\
 &= (0.69098) V_m \cdot (1.38318) \\
 &= 0.955
 \end{aligned}$$

$$= 0.8406 V_m$$

$$2V \cdot 1.1 = m^2 + 1 = 8.188 V_s \quad \approx 1.19 V_s$$

$$\frac{m^2}{\pi^2} \left( \frac{2V}{R_S} \right)^2 = (2V) \frac{mV}{\left( \frac{R_S}{E} \right)} =$$

$$\hookrightarrow \text{Load voltage f.f.} = \frac{1.19 V_S}{1.177 V_S} \approx 1.01$$

$$\hookrightarrow \text{Ripple factor } \gamma = \frac{\sqrt{V_d^2_{\text{rms}} - V_d^2_{\text{avg}}}}{(I_d)_{\text{avg}}} \approx 0.185$$

$$\hookrightarrow \text{Ripple freqn} = 3 * (\text{Supply freqn})$$

$$\hookrightarrow \text{PIV diode} = \sqrt{3} V_S \sqrt{2} = \sqrt{6} V_S \\ \approx (\sqrt{3} V_m)$$

$\hookrightarrow$  as load is Resistive,

$$\text{Avg. load current} = (I_d)_{\text{avg}} = \frac{(V_d)_{\text{avg}}}{R_L}$$

$(I_d)_{\text{avg}}$

$$\hookrightarrow \text{Avg. diode current Rating} = \frac{1}{3} \left\{ \frac{(V_d)_{\text{avg}}}{R_L} \right\}.$$

$$\hookrightarrow \text{Rms load current} = (I_d)_{\text{rms}} = (1.01) (I_d)_{\text{avg}}.$$

$$\hookrightarrow \text{Total load power} = P = (I_d)_{\text{rms}}^2 R_L.$$

Let  $I_D$  is the Rms value of current through a diode.

$$3 I_D^2 R_L = (I_d)_{\text{rms}}^2 R_L \quad \leftarrow \begin{matrix} \text{total} \\ \text{power flow through} \\ \text{transformer.} \end{matrix}$$

$$I_D = 0.58 (I_d)_{\text{avg}} \quad \boxed{I_D = 0.58 (I_d)_{\text{rms}}}$$

$\hookrightarrow$  Each diode must carry an Rms value of current equal to 58% of avg. load current.

- If the rated transformer secondary RMS current is chosen same as that of diode RMS current.
- Transformer Secondary Voltampere =  $3V_S I_D$

$$P_{\text{out}(bI)} = 3 \frac{(V_d)_{\text{avg}} \times 0.58 (I_d)_{\text{avg}}}{1.17}$$

$$= 1.5 (V_d)_{\text{avg}} \cdot (I_d)_{\text{avg}}$$

$$2V_d = 6V \Rightarrow V_d = \frac{6V}{2} = 3V$$

$$(mV)$$

$$P_{\text{out}(bI)} = P_{\text{out}(bI)} \approx 1.5 \times 3V \times 0.58$$

$$= P_{\text{out}(bI)}$$

$$\left\{ \frac{P_{\text{out}(bI)}}{R_s} \right\} \frac{1}{E} = \text{power delivered by source}$$

$$P_{\text{out}(bI)}(10.1) = 2mS(bI) = \text{transformer power output}$$




$$R_{2mS(bI)} = 9 = \text{load resistor value}$$

~~to obtain power delivered to source & to find value of load resistor~~


$$2mS(bI) 82.0 = I_D \cdot P_{\text{out}(bI) 82.0} = I_D^2 R$$

$$2mS(bI) 82.0 = I_D \cdot P_{\text{out}(bI) 82.0} = I_D^2 R$$
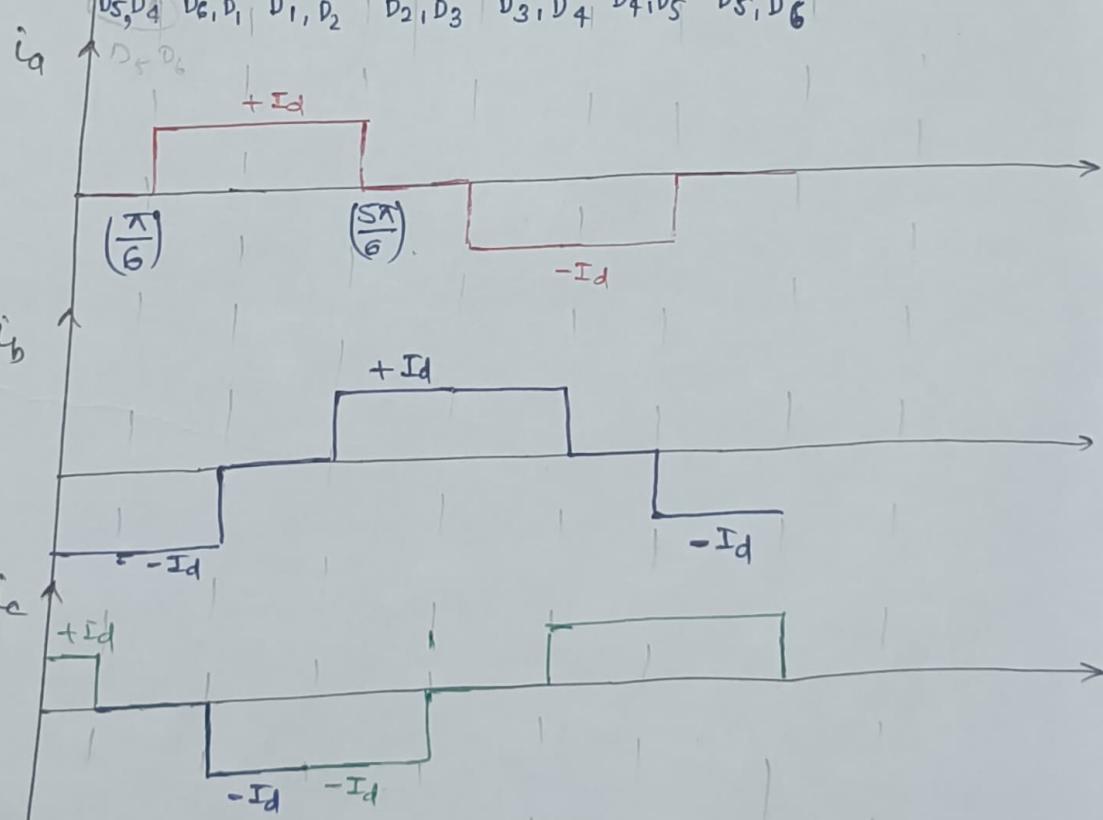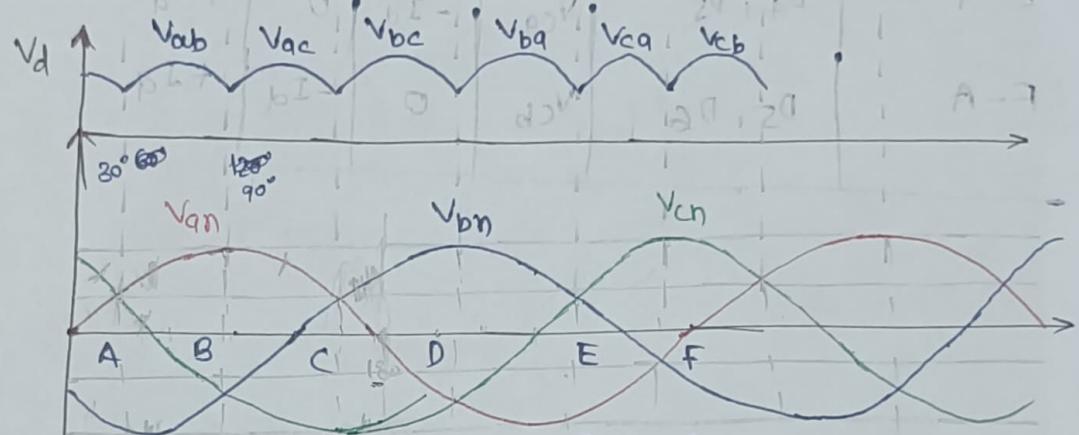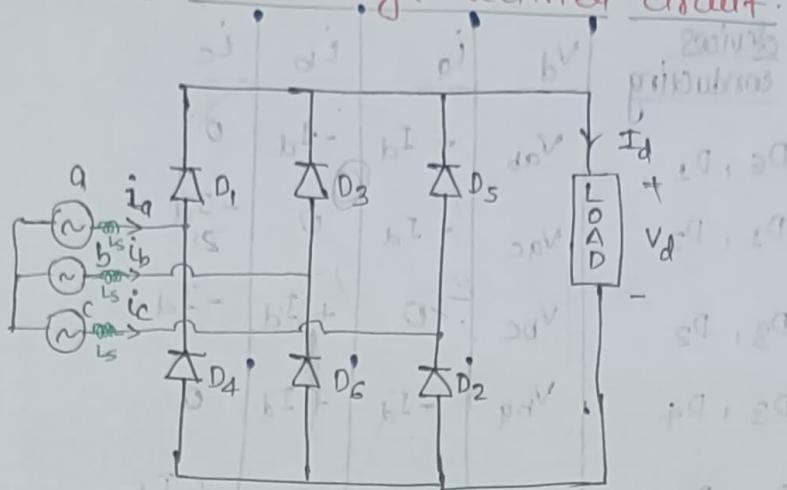
# \* 3-Φ Fullwave Diode bridge rectifier circuit.



| <u>interval</u> | <u>devices conducting</u>       | $v_d$    | $i_q$  | $i_b$  | $i_c$  |
|-----------------|---------------------------------|----------|--------|--------|--------|
| A-B             | D <sub>6</sub> , D <sub>1</sub> | $v_{ab}$ | $+I_d$ | $-I_d$ | 0      |
| B-C             | D <sub>1</sub> , D <sub>2</sub> | $v_{ac}$ | $+I_d$ | 0      | $-I_d$ |
| C-D             | D <sub>3</sub> , D <sub>2</sub> | $v_{bc}$ | 0      | $+I_d$ | $-I_d$ |
| D-E             | D <sub>3</sub> , D <sub>4</sub> | $v_{ba}$ | $-I_d$ | $+I_d$ | 0      |
| E-F             | D <sub>4</sub> , D <sub>5</sub> | $v_{ca}$ | $-I_d$ | 0      | $+I_d$ |
| F-A             | D <sub>5</sub> , D <sub>6</sub> | $v_{cb}$ | 0      | $-I_d$ | $+I_d$ |

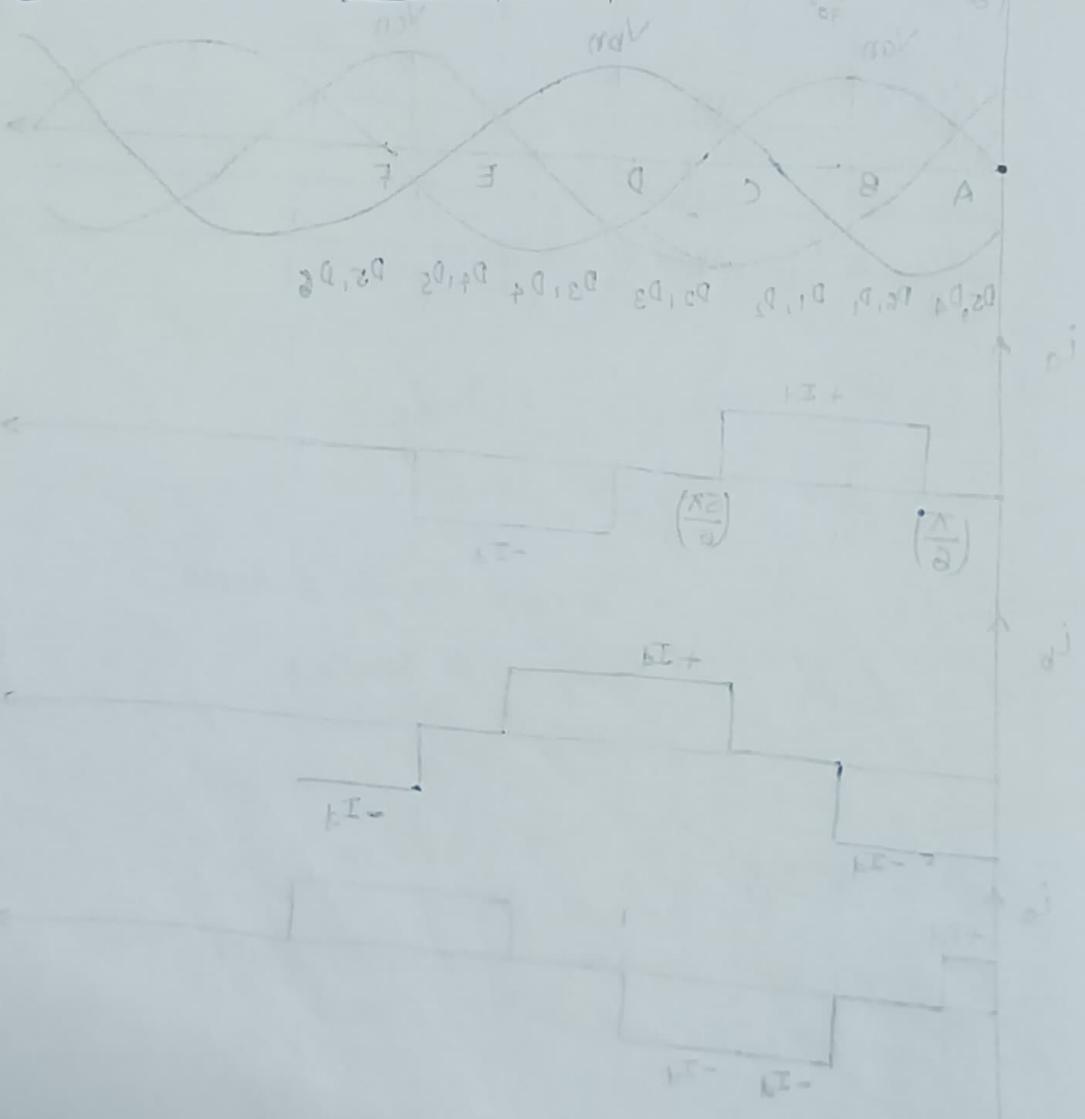

### \* Avg. load voltage

$$V_d = \frac{1}{(2\pi/6)} \int_{\pi/6}^{\pi/2} (V_{ab}) d\omega t$$

$$= \frac{1}{(\frac{2\pi}{6})} \int_{\pi/6}^{\pi/2} [V_m \sin \omega t - V_m \sin(\omega t - 120^\circ)] d\omega t$$

$$= \frac{V_m}{(\frac{2\pi}{6})} \left[ (\cos \omega t) \Big|_{\pi/2}^{\pi/6} - \left\{ \cos(\omega t - 120^\circ) \right\} \Big|_{\pi/2}^{\pi/6} \right] \quad (\text{using } \int \frac{d\omega t}{\omega} = \theta)$$

$$\frac{\sqrt{3}}{(\frac{2\pi}{6})} V_m = \frac{\sqrt{3}}{(\frac{2\pi}{6})} \sqrt{2} V_s \quad \boxed{\frac{\sqrt{3}}{2} - 10 - 0.866}$$

$$= \left( \frac{3}{\pi} \right) \sqrt{2} V_{LL}$$

$V_{LL}$  is the RMS value of line to line voltage

### \* RMS value of current

$$(I_d)_{rms} = \left( \sqrt{\frac{2}{3}} \right) I_d$$

$$\left( \frac{10}{\pi} \right) = 10$$

instantaneous value of fundamental component of  $I_a$  :-

$$I_a = a_1 \cos \omega t + b_1 \sin \omega t$$

$$a_1 = 0 \quad \frac{1}{\pi/2} \int I_d \cos \omega t d\omega t = 0$$

$$b_1 = \frac{1}{\pi/2} \int I_d \sin \omega t d\omega t$$

$$b_1 = \frac{2}{\pi} \int_{\pi/6}^{\pi/2} I_d (\cos \omega t) d\omega t$$

$$b_1 = \frac{2}{\pi} \left[ I_d \left( \cos \omega t \right) \Big|_{\pi/6}^{\pi/2} \right]$$

$$\left( \frac{8}{\pi} \right) = \frac{2}{\pi} \times \frac{2}{\pi} = \frac{2 I_d}{\pi} \left[ \frac{\sqrt{3}}{2} - \left( -\frac{\sqrt{3}}{2} \right) \right]$$

$$\underline{220.0} = \frac{2 I_d}{\pi} (\sqrt{3})$$

$$b_1 = \frac{2\sqrt{3}}{\pi} I_d$$

$$\phi_1 = \tan^{-1} \left( \frac{b_1}{b_1} \right) = 0$$

$$i_{q_1} = b_1 \sin \omega t$$

$$i_{q_1} = \frac{2\sqrt{3}}{\pi} I_d \sin \omega t$$

↳ RMS value of fundamental component of source line current

$$\begin{aligned} &= \frac{(2\sqrt{3})}{\pi} I_d \left[ \frac{(\cos \omega t - \sin \omega t)}{\sqrt{2}} \right] = \frac{\sqrt{6}}{\pi} I_d \end{aligned}$$

↳ RMS value of  $n^{\text{th}}$  harmonic components of line current  $i_{q_h}$  :-

$$i_{q_h} = \left( \frac{i_{q_1}}{h} \right)$$

$h = 5, 7, 11, 13, \text{ etc.}$

- even and triplet harmonics are absent.

↳ Source side apparent power =  $3V_s I_q$

$$S = \frac{3V_s}{\sqrt{3}} \sqrt{\frac{2}{3}} I_d$$



↳ Source side active power =  $3V_s I_{q_1} \cos \phi_1$

$$= 3V_s \frac{\sqrt{6}}{\pi} I_d$$


↳ Source side power factor =  $\frac{3V_s \frac{\sqrt{6}}{\pi} I_d}{3V_s \sqrt{\frac{2}{3}} I_d}$


$$\left[ \left( \frac{3}{\pi} \right) - \frac{\sqrt{6}}{\sqrt{2}} \right] \frac{1}{\pi} = \frac{\sqrt{6}}{\pi} * \frac{\sqrt{3}}{\sqrt{2}} = \left( \frac{3}{\pi} \right)$$
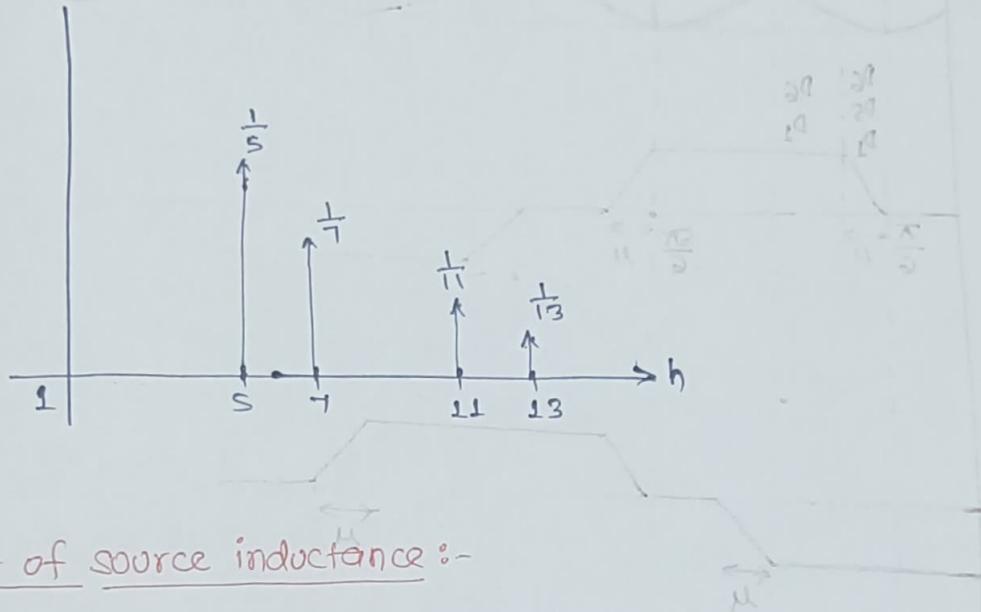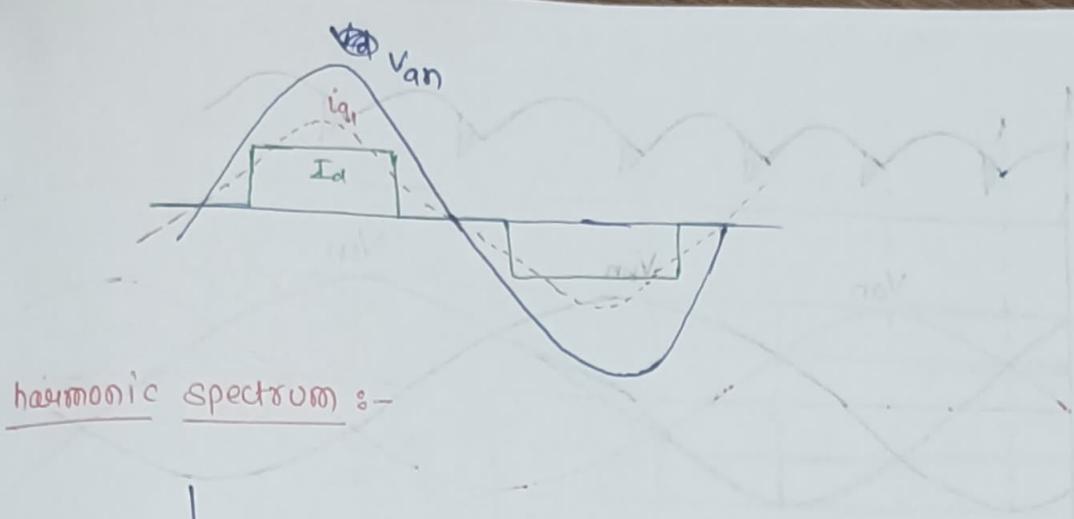
$$\left( \frac{3}{\pi} \right) \frac{I_d}{\pi} = 0.955$$



### \* Effect of source inductance :-

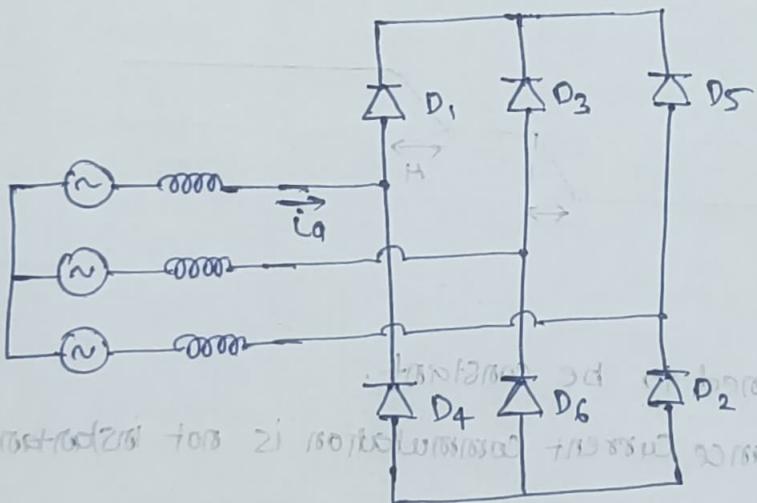

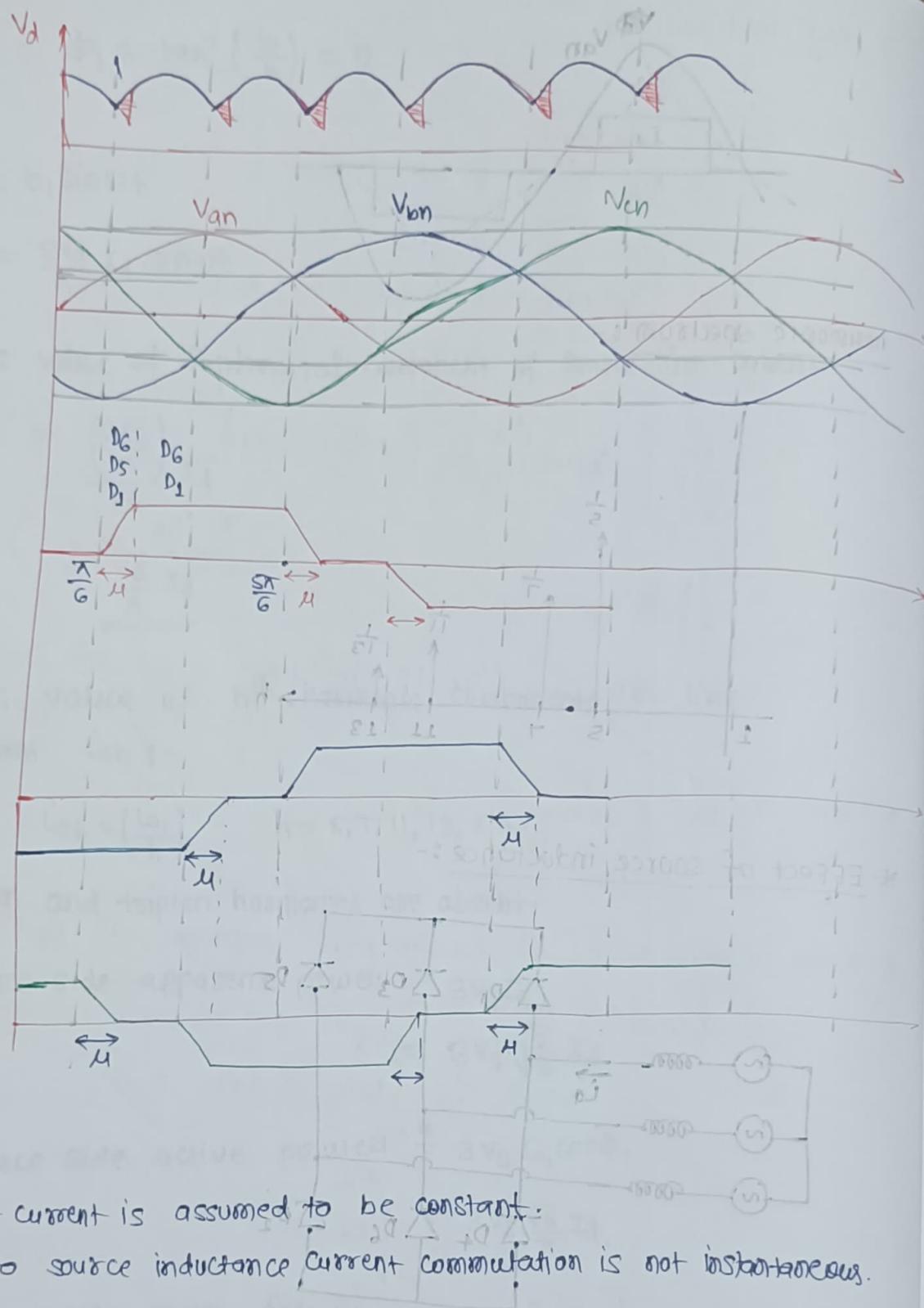


↪ output current is assumed to be constant.

↪ Due to source inductance, current commutation is not instantaneous.

- For  $wt < \frac{\pi}{6}$ ,  $D_5$  and  $D_6$  were conducting.
- For  $wt > \frac{\pi}{6}$ ,  $V_{an}$  is greater than  $V_{bn}$ .
- $D_1$  starts conducting. Due to  $L_s$ ,  $i_u$  rises from zero to  $I_d$  through  $D_1$ , gradually in a period  $\mu$  i.e. during  $(\frac{\pi}{6})$  to  $(\frac{\pi}{6} + \mu)$
- During same interval,  $i_u$  decreases from  $I_d$  to zero through  $D_5$ .
- During  $(\frac{\pi}{6})$  to  $(\frac{\pi}{6} + \mu)$ ,  $D_5$ ,  $D_6$  and  $D_1$  conduct.

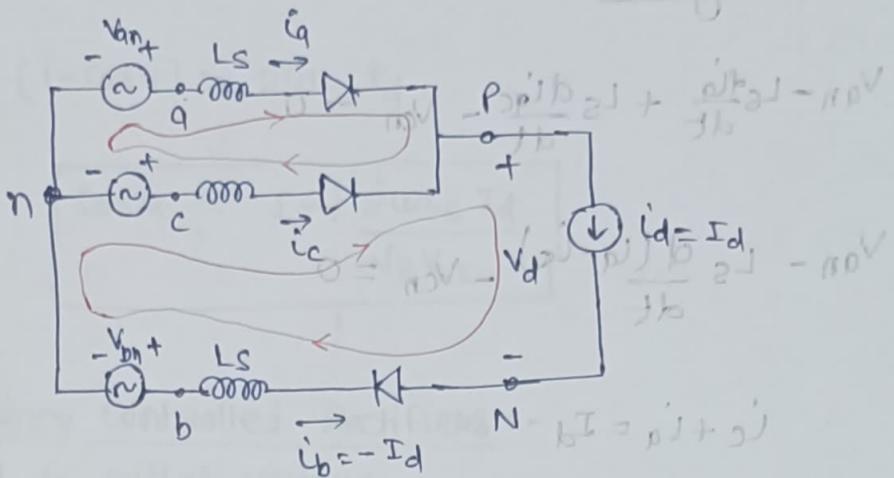during  $(\frac{\pi}{6})$  to  $(\frac{\pi}{6} + \frac{1}{3}\pi)$  eq. ckt: -



eq. ckt. diagram during  $\frac{\pi}{6} < \theta < \frac{\pi}{6} + \frac{1}{3}\pi$

$$-V_{an} + L_s \frac{di_a}{dt} + V_d + L_s \frac{di_b}{dt} + V_{bn} = 0 \quad \text{(during commutation period)}$$

$$\Rightarrow V_{an} = V_d + V_{bn} - L_s \frac{di_b}{dt}$$

$$\text{avg. output voltage } = V_d = \frac{1}{(2\pi)} \left[ \int_{\frac{\pi}{6}}^{\frac{\pi}{6} + \frac{1}{3}\pi} (V_{an} - V_{bn} - L_s \frac{di_b}{dt}) d\omega t \right]$$

$$+ \int_{\frac{\pi}{6} + \frac{1}{3}\pi}^{\frac{\pi}{2}} (V_{an} - V_{bn}) d\omega t \Bigg]$$

$$= \frac{1}{(2\pi/6)} \left[ \int_{\frac{\pi}{6}}^{\frac{\pi}{2}} (V_{an} - V_{bn}) d\omega t - \int_{\frac{\pi}{6} + \frac{1}{3}\pi}^{\frac{\pi}{2}} (-wL_s \frac{di_b}{d\omega t}) d\omega t \right]$$

$$I_{2\pi} = \int_{\frac{\pi}{6}}^{\frac{\pi}{2}} wL_s \left( \frac{3}{\pi} \sin \theta \right) d\omega t$$

$$I_{2\pi} = \left[ \left( \frac{1}{6} + \frac{3}{\pi} \right) 2\omega + \left( \frac{3}{\pi} \right) \omega \right] - \left( \frac{1}{6} \cdot \frac{3}{\pi} \cdot \sin \theta \right) \left[ \frac{3}{\pi} \omega \right] \text{ mV}$$

$$I_{2\pi} = 1.25 V_{LL} - \frac{wL_s}{2\pi} \left( \frac{3}{\pi} \omega \right) I_d$$

$$I_{2\pi} = \left[ \left( \frac{1}{6} + \frac{3}{\pi} \right) 2\omega - \left( \frac{3}{\pi} \right) \omega \right] \text{ mV}$$

\* overlap angle  $\alpha$

$$V_{an} - L_s \frac{di_a}{dt} + L_s \frac{di_c}{dt} - V_{cn} = 0$$

$$V_{an} - L_s \frac{d(i_a - i_c)}{dt} - V_{cn} = 0$$

$$i_c + i_a = I_d$$

$$V_{an} - V_{cn} = L_s \frac{d(i_a - i_c)}{dt}$$

$$= L_s \frac{d}{dt} (i_a - I_d + i_a) = L_s \frac{d}{dt} (2i_a - I_d)$$

$$= L_s \frac{d}{dt} (2i_a) - L_s \frac{d}{dt} I_d = 0 \quad (\because \frac{dI_d}{dt} = 0)$$

$$V_{an} - V_{cn} = 2L_s \frac{d}{dt} i_a$$

$$(V_{an} - V_{cn}) d\omega t = w L_s d i_a$$

$$\int (V_{an} - V_{cn}) d\omega t = \int 2 L_s d i_a$$

$$\left[ \frac{V_m \sin \omega t - V_m \sin(\omega t - \frac{240^\circ}{120})}{\frac{\pi}{6} + u} \right] + \int (V_m \sin \omega t - V_m \sin(\omega t - \frac{240^\circ}{120})) d\omega t = 2w L_s I_d$$

$$V_m \left[ \cos \frac{\pi}{6} - \cos \left( \frac{\pi}{6} + u \right) - \cos \left( \frac{5\pi}{6} \right) + \cos \left( \frac{5\pi}{6} + u \right) \right] = 2w L_s I_d$$

$$V_m \left[ 2 \cos \frac{\pi}{6} - 2 \cos \left( \frac{\pi}{6} + u \right) \right] = 2w L_s I_d$$

$$2 V_m \left[ \cos \frac{\pi}{6} - \left\{ \cos \frac{\pi}{6} \cdot \cos u - \sin \frac{\pi}{6} \cdot \sin u \right\} \right] = 2w L_s I_d$$

$$2V_m \frac{\sqrt{2}}{2} (1 - \cos u) = 2WL_s I_d$$

$$\sqrt{2} V_m (1 - \cos u) = 2WL_s I_d$$

$$\cos u = 1 - \frac{2WL_s I_d}{\sqrt{2} V_{LL}}$$

### \* Linear frequency Controlled Rectifiers :-

#### • controlled dc output voltage

↳ values from +ve max<sup>m</sup> to -ve max<sup>m</sup>.

- controllable devices like thyristors, IGBT, BJT are used.
- commutation of the devices depends on the ac side line freqn.
- Hence the name line freqn rectifiers.
- DC side current is always +ve.
- DC side voltage is +ve (or) -ve.
- +ve voltage and +ve current at dc side indicates rectification mode. power flows from ac side to dc side.


⇒ operating points lie in the first quadrant of  $V_d$ - $I_d$  plane

⇒  $V_d$  (avg. voltage of dc side)

⇒  $I_d$  (avg. current at dc side)

• +ve current and +ve voltage at dc side indicates inversion mode. power flow from dc side to ac side

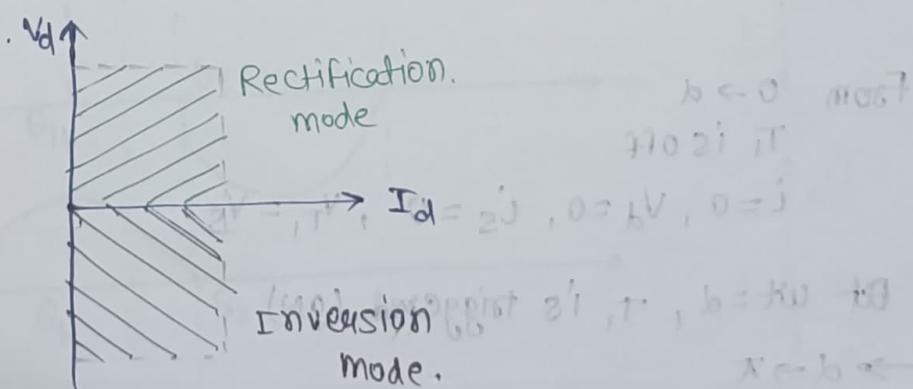⇒ operating points lie in the fourth quadrant of  $V_d$ - $I_d$  plane.





$$0 = fV, \quad i = 2f, \quad \text{and } \frac{dV}{dt} = \frac{2V}{R} = \frac{2V}{2} = 1, \quad 2V = 1V$$

\* Single phase Half wave controlled rectifier: -

\* R-load:-

$$V_{T_1} = (n_2 n_1 - 1) V_S$$

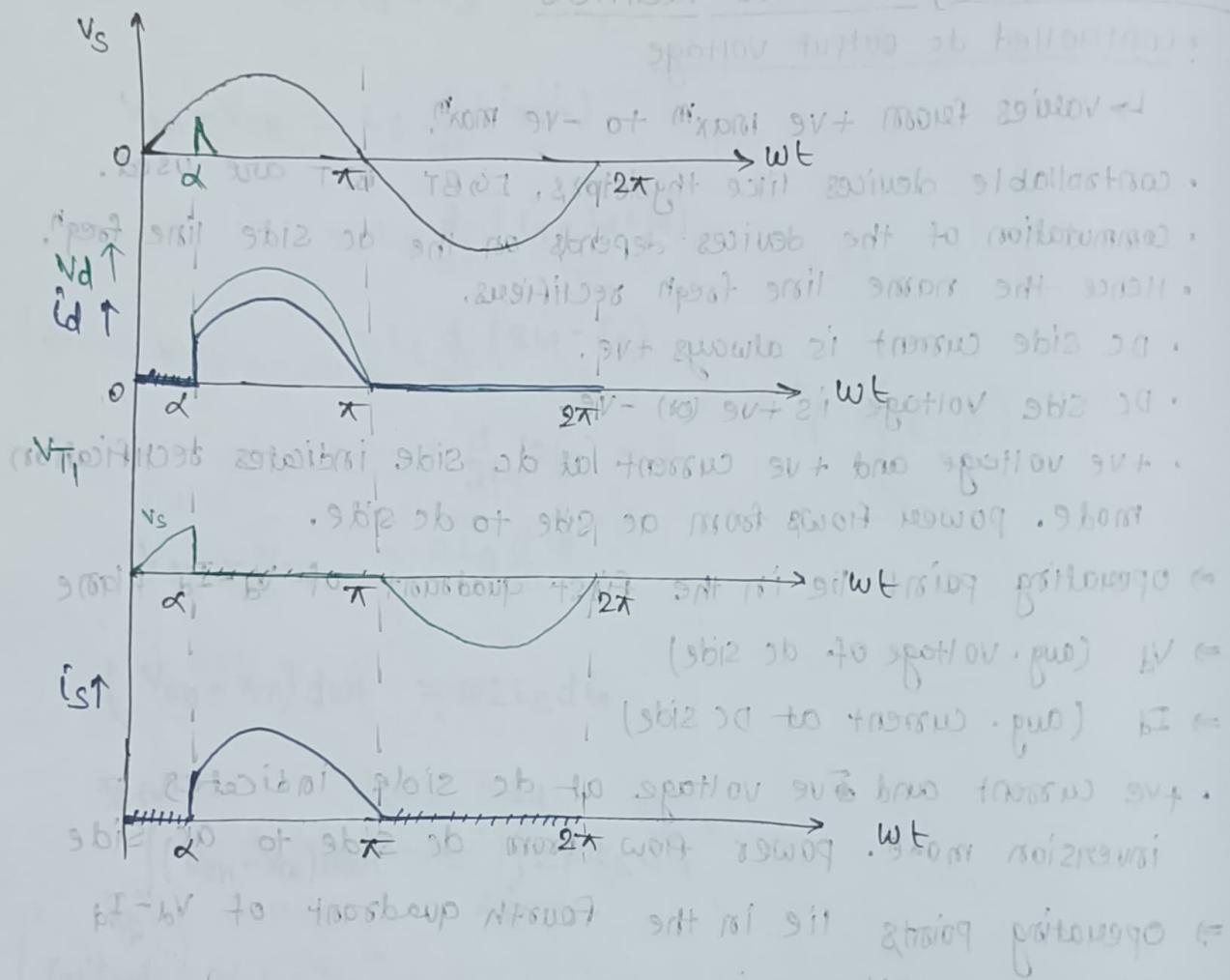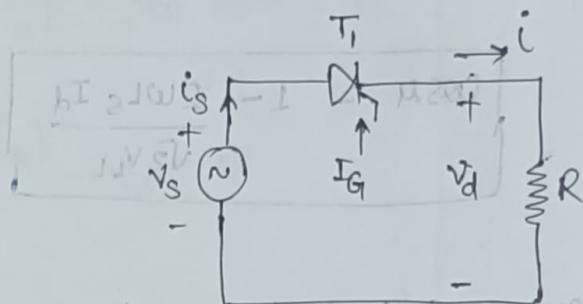

From  $0 \rightarrow \alpha$

$T_1$  is off

$$i = 0, V_d = 0, i_s = 0^2, V_{T_1} = V_S$$

At  $wt = \alpha$ ,  $T_1$  is triggered (ON)

$\hookrightarrow \alpha \rightarrow \pi$

$T_1$  is ON

$$\cdot V_d = V_S, i = \frac{V_d}{R} = \frac{V_S}{R} = \frac{\sqrt{2} V_S}{R} \sin wt, i_s = i, V_T = 0$$

• at  $wt = \pi$ ,  $i = 0$ .  $T_1$  becomes off

$\hookrightarrow \pi - 2\pi$

$T_1$  is off

$$i = 0, v_d = 0, v_T = v_s, i_s = 0$$

\* R-L load :-

$\alpha \rightarrow d$  (device is off)

$$i = 0, v_d = 0, v_L = 0, v_R = 0$$

$$v_T = v_s.$$


$\alpha \rightarrow Q_2$  (Thyristor is on)

$$v_d = Ril + L \frac{di}{dt} = v_s = \sqrt{2} v_s \sin wt$$

$$i =$$

$$v_R = Ril$$

$$v_L(t) = v_s - v_R(t)$$

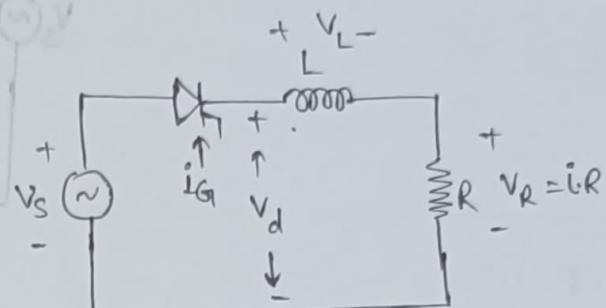


at  $wt = 0_1$




$$\frac{di}{dt} = 0, v_L = 0, v_R = v_s$$

$$\text{area } A_1 = \text{area } A_2$$

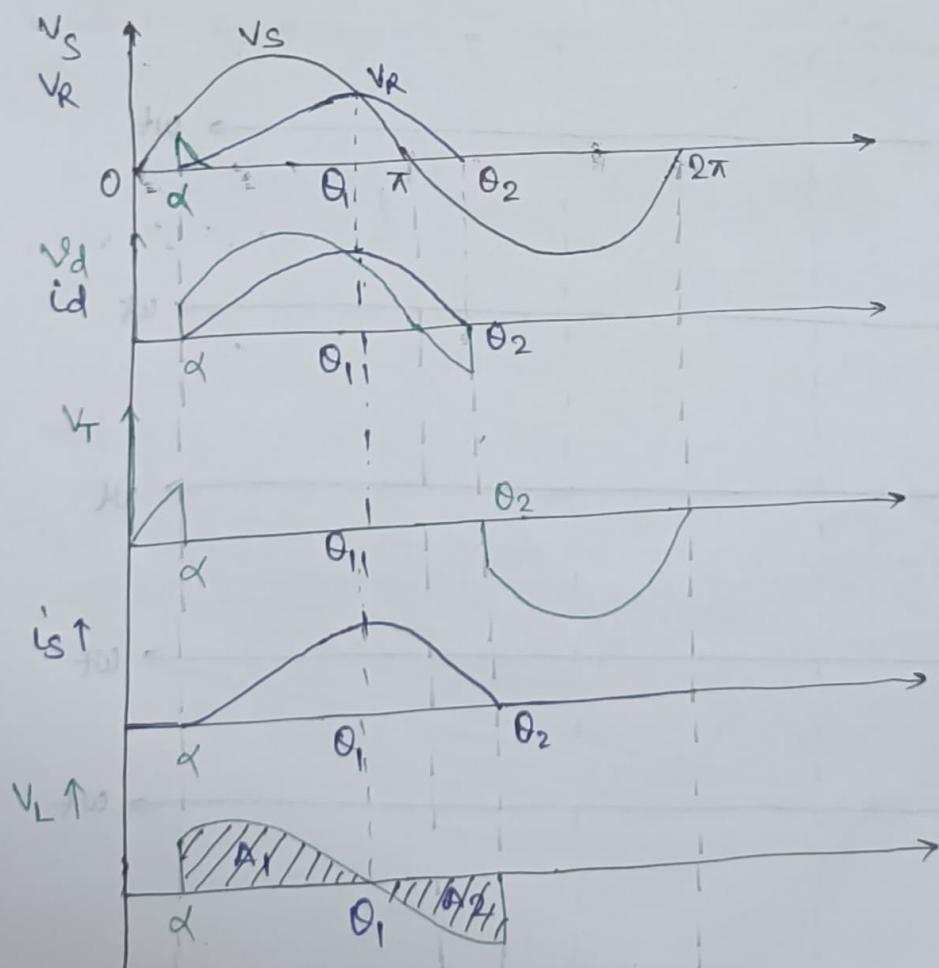
energy stored in the inductor during  $\alpha$  to  $Q_1$  is sent back to ac source during  $0_1$  to  $0_2$ .



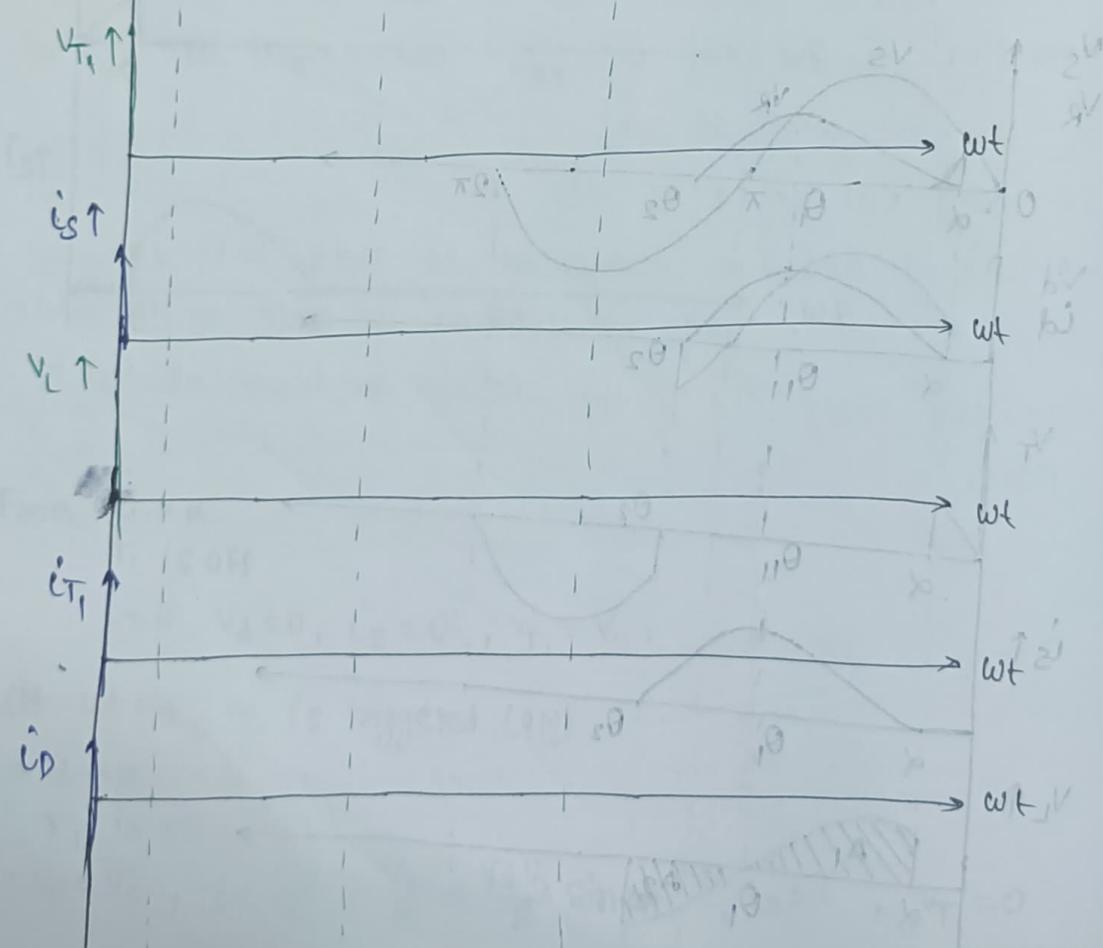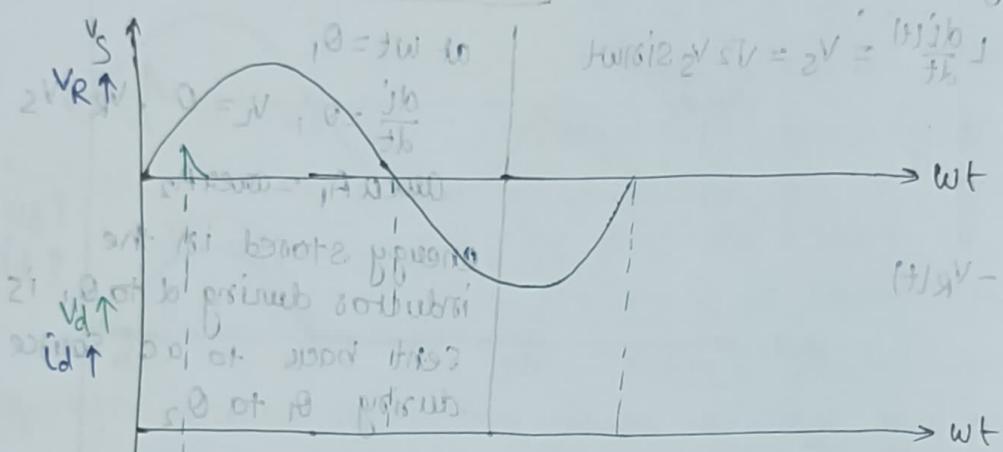
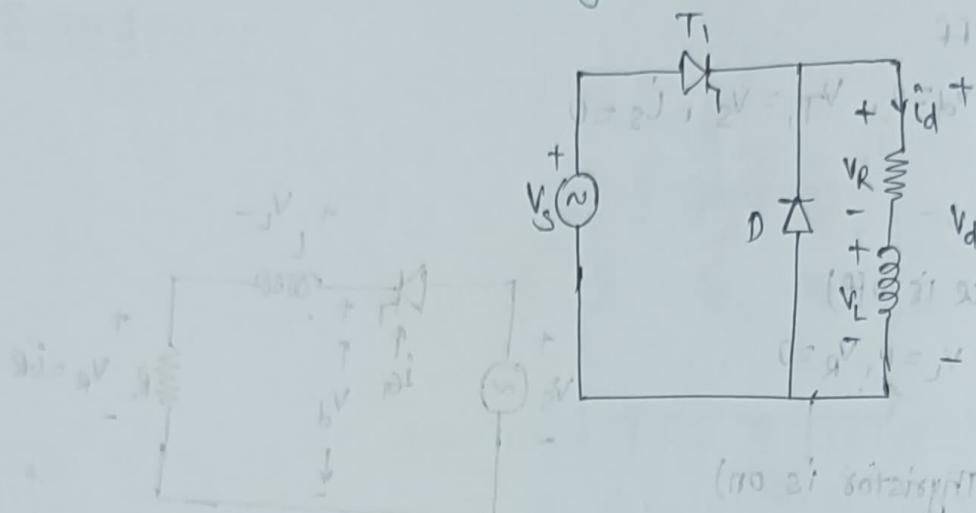
## \* R-L load with a freewheeling diode :-



\* L-E Load :-

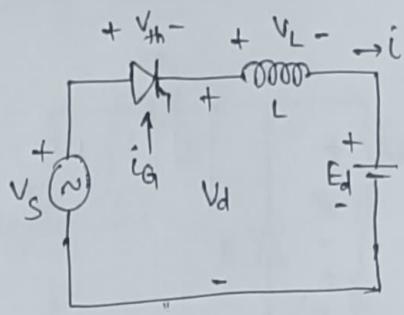


\* R-E Load :-

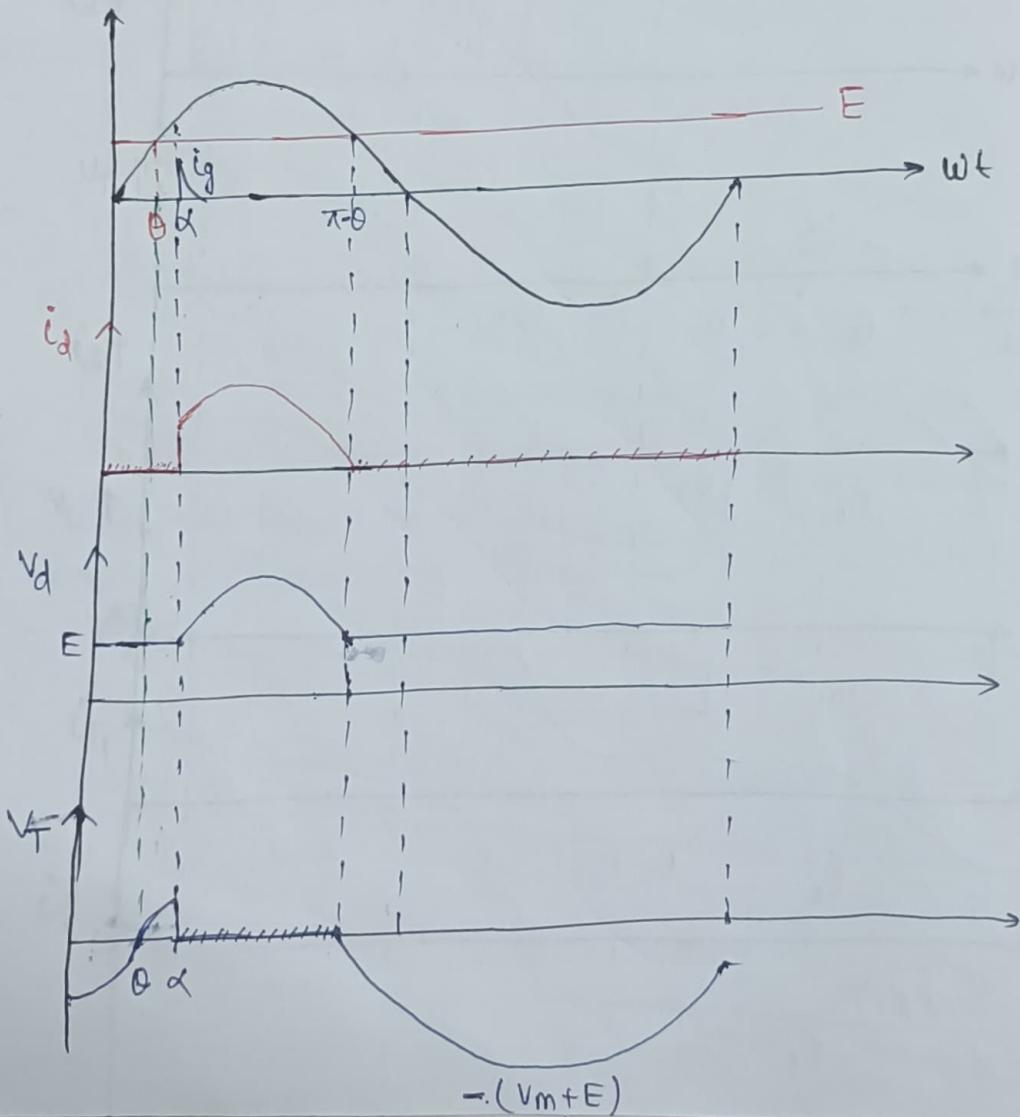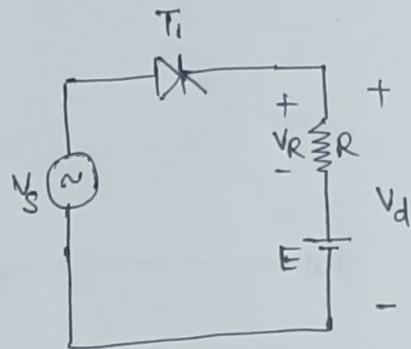

$$i_d = \frac{1}{w_L} \cdot \int (v_s - E_d) dwt$$



$$i_d = \frac{1}{\omega L} \left[ \int_{-\alpha}^{\beta} (V_m \sin \omega t d\omega t - E_d) \int_{-\alpha}^{\beta} d\omega t \right]$$

$$V_T = 0$$

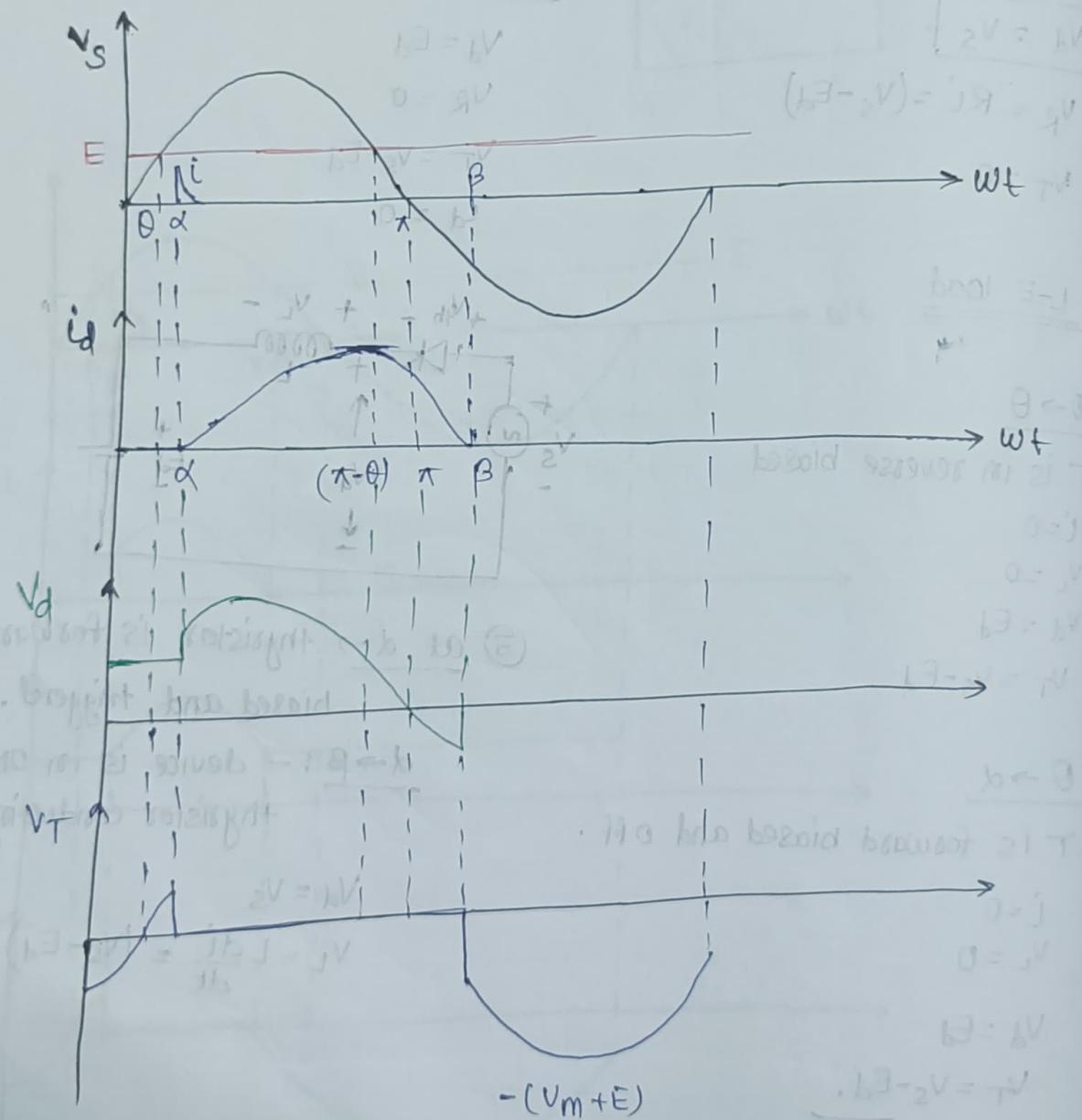

# \* Single-phase fully controlled bridge Rectifier :-

\* R-load

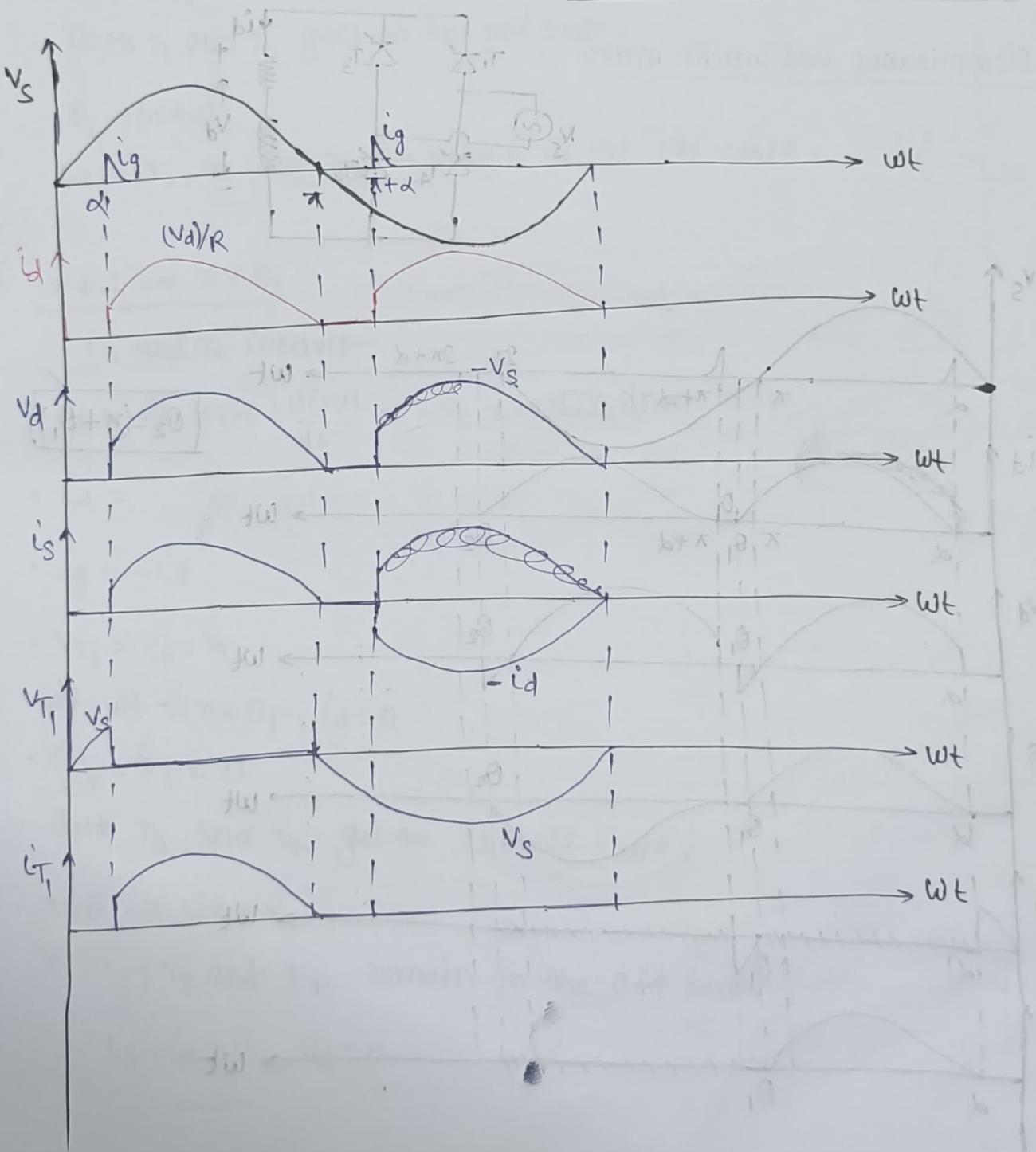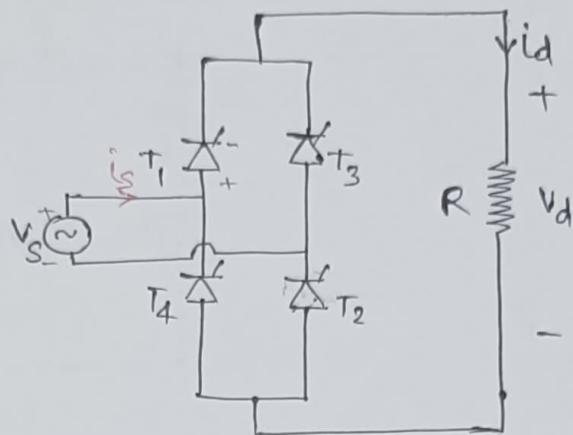

$0 \rightarrow \alpha$

↳ all devices are in off state.



$\alpha \rightarrow \pi$

$T_1$  and  $T_2$  gets turned on. book 2



\* R-L Load :-

• Discontinuous load current mode:-

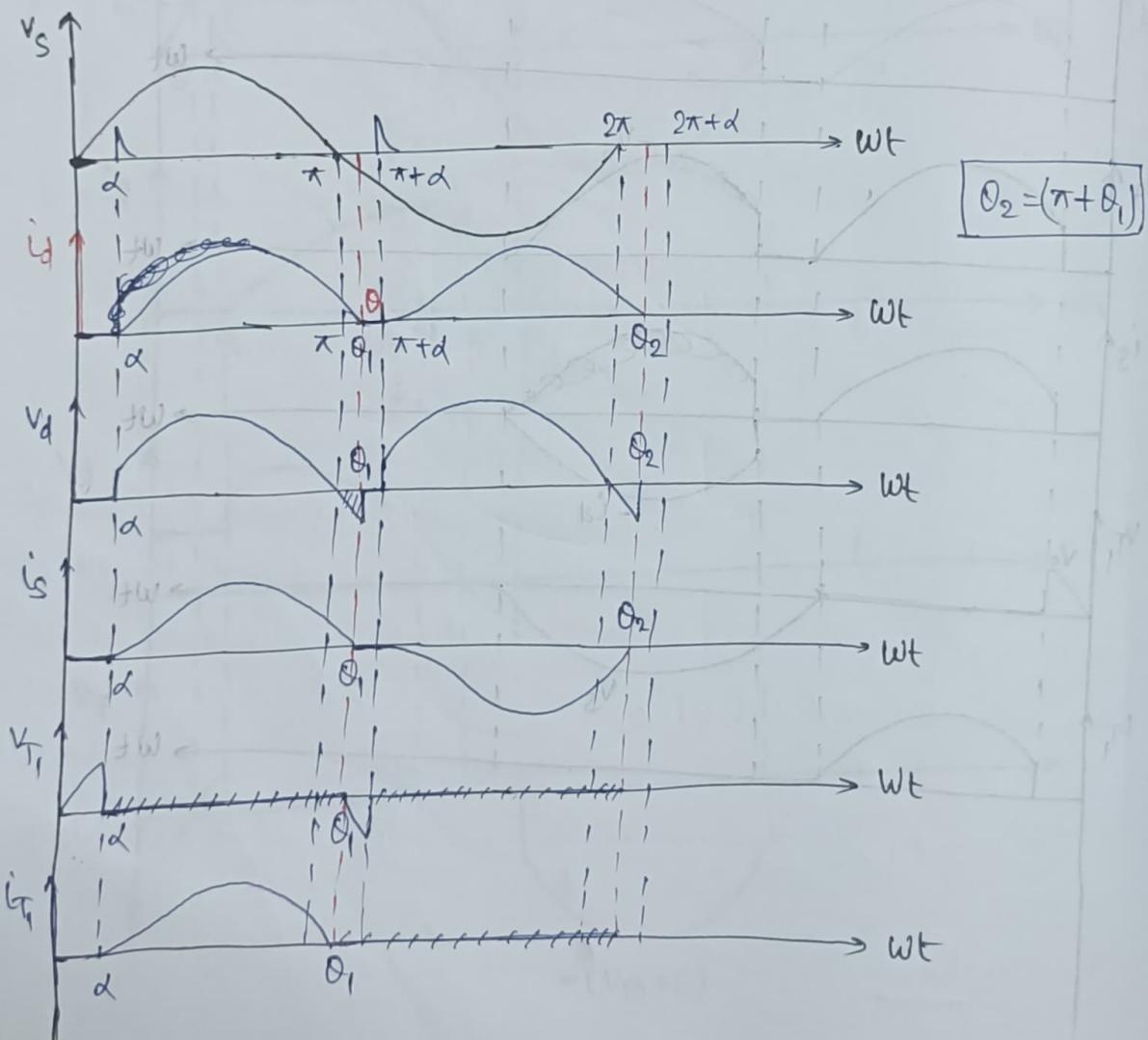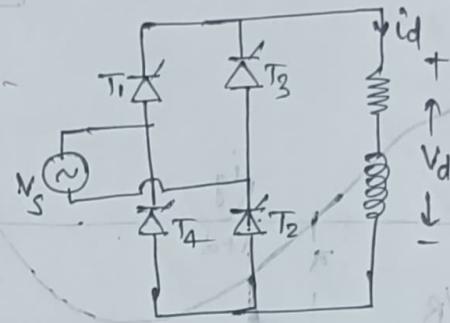

①  $\alpha \rightarrow 0_+$ ,  $T_1$  and  $T_2$  conduct

$$V_d = V_s = R(i_d(t)) + L \frac{di_d(t)}{dt} = \sqrt{2} V_s \sin \omega t$$

$$i_d =$$

$$i_s = i_d$$

$$V_{T_1} = 0, V_{T_2} = 0, V_{T_3} = -V_s$$

② at  $\omega t = \theta_1$ ,  $i_d \approx 0$

$$i_{T_1} = i_{T_2} = 0$$

Both  $T_1$  and  $T_2$  goes to the off state.

$$\theta_1 \rightarrow (\pi + \alpha)$$

$\hookrightarrow T_1, T_2, T_3$ , and  $T_4$  remain in the off state.

③  $\pi + \alpha \rightarrow \pi + \theta_1$

$T_3$  and  $T_4$  conduct

$$V_d = R(i_d(t)) + L \frac{di_d(t)}{dt} = -V_s = -\sqrt{2} V_s \sin \omega t$$

$$i_d =$$

$$i_s = -i_d$$

$$V_{T_1} = V_s = V_{T_2}$$

$$\text{at } \omega t = \pi + \theta_1, i_d \approx 0$$

$$i_{T_3} = i_{T_4} = 0$$



Both  $T_3$  and  $T_4$  go to the off state.

④  $\pi + \theta_1 \rightarrow 2\pi + \alpha$

$T_1, T_2, T_3$  and  $T_4$  remain in the off state.

$$i_s = i_d \approx 0, V_d \approx 0,$$

\* R-L load continuous current mode:-

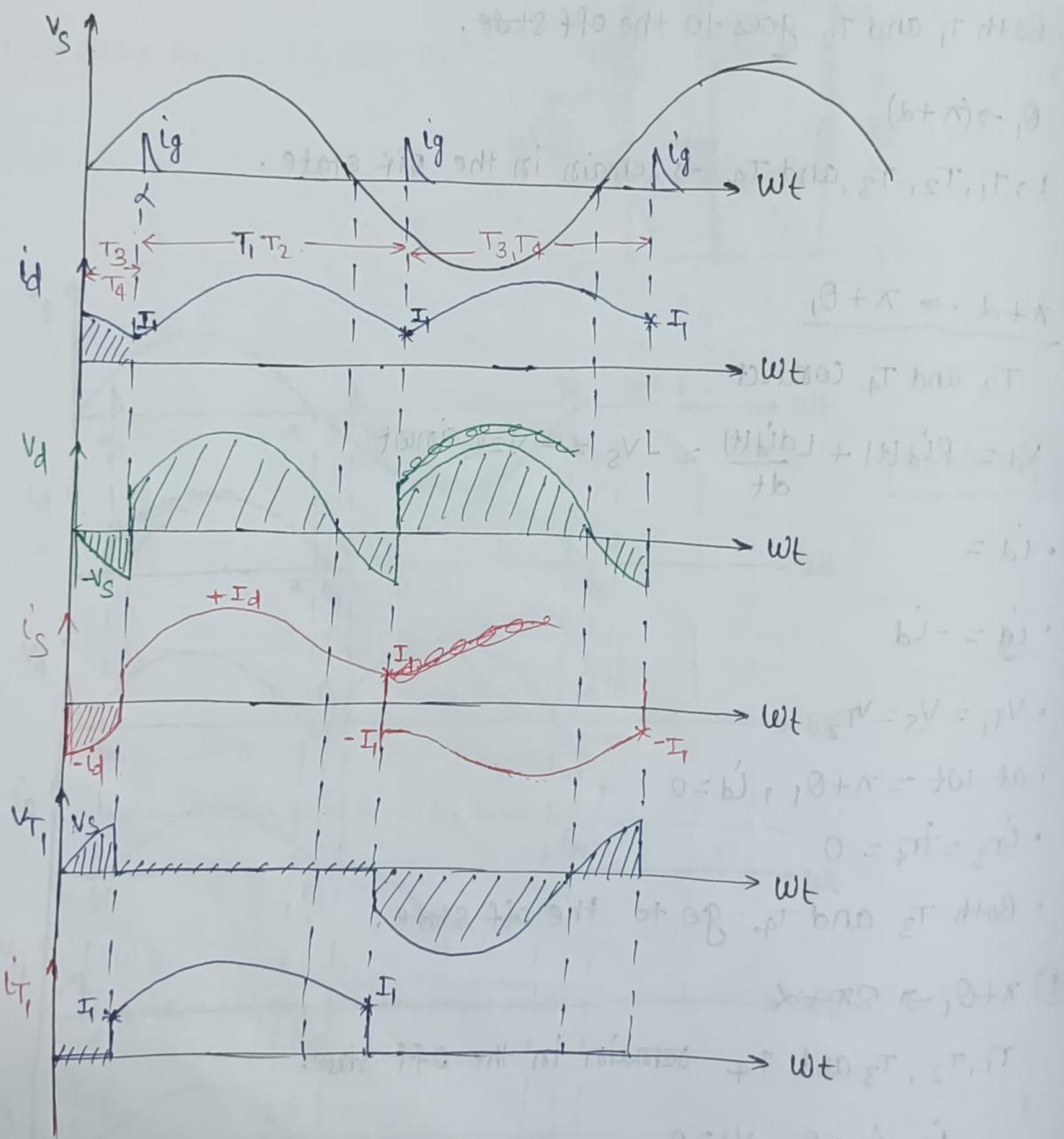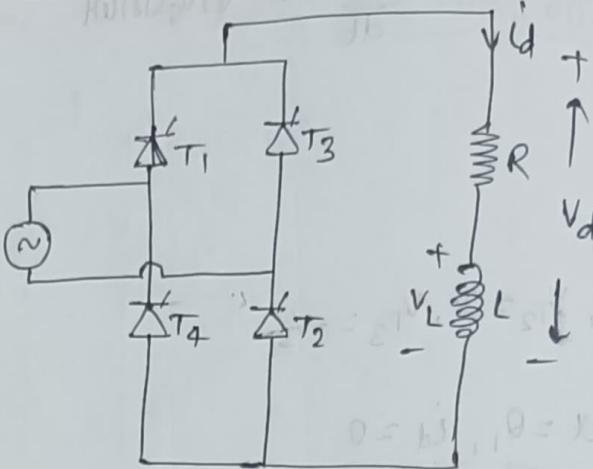

For  $wt < \alpha$ ,  $T_3$  and  $T_4$  were conducting

at  $wt = \alpha$ ,  $i_d = i_s (\neq 0)$

$T_1$  and  $T_2$  are turned on.

$T_3$  and  $T_4$  are line commutated

$\alpha \rightarrow (\pi + \alpha)$

$T_1$  and  $T_2$  conduct

$T_3$  and  $T_4 \rightarrow$  turned off.

$$V_d = V_s = \sqrt{2} V_{ss} \sin wt. = RI_d + L \frac{di_d}{dt}$$

@  $wt = \alpha$ ,  $i_d = I_s$

$$\Rightarrow RI_1 + L \frac{dI_d}{dt} \Big|_{wt=\alpha} = \sqrt{2} V_{ss} \sin \alpha.$$

$$i_d = \text{---}$$

$$\therefore i_s = i_d$$

$$V_{T_3} = -V_s = V_{T_4}$$

at  $\pi + \alpha$ ,  $T_3$  and  $T_4$  are turned on

$T_1$  and  $T_2$  are line commutated.

$(\pi + \alpha) \rightarrow (2\pi + \alpha)$



$T_3$  and  $T_4$  conduct

$$V_d = -V_s$$

$$i_s = -i_d$$

$$V_{T_1} = V_{T_2} = V_s$$

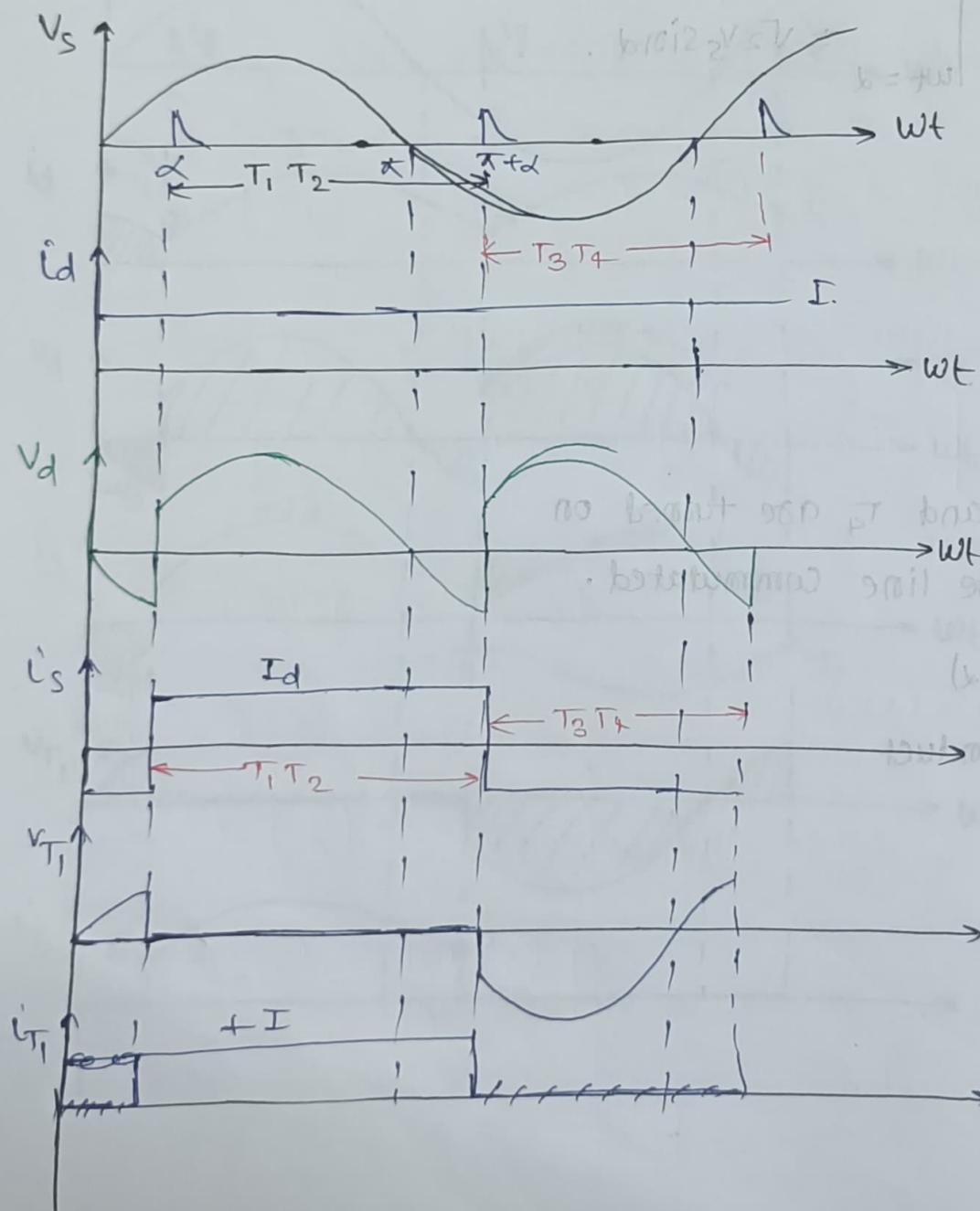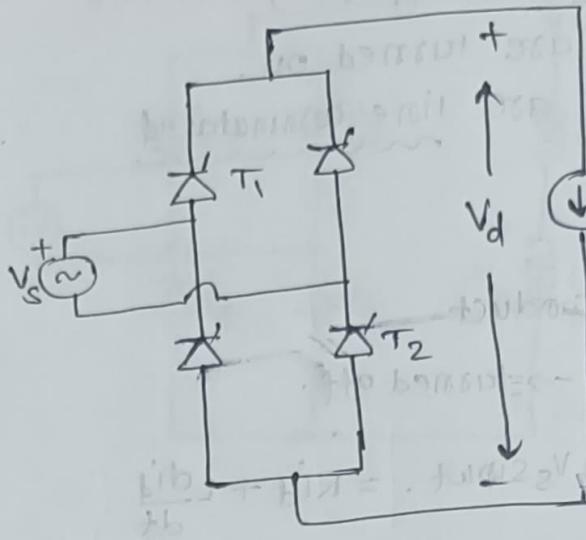\* R-L Load, constant load current  $I_d$  :-



$$\cdot d \rightarrow \pi + d$$

$T_1$  and  $T_2$  conduct.

$T_3$  and  $T_4$  are line commutated.

$$V_d = V_s$$

$$i_s = i_d$$

$$v_{T_3} = -v_s = v_{T_4}$$

$$\cdot \pi + d \text{ to } 2\pi + d$$

$T_3$  and  $T_4$  conduct

$T_1$  and  $T_2$  are line commuted

$$v_d = -v_s$$

$$i_s = -i_d$$

$$v_{T_1} = v_s = v_{T_2}$$

\* Performance parameters:-

\* DC side

$$\cdot (V_d)_{avg.} = \frac{1}{\pi} \int_{\alpha}^{\pi+d} (V_m \sin \omega t) d\omega t$$

$$= \frac{2 V_m}{\pi} \cos \alpha = \frac{2 \sqrt{2} V_s \cos \alpha}{\pi} = 0.9 V_s \cos \alpha$$

$$\cdot (V_d)_{rms} = \left[ \frac{1}{\pi} \int_{\alpha}^{\pi+d} (V_m^2 \sin^2 \omega t) d\omega t \right]^{\frac{1}{2}} = V_s$$

$$= \left[ \frac{V_m^2}{\pi} \left[ \int \left( \frac{1 - \cos 2\omega t}{2} \right) d\omega t \right] \right]^{\frac{1}{2}}$$

\* Avg. power through converter

$$(P_d)_{avg} = (V_d)_{avg} I_d = 0.9 V_s I_d \cos \alpha$$

\* Ripple freqn = 2 \* (line freqn)

\* Voltage Ripple factor  $K_v =$

$$\sqrt{\frac{(V_d)_{rms}^2 - (V_d)_{avg}^2}{(V_d)_{avg}^2}}$$

$$= \sqrt{\frac{(V_d)_{rms}^2}{(V_d)_{avg}^2} - 1} = \sqrt{0.21}$$

$$\begin{aligned} i_s(t) &= a_0 + \sum_{n=1,2,3,\dots}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t \quad (a_0 = 0) \\ i_s(t) &= \sum_{n=1}^{\infty} c_n \sin(n\omega t + \phi_n) \quad ; \quad c_n = \sqrt{a_n^2 + b_n^2} \\ \phi_n &= \tan^{-1}\left(\frac{a_n}{b_n}\right) \end{aligned}$$

$$i_{s1}(t) = g \sin(\omega t + \phi_1) \quad ; \quad g = \sqrt{a_1^2 + b_1^2}$$

$$a_1 = \frac{1}{\pi} \left[ \int_{\alpha}^{\pi+\alpha} I_d \cos \omega t d\omega t + \int_{\pi+\alpha}^{2\pi+\alpha} -I_d \cos \omega t d\omega t \right]$$

$$\begin{aligned} &= \cancel{\left[ I_d (\sin(\alpha) - \sin(2\pi+\alpha)) \right]} + I_d \left( \sin(2\pi+\alpha) - \sin(\pi+\alpha) \right) \\ &= \frac{4I_d}{\pi} \end{aligned}$$

$$= \frac{1}{\pi} \left[ I_d (\sin(\pi+\alpha) - \sin(\alpha)) - I_d (\sin(2\pi+\alpha) - \sin(\pi+\alpha)) \right]$$

$$= -\frac{4I_d}{\pi} \sin \alpha$$

$$b_1 = \frac{1}{\pi} \left[ \int_{\alpha}^{\pi+\alpha} I_d \sin \omega t d\omega t + \int_{\pi+\alpha}^{2\pi+\alpha} -I_d \sin \omega t d\omega t \right] = \frac{4I_d}{\pi} \cos \alpha$$

$$\therefore g = \sqrt{\left(\frac{4I_d}{\pi}\right)^2 (\sin^2 \alpha + \cos^2 \alpha)}$$

$$g = \frac{4I_d}{\pi}$$

$$\phi_1 = +\tan^{-1}\left(\frac{a_1}{b_1}\right) = -\alpha$$

$$\boxed{\therefore i_{s1} = \frac{4I_d}{\pi} \cdot \sin(\omega t - \alpha)}$$

$$\bullet \text{RMS value of } i_{s1} \Rightarrow \left(\frac{2\sqrt{2}I_d}{\pi}\right)$$



RMS value of  $n^{\text{th}}$  harmonics  $\Rightarrow$   $I_{sh} = \left( \frac{|I_s|}{n} \right)$

$$n = 3, 5, 7, 11, 13, 15, \dots$$

RMS value of total source current is

$$I_S = I_d$$

$$I_{sh} = \begin{cases} 0 & \text{for even value of } h \\ \frac{|I_s|}{h} & \text{for odd value of } h \end{cases}$$

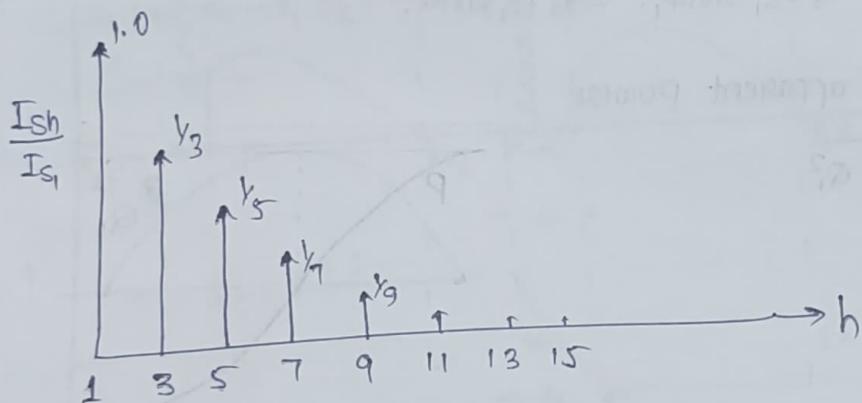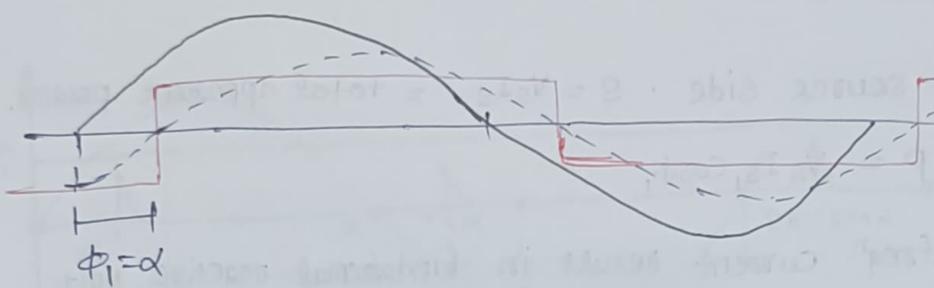

Harmonic spectrum.

$$\text{Total harmonic distortion THD} = \sqrt{\frac{I_s^2 - I_{SI}^2}{I_{SI}^2}} = \sqrt{\frac{\frac{\pi^2}{8} - \frac{28\pi^2}{8}}{\frac{\pi^2}{8}}} = \sqrt{\left(\frac{\pi^2}{8} - 1\right)} = 0.4843 = \underline{\underline{48.43\%}}$$


- Displacement factor  $DF = \cos(-\alpha) = \cos \alpha$ .
- AC side power factor  $= \frac{\text{Actual power}}{\text{Apparent power}} = \frac{V_S I_S \cos \phi}{V_S I_S} = \frac{(2\sqrt{2} I_d) \cos \alpha}{2\sqrt{2}} = 0.9 \cos \alpha$

- Power at the source side  $S = V_S I_S$  = total apparent power.
- Active power  $P = V_S I_S \cos \phi$ ,

↳ Fundamental freqn current result in fundamental reactive volt amperes —  $Q_1 = V_S I_S \sin \phi_1 = V_S I_S \sin \alpha$ .

↳ Fundamental freqn apparent power

- $S_1 = V_S I_S = \sqrt{P^2 + Q_1^2}$

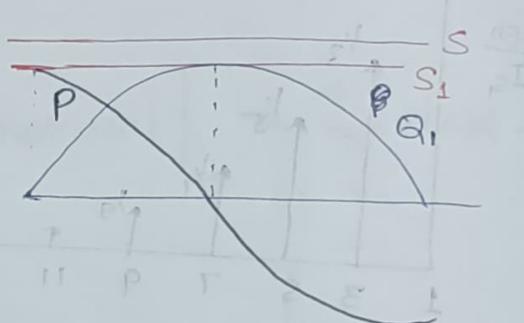

- $(V_d)_{avg \alpha} = \text{Avg. o/p voltage for a triggering angle } \alpha$ .

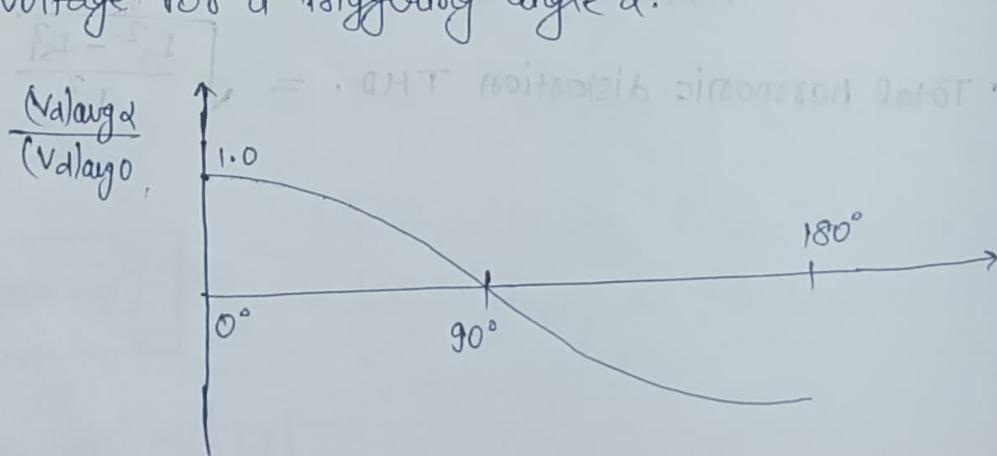




fig. - Normalized  $V_d$  as a function of  $\alpha$ .

06/10/23
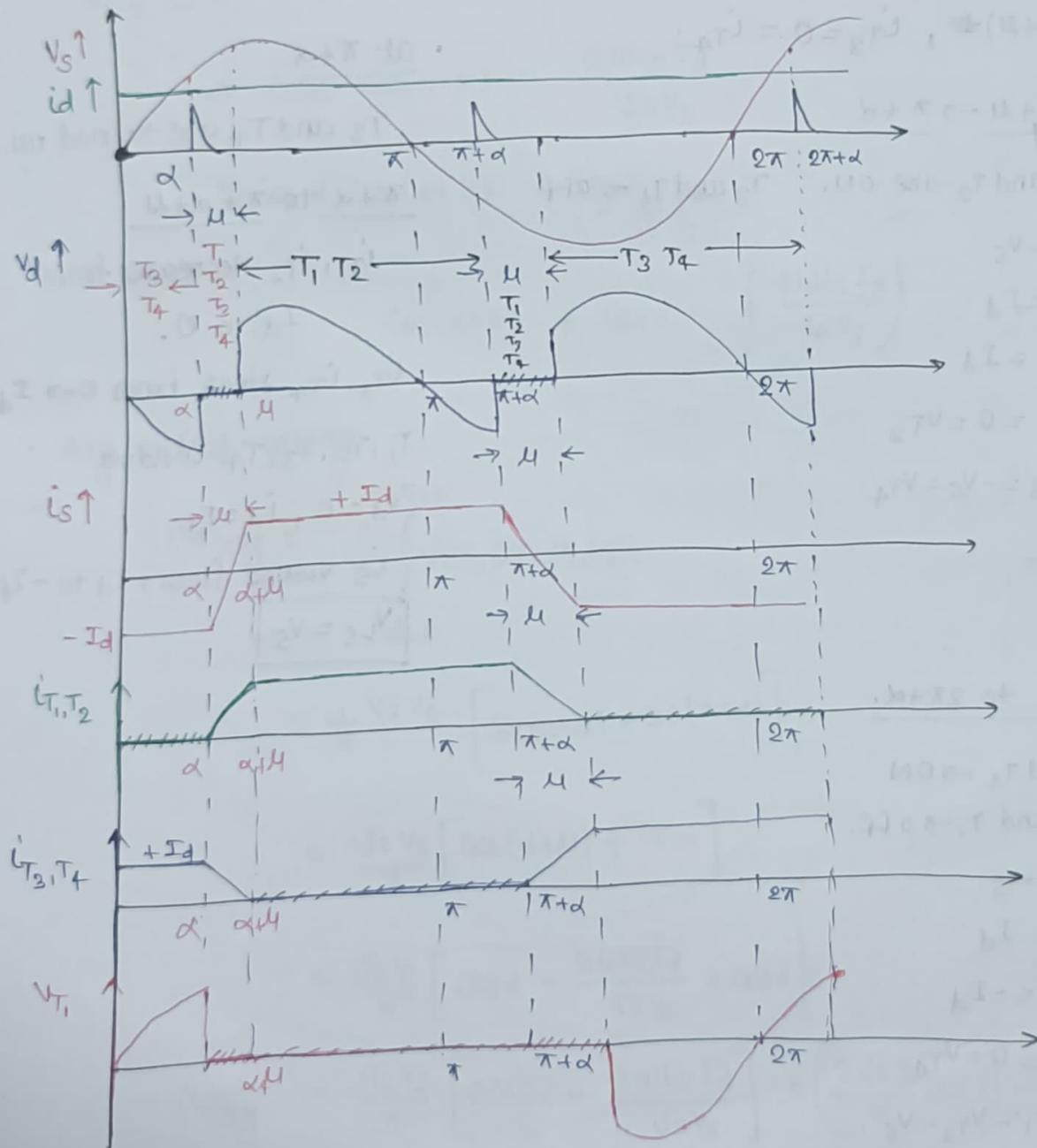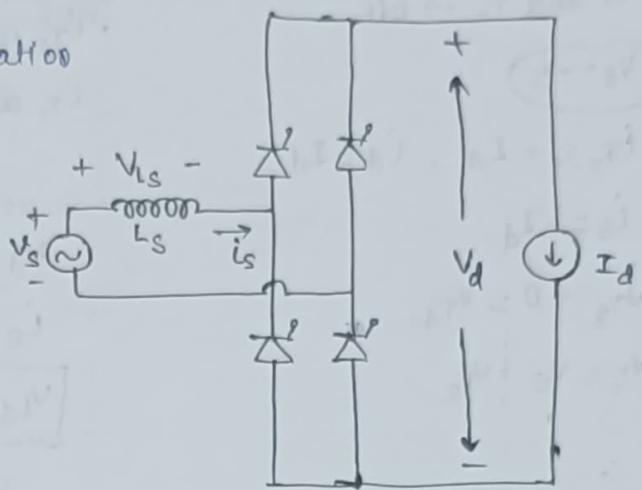
## \* Effect of source inductance:-

- Constant load current  $I_d$ .

↳ The current commutation takes a finite time called  $\alpha$  (or) commutation interval.



dealing 0 to  $\alpha$

$T_3$  and  $T_4 \rightarrow ON$

$T_1$  and  $T_2 \rightarrow OFF$

$$V_d = -V_s$$

$$i_{T_3, T_4} = I_d, i_d \leq I_d$$

$$i_s = -I_d$$

$$V_{T_3} = 0 = V_{T_4}$$

$$V_{T_1} = V_s = V_{T_2}$$

$$V_{L_S} = 0$$

at  $d$ ,  $T_1$  and  $T_2$  are turned ON

$$d \rightarrow d+u$$

$i_{T_3}$  and  $i_{T_4}$  decreases from  $I_d$  to 0

$i_{T_1}$  and  $i_{T_2}$  rise from 0 to  $I_d$

$T_1, T_2, T_3, T_4$  are ON.

$$V_d = 0, i_d = I_d$$

$i_s$  varies from  $-I_d$  to  $I_d$ .

$$V_{L_S} = V_s$$

• At  $(\alpha+u)$ ,  $i_{T_3} = 0 = i_{T_4}$

from  $d+u \rightarrow \pi+\alpha$

$T_1$  and  $T_2$  are ON.  $T_3$  and  $T_4 \rightarrow OFF$

$$V_d = V_s$$

$$i_d = I_d$$

$$i_s = I_d$$

$$V_{T_1} = 0 = V_{T_2}$$

$$V_{T_3} = -V_s = V_{T_4}$$

$$V_{L_S} = 0$$

$T_3$  and  $T_4$  are turned ON

$\pi+\alpha$  to  $\pi+\alpha+u$

$i_{T_1}, i_{T_2}$  decreases from  $I_d$  to 0.

$i_{T_3}, i_{T_4}$  rises from 0 to  $I_d$

$T_1, T_2, T_3, T_4$  conduct

$$V_d = 0, i_d = I_d$$

$i_s$  varies from  $+I_d$  to  $-I_d$

$$V_{L_S} = V_s$$

$\pi+\alpha+u$  to  $2\pi+\alpha$

$T_3$  and  $T_4 \rightarrow ON$

$T_2$  and  $T_1 \rightarrow OFF$

$$V_d = -V_s$$

$$i_d = I_d$$

$$i_s = -I_d$$

$$V_{T_3} = 0 = V_{T_4}$$

$$V_{T_1} = V_{T_2} = V_s$$

$$V_{L_S} = 0$$

during the commutation period  $\alpha$ ,  $T_1, T_2, T_3$  and  $T_4$  are ON.

$$V_{LS} = V_S$$

$$\sqrt{2}V_S \sin \omega t = L_S \frac{d(i_S(t))}{dt} = \omega L_S \frac{d(i_S(t))}{d\omega t}$$

$$\frac{\sqrt{2}V_S}{\omega L_S} \sin \omega t d\omega t = d(i_S(t))$$

integrate both sides from  $\alpha$  to  $\alpha + \mu$

$$\int_{\alpha}^{\alpha+\mu} \frac{\sqrt{2}V_S}{\omega L_S} \sin \omega t d\omega t = \left[ i_S(t) \right]_{\alpha}^{\alpha+\mu} = I_d - I_d$$

$$\frac{\sqrt{2}V_S}{\omega L_S} \left[ \cos(\alpha) - \cos(\alpha + \mu) \right] = 2I_d$$

$$\Rightarrow \cos \alpha - \cos(\alpha + \mu) = \frac{2\omega L_S I_d}{\sqrt{2}V_S}$$

$$\Rightarrow \cos \alpha - \cos(\alpha + \mu) = \left( \frac{2\omega L_S I_d}{\sqrt{2}V_S} \right)$$

$$\Rightarrow \cos(\alpha + \mu) = \cos \alpha - \left( \frac{2\omega L_S I_d}{\sqrt{2}V_S} \right)$$

Avg. output voltage

$$(V_d)_{avg.} = \frac{1}{\pi} \int_{\alpha}^{\pi + \alpha} \sqrt{2}V_S \sin \omega t d\omega t$$


$$= \frac{1}{\pi} \sqrt{2}V_S \left[ \cos(\alpha + \mu) - \cos(\pi + \alpha) \right]$$

$$= \frac{\sqrt{2}V_S}{\pi} \left[ \cos(\alpha + \mu) + \cos \alpha \right]$$

$$= \frac{\sqrt{2}V_S}{\pi} \left[ \cos \alpha - \frac{2\omega L_S I_d}{\sqrt{2}V_S} + \cos \alpha \right]$$


$$(V_d)_{avg.} = \frac{\sqrt{2}V_S}{\pi} \left[ 2\cos \alpha - \frac{2\omega L_S I_d}{\sqrt{2}V_S} \right] = \left( \frac{2\sqrt{2}V_S}{\pi} \cos \alpha \right) - \left( \frac{2\omega L_S I_d}{\pi} \right)$$

## \* Practical Thyristor Converters :-

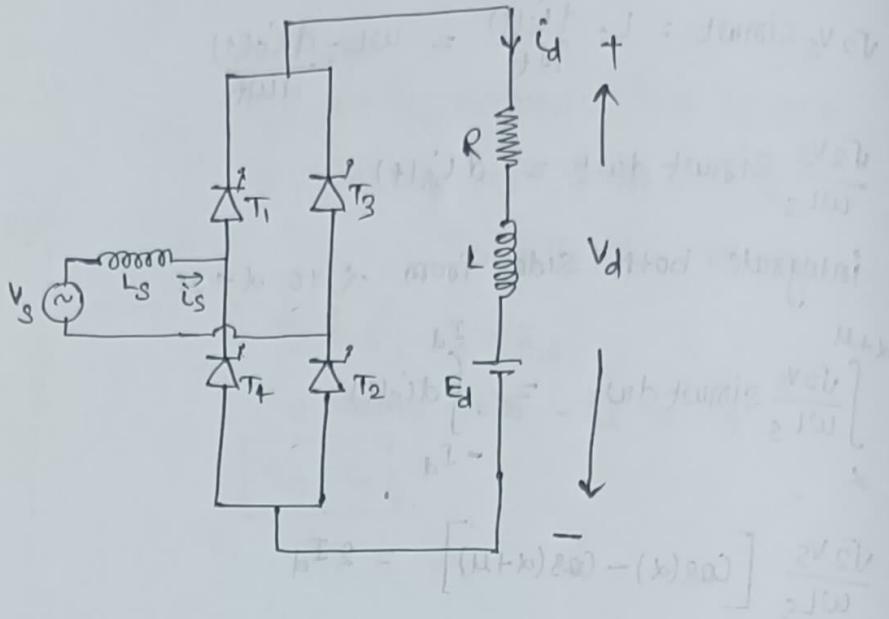

- Shape of the load current depends on the load parameters and firing angle.

### ① Discontinuous load current mode :-

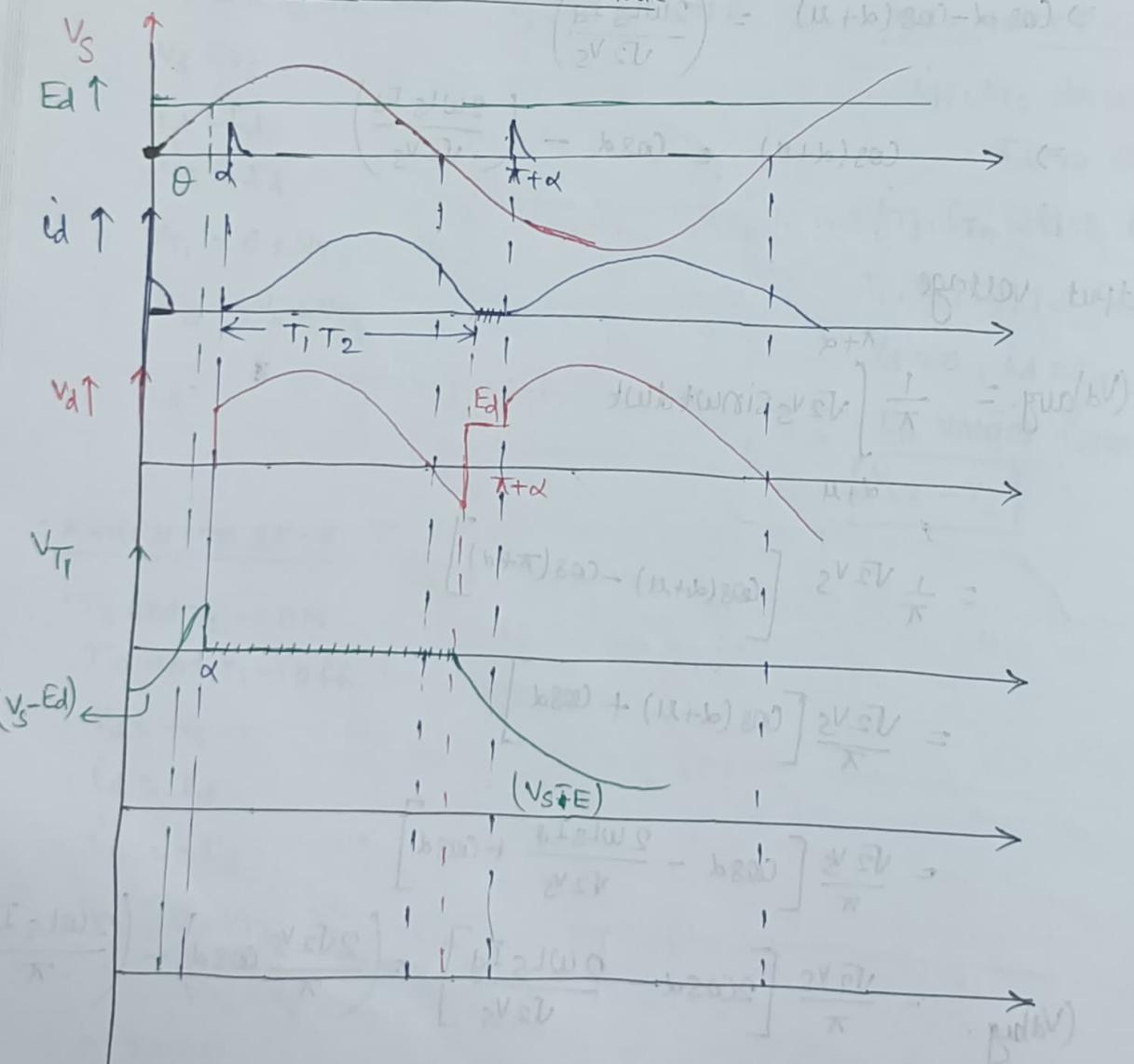

When  $T_1$  and  $T_2$  are conducting,

$$i_d(wt) = \frac{\sqrt{2}V_S}{Z} \sin(wt - \phi) - \frac{Ed}{R} + K e^{-\frac{R}{L}t}$$

at  $wt = d$ ,  $i_d = 0$

$$Z = \sqrt{R^2 + w^2 L^2}$$

$$0 = \frac{\sqrt{2}V_S}{Z} \sin(\alpha - \phi) - \frac{Ed}{R} + K e^{-\frac{R}{L}\frac{d}{w}} \quad \phi = \tan^{-1}\left(\frac{wL}{R}\right)$$


$$\therefore K = \left\{ \frac{Ed}{R} - \frac{\sqrt{2}V_S}{Z} \sin(\alpha - \phi) \right\} \cdot e^{\frac{Rd}{Lw}}$$

$$\boxed{m = \left( \frac{Ed}{\sqrt{2}V_S} \right)}$$

$$\text{Q12} \quad i_d(wt) = \frac{\sqrt{2}V_S}{Z} \sin(wt - \phi) - \frac{Ed}{R} + \left\{ \frac{Ed}{R} - \frac{\sqrt{2}V_S}{Z} \sin(\alpha - \phi) \right\} e^{\frac{Rd}{Lw}}$$

$$= \frac{\sqrt{2}V_S}{Z} \sin(wt - \phi) - \frac{Ed}{R} + \left\{ \frac{Ed}{R} - \frac{\sqrt{2}V_S}{Z} \sin(\alpha - \phi) \right\} e^{\frac{R(d-w)}{Lw}}$$

## 2. Continuous Current mode:-

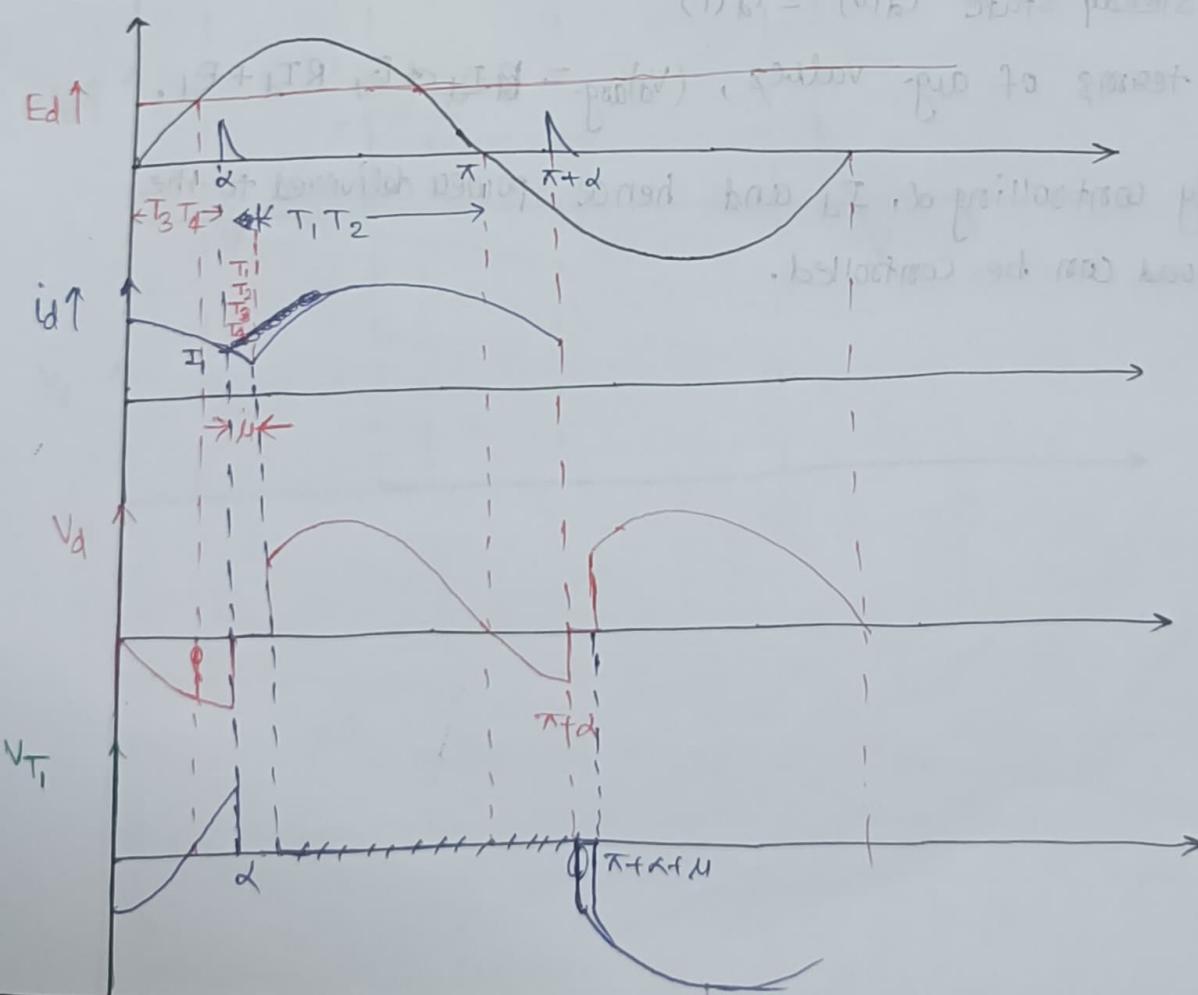

• Avg. value of  $v_d$  is approximately  $\rightarrow$

$$(v_d)_{avg} \approx \frac{2\sqrt{2}V_s}{\pi} \cos \alpha - \frac{2\omega L s(i_d)_{min}}{\pi}$$

↳  $(i_d)_{min}$  is min<sup>m</sup>. value of  $i_d$  that occurs at  $wt = \alpha$ .  
instantaneous value of load voltage —

$$(v_d) = R \cdot i_d + L \cdot \frac{di_d}{dt} + E_d$$


$$\frac{1}{T} \int_0^T v_d dt = \frac{R i_d}{T} \int_0^T i_d dt + \frac{L}{T} \int_0^T di_d + E_d$$

$$\left( \frac{1}{T} \int_0^T v_d dt \right) = \left( \frac{1}{T} \int_0^T \left( R i_d + L \frac{di_d}{dt} + E_d \right) dt \right)$$



• in steady state  $i_d(0) = i_d(T)$

• in terms of avg. values,  $(v_d)_{avg} = R i_d + E_d$ .

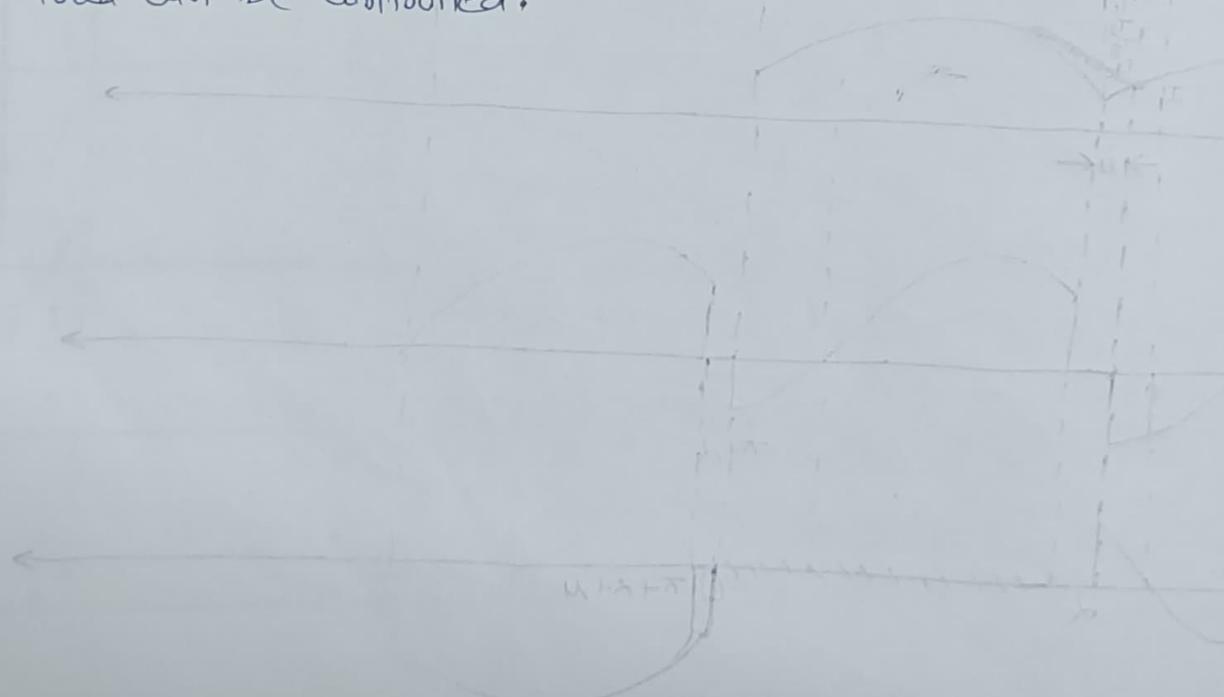↳ By controlling  $\alpha$ ,  $I_d$  and hence power delivered to the load can be controlled.





\* Inverter mode of rectifier Bridge :-

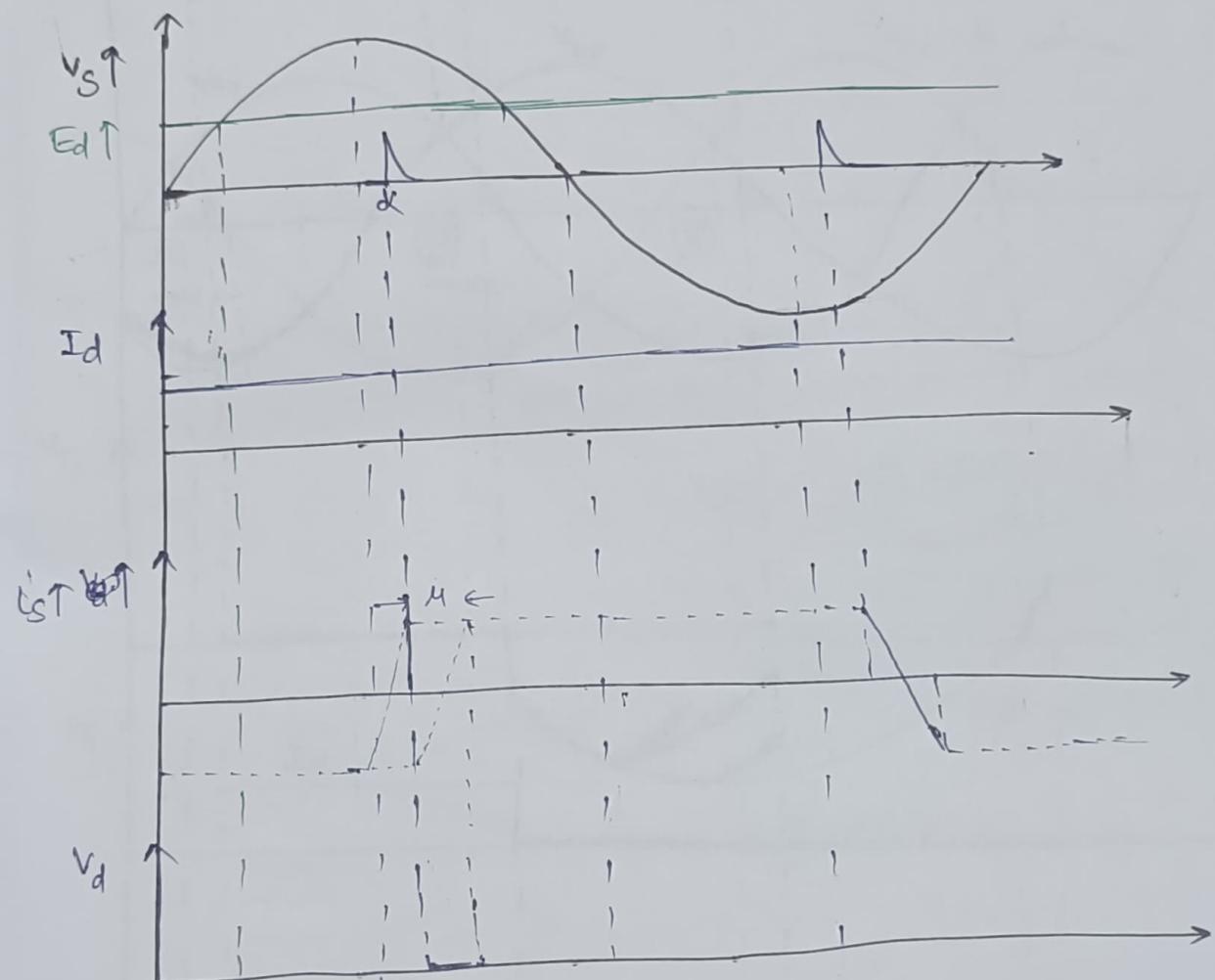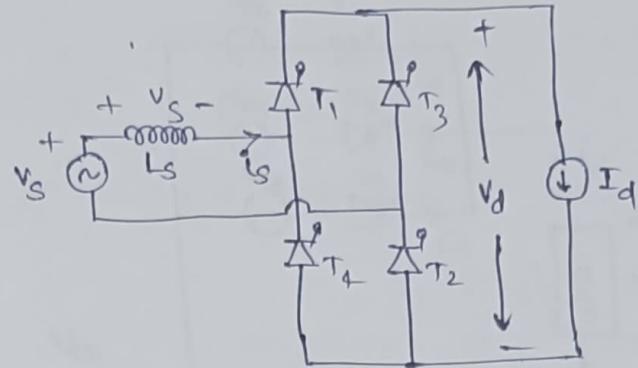

## \* Three-phase half wave controlled Rectifier:-

$i_d \rightarrow \text{constant.}$

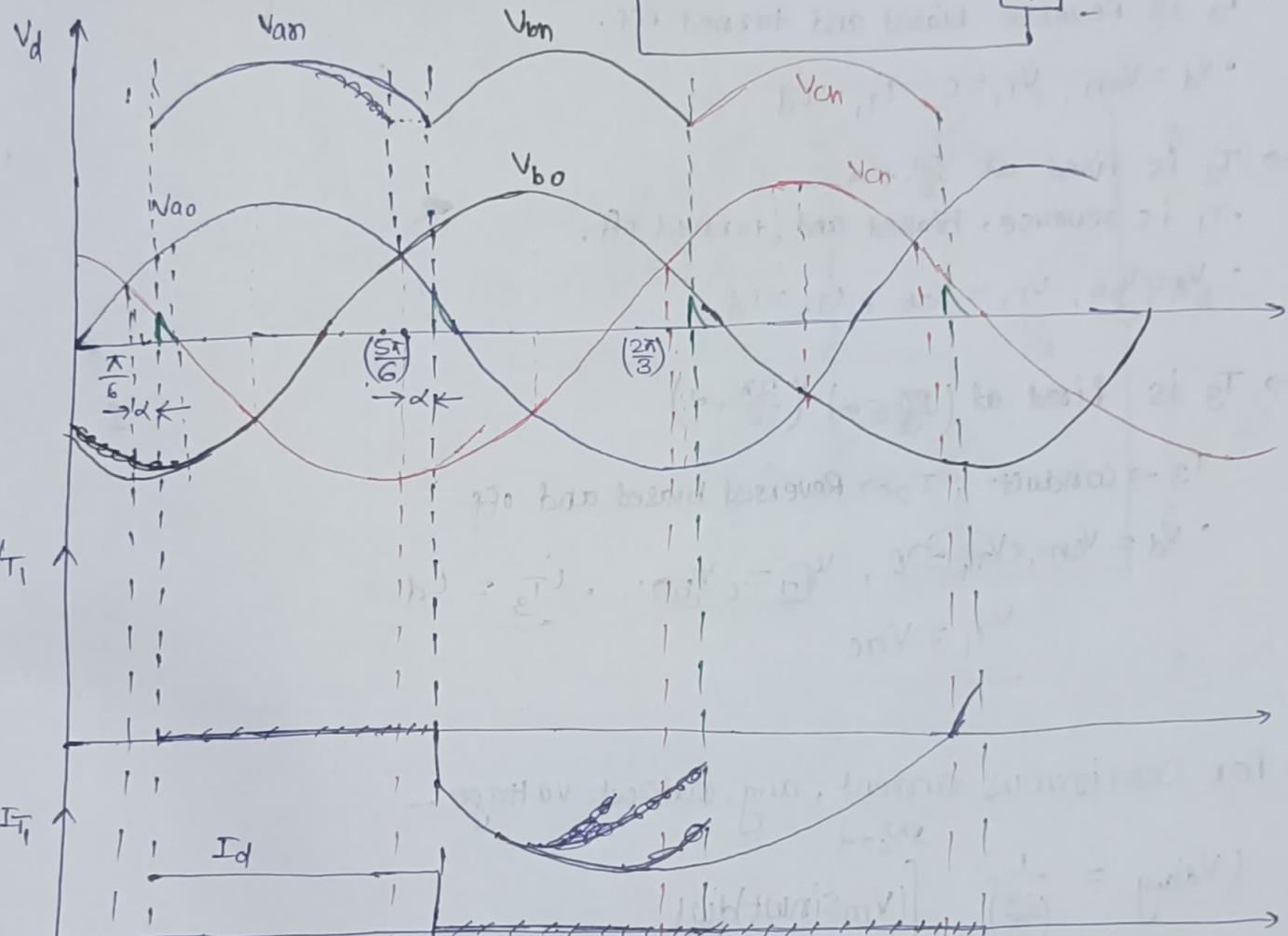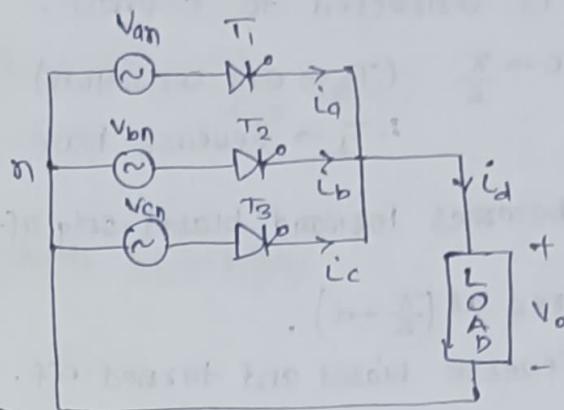

Initially let  $T_3$  alone is in on state  
so load is connected to c-phase.  
during  $0 \rightarrow \frac{\pi}{6}$  ( $T_3 \rightarrow \text{ON condition}$ )  
 $\therefore T_1 \rightarrow \text{Reverse bias} (\because V_{cn} > V_{an})$ .

So,  $T_1$  becomes forward biased only after  $\frac{\pi}{6}$ . (So gate signal provided after  $\frac{\pi}{6}$ ).  
 $T_1$  is fired at  $(\frac{\pi}{6} + \alpha)$ .

$T_3$  is Reverse biased and turned off.

$$\cdot V_d = V_{an}, V_{T_1} = 0, i_{T_1} = i_d$$

$T_2$  is fired at  $\frac{5\pi}{6} + \alpha$

$T_1$  is reverse biased and turned off.

$$\cdot V_d = V_{bn}, V_{T_1} = V_{ab}, i_{T_2} = i_d$$

$T_3$  is fired at  $(\frac{2\pi}{3} + \alpha) (\frac{3\pi}{2} + \alpha)$

$T_3 \rightarrow \text{conduct}, T_2 \rightarrow \text{Reversed biased and off}$

$$\cdot V_d = V_{cn}, V_{T_2} = V_{bo}, V_{T_3} = V_{ac}, i_{T_3} = i_d$$

For continuous current, avg. output voltage:-

$$(V_{d\text{avg.}} = \frac{1}{(\frac{2\pi}{3})} \int_{(\frac{\pi}{6} + \alpha)}^{(\frac{5\pi}{6} + \alpha)} (V_m \sin \omega t) d\omega t$$

$$= \frac{3}{2\pi} \left[ V_m \left\{ \cos \left( \frac{\pi}{6} + \alpha \right) - \cos \left( \frac{5\pi}{6} + \alpha \right) \right\} \right]$$

$$= \frac{3V_m}{2\pi} \left[ \cos \left( \frac{\pi}{6} \right) \cdot \cos \alpha - \sin \left( \frac{\pi}{6} \right) \cdot \sin \alpha - \cos \left( \frac{5\pi}{6} \right) \cdot \cos \alpha + \sin \left( \frac{5\pi}{6} \right) \cdot \sin \alpha \right]$$


$$= \frac{3V_m}{2\pi} \left[ \frac{\sqrt{3}}{2} \cos \alpha - \frac{1}{2} \sin \alpha - \left( -\frac{\sqrt{3}}{2} \cos \alpha \right) + \frac{1}{2} \sin \alpha \right]$$

$$= \frac{3V_m}{2\pi} [\sqrt{3} \cos \alpha]$$

$$= \frac{3\sqrt{3} V_m}{2\pi} \cos \alpha = \frac{3\sqrt{3} V_s}{2\sqrt{2}\pi} \cos \alpha = \frac{3V_L}{\sqrt{2}\pi} \cos \alpha.$$


### Three-phase Controlled Fullwave Rectifiers

constant load current.

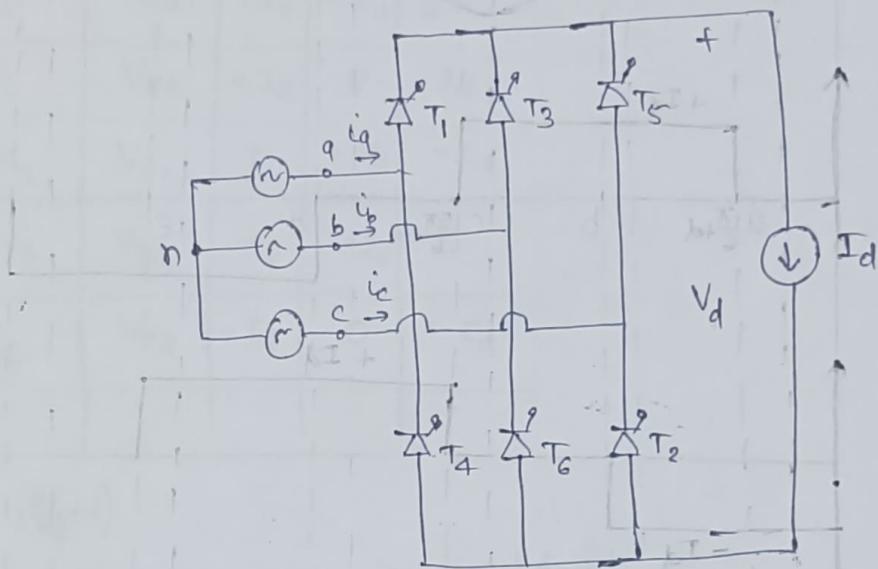

bI+

bI-

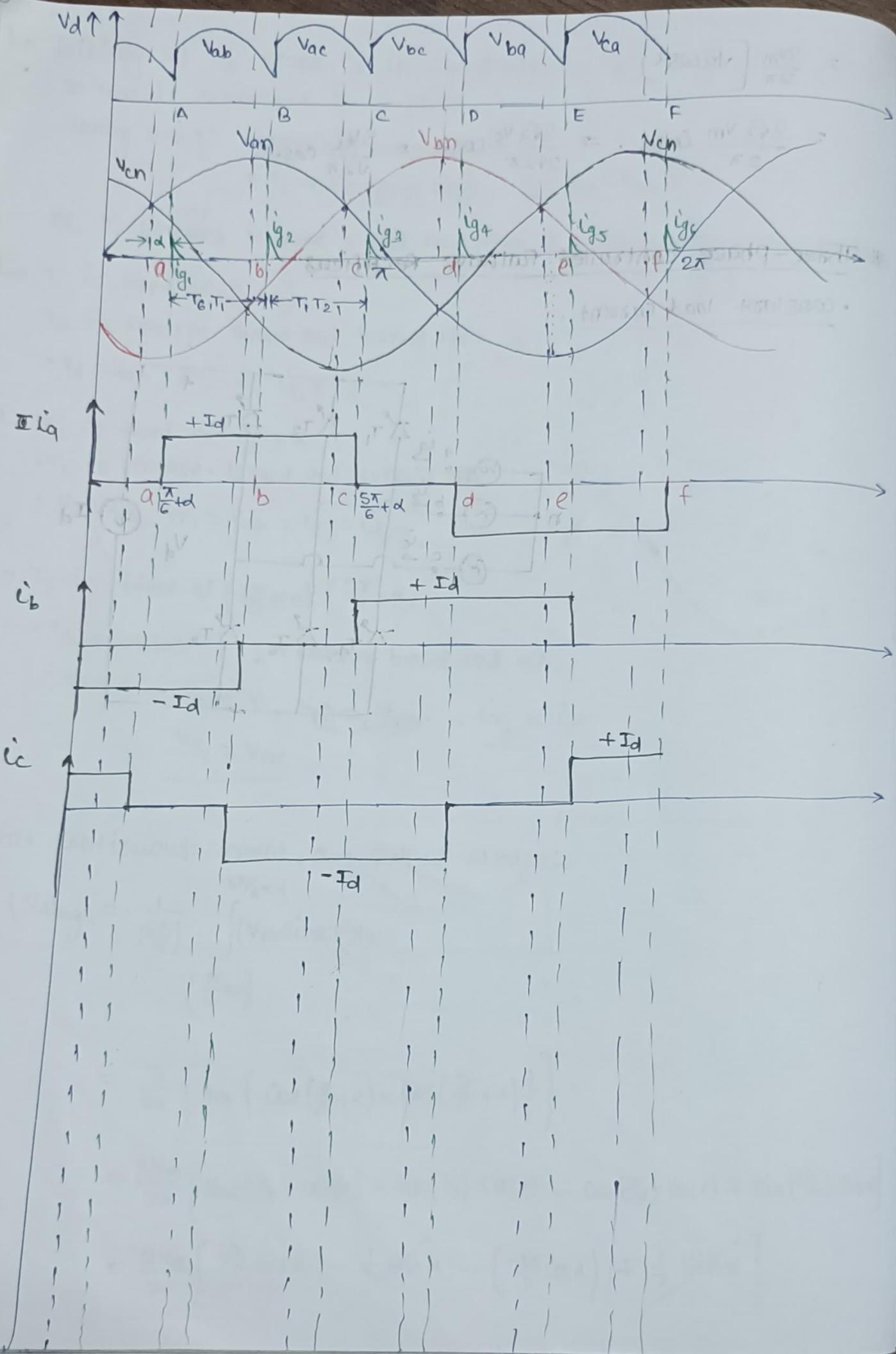

- constant load current.
- earliest instant at which  $T_1$  can be turned on is at  $\pi/6$
- Hence  $\alpha$  is measured from  $\pi/6$ .

(at point b, c phase is most negative so we give  $i_g$  to turn on the  $T_2$ .)  
 say for every  $T$ ,

| Interval          | Devices    | $V_d$    | $i_a$  | $i_b$  | $i_c$  |
|-------------------|------------|----------|--------|--------|--------|
| $A \rightarrow B$ | $T_6, T_1$ | $V_{ab}$ | $+I_d$ | $-I_d$ | 0      |
| $B \rightarrow C$ | $T_1, T_2$ | $V_{ac}$ | $+I_d$ | 0      | $-I_d$ |
| $C \rightarrow D$ | $T_3, T_2$ | $V_{bc}$ | 0      | $+I_d$ | $-I_d$ |
| $D \rightarrow E$ | $T_3, T_4$ | $V_{ba}$ | $-I_d$ | $+I_d$ | 0      |
| $E - F$           | $T_5, T_4$ | $V_{ca}$ | $-I_d$ | 0      | $+I_d$ |

$$\begin{aligned}
 (V_o)_{avg.} &= \frac{1}{\left(\frac{2\pi}{3}\right)} \left[ \int_{\left(\frac{\pi}{6}+\alpha\right)}^{\left(\frac{\pi}{2}+\alpha\right)} V_m \sin \omega t \, d\omega t - V_m \sin(\omega t - 120^\circ) \, d\omega t \right] \frac{1}{\pi} \\
 &= \frac{3V_m}{\pi} \left[ -\cos \omega t \right]_{\frac{\pi}{6}+\alpha}^{\frac{\pi}{2}+\alpha} \\
 &= \frac{3V_m}{\pi} \left[ \cos\left(\frac{\pi}{6}+\alpha\right) - \cos\left(\frac{\pi}{2}+\alpha\right) \right] = \frac{3V_m}{\pi} \left[ \cos \frac{\pi}{6} \cdot \cos \alpha - \sin \frac{\pi}{6} \cdot \sin \alpha \right. \\
 &\quad \left. - \cos \frac{\pi}{2} \cdot \cos \alpha + \sin \frac{\pi}{2} \cdot \sin \alpha \right] = \frac{3V_m}{\pi} \left[ \left( \cos \frac{\pi}{6} - \cos \frac{\pi}{2} \right) \cos \alpha + \left( \sin \frac{\pi}{2} - \sin \frac{\pi}{6} \right) \sin \alpha \right]
 \end{aligned}$$

$$(V_o)_{avg.} = \frac{3\sqrt{6}V_m}{\pi} \cos \alpha = 1.35 V_{LL} \cos \alpha.$$

$$(V_o)_{avg.} = \frac{3\sqrt{3}V_m}{\pi} \cos \alpha = \frac{3V_m}{\pi} \cos \alpha$$

Avg. output power =  $1.35 V_{LL} I_d \cos \alpha$ .

↳ Ac side current  $i_a$  :-

$$i_a = \sum_{n=1}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t$$

$$i_a = a_1 \cos \omega t + b_1 \sin \omega t$$

$$\begin{aligned} a_1 &= \frac{1}{\pi} \left[ \int_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}+\alpha} I_d \cos \omega t d\omega t + \int_{\frac{7\pi}{6}+\alpha}^{\frac{11\pi}{6}+\alpha} -I_d \cos \omega t d\omega t \right] \\ &= \frac{1}{\pi} \left[ I_d \left\{ \sin \left( \frac{5\pi}{6} + \alpha \right) - \sin \left( \frac{\pi}{6} + \alpha \right) \right\} - I_d \left\{ \sin \left( \frac{11\pi}{6} + \alpha \right) - \sin \left( \frac{7\pi}{6} + \alpha \right) \right\} \right] \\ &= \frac{1}{\pi} \left[ I_d \left\{ \sin \frac{5\pi}{6} \cdot \cos \alpha + \cos \frac{5\pi}{6} \cdot \sin \alpha - \sin \frac{\pi}{6} \cdot \cos \alpha - \cos \frac{\pi}{6} \cdot \sin \alpha \right\} \right. \\ &\quad \left. - I_d \left\{ \sin \frac{11\pi}{6} \cdot \cos \alpha + \cos \frac{11\pi}{6} \cdot \sin \alpha - \sin \frac{7\pi}{6} \cdot \cos \alpha - \cos \frac{7\pi}{6} \cdot \sin \alpha \right\} \right] \\ &= -\frac{2\sqrt{3} I_d}{\pi} \sin \alpha \end{aligned}$$

$$b_1 = \frac{1}{\pi} \left[ \int_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}+\alpha} I_d \sin \omega t d\omega t + \int_{\frac{7\pi}{6}+\alpha}^{\frac{11\pi}{6}+\alpha} -I_d \sin \omega t d\omega t \right]$$

$$= \frac{2\sqrt{3} I_d}{\pi} \cos \alpha$$


$$\therefore Q = \sqrt{a_1^2 + b_1^2} = \frac{2\sqrt{3} I_d}{\pi} ; \quad \phi_1 = -\alpha.$$

$$\therefore i_a = \frac{2\sqrt{3} I_d}{\pi} \sin(\omega t - \alpha)$$

$$\hookrightarrow \text{RMS Value of fundamental component } I_{q_1} = \frac{2\sqrt{3}}{\sqrt{2}\pi} I_d = \frac{\sqrt{6}}{\pi} I_d \\ = 0.78 \underline{I_d}$$

$\hookrightarrow$  RMS Value of harmonic components
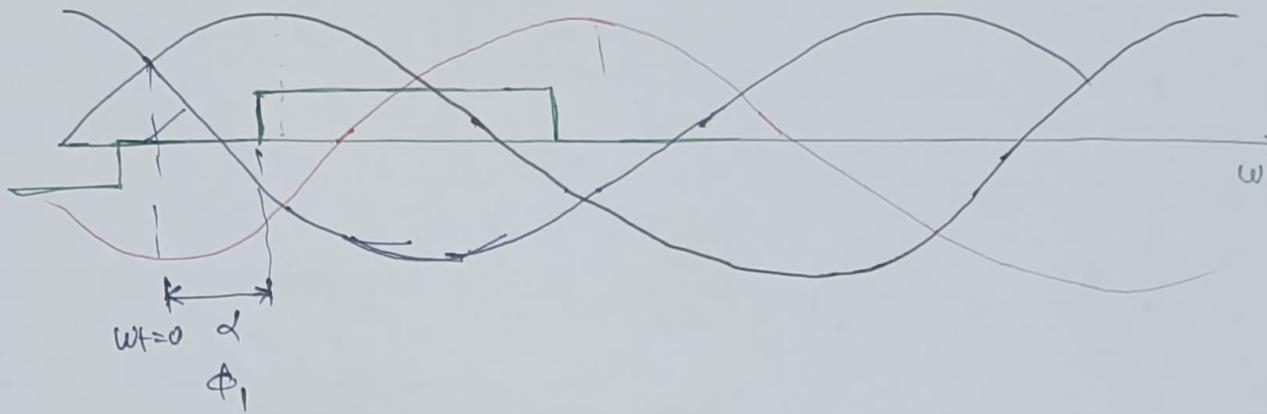
$$I_{ah} = \left( \frac{I_{q_1}}{h} \right) ; h = 6n \pm 1, n = 1, 2, 3, \dots$$



$$\hookrightarrow \text{Total RMS value of phase Current } I_a = \sqrt{\frac{2}{3}} I_d = 0.816 I_d$$

$$\cdot \text{THD} = \sqrt{\frac{I_a^2 - I_{q_1}^2}{I_{q_1}^2}} = .3108\%$$

$$\cdot \text{DPF} = \cos \phi_1 = \cos \alpha$$

$$\cdot \text{power factor} = \frac{\text{actual power}}{\text{apparent power}}$$

$$\begin{aligned} & \frac{3\sqrt{6}}{\pi} \times \cos \alpha \\ & \frac{\sqrt{3} V_{LL} I_{q_1} \cos \alpha}{\sqrt{3} V_{LL} I_a} \\ & = \boxed{\frac{3}{\pi} \cos \alpha} \end{aligned}$$

\* Effect of source inductance:-

$$E, R, L = \text{const}, I_{\text{max}} = I_0; \quad \left( \frac{dI}{dt} \right) = \text{const}$$



$$b_1 = \frac{1}{L} \int [E - L \frac{dI}{dt}] dt$$

$$b_1 = 0.80 \times 10^{-3} = \frac{1}{L} \int [E - L \frac{dI}{dt}] dt$$

$$= \frac{0.80 \times 10^{-3}}{0.80 \times 10^{-3}} = \frac{E - L \frac{dI}{dt}}{L} = 0.1 \text{ V}$$

$$\theta_{20} = \phi_{20} = 79.0^\circ$$



$$\theta_{20} = \phi_{20} = 79.0^\circ$$

$$\left[ \frac{\theta_{20} \cdot 2}{\pi} \right]$$

\* Single Quadrant Converters - Half controlled converters :-
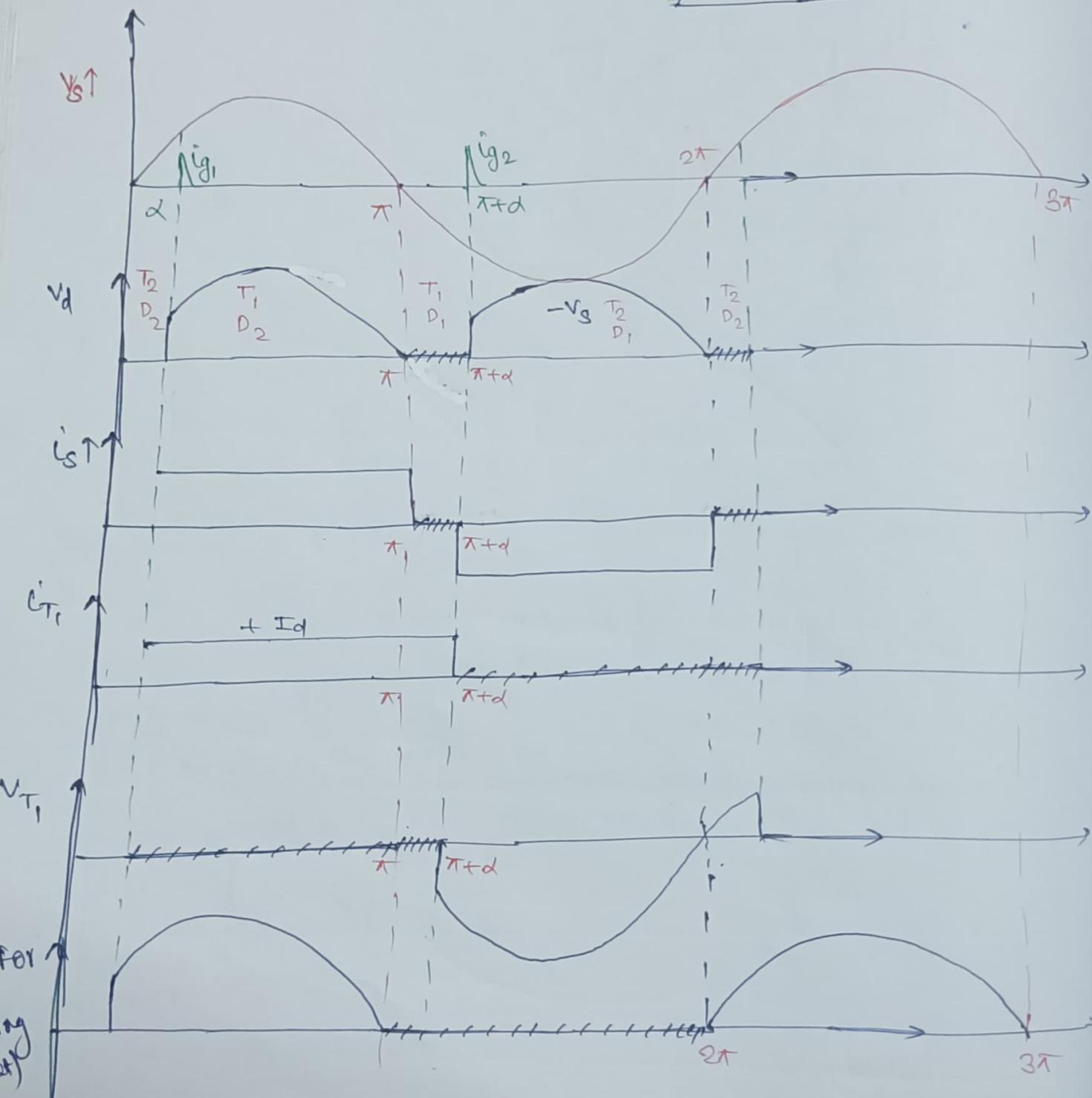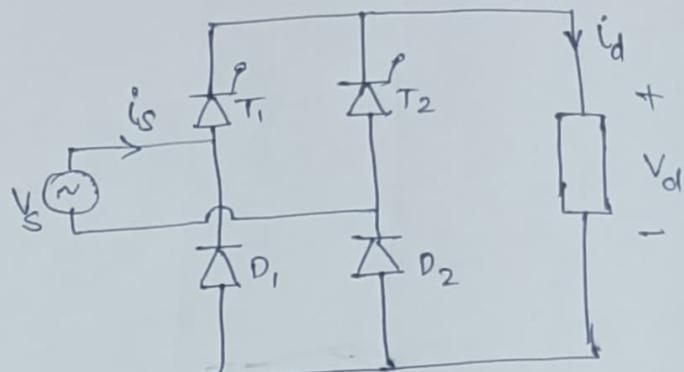
# Symmetrical configuration :-

load current  $i_d$  is constant at  $I_d$ .



at  $\alpha$ :  $T_1$  is turned on

$\alpha \rightarrow \pi$  :  $T_1$  and  $D_2$  conduct.

$$V_d = V_s$$

$$i_s = +I_d$$

$$i_{T_1} = I_d \quad i_{T_2} = 0, i_{D_1} = 0$$

$$i_{D_2} = I_d$$

$\pi \rightarrow \pi + \alpha$

$T_1, D_1$  - Conduct

$$V_d = 0$$

$$i_s = 0$$

$$i_{T_1} = I_d$$

$$i_{D_2} = 0$$

$$i_{D_1} = I_d$$

$$V_{T_1} = 0$$

$\pi + \alpha \rightarrow 2\pi$

$T_2, D_1$  Conduct.

$$V_d = -V_s$$

$$i_s = -I_d$$

$$i_{T_1} = 0, i_{T_2} = I_d$$

$$i_{D_2} = 0.$$

$2\pi \rightarrow 2\pi + \alpha$

$T_2, D_2$  Conduct

$$V_d = 0$$

$$i_s = 0$$

$$i_{T_1} = 0, i_{T_2} = +I_d$$

$$i_{D_2} = I_d.$$

$$V_{T_1} = V_s$$

Half Waving Effect :-

Suppose  $i_{g_2}$  is missing at  $(\pi + \alpha)$  then  $T_1, D_1$  continue to conduct upto  $wt = 2\pi$  giving a load voltage ~~equal to zero~~ equal to zero.

at  $wt = 2\pi$ ,  $D_2$  is forward biased and the conducting devices are  $T_1$  and  $D_2$  so the load voltage is entire positive voltage of source voltage.

under such cond'n the rectifier behaves similar to a uncontrolled half wave rectifier.

This phenomenon is called half waving effect.

at  $\alpha = 0$ :  $T_1$  is turned on


$\alpha \rightarrow \pi$  :  $T_1$  and  $D_2$  conduct.

$$V_d = V_s$$

$$i_s = +I_d$$

$$i_{T_1} = I_d$$

$$i_{D_2} = I_d$$

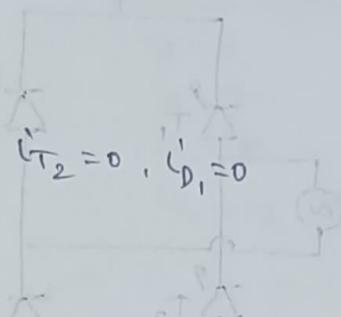

$\pi \rightarrow \pi + \alpha$

$T_1, D_1$  Conduct

$$V_d = 0$$

$$i_s = 0$$

$$i_{T_1} = I_d$$

$$i_{D_2} = 0$$

$$i_{D_1} = I_d$$

$$V_{T_1} = 0$$

$\pi + \alpha \rightarrow 2\pi$

$T_2, D_1$  Conduct.

$$V_d = -V_s$$

$$i_s = -I_d$$

$$i_{T_1} = 0, i_{T_2} = I_d$$

$$i_{D_2} = 0.$$

$2\pi \rightarrow 2\pi + \alpha$

$T_2, D_2$  Conduct

$$V_d = 0$$

$$i_s = 0$$

$$i_{T_1} = 0, i_{T_2} = +I_d$$

$$i_{D_2} = I_d.$$

$$V_{T_1} = V_s$$

\* Half Waving Effect :-





Suppose  $i_{D_2}$  is missing at  $(\pi + \alpha)$  then  $T_1, D_1$  continue to conduct upto  $wt = 2\pi$  giving a load voltage ~~upto~~ equal to zero.

at  $wt = 2\pi$ ,  $D_2$  is forward biased and the conducting devices are  $T_1$  and  $D_2$ . So the load voltage is entire positive voltage of source voltage.

under such cond<sup>n</sup> the rectifier behaves similar to a uncontrolled half wave rectifier.

This phenomenon is called half waving effect.

## # Asymmetrical configuration

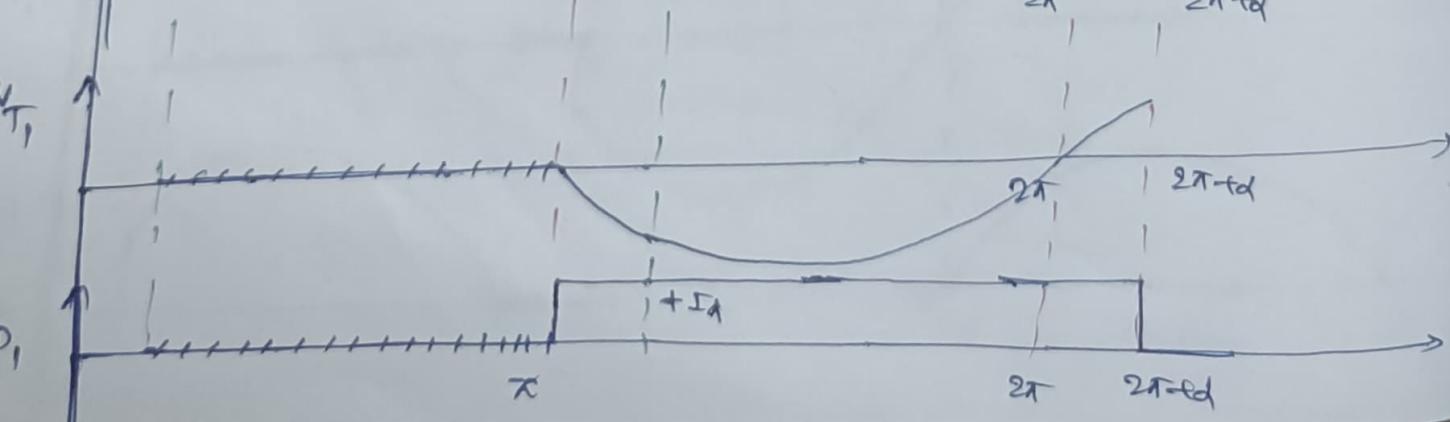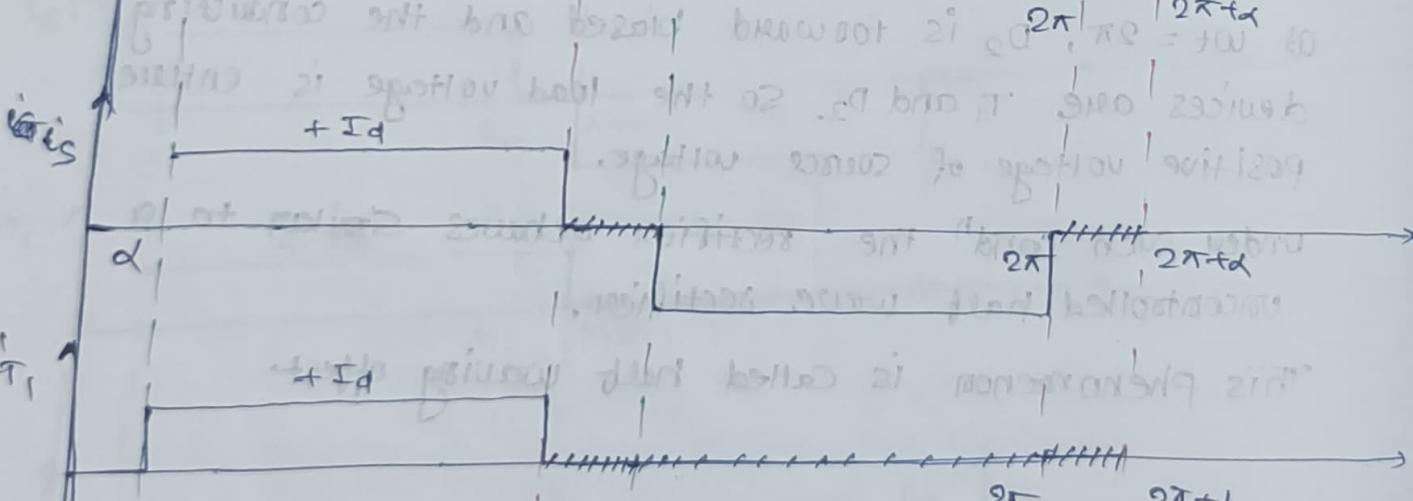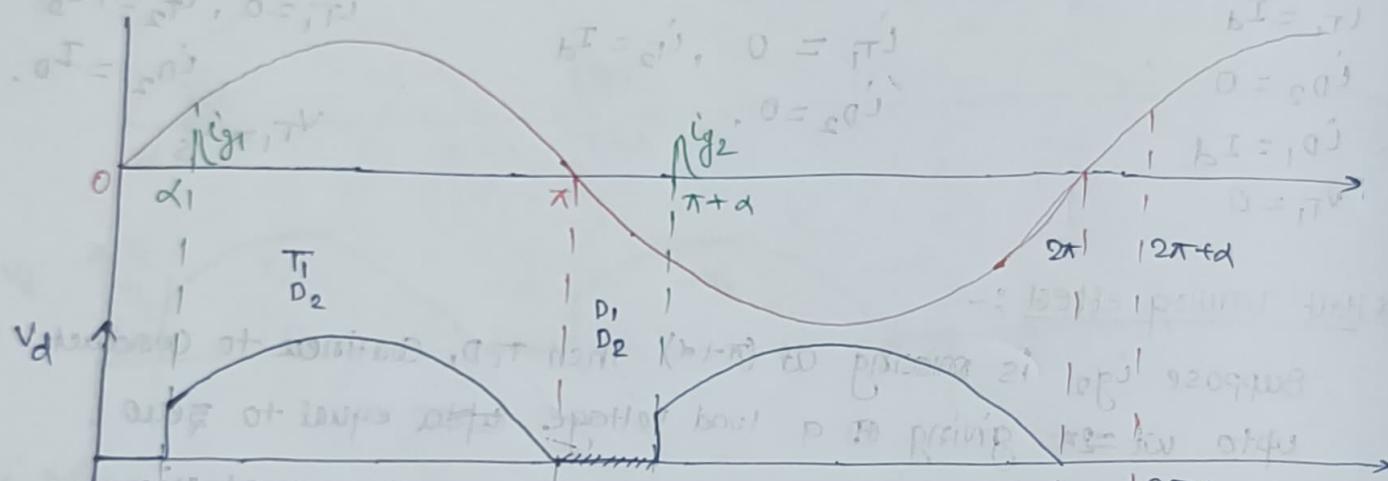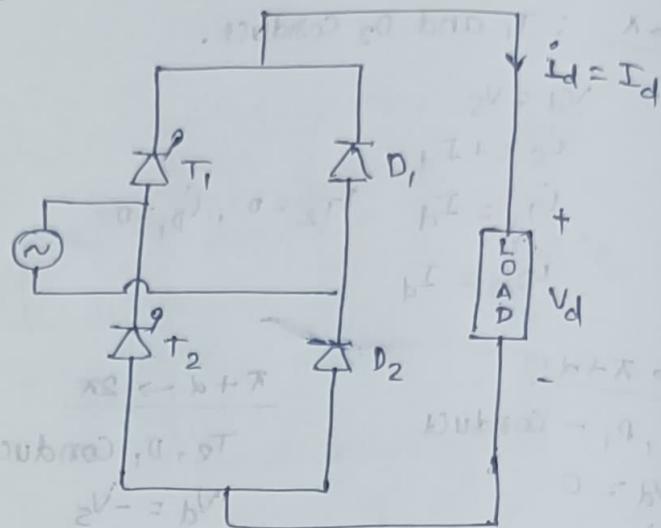

$\alpha \rightarrow \pi$

$T_1, D_2$  conduct

$$V_d = V_S$$

$$i_s = +I_d$$

$$i_{T_1} = I_d$$

$$i_{D_2} = I_d$$

$$V_{T_1} = 0$$

$\pi \rightarrow \pi+\alpha$

$D_1, D_2$  conduct

$$V_d = 0$$

$$i_s = 0$$

$$i_{T_1} = 0$$

$$i_{D_2} = i_{D_1} = I_d$$

$$V_{T_1} = V_S$$

$\pi+\alpha \rightarrow 2\pi$

$T_2, D_1$  conduct

$$V_d = -V_S$$

$$i_s = -I_d$$

$$i_{T_1} = 0; V_{T_1} = V_S$$

$$i_{D_1} = +I_d$$

$2\pi \rightarrow 2\pi+\alpha$

$D_2 \rightarrow ON$

$D_1, D_2 \rightarrow$  conducts

$$V_d = 0$$

$$i_s = 0$$

$$i_{T_1} = 0; V_{T_1} = V_S$$

$$i_{D_1} = i_{D_2} = +I_d$$

↳ prior to  $(\pi+\alpha)$   $D_1$  and  $D_2$  are conducting if  $i_{g_2}$  is missing  
 these devices continue to conduct until  $(2\pi+\alpha)$ . ~~so that~~  
 Then the output voltage is similar to that of Half wave  
 controlled rectifier.

Therefore the possibility of half wavying effect is avoided.

⇒ For asymmetric configuration one more gate pulse is required  
 (i.e. two different gate pulse required.)

### \* Performance parameters

$$\textcircled{1} \quad (V_d)_{\text{avg.}} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d\omega t = \frac{V_m}{\pi} [\cos \alpha - (-1)] = \frac{V_m}{\pi} (1 + \cos \alpha)$$

\textcircled{2} Avg. power through converter

$$P = (V_d)_{\text{avg.}} I_d = \frac{V_m}{\pi} (1 + \cos \alpha) I_d = \frac{V_m I_d}{\pi} [1 + \cos \alpha]$$

$$\textcircled{3} \quad (I_T)_{\text{avg.}} = \frac{1}{2\pi} [(I_d)(\pi-\alpha)]$$

$$\textcircled{4} \quad (I_D)_{\text{avg.}} = \frac{1}{2\pi} [I_d (\pi+\alpha)]$$

$$(E_T)_{rms} = \sqrt{2\alpha + b}$$

$$(I_D)_{rms} = \sqrt{2\alpha + b}$$

$$PIV = V_m = \sqrt{2} V_s$$

$$i_s(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t$$

$$a_0 = 0$$

$$a_1 = \frac{1}{\pi} \left[ \int_0^{2\pi} I_d \cos \omega t d\omega t + \int_{\pi+\alpha}^{2\pi} -I_d \cos \omega t d\omega t \right]$$

$$= -\frac{2I_d}{\pi} \sin \alpha$$

$$b_1 = \frac{1}{\pi} \left[ \int_0^{\alpha} I_d \sin \omega t d\omega t + \int_{\pi+\alpha}^{2\pi} -I_d \sin \omega t d\omega t \right]$$

$$b_1 = \frac{2I_d}{\pi} (1 + \cos \alpha)$$

$$c_1 = \sqrt{a_1^2 + b_1^2}$$

$$= \sqrt{\frac{4I_d^2}{\pi^2} \sin^2 \alpha + \frac{4I_d^2}{\pi} (1 + \cos \alpha)^2}$$

$$= \frac{2I_d}{\pi} \left[ \sqrt{2 + 2 \cos \alpha} \right]$$

$$= \frac{2I_d}{\pi} \left[ \sqrt{2 \left( 1 + 2 \cos \frac{\alpha}{2} \right)} \right]$$


$$\text{Reactance } \frac{mV}{\pi} = \left[ (1 - 1 - 0.82) \right] \frac{mV}{\pi} = 10.4 \text{ mV} \quad \text{①}$$

$$= \frac{2I_d}{\pi} 2 \cos \frac{\alpha}{2} = \frac{4I_d}{\pi} \cos \frac{\alpha}{2}$$

$$[(2\alpha+1) \frac{I_m V}{\pi}] = 1.1 (2\alpha+1) \frac{mV}{\pi} = 1.1 \cdot 10.4 \text{ mV} = 9$$


$$[(2-\pi)(6I)] \frac{1}{\pi} = \text{p.u.(T1)} \quad \text{②}$$
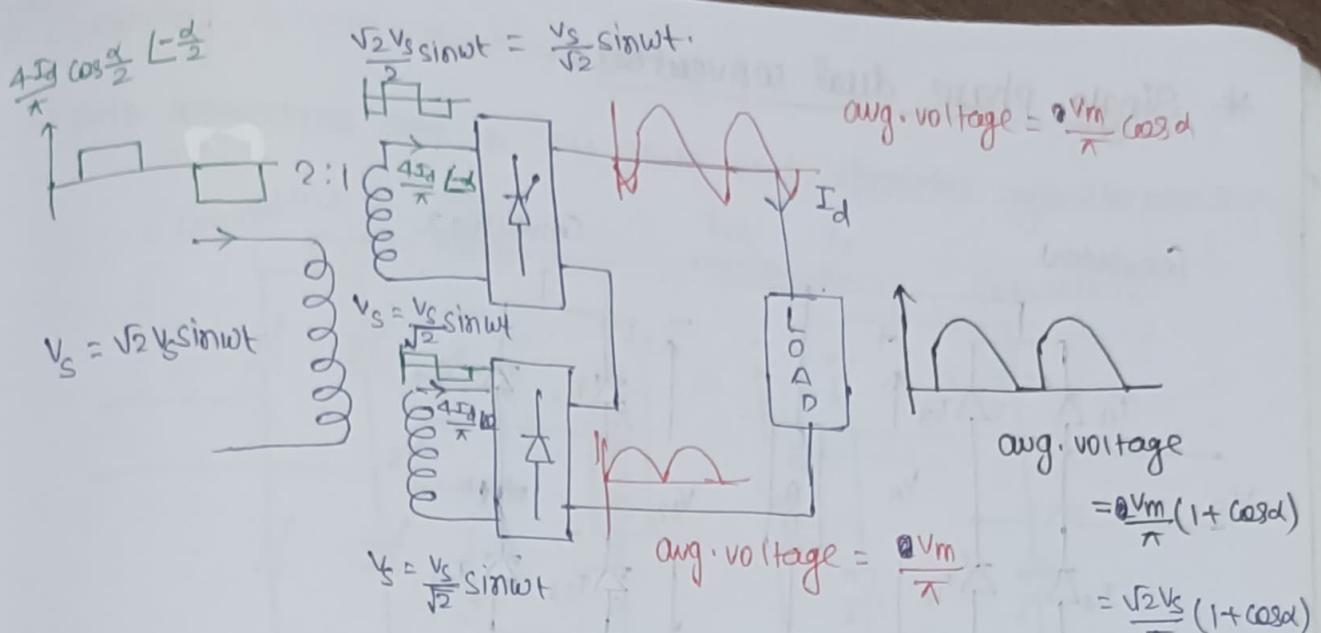
$$[(2-\pi) 6I] \frac{1}{\pi} = \text{p.u.(I)} \quad \text{③}$$




- Uncontrolled Rectifiers and Half controlled Rectifiers  $\Rightarrow$  single quadrant (1st) of  $V_d - I_d$  plane.
- Controlled Rectifiers  $\Rightarrow$  double quadrant (1st & 4th) in  $V_d - I_d$  plane.

### Four quadrant converters :-

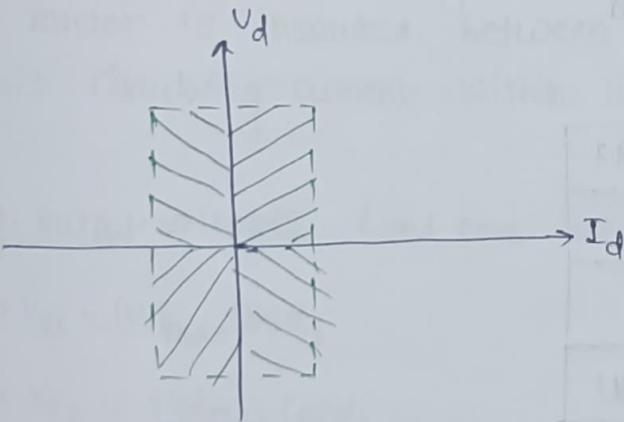

Two fully controlled converters are connected back to back  
 $\Downarrow$   
 Dual converter.

## \* Single-phase dual converters :-

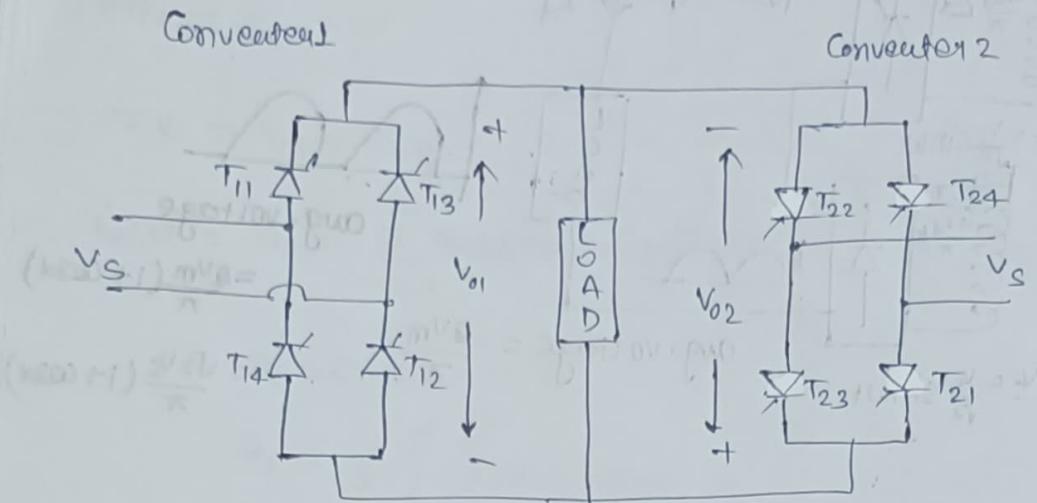

↳ Each converter has the ability to conduct current in one direction only.

↳ Load current is bidirectional.

## \* Non-circulating current operation :-


↳ only one converter operates at a time and carries the entire load current.

| V <sub>o</sub> | I <sub>o</sub> | Converter 1 | Converter 2 |
|----------------|----------------|-------------|-------------|
| +ve            | +ve            | Rectifier   | ---         |
| -ve            | +ve            | Inverter    | ---         |
| -ve            | -ve            | ---         | Rectifier   |
| +ve            | -ve            | ---         | Inverter    |

↳ No current limiting reactor is required.
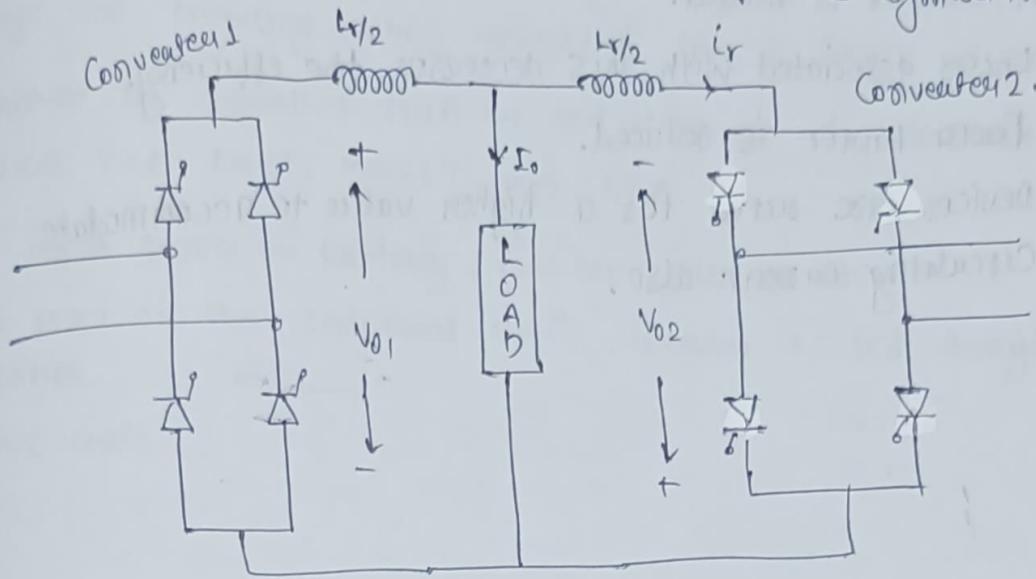
## \* Circulating current operation :-

↳ Both converters are in ON state and operates simultaneously.



For both (+ve) load current and voltage the inverters behaves as a rectifier and Inverter2 behaves as Inverter.

- Avg. voltage of both converters are equal.
- Instantaneous voltages are different.
- This leads to a circulating current between the converters.
- A reactor is inserted between the converters to limit this circulating current within limits.

Avg. output voltages (and one behaves as inverter and other will act as a rectifier.)

$$\cdot V_{01} = (V_0)_{\max} \cos \alpha_1$$

$$\cdot V_{02} = (V_0)_{\max} \cos \alpha_2$$

$$\cdot V_{0L} = -V_{02} = V_0$$

$$\cos \alpha_1 + \cos \alpha_2 = 0$$

$$\Rightarrow \underline{\alpha_1 + \alpha_2 = 180^\circ}$$

↳ At any instant one converter operates as rectifier while the other one operates as inverter.

↳ To reverse the current, the role of the converters are interchanged.

↳ Response is very fast.

## Drawbacks

- ↳ A reactor is needed.
- ↳ Losses associated with this decreases the efficiency.
- Power factor is reduced.
- Devices are rated for a higher value to accommodate circulating current also.



## \* Switch Mode DC-ac Converter (Inverter)

- ↳ An inverter is a ckt. (or) system that delivers ac power at desired voltage and frequency when energized from a source of dc power.
- ↳ Achieved by controlled turn on and turn off of controllable devices like IGBT, MOSFET, GTO, BJT.
- ↳ DC input source → Battery, fuel cell, solar cell etc.
- ↳ In most of the industrial appln., inverter is fed through a rectifier.
- ↳ This conf.

## \* Areas for applications

- variable speed ac motor drives.
- Industrial heating.
- Aircraft / spacecraft power supplies.
- uninterruptable power supplies.
- HVDC systems.
- static VAR compensators.
- Active harmonic filters.
- Electric vehicles.

## \* Classifications of inverters

### ① Voltage Source Inverters (VSI)

- Input dc source is a voltage source.

### ② Current Source Inverters (CSI)

- Input dc source is a current source.

- usually used in high power ac drives.

\* Classification of VSI on the basis of output voltage control.

## ① Square wave inverters

- Output voltage waveform is similar to a square wave.
- Input dc voltage is controlled to get controlled magnitude of ac output.
- The inverter has to control only the frequency.

## ② PWM inverters

- Input dc voltage is constant in magnitude.
- The inverter has to control both the freqn and magnitude.

\* Square wave inverters

### ① Single phase bridge inverter:

#### a) Half Bridge inverter circuit

↳ period of inverter is

selected as  $T = \frac{1}{f}$

f: required output frequency.

R-load

• For  $t < 0$

Let  $T_A^-$  was conducting

• Load current path →

↳ lower source, load and  $T_A^-$

at  $t=0$ ,  $T_A^-$  is turned off forcibly and  $T_A^+$  is turned on


•  $0 \rightarrow T_2$


$T_A^+ \rightarrow \text{ON}$   $T_A^- \rightarrow \text{OFF}$

• Load current path → upper source,  $T_A^+$  and load.

•  $T_2 \rightarrow T$  :  $T_A^- \rightarrow \text{ON}$ ,  $T_A^+ \rightarrow \text{OFF}$ .

Load current path →

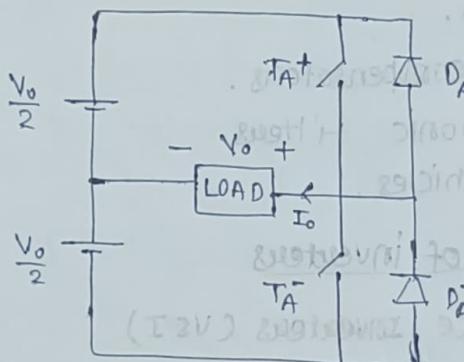

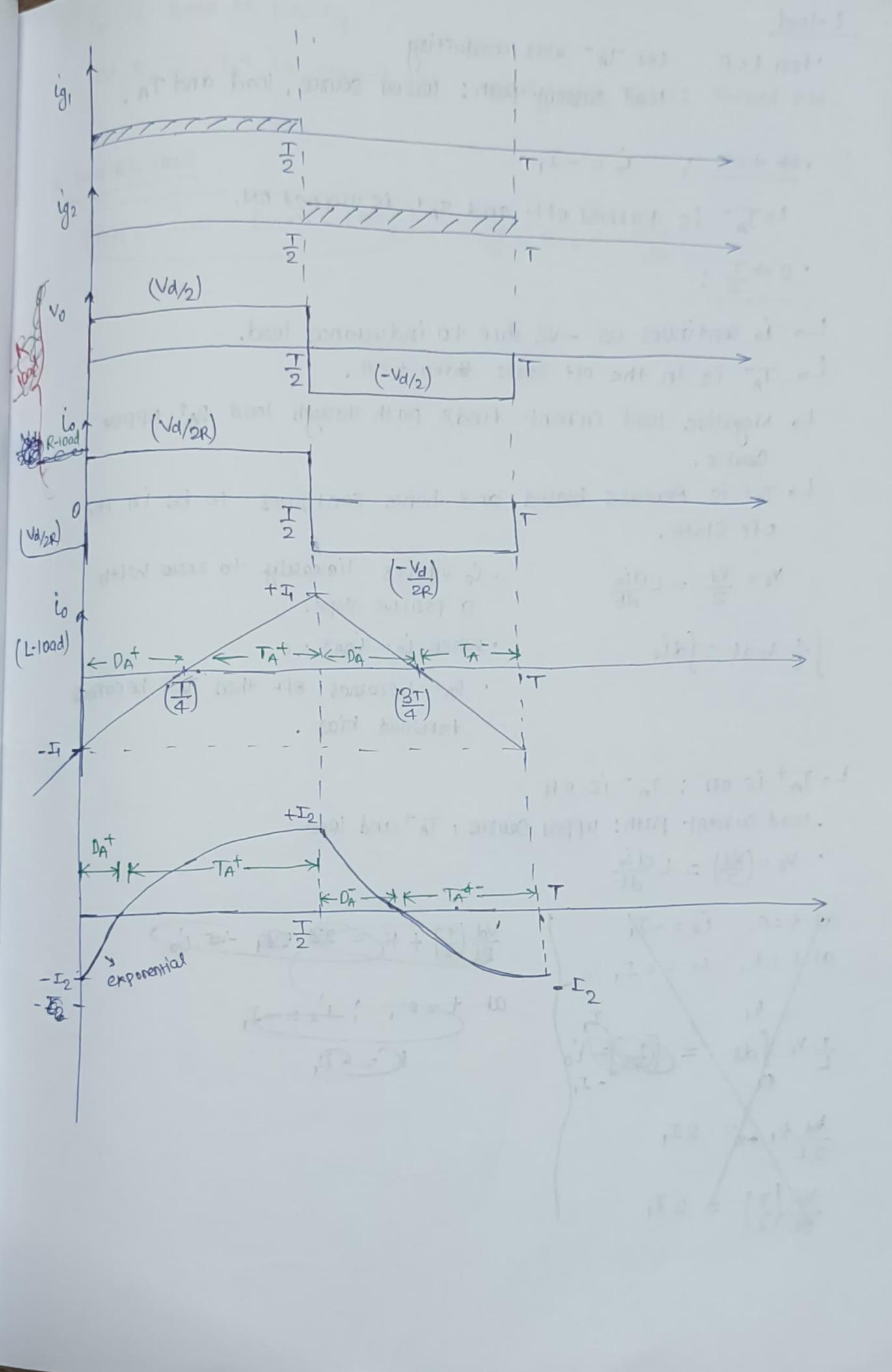

### L-load

• For  $t < 0$ , Let  $T_A^-$  was conducting

load current path: lower source, load and  $T_A$ .

• at  $t=0$ ,  $i_o = -I_1$

↳  $T_A^-$  is turned off and  $T_A^+$  is turned ON.

•  $0 \rightarrow \frac{T}{2}$ :

↳  $i_o$  continues as -ve due to inductance load.

↳  $T_A^-$  is in the off state ~~therefore~~  $t > 0$ .

↳ Negative load current finds path through load  $D_A^+$  upper source.

↳  $T_A^+$  is reverse biased and hence continues to be in the off state.

$$V_o = \frac{V_d}{2} = L \frac{di_o}{dt}$$

$$\int \frac{1}{L} V_o dt = \int di_o$$

•  $i_o$  varies linearly to zero with a positive slope.

• When  $i_o = i_{D_A^+} = 0$ ,

•  $D_A^+$  becomes off then  $T_A^+$  becomes forward bias.

↳  $T_A^+$  is on ;  $T_A^-$  is off

• load current path: upper source,  $T_A^+$  and load

$$V_o = \left( \frac{V_d}{2} \right) = L \frac{di_o}{dt}$$

$$\text{at } t=0, i_o = -I_1$$

$$\text{at } t=t_1, i_o = +I_1$$

$$\frac{1}{L} \int V_o dt = i_o$$

$$\frac{V_d}{2L} t_1 + K = 2I_1$$

$$\frac{V_d}{2L} \left( \frac{T}{2} \right) = 2I_1$$

$$\frac{V_d}{2L} \left( \frac{T}{2} \right) + K = 2I_1 \quad \text{--- (1)}$$

$$\text{at } t=0, i_o = -I_1$$

$$K = -I_1$$

$i_0$  is zero at  $t = T_f$

at  $t = \frac{T}{2}$ ,  $T_A^+$  is turned off forcibly at  $T_A^-$  is turned on.

\* For RL load

$$\boxed{i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-\frac{t}{\tau}}}$$

$$\frac{V_d}{2} = R i_0 + L \frac{di_0}{dt}$$