


Line Frequency Controlled Rectifiers

- **Controlled dc output voltage**

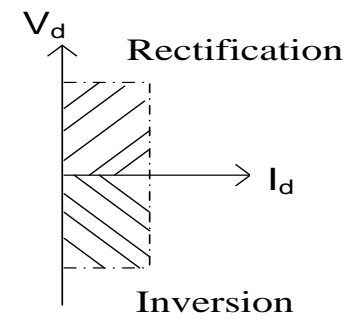 **varies from +ve maximum to –ve maximum.**

- **Controllable devices like thyristors, IGBT BJT are used.**
- **Commutation of the devices depends on the ac side line frequency.**

- **Dc side current is always +ve**
- **Dc side voltage is +ve or -ve.**



- **+ve voltage and +ve current at dc side indicates rectification mode. Power flows from ac side to dc side.**
- **operating points lie in the first quadrant of V_d - I_d plane.**
- **-ve voltage and +ve current at dc side indicates inversion mode. Power flow is from dc side to ac side.**
- **operating points lie in the fourth quadrant of V_d - I_d plane.**

Single phase half wave controlled rectifier

- R load

$0 \rightarrow \alpha$

T_1 is off.

$$i = 0. \quad v_d = 0. \quad i_s = 0 \quad v_{T1} = v_s$$

- At $\omega t = \alpha$, T_1 is triggered on

• $\alpha \rightarrow \pi$

• T_1 is on.

$$v_d = v_s \quad i = v_d / R = v_s / R =$$



$$i_s = i \quad \frac{\sqrt{2}v_s}{R} \sin \omega t$$

- At $\omega t = \pi$, $i = 0$
 T_1 becomes off


• $\pi \rightarrow 2\pi$

T_1 is off.
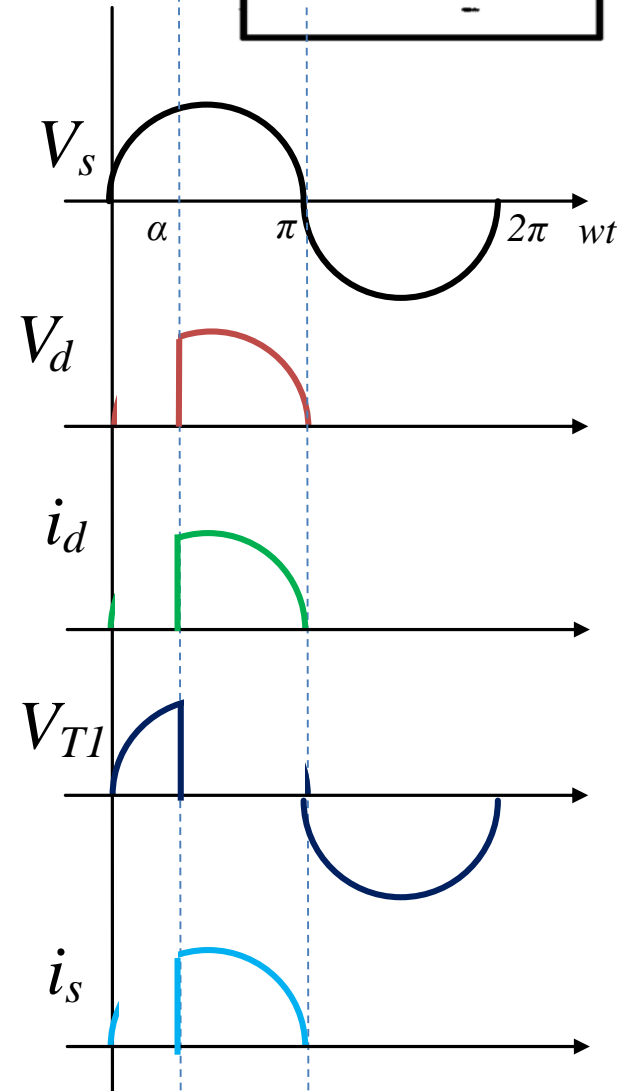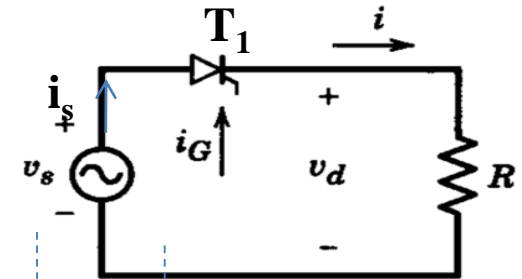
$$i = 0. \quad v_d = 0. \quad i_s = 0 \quad v_{T1} = v_s$$



R-L load

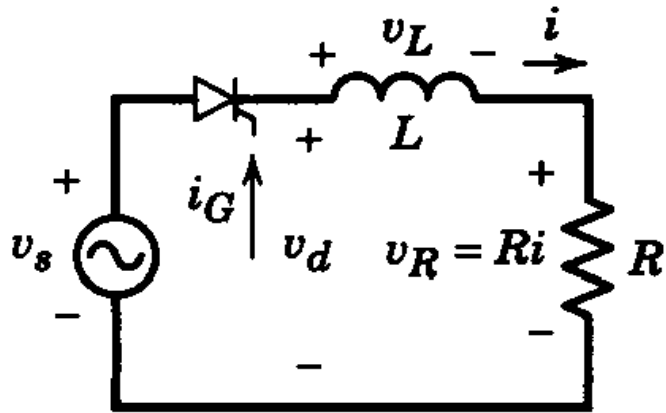

$0 \rightarrow \alpha$

Switching device is off.

$$i = 0 \quad V_d = 0$$

$$V_L = 0, V_R = 0$$

$$V_T = v_s$$


$\alpha \rightarrow \theta_2$


Thyristor is on.

$$V_d = Ri(t) + L \frac{di(t)}{dt} = v_s = \sqrt{2}v_s \sin \omega t$$

$$v_R(t) = Ri(t)$$

$$v_L(t) = v_s - v_R(t)$$

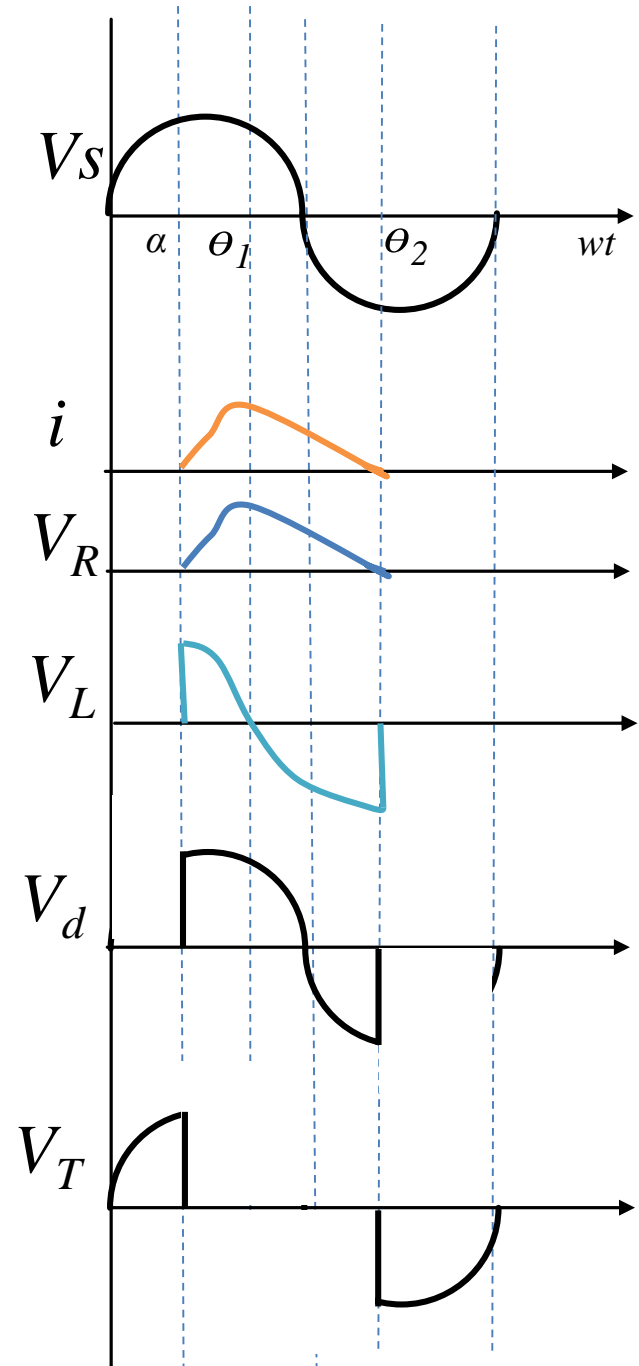

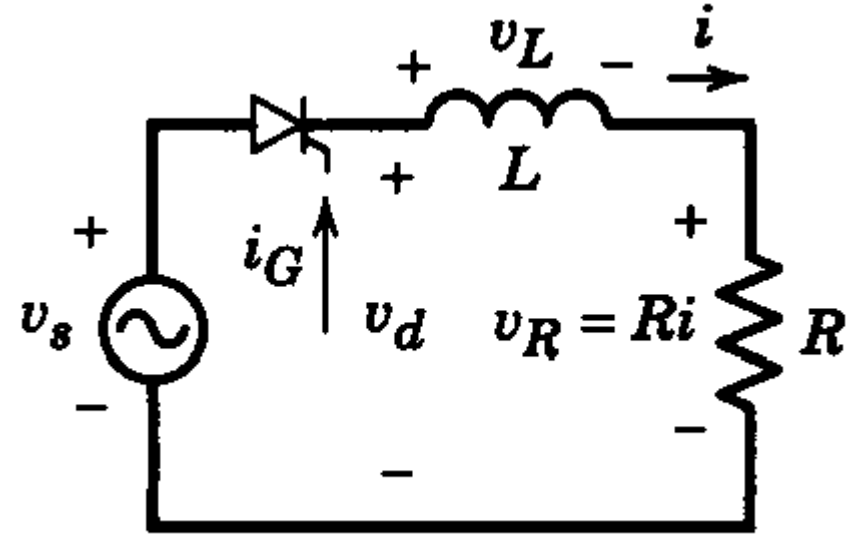


At $\omega t = \underline{\theta_1}$

$di/dt = 0$, $v_L = 0$,



$v_R = v_s$

Area A1 = Area A2

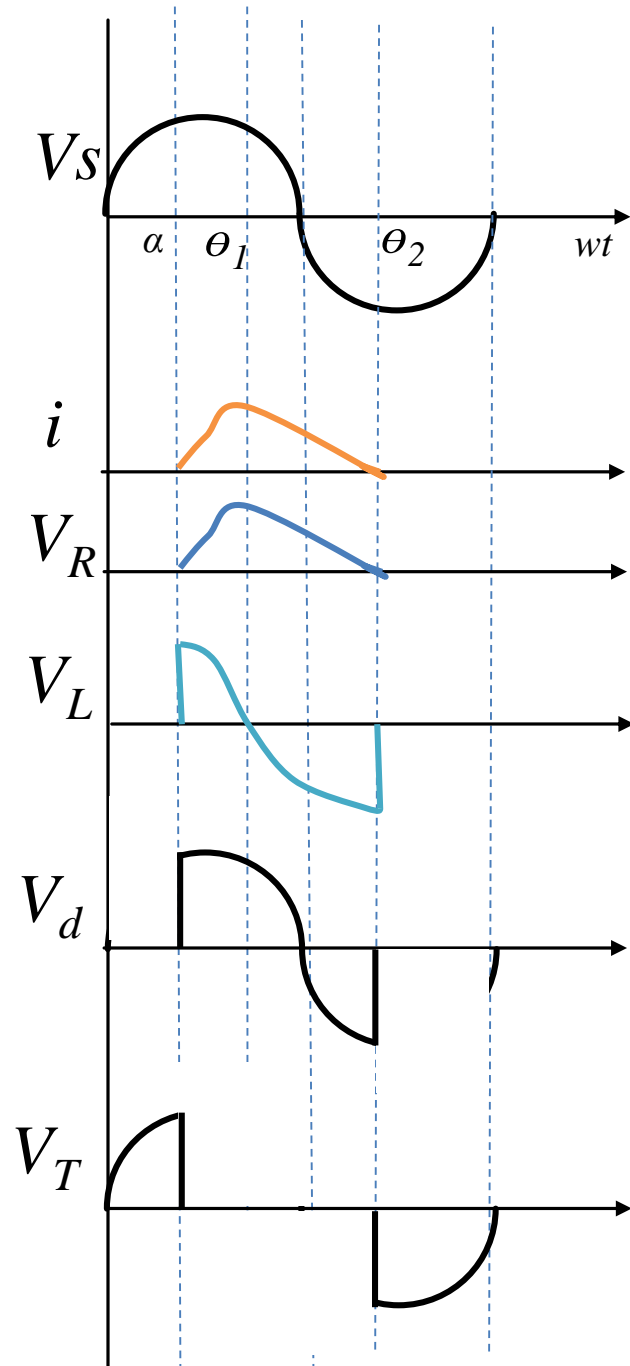
Energy stored in the inductor during α to $\underline{\theta_1}$ is sent back to ac source during $\underline{\theta_1}$ to $\underline{\theta_2}$



R-L load with a freewheeling diode

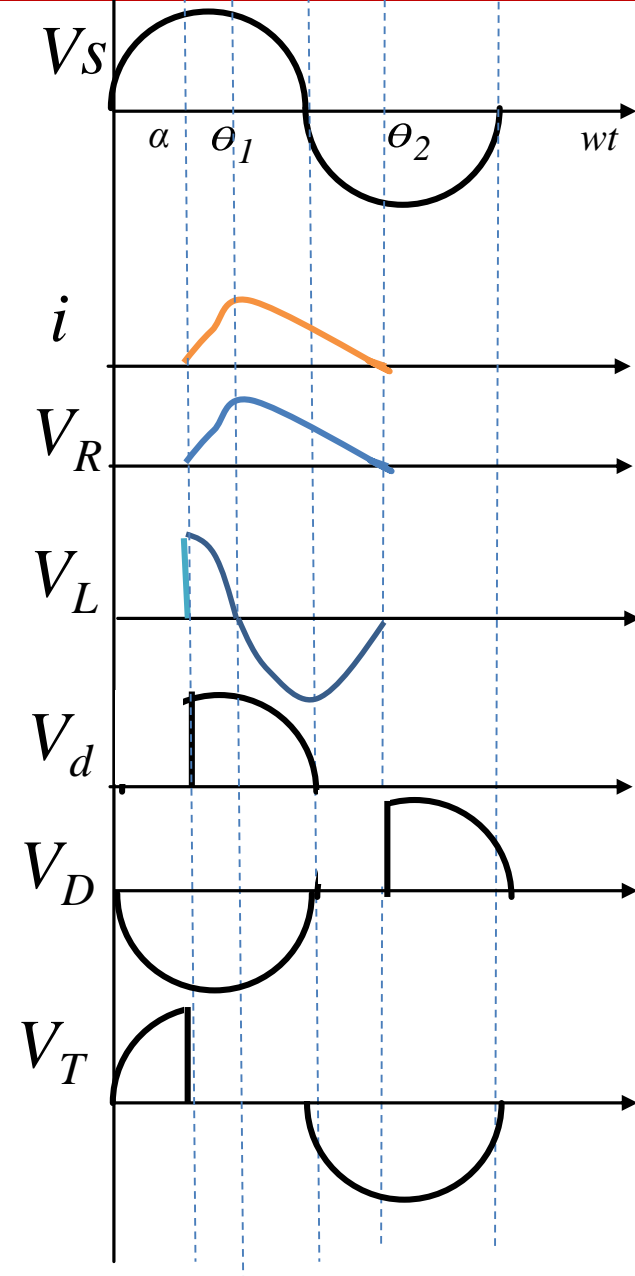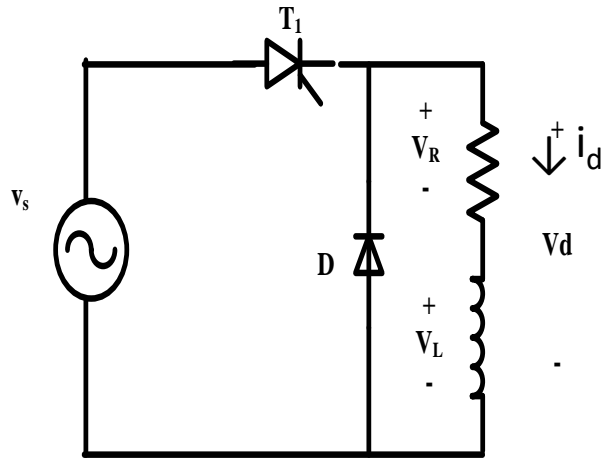

- L-E load

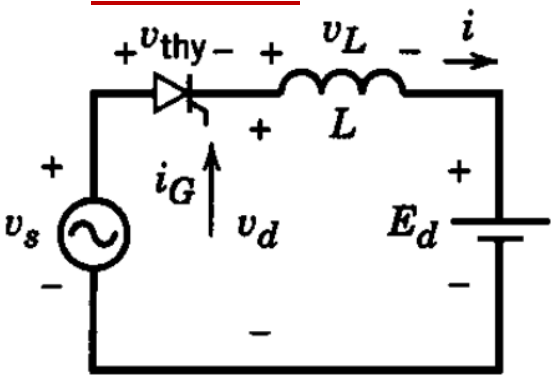

0 → θ

T is reverse biased.

$i = 0$

$V_L = 0$

$V_d = E_d$

$V_T = v_s - E_d$

θ → α

T is forward biased and off.


$i = 0$

$V_d = E_d$

$V_L = 0$

$V_T = v_s - E_d$

L-E load

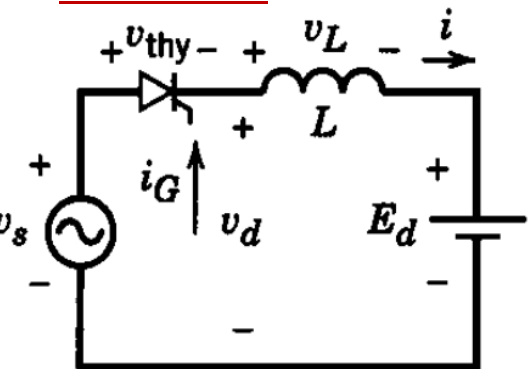

At α Thyristor is forward biased and triggered.

$\alpha \rightarrow \beta$


Thyristor is conducting.

$$V_d = v_s$$

$$V_L = L \frac{di}{dt} = v_s - E_d$$


$$i_d = \frac{1}{\omega L} \int (v_s - E_d) d\omega t$$

$$V_T = 0$$

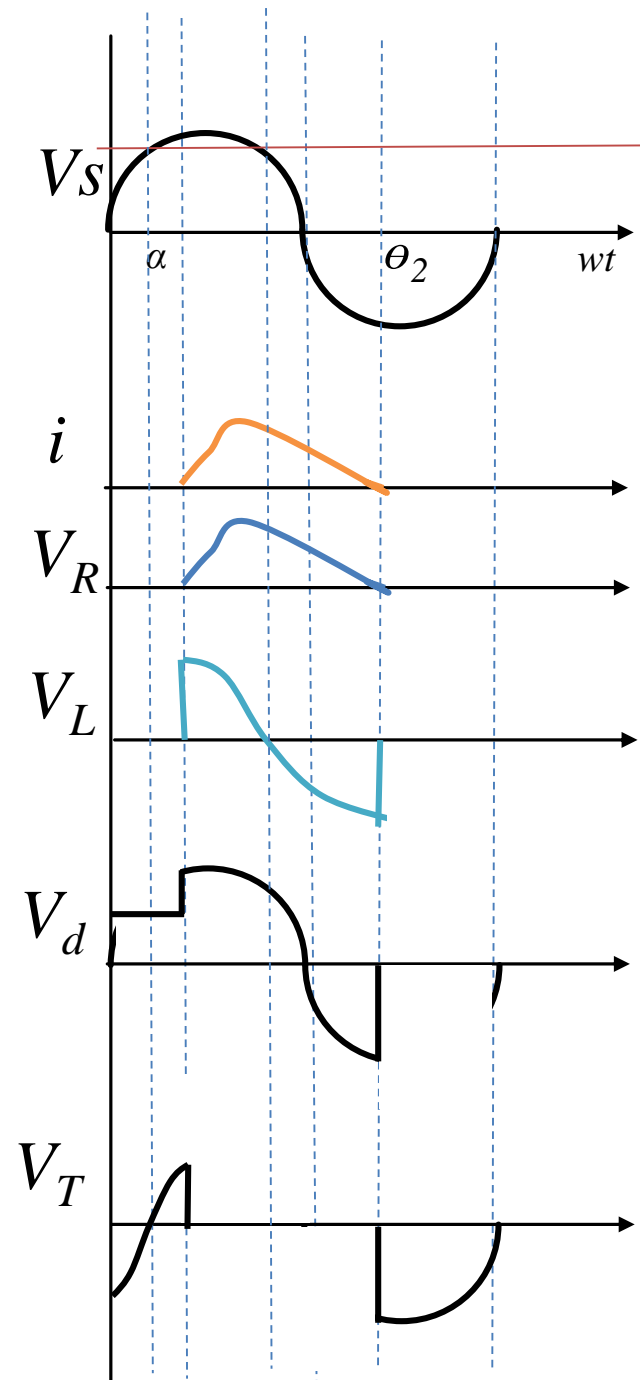

- At β , $i = 0$, T becomes off.
- $\beta \rightarrow 2\pi$
- Thyristor is off
- $i = 0$
- $V_L = 0$
- $V_d = E_d$
- $V_T = v_s - E_d$

- R-E load

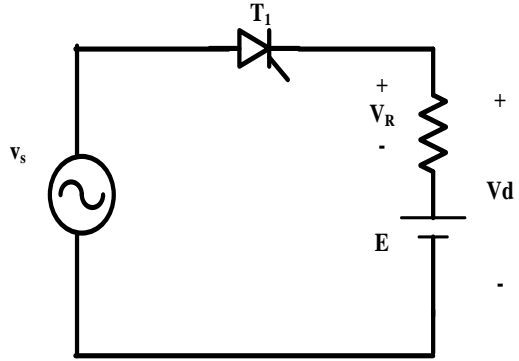

0 → θ

Thyristor is reverse biased.

$i_d = 0$

$v_d = E_d$

$v_R = 0$

$v_T = v_s - E_d$


θ → α


Thyristor is forward biased and in the off state.

$v_d = E_d$

$i_d = 0$ $v_R = 0$

$v_s = v_T + E$

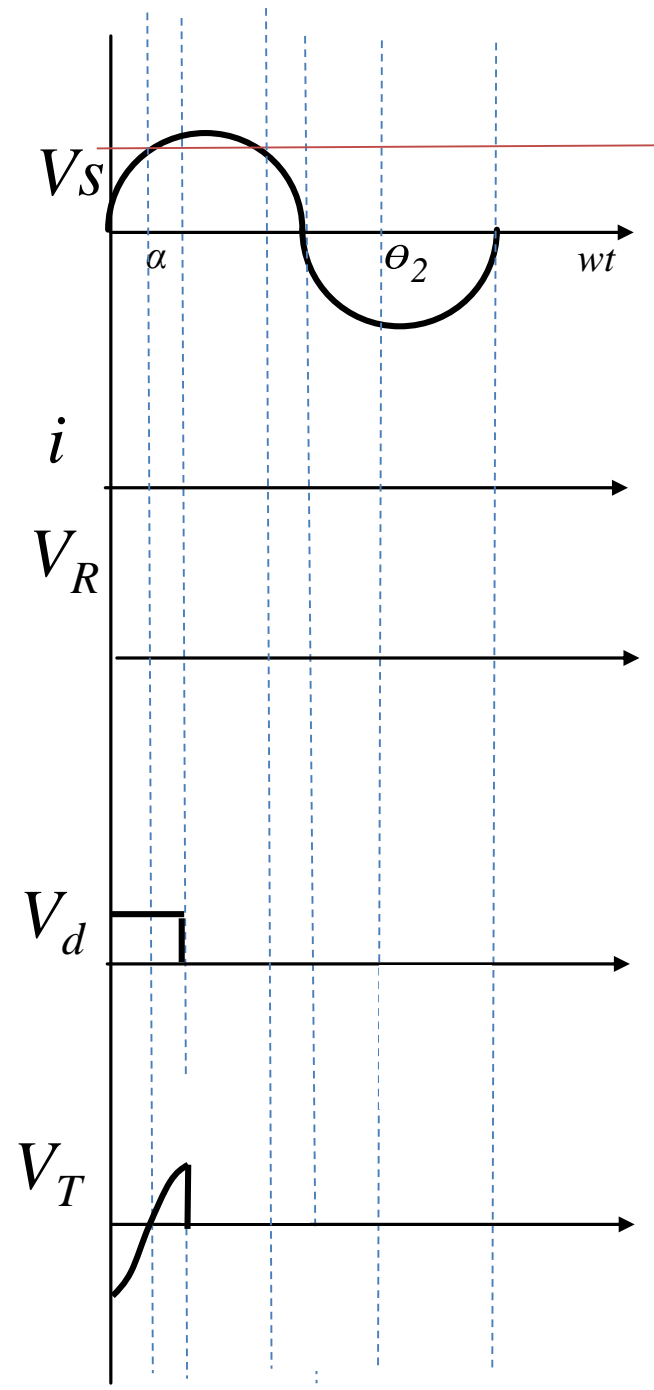

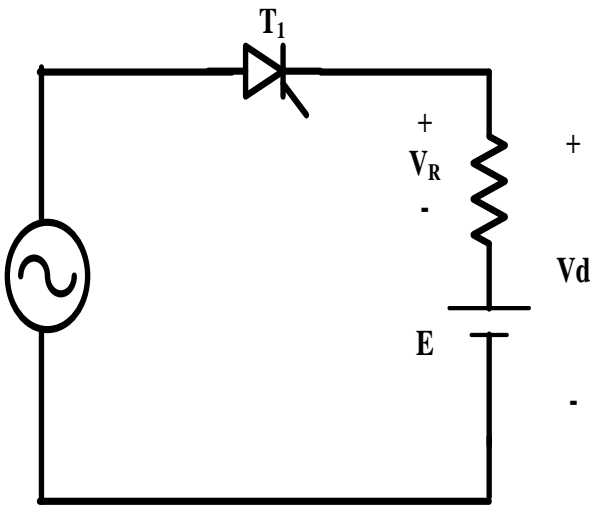

$\alpha \rightarrow \pi - \theta$


Thyristor is forward biased and in the on state.

$$V_d = v_s$$

$$v_R = Ri = v_s - E_d$$

$$i = (v_s - E_d) / R$$

$$V_T = 0$$

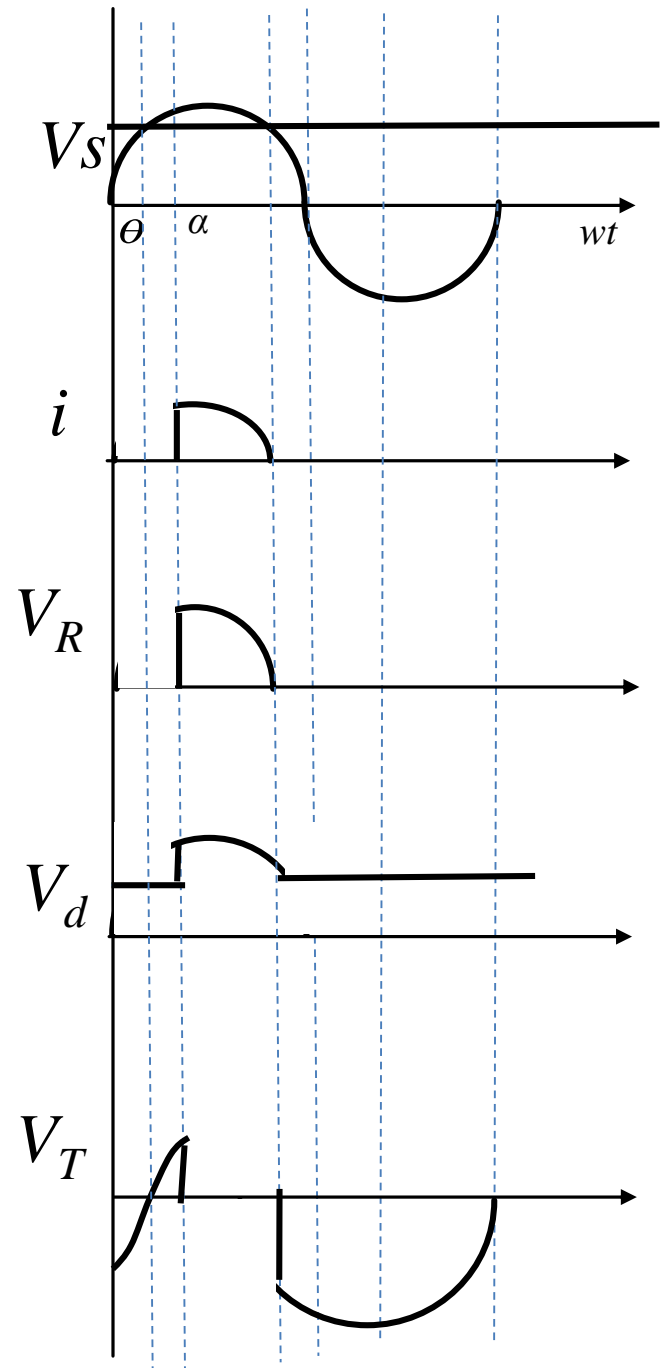

- At $\pi - \theta$,
- $i_d = 0$
- Thyristor becomes off


- $\pi - \theta \rightarrow 2\pi$

- $v_d = E_d$

- $v_R = 0$



- $v_T = v_s - E_d$

Waveform

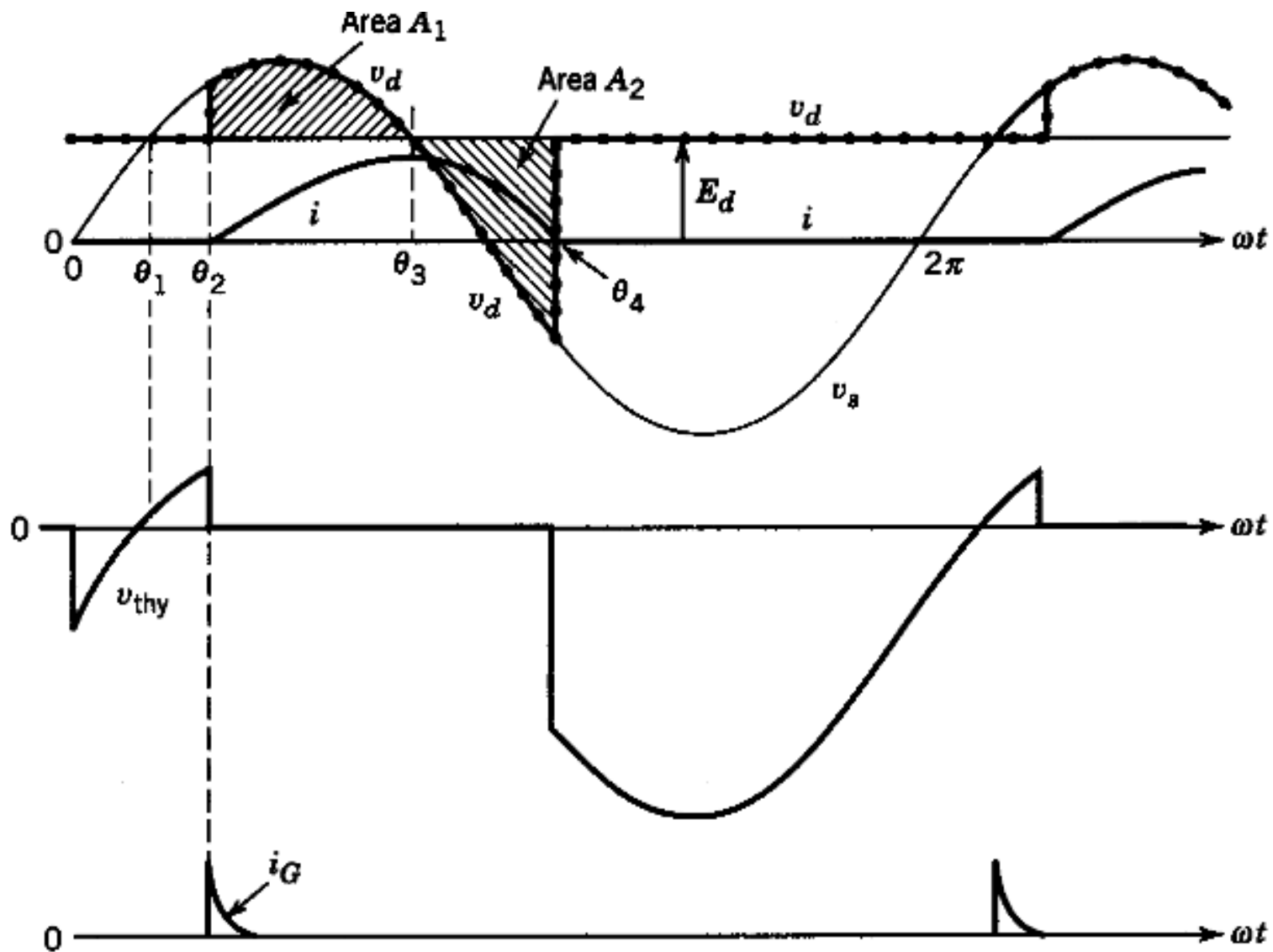

Single phase Fully Controlled bridge rectifier

- R Load

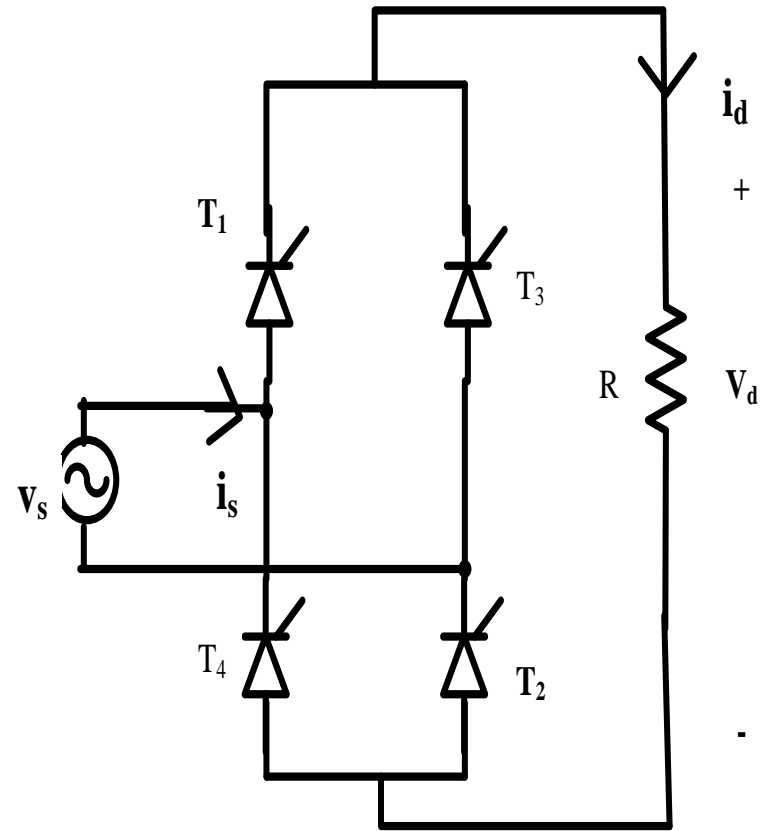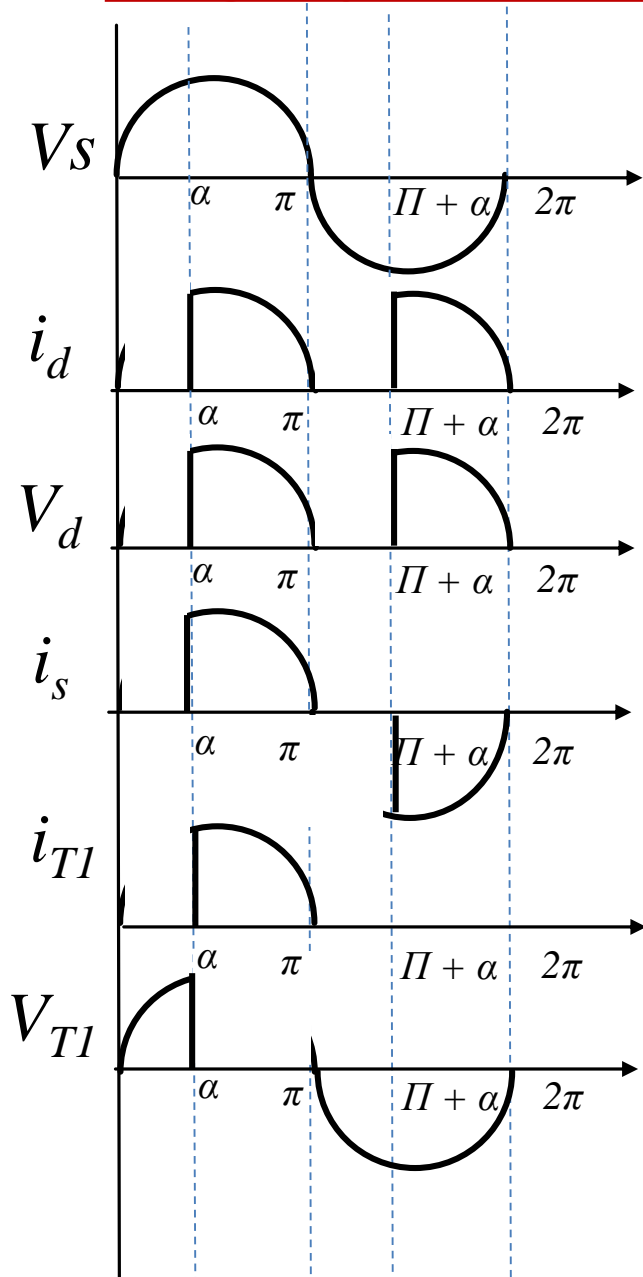


- R – L Load - Discontinuous current mode


- $V_d = \frac{\alpha \rightarrow \theta_1}{Ri_d(t) + L \frac{di_d(t)}{dt}} = V_s = \sqrt{2}v_s \sin \omega t$ T_1 and T_2 conduct
- $i_d = Ri_d(t) + L \frac{di_d(t)}{dt}$
- $i_s = i_d$
- $v_{T1} = 0, v_{T2} = 0$
- $v_{T3} = -V_s$
- At $\omega t = \theta_1, i_d = 0$
- $i_{T1} = i_{T2} = 0$
- Both T_1 and T_2 go to the off state

• $\theta_1 \rightarrow \pi + \alpha$
 T_1, T_2, T_3 and T_4 remain in the off state

$i_s = i_d = 0, v_d = 0,$

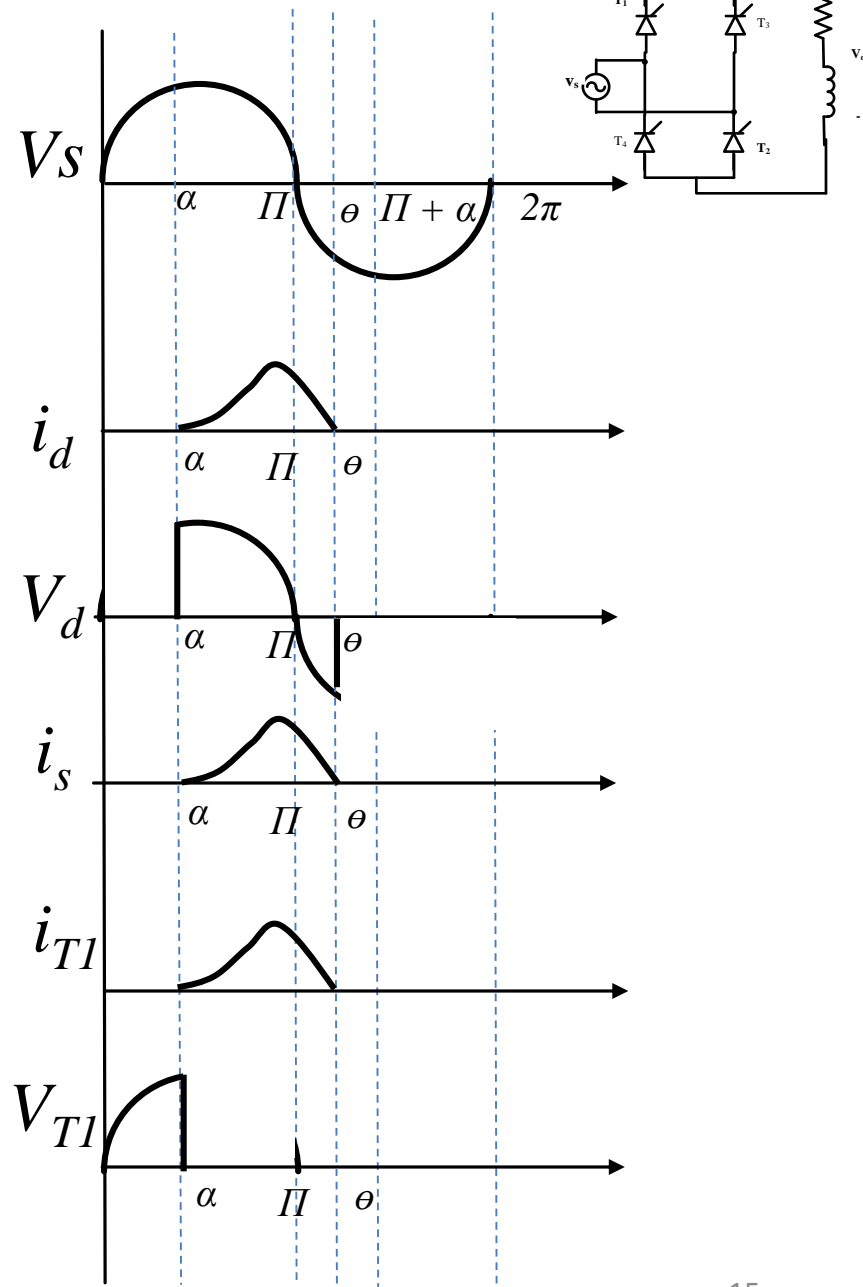

- $\pi + \alpha \rightarrow \pi + \theta_1$ T_3 and T_4 conduct
- $\mathbf{V_d} = Ri_d(t) + L \frac{di_d(t)}{dt} = -\mathbf{V_s} = -\sqrt{2}v_s \sin \omega t$
- $\mathbf{i_d} =$
- $\mathbf{i_s} = -\mathbf{i_d}$
- $\mathbf{v_{T1}} = \mathbf{v_s} = \mathbf{v_{T2}}$
- **At $\omega t = \underline{\pi + \theta_1}$, $\mathbf{i_d} = 0$**
- $\mathbf{i_{T3}} = \mathbf{i_{T4}} = 0$
- **Both T_3 and T_4 go to the off state**
- $\pi + \theta_1 \rightarrow 2\pi + \alpha$
- T_1 T_2 T_3 and T_4 remain in the off state
- $\mathbf{i_s} = \mathbf{i_d} = 0$, $\mathbf{v_d} = 0$,

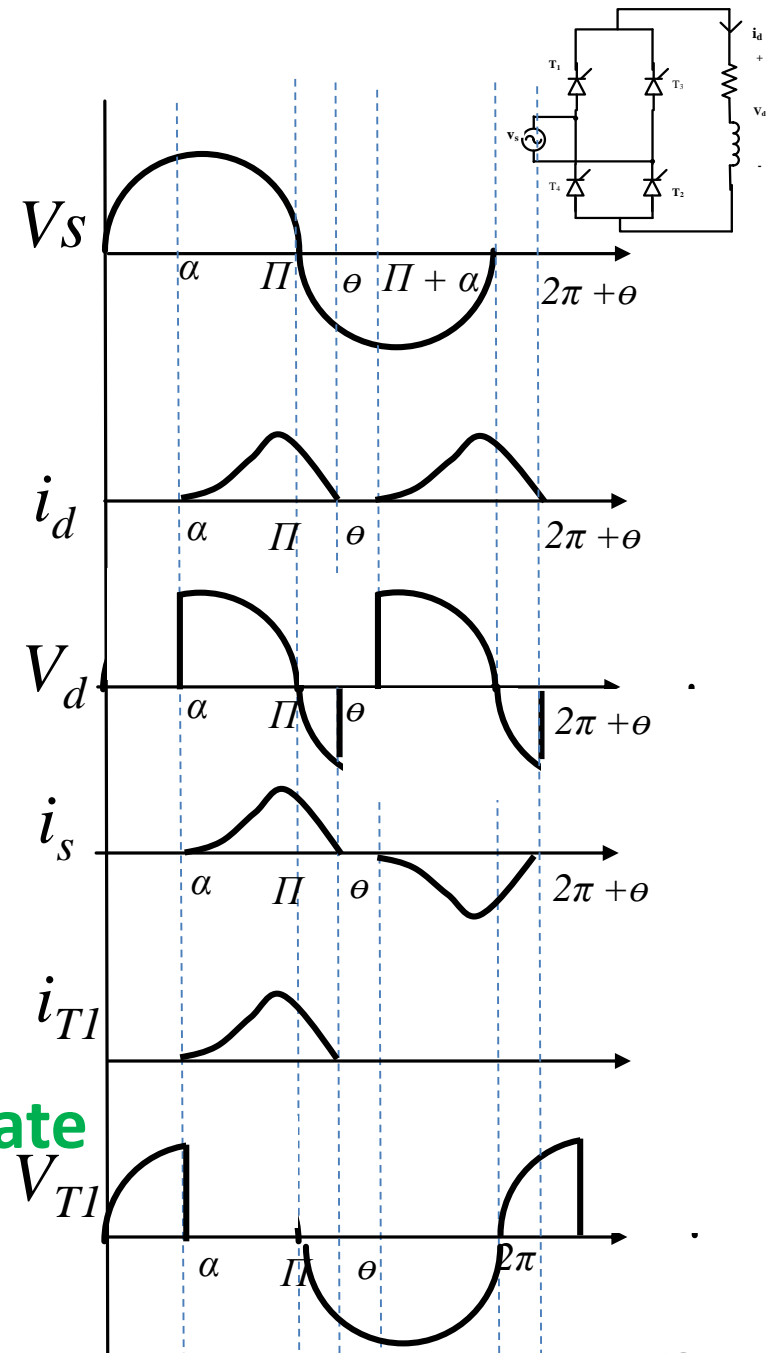

R – L Load, Continuous Current Mode

For $\omega t < \alpha$, T_3 & T_4 were conducting

At $\omega t = \alpha$, $i_d = I_1$ ($\neq 0$)

T_1 and T_2 are turned on

$\alpha \rightarrow \Pi + \alpha$

T_1 and T_2 conduct.

T_3 and T_4 are in the off state


$$V_d = V_s = \sqrt{2}V_s \sin \omega t = Ri_d + L \frac{di_d}{dt}$$



$$i_s = i_d$$

$$V_{T3} = -V_s = V_{T4}$$



At $\omega t = \alpha$, $i_d = +I_1$

$$RI_1 + L \left. \frac{di_d}{dt} \right|_{\omega t = \alpha} = \sqrt{2}V_s \sin \alpha$$

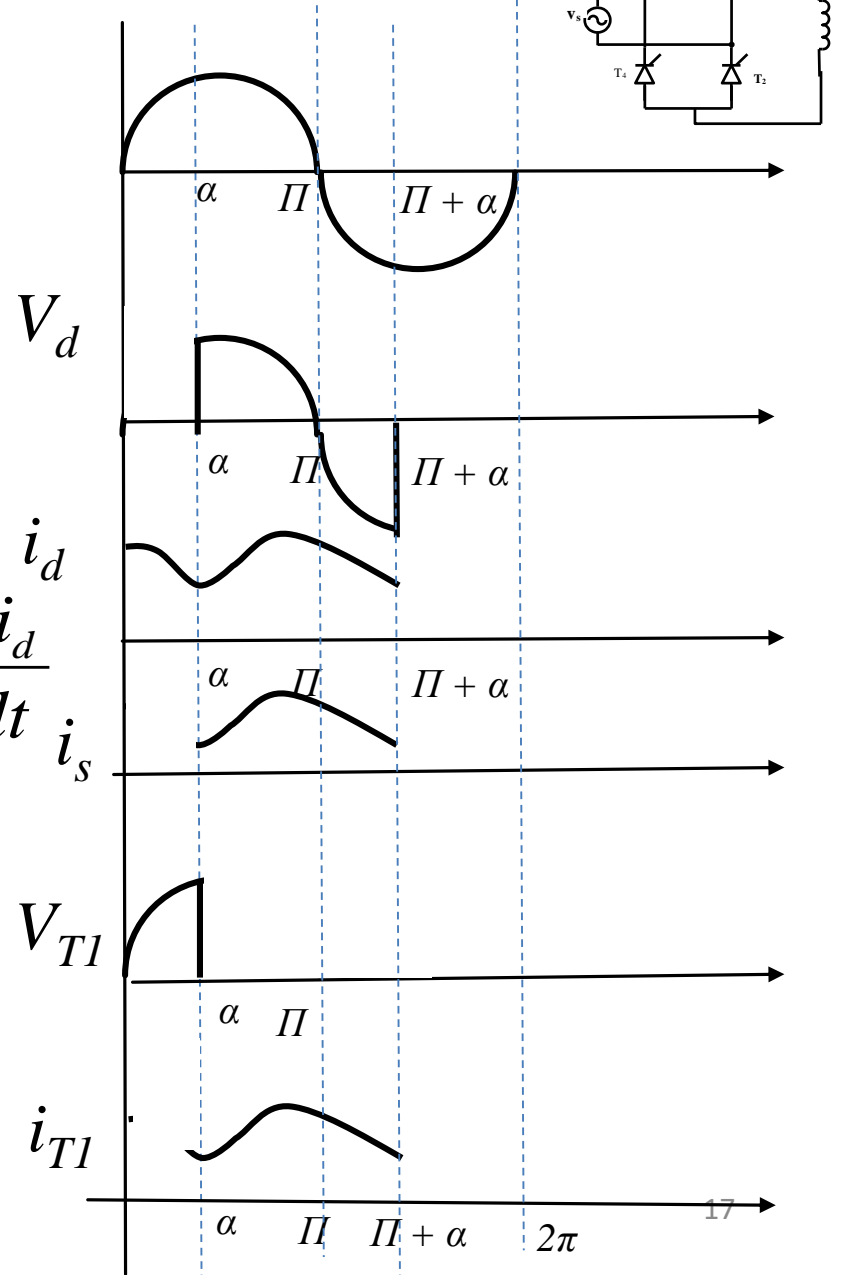


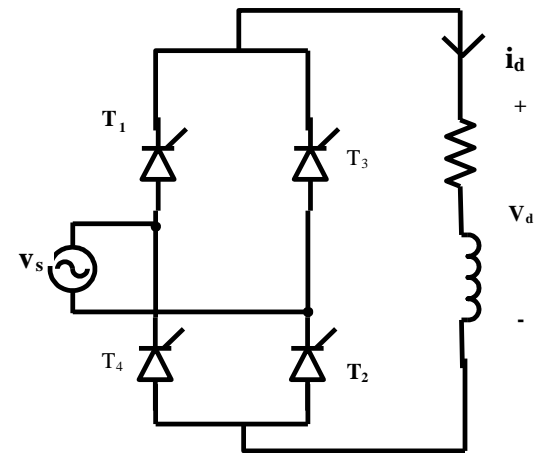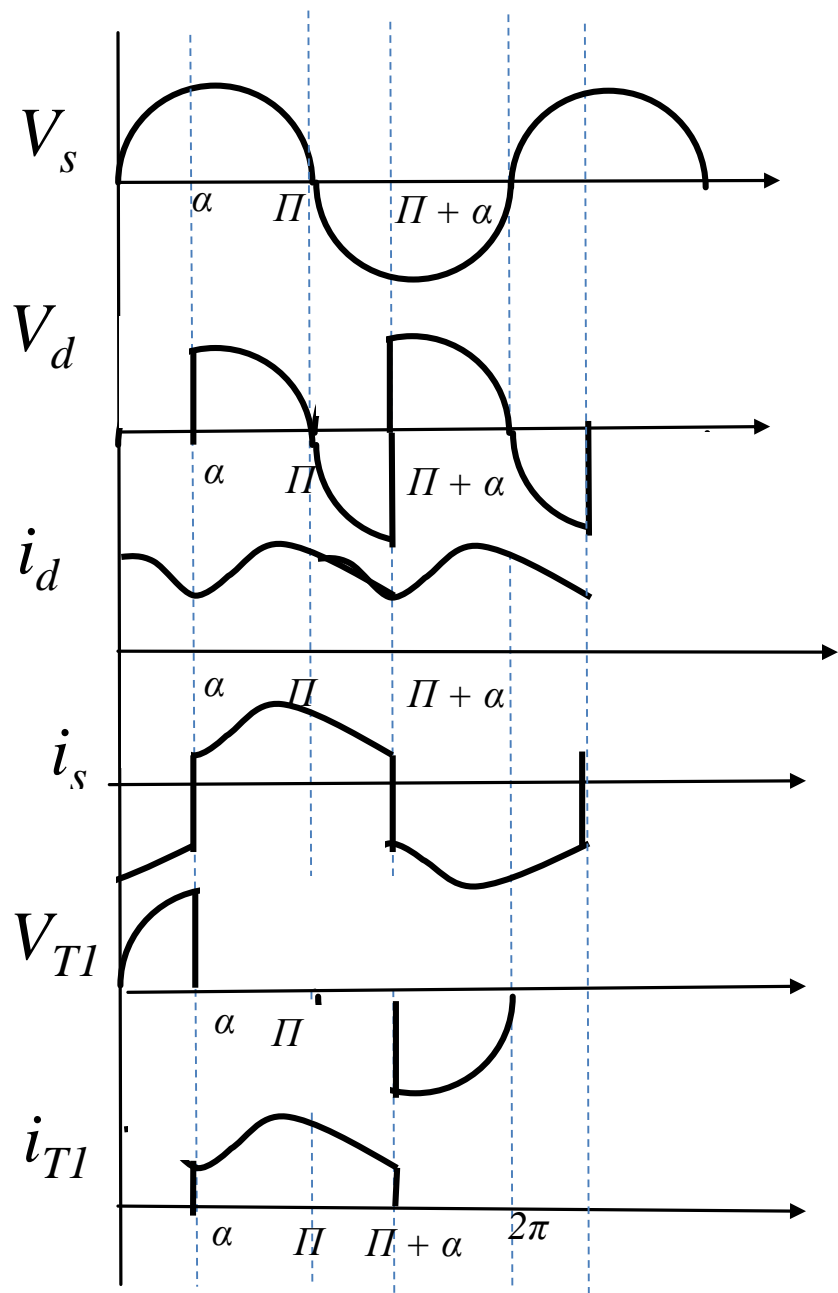

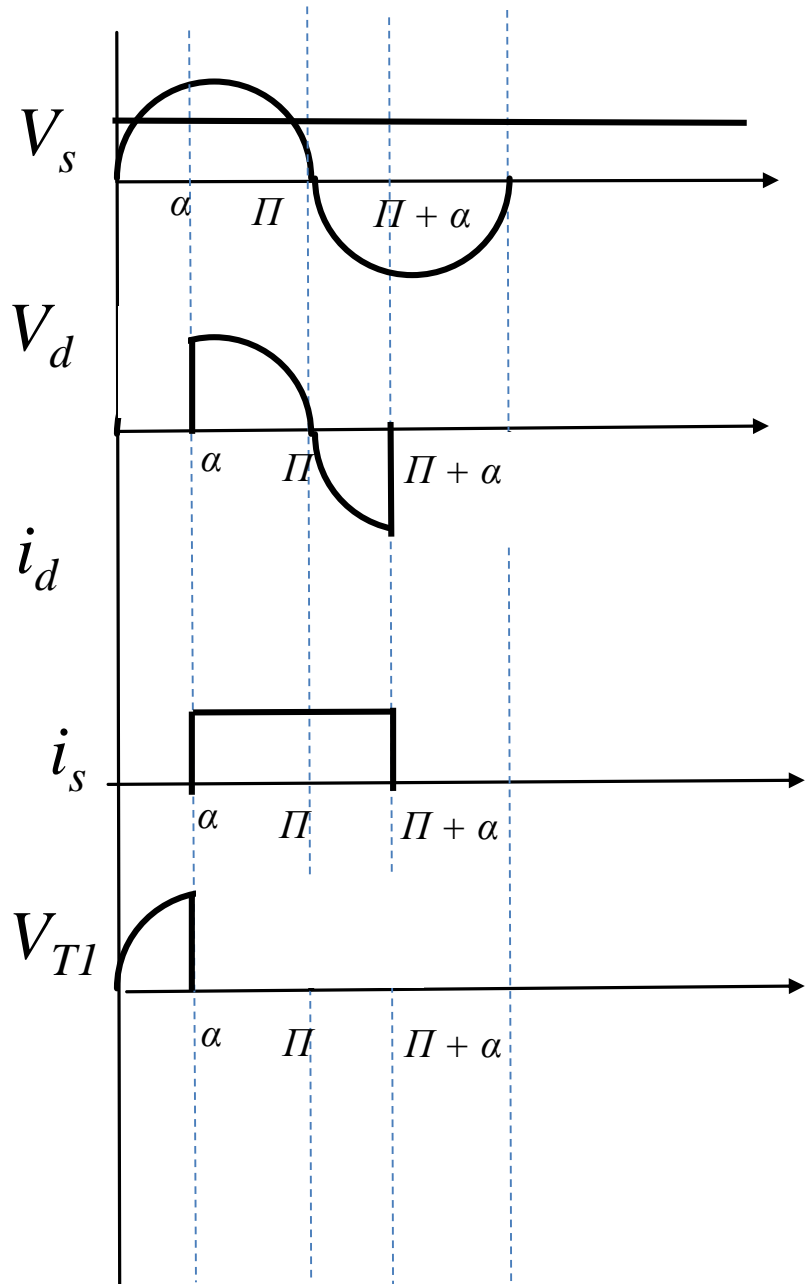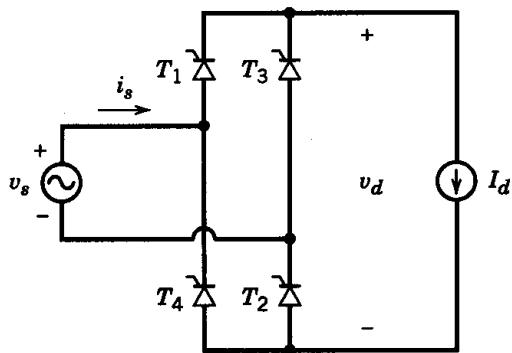- At $\Pi + \alpha$, T_3 and T_4 are turned on
- T_1 and T_2 are line commutated
- $\Pi + \alpha \rightarrow 2\Pi + \alpha$
- T_3 and T_4 conduct.
- $V_d = -V_s$
- $i_s = -i_d$
- $V_{T1} = v_s = V_{T2}$



R – L Load, constant load current I_d

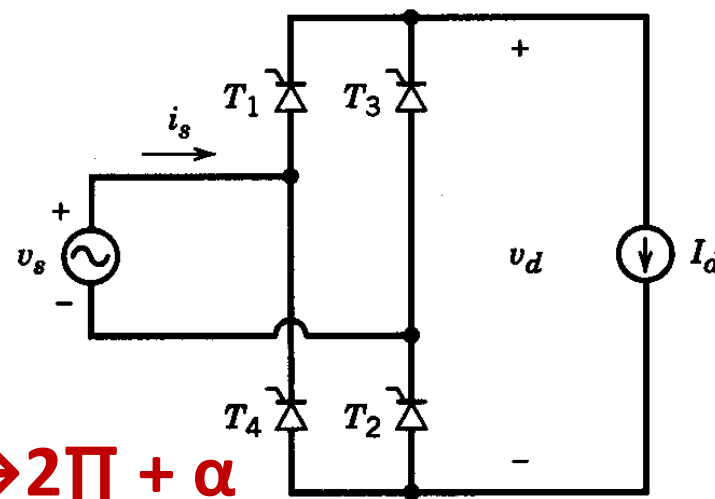

$$\underline{\alpha \rightarrow \Pi + \alpha}$$

T_1 and T_2 conduct,
 T_3 and T_4 are line
 commutated

$$V_d = V_s$$

$$i_s = I_d$$

$$V_{T3} = -v_s = V_{T4}$$

- $\Pi + \alpha \rightarrow 2\Pi + \alpha$
- T_3 and T_4 conduct,
- T_1 and T_2 are line commutated

- $V_d = -V_s$

- $i_s = -I_d$

- $V_{T1} = v_s = V_{T2}$

$$\Pi + \alpha \rightarrow 2\Pi + \alpha$$


T_3 and T_4 conduct,



T_1 and T_2 are line commutated

$$V_d = -V_s$$

$$i_s = -i_d$$

$$V_{T1} = v_s = V_{T2}$$

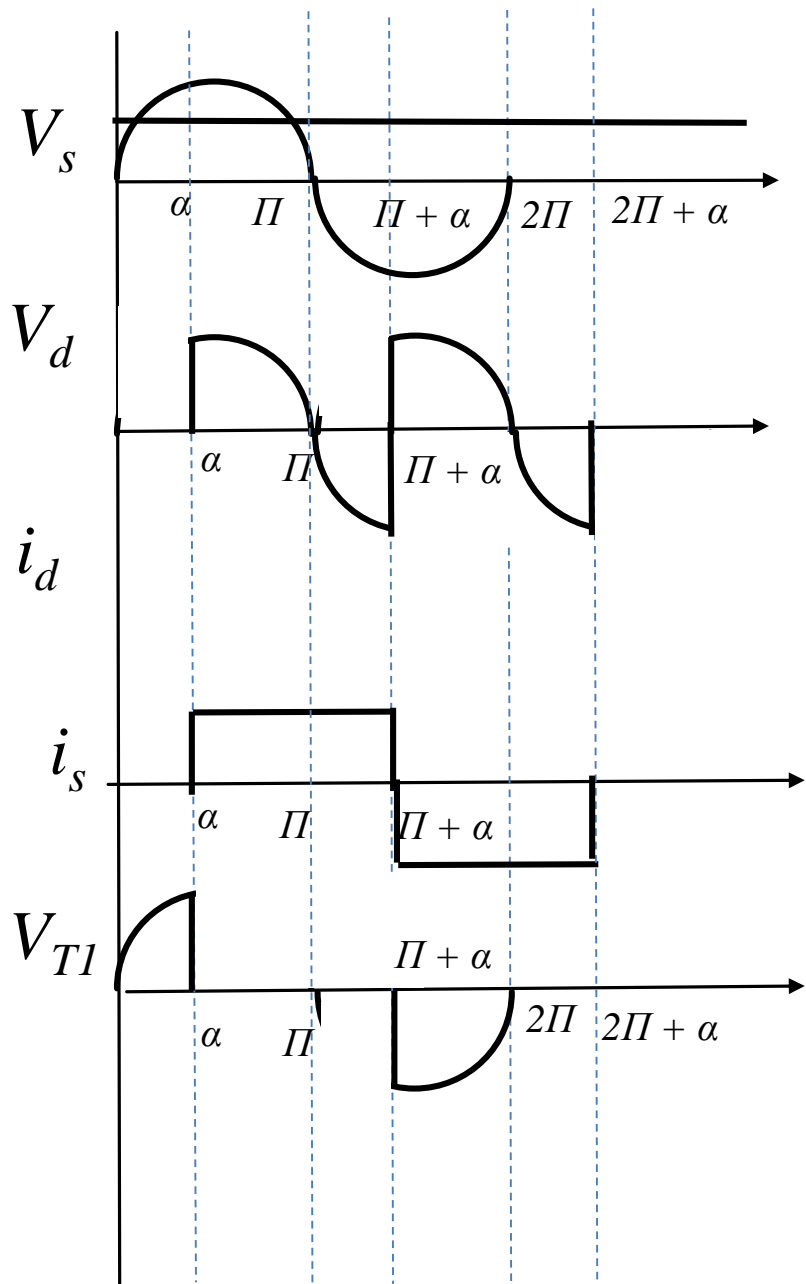

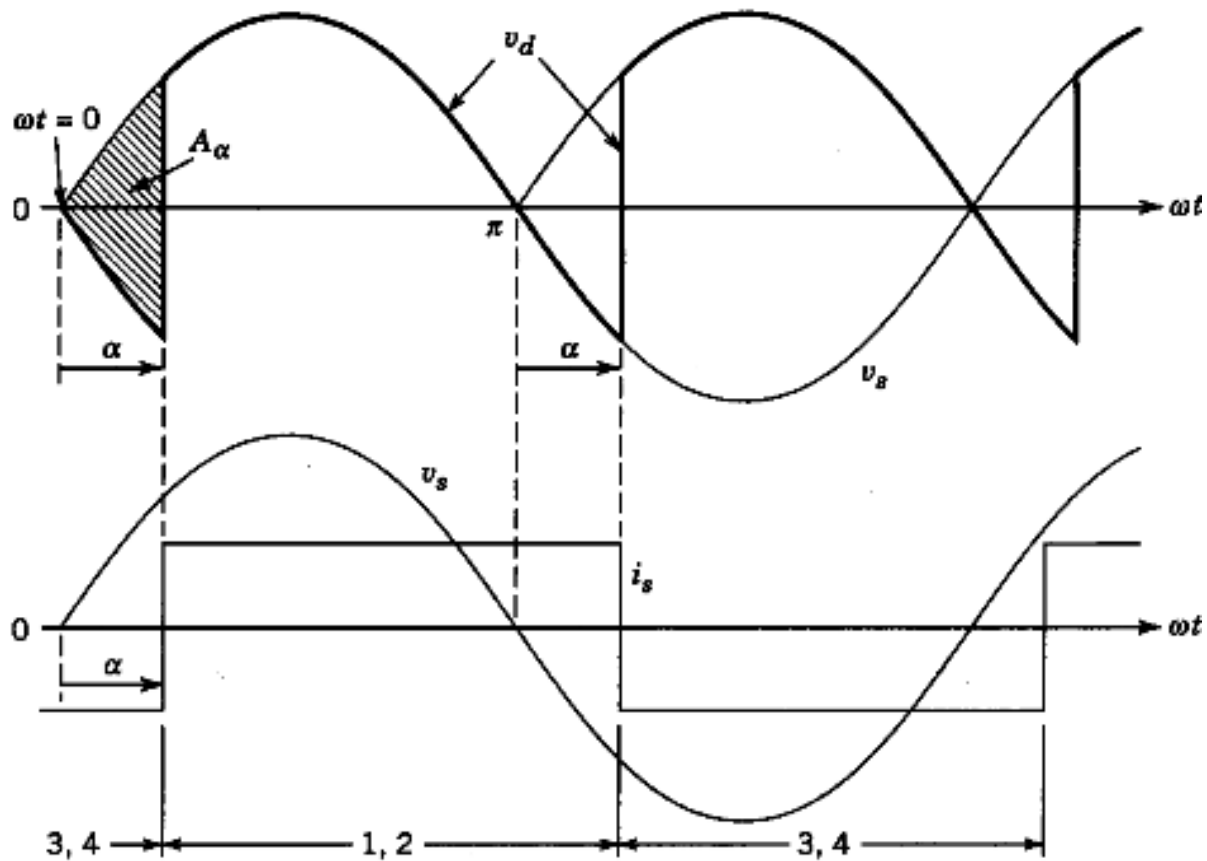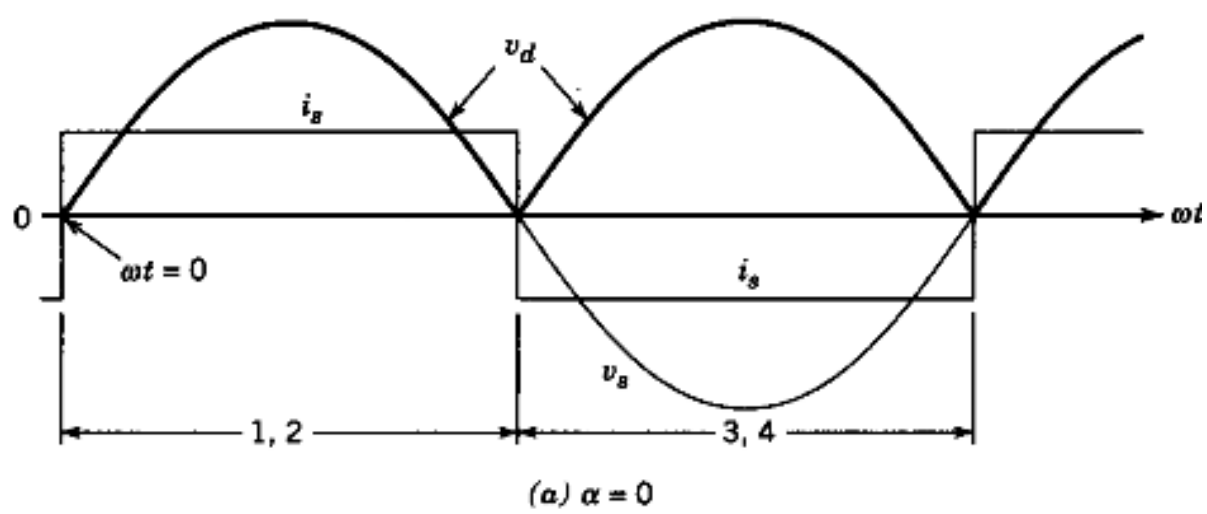

Performance parameters

- DC Side

- Average load voltage

$$V_{davg} = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} (\sqrt{2}V_s \sin \omega t) d\omega t$$
$$= \frac{2\sqrt{2}V_s \cos \alpha}{\pi} = 0.9V_s \cos \alpha$$

$$V_{dRMS} = V_s$$

- Average Power through the converter =

- $P = V_{davg} I_d = 0.9V_s I_d \cos \alpha$

- Ripple frequency = twice the line frequency

- Voltage Ripple Factor $K_v =$

$$i_s(t) = a_0 + \sum_{1,2,3,\dots}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t \quad a_0 = 0$$

$$i_s(t) = \sum_1^{\infty} c_n \sin(n\omega t + \phi_n) \quad c_n = \sqrt{a_n^2 + b_n^2} \quad \phi_n = \tan^{-1} \frac{a_n}{b_n}$$

$$i_{s1}(t) = c_1 \sin(\omega t + \phi_1) \quad c_1 = \sqrt{a_1^2 + b_1^2}$$



$$a_1 = \frac{1}{\pi} \left[\int_{\alpha}^{\pi+\alpha} I_d \cos \omega t \, d\omega t + \int_{\pi+\alpha}^{2\pi+\alpha} -I_d \cos \omega t \, d\omega t \right] = -\frac{4I_d}{\pi} \sin \alpha$$

$$b_1 = \frac{1}{\pi} \left[\int_{\alpha}^{\pi+\alpha} I_d \sin \omega t \, d\omega t + \int_{\pi+\alpha}^{2\pi+\alpha} -I_d \sin \omega t \, d\omega t \right] = \frac{4I_d}{\pi} \cos \alpha$$

$$c_1 = \frac{4I_d}{\pi} \quad \phi_1 = \tan^{-1} \frac{a_1}{b_1} = -\alpha \quad i_{s1} = \frac{4I_d}{\pi} \sin(\omega t - \alpha)$$

- RMS value of i_{s1} $I_{s1} = \frac{2\sqrt{2}I_d}{\pi}$
- RMS value of h^{th} harmonic i_{sh} $I_{sh} = \frac{I_{s1}}{h}$
- $h = 3, 5, 7, \dots$
- RMS value of total source current i_s
- $I_s = I_d$
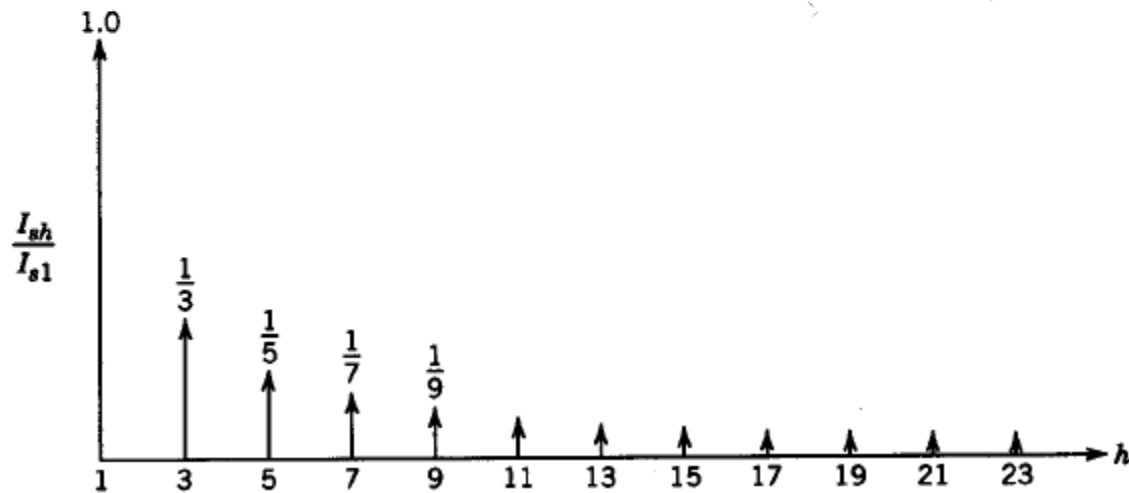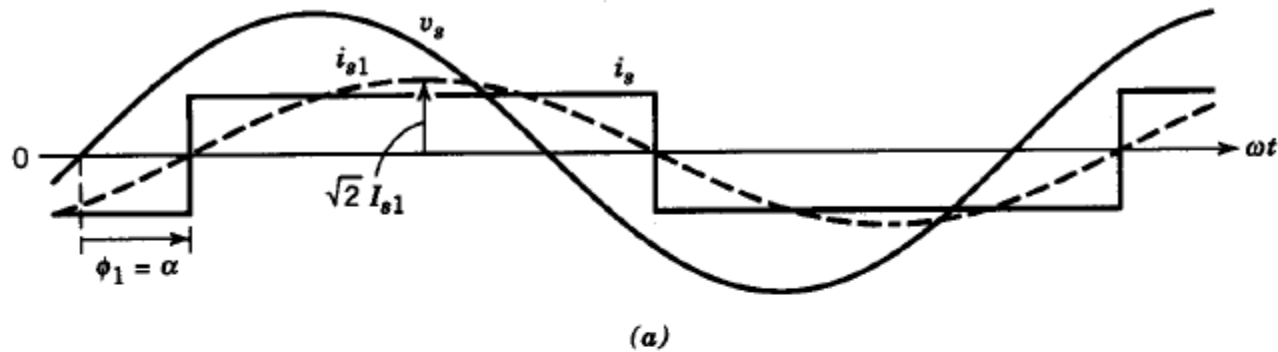
$$I_{sh} = \begin{cases} 0 & \text{for even } h \\ \frac{I_{s1}}{h} & \text{for odd } h \end{cases}$$



Harmonic spectrum

- **Total harmonic distortion THD =**

- $$\sqrt{\frac{I_s^2 - I_{s1}^2}{I_{s1}^2}} = 48.43 \%$$

- **Displacement factor**

- $$DF = \cos(-\alpha) = \cos \alpha$$

- **Ac side Power factor =**


$$\frac{V_s I_{s1} \cos \phi_1}{V_s I_s} = \frac{I_{s1} \cos \phi_1}{I_s} = \frac{2\sqrt{2}}{\pi} \cos \alpha$$

- Power at the source side

Total apparent Power $S = V_s I_s$

Active Power P

$$P = V_s I_{s1} \cos \phi_1$$

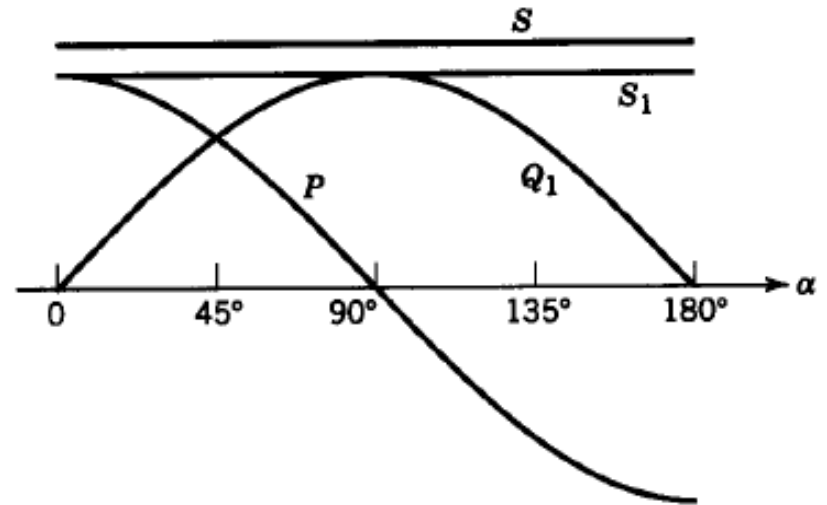


- Fundamental frequency current results in fundamental reactive volt amperes

- $Q_1 = V_s I_{s1} \sin \phi_1 = V_s I_{s1} \sin \alpha$

- Fundamental frequency apparent power

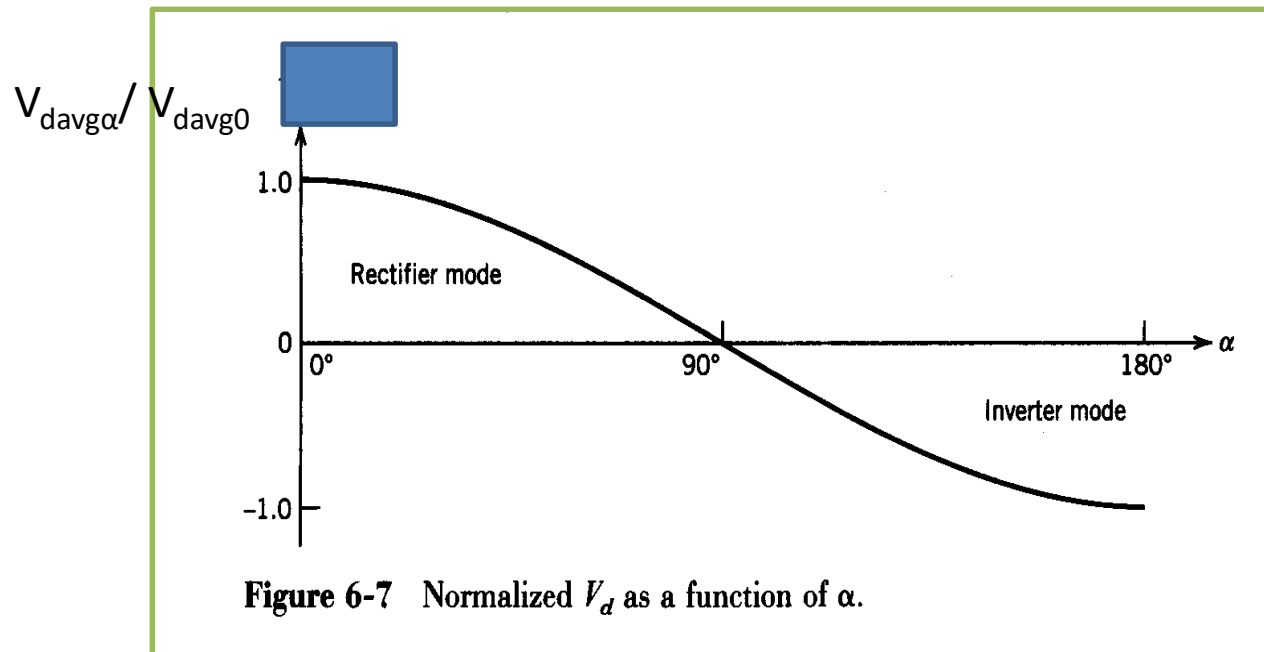- $S_1 = V_s I_{s1} = \sqrt{P^2 + Q_1^2}$



Effect of source inductance

- The current commutation takes a finite time called μ or commutation interval

constant load current I_d

$0 \rightarrow \alpha$

T_3 and T_4 are on
 T_1 and T_2 are off

$$V_d = -V_s$$


$$i_d = I_d$$

$$i_s = -I_d$$


$$V_{T3} = 0 = V_{T4}$$

$$V_{T1} = v_s = V_{T2}$$

At α , T_1 and T_2 are turned on

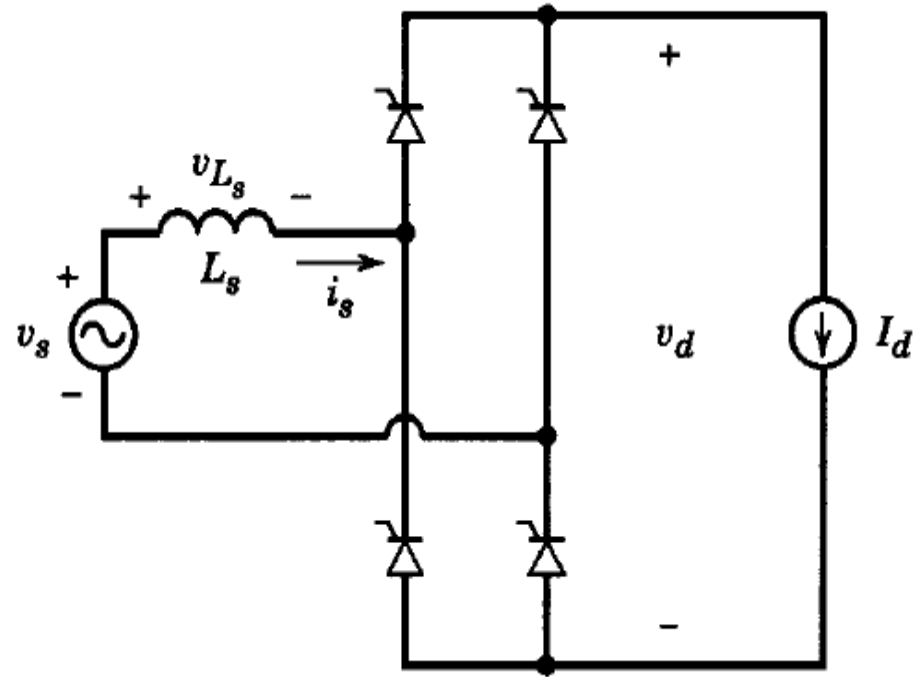

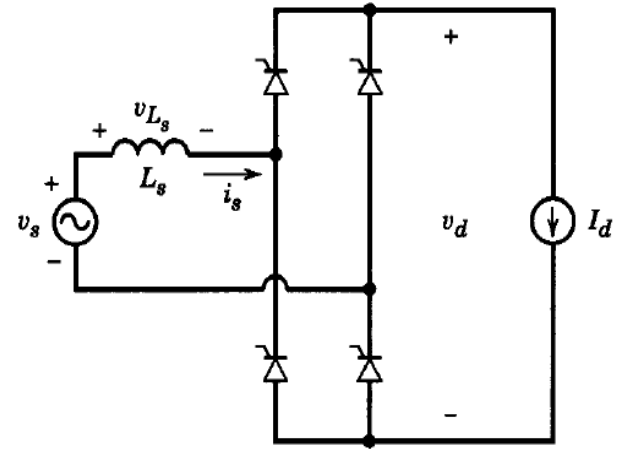- $\alpha \rightarrow \alpha + \mu$
- i_{T3} and i_{T4} decrease from $I_d \rightarrow 0$



i_{T1} and i_{T2} rise from $0 \rightarrow I_d$

T_1, T_2, T_3, T_4 are on

$$V_d = 0, \quad i_d = I_d$$

i_s varies from $-I_d$ to $\rightarrow I_d$.

$$V_{Ls} = V_s$$

At $(\alpha + \mu)$, $i_{T3} = 0 = i_{T4}$ T_3 and T_4 are turned off naturally

- $\alpha + \mu \rightarrow \Pi + \alpha$

T_1 and T_2 are on

T_3 and T_4 are off

$$V_d = V_s$$


$$i_d = I_d$$

$$i_s = I_d$$


$$V_{T1} = 0 = V_{T2}$$

$$V_{T3} = -V_s = V_{T4}$$

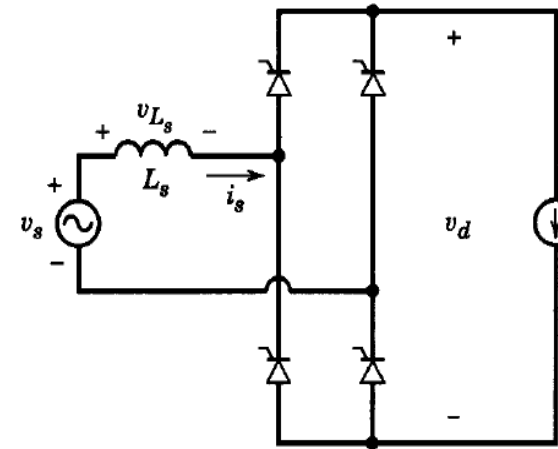At $\Pi + \alpha$, T_3 and T_4 are turned on



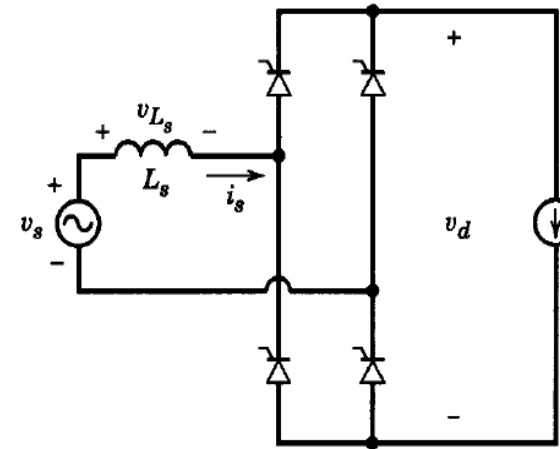- $\Pi + \alpha \rightarrow \Pi + \alpha + \mu$
- i_{T1}, i_{T2} decreases from $I_d \rightarrow 0$



i_{T3}, i_{T4} rises from $0 \rightarrow I_d$

T_1, T_2, T_3, T_4 conduct

$$V_d = 0, \quad i_d = I_d$$

i_s varies from $+I_d$ to $\rightarrow -I_d$.

$$V_{Ls} = V_s$$

At $(\Pi + \alpha + \mu)$, $i_{T1} = 0 = i_{T2}$ T_1 and T_2 are turned off

- $\underline{\Pi + \alpha + \mu \rightarrow 2\Pi + \alpha}$

- T_3 and T_4 are on

- T_1 and T_2 are off

- $V_d = -V_s$


- $i_d = I_d$

- $i_s = -I_d$

- $V_{T1} = v_s = V_{T2}$

- $V_{T3} = 0 = V_{T4}$

- $v_{Ls} = 0$

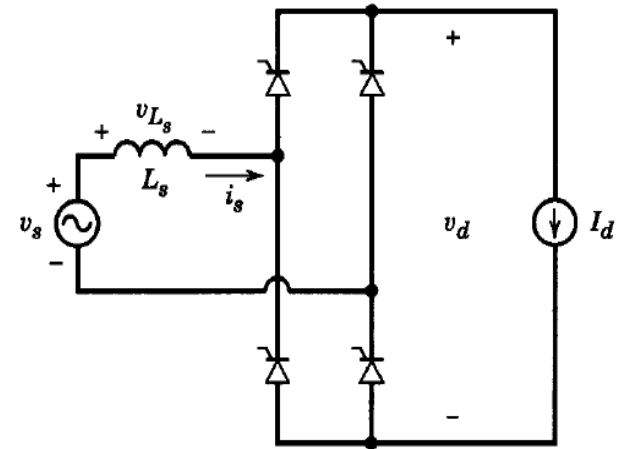

- During the commutation period μ , T_1 , T_2 , T_3 and T_4 are on

$$V_{LS} = V_s$$

$$\sqrt{2}V_s \sin \omega t = L_s \frac{di_s(t)}{dt} = \omega L_s \frac{di_s(t)}{d\omega t}$$

$$\frac{\sqrt{2}V_s}{\omega L_s} \sin \omega t \, d\omega t = di_s(t)$$

$$\int_{\alpha}^{\alpha+\mu} \frac{\sqrt{2}V_s}{\omega L_s} \sin \omega t \, d\omega t = \int_{-I_d}^{+I_d} di_s(t)$$

$$\frac{\sqrt{2}V_s}{\omega L_s} [\cos \alpha - \cos(\alpha + \mu)] = 2I_d$$

$$\cos(\alpha + \mu) = \cos \alpha - \frac{2\omega L_s I_d}{\sqrt{2}V_s}$$

- Average o/p voltage = $V_{davg} =$

$$\frac{1}{\pi} \int_{\alpha+\mu}^{\pi+\alpha} \sqrt{2}V_s \sin \omega t d\omega t =$$

$$= \frac{2\sqrt{2}V_s}{\pi} \cos \alpha - \frac{2\omega L_s I_d}{\pi}$$