

Space Vector PWM

Switching States (Three-Phase)

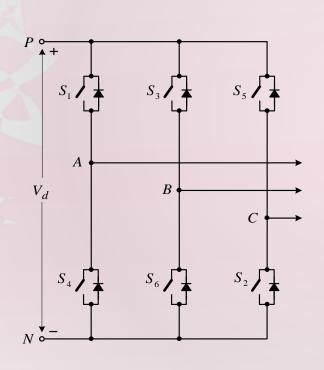

Switching State (Three Phases)	On-state Switch
[PPP]	S_1, S_3, S_5
[000]	S_4, S_6, S_2
[POO]	S_1, S_6, S_2
[PPO]	S_1, S_3, S_2
[OPO]	S_4, S_3, S_2
[OPP]	S_4, S_3, S_5
[OOP]	S_4, S_6, S_5
[POP]	S_{1}, S_{6}, S_{5}

Space Vector Diagram

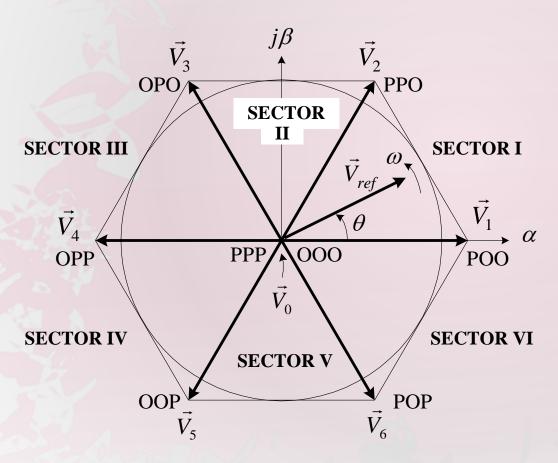

Active vectors: \vec{V}_1 to \vec{V}_6 (stationary, not rotating)

Zero vector: $\vec{V}_{_0}$

Six sectors: I to VI

Space Vectors

Three-phase voltages

$$v_{AO}(t) + v_{BO}(t) + v_{CO}(t) = 0$$
 (1)

Two-phase voltages

$$\begin{bmatrix} v_{\alpha}(t) \\ v_{\beta}(t) \end{bmatrix} = \begin{bmatrix} \cos 0 & \cos \frac{2\pi}{3} & \cos \frac{4\pi}{3} \\ \sin 0 & \sin \frac{2\pi}{3} & \sin \frac{4\pi}{3} \end{bmatrix} \begin{bmatrix} v_{AO}(t) \\ v_{BO}(t) \\ v_{CO}(t) \end{bmatrix}$$
 (2)

Space vector representation

$$\vec{\vec{V}}(t) = v_{\alpha}(t) + j v_{\beta}(t) \tag{3}$$

$$(2) \to (3)$$

$$\vec{V}(t) = \left[v_{AO}(t) e^{j0} + v_{BO}(t) e^{j2\pi/3} + v_{CO}(t) e^{j4\pi/3} \right]$$
 (4)

where $e^{jx} = \cos x + j \sin x$

Space Vectors (Example)

Switching state [POO] $\rightarrow S_1$, S_6 and S_2 ON


$$v_{AO}(t) = V_d, \quad v_{BO}(t) = -\frac{1}{2}V_d, v_{CO}(t) = -\frac{1}{2}V_d$$

$$(5) \rightarrow (4)$$


$$\vec{V_1} = V_d e^{j0}$$

$$\vec{V}_k = V_d e^{j(k-1)\frac{\pi}{3}}$$

$$k = 1, 2, ..., 6.$$

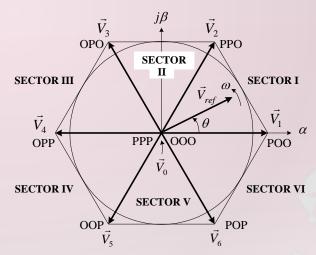

Active and Zero Vectors

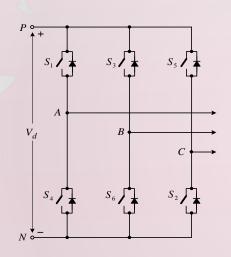

Active Vector: 6
Zero Vector: 1

Redundant switching

states: [PPP] and [OOO]

Space Vector		Switching State (Three Phases)	On-state Switch	Vector Definition	
Zero	$ec{V}_0$	[PPP]	S_1, S_3, S_5	$\vec{V}_0 = 0$	
Vector	v ₀	[000]	S_4, S_6, S_2	V ₀ = 0	
Active Vector	$ec{V}_1$	[POO]	S_1, S_6, S_2	$\vec{V_1} = V_d e^{j0}$	
	$ec{V}_2$	[PPO]	S_1, S_3, S_2	$\vec{V}_2 = V_d e^{j\frac{\pi}{3}}$	
	\vec{V}_3	[OPO]	S_4, S_3, S_2	$\vec{V}_3 = V_d e^{j\frac{2\pi}{3}}$	
	$ec{V}_4$	[OPP]	S_4, S_3, S_5	$\vec{V_4} = V_d e^{j\frac{3\pi}{3}}$	
	\vec{V}_5	[OOP]	S_4, S_6, S_5	$\vec{V}_5 = V_d e^{j\frac{4\pi}{3}}$	
	\vec{V}_6	[POP]	S_1, S_6, S_5	$\vec{V}_6 = V_d e^{j\frac{5\pi}{3}}$	

Reference Vector V_{ref}

Definition


$$\vec{V}_{ref} = V_{ref} e^{j\theta}$$

Rotating in space at ω

$$\omega = 2\pi f \tag{8}$$

Angular displacement
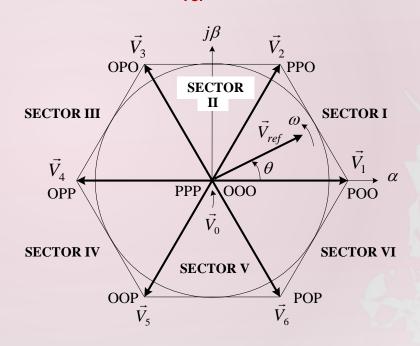
$$\theta(t) = \int_0^t \omega \, dt \qquad \textbf{(9)}$$




Relationship Between V_{ref} and V_{AB}

V_{ref} is approximated by two active and zero vectors

 V_{ref} rotates one revolution, V_{AB} completes one cycle

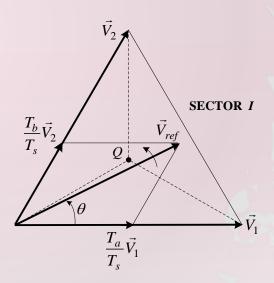Length of V_{ref} corresponds to magnitude of V_{AB}




Dwell Time Calculation

Volt-Second Balancing

$$\begin{cases} \vec{V}_{ref} \ T_s = \vec{V}_1 T_a + \vec{V}_2 T_b + \vec{V}_0 T_0 \\ T_s = T_a + T_b + T_0 \end{cases}$$
 (10)

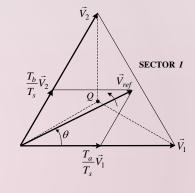 $extbf{\textit{T}_a}$, $extbf{\textit{T}_b}$ and $extbf{\textit{T}_0}$ – dwell times for $\vec{V_1}, \vec{V_2}$ and $\vec{V_0}$



 T_s – sampling period

Space vectors

$$\vec{V}_{ref} = V_{ref} e^{j\theta}, \ \vec{V}_1 = V_d, \vec{V}_2 = V_d e^{j\frac{\pi}{3}} \text{ and } \vec{V}_0 = 0$$
 (11)


(11)
$$\rightarrow$$
 (10)
$$\begin{cases}
\mathbf{Re}: \ V_{ref}(\cos\theta)T_s = V_d T_a + \frac{1}{2}V_d T_b \\
\mathbf{Im}: \ V_{ref}(\sin\theta)T_s = \frac{\sqrt{3}}{2}V_d T_b
\end{cases}$$
(12)

Dwell Times

Solve (12)

$$\begin{cases} T_a = \frac{2T_s V_{ref}}{\sqrt{3} V_d} \sin(\frac{\pi}{3} - \theta) \\ T_b = \frac{2T_s V_{ref}}{\sqrt{3} V_d} \sin\theta \\ T_0 = T_s - T_a - T_b \end{cases}$$
 (13)

V_{ref} Location versus Dwell Times

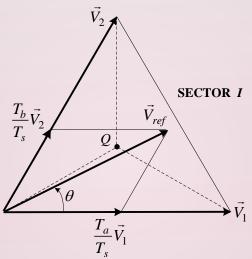

$ec{V}_{ref}$ Location	$\theta = 0$	$0 < \theta < \frac{\pi}{6}$	$\theta = \frac{\pi}{6}$	$\frac{\pi}{6} < \theta < \frac{\pi}{3}$	$\theta = \frac{\pi}{3}$
Dwell Times	$T_a > 0$ $T_b = 0$	$T_a > T_b$	$T_a = T_b$	$T_a < T_b$	$T_a = 0$ $T_b > 0$

Modulation Index

$$\begin{cases} T_a = T_s m_a \sin(\frac{\pi}{3} - \theta) \\ T_b = T_s m_a \sin \theta \\ T_0 = T_s - T_b - T_c \end{cases}$$
 (15)

$$m_a = \frac{2V_{ref}}{\sqrt{3}V_d} \tag{16}$$

Modulation Range


 $V_{ref,max}$

$$V_{ref, \text{max}} = V_d \times \frac{\sqrt{3}}{2} = \frac{\sqrt{3}V_d}{2}$$
 (17)

$$(17) \to (16)$$

$$m_{a,max} = 1 \rightarrow$$

Modulation range: $0 \le m_a \le 1$

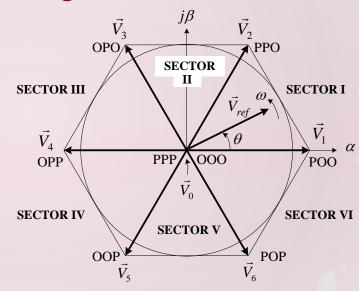

(18)

Switching Sequence Design

Basic Requirement:

Minimize the number of switchings per sampling period T_s

Implementation:


Transition from one switching state to the next involves only two switches in the same inverter leg.

Seven-segment Switching Sequence

Selected vectors: V_0 , V_1 and V_2


Dwell times:

$$T_s = T_0 + T_a + T_b$$

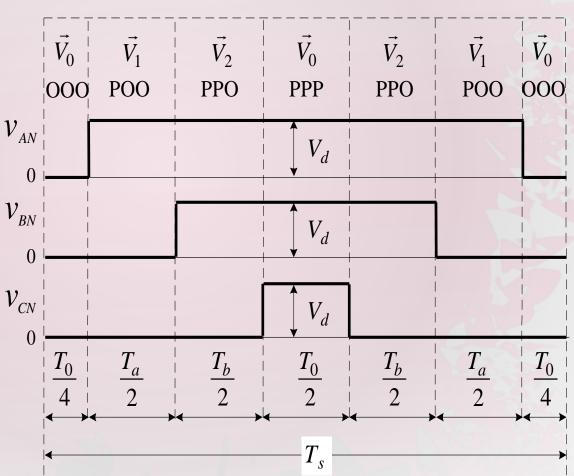


Undesirable Switching Sequence


Vectors V_1 and V_2 swapped

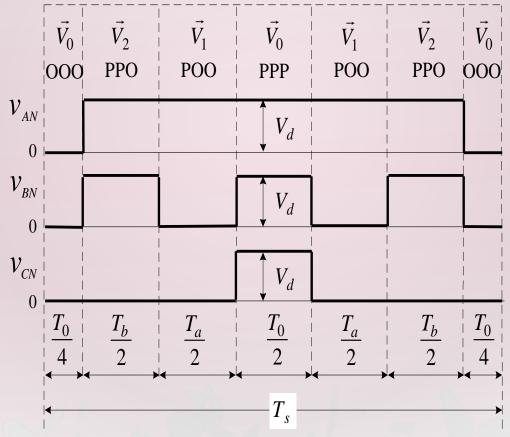


Simulated Waveforms

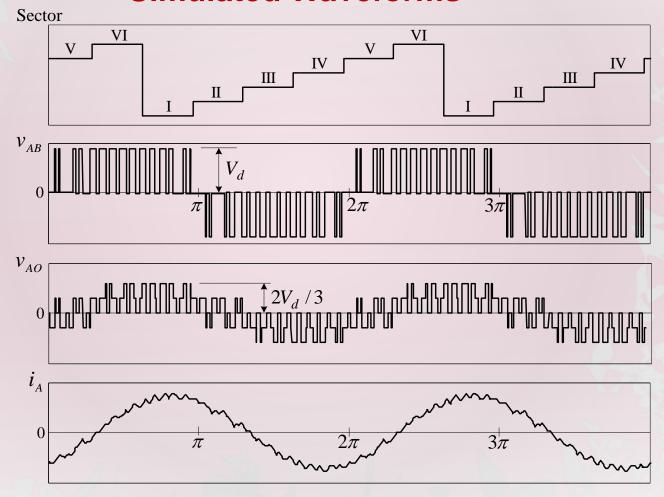


Waveforms and FFT

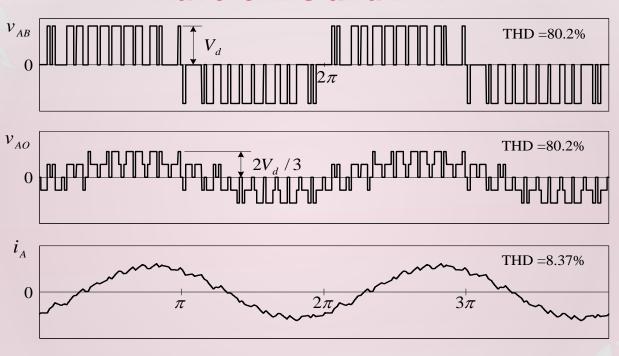


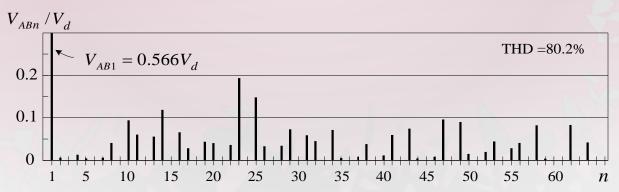

SVPWM - Modified SinePWM

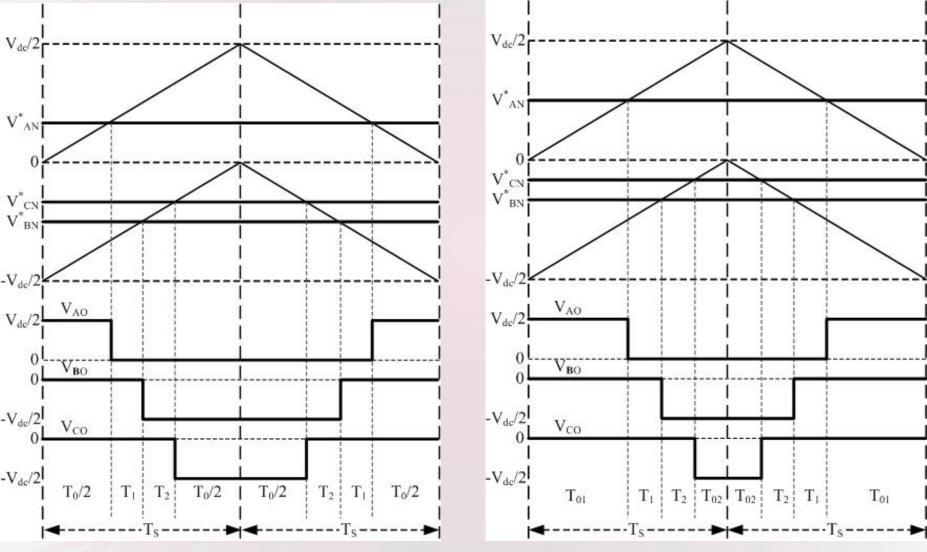

SVPWM - Modified SinePWM

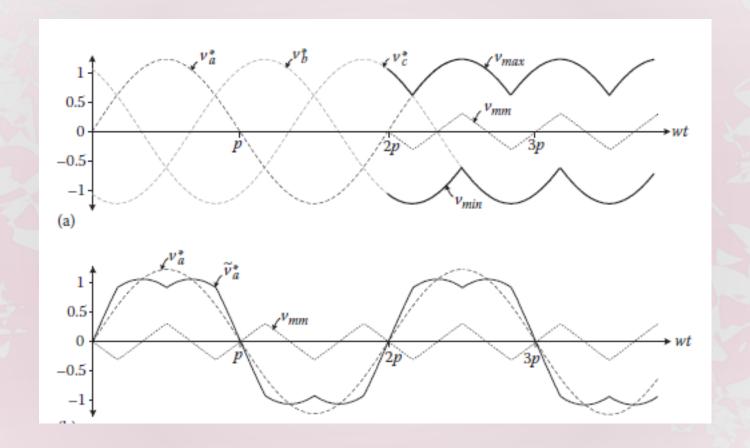

SVPWM - Modified SinePWM

