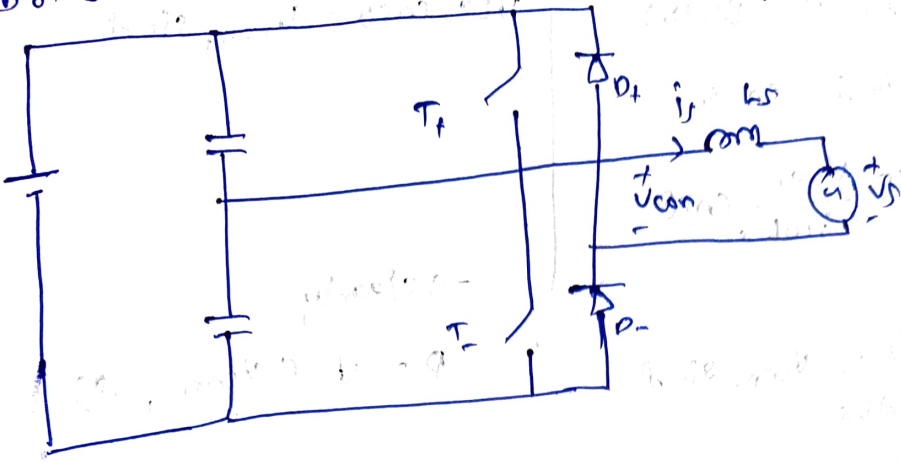


Q4) Regeneration mode of IM through a half bridge inverter.



→ in regenerative mode i.e. rectification mode, the energy is fed back for IM to the source of the system.  
i.e. IM works as asynchronous generator.

$$-V_{con} + V_{LS} + V_s = 0$$

$$\therefore V_{con} = V_{LS} + V_s$$

$V_s = \text{sinusoidal back emf}$

$$V_{LS} = L_s \frac{di_s}{dt}$$

$$\text{or } V_{LS} = j\omega L_s i_s$$

∴ taking fundamental frequency

$$V_{con,1} \approx V_{LS,1} + V_s$$

$$\text{or } V_{con,1} = L_s \frac{di_{s,1}}{dt} + V_s$$


$$\& V_s = V_{con,1} - V_{LS,1}$$

$$V_s = V_{con,1} - j\omega L_s i_{s,1}$$

∴ direction of  $i_s$  decides inverter or rectification mode.  
→ for regenerative i.e. rectification mode,  $i_s$  is -ve or backward direction.

∴ Rectification mode

→  $V_{con,1}$  lags  $V_s$  by  $\phi$

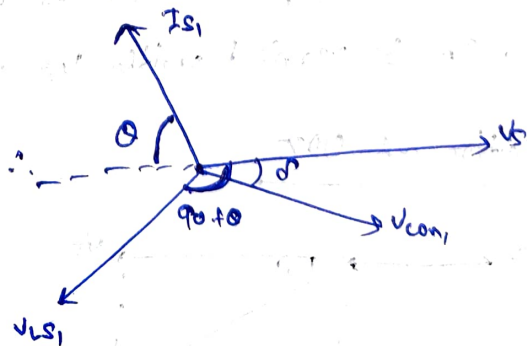

→ real power at ac side

$$P = V_s I_s \cos(180 + \theta)$$

$$\text{or } P = -V_s I_s \cos \theta$$

$$P = -V_s \frac{V_{Ls1}}{j\omega L_s} \cos \theta$$

$$\therefore P = -\frac{V_s}{j\omega L_s} V_{con1} \sin \theta$$

$$\text{or } P = -\frac{V_s^2}{j\omega L_s} \cdot \frac{V_{con1}}{V_s} \sin \theta$$

→ reactive power

$$Q = V_s I_s \sin(180 + \theta)$$

$$= V_s I_s (-\sin \theta)$$

$$= -V_s \frac{V_{Ls1}}{j\omega L_s} \sin \theta$$


$$= -\frac{V_s}{j\omega L_s} [V_s - V_{con1} \cos \theta]$$

$$\text{or } Q = -\frac{V_s^2}{j\omega L_s} \left[ 1 - \frac{V_{con1}}{V_s} \cos \theta \right]$$

∴ value of  $P$  &  $Q$  can be varied by manipulating the value of  $V_{con1}$  &  $\theta$  at  $L_s$  &  $V_s$  fixed.

→  $V_{con1}$  can be varied with  $V_s$  &  $I_s$  constant.

rectification at UPF

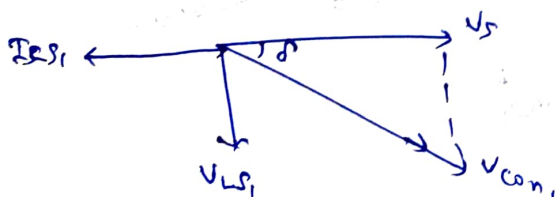

$$V_{con1} = \sqrt{V_s^2 - (\omega L_s I_s)^2}$$

also

$$V_{Ls1} \cos \theta = V_{con1} \sin \theta$$

→ clearly

$$P = f(V_{con1}, \theta)$$

also

$$V_{Ls1} = V_s - V_{con1} \cos \theta$$

$$\rightarrow \text{clearly } Q = f(V_{con1}, \theta)$$