

BUCK CONVERTER

Aim: To study the BUCK CONVERTER output Voltage which has a duty ratio of 0.75

Apparatus:


S.No	Components	Range	Quantity
1.	MOSFET	IRF540	1
2.	Inductor	30 mH	1
3.	Capacitor	100 μ F	1
4.	Diode	1N4004	1
5.	Rheostat	300 Ω / 1.2A	1
6.	Power Supply	0-30V	3
7.	555 Timer	-	1
8.	optocoupler	TCP2504	1
9.	Capacitor	0.1 μ F	1
		0.01 μ F	1
		0.1 μ F	1
10.	Resistor	750 Ω	1
		350 Ω	1
11.	CRO	digital	1

Theory:

A Buck Converter is a DC to DC power Converter that stepdown voltage with stepping up current from its supply to its load. The key principle of Buck Converter is charging & discharging of Inductor and Capacitor.

Applications of Buck Converter:

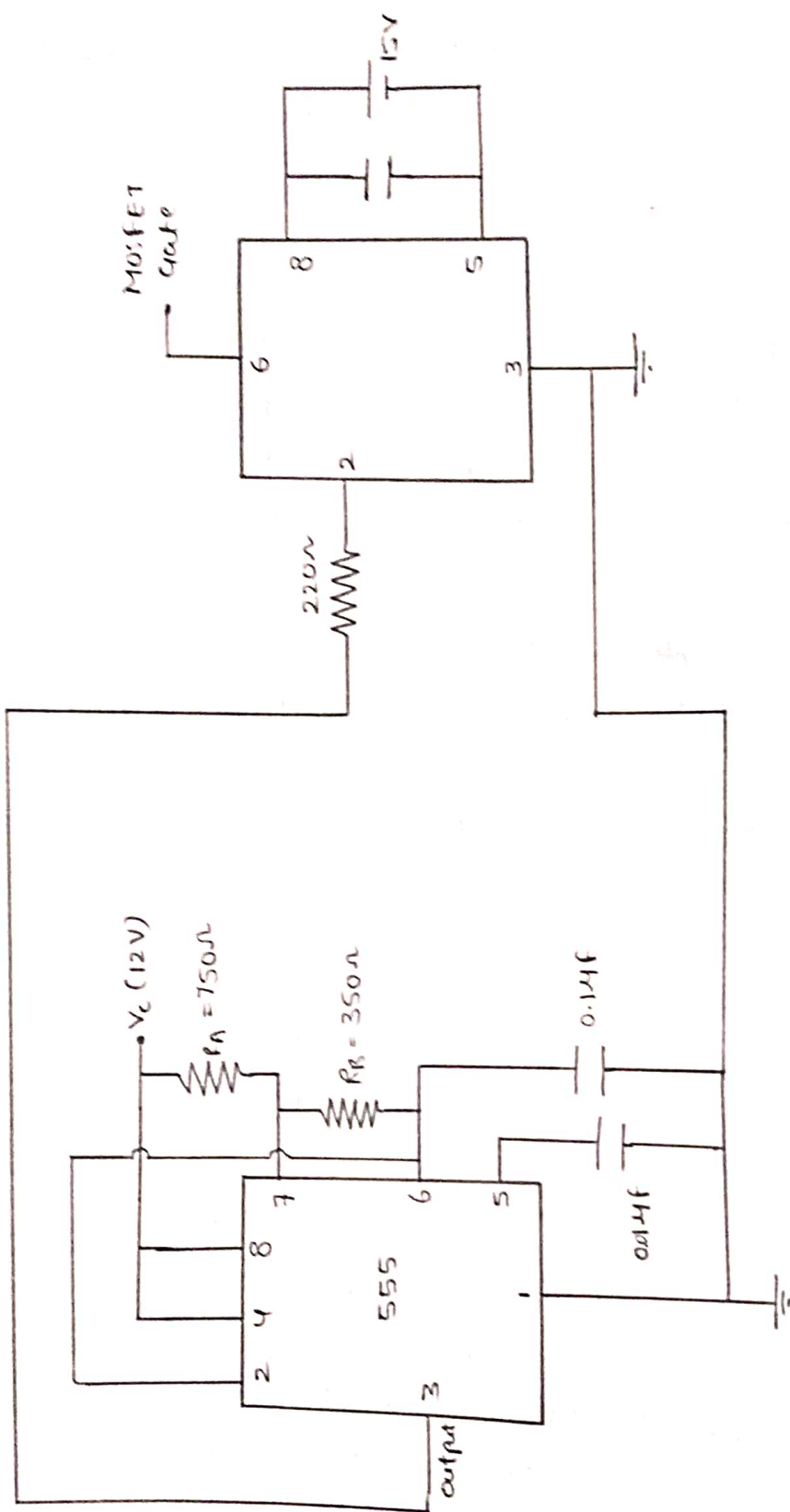- 1) Solar Chargers
- 2) Battery chargers
- 3) Quad Copters & Robotics etc..



procedure:

- 1) Connect the circuit as shown in the fig(a)
- 2) Given 12V to 555 timer the square wave generated not upto good magnitude to drive MOSFET
Hence, we given it to the optocoupler.
- 3) The output of optocoupler is given to fig(b)
- 4) The output waveform are observed in to CRO

Design & Calculations:

$$(V_{in} - V_o) D T_s = V_o (1-D) T_s$$

$$V_o = \frac{D T_s}{T_s} \cdot V_{in} = D V_{in}$$

$$I_s = \alpha I_o$$

$$I_L = I_o + I_c \text{ \& } I_c = I_L - I_o$$

$$\text{Inductor ripple Current (Peak-Peak), } \Delta I_L = \frac{V_{in} D (1-D)}{f_s L}$$

$$\text{Capacitor ripple Voltage (Peak-Peak), } \Delta V_c = \frac{V_{in} D (1-D)}{8 f_s^2 LC}$$

from IC555 Timer;

$$f_s = \frac{1.44}{[R_A + (R_B \times 2)] C}$$

$$T_s = 0.6933 (R_A + 2R_B) C \approx 10 \text{ KHz}$$

$$P.W = 0.693 (R_A + R_B) C \approx 7.5 \text{ KHz}$$

$$\text{Duty Cycle, } D = \frac{P.W}{T_s} \times 100$$

$$= \frac{R_A + R_B}{R_A + 2R_B}$$

Based on R_A & R_B values, $D = 0.75$

($\because R_A = 750 \Omega$, $R_B = 350 \Omega$)

Assuming (P-P) load current $= \Delta I_L = 0.0075 \text{ A}$


$$\Delta I_L = \frac{V_{in} D(1-D)}{f_s L} = \frac{12 \times 0.75(1-0.75)}{10 \times 10^3 \times 30 \times 10^{-3}}$$

$$L = 30 \times 10^{-3} \text{ H} = 30 \text{ mH}$$


Assuming (P-P) load voltage, $\Delta V_L = 0.937 \text{ mV}$

$$\Delta V_L = \frac{V_{in} (1-D) D}{8 f_s^2 L C} = \frac{12 \times (0.75)(0.25)}{8 \times (10 \times 10^3)^2 \times 30 \times 10^{-3} \times 100 \times 10^{-6}}$$
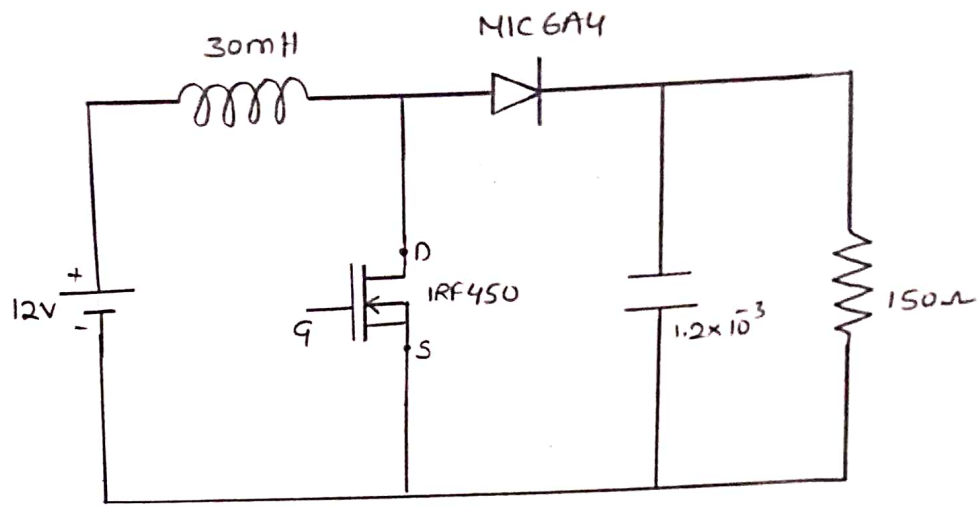
$$C = 100 \times 10^{-6} = 100 \mu\text{F}$$



-fig(b)

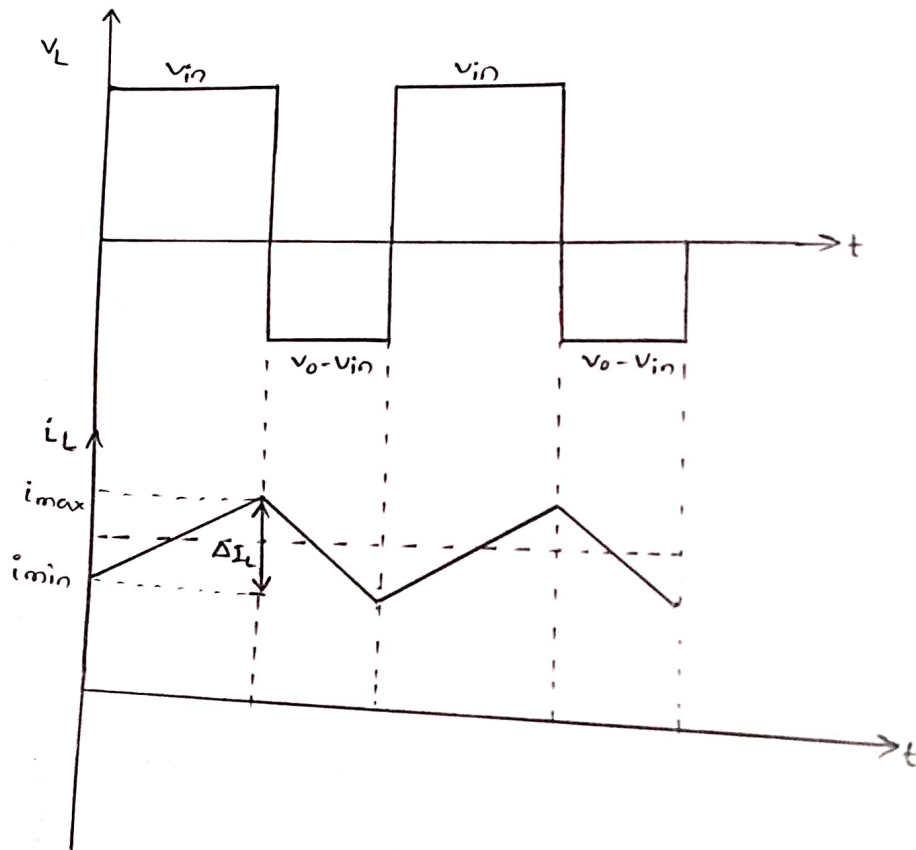

5. BOOST CONVERTER


Aim: To study the boost Converter output voltage which has duty ratio of 0.75

Apparatus:

Sl.No	Component	Range	Quality
1.	MOSFET	IRF540	1
2.	Inductor	30mH	1
3.	Capacitor	100 μ F	1
4.	Diode	41C6A4	1
5.	Rheostat	300 Ω /1.7A	1
6.	Power supply	0-30V	3
7.	555 timer		1
8.	opto Coupler	TCP 2504	1
9.	Capacitor	0.1 μ F	1
		0.01 μ F	1
		0.1 μ F	1
10.	Resistor	750 Ω	1
		350 Ω	1
11.	CRO	digital	1

Theory:

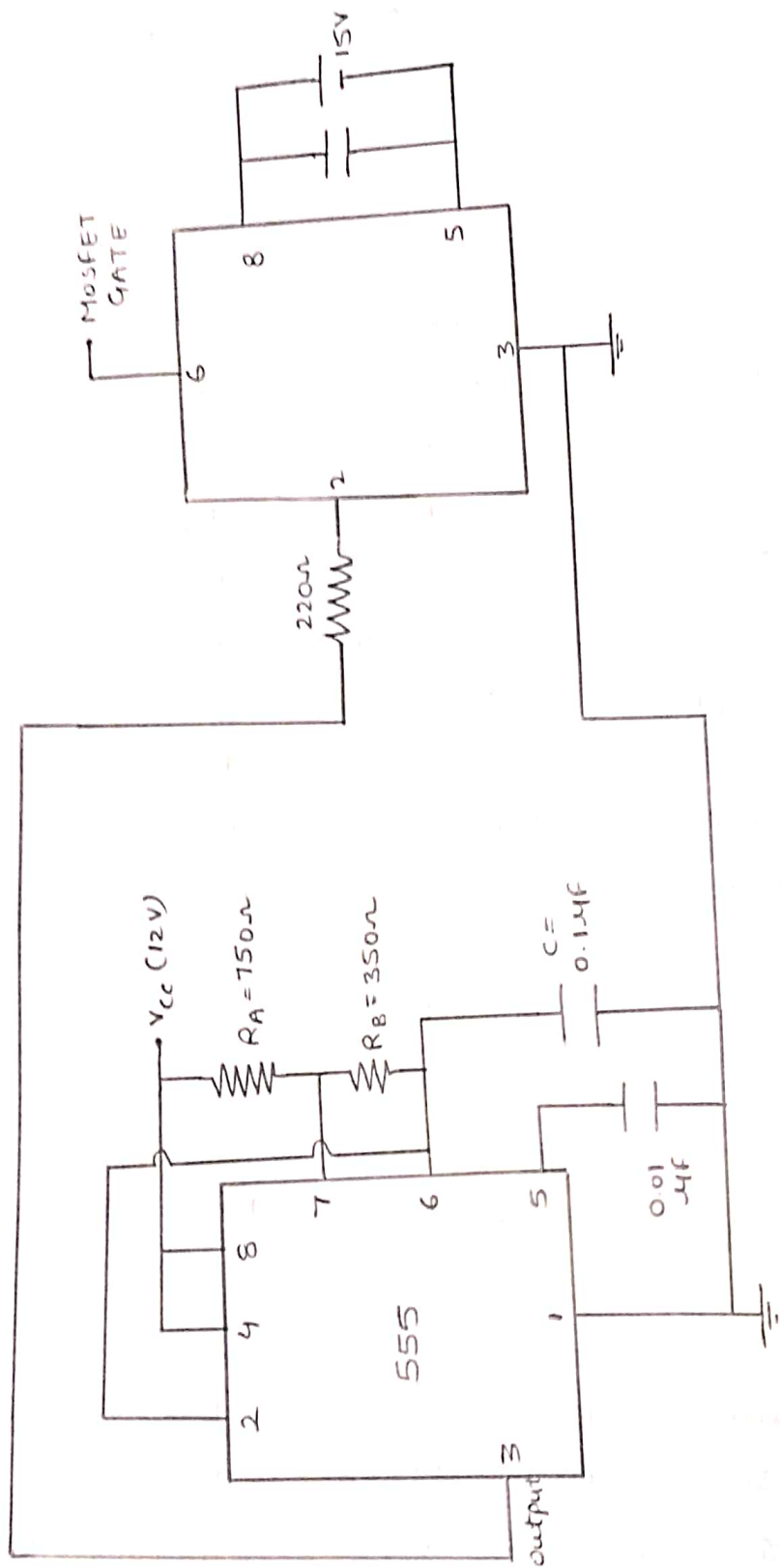A Boost Converter is a DC to DC power Converter that steps up voltage with stepping down current from its supply to its load. The key principle that drives the Boost Converter is the tendency of an Inductor to resist changes in output by creating and destroying a magnetic field. Some of Applications are Communication Applications, Battery power supplies and power Amplifier Applications.



fig(a)

procedure:

- 1) Connect the circuit as shown in the figure
- 2) Given 12V to 555 timer the square wave generated not upto good magnitude to drive MOSFET hence, we give it to the Amplifier.
- 3) The output of optocoupler is given to fig(b)
- 4) The output wave-forms are observed in the CRO

Design & Calculations:

$$V_i T_{ON} = (V_o - V_i) T_{OFF}$$

$$T_{ON} = DT_s \quad \& \quad T_{OFF} = (1-D)T_s$$

$$V_o = \frac{V_i}{1-D}$$

$$\text{Inductor ripple Current (Peak-Peak)}, \Delta I_L = \frac{V_i \cdot D}{f_s L}$$

$$\text{Capacitor ripple voltage (Peak-Peak)}, \Delta V_c = \frac{I_o \cdot D}{f_s C}$$

From 555 (IC) Timer,

$$f_s = f_c = \frac{1.44}{(R_A + 2R_B)C}$$

$$T_s = T_c = \frac{1}{f_c} = 0.6933 (R_A + 2R_B)C = 10 \text{ KHz}$$

$$\text{Pulse width, P.W} = 0.693 (R_A + R_B)C = 7.5 \text{ KHz}$$

$$SW = T_c - \text{P.W}$$

$$\text{Duty cycle, } D = \frac{\text{P.W}}{T_c} \times 100$$

$$= \frac{R_A R_B}{R_A + 2R_B}$$

Based on the R_A & $R_B \rightarrow D \approx 0.75$

($\because R_A = 750 \Omega$, $R_B = 350 \Omega$)

Assuming (P-P) load current, $\Delta I_L = 0.03 \text{ A}$

$$\Delta I_L = \frac{V_{in} D}{f_s L} = \frac{12 \times 0.75}{10 \times 10^3 \times L}$$

$$L = 30 \text{ mH}$$

Assuming (P-P) load voltage, $\Delta V_L =$

$$\Delta V_L = \frac{I_o D}{f_s C} =$$

$$C =$$