

### Module 3

14/3/22

$$\text{Power Factor} = \frac{\text{Active Power}}{\text{Apparent Power}} = \frac{VI \cos \phi}{VI}$$

Assumption:  $V$  &  $I$  are purely sinusoidal.

In power electronics, due to presence of filters - even in R Ckt,  $\text{pf} \neq 1$ .  
We redefine power factor as.

$$P(t) = V(t) \cdot i(t)$$

$$V(t) = V_m \sin \omega t \quad i(t) = \sum_n I_n \sin(n\omega t + \theta_n)$$

$$p(t) = V_m \sin \omega t \times \sum_n I_n \sin(n\omega t + \theta_n)$$

$$= V_m \left[ \sum I_n \sin \omega t \sin n\omega t \cos \theta_n + \sum_n I_n \sin \omega t \cos n\omega t \sin \theta_n \right]$$

\* Consider  $n=1$  & take average value

$$P(t) = V_m \left[ \frac{1}{2\pi} \int_0^{2\pi} I_1 \sin^2 \omega t \cos \theta_1 d\omega t + \frac{1}{2\pi} \int_0^{2\pi} I_1 \sin \omega t \cos \omega t \sin \theta_1 d\omega t \right]$$

$$= V_m \left[ \frac{I_1}{2\pi} \left[ \frac{\cos 2\omega t - 1}{2} \right]_0^{2\pi} \cos \theta_1 + \frac{I_1}{2\pi} \left[ \frac{\sin 2\omega t}{2} \right]_0^{2\pi} \sin \theta_1 \right]$$

$$= \frac{V_m I_1}{2\pi}$$

$$= \frac{V_m I_1}{2} \left[ \cos \theta_1 \right] = \frac{V_m}{\sqrt{2}} \frac{I_1}{\sqrt{2}} \cos \theta_1$$

$$PF = \frac{V_m(\text{rms}) I_1(\text{rms}) \cos \theta_1}{V_m(\text{rms}) I_1(\text{rms})} = \frac{I_1(\text{rms}) \cos \theta_1}{I_1(\text{rms})}$$

Distortion factor  
displacement factor


$$\therefore PF = \text{Distortion factor} \times \text{Displacement factor}$$

We require power factor correction in power electronic circuits to improve the power factor of the load.

$$P(t) = V_m I_1 \cos \theta_1 \sin^2 \omega t$$

$$P(t) = V_m I_1 \cos \theta_1 \sin^2 \omega t$$
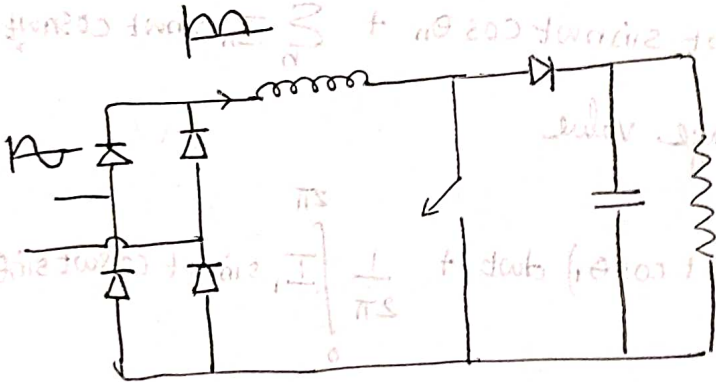
$$P(t) = V_m I_1 \cos \theta_1 \sin^2 \omega t$$



Boost power factor correction of ckt.

- functions:
- 1) Shaping of current - reduce distortion.
  - 2)  $V_{dc}$  controll

$$P(t) \Rightarrow V_m I_1 \cos \theta_1 \sin^2 \omega t$$

$$\Rightarrow V_m I_1 \cos \theta_1 \left[ \frac{1 - \cos 2\omega t}{2} \right]$$

$$= \frac{V_m I_1 \cos \theta_1}{2} - \frac{V_m I_1 \cos \theta_1 \cos 2\omega t}{2}$$

Avg power      Ripple in power

For single phase 100Hz  
so large value capacitance required.

Capacitor has to handle  $V_{dc} \times I_{ripple} = \frac{V_m I_1 \cos \theta_1}{2} \cos 2\omega t$

$$I_{ripple} = \frac{V_m I_1 \cos \theta_1}{2 V_{dc}} \cos 2\omega t$$

$$\text{ripple in voltage} = \Delta V_{dc} = \frac{1}{C\omega} \int_0^{2\pi} I_{ripple} d(\omega t)$$


$$= \frac{1}{C\omega} \left[ \frac{V_m I_1 \cos \theta_1}{2 V_{dc}} \right] \left[ \frac{\sin 2\omega t}{2} \right]$$

Ripple in voltage, maximum

$$\Delta V_{dmax} = \frac{1}{4C\omega} \times \frac{V_m I_1 \cos \theta_1}{V_{dc}}$$


$$C \geq \frac{V_m I_1 \cos \theta_1}{4\omega \Delta V_{dc(max)} \cdot V_{dc}}$$
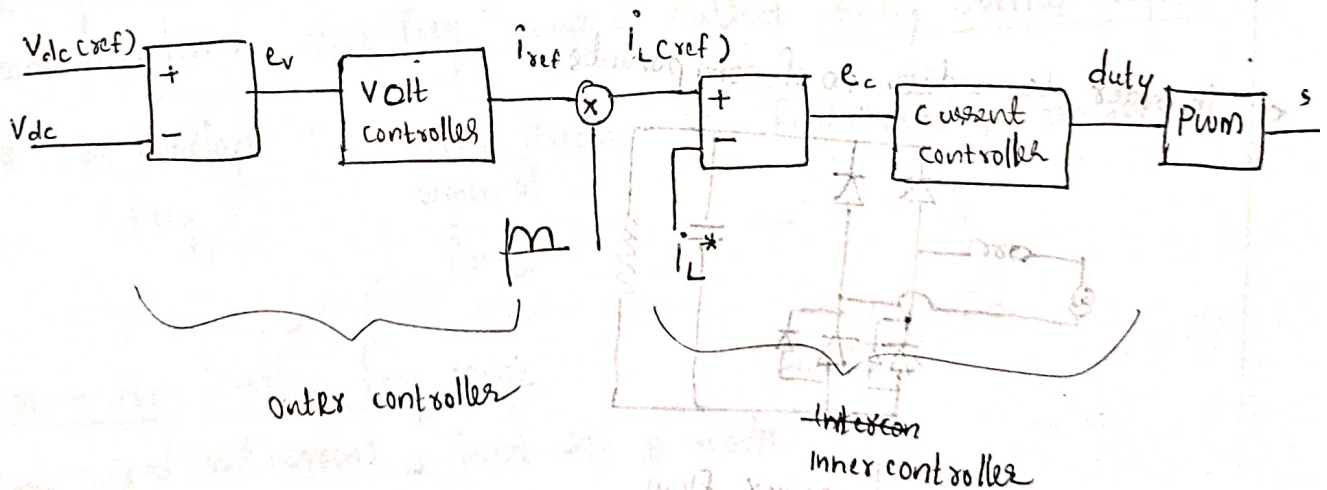
## 15/3/22 Controller Design for Boost PF correction CKT



\* We need inner controller faster than outer controller  
for that we need <sup>larger</sup> Bandwidth.

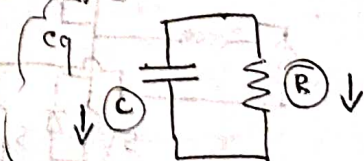\* we keep  $BW = \frac{1}{10}$  " switching freq





Low time const =  $\frac{1}{RC}$   
for faster response

$$BW = \frac{1}{\text{time const}}$$



\* Inductor in AC side is preferred than, Inductor in DC side

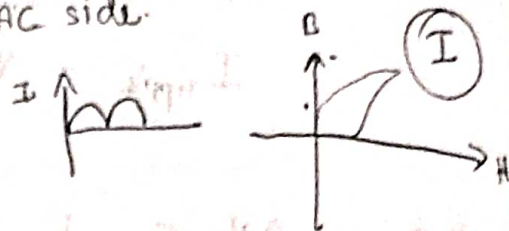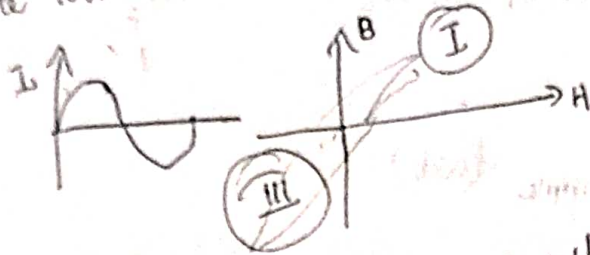
- since low size ~~AC~~ side is required for AC side.




Does not go to saturation so easily

Closes to saturation easily.

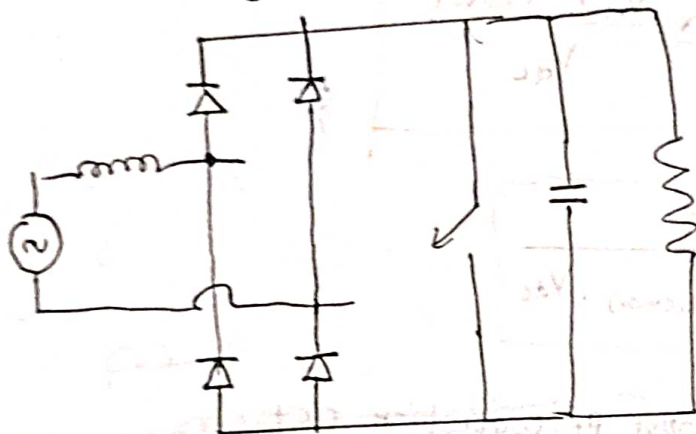
\* So we are shifting inductor to AC side.



\* In order to reduce no of components

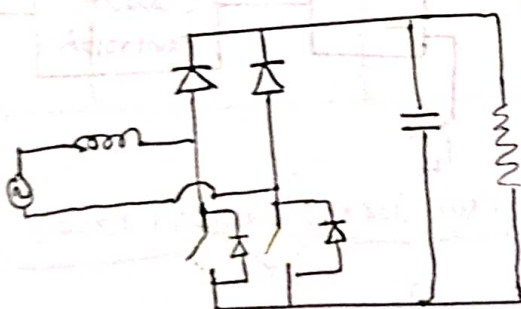

\* For bi-directional power flow

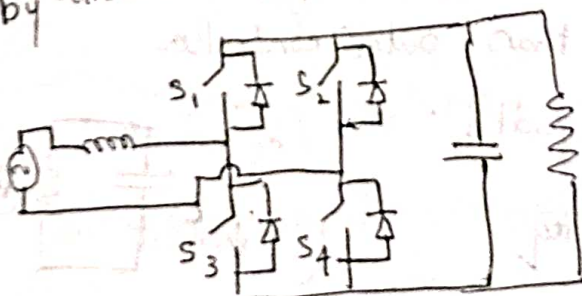

Active front end PFC circuit

ac  $\rightarrow$  dc

$S_3 \rightarrow +ve$

dc  $\rightarrow$  ac

$S_1 \rightarrow +ve$

$S_4 \rightarrow -ve$

$S_2 \rightarrow -ve$