

NAME - KARUNA KUMARI

ROLL NO - M200203EE

BRANCH - POWER ELECTRONICS

SUBJECT - SMRC ASSIGNMENT - 3

Ques 1. Data for Buck Converter

$$V_{ip} = 110V$$

$$r_L = 0.3\Omega, r_s = 0.2\Omega, r_d = 0.2\Omega$$

$$V_{op} = 48V$$

$$r_c = 0.5\Omega, V_r = 0.5V$$

$$I_o = 4.8A$$

$$L = 540\mu H, C = 100\mu F$$

$$f_s = 50kHz$$

$$R = 10\Omega$$

a) Set up state space Averaged Model and to evaluate do.

$$\begin{bmatrix} \Delta \bar{i}_L \\ \Delta \bar{v}_o \end{bmatrix} = \begin{bmatrix} -[r_c + d_0 r_s + (1-d_0)r_d + r_L] & -\frac{1}{L} \\ \frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} \Delta \bar{i}_L \\ \Delta \bar{v}_c \end{bmatrix} + \begin{bmatrix} \frac{d_0}{L} & -\frac{(1-d_0)}{L} & \frac{r_c}{L} \\ 0 & 0 & -\frac{1}{LC} \end{bmatrix} \begin{bmatrix} \Delta \bar{v}_{in} \\ 0 \\ \Delta \bar{t}_o \end{bmatrix} + \begin{bmatrix} \frac{(r_d - r_s)\bar{i}_L}{L} & \frac{\bar{v}_{in} + V_r}{L} \end{bmatrix} \Delta d(t)$$

$$[\Delta \bar{v}_c] = [r_c \quad 1] \begin{bmatrix} \Delta \bar{i}_L \\ \Delta \bar{v}_o \end{bmatrix} + [0 \quad 0 \quad -r_c] \begin{bmatrix} \Delta \bar{v}_{in} \\ 0 \\ \Delta \bar{t}_o \end{bmatrix}$$

$$\begin{bmatrix} \Delta \bar{i}_L \\ \Delta \bar{v}_c \end{bmatrix} = \begin{bmatrix} -[0.5 + d_0 0.2 + (1-d_0) 0.2 + 0.3] & -\frac{1}{540\mu H} \\ \frac{1}{100\mu F} & 0 \end{bmatrix} \begin{bmatrix} \Delta \bar{i}_L \\ \Delta \bar{v}_c \end{bmatrix} + \begin{bmatrix} \frac{d_0}{540\mu H} & -\frac{(1-d_0)}{540\mu H} & \frac{0.5}{540\mu H} \\ 0 & 0 & -\frac{1}{100\mu F} \end{bmatrix} \begin{bmatrix} \Delta \bar{v}_{in} \\ 0 \\ \Delta \bar{t}_o \end{bmatrix} + \begin{bmatrix} \frac{110 + 0.5}{540\mu H} \\ 0 \end{bmatrix} \Delta d(t)$$

$$[\Delta \bar{v}_o] = [0.5 \quad 1] \begin{bmatrix} \Delta \bar{i}_L \\ \Delta \bar{v}_o \end{bmatrix} + [0 \quad 0 \quad -0.5] \begin{bmatrix} \Delta \bar{v}_{in} \\ 0 \\ \Delta \bar{t}_o \end{bmatrix}$$

Inte gel,

$$V_o = d_o V_{in} + (1-d_o) V_r + [r_L + d_o r_s + r_d (1-d_o)] i_o$$

$$4.8 = d_o \times 110 + (1-d_o) 0.5 + [0.3 + 0.2 d_o + 0.2 (1-d_o)] 4.8$$

$$\boxed{d_o = 0.412}$$

→ steady state duty ratio.

b) To evaluate —

$$\frac{\Delta \bar{V}_o(s)}{\Delta d(s)}, \quad \frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{in}(s)}, \quad \frac{\Delta \bar{i}_o(s)}{\Delta d(s)} \quad \text{and} \quad \frac{\Delta \bar{i}_o(s)}{\Delta \bar{V}_{in}(s)}$$

$$\underline{\text{Soln:}} \quad \frac{\Delta \bar{V}_o(s)}{\Delta d(s)} = \frac{\left(\frac{V_{in} + V_r}{Lc} \right) + (1+r_c s_c)}{s^2 + \frac{r_{eff}}{L} s + \frac{1}{Lc}}$$

$$r_{eff} = r_c + r_s + d_o r_s + (1-d_o) r_d$$

$$r_{eff} = 0.5 + 0.3 + 0.412 \times 0.2 + (1-0.412) 0.2 \\ = 1 \Omega$$

$$\frac{\Delta \bar{V}_o(s)}{\Delta d(s)} = \frac{\left(\frac{110 + 0.5}{540 \times 100 \mu s} \right) (1 + 0.5 \times 100 \mu s)}{s^2 + \frac{1}{540 \mu s} s + \frac{1}{540 \mu s \times 100 \mu s}}$$

$$\boxed{\frac{\Delta \bar{V}_o(s)}{\Delta d(s)} = \frac{2046.3 \times 10^6 (1 + 50 \mu s)}{s^2 + 1851.85 s + 18.51 \times 10^6}}$$

$$\frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{in}(s)} = \frac{\left(\frac{d_o}{Lc} \right) (1 + r_c s_c)}{s^2 + \frac{r_{eff}}{L} s + \frac{1}{Lc}}$$

$$\frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{in}(s)} = \left(\frac{0.412}{540.0 \times 10021} \right) [(1 + 0.5 \times 100 \text{ es})] \\ s^2 + 1851.85 s + 18.51 \times 10^6$$

$$\boxed{\frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{in}(s)} = \frac{7.629 \times 10^6 [1 + 50 \text{ es}]}{s^2 + 1851.85 s + 18.51 \times 10^6}}$$

$$\frac{\Delta \bar{i}_L(s)}{\Delta d(s)} = \frac{\left\{ \left(\frac{r_d - r_s}{L} \right) \bar{i}_o + \left(\frac{V_{in} + V_r}{L} \right) \right\} s}{s^2 + \frac{r_{eff}}{L} s + \frac{1}{LC}}$$

$$\boxed{\frac{\Delta \bar{i}_L(s)}{\Delta d(s)} = \frac{0.204 \times 10^6 s}{s^2 + 1851.85 s + 18.51 \times 10^6}}$$

$$\frac{\Delta \bar{i}_L(s)}{\Delta \bar{V}_{in}(s)} = \frac{0.15 \left(\frac{d_o}{L} \right) s}{s^2 + \frac{r_{eff}}{L} s + \frac{1}{LC}}$$

$$= \frac{0.412}{540.0} s \\ s^2 + 1851.85 s + 18.51 \times 10^6$$

$$\boxed{\frac{\Delta \bar{i}_L(s)}{\Delta \bar{V}_{in}(s)} = \frac{-762.96 s}{s^2 + 1851.85 s + 18.51 \times 10^6}}$$

C) When duty ratio is suddenly increased by 5% of d_o .


$$\frac{\Delta V_o(s)}{\Delta d(s)} = \frac{2.762 \times 10^6 s + 5.801 \times 10^{10}}{27 s^2 + 7700 s + 5.5 \times 10^6}$$


$$\frac{\Delta I_L(s)}{\Delta d(s)} = \frac{5.52 s \times 10^6 s + 5.52 \times 10^9}{27 s^2 + 7700 s + 5.5 \times 10^6}$$

$$\Delta V_o(s) = \frac{(2.262 \times 10^6)s + 5.801 \times 10^{10}}{22s^2 + 7700s + 5.5 \times 10^8} \times \frac{0.05}{s}$$

$$\Delta I_o(s) = \frac{5.525 \times 10^6 s + 5.525 \times 10^9}{22s^2 + 7700s + 5.5 \times 10^8} \times \frac{0.05}{s}$$

Plot of Both is attached with this

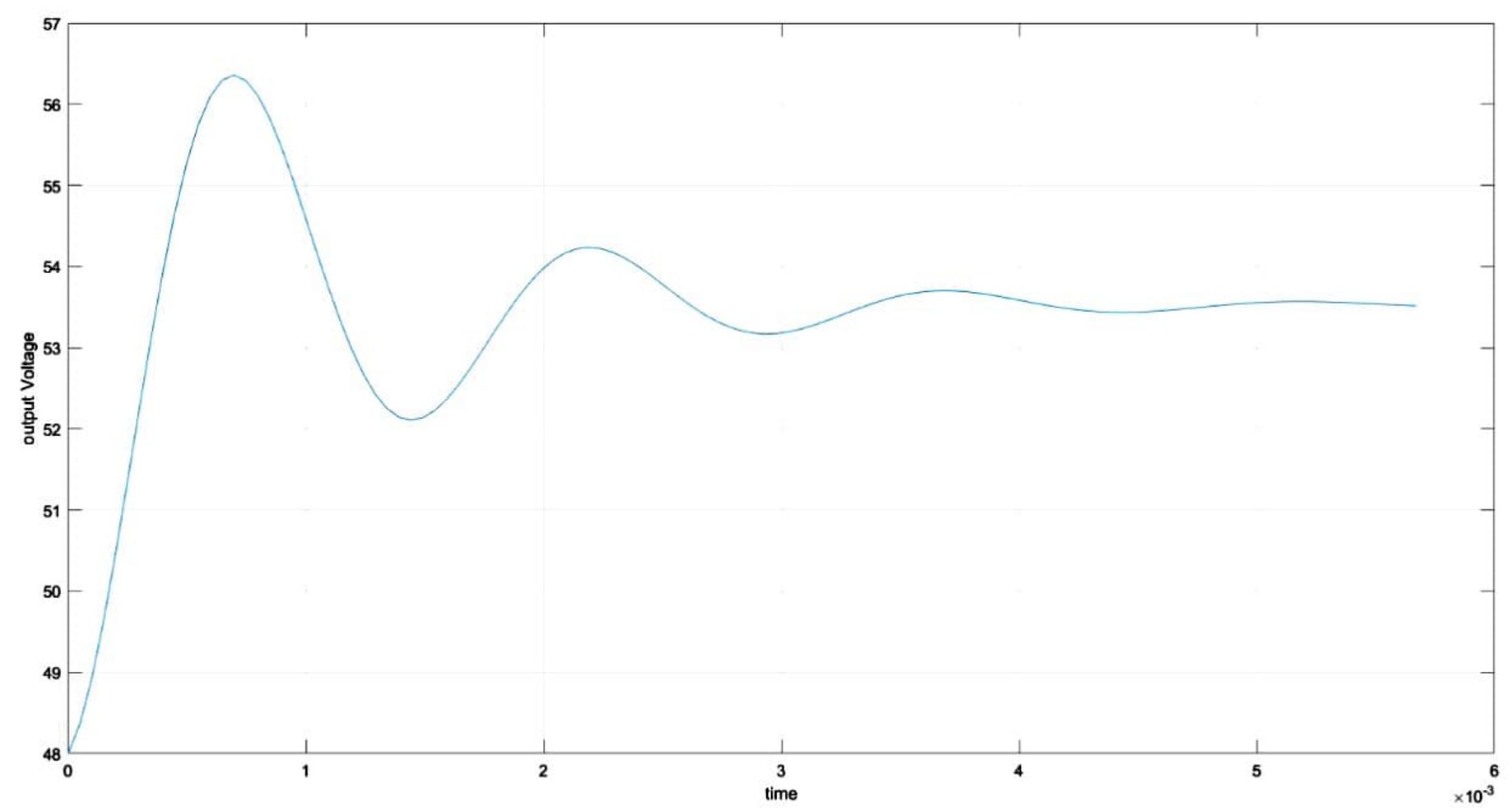

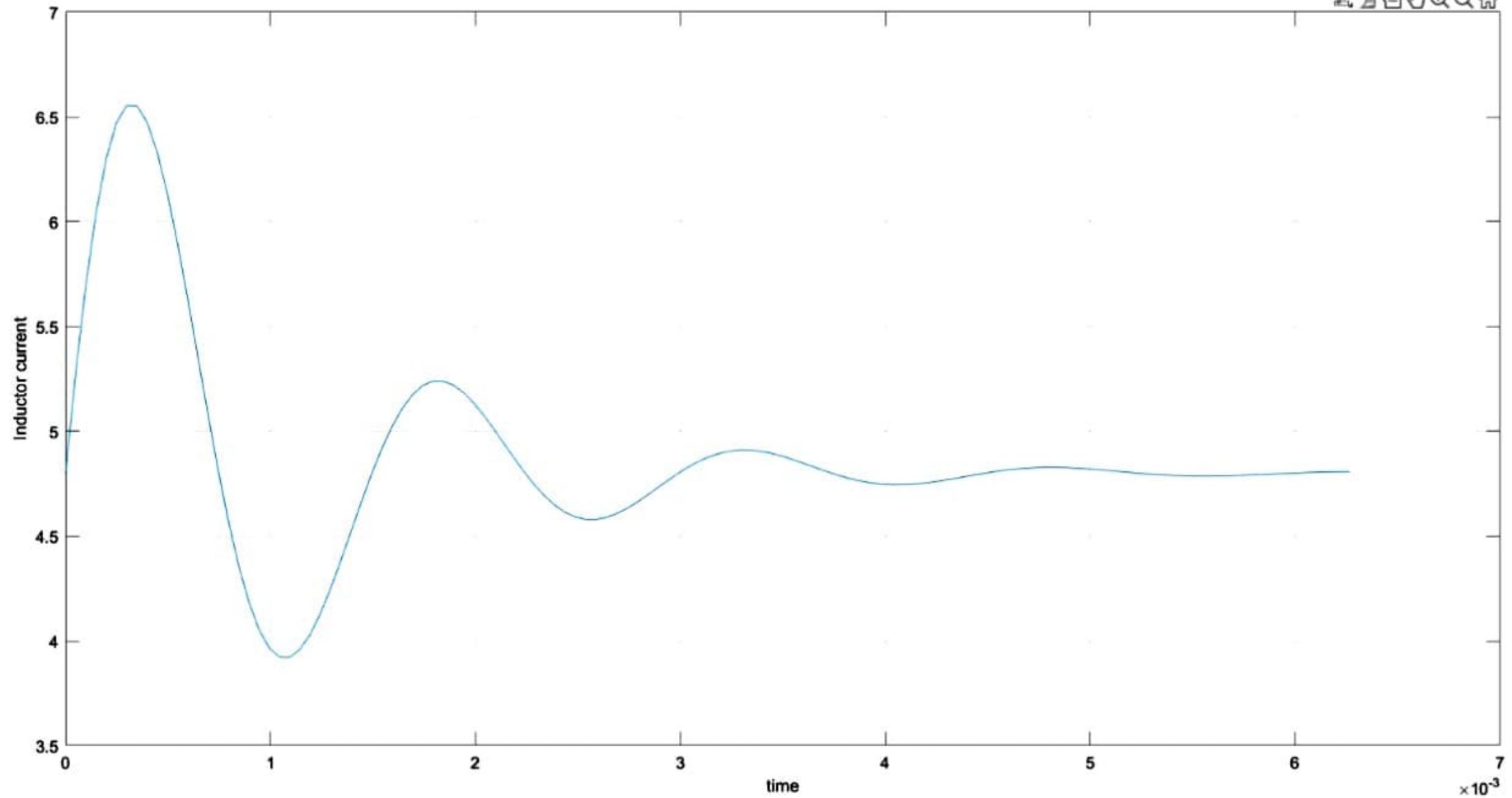


$$\underline{\Delta V_o(s)} = \frac{1.778 \times 10^7 s + 3.43 \times 10^{11}}{41769 s^2 + 1.191 \times 10^8 s + 8.5 \times 10^{11}}$$


$$\underline{\Delta V_o(s)} = \frac{1.778 \times 10^7 s + 3.433 \times 10^{11}}{41769 s^2 + 1.191 \times 10^8 s + 8.5 \times 10^{11}} \times \frac{-10}{s}$$

$$\underline{\frac{\Delta I_o(s)}{\Delta d(s)}} = \frac{3.55 \times 10^7 s + 3.55 \times 10^{10}}{41769 s^2 + 1.191 \times 10^8 s + 3.508 \times 10^{11}}$$

$$\underline{\Delta I_e(s)} = \frac{3.55 \times 10^7 s + 3.55 \times 10^{10}}{41769 s^2 + 1.191 \times 10^8 s + 3.508 \times 10^{11}} \times \frac{-10}{s}$$

Plot of Both Es attached with this

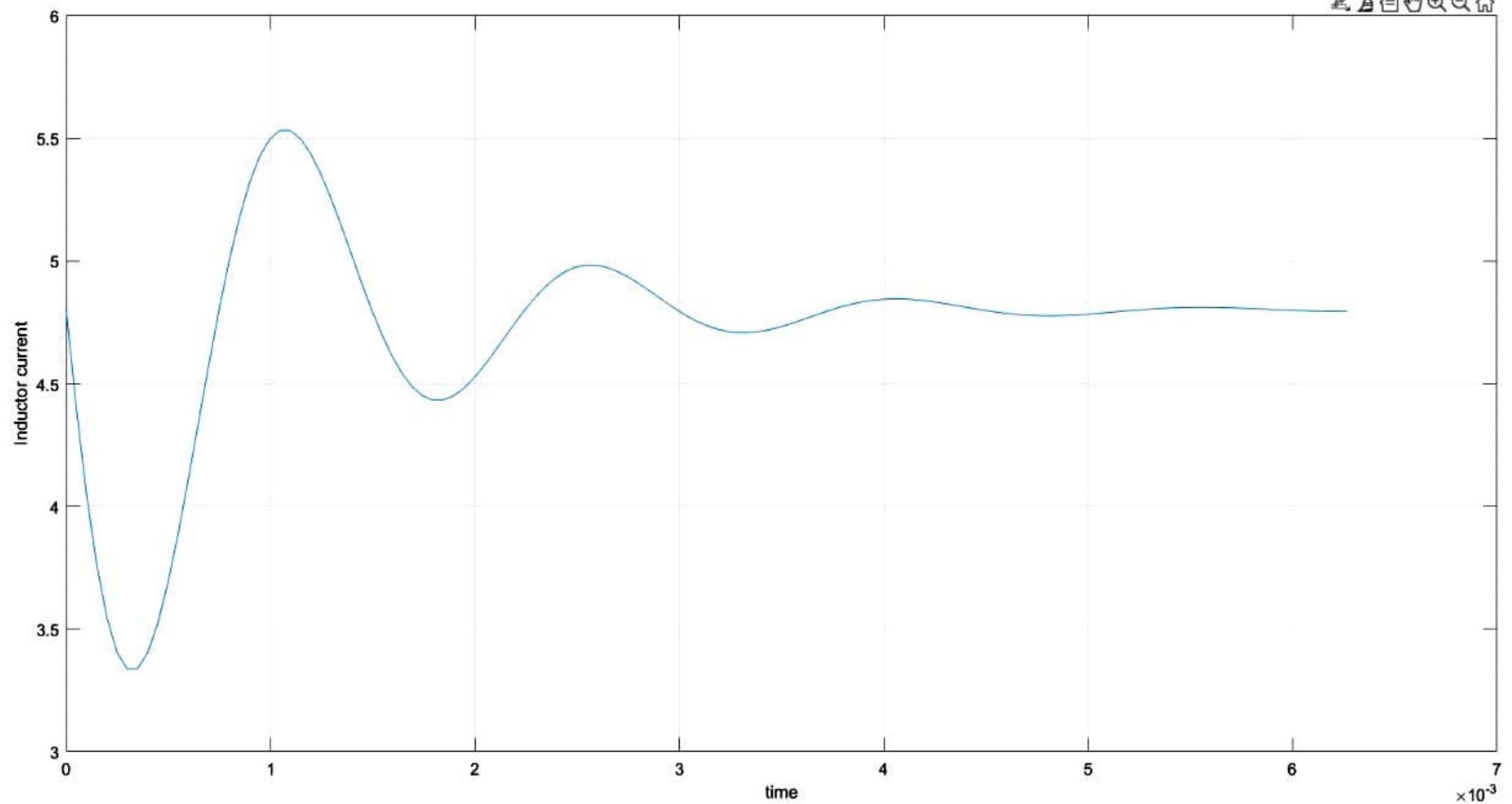

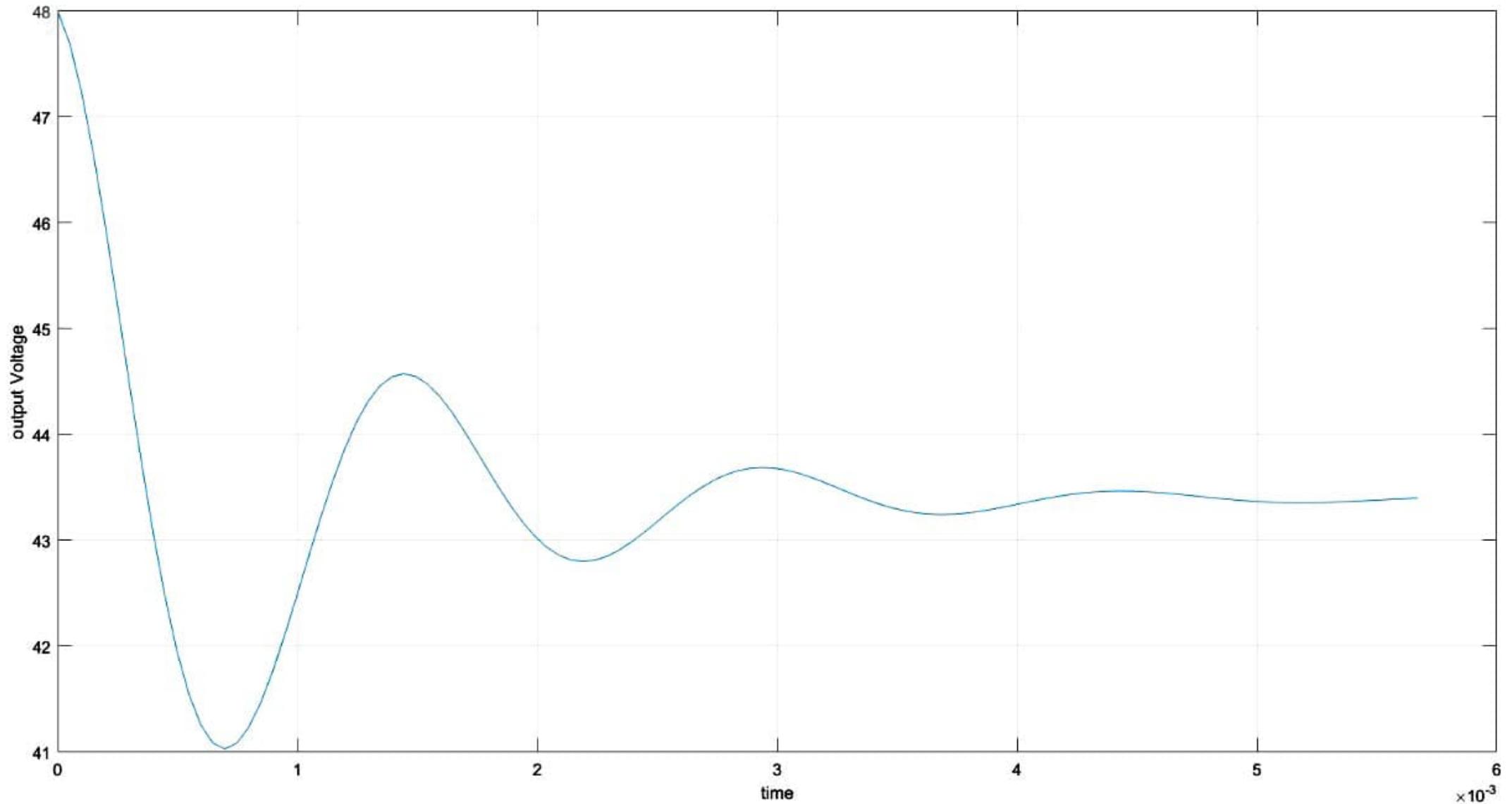

$$e) \frac{\Delta i_L(s)}{\Delta V_{in}(s)} = \frac{85 \cdot 85 s}{s^2 + 1851 \cdot 85 s + 1 \cdot 85 \times 10^2}$$

$$\begin{aligned} \omega &= 2\pi \times 100 \\ &= 200\pi \\ &= 628.31 \text{ rad/sec.} \end{aligned}$$

At 628.31 rad/sec.

$$\text{Gain} = -30 \text{ dB}$$

$$\log \frac{\Delta I_o}{\Delta V_{in}} = -30 \text{ dB}$$

$$\frac{\Delta I_o}{\Delta V_{in}} = 10^{-\frac{30}{20}}$$

$$\frac{\Delta I_o}{\Delta V_{in}} = 0.04$$

$$\Delta I_o = 0.05 \text{ A}$$

$$\Delta V_o(s) = \frac{425 s + 8.5 \times 10^6}{s^2 + 1851 \cdot 85 s + 1.35 \times 10^4}$$

At 628.31 rad/sec

$$\text{Gain} = -6.58$$

$$\frac{\Delta V_o}{\Delta V_{in}} = 10^{-\frac{6.58}{20}}$$

$$\boxed{\Delta V_o = 2.34 \text{ V}}$$

Ques 2. Bode plot $\frac{\Delta \bar{V}_o(s)}{\Delta d(s)}$

$$\frac{\Delta \bar{V}_o(s)}{\Delta d(s)} = \frac{\left(\frac{V_{in} + V_r}{Lc} \right) (1 + r_c s c)}{s^2 + \frac{r_{eff}}{L} s + \frac{1}{Lc}}$$

$$r_{eff} = r_c + r_L + d_o r_s + (1 - d_o) r_d$$

$$V_o = [d_o V_{in} + (1 - d_o) V_r] + [r_L + d_o r_s + r_d (1 - d_o)] i_o$$

$$48 = d_o \times 110 + (1 - d_o) 0.5 + [0.3 + d_o 0.2 + 0.2 (1 - d_o)] 4 \cdot 8$$

$$d_o = 0.412$$

$$\therefore r_{eff} = 0.5 + 0.3 + 0.412 \times 0.2 + (1 - 0.412) 0.2 \\ = 1.2$$

$$\frac{\Delta \bar{V}_o(s)}{\Delta d(s)} = \frac{\left(\frac{110 + 0.5}{540 \times 100 \text{ ms}} \right) (1 + 0.5 \times 100 \text{ ms})}{s^2 + \frac{1}{540 \text{ ms}} s + \frac{1}{540 \text{ ms} \times 100 \text{ ms}}}$$

$$\boxed{\frac{\Delta \bar{V}_o(s)}{\Delta d(s)} = \frac{2046.3 \times 10^6 (1 + 50ms)}{s^2 + 1851.85 s + 18.51 \times 10^6}}$$

When we plot this transfer fn on MATLAB then at $f_{co} = 5 \text{ kHz}$ ie, $\omega = 2\pi \times 5 \text{ kHz} = 3.14 \times 10^4 \text{ rad/sec}$ we get phase delay of $G(j\omega) = +119^\circ$.


Phase delay angle of $K'(j\omega_{co}) = 90^\circ - \text{Phase delay } G(j\omega_{co}) - \text{PM}$

$$0 = 90^\circ - 119^\circ - \text{PM}$$

$$\text{PM} = -119^\circ$$

Hence PM is negative so, it is not possible to design at $f_{co} = 5 \text{ kHz}$.

Bode Diagram

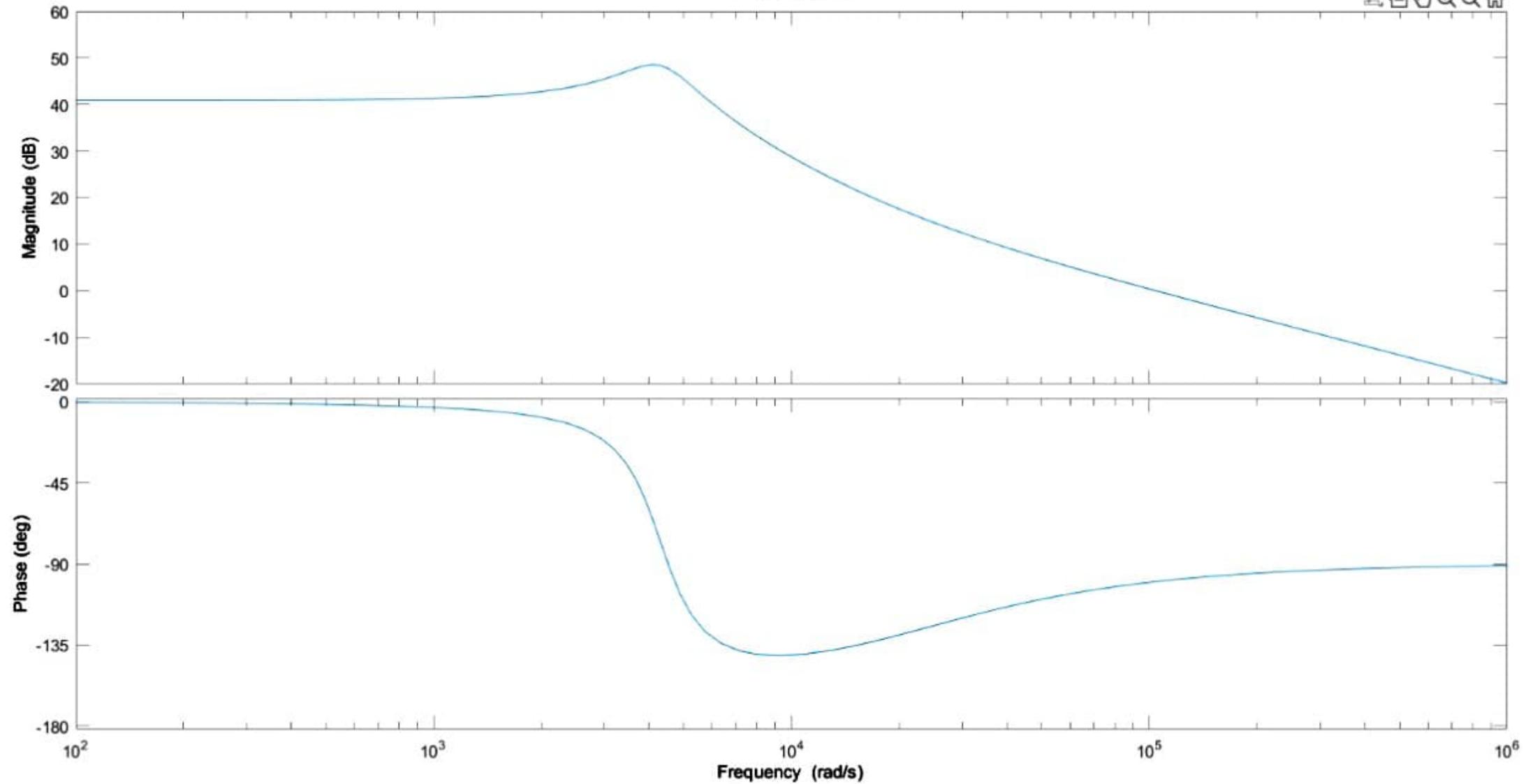

\therefore Now, fixing $P.M = 45^\circ$

$$\therefore \theta = 90^\circ - \text{Phase delay of } G(j\omega_0) - 45^\circ$$

Phase delay of $G(j\omega_0) = 45^\circ$

from the Bode plot we get the frequency corresponding to 45° phase which is 3.7 rad/sec.

$$\omega_c = 3700 \text{ rad/sec.}$$

$$A.M = 48 \text{ dB}$$

$$20 \log |M| = 48$$

$$|M| = 251.18$$

$$\therefore K = \frac{\omega_c}{|G(j\omega_c)|} = \frac{3700}{251.18} = 14.73$$

Hence our system becomes slow and sluggish.

So, Type 1 Compensator is not good for this transfer fun or for Buck converter.

b) $f_{co} = ?$

$P.M = 60^\circ$ — Type 1 Compensator

$$\therefore \theta = 90^\circ - \text{Phase delay of } G(j\omega_0) - P.M$$

$$\theta = 90^\circ - \text{Phase delay of } G(j\omega_0) - 60^\circ$$

Phase delay of $G(j\omega_0) = 30^\circ$

So, from the Bode plot we get ω_c corresponding to phase delay of $G(j\omega_0) = 30^\circ$ is

$$\omega_c = 3.31 \text{ rad/sec.}$$

$$\omega_c = 2\pi f_{co}$$

$$f_{co} = \frac{3.31 \times 10^3}{2\pi}$$

$$f_{co} = 527 \text{ Hz}$$

c) $f_{co} = ?$

$PM = 60^\circ \rightarrow$ by Type 2 Compensator

Phase delay Angle of $\alpha(j\omega_c) = 90^\circ -$ Phase delay angle of
 $a(j\omega_c) - PM$

\therefore Phase delay of $a(j\omega_c) + PM \leq 170^\circ$

$$\begin{aligned}\text{Phase delay of } a(j\omega_c) &= 170^\circ - 60^\circ \\ &= 110^\circ\end{aligned}$$

Now, from the Bode Plot we can get the ω_c corresponding to 110° . i.e,

$$\omega_c = 4.5 \text{ k rad/sec.}$$

$$f_{co} = \frac{4500}{2\pi}$$

$$f_{co} = 716.5 \text{ Hz}$$

d) $f_{co} = ?$

$PM_1 = 60^\circ \rightarrow$ by Type III Compensator

Phase delay of $a(j\omega_c) + PM_1 \leq 250^\circ$

$$\begin{aligned}\text{Phase delay of } a(j\omega_c) &= 250^\circ - 60^\circ \\ &= 190^\circ\end{aligned}$$

Now, from the Bode Plot we can get the ω_c corresponding to the 190° . i.e,

Here According to our design specification $f_s = 50 \text{ kHz}$

$$f_{co} = f_s/10 = \frac{50 \text{ kHz}}{10} = 5 \text{ kHz}$$

$$\therefore f_{co} = 5 \text{ kHz}$$

so, at this frequency, from the bode plot
 Phase delay of $a(j\omega_c) = 110^\circ$. and $G.M = 12.4 \text{ dB}$

e) Designing the Compensator T.O.F in 'b', 'c', 'd'.

Designing Compensator for 'b' part i.e., Type I.

$$f_{co} = 527 \text{ Hz}$$

$$\omega_{co} = 3.31 \text{ krad/sec.}$$

$$|G \cdot M| = 46.1 \text{ dB}$$

$$20 \log |M| = 46.1$$

$$|M| = 801.83$$

$$K = \frac{\omega_{co}}{|G(j\omega_{co})|} = \frac{33100}{801.83} = 163.99$$

$$\boxed{\text{Compensator} = \frac{K}{s} = \frac{164}{s}}$$

for 'c' part

$$\omega_{co} = 4.5 \text{ krad/sec.}, \text{ Phase delay of } G(j\omega_{co}) = 110^\circ$$

$$|G \cdot M| = 48 \text{ dB} \quad PM = 60^\circ$$

$$K(s) = \frac{K(1 + T_2 s)}{s(1 + T_p s)} = \frac{K}{s} \times K'(s)$$

$$\omega_z = \frac{\omega_{co}}{f_k}, \omega_p = f_k \omega_{co}$$

$$f_k = \tan \left\{ \frac{\text{Phase Delay angle of } G(j\omega_{co}) + PM}{2} \right\}$$

$$f_k = \tan \left\{ \frac{110 + 60^\circ}{2} \right\}$$

$$\boxed{f_k = 11.43}$$

$$|K'(j\omega_{co})| = \frac{\sqrt{1+R^2}}{\sqrt{1+\gamma_{f_k}^2}} = f_k = 11.43$$

$$K \times 11.43 = \frac{\omega_{co}}{|G(j\omega_{co})|} = \frac{4500}{251.2}$$

$$\boxed{K = 1.567}$$

$$\begin{cases} |M| = 48 \text{ dB} \\ 20 \log |M| = 48 \\ |M| = 251.2 \end{cases}$$

$$\text{Now, } T_2 = \frac{1}{\omega_{c_2}} = \frac{f_c}{\omega_{c_0}} = \frac{11.43}{4500} = 2.54 \times 10^{-3} \text{ sec.} = T_p$$

$$\omega_p = \frac{1}{T_p}$$

$$\therefore T_p = \frac{1}{\omega_p} = \frac{1}{f_c \omega_{c_0}} = \frac{1}{11.43 \times 4500} = 19.4 \times 10^{-6} \text{ sec.}$$

$$\therefore K(s) = \frac{K}{s} \frac{(1 + T_2 s)}{(1 + T_p s)}$$

$$K(s) = \frac{1.567}{s} \frac{(1 + 2.54 \times 10^{-3} s)}{(1 + 19.4 \times 10^{-6} s)} \rightarrow \begin{array}{l} \text{Type II} \\ \text{compensator} \end{array}$$

for 'd' part (Type III compensator)

$$f_{c_0} = 5 \text{ kHz}$$

$$\omega_{c_0} = 3.14 \times 10^4 \text{ rad/sec.}$$

$$\text{Phase of } G(j\omega_0) \text{ delay} = 119^\circ$$

$$G.M = 12.4 \text{ dB}$$

$$20 \log |M| = 12.4$$

$$|M| = 4.168$$

$$P.M = 60^\circ$$

$$K(s) = \frac{K}{s} \frac{(1 + T_2 s)^2}{(1 + T_p s)^2}$$

$$K \left| K'(j\omega_{c_0}) \right| = \frac{\omega_{c_0}}{|G(j\omega_{c_0})|}$$

$$K'(j\omega_{c_0}) = \frac{(1 + j\frac{1}{K})^2}{(1 + j\frac{1}{K})^2}$$

$$\phi \text{ (Phase Delay Angle)} = 180^\circ - 4 \tan^{-1} \frac{1}{K}$$

$$K = \tan \left\{ \frac{90^\circ + \text{Phase delay of } G(j\omega_0) + P.M}{4} \right\}$$

$$= \tan \left\{ \frac{90^\circ + 119^\circ + 60^\circ}{4} \right\} = 2.38$$

$$K \times |K'(j\omega_{co})| = \frac{\omega_{co}}{|G(j\omega_{co})|}$$

$$|K'(j\omega_{co})| = fc^2 = (2.38)^2 = 5.68$$

$$\therefore K = \frac{\omega_{co}}{5.68 \times |G(j\omega_{co})|}$$

$$K = \frac{31400}{5.68 \times 4.168} = 1326.3$$

$$K = 1326.3$$

$$T_2 = \frac{fc}{\omega_{co}} = \frac{2.38}{31400}$$

$$T_2 = 75.7 \times 10^{-6} \text{ sec.}$$


$$T_P = \frac{1}{fc\omega_{co}} = \frac{1}{2.38 \times 31400}$$

$$T_P = 13.3 \times 10^{-6} \text{ sec.}$$

$$\therefore K(s) = \frac{K}{s} \frac{(1 + T_2 s)^2}{(1 + T_P s)^2}$$

$$K(s) = \frac{1326.3}{s} \frac{(1 + 75.7 \times 10^{-6} s)^2}{(1 + 13.3 \times 10^{-6} s)^2} \rightarrow \text{Type III Compensator.}$$

f) Type I and Type II Compensator Design.

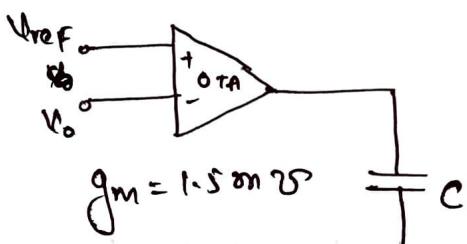

Type I


for Type I

As we know,

$$\frac{K}{s} = \frac{g_m}{s_C}$$

$$C = \frac{g_m}{K} = \frac{1.5 \text{ m}}{164} = 9.1 \text{ pF}$$

$$C = 9.1 \text{ pF}$$

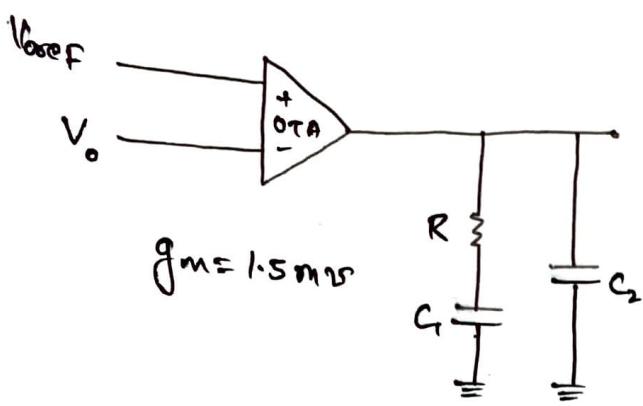

Type II

$$g_m = 1.5 \text{ mS}$$

$$H(s) = \frac{g_m}{C_1 + C_2} \left[\frac{1 + SRC_1}{1 + RS \frac{C_1 C_2}{C_1 + C_2}} \right]$$

$$\frac{g_m}{C_1 + C_2} = K = 1.567$$

$$RC_1 = I_2 = 2.54 \times 10^{-3}$$

$$\frac{RC_2 C_1}{C_1 + C_2} = 19.4 \times 10^{-6} = I_p \quad \rightarrow \textcircled{A}$$

$$\alpha_2 = \frac{19.4 \times 10^{-6}}{2.54 \times 10^{-3}} = 7.63 \times 10^{-3} \text{ F}$$

$\alpha_2 = 7.63 \times 10^{-3} \text{ F}$

$$\frac{g_m}{C_1 + C_2} = 1.567$$

$$\frac{1.5 \text{ mS}}{C_1 + 7.63 \times 10^{-3}} = 1.567$$

$$C_1 + C_2 = \frac{1.5 \text{ mS}}{1.567} = 0.957 \text{ mS}$$

from A

$$\frac{I_2 \times C_2}{C_1 + C_2} = 19.4 \times 10^{-6}$$

$$C_2 = \frac{19.4 \times 10^{-6} \times 0.957 \times 10^{-3}}{2.54 \times 10^{-3}}$$

$$C_2 = 7.31 \mu F$$

$$k = \frac{gm}{C_1 + C_2}$$

$$C_1 + C_2 = 0.952 \text{ m}$$

$$C_1 = 0.952 \text{ m} - 7.31 \mu F$$

$$C_1 = 949 \mu F$$

$$RC_1 = 2.54 \times 10^{-3}$$

$$R = 2.6 \Omega$$

8) Design → opamp Circuit
Type III compensator arrived at part 'e'

$$K = 1326.3$$

$$T_2 = 75.7 \times 10^{-6} \text{ sec.}$$

$$T_P = 13.3 \times 10^{-6} \text{ sec}$$

Choosing $C_2 = 0.1 \mu\text{F}$

$$K = \frac{1}{R_1(C_1 + C_2)}, \quad T_2 = R_2 C_2 = (R_1 + R_3) C_3$$

$$T_P = R_2 \frac{C_1 C_2}{C_1 + C_2} = R_3 C_3$$

$$\frac{V_o(s)}{V_{in}(s)} = -\frac{1}{R_1(C_1 + C_2)s} \frac{(1 + s R_2 C_2)(1 + s(R_1 + R_3) C_3)}{(1 + s R_3 C_3)(1 + s R_2 \frac{C_1 C_2}{C_1 + C_2})}$$

$$T_2 = R_2 C_2$$

$$75.7 \times 10^{-6} = R_2 \times 0.1 \mu\text{F}$$

$$\boxed{R_2 = 0.75 \text{ k}\Omega}$$

$$T_P = R_2 \frac{C_1 C_2}{C_1 + C_2} \Rightarrow \frac{13.3 \times 10^{-6}}{0.75 K} = \frac{C_1 \times 0.1 \mu\text{F}}{C_1 + 0.1 \mu\text{F}}$$

$$0.017 [C_1 + 0.1] = 0.1 C_1$$

$$C_1 + 0.1 = 5.88 C_1$$

$$0.1 = 4.88 C_1$$

$$\boxed{C_1 = 20.4 \text{ nF}}$$

$$\text{Now, } K = \frac{1}{R_1(C_1 + C_2)}$$

$$1326.3 = \frac{1}{R_1[20.4 \text{ nF} + 0.1 \mu\text{F}]}$$

$$\boxed{R_1 = 6.26 \text{ k}\Omega}$$

$$\text{Now, } T_2 = R_2 C_2 = [R_1 + R_3] C_3 \\ = R_1 C_3 + R_3 C_3$$

$$T_2 = R_1 C_3 + T_P \Rightarrow 75.7 \times 10^{-6} = 6.26 K \times C_3 + 13.3 \times 10^{-6}$$

$$C_3 = 9.96 \text{ nF}$$

Now, $I_2 = (R_1 + R_3) C_3$


$$75.7 \times 10^{-6} = [6.26 \text{ k}\Omega + R_3] \times 9.96 \text{ nF}$$

$$R_3 = 1.34 \text{ k}\Omega$$

\therefore Design values are,

$$R_1 = 6.26 \text{ k}\Omega, R_2 = 0.75 \text{ k}\Omega, R_3 = 1.34 \text{ k}\Omega,$$
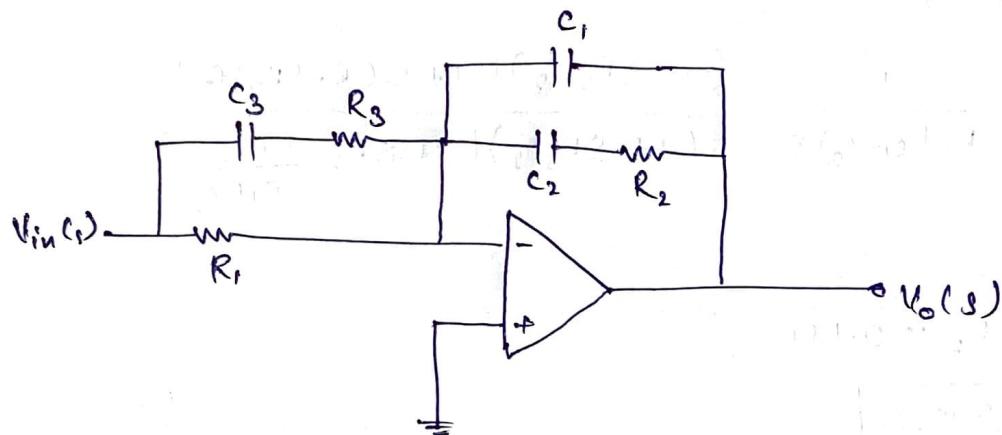
$$C_1 = 20.4 \text{ nF}, C_2 = 0.1 \mu\text{F}, C_3 = 9.96 \text{ nF}$$



Type III Compensator.


Ques 8. Type I Compensator, with P.M = 60°

a) To obtain $\frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{in}(s)}$, $\frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{ref}(s)}$, $\frac{\Delta \bar{I}_L(s)}{\Delta \bar{V}_{in}(s)}$, $\frac{\Delta \bar{I}_L(s)}{\Delta \bar{V}_{ref}(s)}$

for close loop Buck converter

Soln: for 2 'e' part
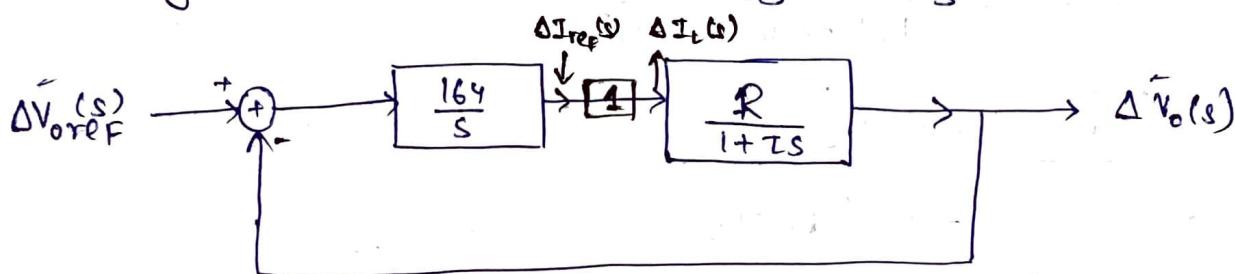
$$\text{Type I Compensator} = \frac{1K}{s} = \frac{164}{s}$$



$$T = RC = 10 \times 100\mu F = 1 \text{ msec.} \quad \therefore \frac{R}{1+Ts} = \frac{10}{1+10^{-3}s}$$

$$\frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{oref}(s)} = \frac{\frac{164}{s} \times \frac{10}{1+10^{-3}s}}{1 + \frac{164}{s} \times \frac{10}{1+10^{-3}s}}$$

$$= \frac{1640}{s[1+10^{-3}s] + 1640} = \frac{1640}{10^3 s^2 + s + 1640}$$

$$\boxed{\frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{oref}(s)} = \frac{1640000}{s^2 + 1000s + 1640000}}$$

$$-1ly \quad \frac{\Delta \bar{i}_L(s)}{\Delta \bar{V}_{oref}(s)} = \frac{\frac{R}{1+Ts}}{1 + \frac{Ki}{s} \times \frac{R}{1+Ts}}$$

$$= \frac{\frac{10}{1+10^{-3}s}}{1 + \frac{164}{s} \times \frac{10}{1+10^{-3}s}} = \frac{10s}{s[1+10^{-3}s] + 1640}$$

$$\boxed{\frac{\Delta \bar{i}_L(s)}{\Delta \bar{V}_{oref}(s)} = \frac{1000s}{s^2 + 1000s + 1640000}}$$

$$\frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{in}(s)} = \frac{\left(\frac{d_o}{LC}\right)(1+s(r_e))}{s^2 + \frac{r_{eff}}{L}s + \frac{1}{LC}}$$

$$1 + \frac{Ki}{s} \times \frac{\left(\frac{d_o}{LC}\right)(1+s(r_e))}{s^2 + \frac{r_{eff}}{L}s + \frac{1}{LC}}$$

$$\frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{in}(s)} = \frac{\left(\frac{0.412}{540\mu F \times 100\mu F}\right)[1 + 0.5 \times 100\mu F s]}{s(s^2 + 1851.8s + 18.51 \times 10^6) + 164 \left(\frac{0.412}{540\mu F \times 100\mu F}\right)(1 + 0.5 \times 100\mu F s)}$$

$$\frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{in}(s)} = \frac{7.63 \times 10^6 s [1 + 50s]}{s^3 + 1851.85 s^2 + 18.51 \times 10^6 s + 1251.25 \times 10^6 s [1 + 50s]}$$

$$\begin{aligned} \frac{\Delta \bar{i}_L(s)}{\Delta \bar{V}_{in}(s)} &= \frac{\left(\frac{d_o}{L}\right) s}{s^2 + \frac{r_{eff}}{L} s + \frac{1}{LC}} \\ &\quad \cdot \left(1 + \frac{k_i}{s} \times \frac{\left(\frac{d_o}{L}\right) s}{s^2 + \frac{r_{eff}}{L} s + \frac{1}{LC}} \right) \\ &= \frac{\left(\frac{0.412}{540.4}\right) s^2}{s^3 + 1851.85 s^2 + 18.51 \times 10^6 s + 164 \left(\frac{0.412}{540.4}\right) s} \\ &= \frac{762.96 s^2}{s^3 + 1851.85 s^2 + 18.51 \times 10^6 s + 125125.9 \times 10^6 s} \end{aligned}$$

$$\frac{\Delta \bar{i}_{LL}(s)}{\Delta \bar{V}_{in}(s)} = \frac{762.96 s}{s^2 + 1851.85 s + 18.51 \times 10^6 + 125125.9 \times 10^6}$$

$$\boxed{\frac{\Delta \bar{i}_{LL}(s)}{\Delta \bar{V}_{in}(s)} = \frac{762.96 s}{s^2 + 1851.85 s + 125144.4 \times 10^6}}$$

b) Time - domain response plot using MATLAB
for $\bar{V}_o(t)$ and $\bar{i}_L(t)$ when r_{eff} changes from 48V to 40V.

$$\frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{ref}(s)} = \frac{1.64 \times 10^6}{s^2 + 1000 s + 1.64 \times 10^6}$$

where $\Delta \bar{V}_{ref}(s) = 48V \rightarrow 40V$

$$\Delta \bar{V}_o(s) = \frac{1.64 \times 10^6 \times 48}{s^3 + 1000 s^2 + 1.64 \times 10^6 s}$$

Ansatz

When V_{ref} changes from 48V to 40V.

$$V_{ref}(t) = V(\infty) - [V(\infty) - V(0)] e^{-t/T}$$

$$= 48 - [48 - 40] e^{-t/1m}$$

$$= 48 - 8 e^{-1000t}$$

$$\begin{aligned} T &= RC \\ &= 10 \times 1000 \\ &= 1m \end{aligned}$$

$$V_{ref}(s) = \frac{48}{s} - \frac{8}{s + 1000}$$

$$\therefore \Delta \bar{V}_o(s) = \frac{1.64 \times 10^6}{s^2 + 1000s + 1.64 \times 10^6} \times \left[\frac{48}{s} - \frac{8}{s + 1000} \right]$$

$$= \frac{1.64 \times 10^6}{s^2 + 1000s + 1.64 \times 10^6} \left[\frac{48s + 48000 - 8s}{s(s+1000)} \right]$$

$$\Delta \bar{V}_o(s) = \frac{1.64 \times 10^6 [40s + 48000]}{s^4 + 2000s^3 + 2.64 \times 10^6 s^2 + 1.64 \times 10^9 s}$$

$$= \frac{65600000s + 7872 \times 10^7}{s^4 + 2000s^3 + 2.64 \times 10^6 s^2 + 1.64 \times 10^9 s}$$


$$\boxed{\Delta V_o(t) = 280\sqrt{139} \sin(100\sqrt{139}t) - \frac{5560 \cos(100\sqrt{139}t)}{139}}$$

$$\cdot e^{-500t} + 48 - 8 e^{-1000t}}$$

Time Domain Response plot of $\bar{V}_o(t)$ is given by the MATLAB is attached with the page.

Step Response

Esc □ × ⊞ ⊞ ⊞ ⊞

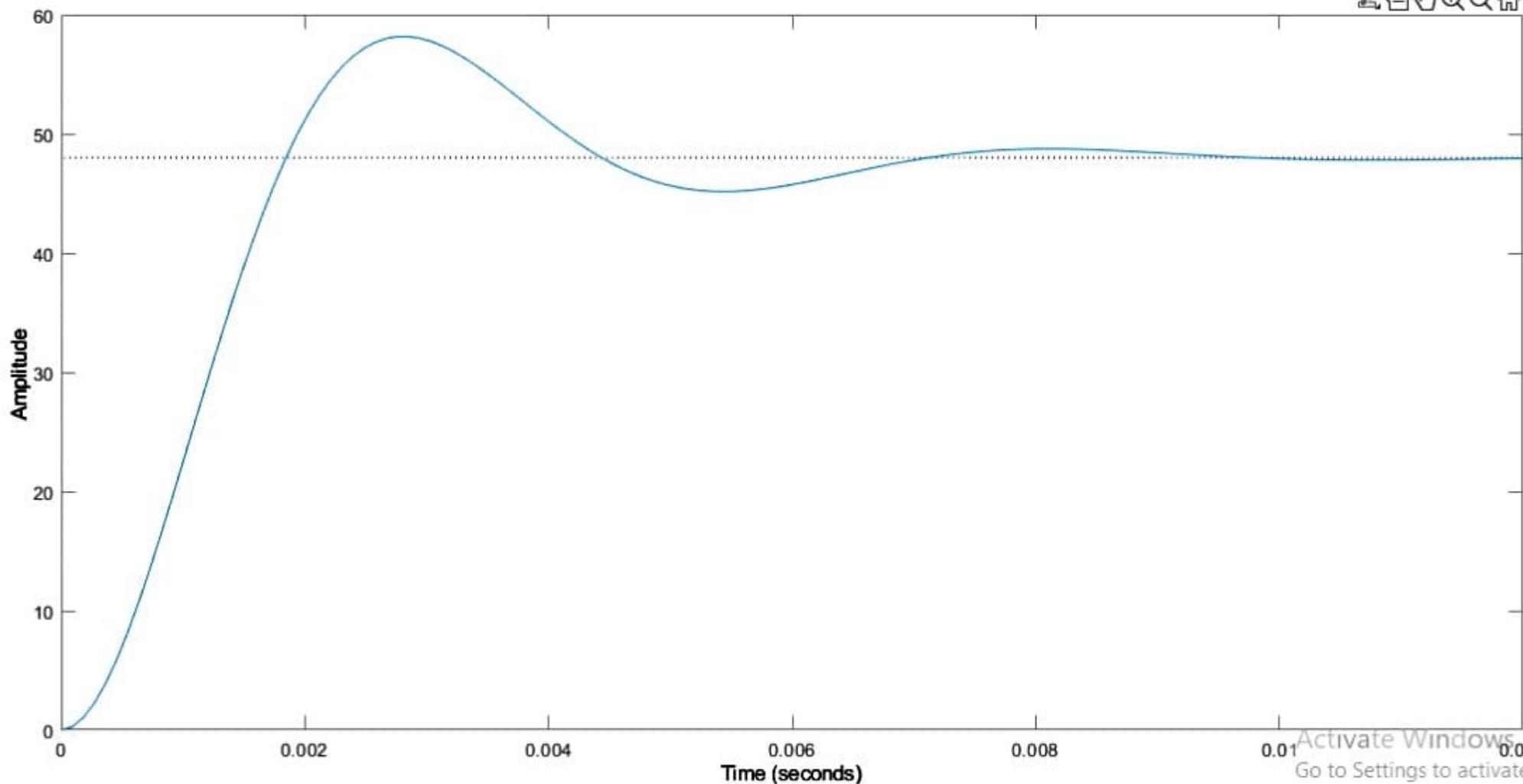

Activate Windows
Go to Settings to activate Windows

$$\rightarrow \text{Hence } \frac{\Delta \bar{i}_L(s)}{\Delta \bar{V}_{\text{ref}}(s)} = \frac{10000s}{s^2 + 1000s + 1640000}$$

$$\begin{aligned} \Delta \bar{i}_L(s) &= \frac{10^4 s}{s^2 + 10^3 s + 164 \times 10^4} \times \left[\frac{40s + 48000}{s(s+1000)} \right] \\ &= \frac{10^4 [40s^2 + 48000s]}{s^4 + 2 \times 10^3 s^3 + 2640000s^2 + 164 \times 10^4 s} \end{aligned}$$


$$\Delta \bar{i}_L(s) = \frac{10^4 [40s + 48000]}{s^3 + 2 \times 10^3 s^2 + 2640000s + 164 \times 10^4}$$

ANSWER

Time response plot using MATLAB is attached with this question.

Conclusion

Step Response

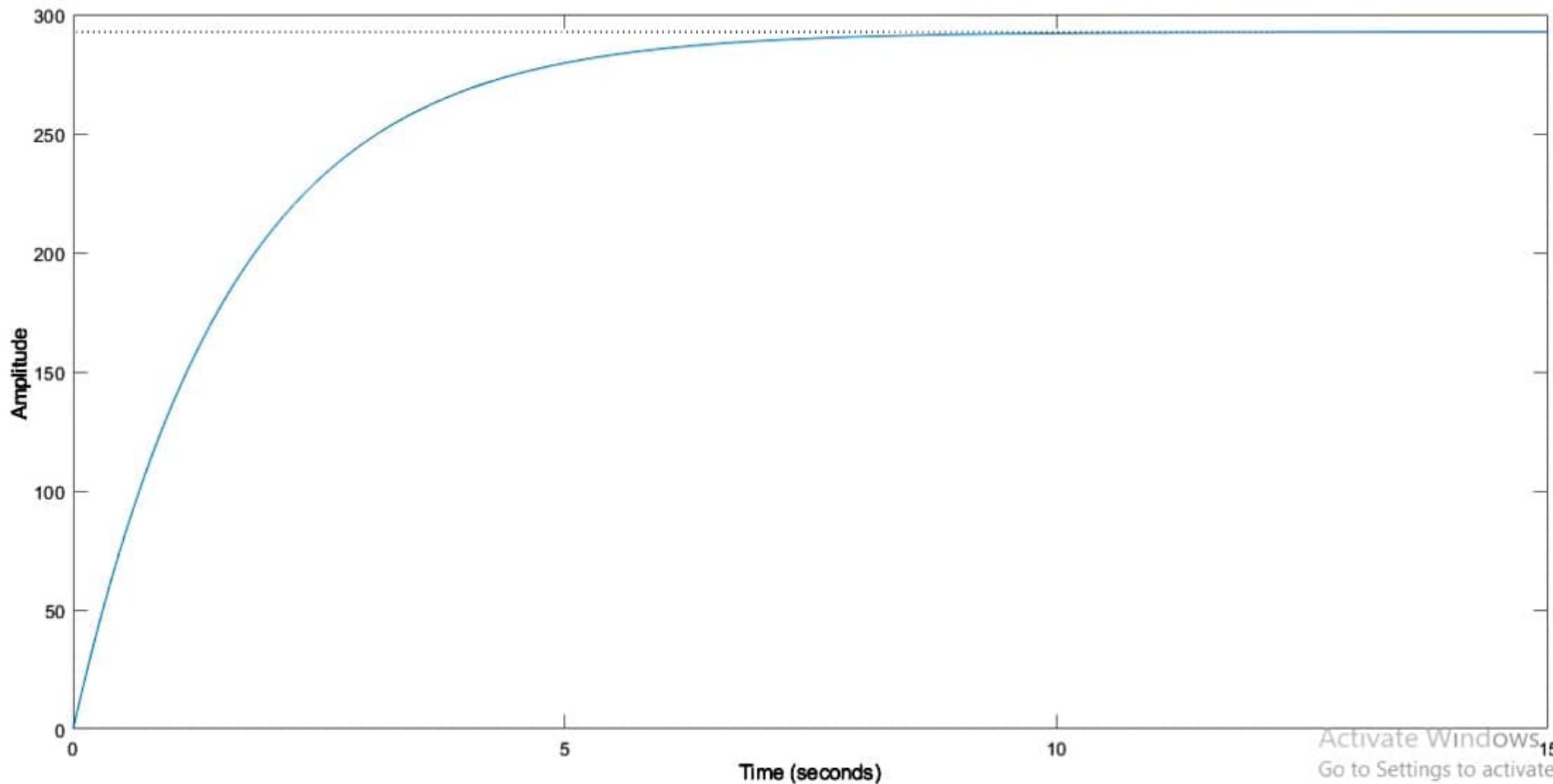

Activate Windows
Go to Settings to activate Windows 15

C) To obtain time domain response plot for $v_o(t)$ and $i_L(t)$ for V_{in} suddenly changes from 110V to 100V.

Soln: $V_{in} = 110 \rightarrow 100$

$$V_{in}(t) = V_{(d)} - [V_{(s)} - V_{(0)}] e^{-\frac{t}{\tau}} \\ = 110 - [110 - 100] e^{-\frac{1000t}{100}} \\ = 110 - 10 e^{-10t}$$


$$V_{in}(s) = \frac{110}{s} - \frac{10}{s + 1000} = \frac{110s + 11 \times 10^4 - 10s}{s(s + 1000)} \\ = \frac{100s + 11 \times 10^4}{s(s + 1000)}$$

$$\frac{\Delta V_o(s)}{V_{in}(s)} = \frac{7.63 \times 10^6 s [1 + 50s]}{s^3 + 18s^2 + 18.51 \times 10^6 s + 12s^2 + 12s^2 + 62.5s^2} \cdot \frac{s(s + 1000)}{s(s + 1000)}$$

$$\Delta V_o(s) = \frac{3815s^2 + 76719.65 \times 10^4 s + 8.93 \times 10^{10}}{s^4 + 65414.35s^3 + 1333.4 \times 10^4 s^2 + 1269 \times 10^9 s}$$

Time Response plot using MATLAB is attached with this ques.

Step Response

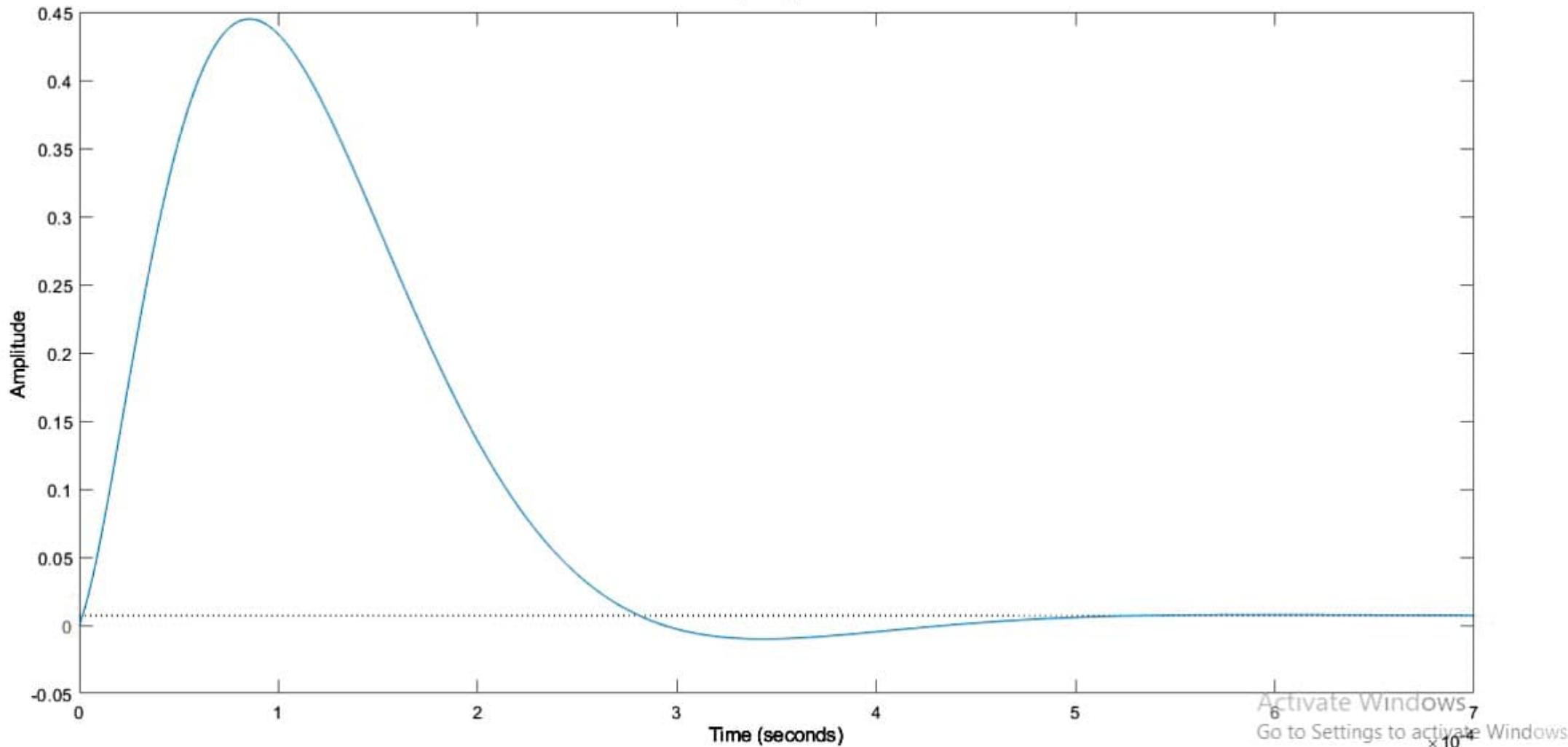

$$-\frac{1}{11y} \frac{\Delta i_L(s)}{\Delta v_{in}(s)} = \frac{762.96 s}{s^2 + 1851.85 s + 125144.4 \times 10^6}$$

$$\begin{aligned} \Delta i_L(s) &= \frac{762.96 s}{s^2 + 1851.85 s + 125144.4 \times 10^6} \times \frac{40s + 48000}{s(s+10^3)} \\ &= \frac{762.96 [40s + 48000]}{s^3 + 1851.85 s^2 + 125144.4 \times 10^6 s + 1000s^2 + \\ &\quad + 1851.85 \times 10^3 s + 125144.4 \times 10^9} \end{aligned}$$

$$\Delta i_L(s) = \frac{762.96 [40s + 48000]}{s^3 + 2851.85 s^2 + 125.14 \times 10^9 s + 125.14 \times 10^{12}}$$


Time response plot using MATLAB

attached with this ques.

Following is the time response plot of the system.

It is observed that the system is stable.

Step Response

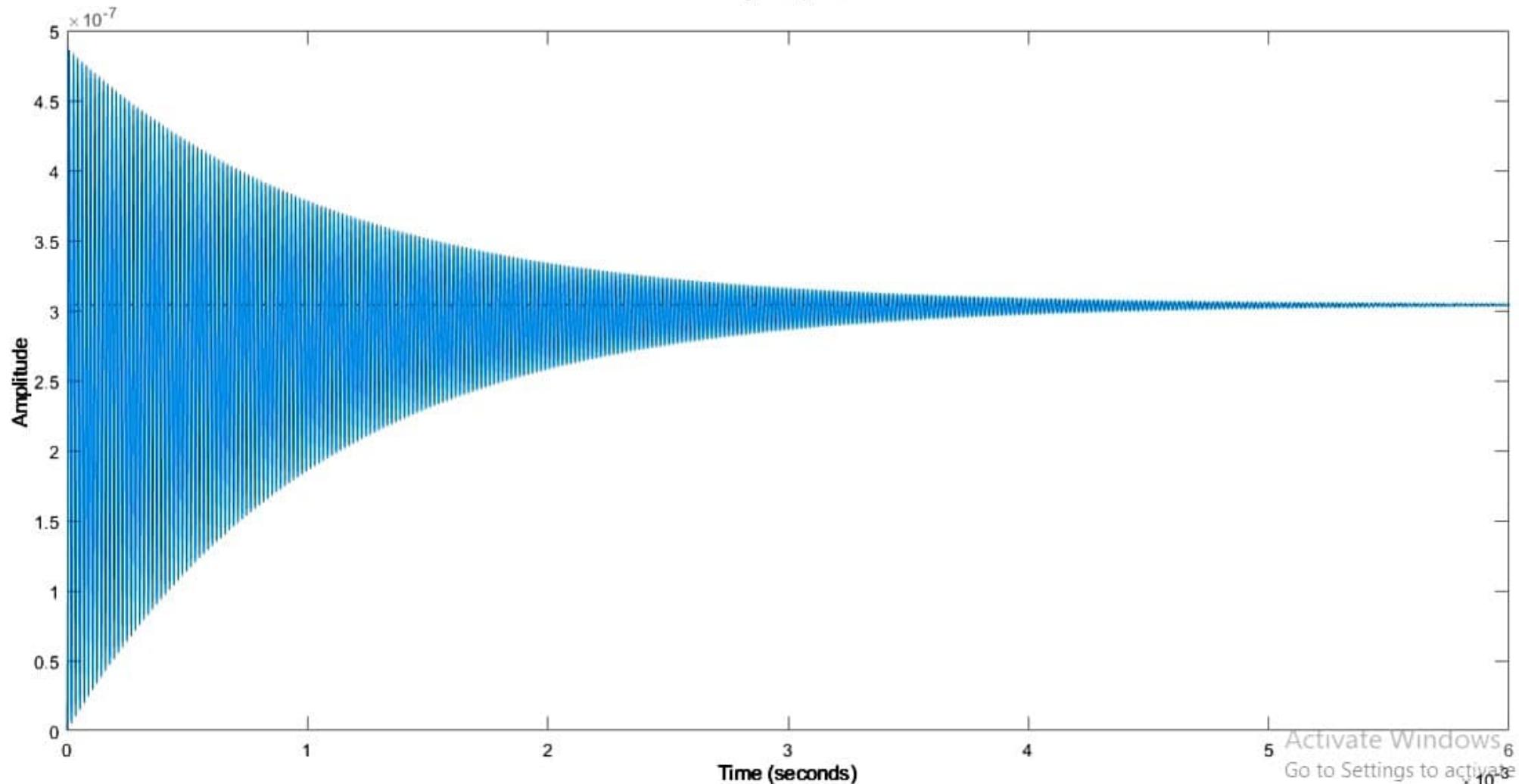

Activate Windows
Go to Settings to activate Windows.
 $\times 10^{-3}$

Ques 4.

a) Buck Converter Controlled using Current Mode Control

$$P_{c, \text{peak}} = 6A$$

$$\text{gain} = 0.5V/A$$

To Design \rightarrow PI Controller for outer Voltage Control loop,

$$t_r = 1 \text{ msec}$$

Soln:- rise time $= t_r = \frac{1}{\alpha}$

$$\alpha = \frac{1}{t_r} = \frac{1}{1 \text{ msec}} = 1000$$

$$\boxed{\alpha = 1000}$$

$$K_p = \frac{\alpha T}{R}$$

$$T = RC$$

$$= 10 \times 100 \mu F$$


$$T = 1 \text{ msec}$$


$$K_p = \frac{1000 \times 1 \text{ msec}}{10}$$

$$\boxed{K_p = 0.1}$$

$$K_i = \frac{\alpha}{R} = \frac{1000}{10} = 100$$

$$\boxed{K_i = 100}$$

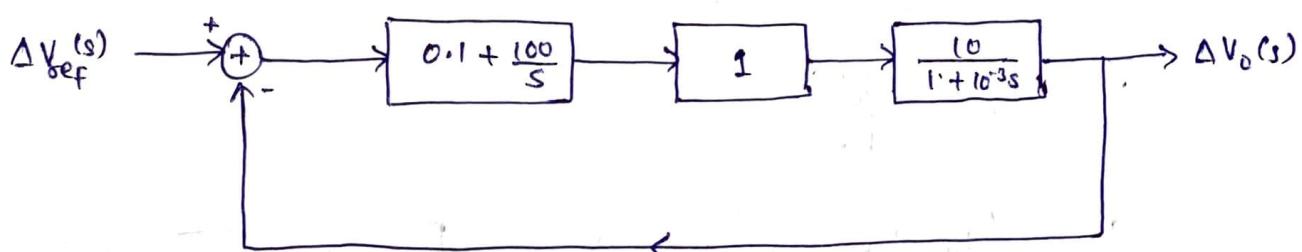

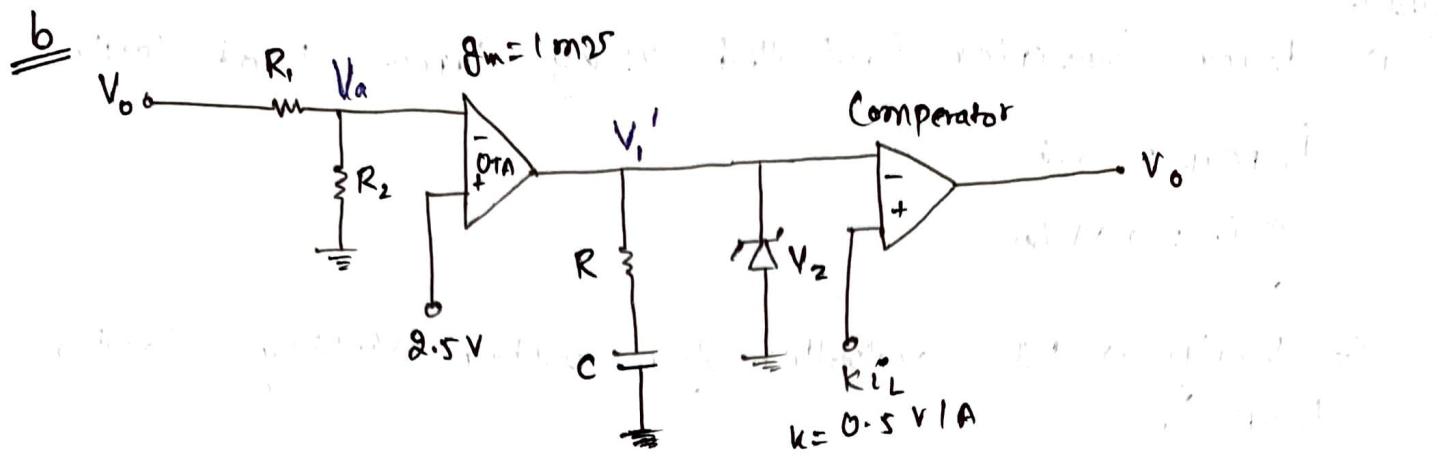

$$H(s) = -\frac{R_2}{R_1 + R_2} \times g_m \times \left[R + \frac{1}{C s} \right]$$

$$f_c = \frac{1}{2\pi RC}$$

$$\begin{aligned} H(s) &= -\frac{R_2 g_m}{R_1 + R_2} \times \frac{R}{s} \times \frac{1 + \frac{1}{SRC}}{1 + SRC} \\ &= -\frac{R_2 g_m}{R_1 + R_2} \times R \times \frac{1 + \frac{1}{RCS}}{1 + SRC} \end{aligned}$$

$$f_2 = \frac{1}{2\pi RC}$$

$$f_p = \frac{C_1}{2\pi R_2 C}$$

$$|A(f_c)| = A_0 \sqrt{\frac{1 + \left(\frac{f_2}{f_c}\right)^2}{1 + \left(\frac{f_c}{f_p}\right)^2}}$$

$$\therefore f_2 = \frac{f_c^2}{f_p}$$

$$\begin{aligned} f_p &= \sqrt{\tan^2(\text{boost} \times \frac{\pi}{180}) + 1} \times f_c \\ &= 27.5 \text{ kHz} \quad | \text{ for Boost } \Theta = 50^\circ \end{aligned}$$


$$f_2 = \frac{f_c^2}{R_p} = 3.64 \text{ kHz}$$

from the OTA plot,

$$\therefore R_p = 1.685 \text{ k}\Omega$$

$$C = 25.95 \text{ nF}$$

c)

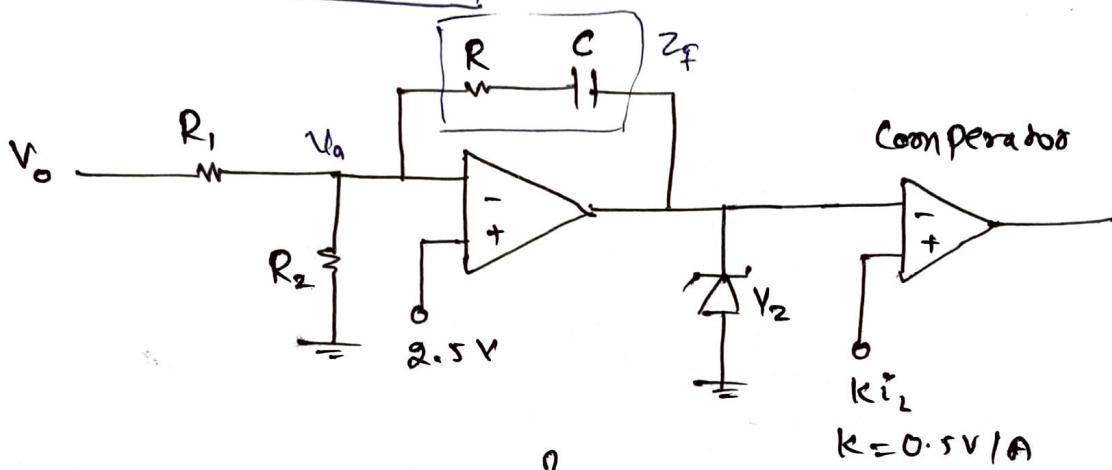

Component values = ?

$$H(s) = \frac{Z_f}{Z_i} = -\frac{R \cdot \frac{1}{Cs}}{\frac{R + \frac{1}{Cs}}{R_1}} \times \frac{R_2}{R_1 + R_2}$$

$$H(s) = \frac{1 + C_s R s}{C_1 R s + R_1 C_1 R_s s^2}$$

$$f_{p1} = \frac{1}{2\pi R}$$

$$f_{z1} = \frac{1}{2\pi R C}$$

$$\therefore C = \frac{1}{2\pi R f_{z1}}$$

$$R = \frac{f_{p0} \times R_1}{f_{z1}}$$

$$S^2 R_1 C_1 R + S R_1 C_1 = 0$$

$$S R_1 C_1 R + R_1 C_1 = 0$$

$$S = -\frac{R_1 C_1}{R_1 C_1 R}$$

$$\omega = \frac{1}{R}$$

$$f_p = \frac{1}{2\pi R}$$

By putting all the values from the
OTA Results we get

$$R = 1.2 \text{ k}\Omega$$

$$C = 2.2 \text{ nF}$$

Boost Converter Data

$$V_{in} = 48V, V_{out} = 110V, I_{out} = 4A, f_s = 50\text{kHz}$$

$$L = 270\mu\text{H}, C = 330\mu\text{F}, r_d = 0.3\Omega, r_s = 0.1\Omega, r_a = 0.1\Omega$$

$$R_L = 27.5\Omega, r_c = 0.1\Omega$$

$$V_r = 0.5V$$

Ques 1.

a) State Space Averaged Model

$$\begin{bmatrix} \Delta \bar{i}_L \\ \Delta \dot{\bar{v}}_c \end{bmatrix} = \begin{bmatrix} -[\frac{r_d + d_o r_s + (1-d_o)(r_d + r_c)}{L}] & -\frac{1-d_o}{L} \\ 0 & \frac{1-d_o}{C} \end{bmatrix} \begin{bmatrix} \Delta \bar{i}_L \\ \Delta \bar{v}_c \end{bmatrix} + \begin{bmatrix} \frac{1}{L} & -\frac{1-d_o}{L} & \frac{(1-d_o)r_c}{L} \\ 0 & 0 & -\frac{1}{C} \end{bmatrix} \begin{bmatrix} \Delta \bar{v}_{in} \\ V_r \\ \Delta \bar{i}_o \end{bmatrix} + \begin{bmatrix} \frac{(r_d - r_s + d_o r_c)}{(1-d_o)L} \bar{i}_o & + \frac{V_o + V_r}{L} \\ -\frac{I_o}{(1-d_o)C} \end{bmatrix} [\Delta d(+)]$$

$$[\Delta \bar{v}_o] = [(1-d_o)r_c] \begin{bmatrix} \Delta \bar{i}_L \\ \Delta \bar{v}_c \end{bmatrix} + [0 \ 0 \ -r_c] \begin{bmatrix} \Delta \bar{v}_{in} \\ V_r \\ \Delta \bar{i}_o \end{bmatrix} + \left[\begin{array}{c} -r_c \bar{i}_o \\ \hline 1-d_o \end{array} \right] [\Delta d]$$

$$\begin{bmatrix} \Delta \dot{\bar{i}}_L \\ \Delta \dot{\bar{v}}_c \end{bmatrix} = \begin{bmatrix} -[\frac{0.3 + 0.1d_o + (1-d_o)(0.2)}{270\mu\text{H}}] & -\frac{1-d_o}{270\mu\text{H}} \\ -\frac{1-d_o}{330\mu\text{F}} & 0 \end{bmatrix} \begin{bmatrix} \Delta \bar{i}_L \\ \Delta \bar{v}_c \end{bmatrix} + \begin{bmatrix} \frac{1}{270\mu\text{H}} & -\frac{1-d_o}{270\mu\text{H}} & \frac{(1-d_o)0.1}{270\mu\text{H}} \\ 0 & 0 & -\frac{1}{330\mu\text{F}} \end{bmatrix} \begin{bmatrix} \Delta \bar{v}_{in} \\ V_r \\ \Delta \bar{i}_o \end{bmatrix} + \begin{bmatrix} \frac{0.1d_o \times 4}{(1-d_o)270\mu\text{H}} & + \frac{48.5}{270\mu\text{H}} \\ -\frac{4}{(1-d_o)330\mu\text{F}} \end{bmatrix} [\Delta d(+)]$$

Steady state duty ratio 'd_o'

$$V_o = \left(\frac{V_{in}}{1-d_o} - V_r \right) - I_o \left\{ \frac{r_d + d_o r_s}{(1-d_o)^2} + \frac{r_d + d r_c}{1-d_o} \right\}$$

$$110 = \left(\frac{48}{1-d_o} - 0.5 \right) - 4 \left\{ \frac{0.3 + 0.1d_o}{(1-d_o)^2} + \frac{0.1 + 0.1d_o}{1-d_o} \right\}$$

$$d_o = 0.6043$$

b) Evaluate,

$$\frac{\Delta \bar{V}_o(s)}{\Delta d(s)}, \quad \frac{\Delta \bar{V}_o(s)}{\Delta \bar{V}_{in}(s)}, \quad \frac{\Delta \bar{i}_L(s)}{\Delta d(s)}, \quad \frac{\Delta \bar{i}_L(s)}{\Delta \bar{V}_{in}(s)}$$

$$\text{Soln:-} \quad \frac{\Delta \bar{V}_o(s)}{\Delta d(s)} = \left[\frac{(1-d_o)V_o}{LC} \right] \left[1 - \frac{sLI_o}{(1-d_o)^2 V_o} \right] \frac{s^2 + \frac{r_{eff}}{L} s + \frac{(1-d_o)^2}{LC}}{s^2 + \frac{r_{eff}}{L} s + \frac{(1-d_o)^2}{LC}}$$

$$\text{Where } r_{eff} = r_L + d_o r_s + (1-d_o)(r_d + r_c) \\ = 0.8 + 0.6043 \times 0.1 + (1-0.6043)[0.2] \\ = 0.4396$$

$$\frac{\Delta \bar{V}_o(s)}{\Delta d(s)} = \left[\frac{(1-0.6043) \times 110}{270 \times 1 \times 330.4} \right] \left[1 - \frac{s \times 270 \times 4}{(1-0.6043)^2 \times 110} \right] \frac{s^2 + \frac{0.4396}{270 \times 1} s + \frac{(1-0.6043)^2}{270 \times 1 \times 330.4}}{s^2 + \frac{0.4396}{270 \times 1} s + \frac{(1-0.6043)^2}{270 \times 1 \times 330.4}}$$

$$\boxed{\frac{\Delta \bar{V}_o(s)}{\Delta d(s)} = 488.51 \times 10^{-6} \left[1 - \frac{62.7 \times 10^{-6} s}{s^2 + 1628.14 s + 1.75 \times 10^6} \right]}$$

$$\frac{\Delta \bar{i}_L(s)}{\Delta d(s)} = \frac{\alpha s + \left(\frac{1-d_o}{BL} \right)}{s^2 + \frac{r_{eff}}{L} s + \frac{(1-d_o)^2}{LC}}$$

$$\alpha = \frac{r_d + r_s + d_o r_c}{(1-d_o)L} + \frac{V_o + V_r}{L}$$

$$\alpha = \frac{0.6043 \times 0.1}{(1-0.6043)270 \times 1} + \frac{110.5}{270 \times 1} = 0.409 \times 10^6$$

$$\frac{\Delta \bar{I}_L(s)}{\Delta d(s)} = 0.409 \times 10^6 s - \left[\frac{1 - 0.6043}{\beta \times 2704} \right]$$

$$s^2 + \frac{0.439 \beta}{2704} s + \frac{(1 - 0.6043)^2}{2704 \times 3304}$$

$$\beta = \frac{-I_0}{(1-d_0)c} = \frac{-4}{(1-0.6043) \times 3304} = -0.306 \times 10^6$$

$$\frac{\Delta \bar{I}_L(s)}{\Delta d(s)} = 0.409 \times 10^6 s - \left[\frac{1 - 0.6043}{-306 \times 10^6 \times 2704} \right]$$

$$s^2 + 1628.14 s + 1.85 \times 10^6$$

$$\boxed{\frac{\Delta \bar{I}_L(s)}{\Delta d(s)} = \frac{0.409 \times 10^6 s + 4.7 \times 10^{-6}}{s^2 + 1628.14 s + 1.85 \times 10^6}}$$



$$\boxed{\frac{\Delta I_L(s)}{\Delta V_{in}(s)} = \frac{1.934 \times 10^{30} s}{5.223 \times 10^{26} s^2 + 8.5 \times 10^{27} s + 3.66 \times 10^{23}}}$$

$$\boxed{\frac{\Delta V_o(s)}{\Delta V_{in}(s)} = \frac{7.652 \times 10^{28} s + 2.319 \times 10^{33}}{5.223 \times 10^{26} s^2 + 8.5 \times 10^{29} s + 9.173 \times 10^{32}}}$$

C



$$\Delta V_o(s) = \frac{-1.674 \times 10^{46} s^2 - 265 \times 10^{50} s + 7.343 \times 10^{54}}{1.65 \times 10^{46} s^2 + 2.69 \times 10^{49} s + 2.908 \times 10^{52}} \times \frac{10^6}{s}$$
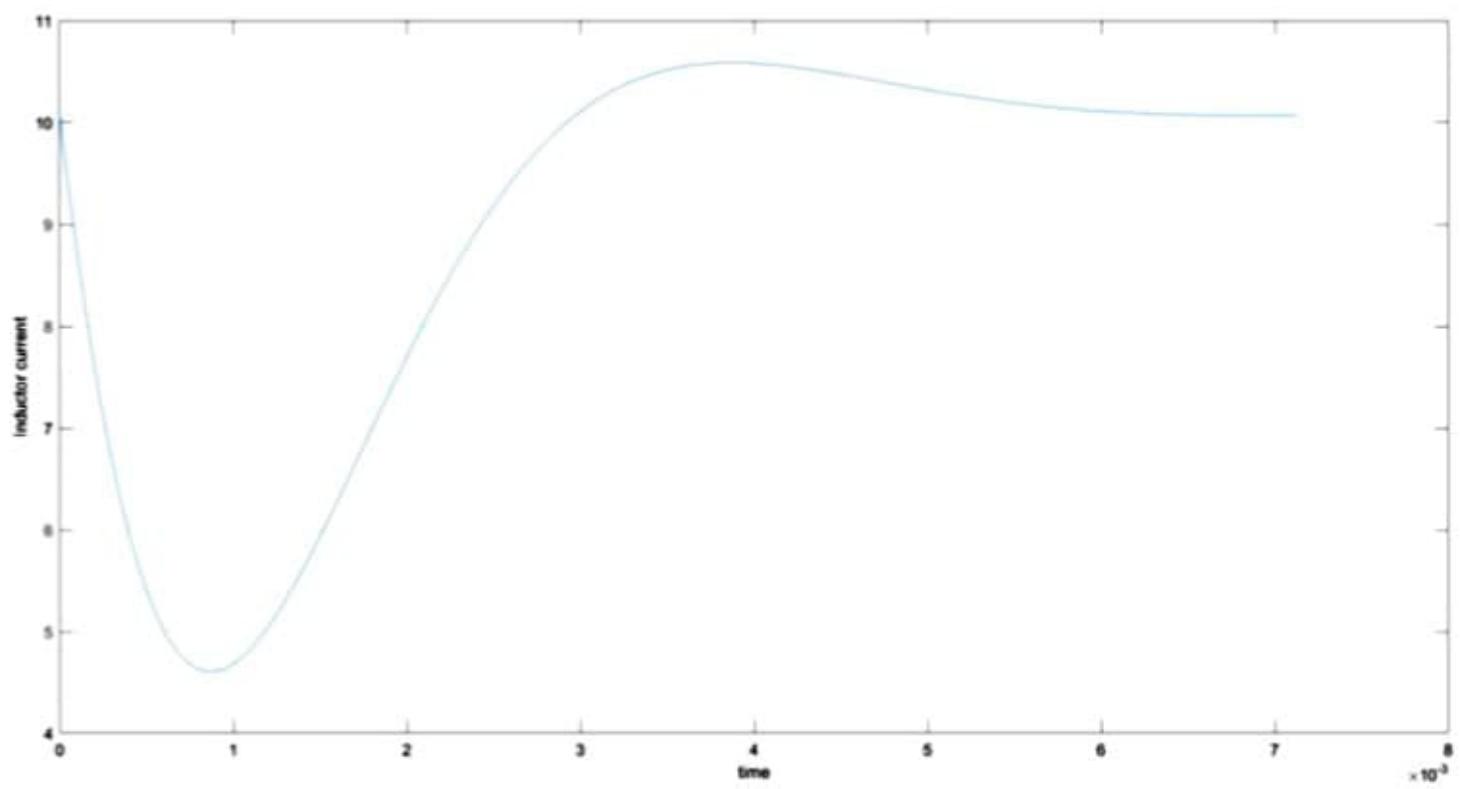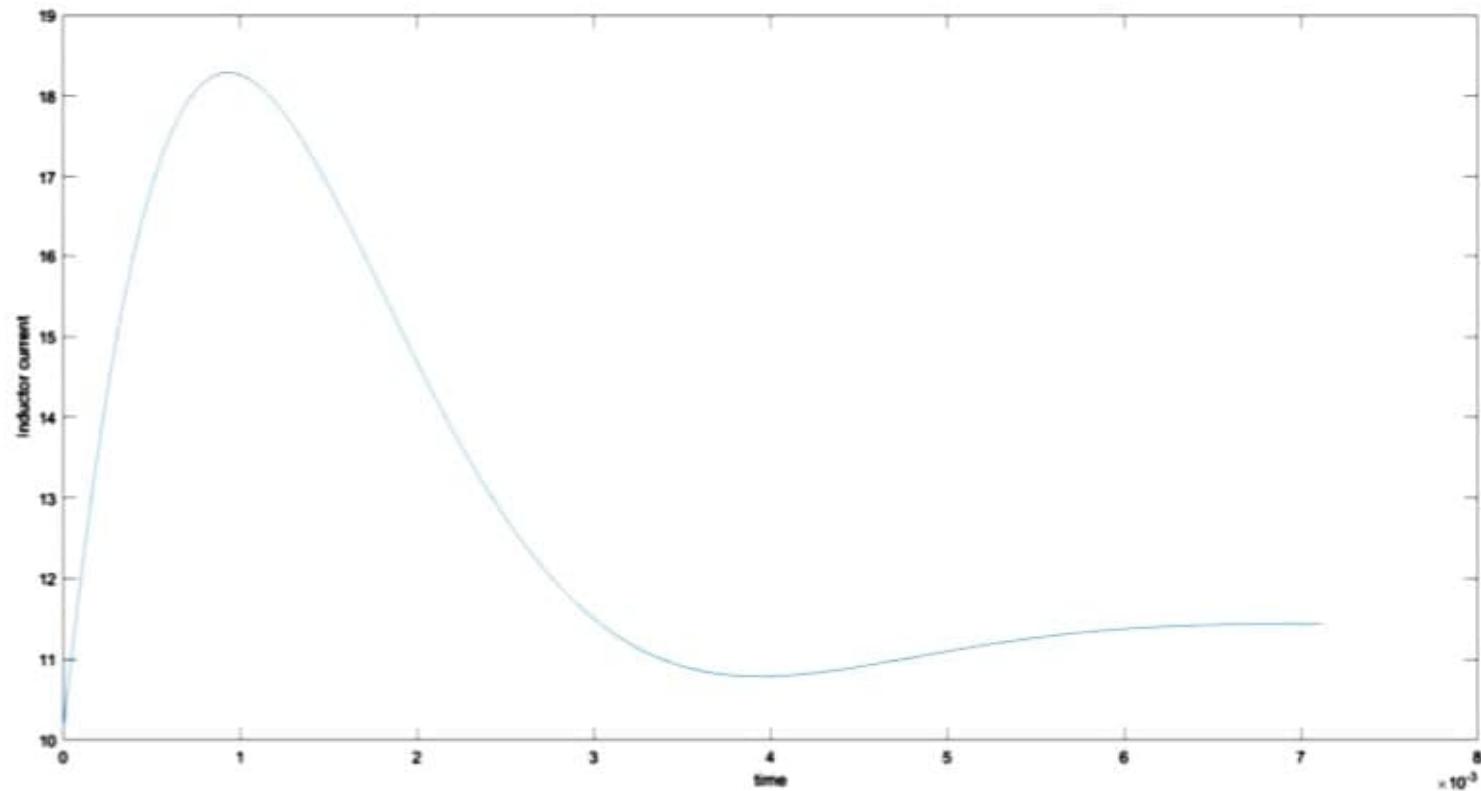
$$\Delta I_L(s) = \frac{8.592 \times 10^{32} s + 9.378 \times 10^{34}}{2.089 \times 10^{27} s^2 + 3.4 \times 10^{29} s + 3.66 \times 10^{23}} \times \frac{10^6}{s}$$



$$\underline{\Delta V_o(s)} = \frac{7.652 \times 10^{28} s + 8.31 \times 10^{33}}{5.22 \times 10^{26} s^2 + 8.5 \times 10^{29} s + 9.17 \times 10^{32}} \times \frac{-4}{5}$$

$$\underline{\Delta I_L(s)} = \frac{1.934 \times 10^{30} s}{5.23 \times 10^{26} s^2 + 8.502 \times 10^{29} s + 9.17 \times 10^{32}} \times \frac{-4}{5}$$

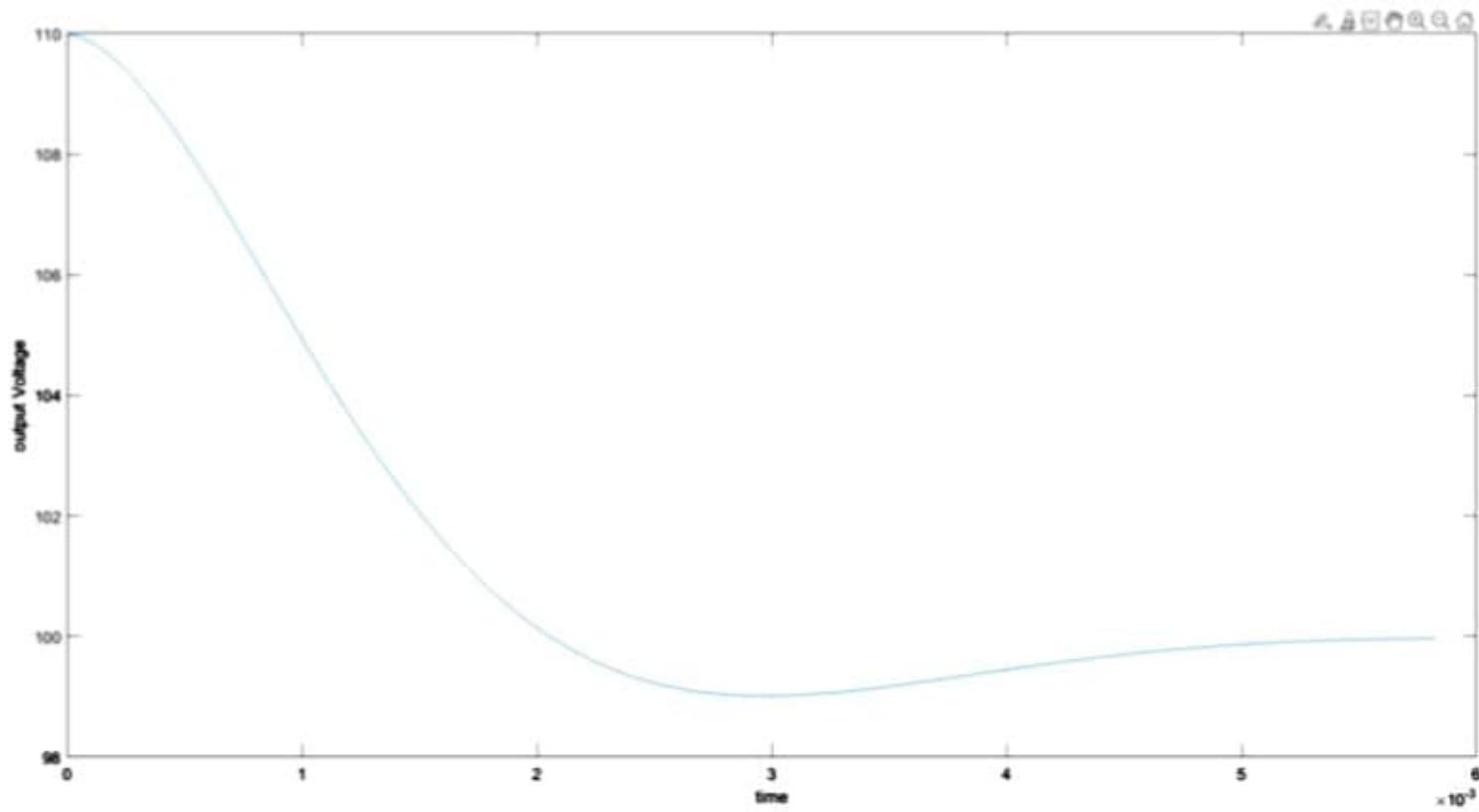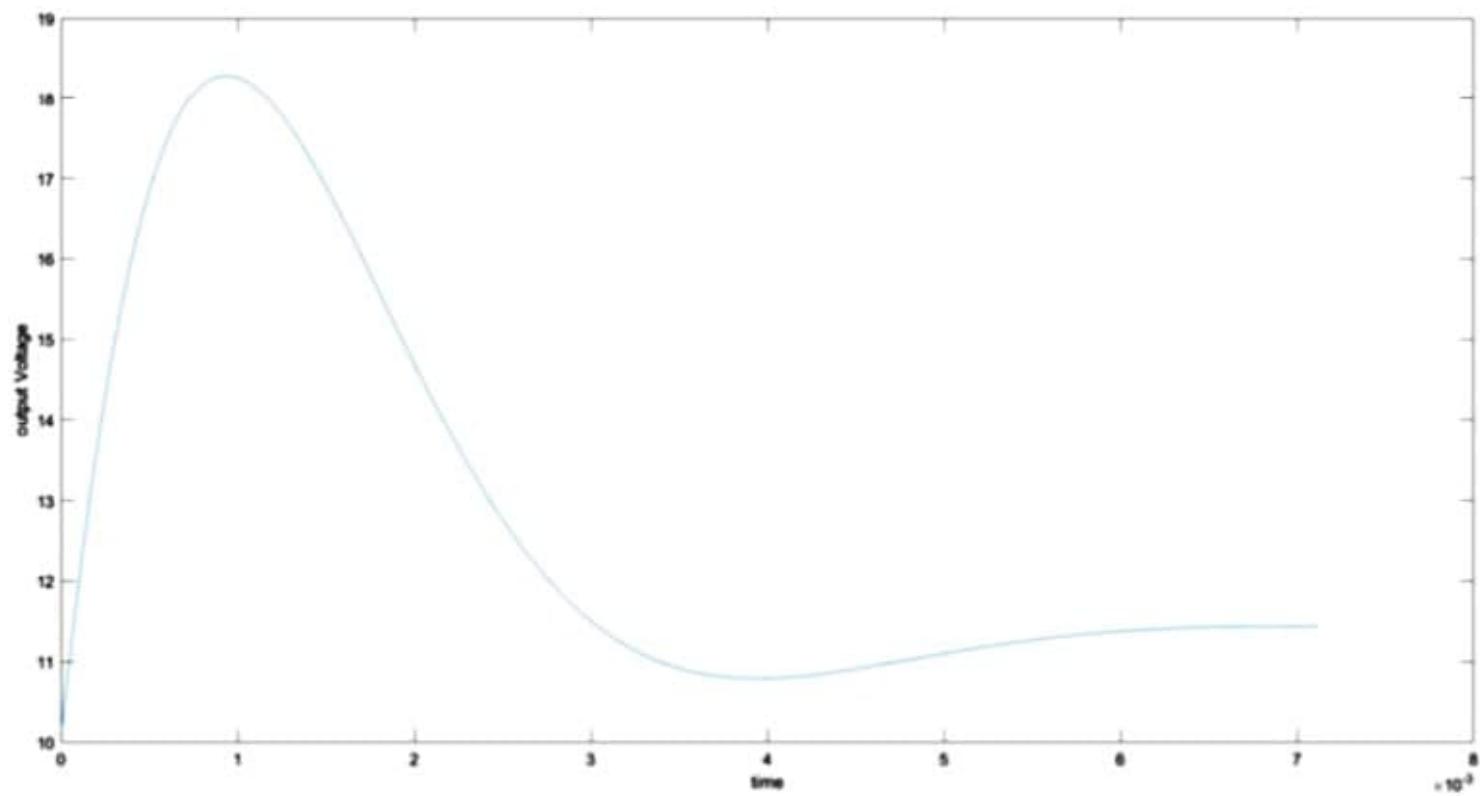

Ques 2.

a) $\frac{\Delta \bar{V}_o(s)}{\Delta d(s)} = \frac{488.51 \times 10^6 [1 - 62.7 \times 10^{-6} s]}{s^2 + 1628.14s + 1.75 \times 10^6}$

$f_{co} = 5 \text{ kHz}$, $PM = 45^\circ \rightarrow$ Bode plot.

Type I $= \frac{K}{s} = K(s)$

Phase Delay Angle of $K(j\omega_0) = 90^\circ -$ Phase delay of $G(j\omega_0) - PM$

$$|K'(j\omega_0)| = 1$$

$$\text{angle} = 0^\circ$$

($\omega_0 = 2\pi f = 3.14 \times 10^4 \text{ rad/sec}$)
 \therefore for $f_{co} = 5 \text{ kHz}$, the angle $G(j\omega_0) = -122^\circ$

\therefore Phase delay of $G(j\omega_0) = 16.4^\circ$

$$\therefore \phi = 90^\circ - 122^\circ - PM$$

$$PM = 90^\circ - 32^\circ$$

\therefore Type I design is not possible if the cross over is specified at 5 kHz since PM is usually specified between 45° to 60° .


b) To find f_{co} for Type I compensator having $PM = 60^\circ$

$$\phi = 90^\circ - \text{Phase delay of } G(j\omega_0) - 60^\circ$$

$$\text{Phase delay of } G(j\omega_0) = 30^\circ$$

\therefore from the Bode plot, Phase having 30° , the corresponding $f_{co} = 80.9 \text{ Hz}$
 $\omega_{gc} = 508.3 \text{ rad/sec}$

Bode Diagram

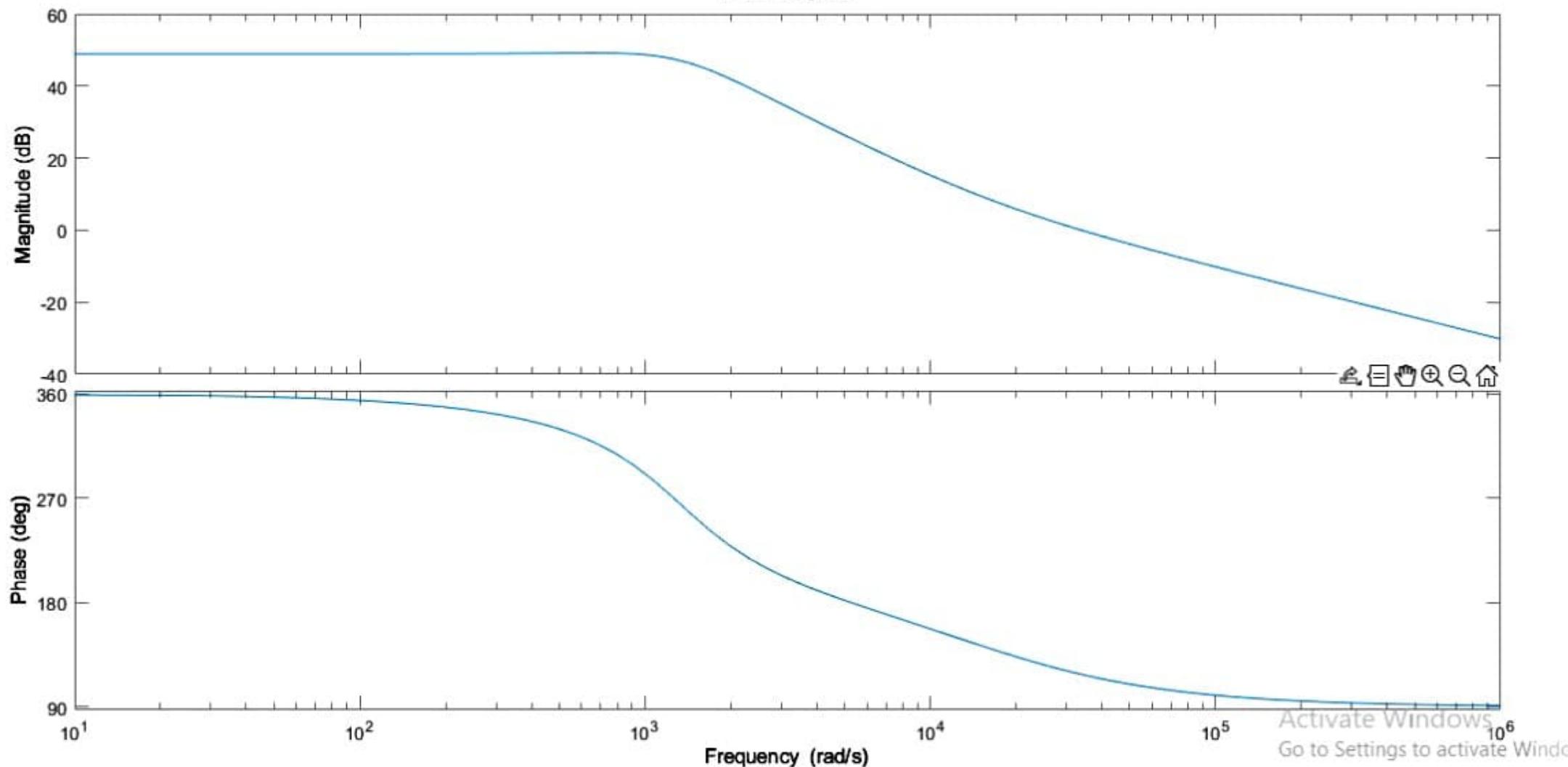

c) $f_{co} = ?$ for Type II Compensation, $PM = 60^\circ$

$$\begin{aligned}\text{Phase delay of } \alpha(j\omega_{co}) &= 180^\circ - PM \\ &= 180^\circ - 60^\circ \\ &= 120^\circ\end{aligned}$$

Now from the Bode Plot we can get the f_{co} corresponding to 120° i.e., $(360^\circ - 120^\circ = 240^\circ)$

$$f_{co} = 240 \text{ Hz}$$

$$\therefore \omega_{co} = 2\pi f = 1570 \text{ rad/sec.}$$

d) $f_{co} = ?$

$PM = 60^\circ \rightarrow \text{Type III Compensation}$

Phase delay of $\alpha(j\omega_{co}) + PM \leq 240^\circ$

$$\text{Phase delay of } \alpha(j\omega_{co}) = 240 - 60^\circ = 180^\circ$$

Now, from the Bode plot we can get the f_{co} corresponding to 180°

$$\text{Phase} = 360^\circ - 180^\circ = 180^\circ$$

f_{co} corresponding to $180^\circ = 1.11 \text{ KHz}$

$$f_{co} = 1100 \text{ Hz}$$

$$\therefore \omega_{co} = 2\pi \times 1100 = 6908 \text{ rad/sec.}$$

e) To Design Compensator $T_0 F$ in 'b', 'c', 'd' part
for 'b' part

$$f_{co} = 81 \text{ Hz}$$

$$\omega_{co} = 50 \text{ rad/sec.}$$

$$|G \cdot M| = 49 \text{ dB}$$

$$20 \log |M| = 49 \text{ dB}$$

$$|M| = 281.83$$

$$\therefore K = \frac{\omega_{co}}{|G(j\omega_0)|} = \frac{50}{281.83} = 1.81$$

$$\therefore K(s) = \frac{1.81}{s} \rightarrow \text{Type I compensation.}$$

for 'c' part

$$\omega_{co} = 1570 \text{ rad/sec.}$$

Phase delay = 110°

$$|G \cdot M|_{dB} = 46 \text{ dB}$$

$$PM = 60^\circ$$

$$20 \log |M| = 46$$

$$|M| = 200$$

$$K(s) = \frac{K}{s} \frac{(1 + \tau_2 s)}{(1 + \tau_p s)} = \frac{K}{s} \times K'(s)$$

$$\omega_2 = \frac{\omega_{co}}{f_K}, \quad \omega_p = \frac{f_K \omega_{co}}{2}$$

$$f_K = \tan \left\{ \frac{\text{Phase Delay angle of } G(j\omega_0) + PM}{2} \right\}$$

$$f_K = \tan \left\{ \frac{110^\circ + 60^\circ}{2} \right\}$$

$$f_K = 11.43$$

$$\therefore |K'(j\omega_0)| = K = 11.43$$

$$K \times 11.43 = \frac{\omega_{c0}}{|G(j\omega_0)|}$$

$$K = \frac{1570}{11.43 \times 200}$$

$$K = 0.687$$

$$T_2 = \frac{f_c}{\omega_{c0}} = \frac{11.43}{1570}$$

$$T_2 = 7.2 \text{ msec.}$$

$$T_p = \frac{1}{f_c \omega_{c0}} = \frac{1}{1570 \times 11.43}$$

$$T_p = 55.7 \mu\text{sec}$$

$$\therefore K(s) = \frac{K}{s} \frac{(1 + T_2 s)}{(1 + T_p s)}$$

$$K(s) = \frac{0.687}{s} \frac{(1 + 7.2 \times 10^{-3} s)}{(1 + 55.7 \times 10^{-6} s)}$$

Type II
Compensation

"for d part"

$$f_{c0} = 1100 \text{ Hz}$$

Phase delay = 190°

$$\omega_{c0} = 6908 \text{ rad/sec.}$$

$$K(s) = \frac{K}{s} \frac{(1 + T_2 s)^2}{(1 + T_p s)^2}$$

$$K |K'(j\omega_0)| = \frac{\omega_{c0}}{|G(j\omega_0)|}$$

$$|K'(j\omega_0)| = K^2$$

$$K = \tan \left\{ \frac{90^\circ + \text{Phase delay of } G(j\omega_0) + PM}{4} \right\}$$

$$K = \tan \left\{ \frac{90 + 190^\circ + 60^\circ}{4} \right\}$$

$$f_k = 11.43$$

$$|K'(j\omega_{co})|_r = f_k^2 = (11.43)^2 = 130.64$$

$$\left| G(j\omega_B) \right|_{dB} = 23dB$$

$$20 \log |M| = 23$$

$$|M| = 14.12$$

$$K = \frac{\omega_{co}}{|K'(j\omega_{co})| |a(j\omega)|}$$

$$K = \frac{6908}{130.64 \times 14.12}$$

$$K = 3.74$$

$$T_2 = \frac{f_k}{\omega_{co}} = \frac{11.43}{6908}$$

$$= 1.6 \text{ msec}$$

$$T_p = \frac{1}{K\omega_{co}} = \frac{1}{11.43 \times 6908}$$


$$= 12.6 \text{ usec.}$$

$$\therefore K(s) = \frac{K}{s} \frac{(1 + T_2 s)^2}{(1 + T_p s)^2}$$

$$K(s) = \frac{3.74}{s} \frac{(1 + 1.6 \times 10^{-3} s)^2}{(1 + 12.6 \times 10^{-6} s)^2}$$

Type III
Compensation

f) Design Circuits

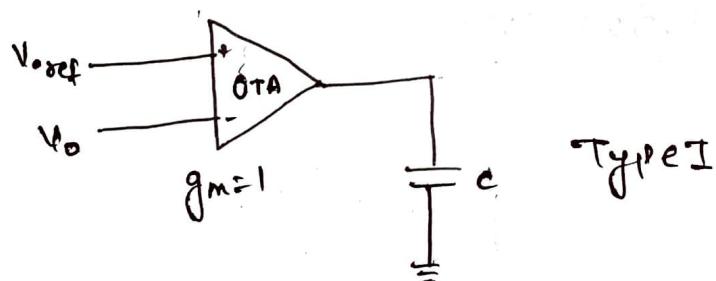


As we know,

$$\frac{K}{s} = \frac{g_m}{s \cdot C}$$

$$K = \frac{g_m}{C}$$

$$C = \frac{g_m}{K} = \frac{10n}{1.81}$$

$$C = 552.4 \text{ nF}$$

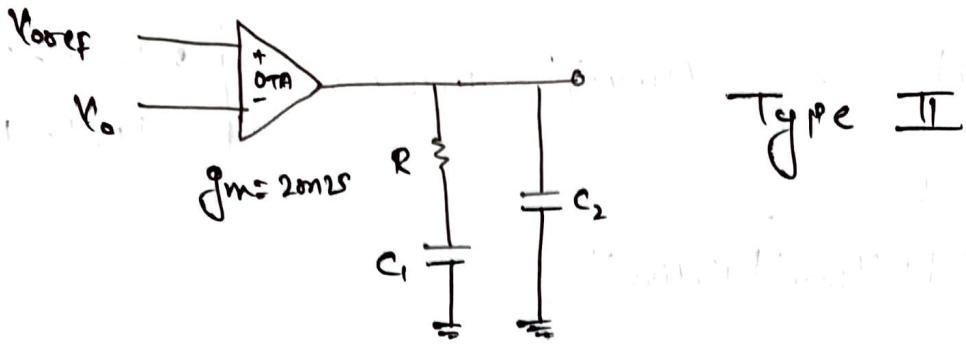

$$H(s) = \frac{g_m}{\frac{G + C_2}{s}} \left[\frac{1 + SRC_1}{1 + SRC_1 C_2} \right]_{C_1 + C_2}$$

$$\frac{g_m}{C_1 + C_2} = 0.733$$

$$RC_1 = 7.13 \times 10^{-3}$$

$$\frac{R_2 C_2 C_1}{C_1 + C_2} = 54.6 \times 10^{-6}$$

$$C_1 + C_2 = \frac{2m}{0.733} = 2.728 \times 10^{-3}$$

$$C_2 = \frac{54.4 \times 10^{-6} \times 2.728 \times 10^{-3}}{7.13 \times 10^{-3}}$$

$$C_2 = 20.89 \mu F$$


$$C_1 = 2707 \mu F$$

$$R = \frac{7.13 \times 10^{-3}}{2707 \times 10^{-6}}$$

$$R = 2.63 k\Omega$$

Ques 3. a) Type III Compensator, $PM = 60^\circ$, close loop Control block diagram in MATLAB.

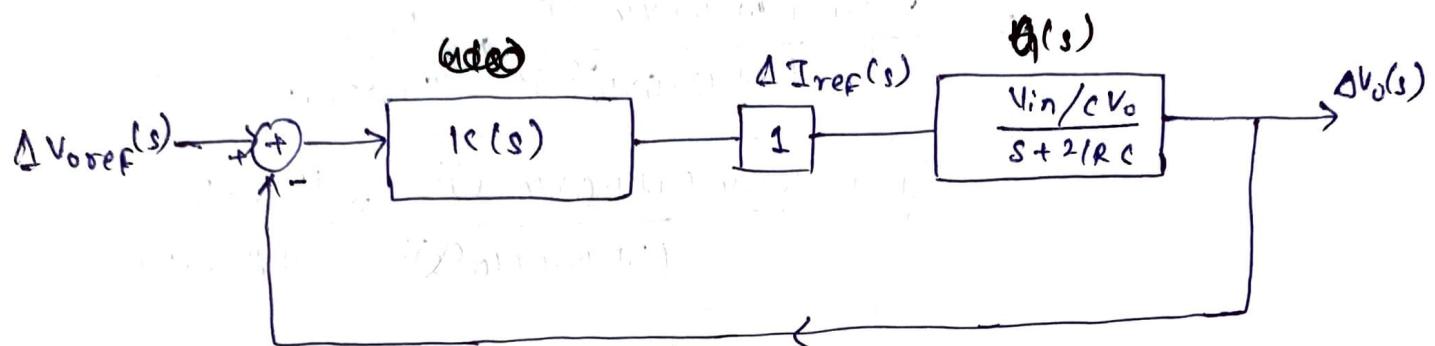
Soln:- $K(s) = \frac{3.74}{s} \frac{(1 + 1.6 \times 10^{-3}s)^2}{(1 + 12.6 \times 10^{-6}s)^2}$




$$G(s) = \frac{V_{in}/cV_o}{s + 2/Rc} = \frac{48/330\mu \times 110}{s + \frac{2}{27.5 \times 330\mu}}$$

$$= \frac{0.0013 \times 10^6}{s + \frac{2}{9075\mu}}$$

$$G(s) = \frac{1322.3}{s + 220.38}$$

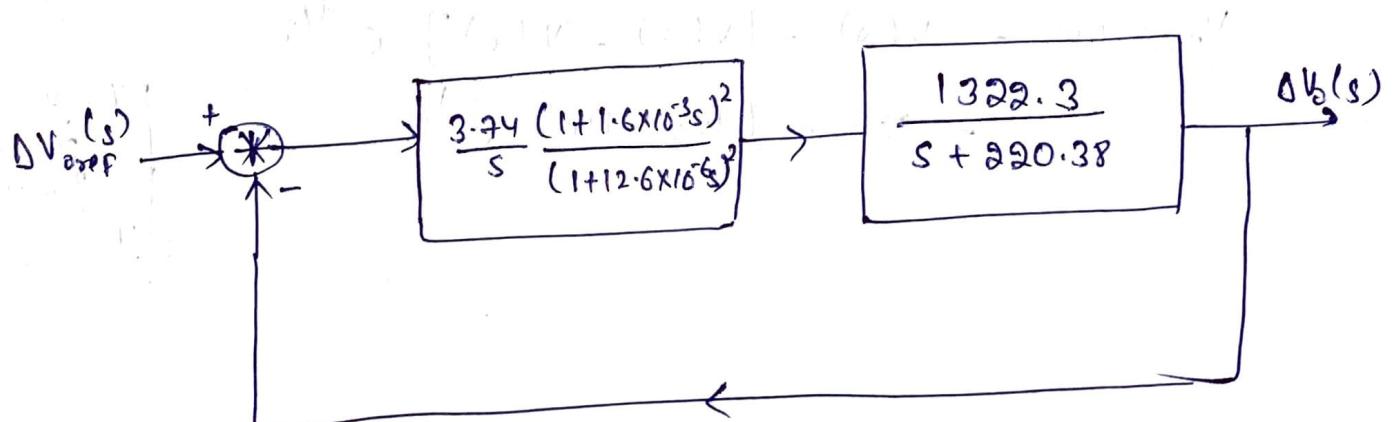

close loop Block diagram with MATLAB Model is attached with file.

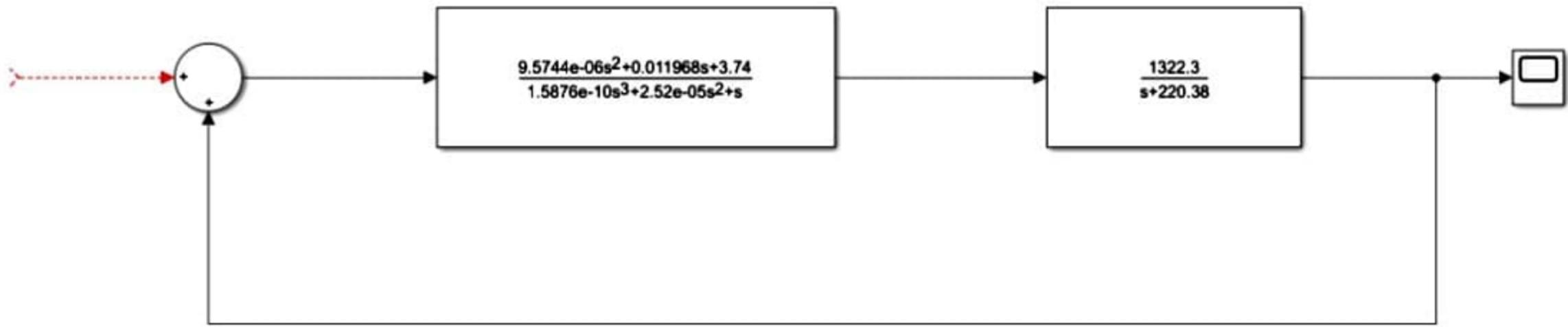

Ques 3.

b and c part planeforms are shown using MATLAB.

