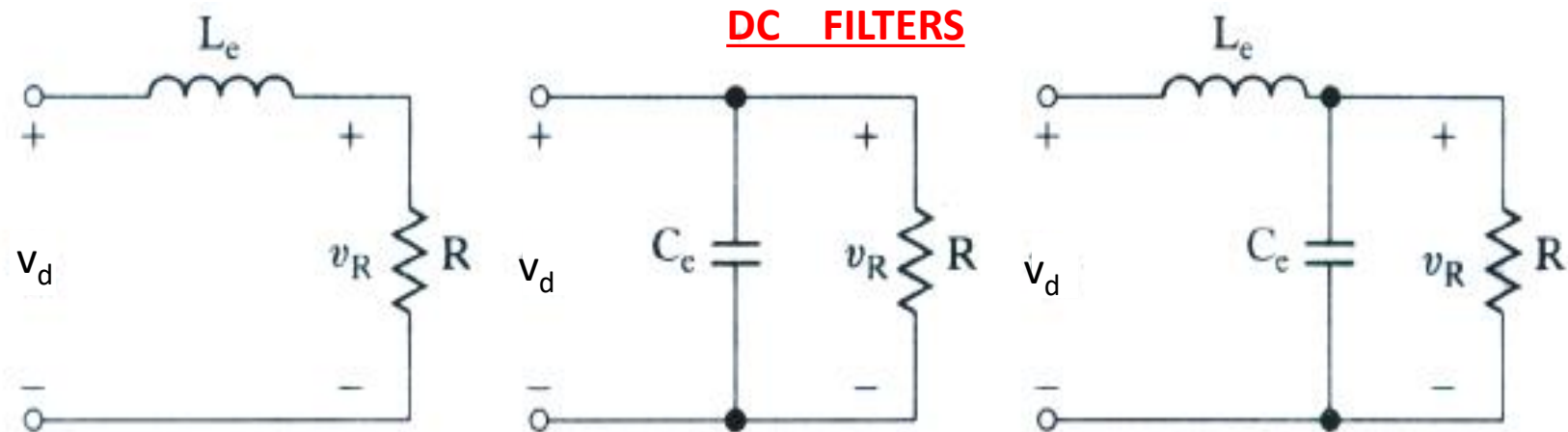


# Rectifier circuit design

- Determination of the rating of semiconductor diodes
  - average current, rms current, peak current and peak inverse voltage
- Design of filters at the output (dc side) to remove voltage harmonics. These filters are called dc filters.

They are L, C and LC type



➤ Design of filters at the input (ac side) to remove current harmonics. These filters are called ac filters. ac filters are usually of LC type.

- DC FILTERS
- To design a dc filter circuit, knowledge of the magnitude and frequency of harmonics at the dc side is required.
- Output voltage is

$$v_d(\omega t) = V_{dav} + \sum_{n=1,2,3,\dots}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

$$V_{dav} =$$

$$\frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t = \frac{2V_m}{\pi}$$

$$a_n = \frac{1}{\pi / 2} \int_0^{\pi} V_m \sin \omega t \cos n\omega t \, d\omega t$$

$$= \frac{4V_m}{\pi} \sum_{n=2,4,6,\dots}^{\infty} \frac{-1}{(n-1)(n+1)}, n = 2, 4, 6, \dots$$


$$b_n = \frac{2}{\pi} \int_0^{\pi} V_m \sin \omega t \sin n\omega t \, d\omega t = 0$$

$$v_d(t) = \frac{2v_m}{\pi} - \frac{4v_m}{3\pi} \cos 2\omega t - \frac{4v_m}{15\pi} \cos 4\omega t - \frac{4v_m}{35\pi} \cos 6\omega t - \dots$$

- **Output voltage of the full wave rectifier contains only even harmonics.**
- **Second harmonic at 100Hz is the most dominant harmonic.**

- L filter to reduce ripple in output current

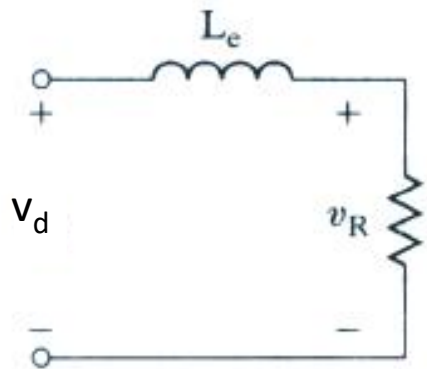A single phase bridge rectifier is supplied from a 220V, 50Hz source. Load resistance is 500  $\Omega$ . Calculate the value of series inductor L that limits the rms ripple current to be less than 5% of  $I_{dc}$



$$v_d(t) = \frac{2v_m}{\pi} - \frac{4v_m}{3\pi} \cos 2\omega t - \frac{4v_m}{15\pi} \cos 4\omega t - \frac{4v_m}{35\pi} \cos 6\omega t - \dots$$

$$i_d(t) = \frac{2v_m}{\pi R} - \frac{\frac{4v_m}{3\pi} \cos 2\omega t - \frac{4v_m}{15\pi} \cos 4\omega t - \frac{4v_m}{35\pi} \cos 6\omega t - \dots}{\sqrt{R^2 + (n\omega L)^2} \left\langle \tan^{-1} \frac{n\omega L}{R} \right\rangle}$$

$$i_d(t) = \frac{2v_m}{R\pi} - \frac{4v_m}{\pi \sqrt{R^2 + (n\omega L)^2}} \left[ \frac{1}{3} \cos(2\omega t - \theta_2) + \frac{1}{15} \cos(4\omega t - \theta_4) + \dots \right]$$

$$\theta_n = \tan^{-1} \frac{n\omega L}{R}$$

DC value of output current

$$I_{dc} = \frac{2v_m}{\pi R}$$

RMS value of ripple current  $I_{ac}$

$$I_{ac}^2 = \frac{(4v_m)^2}{2\pi^2(R^2 + (2\omega L)^2)} \left[ \frac{1}{3} \right]^2 + \frac{(4v_m)^2}{2\pi^2(R^2 + (4\omega L)^2)} \left[ \frac{1}{15} \right]^2 + \dots$$

**Neglecting all harmonics other than predominant second harmonic**

$$I_{ac}^2 = \frac{(4v_m)^2}{2\pi^2(R^2 + (2\omega L)^2)} \left[ \frac{1}{3} \right]^2$$

$$RF = \frac{I_{ac}}{I_{dc}} =$$

$$L =$$