


# SMRC TEST - 2

NAME - KARUNA KUMARI

ROLL NO - M200203EE


BRANCH - POWER ELECTRONICS

Ques. Effect of leakage inductance

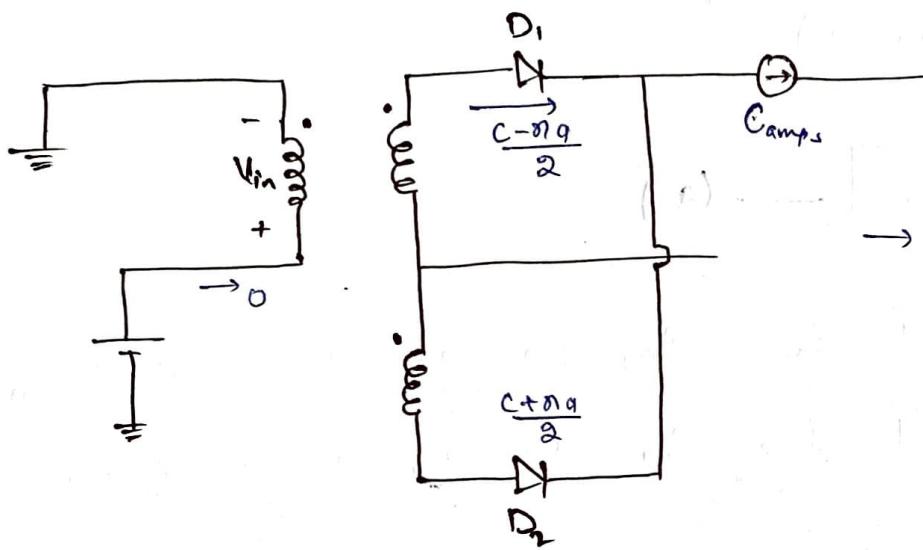

→ Considering the switching on  $S_2$ .

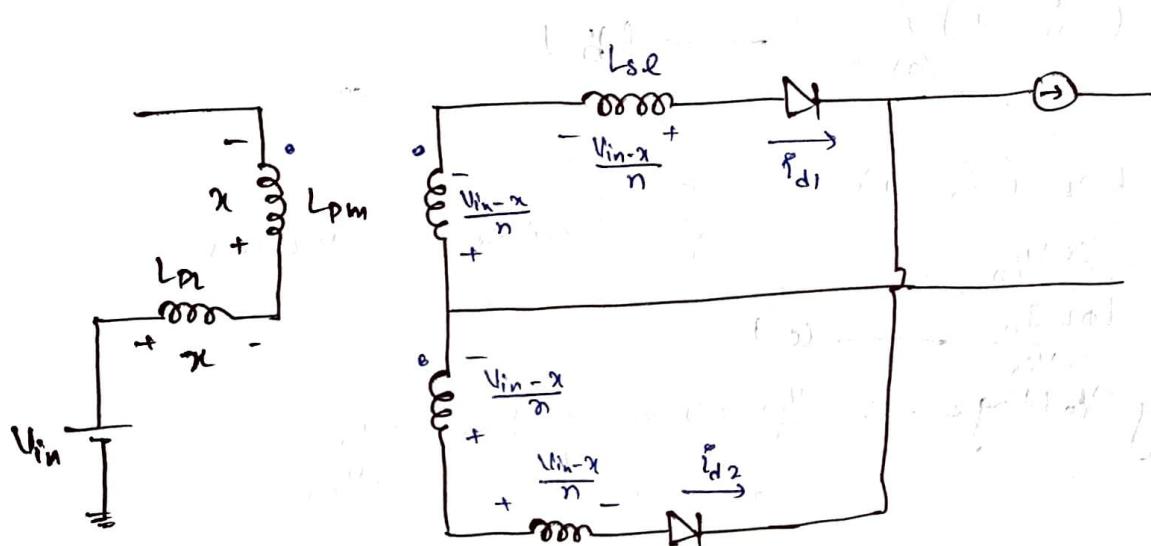Now, cut at the instant  $S_2 \rightarrow \text{ON}$ .



$$\text{So, } i_{p2} = \frac{i_{d2} - i_{d1}}{n}$$

$$\therefore \frac{di_{p2}}{dt} = \frac{1}{n} \left( \frac{di_2}{dt} - \frac{di_1}{dt} \right)$$

$$= \frac{1}{n} \left[ \frac{V_{in} - n}{n L_{se}} - \left( -\frac{V_{in} - n}{n L_{se}} \right) \right]$$

$$\frac{di_{P2}}{dt} = \frac{2(V_{in} - x)}{n^2 L_{se}}$$

$$x = L_{PL} \frac{di_{P2}}{dt} = \frac{2L_{PL}}{n^2 L_{se}} (V_{in} - x)$$

$$\text{But } L_{PL} = n^2 L_{se}$$

$$x = 2(V_{in} - x)$$

$$3x = 2V_{in}$$

$$x = \frac{2}{3} V_{in} \quad \text{--- (a)}$$

$\therefore$  Time required for  $i_{P2}$  to go from 0 to  $\frac{c}{n} - a$

Time required for  $i_d$  to go from  $\frac{c-a}{2}$  to 0

Time required for  $i_s$  to go from  $\frac{c+a}{2}$  to c

$$= L_{PL} \left( \frac{c}{n} - a \right) / \sigma \quad \text{--- (b)}$$

$$\therefore = \frac{3 L_{PL} \left( \frac{c}{n} - a \right)}{2 V_{in}} \quad \left\{ \begin{array}{l} \text{Placing } x \text{ values.} \\ \text{--- (c)} \end{array} \right.$$

$$\approx \frac{3}{2} \frac{L_{PL} I_0}{n V_{in}}$$

$$\therefore \text{loss of Voltage} = \frac{V_{in} \times 2 \times \frac{3}{2} L_{PL} \frac{I_0}{n V_{in}}}{\sigma} \quad \text{--- (d)}$$

$$= \frac{3 f_s L_{PL} I_0}{\sigma^2}$$

$$\therefore V_o = \frac{2dV_{in}}{n} - \frac{3f_s L_{PL} I_0}{n^2}$$

for ratio

$$\frac{V_o}{V_{in}} = \frac{2d}{n} - \frac{3f L_{PL} I_o}{n^2 V_{in}}$$

So, if  $L_{PL} \uparrow$  then the ratio values get decreased.

∴ Moto, If seeing from eq<sup>n</sup> (c)

$I_o$  is inversely proportional to  $L_{PL}$ . So if leakage inductance increases,  $I_o$  gets decreased.

Ques 2. Given

$$V_{in} = 400 \text{ V}$$

$$L = 70 \text{ mH}$$

$$C = 290 \text{ nF}$$

$$f_s = 25 \text{ kHz}$$

$$n = 11$$

$$V_{out} = 12 \text{ V}$$

Primary self inductance =  $2.2 \text{ mH}$

$$C_1 = C_2 = C = 3.3 \text{ nF}$$

$$I_o = 10 \text{ A}$$


a)

$$n = \frac{I_o}{I_p}$$

$$I_p = 10/11 = 0.909$$

$$\boxed{I_p = 0.909 \text{ A}}$$

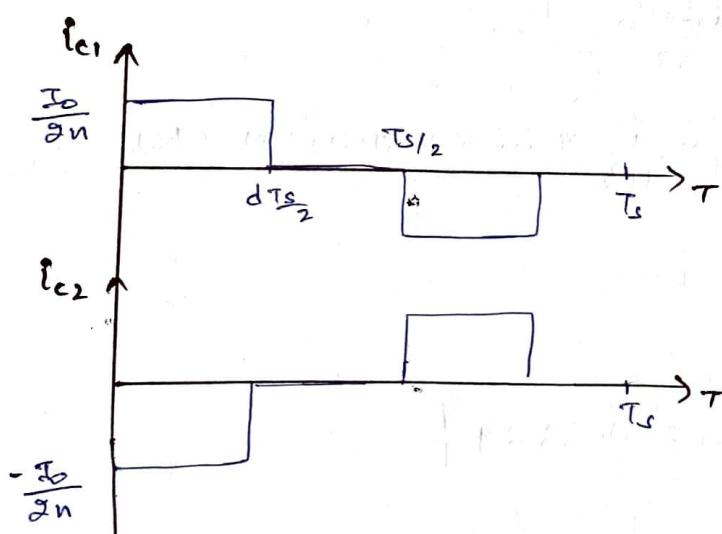$C_1$  and  $C_2 = C$  function as voltage splitting capacitor  
 $i_{c1}$  and  $i_{c2}$  have the following approximate shape.



$$I_{c1} = \frac{I_o}{2n} = \frac{I_p}{2}$$

$$= \frac{0.909}{2} = 0.4545 \text{ A.}$$

$$I_{C_1} = 0.4545 \text{ A}$$

$$I_{C_2} = -\frac{I_o}{2n} = -\frac{I_p}{2} = -0.4545 \text{ A}$$

$$\therefore I_{C_1} = 0.4545 \text{ A}$$

$$, I_{C_2} = -0.4545 \text{ A}$$

b) leakage inductance = 3%

$$V_o = 12 \text{ V}$$

$$\begin{aligned} \text{leakage inductance} &= 3\% \text{ of } 2.2 \text{ mH} \\ &= 0.03 \times 2.2 \text{ mH} \\ &= 0.081 \text{ mH} \end{aligned}$$

$$V_o = \frac{d V_{in}}{n} - \text{Voltage loss}$$


$$= \frac{d V_{in}}{n} - \frac{3}{2} \frac{f_o L_o I_o}{n^2}$$

$$12 = d \times \frac{400}{11} - \frac{3}{2} \times \frac{1}{11^2} \times 25 \text{ k} \times 0.081 \text{ m} \times 10$$

$$d = 0.3369$$

$$\therefore \boxed{\text{Duty ratio} = 0.3369}$$

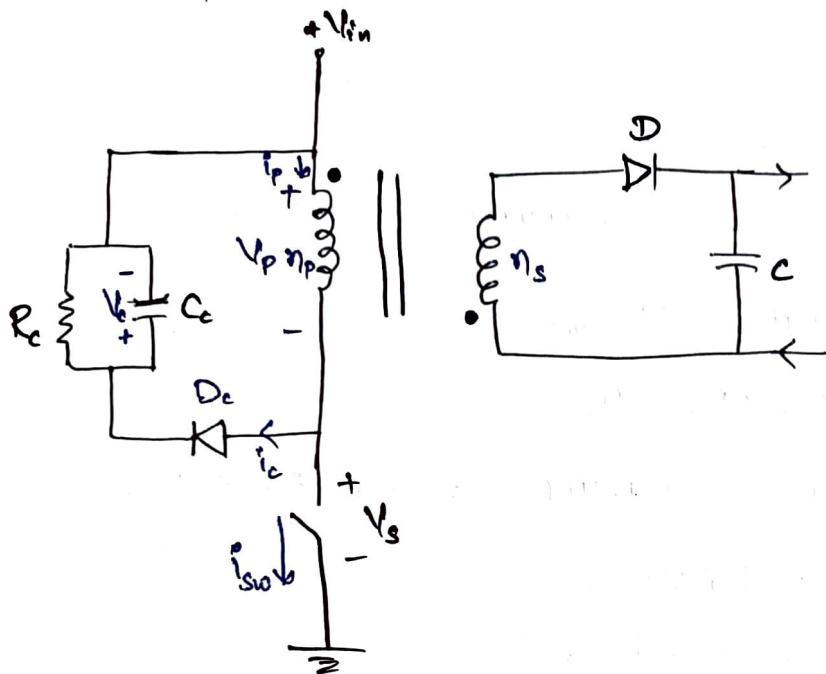
### Ques 3. Need for and Operation of Voltage Clamp Circuit in flyback converters :-



As the sw → off

$V_s$  changes from  $\approx 0$  to  $V_{in} + V_c$  where  $V_c$  is the steady state DC voltage across  $C_c$ .

Clamped voltage across switch.

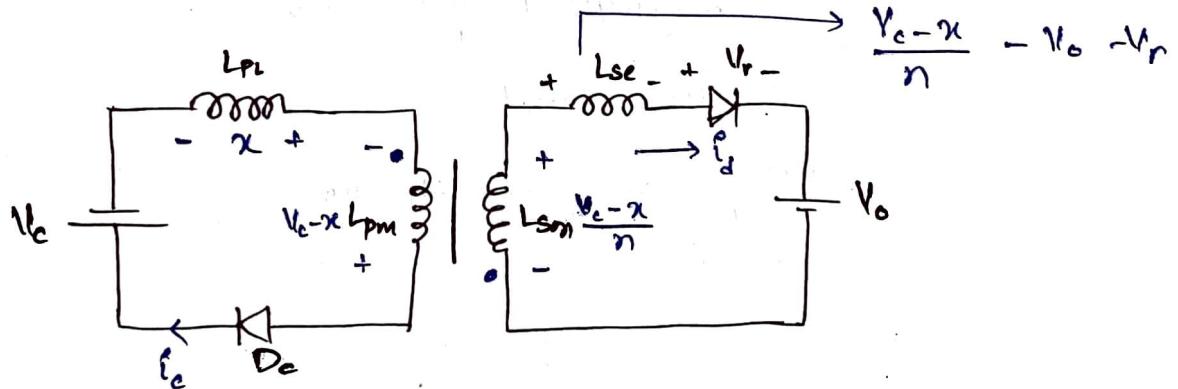

$$\text{Now, } \frac{\text{flux linkage change}}{\text{Voltage}} = \frac{L_{PL} I_p}{x} = \frac{L_{se} (n I_p)}{\frac{V_c - x}{n} - V_0 - V_r}$$

$$\frac{L_{PL} I_p}{x} = \frac{L_{se} n^2 I_p}{V_c - x - n (V_0 + V_r)}$$

$$\Rightarrow L_{PL} I_p V_c - L_{PL} I_p x - L_{PL} I_p n V_0 - L_{PL} I_p n V_r = L_{se} n^2 I_p$$

$$\therefore \frac{L_p}{L_s} = n^2$$

$$\therefore L_{se} = L_p / n^2$$

$$L_{PL} I_P V_c - L_{PL} I_D \chi - L_{PL} I_P n V_o - L_{PL} I_P n V_r = \frac{L_{PL} \times \pi^2 I_P}{n^2} = L_{PL} \chi I_P$$

$$L_{PL} I_P [V_c - n(V_o + V_r)] = 2 L_{PL} \chi I_P$$

$$\boxed{\chi = \frac{V_c - n(V_o + V_r)}{2}}$$

Conduction time of  $D_c$ ,

$$t_c = \frac{\text{Change in flux linkage}}{\text{Voltage.}}$$


$$t_c = \frac{L_{PL} I_P}{\chi} = \frac{L_{PL} I_P \cdot 2}{V_c - n(V_o + V_r)}$$

$$\left| \begin{array}{l} \frac{L_e}{2} = L_{PL} \\ 2L_{PL} = L_e \end{array} \right.$$

$$\boxed{t_c = \frac{L_e I_P}{V_c - n(V_o + V_r)}}$$

$\rightarrow t_c$  is the current transfer time

Once, the  $D_c$  current goes to 0,

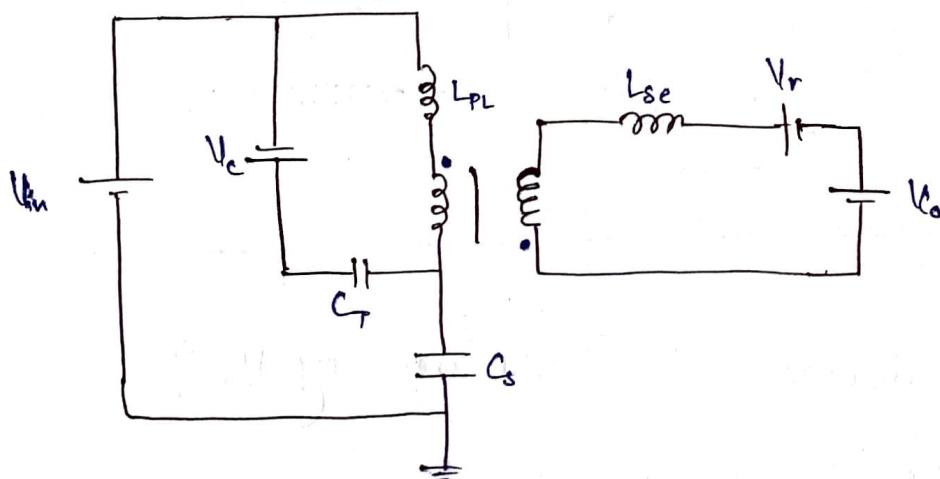




Voltage across switch, primary, diode current, primary current oscillate and settle down with oscillation frequency decided by  $L_e$ ,  $(C_T + C_o)$ .

$$V_{\text{es}} = V_{\text{in}} + V_r \rightarrow \text{Initial Voltage}$$

$$V_{\text{secondary}} = V_o + V_r$$

$$V_{\text{primary}} = n(V_o + V_r)$$

blank form

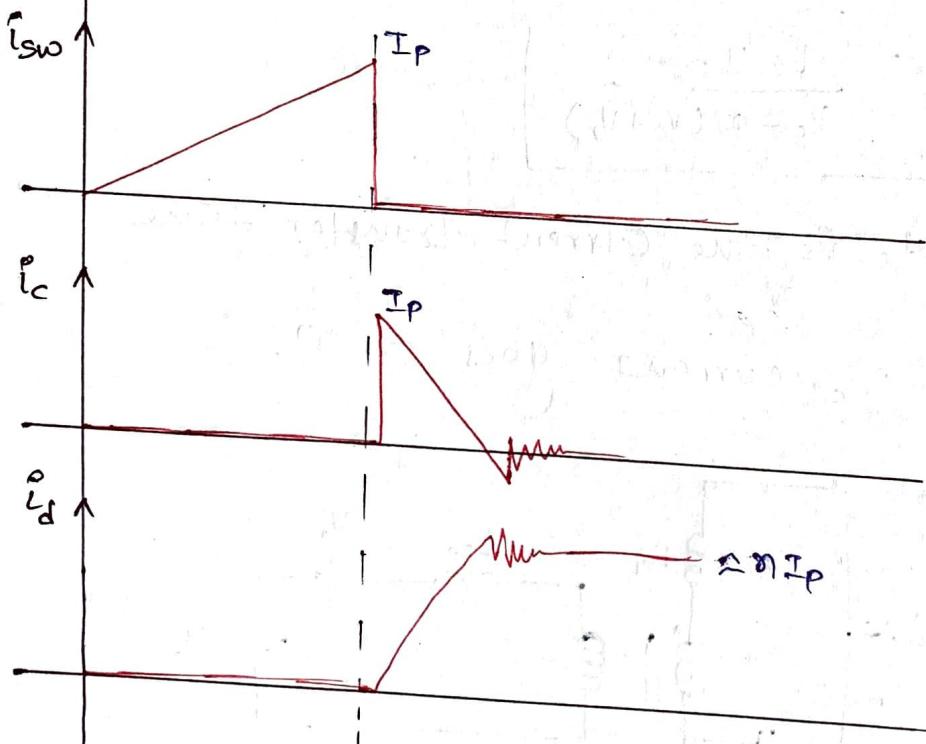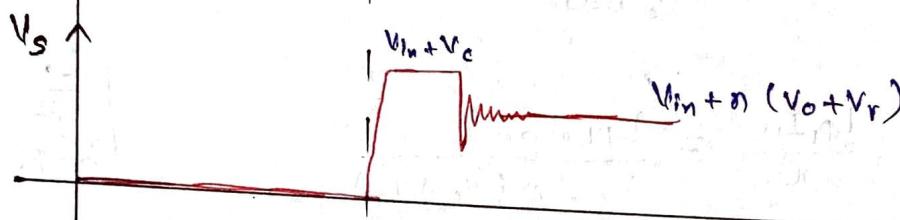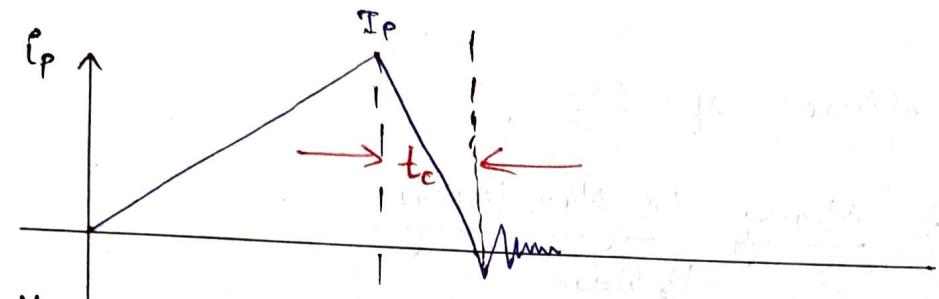

→ What decides the value of  $V_o$ ?

$$(L_o)_{\text{avg}} = \frac{1}{2} \times I_p \times t_c$$

$$= \frac{1}{2} I_p \cdot \frac{L_o I_p}{V_o - n(V_o + V_r)} \times f_s$$

$$(I_c)_{\text{avg}} = \frac{1}{2} \cdot \frac{L_e I_p^2 f_s}{V_c - n(V_o + V_r)}$$

Avg Power into  $R_o \parallel C_o$

$$P_{\text{avg}} = V_c \cdot (I_c)_{\text{avg}}$$

$$P_{\text{avg}} = P_c = \frac{1}{2} \frac{L_e I_p^2 f_s V_c}{(V_c - n(V_o + V_r))}$$

Note :-

$$P_c \text{ always } > \frac{1}{2} L_p I_p^2 f_s$$

$$\text{i.e., } P_c \text{ always } > P_{\text{in}}$$

In steady state,

$$P_c = \frac{V_c^2}{R_c}$$

$\therefore R_c$  needed to maintain a chosen  $V_c$  is

$$R_c = \frac{V_c^2}{P_c} = \frac{V_c^2}{\frac{1}{2} \frac{L_e I_p^2 f_s V_c}{V_c - n(V_o + V_r)}}$$

$$R_c = \frac{2 V_c [V_c - n(V_o + V_r)]}{f_s L_e I_p^2}$$

Frequency of  $I_c$  is ' $f_s$ '.

→ How to select Clamp Capacitor?

Ans → Clamp voltage is a dc voltage with ripple so that we select Clamp capacitor such that the ripple will be small.

Importance of Capacitor is that it is very small as compared to the resistance at switching frequency.

$$\therefore \frac{1}{2\pi f_s R_c C_o} \ll \frac{1}{20} \rightarrow \text{this much small.}$$

$$\boxed{\frac{1}{2\pi f_s C_o} \ll R_c} \rightarrow \text{To reduce the ripple in } V_o.$$

Now,

$$P_{in} = \frac{1}{2} L_p I_p^2 f_s$$

$$P_c = \frac{1}{2} L_e I_p^2 f_s \frac{V_c}{V_c - n(V_o + V_r)}$$

$\therefore$  Power transferred by Secondary

$$= P_{in} - P_c$$

$$= \frac{1}{2} L_p I_p^2 f_s - \frac{1}{2} L_e I_p^2 f_s \frac{V_c}{V_c - n(V_o + V_r)}$$

$$= \frac{1}{2} L_p I_p^2 f_s - \frac{1}{2} \frac{L_e}{L_p} L_p I_p^2 f_s \cdot \frac{V_c}{V_c - n(V_o + V_r)}$$

$$= \frac{1}{2} L_p I_p^2 f_s \left[ 1 - \frac{L_e}{L_p} \frac{V_c}{V_c - n(V_o + V_r)} \right]$$

$$= P_{in} \left[ 1 - \frac{L_e}{L_p} \frac{V_c}{V_c - n(V_o + V_r)} \right]$$

Efficiency [considering only clamp loss]


$$\eta = \left[ 1 - \frac{L_e}{L_p} \frac{V_c}{V_c - n(V_o + V_r)} \right] \times 100\%$$

$$\left\{ \begin{array}{l} \frac{L_e}{L_p} = \frac{(1-k^2)L_p}{L_p} \\ = 1-k^2 \end{array} \right.$$

Ques.

a) The magnetic flux density in the core in a push pull converter switching at 50 kHz is found to oscillate between  $-0.1 \text{ wb/m}^2$  and  $+0.3 \text{ wb/m}^2$  because of following reasons -

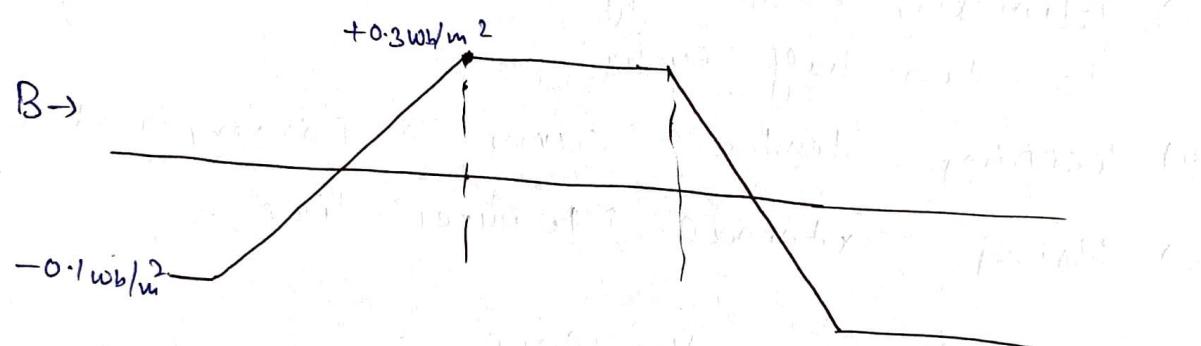- i) As the voltage applied to the primary winding and flux can not change the flux density of core goes to some level as  $0.3 \text{ wb/m}^2$ .
- ii) flux change in core during upward travel will be less than the flux change in core during downward travel.  $\therefore$  Core flux will travel in 3rd quadrant.



- iii) When the volt-second product dumped into Primary 1 when  $S_1 \rightarrow \text{ON}$  is different from volt-second product dumped into primary-2 when  $S_2 \rightarrow \text{ON}$ . This can result in any kind of asymmetry in the flux density, and hence oscillate between  $-0.1 \text{ wb/m}^2$  to  $0.3 \text{ wb/m}^2$ .

## b) flux walking problem in a full-bridge converter

This is due to the —

Duty ratio differences in two half cycles, different switching times of  $s_1$  and  $s_2$ , different conduction drops of  $s_1$  and  $s_2$ , diffusion difference in resistances of primary 1 and primary 2 and secondary 1 and secondary 2, different in characteristics etc.

### Solution for this

- 1) Handling it at problem source level.
- 2) Paying attention to symmetry of elements.
- 3) Minimize the differences between duty ratios in two half cycles.
- 4) Keeping identical turns in primary and secondary.
- 5) Using External Measures like
  - a) Capping the core
  - b) Match switches & avoid BJT's and used MOSFET
  - c) Add primary resistance
  - d) Using Current mode Control etc.

This solution will not work in case of pushpull converter because

For push pull converter we use everything of same ratings and there is also also the effect of leakage inductance.

Ques 6.

Given

$$V_{in} = 250 - 400 \text{ V}$$

$$V_o = 12 \text{ V}$$

$$\text{P-P ripple} < 120 \text{ mV}$$

$$\text{Rating of MOSFET} = 1000 \text{ V}$$

$$I_o = 2 - 6 \text{ A}$$

$$f_s = 50 \text{ kHz}$$

$$C_x \text{ ESR} = 30 \mu\text{s}$$

$$B_m = 0.2 \text{ wb/m}^2$$

$$J = 3 \text{ A/mm}^2$$

$$k_s = 0.35$$

transformer thickness = 1 mm

Creeping distance = 8 mm.

Soln:-

$$P_{on P} = 12 \times 6 = 72 \text{ W}$$

$$P_{on min} = 12 \times 2 = 24 \text{ W}$$

$$\text{Now, } 1.3 [V_{in max} + n(V_o + V_r)] = 0.8 V_R$$

$$\text{Let } V_r = 1 \text{ V}$$

$$1.3 [400 + n(12+1)] = 0.8 \times 1000$$

$$n = 16.56 \text{ turns}$$
  
$$\therefore [n \approx 17 \text{ turns}]$$

$$\text{Now, } L_{P \text{ min}} = \left( \frac{n(V_o + V_r) V_{in max}}{D(V_o + V_r) + V_{in max}} \right)^2 \times \frac{1}{2 f_s P_{on min}}$$

$$L_{P \text{ min}} = \left( \frac{17(12+1) \times 400}{16(13) + 400} \right)^2 \times \frac{1}{2 \times 50 \times 10^{-3} \times 24}$$

$$[L_{P \text{ min}} = 8.44 \text{ mH}]$$

## Secondary RMS Calculation

$$d_{\min} = \frac{n(V_o + V_r)}{n(V_o + V_r) + V_{\max}}$$

$$d_{\min} = \frac{17 \times 13}{17 \times 13 + 400} = 0.355$$

$$d_{\max} = \frac{17 \times 13}{17 \times 13 + 250} = 0.469$$

$$I_{p\max} + I_{p\min} = \frac{2 P_{o\max}}{n V_o (1 - d_{\min})}$$

$$= \frac{2 \times 72}{17 \times 12 (1 - 0.355)}$$

$$\Rightarrow I_{p\min} + I_{p\max} = 1.09 \text{ A} \quad \text{---(i)}$$

$$-I_{p\min} + I_{p\max} = \frac{n(V_o + V_r)(1 - d_{\min})}{L_p f_s}$$

$$= \frac{17 \times 13 (1 - 0.355)}{8.44 \text{ m} \times 50 \text{ Hz}}$$

$$-I_{p\min} + I_{p\max} = 0.3377 \quad \text{---(ii)}$$

from (i) and (ii)

$$I_{p\max} = 0.71 \text{ A}$$

$$I_{p\min} = 0.38 \text{ A}$$

$$I_{\text{secondary}} = \left( \frac{n I_{p\max} + n I_{p\min}}{2} \right) \sqrt{1 - d_{\min}}$$

$$= 17 \left( \frac{0.71 + 0.38}{2} \right) \sqrt{1 - 0.355}$$

$$(I_{\text{sec.}})_{\text{rms}} = 7.43 \text{ A}$$

$$I_{\text{avg}} = I_0 = 6 \text{ A}$$

$$(I_d)_{\text{peak}} = 17 \times 0.21 = 12.07 \text{ A}$$

$$I_d \text{ peak} = 12.07 \text{ A}$$

$$I_{d \text{ avg}} = 17 \times \frac{1.09}{2} (1 - 0.355)$$

$$I_{d \text{ avg}} = 5.97 \text{ A}$$

### Primary Calculation

$$I_{p \text{ max}} + I_{p \text{ min}} = \frac{2 I_{d \text{ max}}}{n(1 - d_{\text{max}})}$$

$$I_{p \text{ max}} + I_{p \text{ min}} = \frac{2 \times 6}{17(1 - 0.469)} = 1.31 \text{ A} \quad \textcircled{A}$$

$$I_{p \text{ max}} - I_{p \text{ min}} = \frac{17 \times 13 (1 - 0.469)}{8.44 \times 50 \times 10^{-6}} \text{ A}$$

$$I_{p \text{ max}} - I_{p \text{ min}} = 0.278 \quad \textcircled{B}$$

from  $\textcircled{A}$  and  $\textcircled{B}$

$$I_{p \text{ max}} = 0.79 \text{ A}$$

$$I_{p \text{ min}} = 0.52 \text{ A}$$

$$(I_{\text{primary}})_m = \frac{I_{p \text{ max}} + I_{p \text{ min}}}{2} \sqrt{d_{\text{max}}} = \frac{1.31}{2} \sqrt{0.469}$$

$$(I_{\text{primary}})_m = 0.448 \text{ A}$$

$$i_{\text{peak}} = I_{p \text{ max}} = 0.79 \text{ A}$$

$$i_{\text{avg}} = \frac{0.79 + 0.52}{2} \times 0.469$$

$$i_{\text{avg}} = 0.307 \text{ A}$$

Ratings -

MOSFET : peak = 0.79A , avg = 0.302A ;  $I_{RMS} = 0.448A$

Diode : peak = 12.07A , avg = 6A ;  $RMS = 7.43A$

Now, Area Product Calculation

$$A_w = n_p A_{primary} + n_s A_{secondary}$$

$$= \frac{n_p}{k_s} \left( A_p + \frac{A_s}{n} \right)$$

$$= \frac{n_p}{0.35} \left( 0.1523 + \frac{1.7135}{17} \right)$$

$$\boxed{A_w = 0.7348 n_p \text{ mm}^2}$$

$$A_p = A_c \cdot A_w$$

$$= 0.2348 n_p \times \frac{0.0322 \times 10^{-6}}{n_p}$$

$$\boxed{A_p = 93.663 \text{ mm}^4}$$

We will use here

EE 40 / 17 / 12

here,  $A_c = 149 \text{ mm}^2$

$$A_w = 2 \times 10.5 \times \frac{(18.6 - 12.5)}{2}$$

$$\boxed{A_w = 169.05}$$

$$A_p = 2518.2 \text{ mm}^4 > 23063 \text{ mm}^4$$

$\therefore$  Overall Height = 21

Usable Height = 15mm

$$\Phi_w = 0.7836 n_p$$

$$n_p = \frac{169.05}{0.7836}$$

$$n_p = 223.2 \text{ turns}$$

$$n_s = \frac{n_p}{n_s}$$

$$n_s = \frac{223}{17} = 13.11$$

$$n_s = 14 \text{ turns}$$

$\therefore$  hence we can use

$$\boxed{\begin{aligned} n_p &= 224 \text{ turns} \\ n_s &= 14 \text{ turns} \end{aligned}}$$

## Ques 2. Boost Converter

$$V_i = 10.8 - 18.6 \text{ V}$$

$$V_o = 24 \text{ V}$$

$$L = 80 \mu\text{H}$$

$$C = 680 \mu\text{F}$$

$$I = 40 \text{ ms family}$$

$$f_s = 25 \text{ kHz}$$

$$I_o = 2.4 \text{ A}$$

$$\text{Sensing gain} = 0.25 \text{ V/A}$$

To Design :- CT using  
Suitable toroidal  
ferrite core

## Soln:- Boost converter

### for Duty Cycle

$$V_o = \frac{V_{in}}{1-D}$$

$$24 = \frac{10.8}{1-D}$$

$$D = 0.55$$

$$24 = \frac{12.6}{1-D}$$

$$D = 0.433$$

$$\therefore \text{Using } D_{max} = 0.55$$

$$\text{Now, } P_{op} = P_{in}$$

$$V_{in} I_{in} = V_o I_o$$

$$V_{in} I_{in} = \frac{V_{in} I_o}{1-D}$$

$$I_{in} = \frac{I_o}{1-D}$$

$$\therefore I_{in\ min} = \frac{2}{1-0.55} = 4.44 \text{ A}$$

$$I_{in\ max} = \frac{4}{1-0.55} = 8.88 \text{ A}$$

$$\text{Sensing gain} = 0.25 \text{ V/A}$$

$$\text{for } 2 \text{ A}, V = 2 \times 0.25 = 0.5 \text{ V}$$

$$\text{for } 4 \text{ A}, V = 4 \times 0.25 = 1 \text{ V}$$

Now,

$$I = 8.8 \text{ A}, V = 1V, d_{\max} = 0.55, V_{FW} = 0.6, f_s = 25 \text{ kHz}$$

$$nL_m \geq \frac{100 d_{\max} (V + V_{FW})}{I m f_s}$$

$$I_m = \frac{d (V + V_{FW})}{n L_m f_s} \leq 1\% \text{ of } I$$

$$\therefore I_m = 0.01 \times 8.8$$

$$I_m = 0.088 \text{ A}$$

Now,

$$nL_m = \frac{100 \times 0.55 (1 + 0.6) \times 1000}{100 \times 0.088 \times 25 \text{ kHz}}$$

$$nL_m = 400 \text{ mH T}$$

Now, Preparing Chart

	$A_L (\text{nH/Turn}^2)$	$n$	$(I_s)_{\text{rms}} (\text{A})$	$B_m (\text{Wb/m}^2)$
T <sub>10</sub>	765	523	0.012 A	0.012
T <sub>12</sub>	1180	339	0.019	0.0124
T <sub>16</sub>	1482	270	0.0243	—
T <sub>20</sub>	1130	354	0.0186	—
T <sub>27</sub>	1851	217	0.0303	—
T <sub>32</sub>	2429	165	0.0399	—
T <sub>45</sub>	2367	169	0.0389	—

$A_L$  value straight ways gives  $L_m$  value.

$$\text{for } T_{10} \rightarrow n \times 765 = 400 \text{ mH}$$

$$n = \frac{400}{765} = 522.87$$

$$\text{Now, } (I_s)_{\text{rms}} = \frac{I}{n} \sqrt{d_{\max}}$$

$$= \frac{8.88}{522.87} \sqrt{0.55} = 0.012$$

## Calculating $B_m$

$$B_m = \frac{d_{max} \times (V + V_{FBD})}{n f_s A_c}$$

$$= \frac{0.85 (1 + 0.6)}{593 \times 251 \times A_c}$$

for  $A_c$

$$J = I/A$$

Considering  $J = 2.5 \text{ A/mm}^2$

$$A_c = \frac{I_m}{J} = \frac{0.012}{2.5}$$

$$A_c = 4.8 \text{ mm}^2$$

Placing in  $B_m$

$$B_m = \frac{0.5 \times 1.6}{593 \times 251 \times 4.8}$$

$$\boxed{B_m = 0.012 \text{ Wb/m}^2}$$

$\therefore$  choosing T45 / 16gT [1 swg 40]

$$J = 2.5 \text{ A/mm}^2$$

$$A = I/J = \frac{(I_m)_{\text{swg}}}{J} = \frac{0.0389}{2.5} = 15.5 \text{ mm}^2$$

$$A = \frac{\pi d^2}{4}$$

$$d = \sqrt{\frac{(15.5)^2 \times 4}{\pi}}$$

$$\boxed{d = 0.141 \text{ m}}$$

$\therefore$  By seeing 'd' value we see the chart of swg .  $\therefore$  for  $d = 0.141 \text{ m}$  we select swg 40

Now, Power rating of zener diode

With  $n = 169$ ,  $I = 8.8 \text{ A}$ ,  $V = 19.2 \text{ V}$

$$R_s = \frac{V}{I/I_n} = \frac{1}{8.8/169} = 19.252 \Omega$$

$$(I_s)_{\text{avg}} = \frac{I}{n} \sqrt{d} = \frac{8.8}{169} \sqrt{0.55} = 0.038 \text{ A}$$

Power in  $R_s = (I_{\text{avg}})^2 \times R$

$$= (0.038)^2 \times 19.2$$

$$\boxed{P_{R_s} = 0.03 \text{ W}}$$

$\therefore 19.2 \text{ e} / 1/4 \text{ w}$  Resistance  $\rightarrow$  Design.

$$P_g = \frac{\ln I_m^2 R_s}{2} = \frac{2367 n \times (0.088)^2 \times 25 \text{ K}}{2} = 229.12 \text{ eW}$$

$$\boxed{P_g = 229.12 \text{ eW}}$$