


6/5/22

Zero voltage switching clamped voltage (ZVS - CV) Topology

Previous case : peak inverse voltage = $2V_d$.

modification is made to clamp reverse voltage to source voltage.

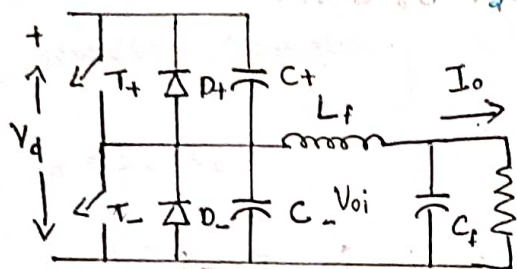
selected such that $f_0 = \frac{1}{2\pi\sqrt{L_f C}}$ is very large compared to switching freq.



① switches turn on and turn off at zero voltage

② Peak voltage across switch is clamped to the i/p DC voltage.

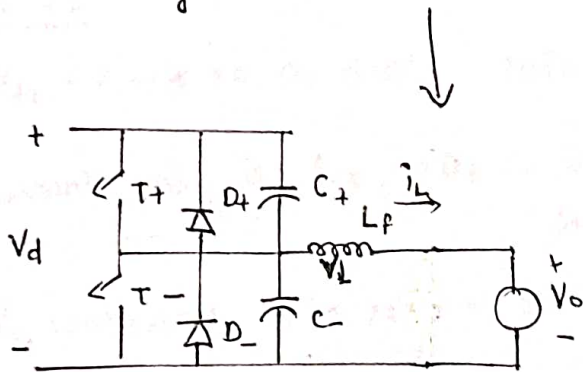③ C_f is considered as very large and hence load is replaced by a voltage source V_o .




Initial condition - before t_0

- ① T_+ is on & T_- is off
- ② $V_L = V_d - V_o$ (constant)
- ③ D_+ & D_- reverse biased.
- ④ $V_{C+} = 0$ & $V_{C-} = V_d = V_{oi}$
- ⑤ $V_{T+} = 0$

At $t = t_0$, T_+ is turned off at zero voltage due to V_{C+} .


Voltage across

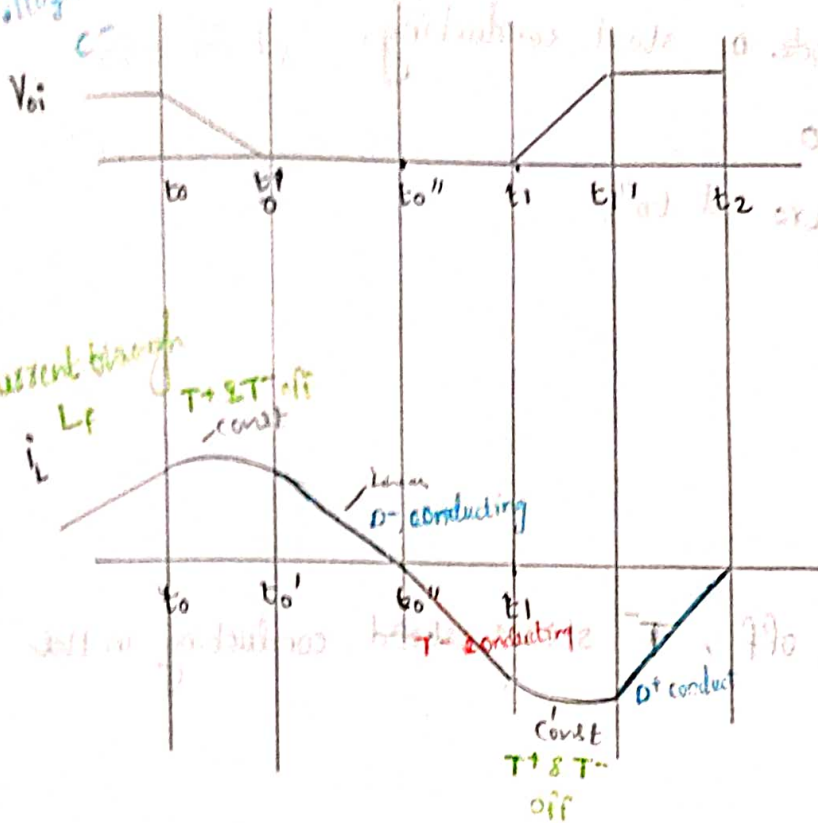


$t_0 \rightarrow t_0'$

① T^+ , T^- , D^+ and D^- are in off state.

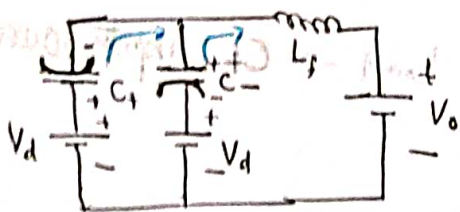② Since C_- has an eqv voltage of V_d equivalent circuit can be redrawn as



Theremin equivalent

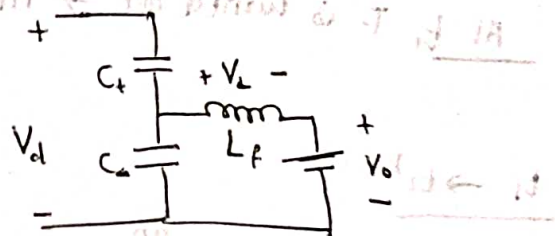

$$C = C_+ + C_- = \frac{1}{2}C + \frac{1}{2}C = C$$

③ Inductance current $i_L = I_o = i_{C+} + i_{C-}$

④ V_{C+} changes linearly from 0 to V_d .

⑤ V_{C-} decreases linearly from V_d to zero.

$$V_{C-} = V_{oi} = V_d - V_{C+}$$

$$⑥ \quad C_+ = C_- \quad \} \quad i_{C+} = i_{C-} = \frac{i_L}{2}$$

At t_0' : $V_{oi} = 0$, so diode D_- start conducting.

$$① \quad V_{C-} = V_{oi} = V_d = 0$$

② i_L decreases linearly to zero at t_0'' .

At :

At t_0'' when D_- becomes off, T_- starts ~~start~~ conducting in the -ve direction.

$t_0'' \rightarrow t_1$

i_L flows through T_- & $V_L = -V_o$

At t_1 T_- is turned off \rightarrow maximum voltage that comes across T_+ is V_d .

$t_1 \rightarrow t_1'$

T_+ and T_- are off

Negative i_L flows through C

C_+ discharges from V_d to 0 through Load $\rightarrow C_+$, input source.

C_- gets charged from 0 to V_d .

$t_1' \rightarrow t_2$

When V_{C+} is zero, D_+ conducts negative i_L

$V_L = V_d - V_o$ is +ve ($V_d > V_o$ - current rises)

$\frac{di_L}{dt}$ is +ve.

T_+ ~~starts~~ is gated while D_+ is conducting

T_+ starts conducting when D_+ become off when i_L is reduced to zero at t_2 .