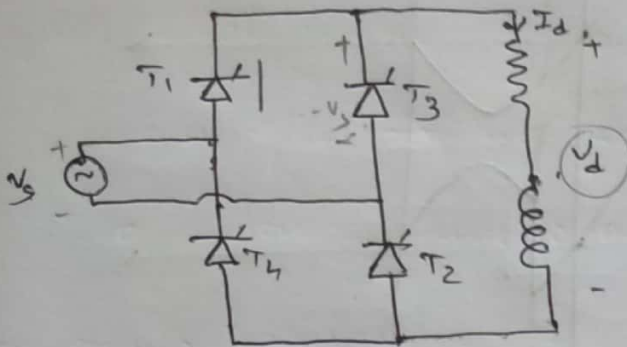


* for RL load

② continuous conduction mode



$\omega t < \alpha$, T_3 & T_4 are conducting

At $\omega t = \alpha$, $i_d = I_1 (\neq 0)$

$$V_d = -V_s$$

$$I_s = -I_d$$

$$V_{T_1} = V_s$$

$\omega t > \alpha$, T_3 & T_4 are

($\alpha \rightarrow \pi + \alpha$)

line commutated

T_1 & T_2 are ON

$$V_d = V_s = R i_d(\omega t) + L \frac{di_d(\omega t)}{dt}$$

$$\sqrt{2} V_s \sin \omega t = R i_d + L \frac{di_d}{dt}$$

$$\text{at } \omega t = \alpha, i_d = +I_1$$

$$R I_1 + L \left. \frac{di_d}{dt} \right|_{\omega t = \alpha} = \sqrt{2} V_s \sin \alpha$$


$$i_s = i_d$$

$$i_d = \frac{V_m}{Z} \sin(\omega t - \theta) + A_1 e^{-t/\tau}$$

$$\text{at } \omega t = \alpha, i_d = I_1$$


$$A_1 = \left(I_1 - \frac{V_m}{Z} \sin(\alpha - \theta) \right) e^{+\alpha/\tau}$$
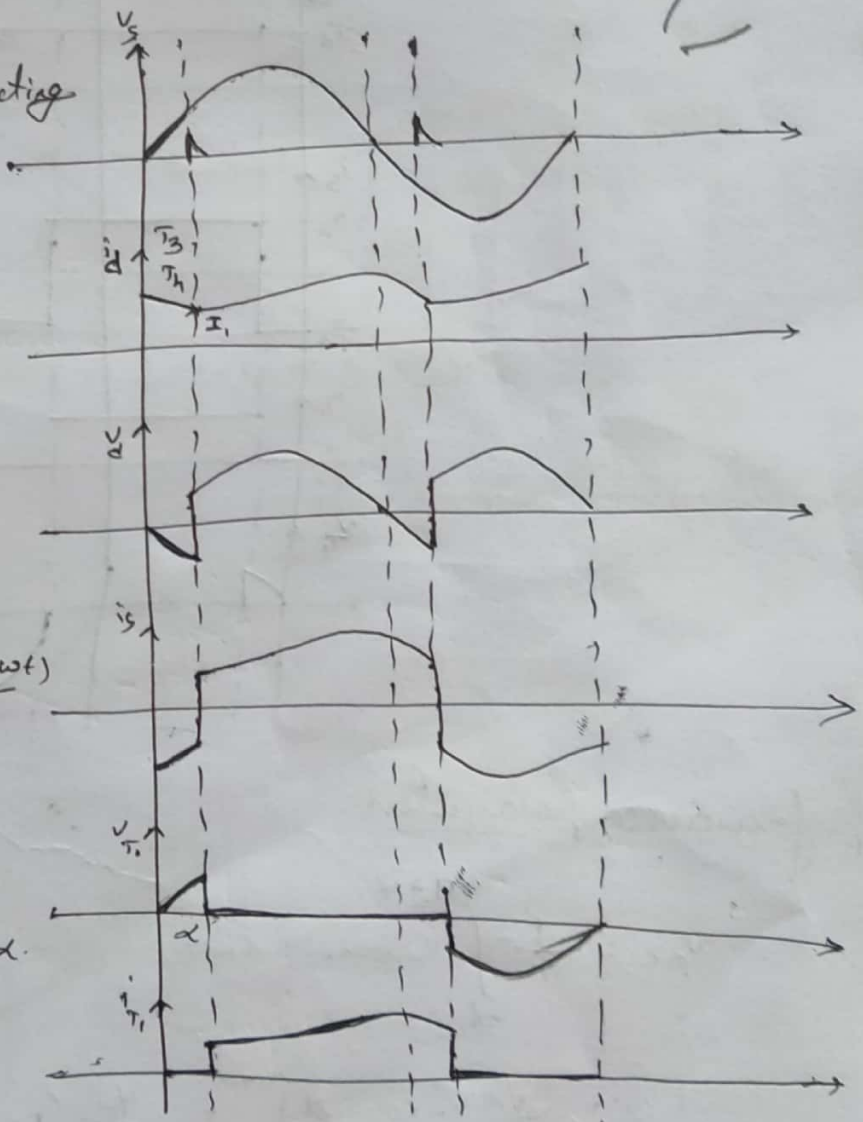
$$i_d = \frac{V_m}{Z} \sin(\omega t - \theta) + \left(I_1 - \frac{V_m}{Z} \sin(\alpha - \theta) \right) e^{\frac{\alpha}{\omega \tau}}$$



③ load current is constant

load inductance
is very high

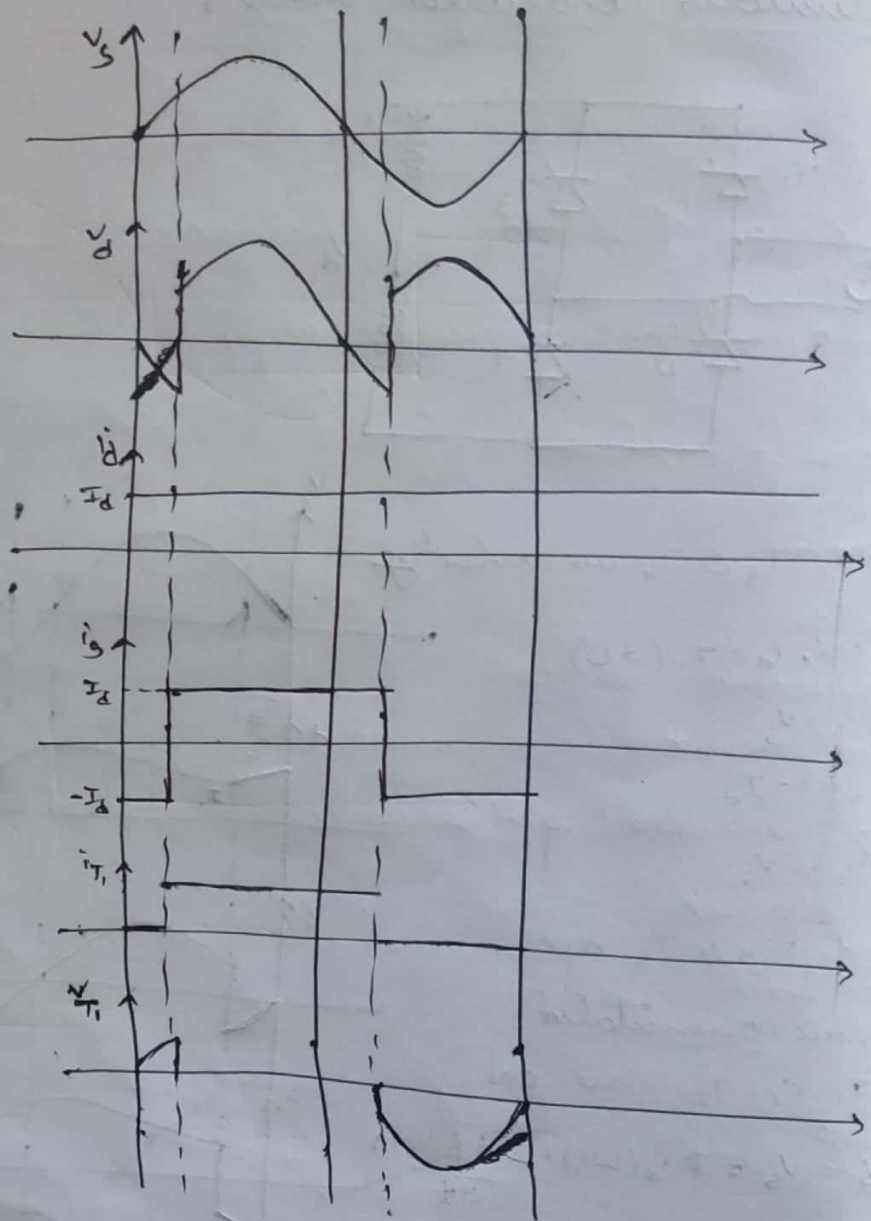

performance parameters:

$$V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, d\omega t$$

$$V_{dc} = \frac{V_m}{\pi} (-\cos \omega t)_{\alpha}^{\pi+\alpha} = \frac{V_m}{\pi} (1 - \cos \alpha) = \frac{V_m}{\pi} (\cos(\pi+\alpha) - \cos \alpha)$$

($\cos \alpha = 1$)
 $I_d = \frac{2V_m}{\pi R}$
 $\rightarrow \boxed{I_{dc} = \frac{2V_m}{\pi R} (\cos \alpha)}$

$$\boxed{V_{dc} = \frac{2V_m}{\pi} \cos \alpha}$$

$$V_{rms} = \left[\frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m^2 \sin^2 \omega t \, d\omega t \right]^{1/2}$$

$$= \frac{V_m}{\sqrt{2}} = V_s$$

$$\text{Average power} = V_{\text{avg}} I_d = \frac{2 V_m I_d \cos \alpha}{\pi}$$

Ripple frequency of o/p voltage = 2 times supply frequency

$$\text{voltage RF} = \sqrt{\frac{V_{\text{RMS}}^2 - V_{\text{avg}}^2}{V_{\text{RMS}}^2}}$$


$$i_s(t) = a_0 + \sum_{n=1,2,3}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t$$

$$a_0 = a_n = 0$$



$$b_n = \frac{2}{2\pi} \left[\int_{\alpha}^{\pi+\alpha} I_d \sin \omega t \sin n\omega t dt + \int_{\pi+\alpha}^{2\pi+\alpha} I_d \sin \omega t \sin n\omega t dt \right]$$

$$b_n = \frac{I_d}{2\pi} \left[\int_{\alpha}^{\pi+\alpha} (\sin(1-n)\omega t + \sin(1+n)\omega t) dt + \int_{\pi+\alpha}^{2\pi+\alpha} (\sin(1-n)\omega t + \sin(1+n)\omega t) dt \right]$$
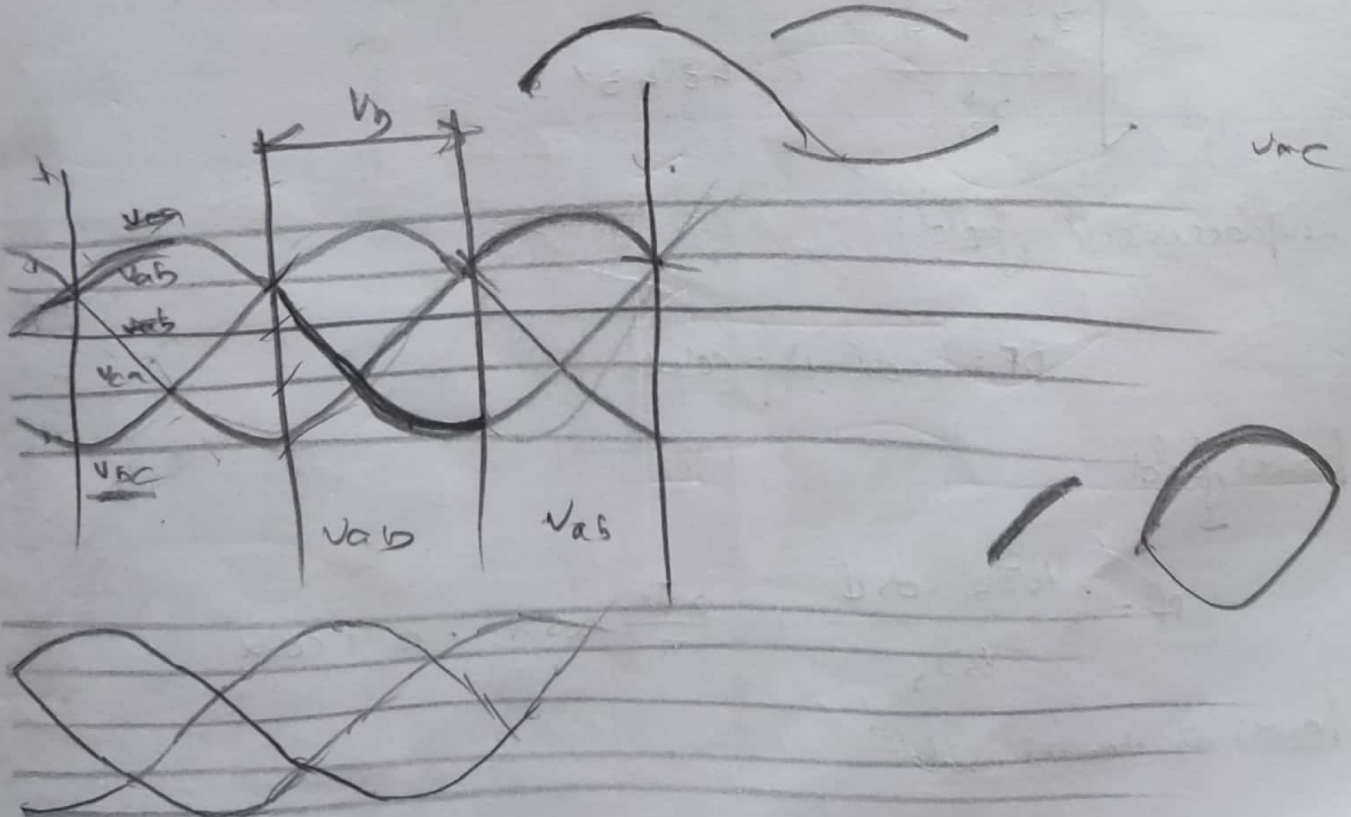
$$\int_{\pi+\alpha}^{2\pi+\alpha} (\sin(1-n)\omega t + \sin(1+n)\omega t) dt$$


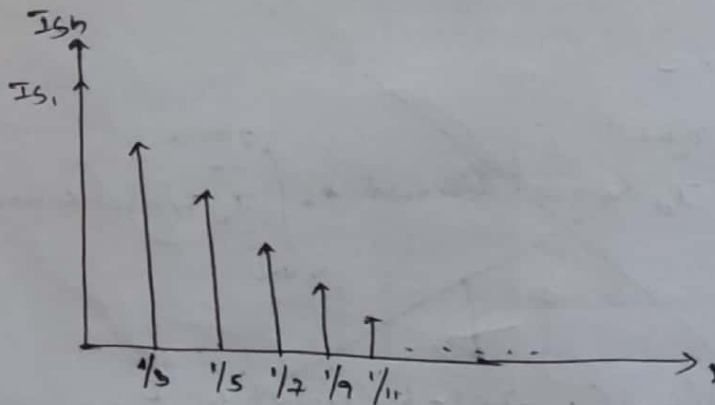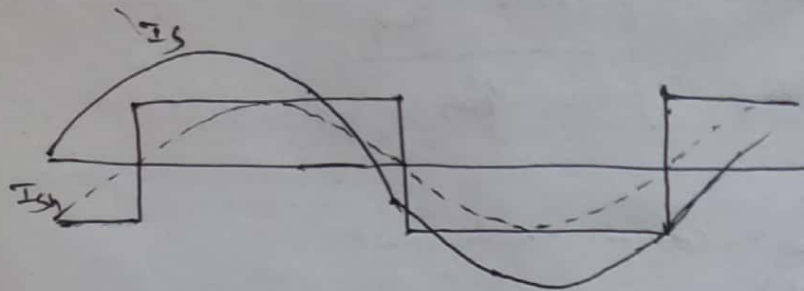
$$I_{sh} = \begin{cases} 0 & \text{for even } h \\ \frac{I_{s1}}{h} & \text{for odd } h \end{cases}$$



* Total harmonic distortion: (THD)

$$\sqrt{\frac{I_s^2 - I_{s1}^2}{I_{s1}^2}} = 48.43\%$$

* Displacement factor:

$$DF = \cos(-\alpha) = \cos \alpha$$

* power factor:

$$PF = \frac{V_s I_{s1} \cos \phi}{V_s I_s} = \frac{2\sqrt{2}}{\pi} \cos \alpha = 0.9 \cos \alpha$$

* power at source side:

$$\text{Total apparent power} = V_s I_s$$



$$\text{Active power } P = V_s I_{s1} \cos \phi$$

* fundamental frequency current results in fundamental reactive power



$$Q_1 = V_s I_{s1} \sin \phi_1 = V_s I_{s1} \sin \alpha$$

* fundamental frequency apparent power:
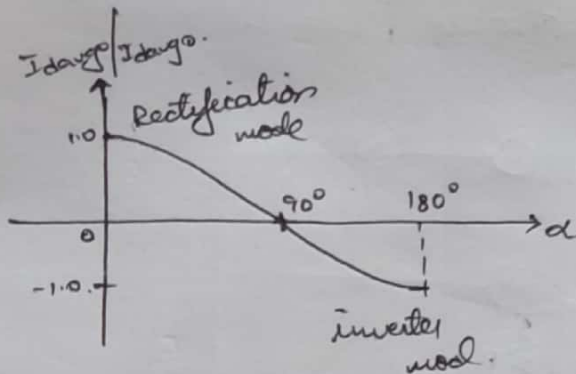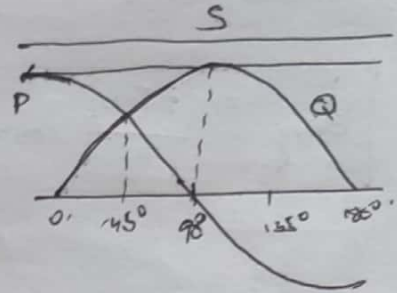
$$S_1 = V_s I_{s1} = \sqrt{P^2 + Q_1^2}$$



* Effect of source inductance (L_s):

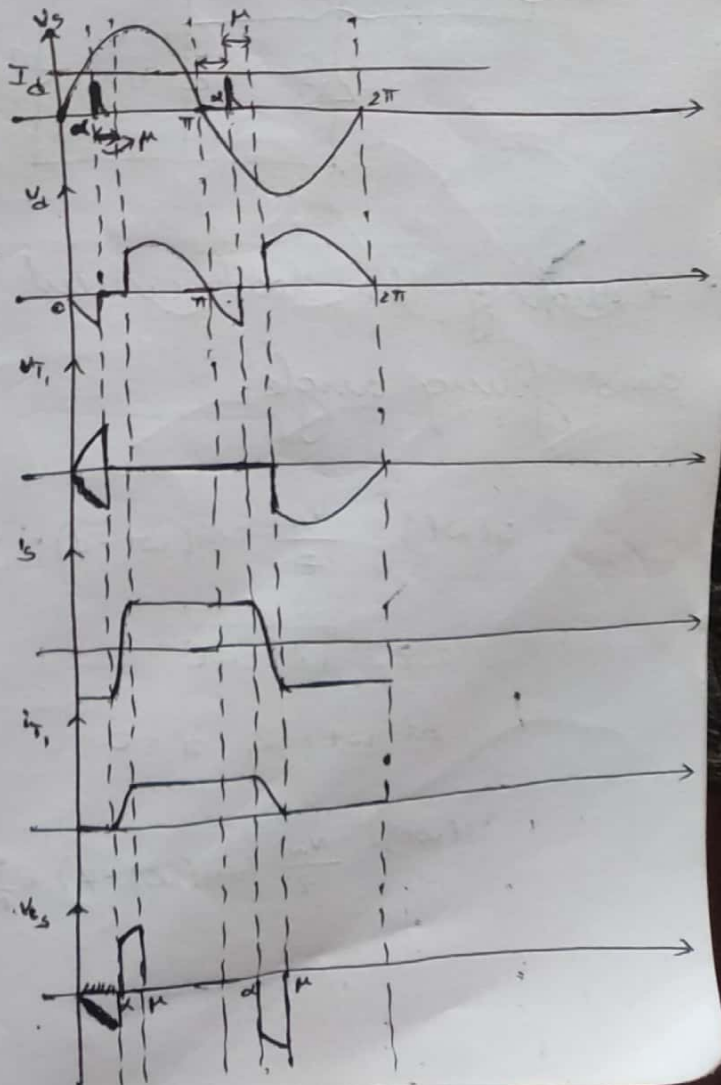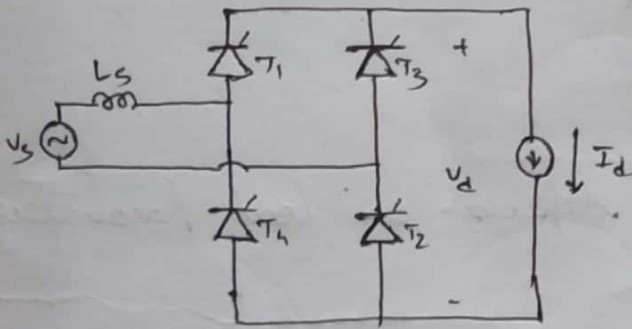

$\alpha \rightarrow \mu$

$$V_s = V_{Ls}$$

$$V_m \sin \omega t = L_s \frac{di_s}{dt}$$

$$V_m \sin \omega t = \omega L_s \frac{di_s}{d\omega t}$$

$$\int_{\alpha}^{\alpha+\mu} \sin \omega t d\omega t = \int_{-I_d}^{I_d} \frac{\omega L_s di_s}{V_m}$$

$$[-\cos \omega t]_{\alpha}^{\alpha+\mu} = \frac{2 I_d \omega L_s}{V_m}$$

$$\cos \alpha - \cos(\alpha+\mu) = \frac{2 I_d \omega L_s}{V_m}$$


$$\cos(\alpha + \mu) = \cos \alpha - \frac{2 I_D \omega L_s}{V_m}$$

$$V_{\text{avg}} = \frac{1}{\pi} \int_{\alpha + \mu}^{\pi + \alpha} V_m \sin \omega t \, d\omega t$$

$$= \frac{V_m}{\pi} [\cos(\alpha + \mu) - \cos(\pi + \alpha)]$$

$$V_{\text{avg}} = \frac{2\sqrt{2}V_s}{\pi} \cos \alpha - \frac{2\omega L_s I_D}{\pi}$$

* practical thyristor converters:

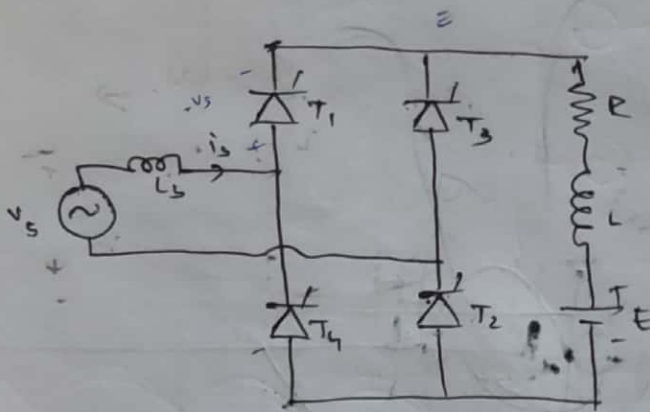

* shape of the load current depends on load parameters and firing angle.

$$i_L(\omega t) = \frac{V_m}{Z} \sin(\omega t - \phi) + \frac{E}{R} + K e^{-\frac{R}{L}t}$$


$$Z = \sqrt{R^2 + \omega L^2}$$

$$\text{at } \omega t = \alpha, i_L = 0$$


$$i_L(\omega t) = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + \left[\frac{E}{R} - \frac{V_m}{Z} \sin(\omega t - \phi) \right] e^{\frac{R}{\omega L}} e^{-\frac{R}{L}t}$$

→ Discontinuous mode:
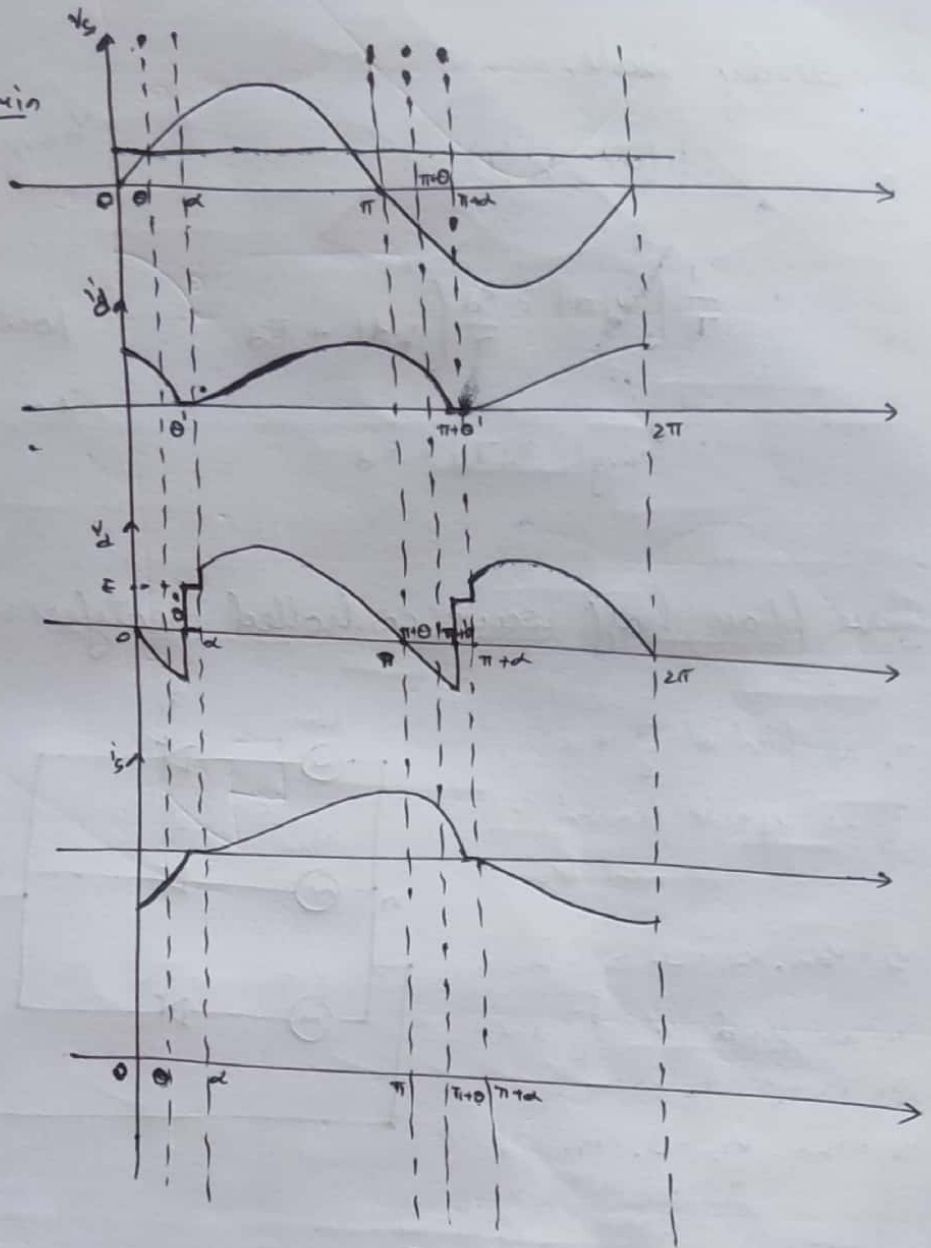
$$V_{avg} = \frac{2\sqrt{2}V_s}{\pi} \cos \alpha - \frac{2\omega L_s I_{dmin}}{\pi}$$



→ continuous mode:

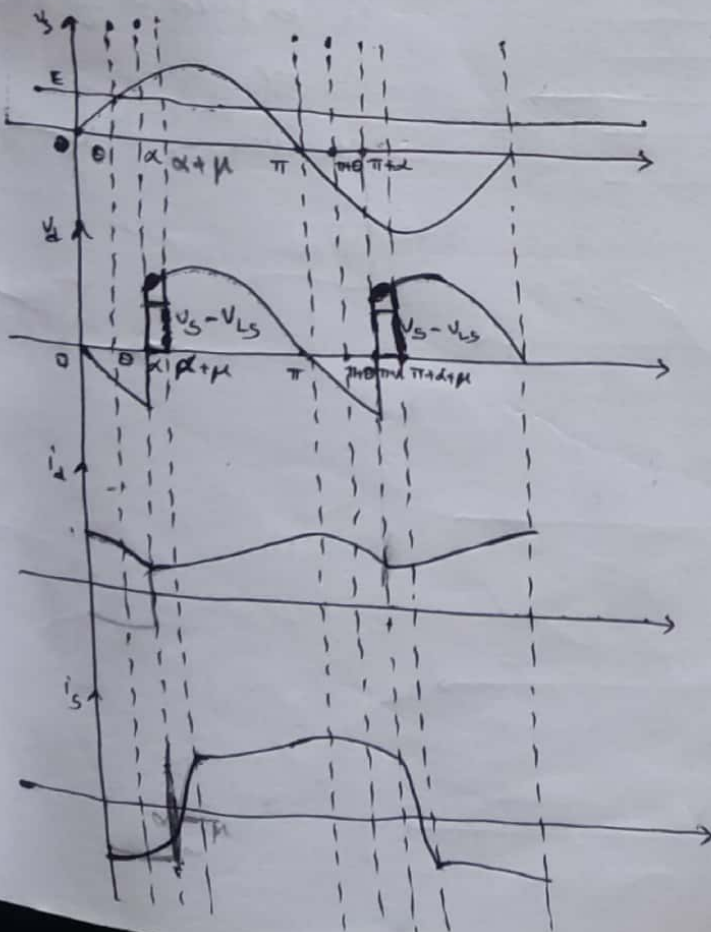

- * Back emf is low or torque is very high, then the current will be continuous
- * armature inductance is large

$$V_{avg} = \frac{2V_m}{\pi} \cos \alpha - \frac{2\omega L_s I_{dmin}}{\pi}$$

I_{dmin} is at $\omega t = \alpha$

$$V_d = R_d i_d + L_d \frac{di_d}{dt} + E_d$$

$$\frac{1}{T} \int_0^T V_d dt = \frac{R_d}{T} \int_0^T i_d dt + \frac{L_d}{T} \int_0^T \frac{di_d}{dt} dt + E_d$$

In steady state, $i_d(0) = i_d(T)$

$V_{d,avg}$ can be controlled by ' α '

$$\therefore \frac{1}{T} \int_0^T v_d dt = \frac{\delta_d}{T} \int_0^T i_d dt + E_d$$

\therefore power delivered to load can be controlled by ' α '.

$$\therefore V_{d,avg} = \delta_d I_d + E_d$$

* Three phase half wave controlled rectifier:

T_1 is fired at $\frac{\pi}{6} + \alpha$


T_3 is reverse biased & turned off

$$v_d = v_{an}, v_{T1} = 0, i_{T1} = i_d$$

T_2 is fired at $\frac{5\pi}{6} + \alpha$

T_1 is off, T_2 is ON

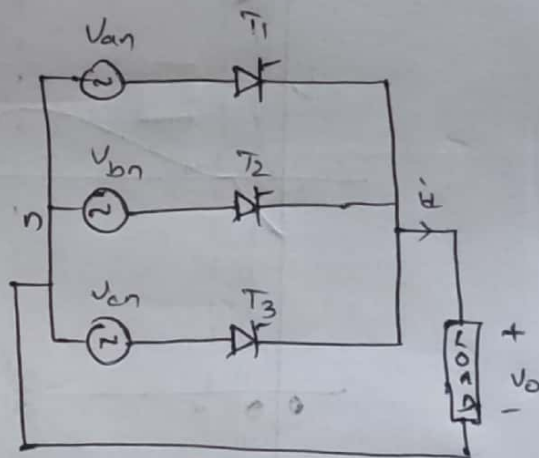
$$v_d = v_{bn}, v_{T2} = 0, i_{T2} = i_d$$



T_3 is fired at $\frac{7\pi}{6} + \alpha$

T_2 off, T_3 ON
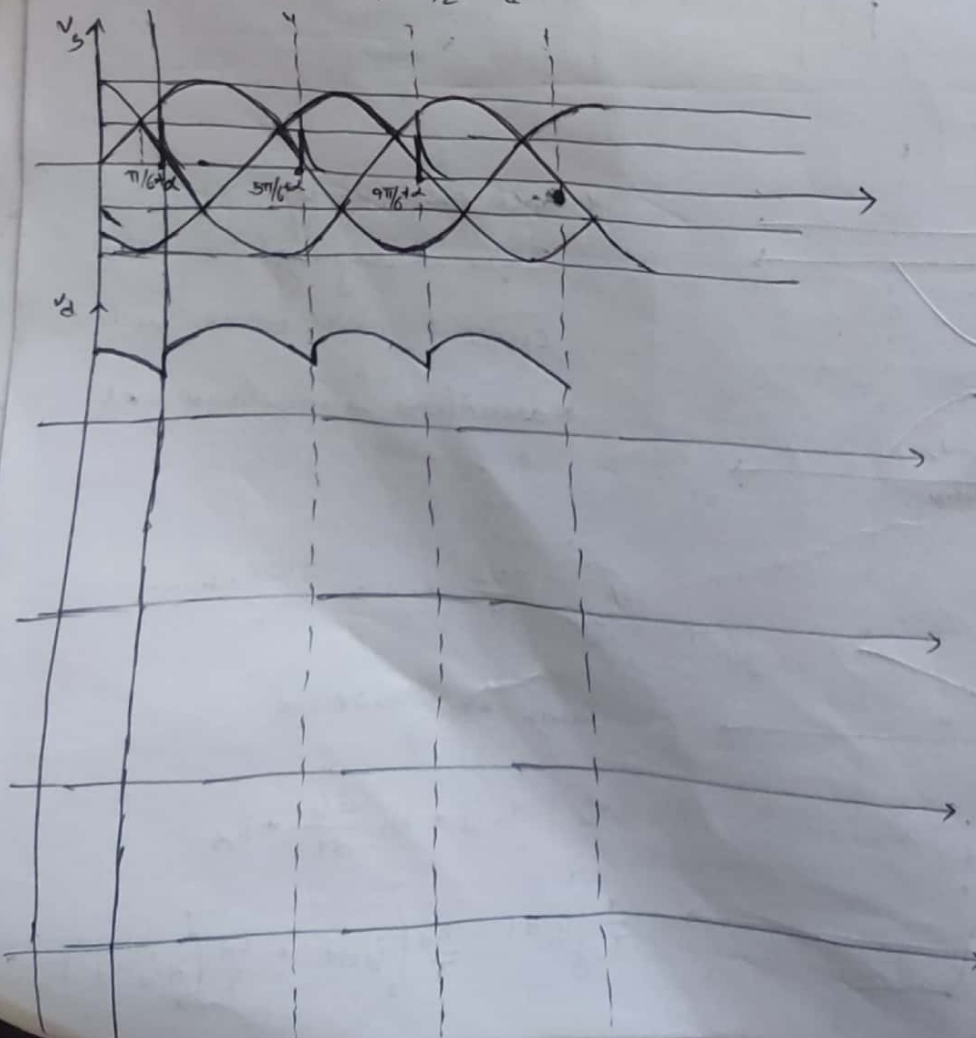
$$v_d = v_{cn}, v_{T3} = 0, i_{T3} = i_d$$



for continuous current:

$$V_{avg} = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{\pi/6+\alpha+2\pi} v_m \sin \omega t d\omega t = \frac{3V_m}{2\pi} \left[\cos\left(\frac{\pi}{6} + \alpha\right) - \cos\left(\frac{3\pi}{6} + \alpha\right) \right]$$


$$= \frac{3V_m}{2\pi} \left[\cos\left(\frac{\pi}{6} + \alpha\right) - \cos\left(\pi - \frac{\pi}{6} + \alpha\right) \right]$$

$$= \frac{3V_m}{2\pi} \left[2 \cos\left(\frac{\pi}{6} + \alpha\right) \right]$$

$$= \frac{3V_m}{\pi} \left[\cos\left(\frac{\pi}{6} + \alpha\right) \right]$$


$$= \frac{3\sqrt{3}V_L}{\sqrt{2}\pi} \cos \alpha = \frac{3V_{LL}}{\sqrt{2}\pi} \cos \alpha$$

* Three phase full control rectifier

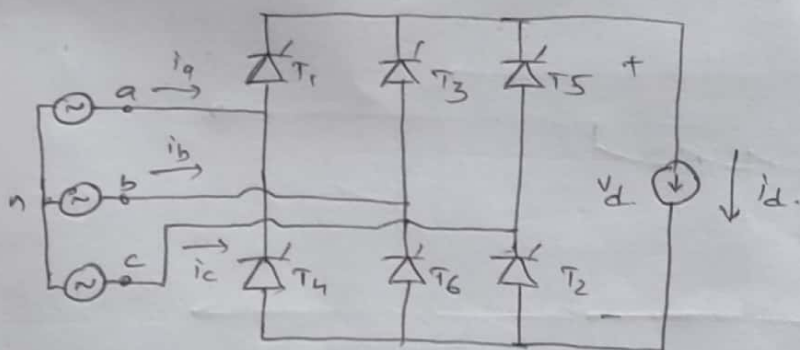

* constant load current:

Interval	Devices	$-V_d$	i_a	i_b	i_c
A → B	T_1, T_6	V_{ab}	$+I_d$	$-I_d$	0
B → C	T_1, T_2	V_{ac}	$+I_d$	0	$-I_d$
C → D	T_2, T_3	V_{bc}	0	$+I_d$	$-I_d$
D → E	T_3, T_4	V_{ba}	$-I_d$	$+I_d$	0
E → F	T_4, T_5	V_{ca}	$-I_d$	0	$+I_d$
F → A	T_5, T_6	V_{cb}	0	$-I_d$	$+I_d$

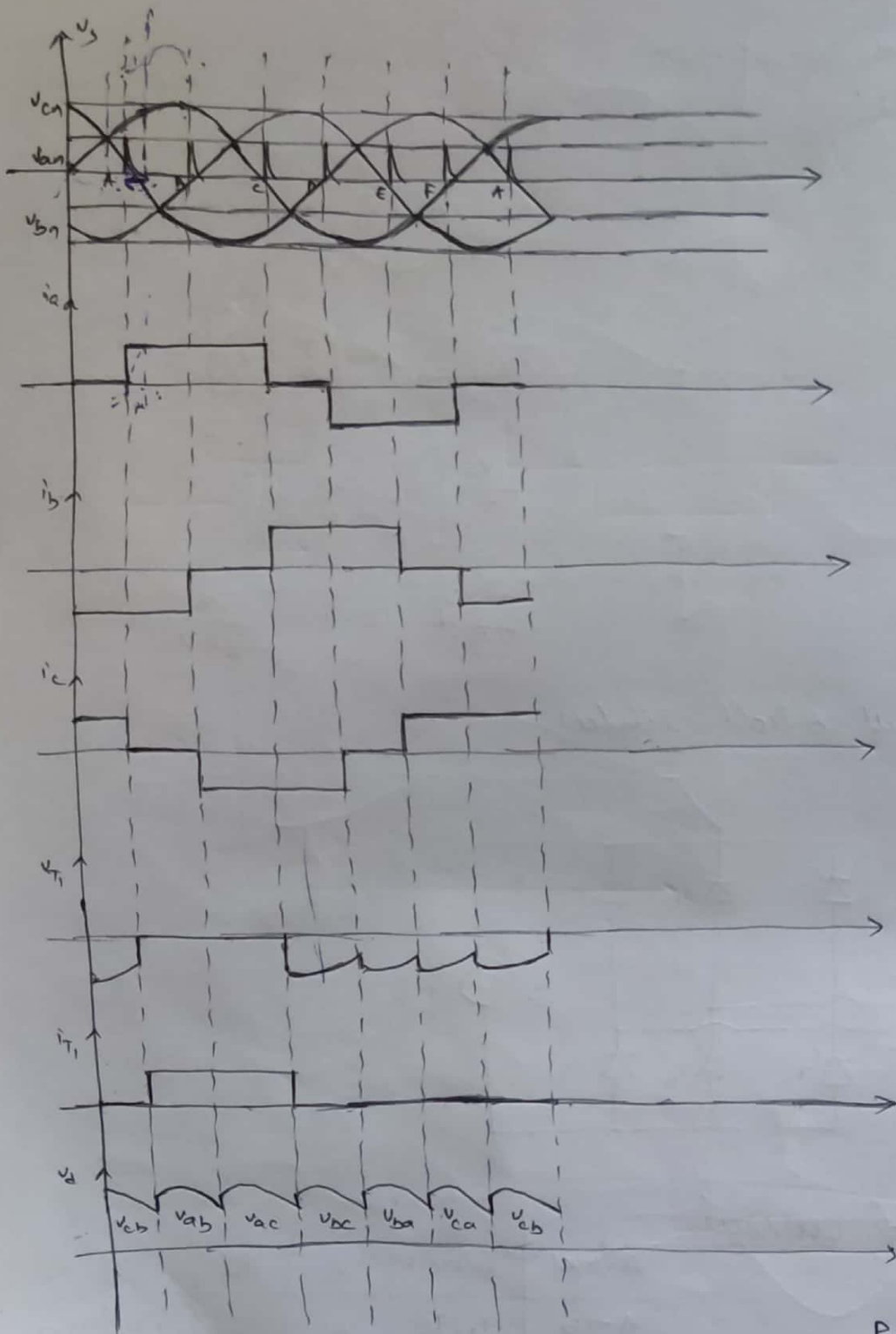

$$PIV = \sqrt{3} V_{m1}$$

$$\begin{aligned}
 V_{davg} &= \frac{3}{\pi} \int_{\pi/6+\alpha}^{\pi/2+\alpha} V_m \sin \omega t \, d\omega t - \int_{\pi/6+\alpha}^{\pi/2+\alpha} V_m \sin(\omega t - 120^\circ) \, d\omega t \\
 &= \frac{3V_m}{\pi} \left[\cos\left(\frac{\pi}{6} + \alpha\right) - \cos\left(\frac{\pi}{2} + \alpha\right) \right] - \left[\cos\left(\frac{\pi}{6} + \alpha - 120^\circ\right) - \cos\left(\frac{\pi}{2} + \alpha - 120^\circ\right) \right] \\
 &= \frac{3V_m}{\pi} \left[\cos\left(\frac{\pi}{6} + \alpha\right) + \sin \alpha \right] - \left[\cos(\alpha - 90^\circ) - \cos(\alpha - 30^\circ) \right] \\
 &= \frac{3V_m}{\pi} \left[\cos \frac{\pi}{6} \cos \alpha - \sin \frac{\pi}{6} \sin \alpha + \sin \alpha \right] = \frac{3V_m}{\pi} \left[\frac{\sqrt{3} \cos \alpha}{2} + \frac{\sin \alpha}{2} \right] \\
 &\quad - \left[\cos(90^\circ - \alpha) - \cos(30^\circ - \alpha) \right] \\
 &\quad - \sin \alpha + \cos(30^\circ - \alpha)
 \end{aligned}$$

$$= \frac{3\sqrt{6} V_s}{\pi} \cos \alpha = 1.35 V_{LL} \cos \alpha$$

* Average output power:

$$P_{avg} = V_{davg} \times I_{davg} = 1.35 V_{LL} \times I_d \cos \alpha$$

* AC side current i_a :

$$= \sum_{n=1}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t$$

$$i_a = a_1 \cos \omega t + b_1 \sin \omega t$$

$$a_1 = \frac{1}{\pi} \left[\int_{\pi/6+\alpha}^{\frac{5\pi}{6}+\alpha} I_d \cos \omega t d\omega t - \int_{\frac{7\pi}{6}+\alpha}^{\frac{11\pi}{6}+\alpha} I_d \cos \omega t d\omega t \right]$$

$$a_1 = \frac{I_d}{\pi} \left[\sin\left(\frac{5\pi}{6}+\alpha\right) - \sin\left(\frac{\pi}{6}+\alpha\right) - \sin\left(\frac{11\pi}{6}+\alpha\right) + \sin\left(\frac{7\pi}{6}+\alpha\right) \right]$$

$$a_1 = \frac{I_d}{\pi} \left[\sin\left(\pi - \frac{\pi}{6} + \alpha\right) - \sin\left(\frac{\pi}{6} + \alpha\right) - \sin\left(2\pi - \frac{\pi}{6} + \alpha\right) + \sin\left(\pi + \frac{\pi}{6} + \alpha\right) \right]$$

$$a_1 = \frac{-2\sqrt{3} I_d}{\pi} \sin \alpha$$

$$b_1 = \frac{1}{\pi} \left[\int_{\pi/6+\alpha}^{\frac{5\pi}{6}+\alpha} I_d \sin \omega t d\omega t - \int_{\frac{7\pi}{6}+\alpha}^{\frac{11\pi}{6}+\alpha} I_d \sin \omega t d\omega t \right]$$

$$b_1 = \frac{I_d}{\pi} \left[\cos\left(\frac{\pi}{6}+\alpha\right) - \cos\left(\frac{5\pi}{6}+\alpha\right) - \cos\left(\frac{7\pi}{6}+\alpha\right) + \cos\left(\frac{11\pi}{6}+\alpha\right) \right]$$

$$b_1 = \frac{I_d}{\pi} \left[\cos\left(\frac{\pi}{6}+\alpha\right) - \cos\left(\pi - \frac{\pi}{6} + \alpha\right) - \cos\left(\pi + \frac{\pi}{6} + \alpha\right) + \cos\left(2\pi - \frac{\pi}{6} + \alpha\right) \right]$$

$$b_1 = 0$$



$$i_a = \frac{2\sqrt{3} I_d}{\pi} \sin(\omega t - \alpha)$$

* RMS value of fundamental component is

$$i_{a1(rms)} = \frac{\frac{2\sqrt{3} I_d}{\pi}}{\sqrt{2}} = \frac{\sqrt{6} I_d}{\pi} = 0.78 I_d$$

* RMS value of harmonic components $I_{ah} = \frac{I_{ar}}{h}$

$$h = 6n \pm 1, (n = 1, 2, 3, \dots)$$

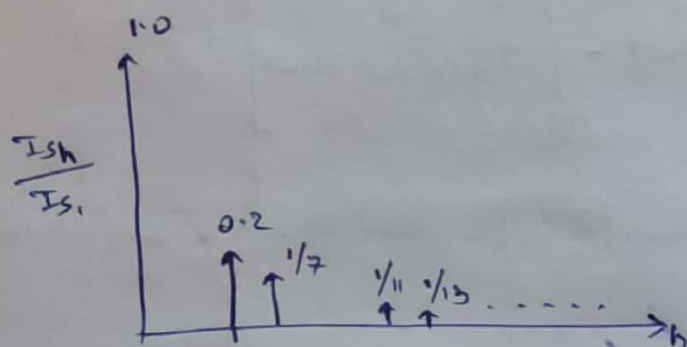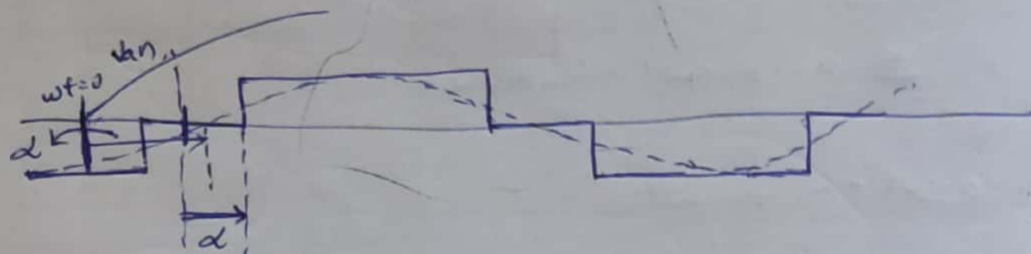

* Total RMS value of phase current $I_a =$



$$\sqrt{\frac{2}{3}} I_d = 0.816 I_d$$

$$\begin{aligned} * THD &= \sqrt{\frac{I_s^2 - I_{s1}^2}{I_{s1}^2}} = \sqrt{\frac{(0.816)^2 I_d^2 - (0.78)^2 I_d^2}{(0.78)^2 I_d^2}} \\ &= 31.08\% \end{aligned}$$

$$* DPF = \cos \phi_1 = \cos \alpha$$

$$* \text{power factor} = \frac{V_s I_{s1} \cos \phi}{V_s I_s} = \frac{I_a \cos \phi}{I_a} = \frac{3}{\pi} \cos \alpha = 0.96 \cos \alpha$$

* Effect of source inductance:

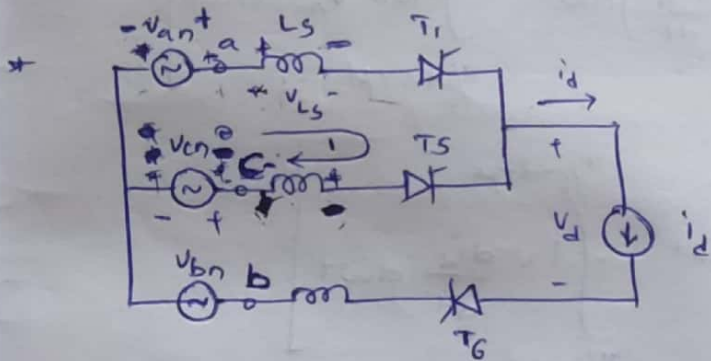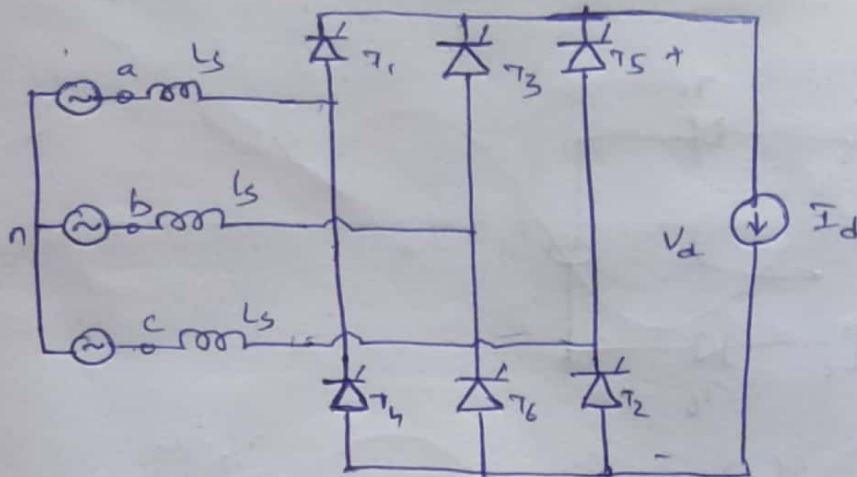

$$\pi/6 + \alpha \longrightarrow \pi/6 + \alpha + \mu$$

T_1, T_5, T_6 conducts

KVL Loop 1:

$$V_{an} - V_{LS} - V_{LS} - V_{cn} = 0$$

$$V_{ac} - 2V_{LS} = 0$$

$$V_{ac} = \sqrt{2}V_s \sin(\omega t) - \sqrt{2}V_s \sin(\omega t + 120)$$

$$V_{ac} - L_s \frac{di_a}{dt} - L_s \frac{di_c}{dt} = 0 \quad \sqrt{2}V_s \sin \omega t - \sqrt{2}V_s \sin(\omega t + 120) = 2L_s \frac{di}{dt}$$

$$V_{ac} - 2L_s \frac{di_a}{dt} = 0$$

$$V_{ac} = 2L_s \frac{di_a}{dt}$$

$$\int_{\pi/6 + \alpha}^{\pi/6 + \alpha + \mu} \sqrt{2}V_s \sin \omega t - \sqrt{2}V_s \sin(\omega t + 120) d\omega t = 2\omega L_s \int_{\pi/6 + \alpha}^{\pi/6 + \alpha + \mu} di$$


$$\frac{\sqrt{2}V_s}{2\omega L_s} \left[\cos\left(\frac{\pi}{6} + \alpha\right) - \cos\left(\frac{\pi}{6} + \alpha + \mu\right) + \cos\left(\frac{\pi}{6} + \alpha + \mu + 120\right) - \cos\left(\frac{\pi}{6} + \alpha + 120\right) \right]$$

$$= I_d$$

$$I_d = \frac{\sqrt{6}V_s}{2\omega L_s} (\cos \alpha - \cos(\mu + \alpha))$$

$$\cos(\alpha + \mu) = \cos \alpha - \frac{\omega L_s I_d}{V_{LL}}$$
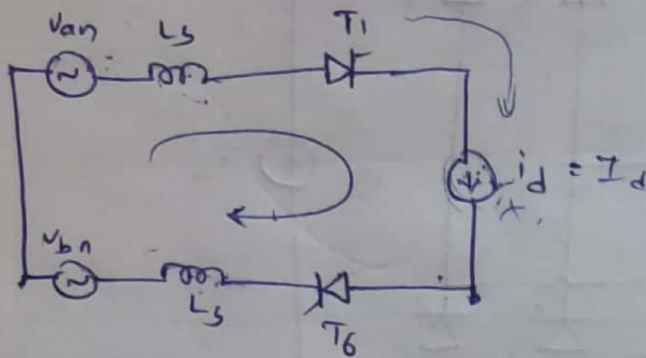
$$+ \frac{\pi}{6} + \alpha + \mu \rightarrow \frac{\pi}{2} + \alpha$$



$$V_{avg} = \frac{3}{\pi} \left[\int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{6} + \alpha + \mu} (v_{an} - v_{bn} - L_s \frac{di_d}{dt}) d\omega t + \int_{\frac{\pi}{6} + \alpha + \mu}^{\frac{\pi}{2} + \alpha} (v_{an} - v_{bn}) d\omega t \right]$$

$$V_{avg} = \frac{3}{\pi} \left[\int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} (v_{an} - v_{bn}) d\omega t - \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{6} + \alpha + \mu} L_s \frac{di_d}{dt} d\omega t \right]$$


$$V_{avg} = \left[\frac{3V_m}{\pi} \left[\cos\left(\frac{\pi}{6} + \alpha\right) - \cos\left(\frac{\pi}{2} + \alpha\right) + \cos\left(\frac{\pi}{6} + \alpha - 120^\circ\right) - \cos\left(\frac{\pi}{6} + \alpha - 120^\circ\right) \right] - \omega L_s \int_0^{I_d} di_d \right]$$


$$V_{avg} = \left[1.35 V_{LL} \cos \alpha - \frac{3\omega L_s}{\pi} I_d \right]$$

* Single quadrant converters - Half controlled converters

① symmetrical connection:

load current is constant
 I_d

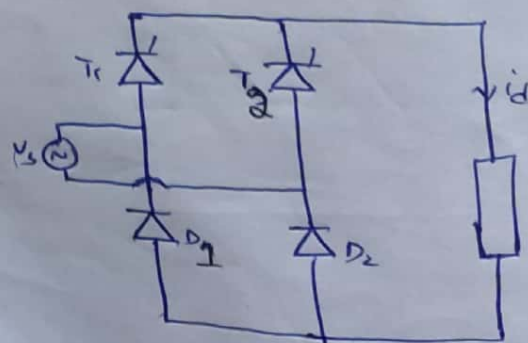

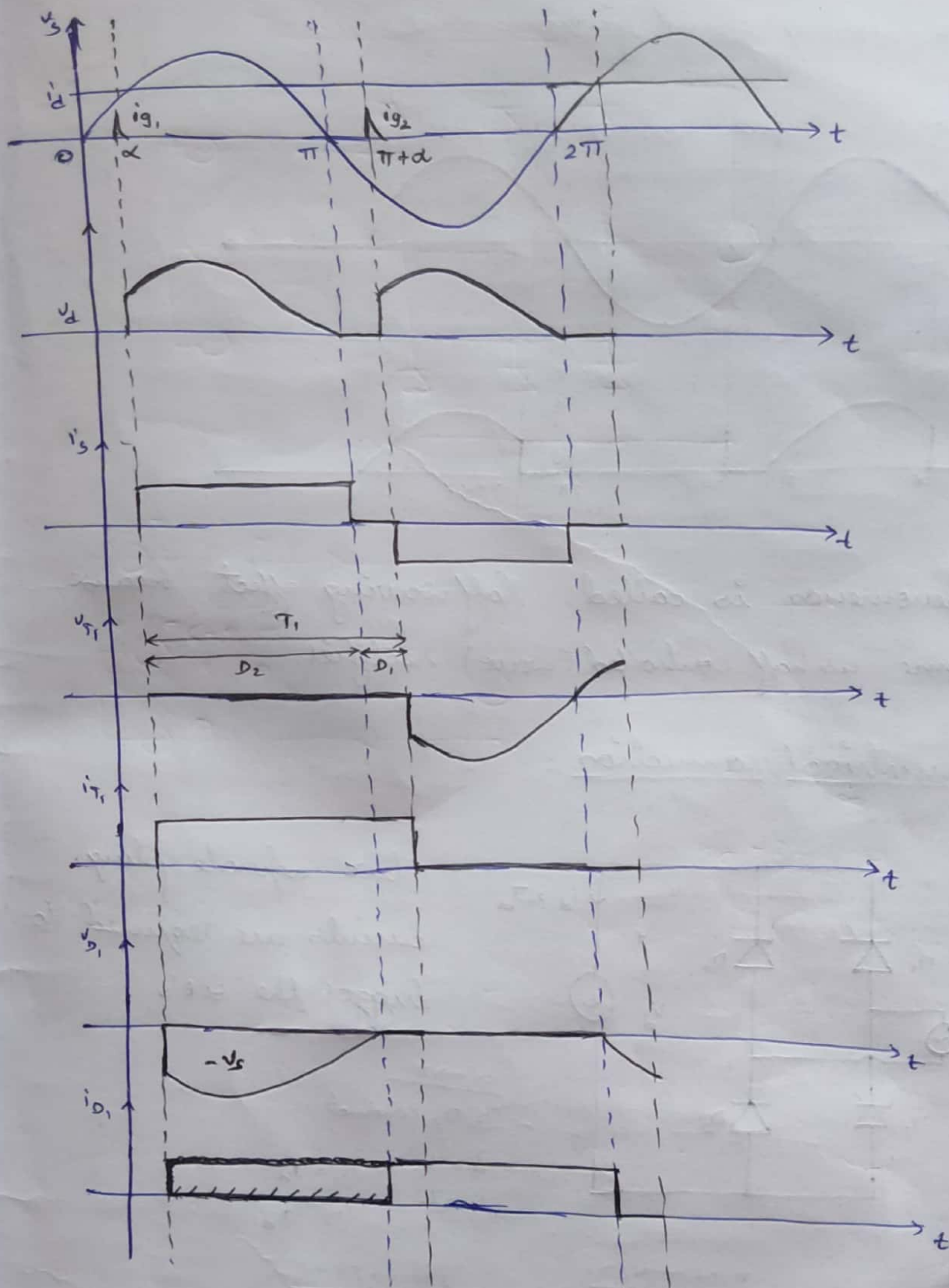

$\alpha \rightarrow \pi$

T_1, D_2 conduct

$$v_d = v_s$$

$$i_s = +i_d$$

$$i_{T1} = i_d, i_{T2} = 0, i_{D1} = 0$$

$$i_{D2} = i_d$$

$\pi \rightarrow \pi + \alpha$

T_1, D_1 conduct

$$v_d = 0$$

$$i_s = 0$$

$$v_{T1} = 0$$

$$i_{T1} = i_d$$

$$v_{D1} = 0$$

$$i_{D1} = i_d$$

$\pi + \alpha \rightarrow 2\pi$

T_2, D_1 conduct

$$v_d = -v_s$$

$$i_s = -i_d$$

$$v_{T1} = v_s$$

$$i_{T1} = 0$$

$$v_{D1} = 0$$

$$i_{D1} = i_d$$

$2\pi \rightarrow 2\pi + \alpha$

T_2, D_2 conduct

$$v_d = 0$$

$$i_s = 0$$


$$v_{T1} = v_s$$

$$i_{T1} = 0$$

$$v_{D1} = v_s$$


$$i_{D1} = 0$$

* If i_{g2} is missing or not given

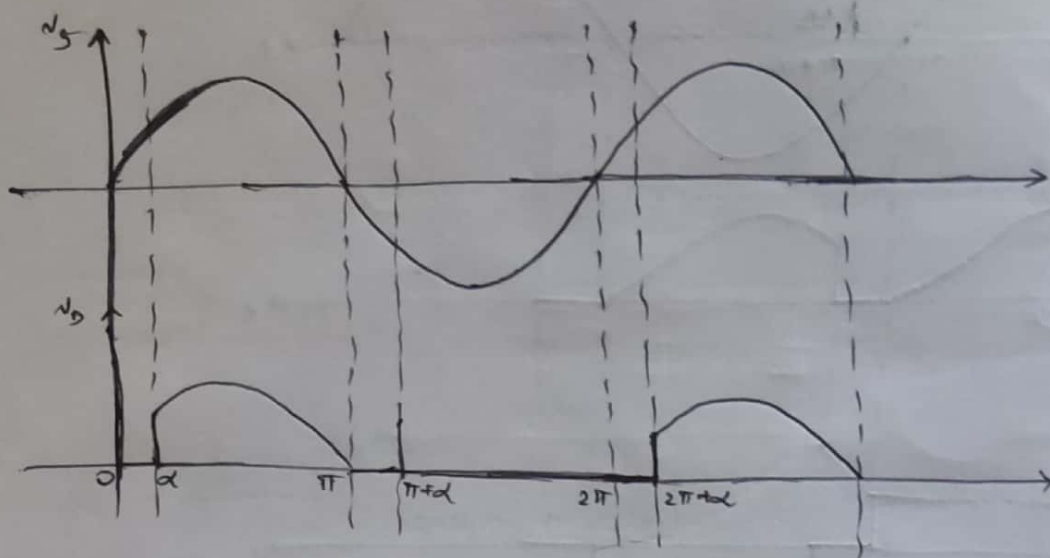

This phenomenon is called half waving effect, because it is same as half controlled (wave) rectifier

② Asymmetrical connection:

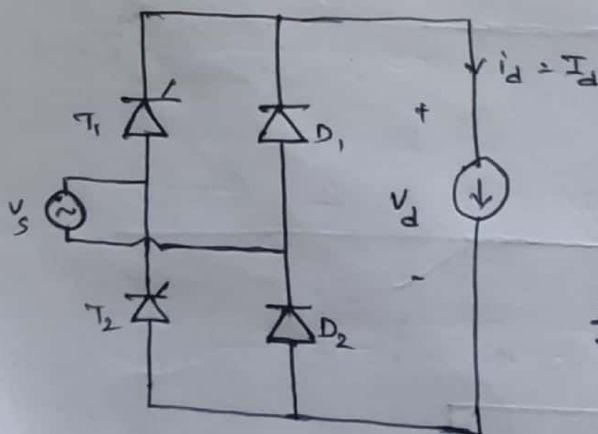

Two separate gating circuits are required to trigger the SCR's

$\alpha \rightarrow \pi$

T_1, D_2 conduct

$$v_d = v_s$$

$$i_s = i_d$$

$$i_{T_1} = i_d$$

$$i_{D_2} = i_d$$

$\pi \rightarrow \pi + \alpha$

D_1, D_2 conduct

$$v_d = 0$$

$$i_s = 0$$

$$i_{T_1} = 0$$

$\pi + \alpha \rightarrow 2\pi$

T_2, D_1 conduct

$$v_d = -v_s$$

$$i_s = -i_d$$

$$i_{T_2} = 0$$

$$i_{D_1} = 0$$


$2\pi \rightarrow 2\pi + \alpha$

D_1, D_2 conduct

$$v_d = 0$$

$$i_s = 0$$

$$i_{T_1} = 0$$

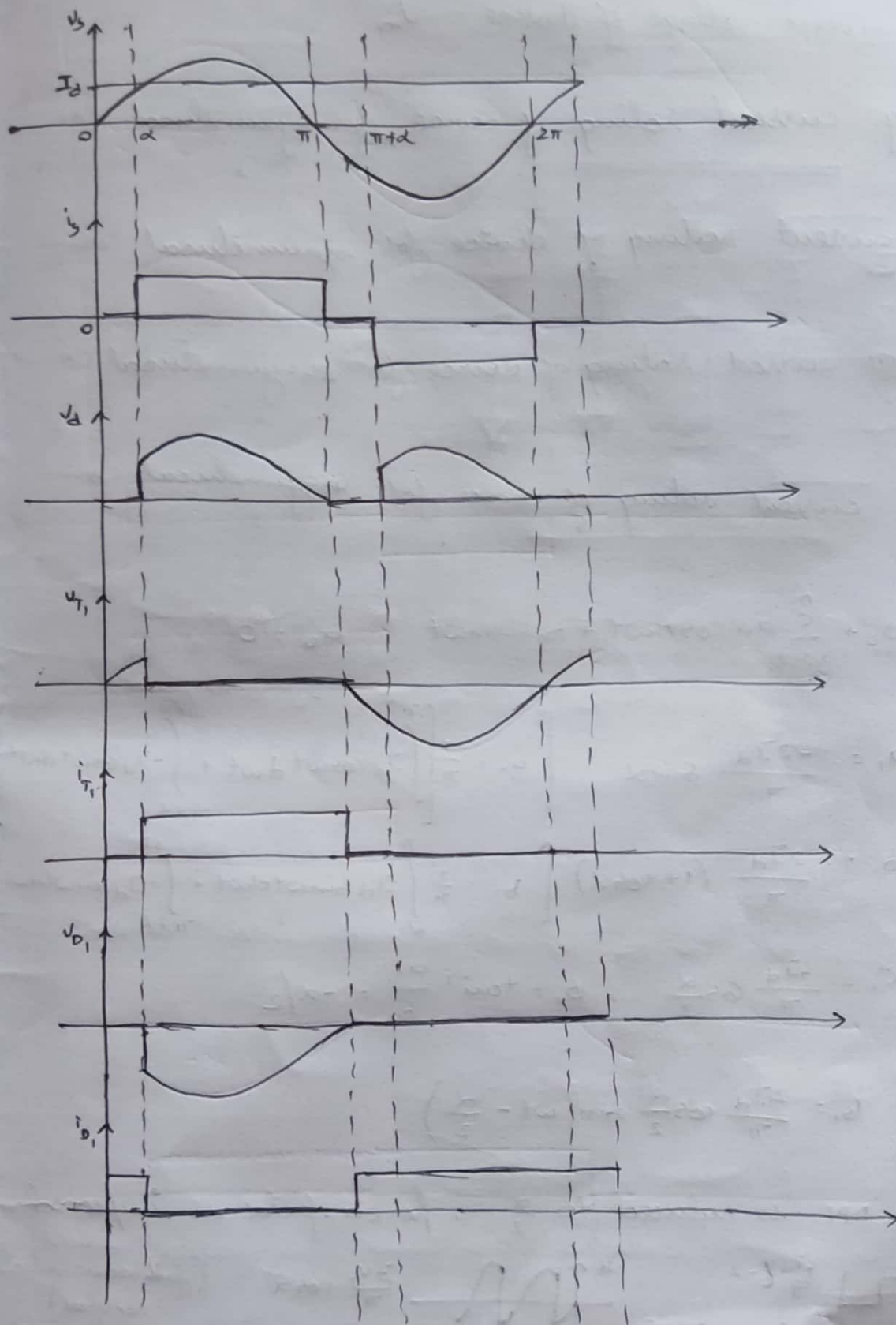

* DC side:

* Average load voltage, $V_{\text{avg}} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t$

$$= \frac{\sqrt{2} V_s}{\pi} [1 + \cos \alpha]$$

* Average power through the converter

$$P = V_{\text{avg}} I_d = \frac{\sqrt{2} V_s I_d}{\pi} [1 + \cos \alpha]$$

* peak inverse voltage of device = V_m

* Average current rating of device for symmetrical con.

* RMS current rating of device for symmetrical con

* Average current rating of device for asymmetrical con

* RMS current rating of device for asymmetrical con

$$* i_s(t) = a_0 + \sum_{n=1,2,3,\dots}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t, \quad a_0 = 0$$


$$a_1 = \frac{-2I_d}{\pi} \sin \alpha \quad \left[a_1 = \frac{1}{\pi} \left[\int_{\alpha}^{\pi} I_d \cos \omega t d\omega t + \int_{\pi+\alpha}^{2\pi} -I_d \cos \omega t d\omega t \right] \right]$$

$$b_1 = \frac{2I_d}{\pi} (1 + \cos \alpha) \quad \left[b_1 = \frac{1}{\pi} \left[\int_{\alpha}^{\pi} I_d \sin \omega t d\omega t + \int_{\pi+\alpha}^{2\pi} -I_d \sin \omega t d\omega t \right] \right]$$

$$C_1 = \frac{4I_d}{\pi} \cos \frac{\alpha}{2}, \quad \phi_1 = \tan^{-1} \frac{a_1}{b_1} = -\alpha/2$$

$$i_s = \frac{4I_d}{\pi} \cos \frac{\alpha}{2} \sin \left(\omega t - \frac{\alpha}{2} \right)$$

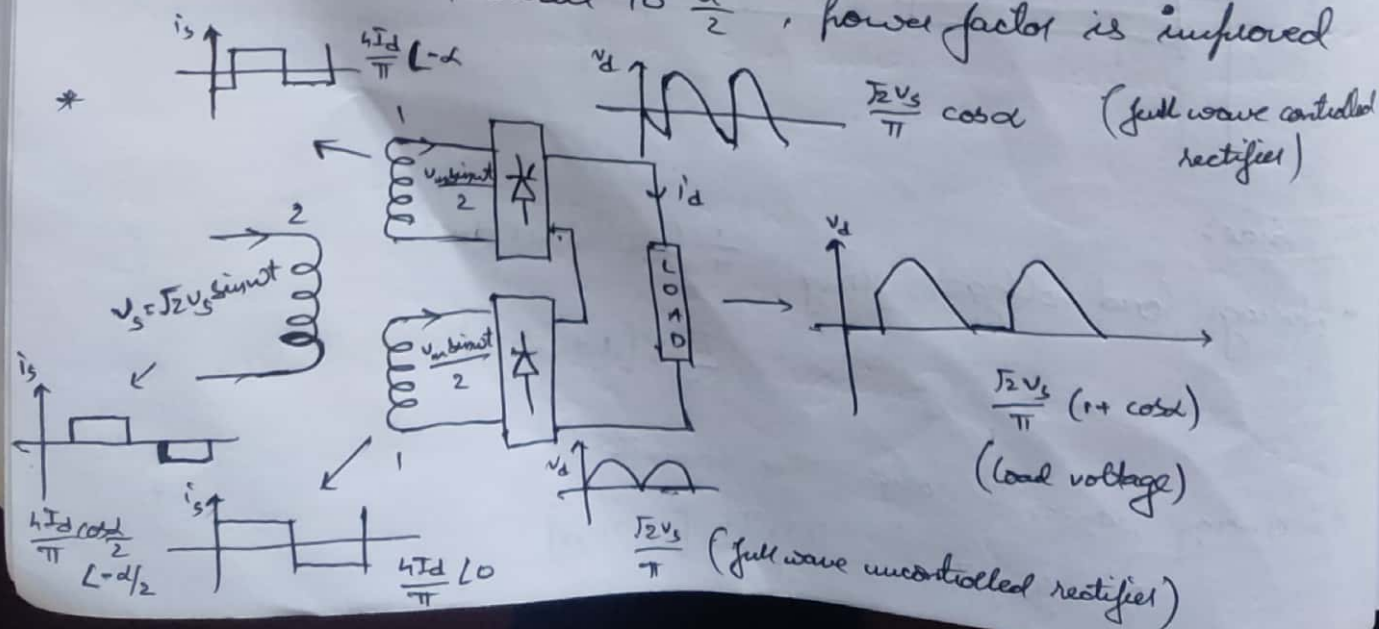As DPF is reduced to $\frac{\alpha}{2}$, power factor is improved



* If full wave controlled rectifier & full wave uncontrolled rectifier are connected in series so o/p voltage will be sum of both

$$* i_s = \frac{4I_d}{\pi} (\cos \alpha - j \sin \alpha) + \frac{4I_d}{\pi} \cos 0$$

$$i_s = \frac{4I_d}{\pi} (\cos \alpha + \cos 0) - j \frac{4I_d}{\pi} \sin \alpha$$

$$i_s = \frac{4I_d}{\pi} \left(2 \cos \frac{\alpha}{2} \cos \frac{\alpha}{2} \right) - j \frac{4I_d}{\pi} \sin \alpha$$

$$i_s = \frac{4I_d}{\pi} \cos \frac{\alpha}{2} \angle -\alpha/2$$


* Uncontrolled & Half controlled \rightarrow (1st quadrant)

* Controlled rectifiers (1st & 4th quadrant)


* Four Quadrant Converters:

Two converters are connected back - back (full controlled)

- Dual converters

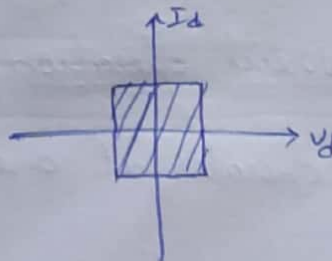

* Single phase Dual converters:

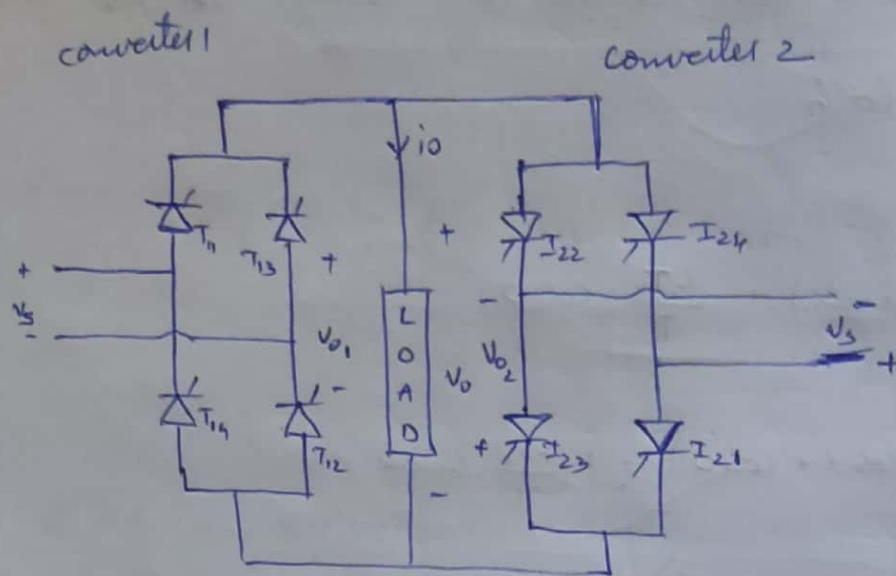

* when triggering angle, $\alpha_1 < 90^\circ$, V_{o1} is +ve, V_o is positive

$\alpha_1 > 90^\circ$, V_{o1} is -ve, V_o is negative

$\alpha_2 < 90^\circ$, V_{o2} is +ve, V_o is negative

$\alpha_2 > 90^\circ$, V_{o2} is -ve, V_o is positive

* Each converter has the ability to conduct current in one direction only

* so load current is bidirectional

① Non-circulating current operation:

* only one converter operates at one time and carries entire load current

* +ve current \rightarrow converter 1 is ON


* -ve current \rightarrow converter 2 is ON

* No current limiting reactor is required because only one converter is ON at a time

* slow & sluggish

② Circulating current operation:

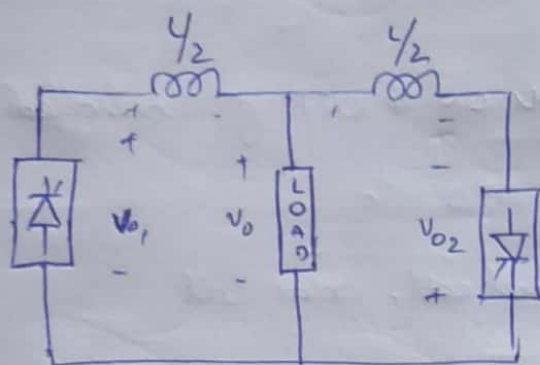- * Average voltages of both converters are equal.
- * All the devices are on (can give gate pulse to any device)



- * Instantaneous voltages are different
- * This leads to circulating current between the 2 converters
- * A reactor is inserted in between the converters to limit this current within limits.

→ Average o/p voltages:

$$V_{o1} = V_{om} \cos \alpha_1 = \frac{2\sqrt{2}V_s}{\pi} \cos \alpha_1$$

$$V_{o2} = V_{om} \cos \alpha_2 = \frac{2\sqrt{2}V_s}{\pi} \cos \alpha_2$$

$$V_{o1} = -V_{o2} = V_o$$

$$\cos \alpha_1 + \cos \alpha_2 = 0$$

$$\boxed{\alpha_1 + \alpha_2 = 180^\circ}$$

- * At any instant one converter operates as rectifier while the other one operates as inverter
- * To reverse the current, roles of converter are interchanged
- * Response is very fast

Drawbacks:

- * A reactor is needed
- * Losses are more, less efficiency, low power factor.
- * Devices are rated for high value to accommodate circulating currents